

(i) positive feedback :-

when i/p & sample^{o/p} are in same phase.
 ⇒ used in oscillator

(ii) negative feedback :- when i/p & sample o/p
 are in 180° out of phase.


⇒ used in Amplifiers.

	Gain
i) Voltage Amplifier	$A_v = \frac{V_o}{V_i}$
ii) Current Amplifier	$A_I = \frac{I_o}{I_i}$
iii) Transistance Amplifier	$R_m = \frac{V_o}{I_i}$ where R_m is gain
Transconductance Amplifier	$G_{m} = \frac{I_o}{V_i}$

Feedback Amplifiers :-

- (i) Voltage Series
- (ii) Voltage Shunt
- Current Series
- (iii) Current Series
- (iv) Current Shunt

Hybrid Model for Voltage Amplifier:

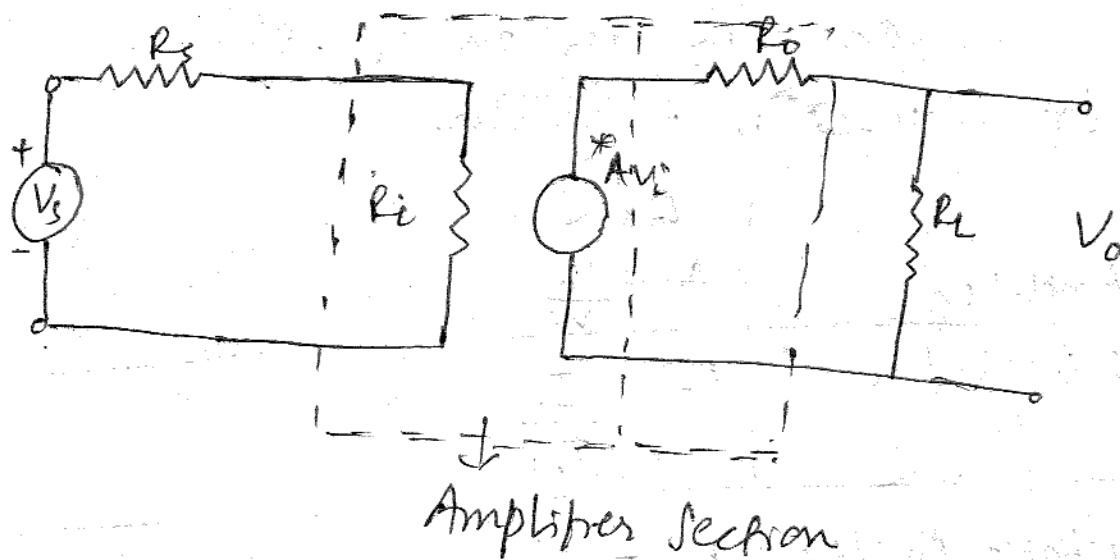


* $A \rightarrow$ Amplification factor

$$A_v = \frac{V_o}{V_i}$$

$$\Rightarrow V_o = A_v V_i$$

Current Amplifier Ckt:-

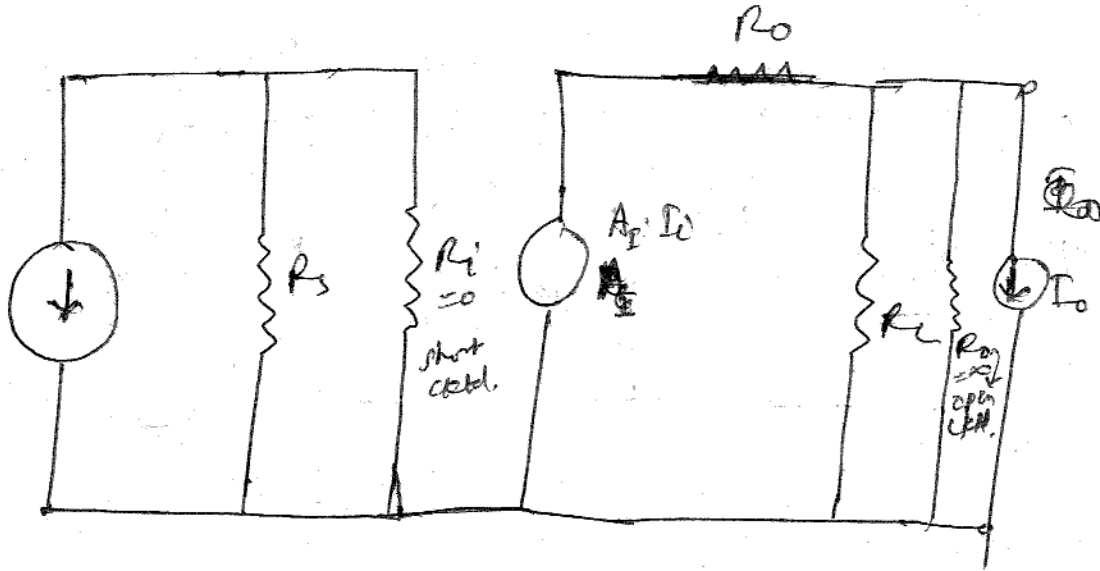


open ckt - High resistance
 short ckt - Low resistance.

$$I_o = A_i I_o$$

Transfer

20/6/11


Voltage Amplifier:-

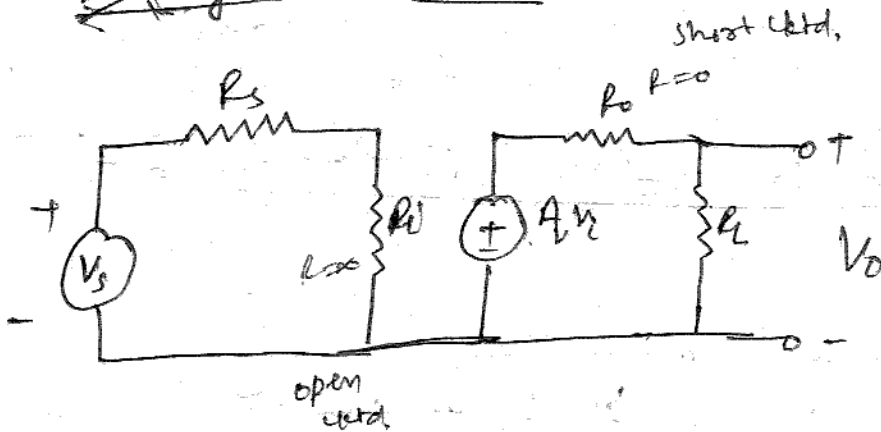


O.C
 $V_o \uparrow$
 $I = 0$
 $R = \infty$

S.C.
 $V_i = 0$
 $I = \text{max}$
 $R = 0$

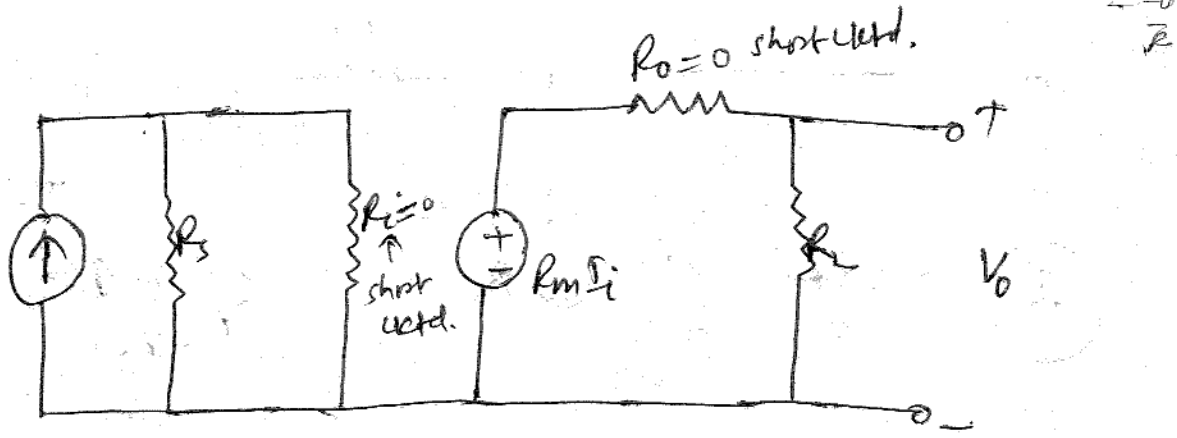
Transresistance Amplifier: - $\frac{V_o}{I_i}$



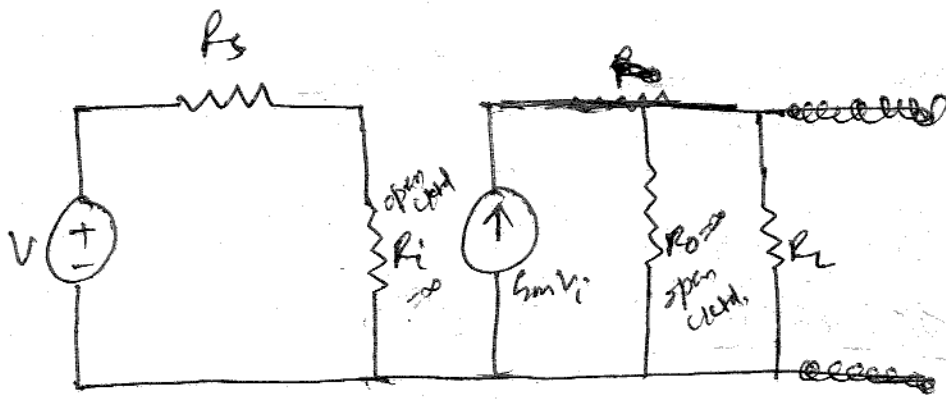Transconductance Amplifier: - $\frac{I_o}{V_i}$



23/6/14 Effect of Negative feedback: -

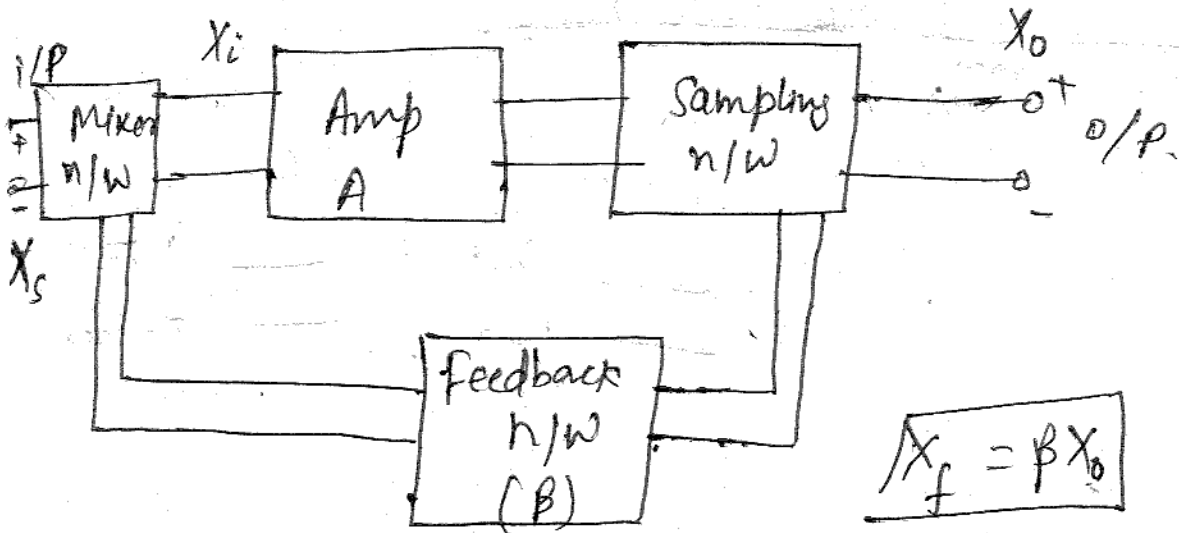

$$X_f = \beta X_o$$

X_f = feedback voltage or current

$$X_i = X_s + (-X_f) \quad \text{--- (1)}$$

where amplifier

$$A_f = \frac{X_o}{X_s} \quad , \quad A_f = \text{feedback gain}$$

--- (2)

$\alpha =$

$\beta =$ feedback gain
feedback factor.

$$A, \text{ Gain} = \frac{O/P}{I/P} = \frac{X_o}{X_i} \quad \text{gain without feedback or open loop ckt.}$$

From (1)

$$X_s = X_i + X_f.$$

Sub this in (2)

$$A_f = \frac{X_o}{X_s} = \frac{X_o}{X_i + X_f}$$

Dividing num^r & denom^r by X_i

$$A_f = \frac{X_o / X_i}{1 + \frac{X_f}{X_i}} \Rightarrow A_f = \frac{A}{1 + \frac{X_f}{X_i}}$$

$$\therefore X_f = \beta X_o$$

$$\Rightarrow A_f = \frac{A}{1 + \beta X_o} = \frac{A}{1 + \beta A}$$

$$A_f = \frac{A}{1+BA}$$

⇒ Without feedback A_f is more,
with feedback A_f is less.

Stability of gain

Step 1:- Write the gain of your feedback Amplifier.

$$A_f = \frac{A}{1+BA} \quad \text{--- (1)}$$

Step 2 Diff (1) w.r to A,

$$\frac{d(A_f)}{dA} = \frac{-1(1+BA) - A \frac{d}{dA}(1+BA)}{(1+BA)^2}$$

$$= \frac{(1+BA) - A(B)}{(1+BA)^2}$$

$$= \frac{1}{(1+BA)^2}$$

Step 3 :-

$$d(A_f) = \frac{1}{(1+BA)^2} dA$$

Step 4 . Dividing both sides by A_f .

$$\frac{dA_f}{A_f} = \frac{dA}{A_f (1+BA)^2}$$

$$\frac{dA_f}{A_f} = \frac{dA}{\frac{A}{(1+BA)} (1+BA)^2}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A(1+BA)}$$

$$\frac{dA_f}{(A_f) dA} = \frac{1}{A(1+BA)}$$

$$S = \frac{\frac{dA_f}{A_f}}{\frac{dA}{A}} = \frac{1}{1+BA}$$


$S = \text{sensitivity}$.

$$\text{Desensitivity, } D = \frac{1}{S} = 1+BA$$


Effect of -ve feedback in I/P & O/P

Resistance :-

(1) Voltage series feedback Amplifier :-

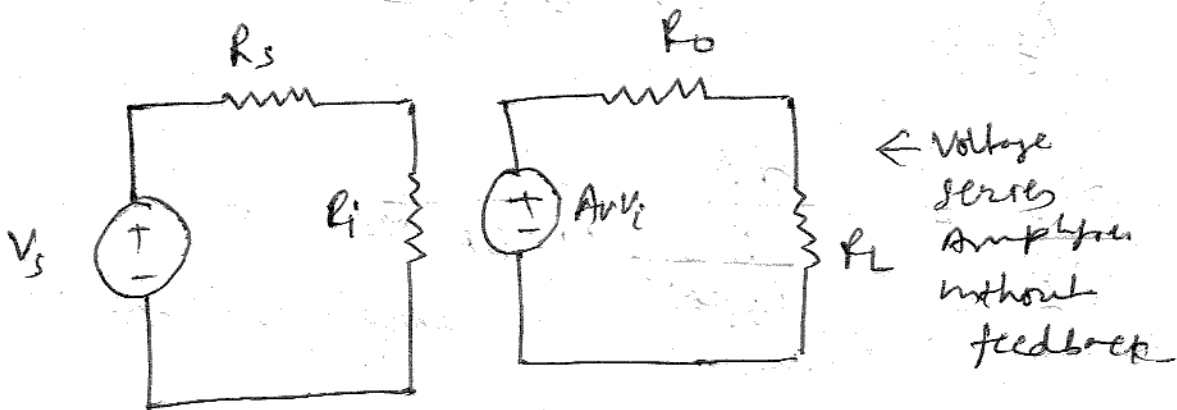

Calculation of I/P resistance :-

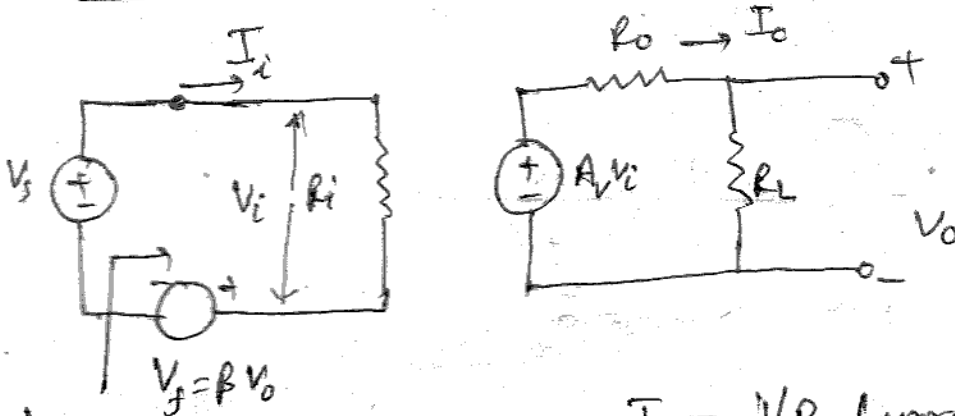

$$R_{if} = \frac{V_s}{I_i}$$

$I_i =$ I/P Current

$I_o =$ O/P Current

$R_{if} =$ I/P resistance with feedback

Applying KVL to I/P loop.

Sum of all voltage sources

= Sum of voltage drops.


$$V_s - R_i I_i - V_f = 0$$

$$\Rightarrow V_s = R_i I_i + V_f$$

$$\Rightarrow V_s = R_o I_i + \beta V_o \quad \text{--- (1)}$$

Applying KVL to O/P

voltage Divider rule

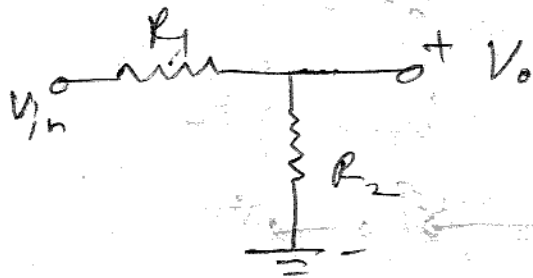

$$V_o = \frac{V_{in} R_2}{R_1 + R_2}$$

$$V_o = A_v v_i \frac{R_o}{R_o + R_L}$$

where, $A_v = A_v \frac{R_L}{R_o + R_L}$

$$= \left(\frac{A_v R_L}{R_o + R_L} \right) v_i = A_v \cdot v_i \quad \text{--- (2)}$$

$$= A_v \cdot (I_i R_i)$$

Put (2) in (1)


$$V_s = R_i I_i + \beta \cdot A_v \cdot I_i R_i$$

$$= R_i I_i (1 + \beta A_v)$$

$$\therefore R_{if} = \frac{V_s}{I_i} = \frac{R_i I_i (1 + \beta A_v)}{I_i}$$

$$R_{if} = R_i (1 + \beta A_v)$$

Calculation of o/p resistance :-

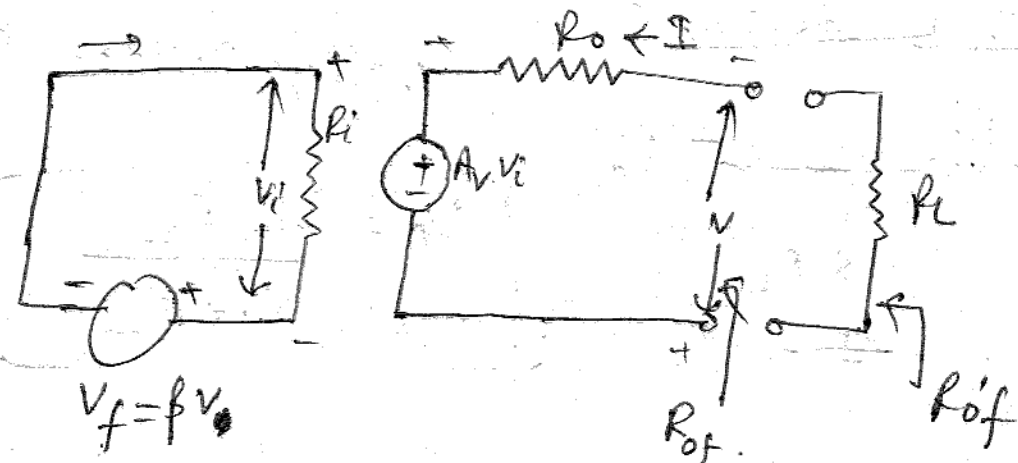

Make source = 0

and disconnect load resistance

Applying KVL to o/p loop

$$A_v V_i + I R_o - V = 0$$

$$\Rightarrow A_v V_i - V = -I R_o$$

$$\Rightarrow \underline{I =}$$

$$I R_o = V - A_v V_i$$

$$I = \frac{V - A_v V_i}{R_o}$$

applying

1/p KVL

$$-V_i - V_f = 0$$

$$\Rightarrow V_i = -V_f = -\beta V_o$$

$$\Rightarrow V_i = -\beta V_o$$

$$I = \frac{V - A_i(-\beta V_o)}{R_o}$$

$$= \frac{V + \beta A_i V_o}{R_o}$$

$$= \frac{V(1 + \beta A_i)}{R_o}$$

$$\Rightarrow R_o = \frac{V(1 + \beta A_i)}{I}$$

$$\Rightarrow \frac{V}{I} = \frac{R_o}{1 + \beta A_i}$$

$$\Rightarrow R_{of} = \frac{R_o}{1 + \beta A_i}$$

$$R_o'f = R_{of} \parallel R_L$$

$$= \frac{R_{of} R_L}{R_{of} + R_L}$$

$$= \frac{R_o R_L}{1 + \beta A_i} = \frac{R_o R_L}{1 + \beta A_i} \cdot \frac{R_o + R_L}{R_o + R_L} = \frac{R_o R_L (R_o + R_L)}{(1 + \beta A_i)(R_o + R_L)}$$

$$= \frac{R_o R_L}{1 + \beta A_v} \times \frac{1 + \beta A_v}{R_o + R_L (1 + \beta A_v)}$$

$$R_{o_f} = \frac{R_o R_L}{R_o + R_L (1 + \beta A_v)}$$

$$\Rightarrow R_{o_f} = \frac{R_o R_L}{R_o + R_L + \beta A_v \cdot R_L}$$

Dividing Nr & denom^r by $(R_o + R_L)$

$$R_{o_f} = \frac{\frac{R_o R_L}{R_o + R_L}}{\frac{R_o + R_L}{R_o + R_L} + \frac{\beta A_v \cdot R_L}{R_o + R_L}}$$



$$R_{o_f} = \frac{R_o'}{1 + \beta A_v}$$

where,

$$R_o' = \frac{R_o R_L}{R_o + R_L}$$

$$\& A_v = \frac{A_v \cdot R_L}{R_o + R_L}$$

Current Shunt feedback Amplifier

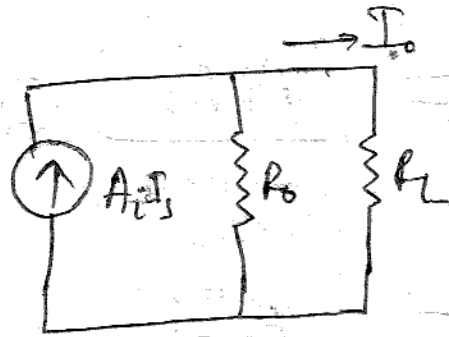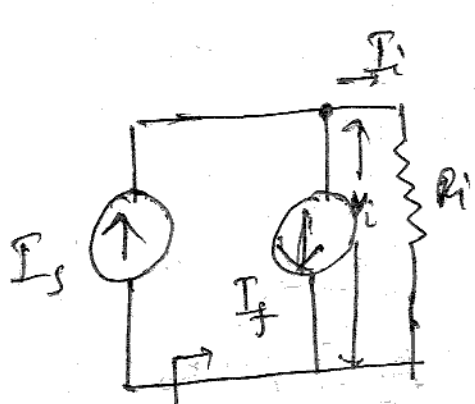



$$R_{if} = \frac{V_i}{I_s}$$

~~$$I_f = \beta I_o$$~~

$$I_f = \beta I_o$$

Applying KCL,

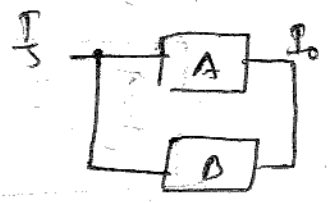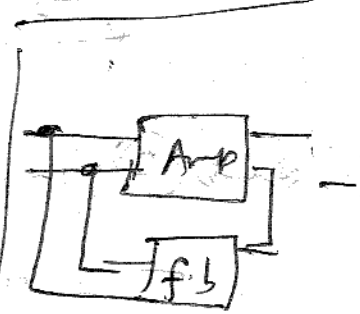Sum of incoming current = sum of outgoing current



$$I_f = \beta I_o$$


$$I_s = I_f + I_i = \beta I_o + I_i \quad \text{--- (1)}$$

Current divider rule in o/p loop.

Current flowing through R_1 across R_2

$$I_1 = \frac{I R_2}{R_1 + R_2}$$

$$I_2 = \frac{I R_1}{R_1 + R_2}$$

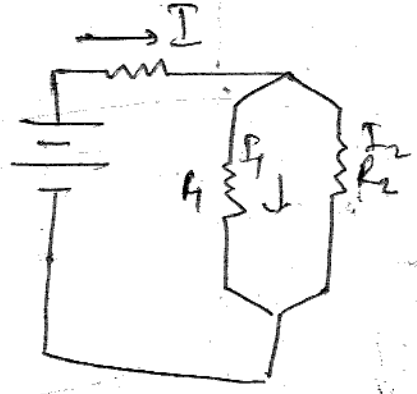

$$\therefore I_o = \frac{A_i I_i R_o}{R_o + R_L}$$

$$= \left(\frac{A_i R_o}{R_o + R_L} \right) I_i$$

$$= A_I I_i$$

where,

$$A_I = \frac{A_i R_o}{R_o + R_L}$$

$$\Rightarrow \boxed{I_o = A_I I_i} \quad \text{--- (2)}$$

Sub (2) in (1)

$$I_s = I_i + \beta (A_i I_i)$$

$$\boxed{I_s = I_i (1 + \beta A_i)}$$


$$R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i (1 + \beta A_i)}$$

$$\boxed{R_{if} = \frac{R_i}{1 + \beta A_i}}$$

where $R_i = \frac{V_i}{I_i}$

o/p resistance! -

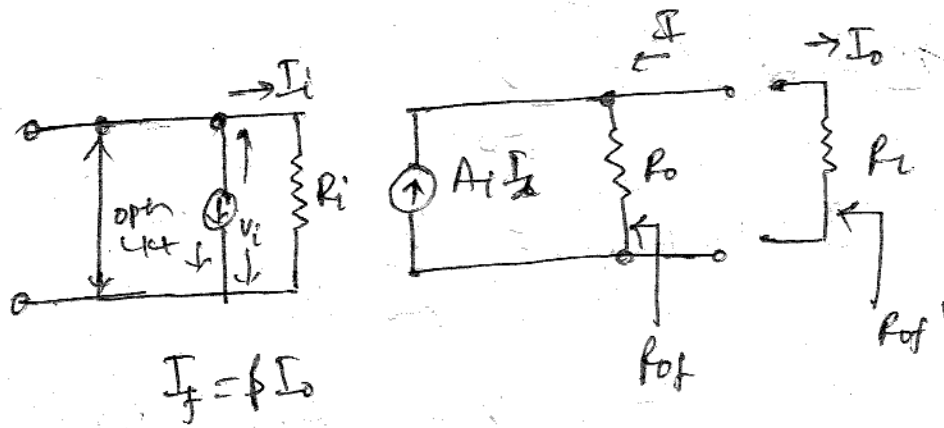Make source = 0
and disconnect the load resistance



$$I_f = \beta I_o$$

Applying KCL to o/p loop.

$$A_i I_i + I = \frac{V}{R_o}$$

$$\Rightarrow I = \frac{V}{R_o} - A_i I_i \quad \text{--- (1)}$$

Applying KVL to i/p part,

$$I_f + I_i = 0$$

$$I_f = -I_i$$

$$\Rightarrow \beta I_o = -I_i$$

$$\Rightarrow I_i = -\beta I_o$$

$$= -\beta(-I)$$

$$I_i = \beta I \quad \text{--- (2)}$$

Sub ② in ①

$$I = \frac{V}{R_0} - A_i \beta I$$

$$\Rightarrow I + A_i \beta I = \frac{V}{R_0}$$

$$\Rightarrow I(1 + A_i \beta) = \frac{V}{R_0}$$

$$\Rightarrow \frac{V}{I} = R_0(1 + \beta A_i)$$

~~$R_{of} = \frac{V}{I}$~~

$$\Rightarrow \boxed{R_{of} = R_0(1 + \beta A_i)}$$

$$R_{of}' = R_{of} \parallel R_L$$

$$= \frac{R_{of} R_L}{R_{of} + R_L}$$

$$= \frac{R_0(1 + \beta A_i) R_L}{R_0(1 + \beta A_i) + R_L}$$

$$= \frac{R_0 R_L (1 + \beta A_i)}{R_0 + R_L + \beta A_i R_0}$$

$$= \frac{R_0 R_L (1 + \beta A_i)}{R_0 + R_L}$$

$$\frac{R_0 R_L}{R_0 + R_L} + \frac{\beta A_i R_0 R_L}{R_0 + R_L}$$

$$= \frac{R_0' (1 + \beta A_i')}{1 + \beta A_i' \beta I}$$