


★ FEEDBACK AMPLIFIER

- In a feedback amplifier we sample the output voltage or current by means of a sampling network and apply these sampled signal to the i/p through a two port n/w referred to as the feedback n/w. \downarrow
- The sample is taken from o/p which is in phase with i/p signal is called +ve feedback.
- The sample is out of phase from the i/p signal is known as -ve feedback.

→ Classification on the basis of +ve and -ve feedback

- I) Voltage amplifier
- II) Current amplifier
- III) Transconductance amplifier
- IV) Transresistance amplifier

Voltage Amplifier

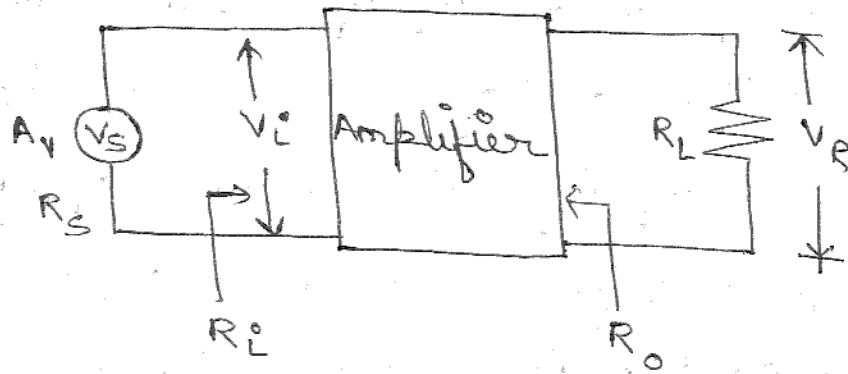

$$R_i \gg R_S$$

$$R_L \gg R_O$$

$$V_L \approx V_S$$

$$V_O \approx A_V \cdot V_L \approx A_V \cdot V_S$$

The voltage o/p is proportional to voltage i/p. The proportionality factor do not depends on the mag. of source and load resistance. Hence, the ampli is called voltage amplifier.

For ideal amplifier R_i should be infinite and R_L should be zero.


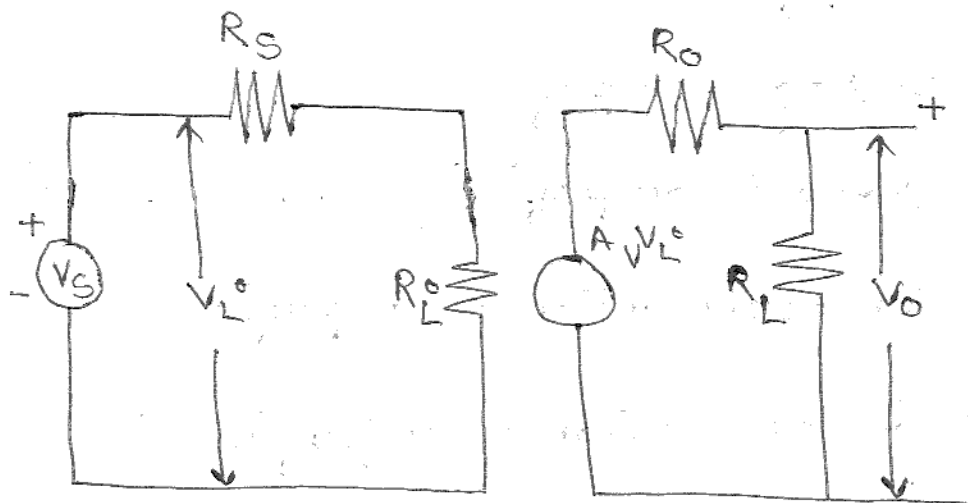


Fig : Thevenin's eq. ckt

Current Amplifier

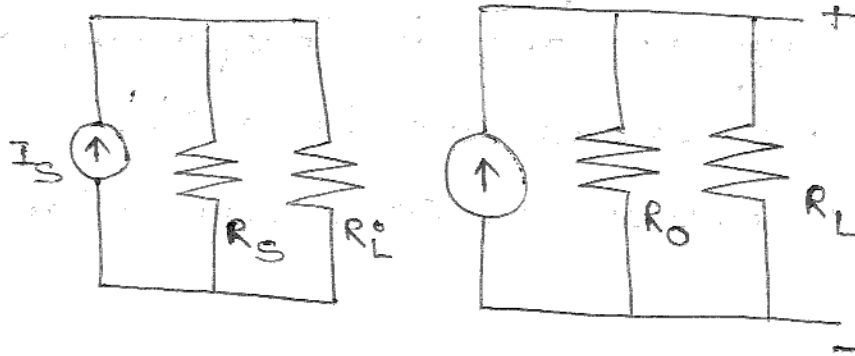


If $R_L \rightarrow 0$ then $I_L \approx I_o$

If $R_o \rightarrow \infty$ then $I_L \approx I_o$

The current of i_p is proportional to the signal current. The proportionality factor is independent of source and load resistance with which is called as current amplifier.

Transconductance Amplifier

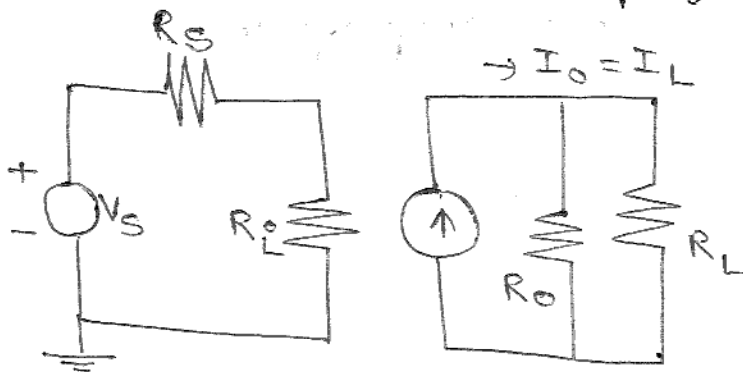


$$R_L \gg R_s$$

$$R_o \gg R_L$$


output ~~the~~ current is proportional to the i/p signal voltage. The proportionality constant is independent of magnitude and source and load resistance. This is known as transconductance ampli.

Transresistance Amplifier

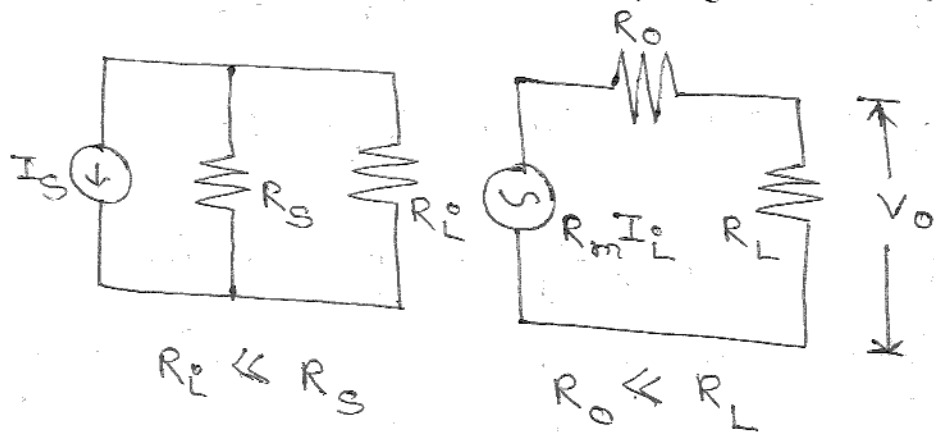


output voltage is proportional to the i/p signal current. The proportionality constant is independent of source and load resistance. This is known as transresistance amplifier.


★ Sampling Network

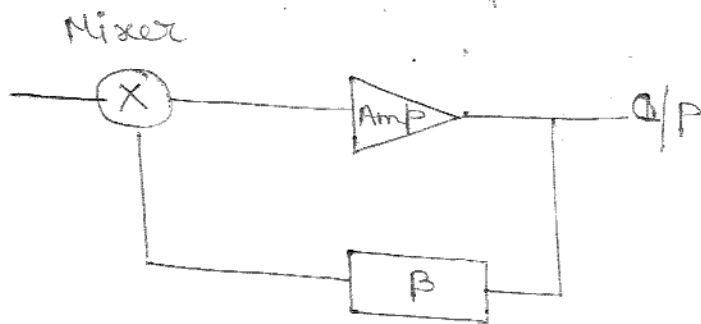

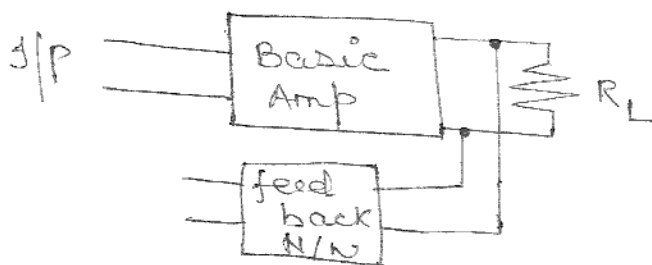- Two types of sample output can be taken out from any circuit for the feedback n/w to get the desired output. The sampling parameters either may be voltage or current. For current sampling the output current is sampled by connecting the feedback n/w in series with the output.
- For voltage sample output voltage is sampled by connecting the feedback n/w in parallel with the output.



voltage (or) Node sampling

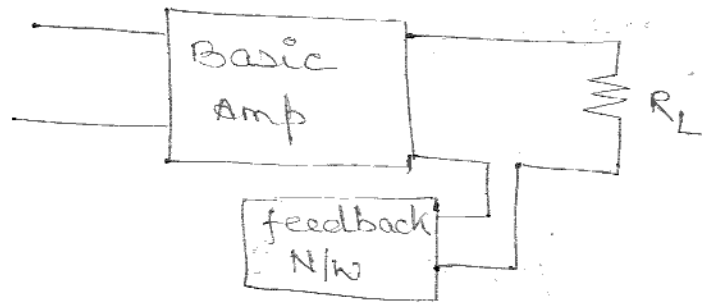

★ Feedback Network

It consists of resistors, capacitors and inductors.

$$V_f = \beta \cdot V_o$$

where,

β = feedback factor or feedback ratio

Its value lies b/w 0 and 1.


- For CE amplifier $\beta > 1$.

★ Mixer Network


→ Two types

- Series
- Shunt

- Series

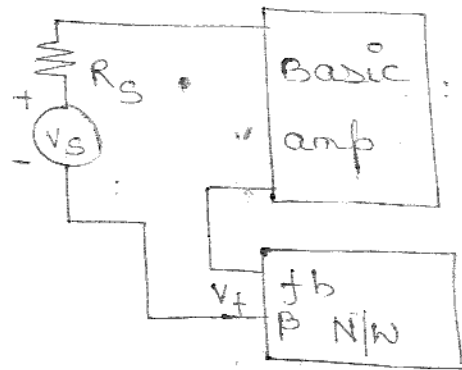

- Shunt

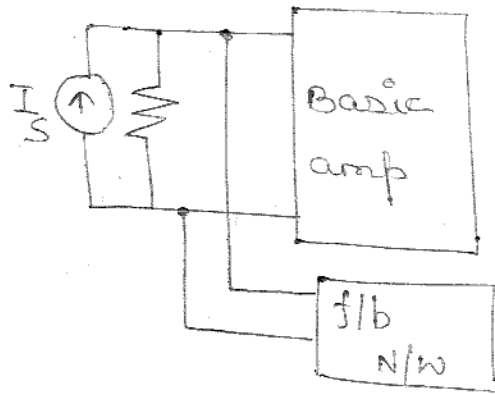


By connecting the sampled output may be the voltage of the current and f/b op to the i/p in series or shunt will provide the high i/p impedance to the circuit.

★ Types Of Feedback Amplifier

- Voltage series f/b amp
- Current series " "
- Voltage shunt " "
- Current shunt " "

O/P I/P
 • Voltage Series

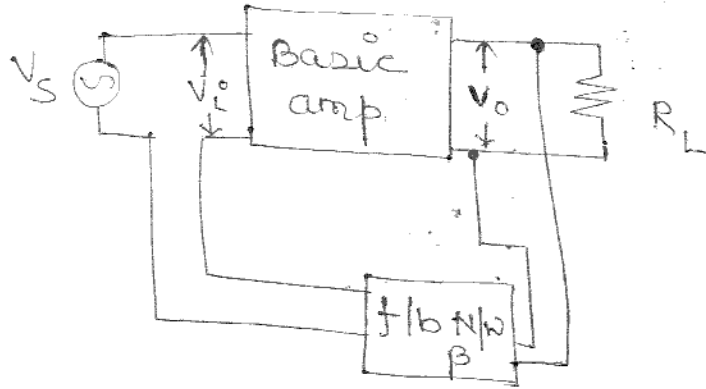


$$V_f = \beta V_o$$

$$A = \frac{V_o}{V_i^o} = \text{Gain}$$

Voltage series $A_f = \frac{V_o}{V_S}$


• Current Series

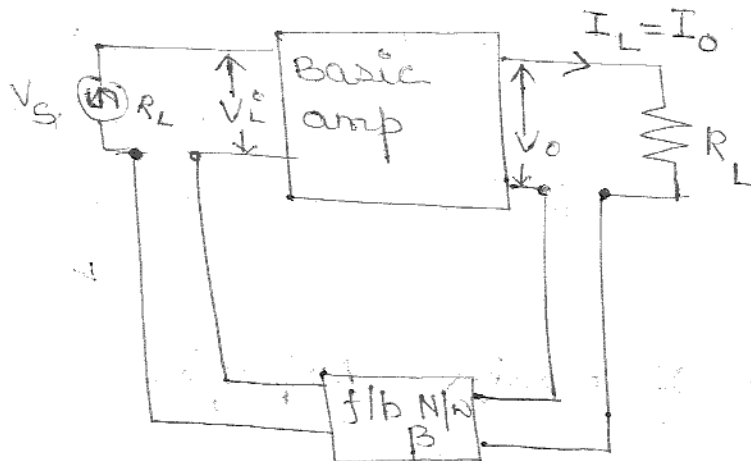


$$V_f = \beta I_o$$

$$A = \frac{I_o}{V_i^o}$$

★ Voltage Shunt

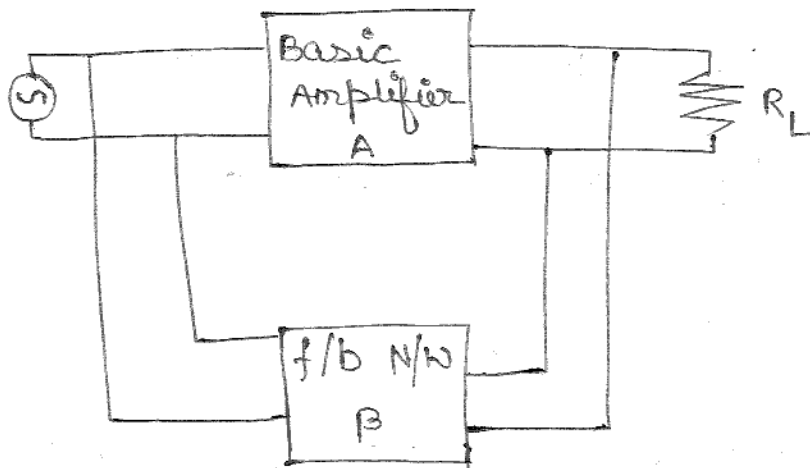

★ Current Shunt

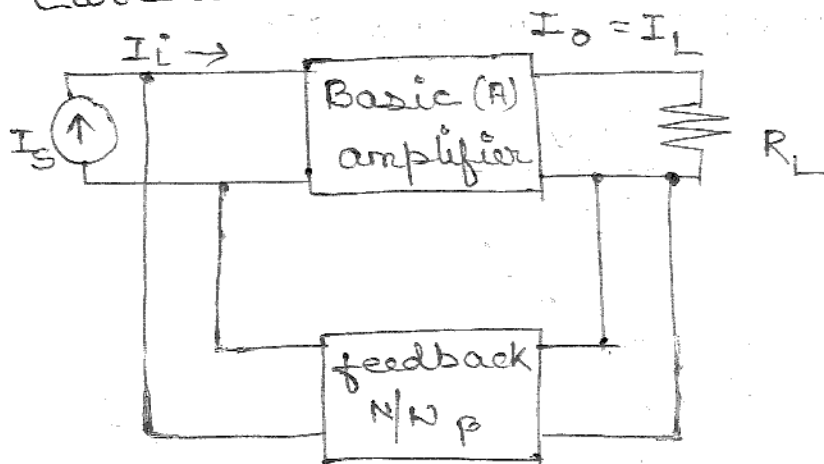

★ Gain with feedback

The symbol A is used to represent transfer gain of basic amplifier without feedback and symbol A_f is used to represent with feedback.

$$A = \frac{x_o}{x_i} \quad , \quad A_f = \frac{x_o}{x_s}$$

where

x_o = o/p voltage or current

x_i = i/p voltage or current

x_s = source voltage or current

$$x_i = x_s + (-x_f)$$

$\Rightarrow x_f$ = feedback voltage or f/b current

$$\therefore A_f = \frac{x_o}{x_s} = \frac{x_o}{x_i + x_f}$$

\div by x_i to num and deno

$$A_f = \frac{x_o/x_i}{1 + x_f/x_i}$$

$$A_f = \frac{A}{1 + \left(\frac{x_f}{x_i}\right)}$$

where

$$A = \frac{x_o}{x_i}$$

$$A_f = \frac{A}{1 + \beta A} \quad ; \quad \left(\beta = \frac{x_f}{x_i} \right)$$

ly.

$$A_{vf} = \frac{A_v}{1 + A_v \beta}$$

$A_v \rightarrow$ open loop gain

$\beta \rightarrow$ feedback factor

* Loop Gain \approx

The difference $s/l \times c$ is multiplied by the gain A is passing through the amplifier is multiplied by β in transmission through the feedback n/w and is multiplied by -1 in the mixing. The gain of the loop place is the product of $-A\beta$ this is known as loop gain of return ratio.

* Transfer Ratio or Gain

The ratio of o/p signal to the i/p signal of the basic amplifier is represented by A.

$$\frac{V}{V_i} = A_v \Rightarrow \text{Voltage gain} \quad \text{--- (1)}$$

$$\frac{I}{I_i} = A_i \Rightarrow \text{Current gain} \quad \text{--- (2)}$$

$$\frac{I}{V_i} = G_m \Rightarrow \text{Transconductance} \quad \text{--- (3)}$$

$$\frac{V}{I_i} = R_m \Rightarrow \text{Trans resistance} \quad \text{--- (4)}$$

* Cutoff frequency with feedback

W.K.T.

$$A_f = \frac{A}{1 + \beta A} \quad \text{using this eq, we can}$$

write

$$A_{f \text{ mid}} = \frac{A_{\text{mid}}}{1 + \beta A_{\text{mid}}} \quad \text{--- (1)}$$

$$A_{f \text{ low}} = \frac{A_{\text{low}}}{1 + \beta A_{\text{low}}} \quad \text{--- (2)}$$

$$A_{f \text{ high}} = \frac{A_{\text{high}}}{1 + \beta A_{\text{high}}} \quad (3)$$

* Advantages of -ve feedback

- High i_p resistance of the voltage end can be made high.
- Low o_p resistance of a voltage amplifier can be lowered.
- which improves the freq. response of amplifier.
- Significant improvement in the linearity of operation of feedback amplifier.

* Distortion in feedback



• Frequency distortion

The feedback o_p doesn't contain reactive element. The overall gain is not a function of frequency.

* Noise And Non-linear distortion

The signal feedback reduces the amount of noise signal and non-linear distortion for considerable improvements.

- Input and output resistance

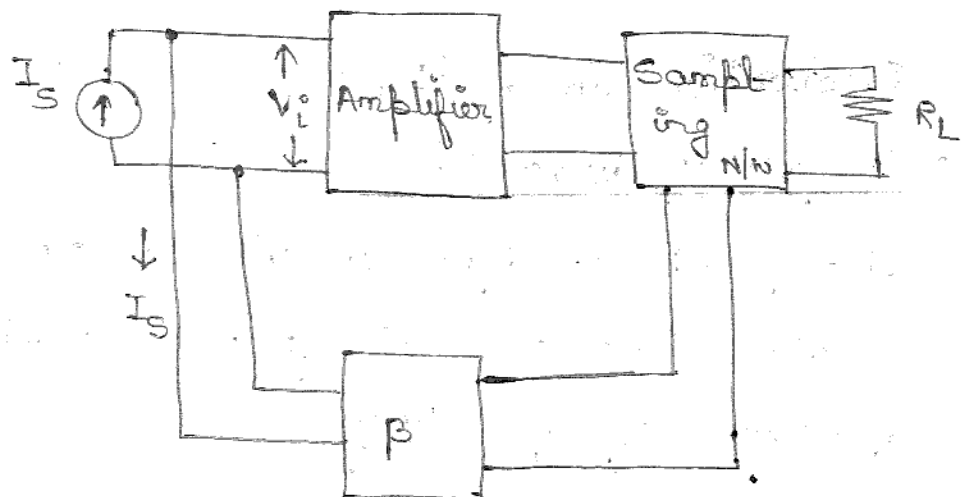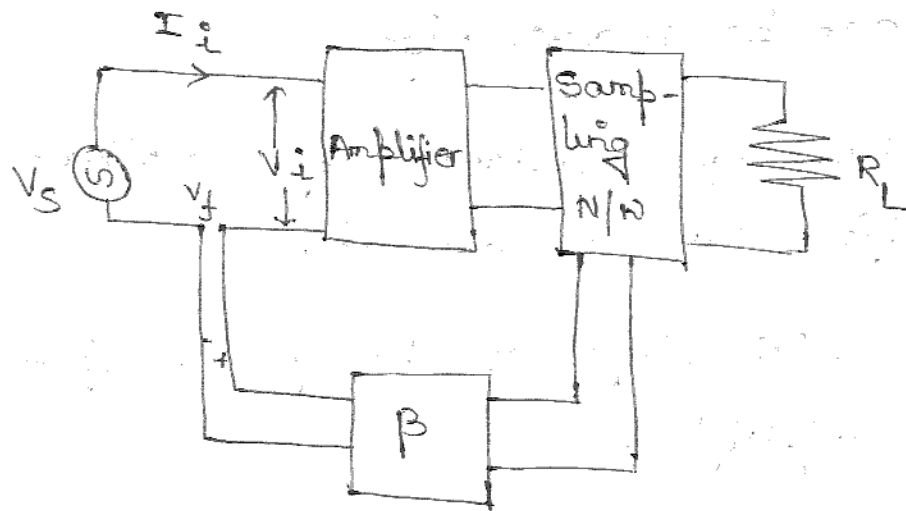


i The feedback signal is added to the ip in series with the applied voltage. It increases the input resistance. Since V_f opposes V_s

ii If f/b signal is added to the ip at shunt to the applied voltage it decreases the ip resistance. Since $I_s = I_i + I_f$

iii The current I_s drawn from the signal source is increased over.

• Voltage series feedback

Input Resistance

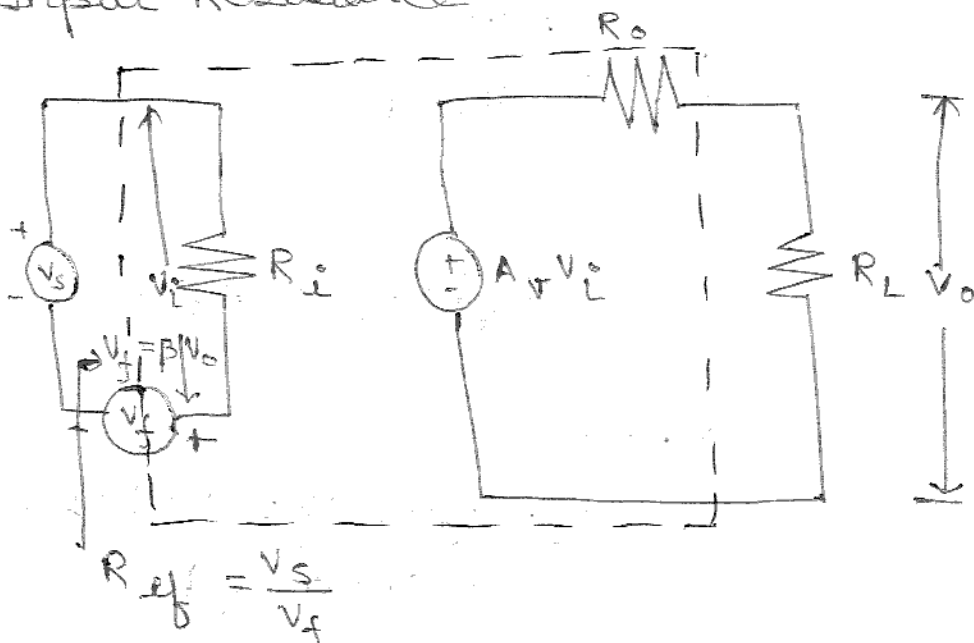

The voltage series feedback topology with amplifier is replaced by thevenin's model and A_v represents the open ckt voltage gain taking R_s into account ($R_s =$ part of amplifier).

i/p resistance with ffb

$$R_{if} = \frac{V_s}{I_i} \quad \text{--- (1)}$$

Applying KVL to the i/p side

$$V_s = I_i R_i + V_f$$

$$= I_i R_i + \beta V_o \quad \text{--- (2)}$$

o/p voltage V_o is given as

$$V_o = \frac{A_v V_i R_L}{R_o + R_L}$$

$$= A_v \frac{I_i R_i}{\beta} = A_v V_L \quad \text{--- (3)}$$

where

$A_v =$ open ckt voltage gain without ffb

A_v = Voltage gain with f/b with R_L
into account

Sub V_o from eq (3) in eq (2)

$$V_s = I_i R_i + \beta V_o$$

$$V_s = I_i R_i + \beta A_v V_i$$

$$V_s = V_i (1 + \beta A_v)$$

$$V_s = V_i (1 + \beta A_v)$$

$$V_s = I_i R_i (1 + \beta A_v)$$

$$\div I_i$$

$$\frac{V_s}{I_i} = R_i (1 + \beta A_v)$$


$$\Rightarrow \boxed{R_{if} = R_i [1 + \beta A_v]}$$

Here,

$$R_{if} = \frac{V_s}{I_i}$$

Output resistance

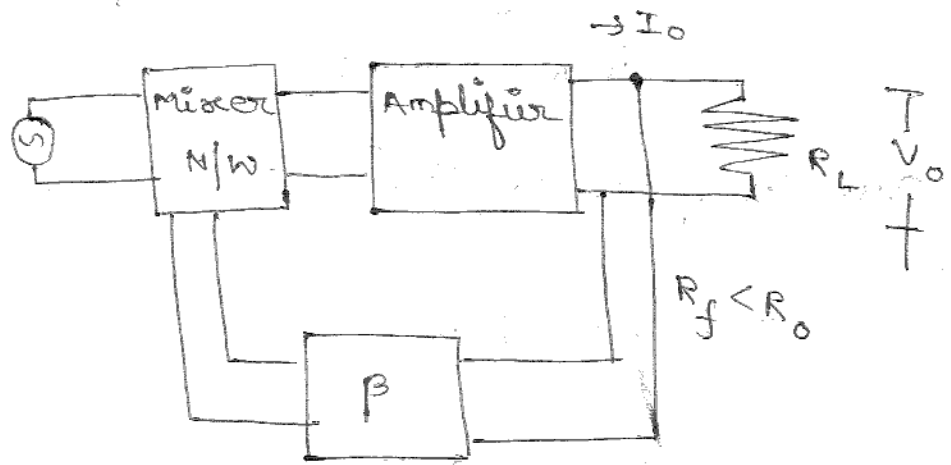
The -ve f/b which samples the op voltage regardless of how this op signal is returned to the i/p.



In -ve f/b which is used in the f/b amplifier tends to increase the o/p resistance.

- Voltage series feedback

Output Resistance

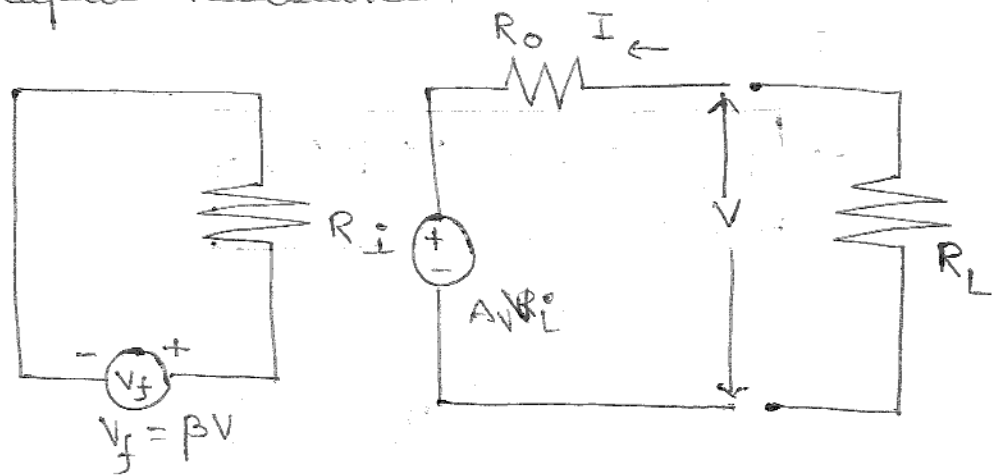

In this topology o/p resistance can be measured by shorting the i/p source $V_s = 0$. The o/p terminal with R_L is connected.

Applying KVL to op side

$$A_v V_i + I R_o - V = 0$$

$$I R_o = V - A_v V_i$$

$$I = \frac{V - A_v V_i}{R_o} \quad \text{--- (1)}$$

if voltage

$$V_i = -V_f = -\beta V \quad \text{--- (2)}$$

Subst V_i from eq (2) to eq (1)

$$I = \frac{V + A_v \beta V}{R_o}$$

$$I = \frac{V [1 + A_v \beta]}{R_o}$$

$$R_{of} = \frac{V}{I} = \frac{R_o}{[1 + A_v \beta]}$$

where,

A_v = open loop gain without taking R_L into account.

$$R_{of}' = R_{of} \parallel R_L$$

$$R_{of}' = \frac{R_{of} R_L}{R_{of} + R_L}$$

Sub R_{of} in above eq

$$R_{of}' = \frac{R_o R_L}{1 + A_v \beta} \frac{R_o}{\frac{R_o}{1 + A_v \beta} + R_L}$$

$$R_{of}' = \frac{R_o R_L}{R_o + R_L (1 + A_v \beta)}$$

$$= \frac{R_o R_L}{R_o + R_L + R_L \beta A_v}$$

Divide num and deno. by $(R_o + R_L)$

$$R_{of}' = \frac{\frac{R_o R_L}{R_o + R_L}}{\frac{R_o + R_L + R_L \beta A_v}{R_o + R_L}}$$

$$\text{Put } \frac{R_o R_L}{R_o + R_L} = R_L'$$

$$\frac{A_v R_L}{R_o + R_L} = A_v$$

$$R_{of}' = \frac{R_L'}{1 + \beta A_V}$$

Here, A_V = open loop voltage gain taking R_L into account.

* Method Of Identifying Feedback Topology And Analysis Of A Feedback Amplifier

To analyse the feedback amplifier i.e. necessary to go through four types of f/b. type of sampling n/w.

1) By shorting o/p $V=0$, if feedback signal becomes zero then it is said as voltage shunt sampling.

2) By opening the o/p loop $I=0$ with f/b signal = 0 then it is represented as current shunt.

• To find out the type of mixing signal

↳ The f/b signal is subtracted from externally applied voltage i.e. series mixing.

ii) The f/b is subtracted from externally applied current i.e. shunt mixing.

- Find the i/p circuit

1) Voltage shunt sampling makes $V=0$ by shorting the o/p.

ii) For current sampling by making the opening o/p.

- Find the o/p ckt

1) For series mixing $I=0$ by opening the i/p loop.

ii) For shunt mixing $V=0$ by shorting the i/p.

- Optional

1) Replace each active device by its h-parameter model at low frequency.


- Find the open loop gain A of the amplifier!

- Indicate X_f and X_o on the ckt and evaluate $\beta = X_f \cdot X_o$

- From A and β find A_f or A_{m_f} , R_{o_f} , R_{i_f} and R_{o_f}' .

* Analysis of feedback amplifier

- Transistor Emitter follower

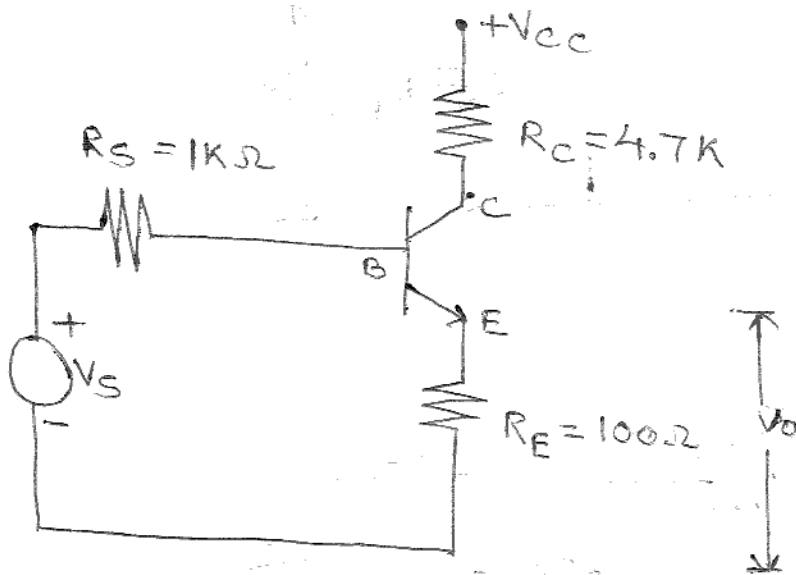


- 1) If $V_o = 0$ the feedback signal becomes zero. Hence, it is voltage shunt.


$\Rightarrow V_f$ is subtracted from the externally applied signal source V_s . Hence, it is series mixing.

Step 2 \rightarrow To find i/p ckt set $V_o = 0$. Hence V_s is in series with R_s and R_E . R_s appears b/w base and emitter.

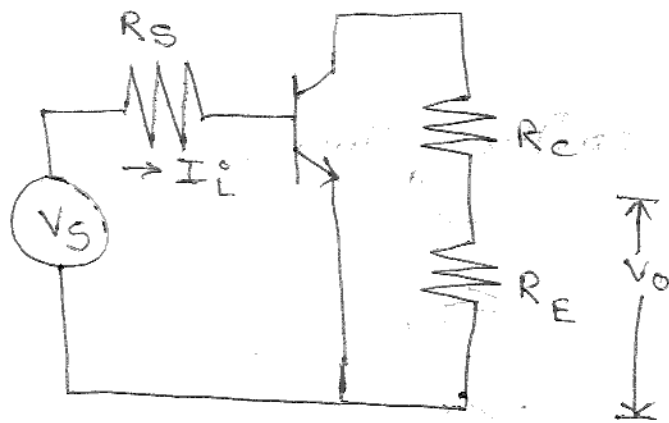\Rightarrow For o/p ckt set the value of $I_i = I_b = 0$



Step 4

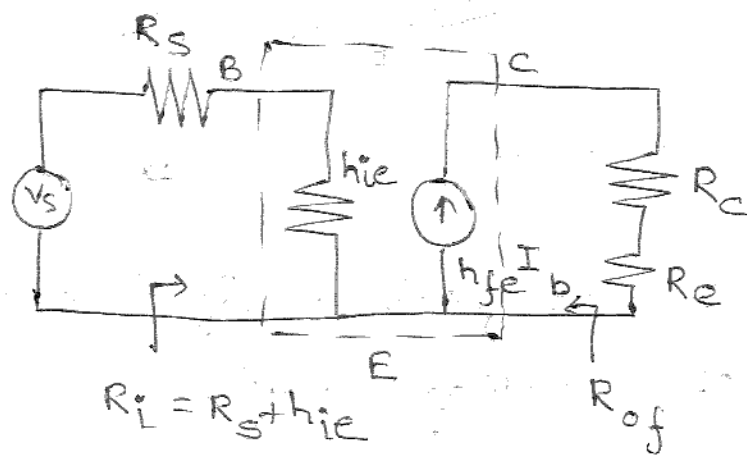

Step 5. Find open loop gain

$$A_V = \frac{V_o}{V_s} = \frac{h_{fe} I_b R_e}{V_s} \quad \text{--- (1)}$$

Applying KVL to i/p loop

$$V_s = I_b (R_s + h_{ie}) \quad \text{--- (2)}$$

Sub (2) in (1)

$$A_V = \frac{h_{fe} \cancel{I_b} R_e}{\cancel{I_b} (R_s + h_{ie})}$$

$$A_V = \frac{h_{fe} R_e}{R_s + h_{ie}}$$

Step 6. Indicate the value of V_o and V_f .

$$\beta = \frac{V_f}{V_o} = 1$$

Step 7. Calculate D , A_{vf} , R_{if} , R_{of}

$$D = \text{Desensitivity} = 1 + \beta A_V$$

$$\text{if } A_V = 2.3, \beta = 1$$

$$D = 3.3$$

$$A_{vf} = \frac{A_v}{D} = 0.7$$

$$R_i = R_s + h_{ie}$$

$$\text{if } h_{ie} = 1.1 \text{ K}\Omega$$

$$R_i = 2.1 \text{ K}\Omega$$

$$R_o = \infty$$


$$\Rightarrow R_{of} = \infty$$

$$R_{of}' = \frac{R_o}{D} = \frac{R_e}{D} = \frac{100}{3.38} = 29.58 \Omega$$

* Current Series Feedback

This topology is shown below in the ckt.

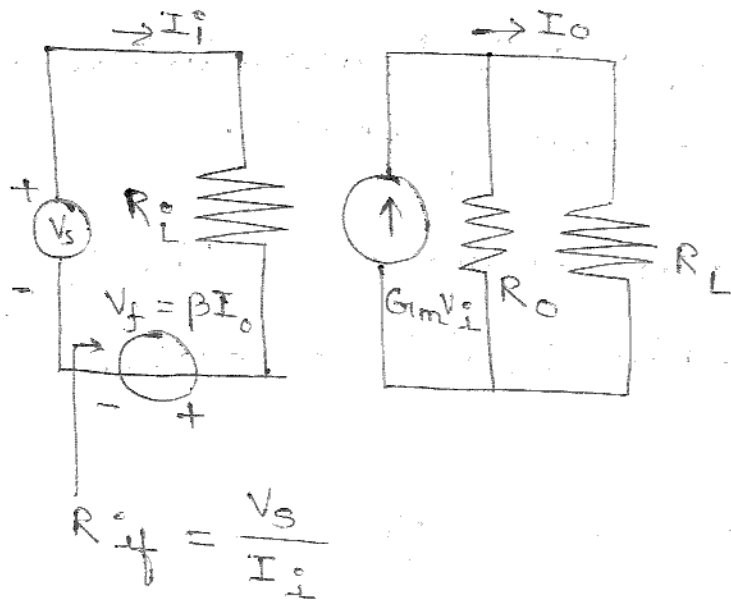The amplifier equivalent ip ckt is represented by thevenin's equivalent and o/p ckt is represented by Norton's equivalent ckt.



I/p resistance with feedback

$$R_{if} = \frac{V_s}{I_i}$$

by applying KVL to i/p side

$$V_s - I_i R_o - V_f = 0$$

$$V_s = I_i R_o + V_f = 0$$

$$V_s = I_i R_o + \beta I_o \quad \text{--- (5)}$$

$$I_o = \frac{G_m V_i R_o}{R_o + R_L} = \frac{G_M V_i}{R_o + R_L} \quad \text{--- (6)}$$

where

$$G_M = \frac{G_m R_o}{R_o + R_L}$$

$G_{om} \rightarrow$ Open ckt transconductance without feedback.

$G_M \rightarrow$ Transconductance without fb while R_L into account.

Subst I_o in eq (5)

$$V_S = I_i R_i + \frac{\beta G_{om} V_i R_o}{R_o + R_L}$$


$$V_S = I_i R_i + \beta V_i G_M$$

$$V_S = I_i R_i + \beta I_i R_i G_M$$

$$V_S = I_i R_i [1 + \beta G_M]$$

$$R_{of} = \frac{V_S}{I_i} = R_i [1 + \beta G_M] \quad \text{--- (7)}$$

o/p resistance

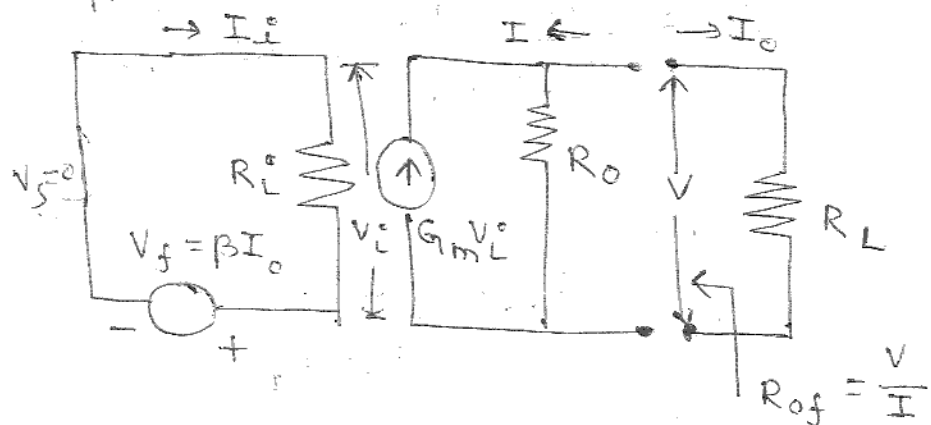

In this topology the resistance is measured by shorting the i/p $V_S = 0$ with R_L is disconnected.

Applying KCL to o/p node

$$I = \frac{V}{R_o} - G_m V_i \quad \text{--- (8)}$$

I/P voltage is given as

$$V_i = -V_f = -\beta I_o$$

$$V_i = \beta I \quad \text{--- (9)} \quad \because I = -I_o$$