

$$= \frac{R_o' (1 + \beta A_i)}{1 + \beta A_i \beta_i}$$

JS
10/6/19

26/6/14

Methodology of Feedback Amplifiers &

analysis:-

→ To analyse the feedback amplifier, it is necessary to go for following steps:-

Step 1:- Identify topology type of feedback.

(a) To find the type of Sampling Network,

(i) By shorting the o/p $V_o = 0$, if feedback signal X_f becomes zero, then we can say that it is voltage sampling.

(ii) By opening the o/p loop, $I_o = 0$, if feedback signal X_f becomes zero, then we can say that it is current sampling.

(b) To find the type of mixing n/w is:

- (i) If the feedback signal is subtracted from the externally applied signal, as a voltage, in the i/p loop we can say that it is series mixing.
- (ii) If the feedback signal is subtracted from the externally applied signal, as a current, in the i/p loop, we can say that it is shunt mixing.

Step 2: - Find the i/p ckt,

(i) for voltage sampling, make $V_o = 0$
by shorting the o/p loop.

(ii) for current sampling, make $I_o = 0$,
by opening the o/p loop,
(^{or} open ckt)

Step 3: - Find the o/p ckt,

(i) for series mixing make, $I_i = 0$
by opening the i/p loop

(ii) for shunt mixing make $V_i = 0$

by shorting the i/p.

Step 4:- Replace each active device by its H-parameter model at low frequency.

Step 5:- Find the open loop gain; i.e. (without feedback) denoted as A of Amplifier.

Step 6:- Indicate X_f and X_o on the circuit &

evaluate $\beta = \frac{V_f}{V_o}$.

Step 7:- From A and β find D


i.e. ~~Des~~ Desensitivities, A_f = feedback gain,

R_{if} = i/p resistance with feedback.

R_{of} = o/p resistance with feedback.

R

Analysis :-

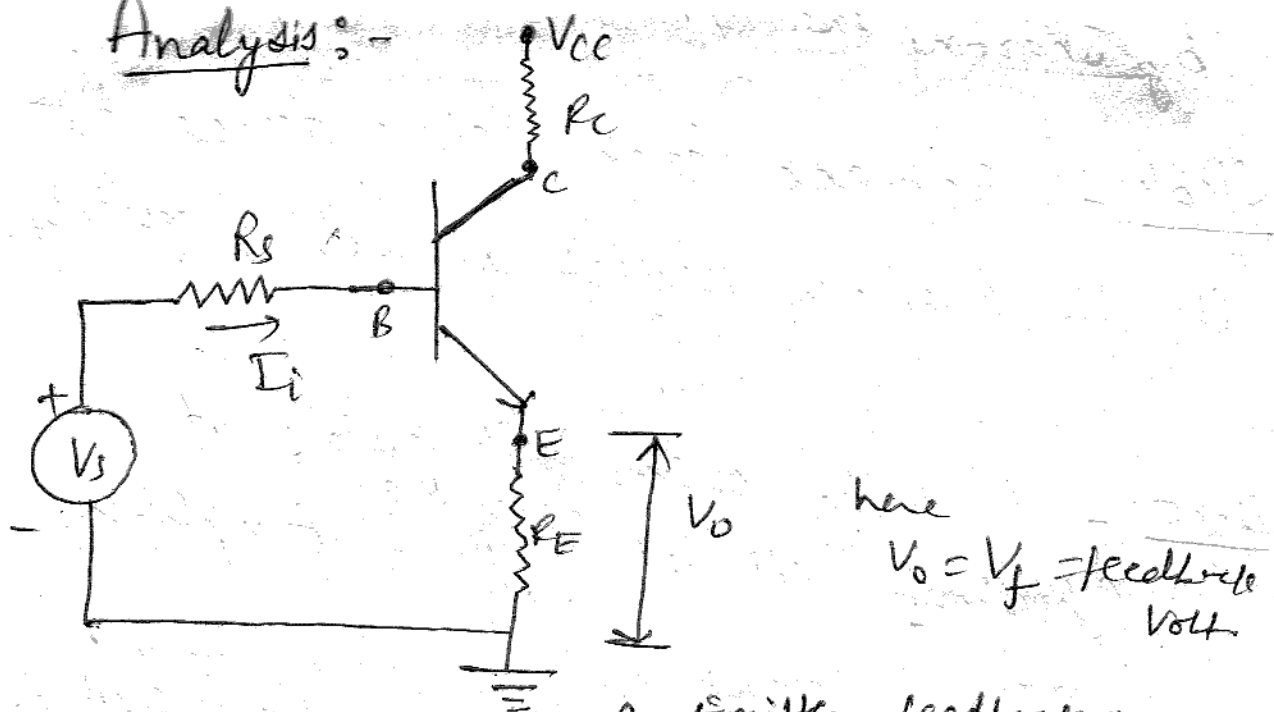

Step 1 (a)

→ It is voltage sampling,

from emitter, feedback is given to base.

If $V_o = 0$,
feedback voltage $V_f = 0$

→ it is voltage sampling

Step 1(b)

To find type of mixing w/wth,

Apply KVL in 1/P loop,

$$\cancel{-V_s + I_i R_s + V_o = 0}$$

$$\Rightarrow -V_s + \cancel{I_i R_s} + I_i R_e = 0$$

$$\Rightarrow V_s = \cancel{I_i R_s} + I_i R_e$$


$$V_s - I_i R_s - V_o = 0$$

$$\Rightarrow V_s - I_i R_s - V_f = 0$$



→ series mixing

Since feedback voltage is subtracted from source voltage (ie externally applied signal)

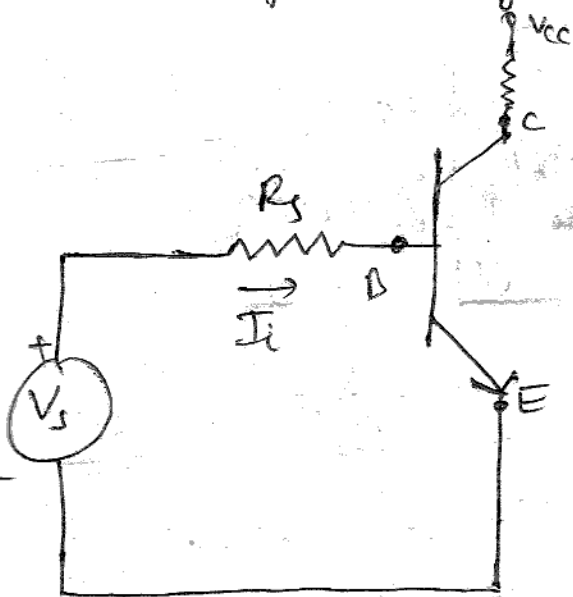Step 2 for voltage sampling, make $V_o = 0$.




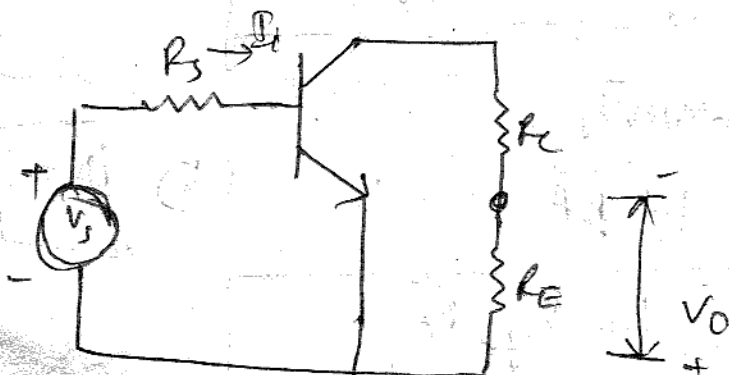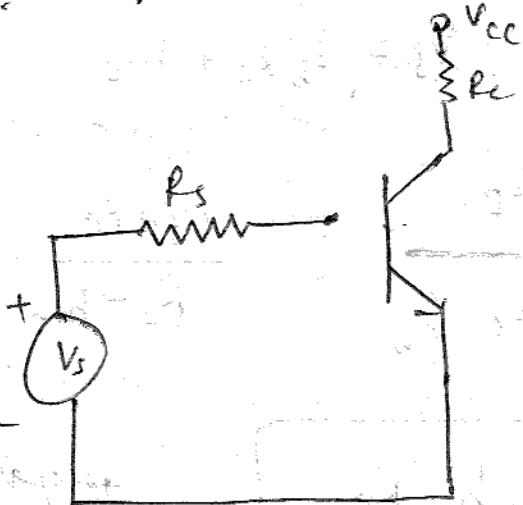Step 3:- for series mixing, make $I_i = 0$



28/5/14

$A_v = \frac{V_o}{V_i}$

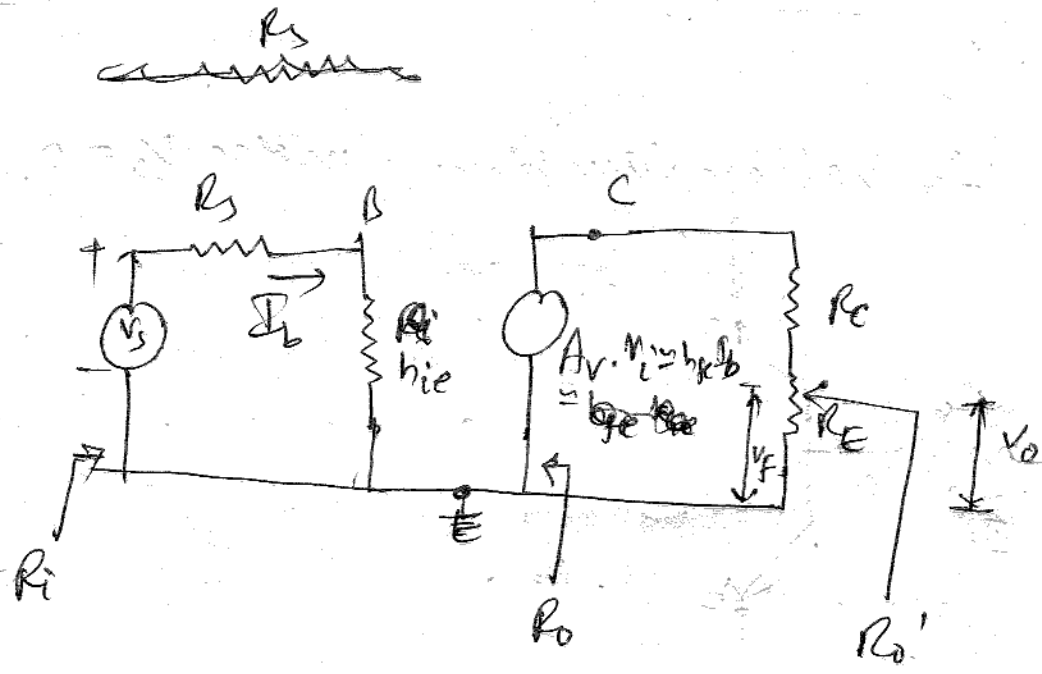

$A_v = \frac{V_o}{V_i}$

$V_o = h_{fe} I_b \times R_E$

$V_s = I_b R_s + h_{ie} I_b$

$A_v = \frac{h_{fe} I_b \times R_E}{I_b R_s + h_{ie} I_b} = \frac{h_{fe} R_E}{R_s + h_{ie}}$

(i) $A_v = \frac{h_{fe} R_E}{R_s + h_{ie}}$

for

$\therefore V_f = \beta V_b$

$\beta = \frac{V_f}{V_b}$

Sensitivity

(ii) $D = 1 + \beta A$

(iii)

$\beta = 1$

$D = 1 + \frac{h_{fe} R_E}{R_s + h_{ie}}$

^{Voltage}
 $A_{vf} = \text{gain with feedback.}$

$$\therefore D = 1 + \beta A$$

$$A_{vf} = \frac{A}{1 + \beta A} = \frac{A}{D} = \frac{A_v}{1 + \frac{h_{fe} R_E}{R_s + h_{ie}}}$$

$$A_{vf} = \frac{A_v}{1 + \frac{h_{fe} R_E}{R_s + h_{ie}}}$$

~~$$A_{vf} = A_v (R_s)$$~~

$$A_{vf} = \frac{h_{fe} R_E}{R_s + h_{ie} + h_{fe} R_E}$$

$$A_{vf} = \frac{h_{fe} R_E}{R_s + h_{ie} + h_{fe} R_E}$$

$R_{if} =$ i/p resistance with feedback,

$$R_{if} = R_i (1 + \beta A_v)$$

$$R_{if} = R_i D$$

$$R_{if} = (R_s + h_{ie}) D$$

Now, $R_o \approx \infty$ By open ckting.

$$R_{of} = \frac{R_o}{1 + \beta}$$


$$\Rightarrow R_{of} = \infty$$

R_{of} = o/p resistance without $R_L = \infty$




R_{of}' = o/p resistance with feedback = R_e

$$\begin{aligned} R_{of}' &= R_{of} \parallel R_e \\ &= \infty \parallel R_e \\ &= R_e \end{aligned}$$

Q2 Find the sampling n/w

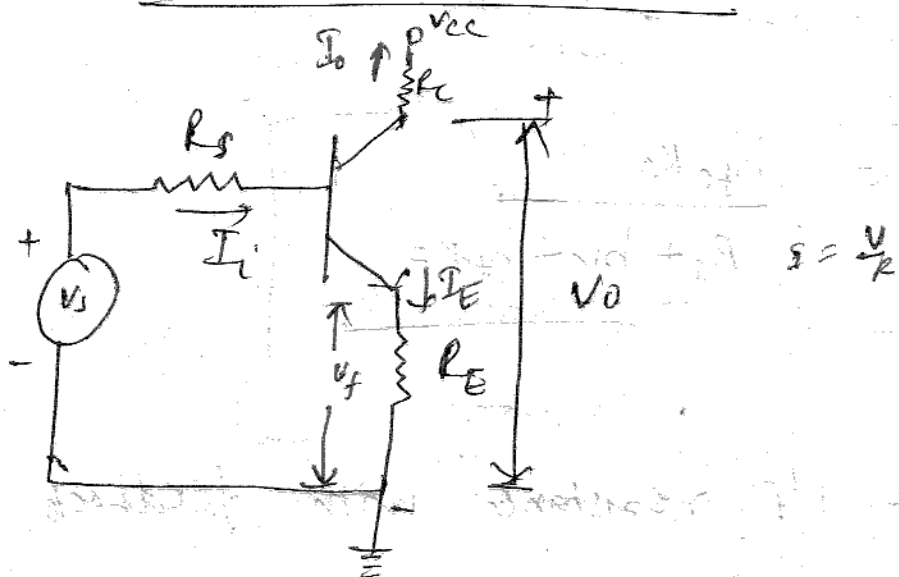

\Rightarrow Current series

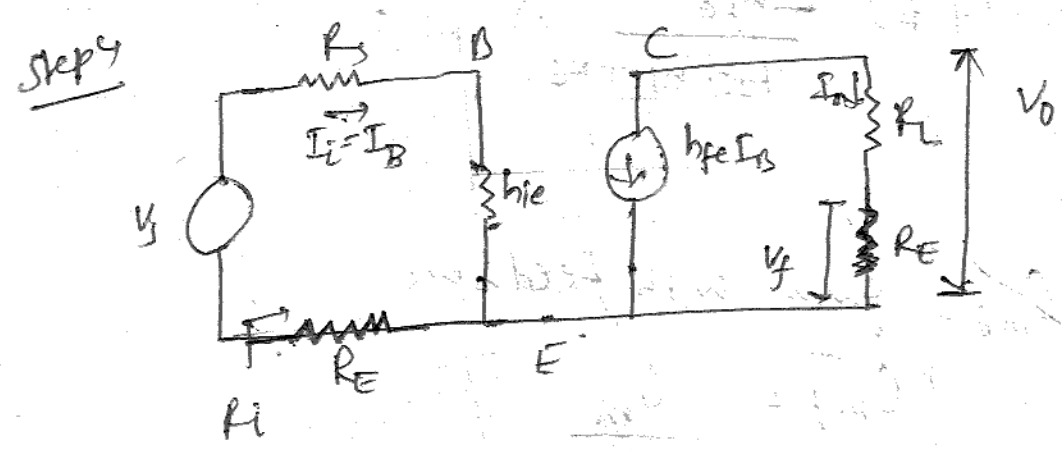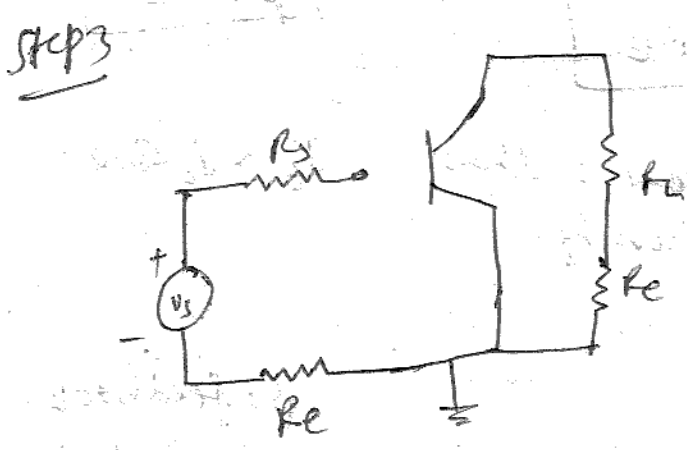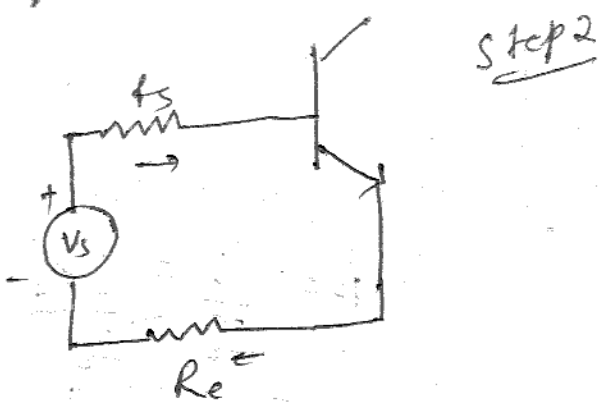

O/P → current
 I/P → voltage.

$$\text{Gain} = \frac{I_o}{V_i} \Rightarrow G_m = \frac{I_o}{V_i}$$

also, $I_o = -h_{fe} I_B$

in loop 1,

$$G_m = \frac{-h_{fe} I_B}{V_i} \quad V_i = I_B (R_s + h_{ie} + R_E)$$

$$G_m = \frac{-h_{fe} I_B}{I_B (R_s + h_{ie} + R_E)} = \frac{-h_{fe}}{R_s + h_{ie} + R_E}$$

$$G_m = \frac{-h_{fe}}{R_s + h_{ie} + R_E}$$

$$\beta = \frac{-I_o R_E}{I_o} = R_E$$

$$\beta = -R_E$$

$$\beta = \frac{V}{I_o} = \frac{I_o R_E}{I_o}$$

$$\beta = R_E$$

⇒ minus sign indicates that I_E & I_o are opposite, flowing.

Sensitivity, $D = (1 + \beta) G_m$

β = feedback factor

$$D = (1 + \beta) \left(\frac{-h_{fe}}{R_s + h_{ie} + R_E} \right)$$

G_{mf} = gain with feedback

$$G_{mf} = \frac{G_m}{D}$$

$$G_{mf} = \frac{-h_{fe}}{R_s + h_{ie} + R_E} \cdot \frac{1}{(1 + \beta) \left(\frac{-h_{fe}}{R_s + h_{ie} + R_E} \right)}$$

$$= \frac{h_{fe}}{R_s + h_{ie} + R_E}$$

$$G_{mf} = \frac{-h_{fe}}{R_s + h_{ie} + R_E} \quad \neq \quad \frac{(1+\beta)h_{fe}}{R_s + h_{ie} + R_E}$$

$$= \frac{-h_{fe}}{R_s + h_{ie} + R_E} \times \frac{R_s + h_{ie} + R_E}{(1+\beta)h_{fe}}$$

$$= \frac{-1}{1+\beta}$$

$$G_{mf} = \frac{-1}{1+\beta}$$

Desensitivity,

$$D = 1 + \beta G_m$$

$$= 1 + \beta \left(\frac{-h_{fe}}{R_s + h_{ie} + R_E} \right)$$

$$= \frac{R_s + h_{ie} + R_E - \beta h_{fe}}{R_s + h_{ie} + R_E}$$

$$G_{mf} = \frac{G_m}{D}$$

$$= \frac{\frac{-h_{fe}}{R_s + h_{ie} + R_E}}{\frac{R_s + h_{ie} + R_E - \beta h_{fe}}{R_s + h_{ie} + R_E}}$$

$$\beta = -R_E$$

$$G_{mf} = \frac{-h_{fe}}{R_s + h_{ie} + R_E + R_E h_{fe}}$$

$$G_{mf} = \frac{-h_{fe}}{R_s + h_{ie} + R_E (1 + h_{fe})}$$