

05/07/11

## To Find the type of Sampling Network

1. By shorting the output  $V_o = 0$ , if feedback signal  $\alpha_f \rightarrow 0$ , then we can say that it is voltage sampling.
2. By opening the output loop  $I_o \neq 0$ . If feedback signal  $\alpha_f$  become zero then we can say that it is current sampling.

## To find the type of mixing network

- 3) If the feedback signal is subtracted from the externally applied signal as a voltage in the input loop, we can say that it is series mixing.
- 4) If the feedback signal is subtracted from the externally applied signal as a current in the input loop, we can say that it is shunt mixing.
- 5) Replace each active device by its h parameter model at low frequency.

6. Find the open loop gain (gain without feedback).


A of the Amplifier

7. Indicate  $x_f$  and  $x_o$  on the circuit and Evaluate  $\beta = \frac{x_f}{x_o}$ .

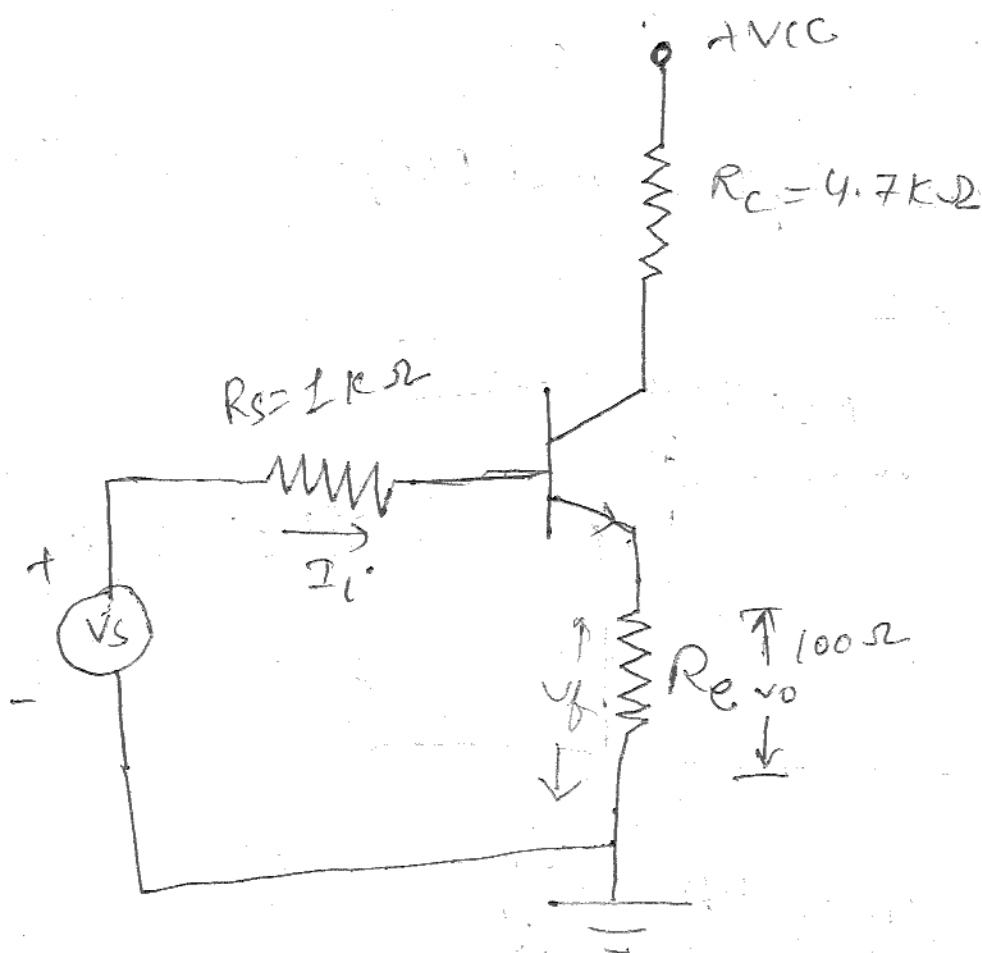8. From A and  $\beta$  find D (Desensitivity)

$A_f$ ,  $R_{if}$ ,  $R_{of}$  and  $R'_{of}$  (taking  $R_c$  into account)

Ex voltage series feedback (for analysis)




1. Identify topology

By shorting O/P voltage  $V_o = 0$ , feedback signal becomes zero and hence it is voltage sampling.


looking at figure (writing  $v_f$ ) the feedback signal  $v_f$  is subtracted from the externally applied signal  $v_s$  and hence it is series mixing. Combining two conditions, we can say that it is voltage series feedback amplifier.

2. Find the input and output circuit

I/P CKT

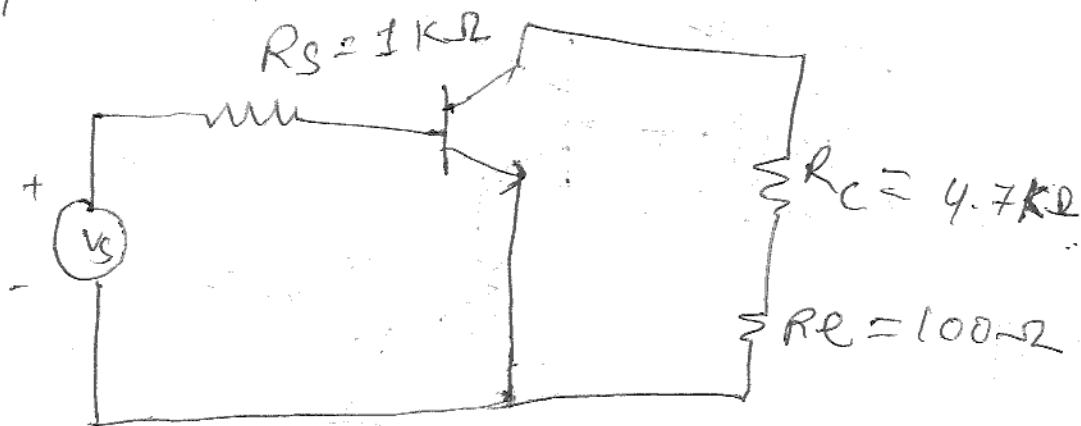

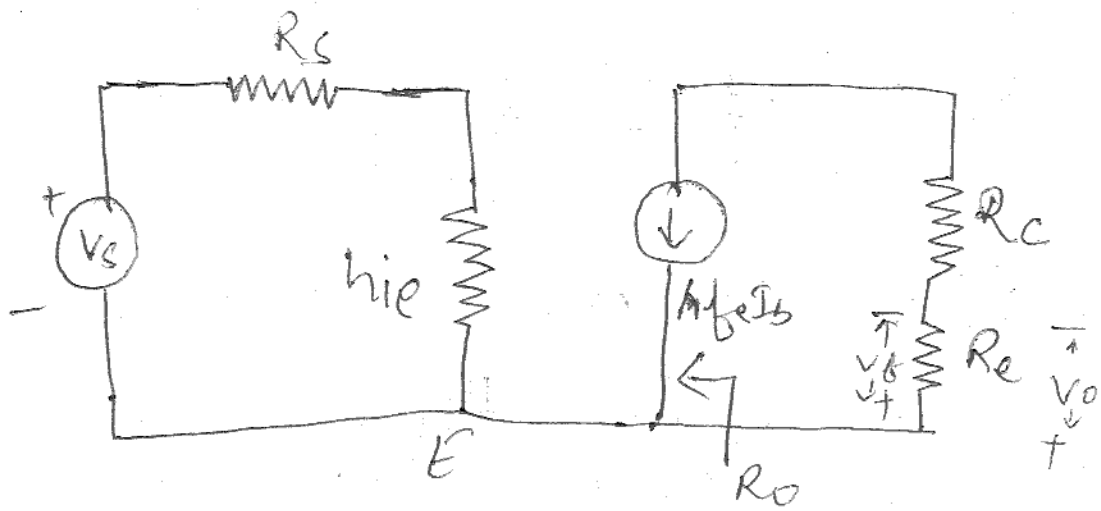3. Replace transistor by  $h$  parameter equivalent circuit.



Open loop gain :-

$$A_v = \frac{V_o}{V_s} = \frac{h_{fe} I_b R_e}{V_s}$$

$$V_s = I_b R_s + I_b h_{ie}$$

$$A_v = \frac{h_{fe} I_b R_e}{I_b (R_s + h_{ie})}$$

$$A_v = \frac{h_{fe} R_e}{R_s + h_{ie}}$$

$$h_{fe} = 50 \quad R_e = 100$$

$$R_s = 1k\Omega \quad h_{ie} = 1.1k\Omega$$

$$A_v = \frac{50 \times 100}{1 + 1.1} = 2.38$$

$$\beta = \frac{V_f}{V_o} = 1$$

$$D = 1 + A\beta \\ = 1 + (2.38) \cdot 1 \\ = 3.38$$

$$A_{vf} = \frac{A}{1 + A\beta} = \frac{2.38}{3.38} = 0.7$$

$$R_i = R_s + h_{ie} = 1k + 1.1k = 2.1k$$

$$R_{if} = R_i D = (2.1k)(3.38) \\ = 7.098k$$

$$R_o = \alpha, R_{of} = \alpha, R'_{of} = \frac{R_o'}{D} \quad R_o' = R_e$$

$$R'_{of} = \frac{R_e}{D} = \frac{100}{3.38} \\ = 29.58 \Omega$$

06/7/11

## UNIT - II

### OSCILLATORS

Barkhausen criteria :-

The frequency at which a sinusoidal oscillator will operate is the frequency for which total shift introduced as a signal proceeds from the input terminals, through the amplifier and feedback N/W and ~~the~~ again to the input is precisely zero.

of course an integral multiple of  $2\pi$ .

Stated more precisely the frequency of a sinusoidal oscillator is determined by the condition that the loop gain phase shift is zero.


Oscillations will not be sustained if at the oscillator frequency, the magnitude of the product of the transfer gain of the amplifier and the magnitude of the feedback factor of the feedback N/W (The magnitude of the loop gain) are less than unity.

The condition of unity loop gain  
 $-A\beta = 1$  is called a Barkhausen  
 criteria. This condition implies of course  
 more than magnitude of  $|A\beta| = 1$  and  
 that the phase of  $-A\beta$  is zero.

The above principles are consistent  
 with the feedback formula


$$A_f = \frac{A}{1 + A\beta} \quad \text{for if } -A\beta = 1$$

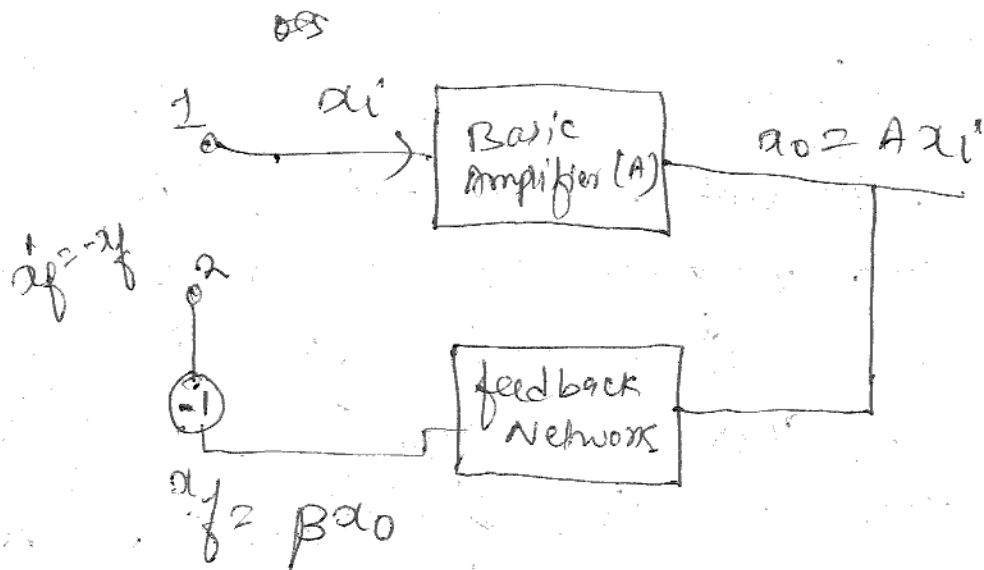then  $A_f \rightarrow \infty$  which may be  
 interpreted to mean that there  
 exist an output voltage even in the  
 absence of an externally applied  
 signal voltage.



Oscillator

# RC PHASE SHIFT OSCILLATOR :-

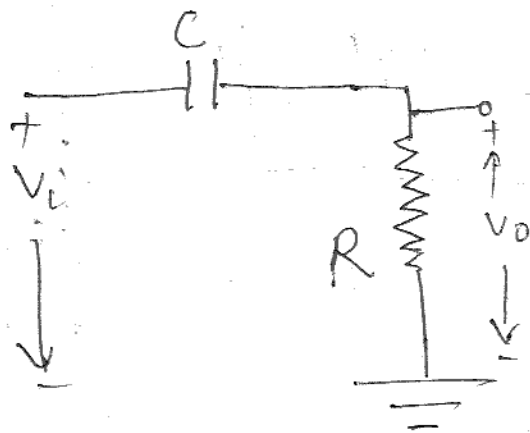

$$Z = R - \frac{j}{\omega C}$$


$$X_C = Z \angle -\phi$$

$$V_i = V_m \sin \omega t$$



$$I = \frac{V_m / \sqrt{2}}{|Z| \angle -\phi}$$

$$V = |I| \angle +\phi$$

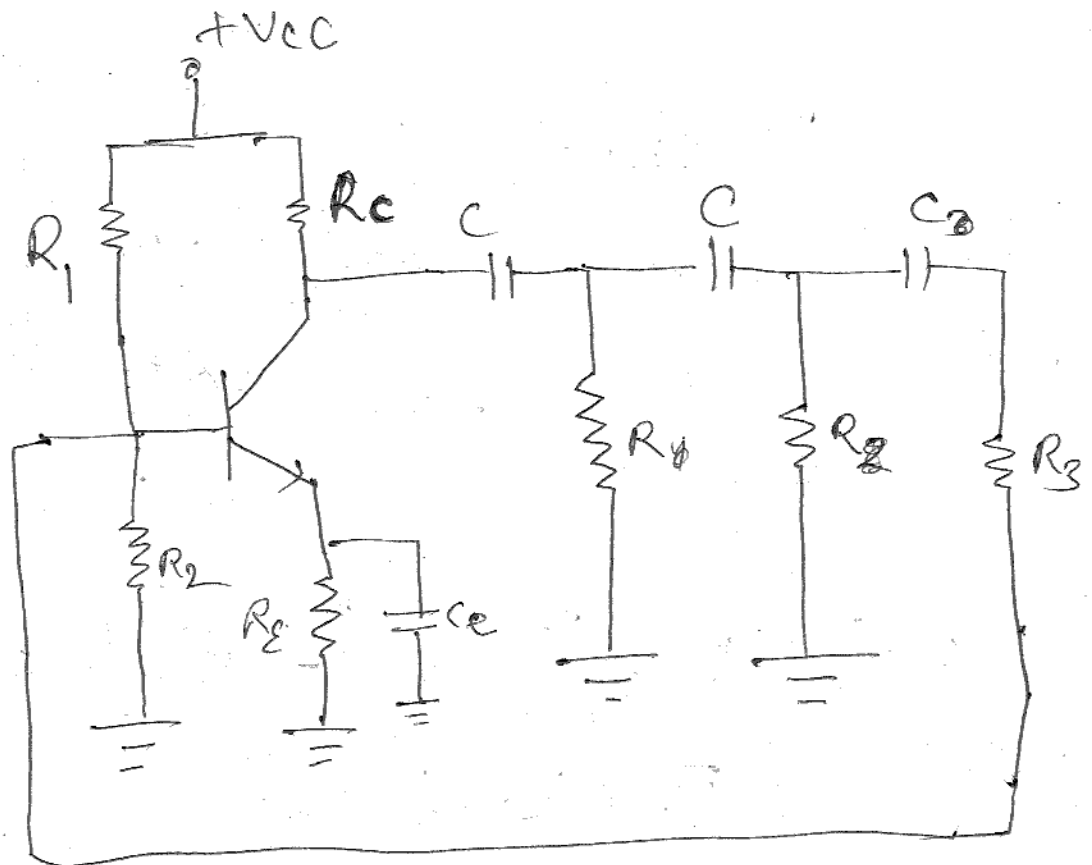The positive phase angle  $+\phi$  indicates that the current leads applied voltage by angle  $\phi$ .





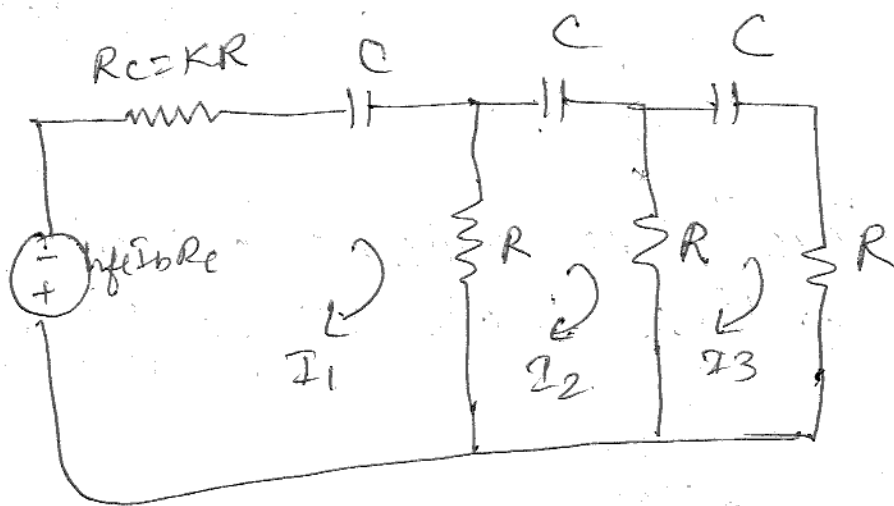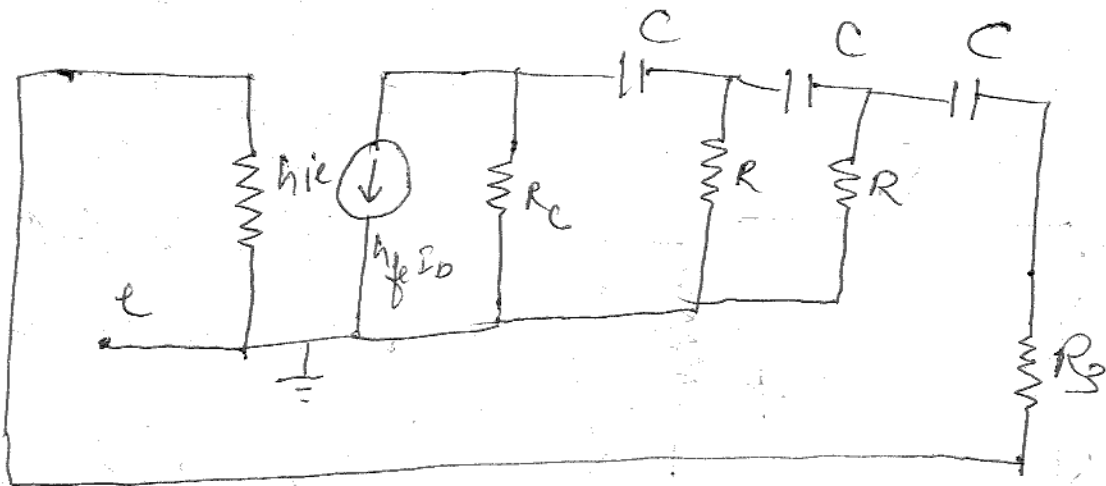

$$D = \begin{bmatrix} (K+1)R + \frac{1}{sC} & -R & 0 \\ -R & 2R + \frac{1}{sC} & -R \\ 0 & -R & 2R + \frac{1}{sC} \end{bmatrix}$$

$$\Delta = \left( (K+1)R + \frac{1}{sC} \right) \left[ \left( 2R + \frac{1}{sC} \right)^2 - R^2 \right] + R \left[ -R \left( 2R + \frac{1}{sC} \right) + 0 \right]$$

$$\Delta = \left[ (K+1)R + \frac{1}{sC} \right] \left[ 4R^2 + \frac{1}{s^2C^2} + \frac{4R}{sC} - R^2 \right]$$

$$+ \left[ -2R^3 - \frac{R^2}{sC} \right]$$

$$= \left\{ \frac{(K+1)RSC + 1}{sC} \right\} \left\{ \frac{4R^2s^2C^2 + 1 + 4RSC - R^2s^2C^2}{s^2C^2} \right\}$$

$$- \left[ \frac{2R^3sC + R^2}{sC} \right]$$

$$= \left\{ \frac{KSRc + RSc + 1}{sC} \right\} \left\{ \frac{3R^2s^2C^2 + 4RSC + 1}{s^2C^2} \right\} - \left\{ \frac{2R^3sC + R^2}{sC} \right\}$$

$$= \frac{[3Ks^3R^3C^3 + 4Ks^2R^2C^2 + KSRc + 3R^3s^3C^3 + 4R^2s^2C^2 + RSc + 3R^2s^2C^2 + 4RSC + 1]}{s^3C^3} - \frac{2R^3sC + R^2}{sC}$$

$$= \frac{3R^3s^3C^3(K+1) + s^2R^2C^2(4K+7) + SRC(K+4) + 1 - (2R^3s^3C^3 + R^2s^2C^2)}{s^3C^3}$$

$$= \frac{3R^3s^3C^3(K+1) - 2R^3s^3C^3 + s^2R^2C^2(4K+7) - R^2s^2C^2 + SRC(K+5) + 1}{s^3C^3}$$

$$\frac{2 + R^3 s^3 c^3 (3K+1) + s^2 R^2 c^2 (4K+6) + s R c (K+5)}{s^3 c^3}$$

$$\Delta I_3 = \begin{bmatrix} (K+1)R + \frac{1}{sc} & -R & -h_{fe} I_b K R \\ -R & 2R + \frac{1}{sc} & 0 \\ 0 & -R & 0 \end{bmatrix}$$

$$= \left[ (K+1)R + \frac{1}{sc} \right] \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} + R \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} - h_{fe} I_b K R$$

$$(R^2 = 0)$$

$$\Delta I_3 = -h_{fe} I_b K R^3$$

$$I_3 = \frac{\Delta I_3}{\Delta} = \frac{-h_{fe} I_b K R^3 s^3 c^3}{(3K+1)R^3 s^3 c^3 + (4K+6)s^2 R^2 c^2 + (K+5) s R c + 1}$$

$I_3$  = output current of the feedback circuit

$I_b$  = Input current of the amplifier

$I_c = h_{fe} I_b$  = input current of the feedback circuit.

$$\beta = \frac{\text{output of feedback ckt}}{\text{Input of feedback ckt}}$$

$$= \frac{I_3}{h_{fe} I_b}$$

$$A = \frac{\text{Output of Amplifier circuit}}{\text{Input to Amplifier ckt}}$$

$$= \frac{h_{fe} I_b}{I_b} = h_{fe}$$

$$A\beta = \frac{h_{fe} I_3}{h_{fe} I_b} = \frac{I_3}{I_b}$$

$$A\beta = \frac{I_3}{I_b} = \frac{-h_{fe} K R^3 s^3 C^3}{(3K+1) R^3 C^3 s^3 + (4K+6) R^2 s^2 C^2 + (K+5) s R C + 1}$$

Sub  $s = j\omega$ ,  $s^2 = (j\omega)^2 = j^2 \omega^2 = -\omega^2$

$$s^3 = (j\omega)^3 = j^2 \cdot j\omega^3 = -j\omega^3$$

$$A\beta = \frac{I_3}{I_b} = \frac{-h_{fe} \cdot KR^3 (-j\omega^3) C^3}{(3K+1) R^3 C^3 (-j\omega^3) + (4K+6) R^2 C^2 + (K+5) (j\omega) RC + 1}$$

$$= \frac{+ h_{fe} jKR^3 C^3 \omega^3}{-j(3K+1) R^3 C^3 \omega^3 - (4K+6) R^2 C^2 + j(K+5) \omega RC + 1}$$

$$= \frac{h_{fe} jKR^3 C^3 \omega^3}{[1 - (4K+6) R^2 C^2 \omega^2] + j[\omega RC(K+5) - 3K\omega^3 C^3 R^3]}$$

$$A\beta = \frac{h_{fe} jKR^3 C^3 \omega^3}{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] + j[\omega RC(K+5) - 3K\omega^3 C^3 R^3]}$$

$$A\beta = \frac{h_{fe} jKR^3 C^3 \omega^3}{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] + j\omega [RC(K+5) - 3K\omega^2 C^3 R^3]}$$

Dividing Numerator and denominator by  $j\omega^3 R^3 C^3$

$$A\beta = \frac{K h_{fe}}{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] - j\omega^3 R^3 C^3}$$

$$\frac{K h_{fe}}{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] - j\omega^3 R^3 C^3} = \frac{j\omega [3K\omega^2 C^3 R^3] + [KRC]}{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] - j\omega^3 R^3 C^3}$$

Replacing  $\frac{1}{J} = -J'$

$$\Sigma K_{life}$$

---

32

34  
rc-

3