

05/07/11

To Find the type of Sampling Network

1. By shorting the output $V_o = 0$, if feedback signal $x_f \rightarrow 0$, then we can say that it is voltage sampling.

2. By opening the output loop $i_o = 0$. If feedback signal x_f become zero then we can say that it is current sampling.

To find the type of mixing network

3) If the feedback signal is subtracted from the externally applied signal as a voltage in the input loop, we can say that it is series mixing.

4) If the feedback signal is subtracted from the externally applied signal as a current in the input loop, we can say that it is shunt mixing.

5) Replace each active device by its h parameters model at low frequency.


6. Find the open loop gain (gain without feedback).

A of the Amplifier

7. Indicate x_f and x_o on the circuit and evaluate $\beta = \frac{x_f}{x_o}$.

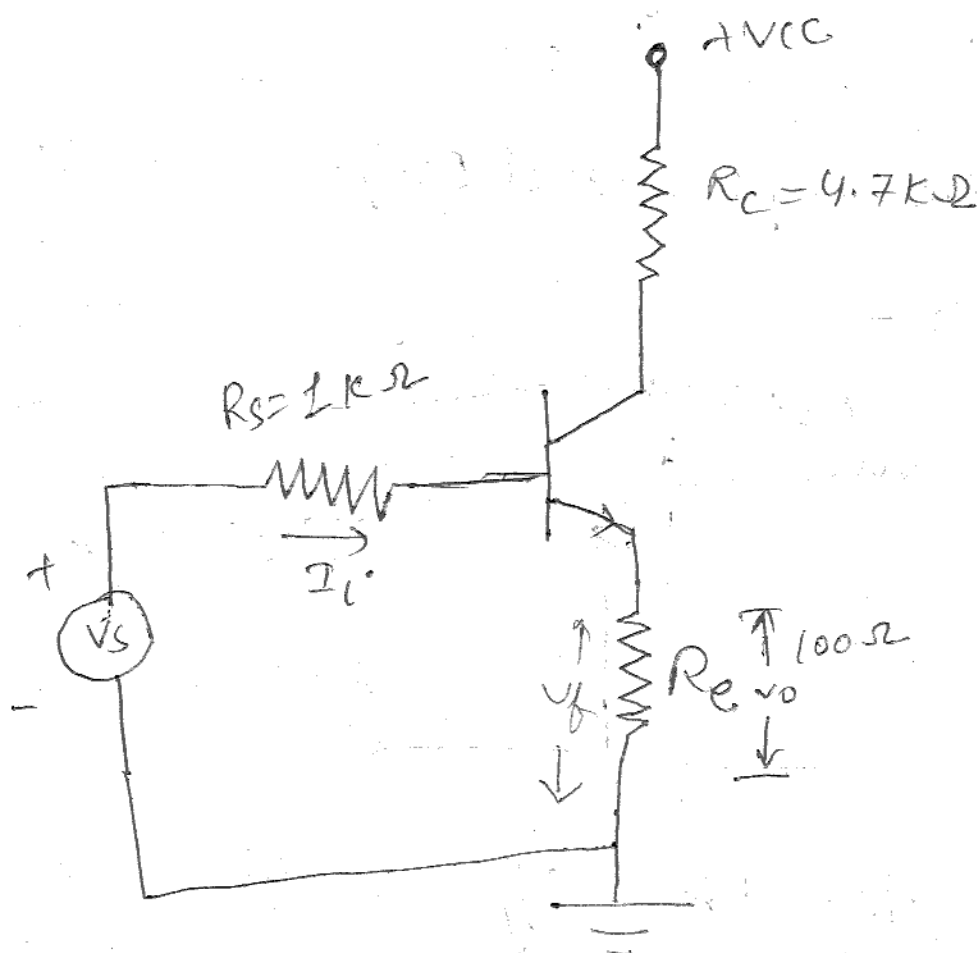8. From A and β find D (Desensitivity) A_f , R_{if} , R_{of} and R'_{of} (taking R_e into account)

Ex voltage series feedback (for analysis)




1. Identify topology

By shorting O/P voltage $V_o = 0$, feedback signal becomes zero and hence it is voltage sampling.


Looking at figure (writing V_f) the feedback signal V_f is subtracted from the externally applied signal V_s and hence it is series mixing. Combining two conditions, we can say that it is voltage series feedback amplifier.

2. Find the input and output circuit

I/P CKT

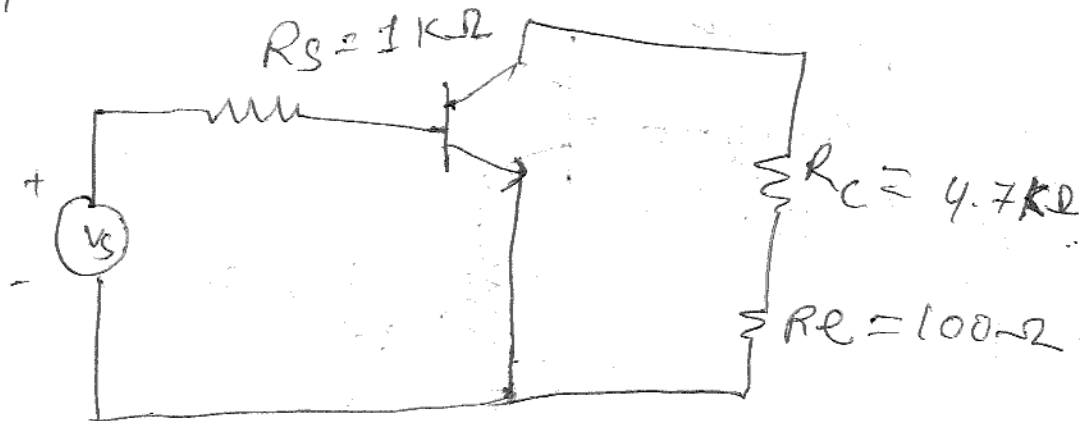

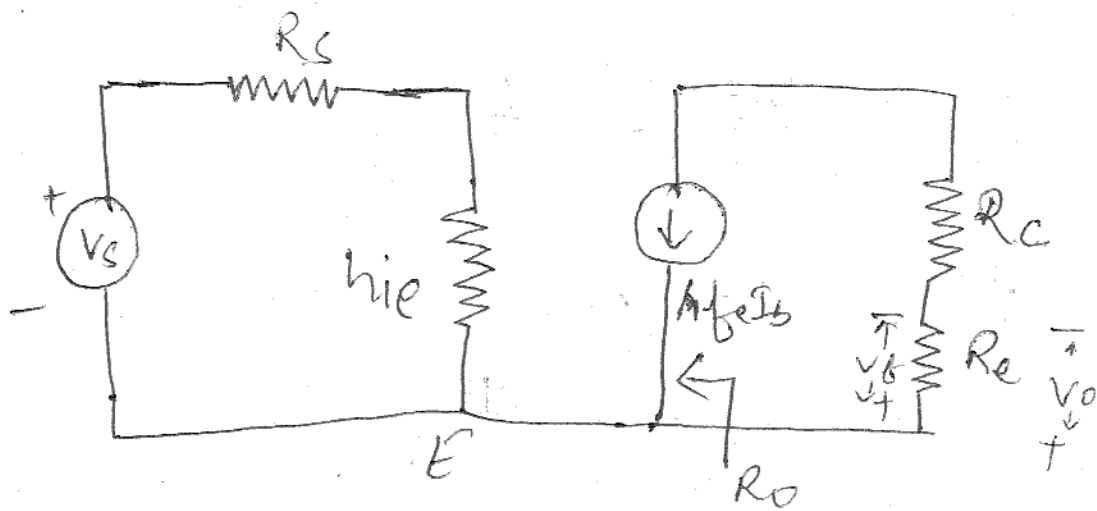3. Replace transistor by h parameters equivalent circuit.



Open loop gain :-

$$A_v = \frac{V_o}{V_s} = \frac{h_{fe} I_b R_e}{V_s}$$

$$V_s = I_b R_s + I_b h_{ie}$$

$$A_v = \frac{h_{fe} I_b R_e}{I_b (R_s + h_{ie})}$$

$$A_v = \frac{h_{fe} R_e}{R_s + h_{ie}}$$

$$h_{fe} = 50 \quad R_e = 100$$

$$R_s = 1K \quad h_{ie} = 1.1K$$

$$A_v = \frac{50 \times 100}{1 + 1.1} = 2.38$$

$$\beta = \frac{V_f}{V_o} = 1$$

$$\begin{aligned} D &= 1 + A\beta \\ &= 1 + (2.38) \cdot 1 \\ &= 3.38 \end{aligned}$$

$$A_{vf} = \frac{A}{1 + A\beta} = \frac{2.38}{3.38} = 0.7$$

$$R_e = R_s + h_{ie} = 1k + 1.1k = 2.1k$$

$$\begin{aligned} R_{if} &= R_e D = (2.1k)(3.38) \\ &= 7.098k \end{aligned}$$

$$R_o = \alpha, R_{of} = \alpha, R'_{of} = \frac{R_o'}{D} \quad R_o' = R_e$$

$$\begin{aligned} R'_{of} &= \frac{R_e}{D} = \frac{100}{3.38} \\ &= 29.58 \Omega \end{aligned}$$

06/7/11

UNIT - II

OSCILLATORS

Barkhausen criteria :-

The frequency at which a sinusoidal oscillator will operate is the frequency for which total shift introduced as a signal proceeds from the input terminals, through the amplifier and feedback N/W and ~~the~~ again to the input is precisely zero.

of course an integral multiple of 2π .

Stated more precisely the frequency of a sinusoidal oscillator is determined by the condition that the loop gain phase shift is zero.

Oscillations will not be sustained if at the oscillator frequency, the magnitude of the product of the transfer gain of the amplifier and the magnitude of the feedback factor of the feedback N/W (


The magnitude of the loop gain) are less than unity.

The condition of unity loop gain $-AB = 1$ is called a Barkhausen criteria. This condition implies of course more than magnitude of $|AB| = 1$ and that the phase of $-AB$ is zero.

The above principles are consistent with the feedback formula


$$A_f = \frac{A}{1 + AB} \quad \text{for if } -AB = 1$$

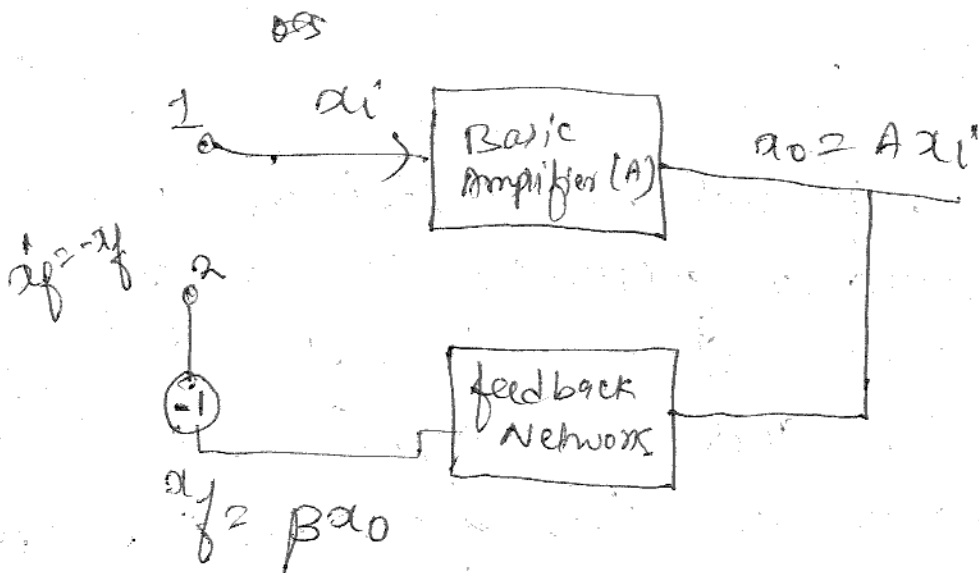then $A_f \rightarrow \infty$ which may be interpreted to mean that there exist an output voltage even in the absence of an externally applied signal voltage.



Oscillator

RC PHASE SHIFT OSCILLATOR :-

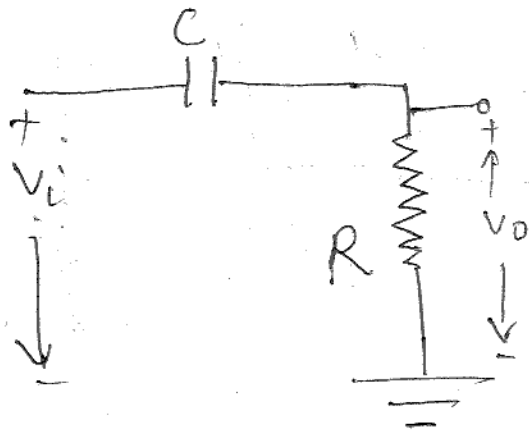

$$Z = R - \frac{j}{\omega C}$$


$$X_C = Z \angle -\phi$$



$$V_i = V_m \sin \omega t$$

$$I = \frac{V_m / \sqrt{2}}{|Z| \angle -\phi}$$

$$I = |I| \angle +\phi$$

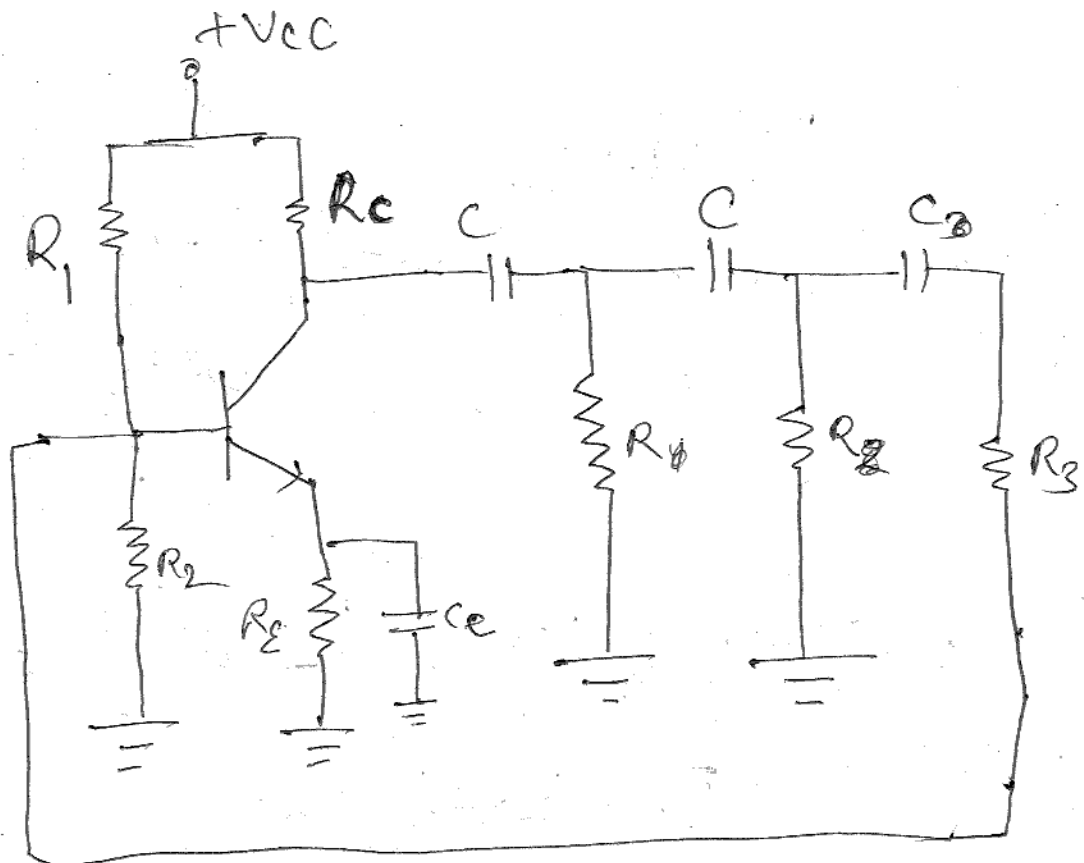The positive phase angle $+\phi$ indicates that the current leads applied voltage by angle ϕ .



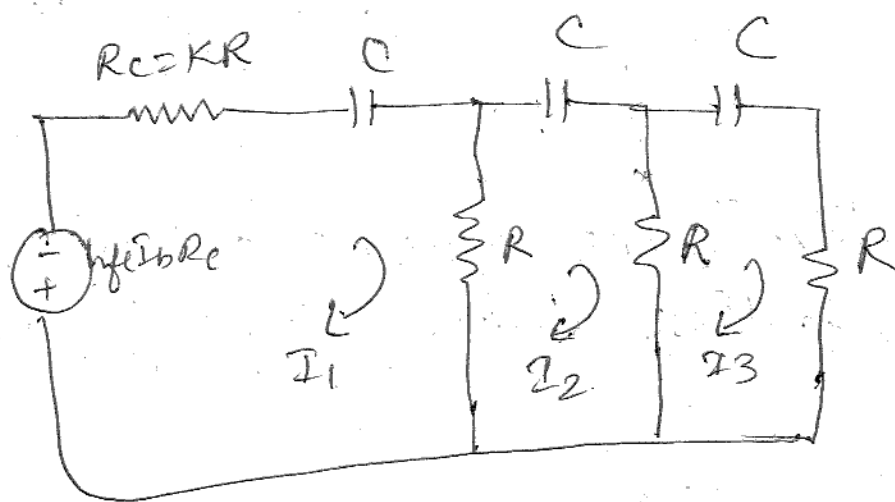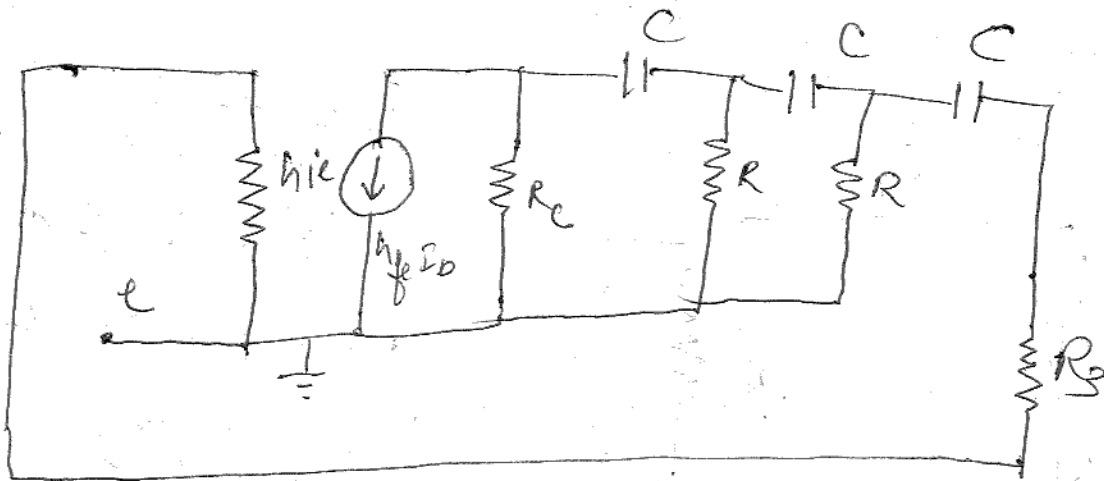

$$D = \begin{bmatrix} (K+1)R + \frac{1}{sC} & -R & 0 \\ -R & 2R + \frac{1}{sC} & -R \\ 0 & -R & 2R + \frac{1}{sC} \end{bmatrix}$$

$$\Delta = \left((K+1)R + \frac{1}{sC} \right) \left[\left(2R + \frac{1}{sC} \right)^2 - R^2 \right] + R \left[-R \left(2R + \frac{1}{sC} \right) + 0 \right]$$

$$\Delta = \left[(K+1)R + \frac{1}{sC} \right] \left[4R^2 + \frac{1}{s^2C^2} + \frac{4R}{sC} - R^2 \right]$$

$$+ \left[-2R^3 - \frac{R^2}{sC} \right]$$

$$= \left\{ \frac{(K+1)RSC + 1}{sC} \right\} \left\{ \frac{4R^2s^2C^2 + 1 + 4RSC - R^2s^2C^2}{s^2C^2} \right\}$$

$$- \left[\frac{2R^3sC + R^2}{sC} \right]$$

$$= \left\{ \frac{KSRc + RSc + 1}{sC} \right\} \left\{ \frac{3R^2s^2C^2 + 4RSC + 1}{s^2C^2} \right\} - \left\{ \frac{2R^3sC + R^2}{sC} \right\}$$

$$= \left[\frac{3Ks^3R^3C^3 + 4Ks^2R^2C^2 + KSRc + 3R^3s^3C^3 + 4R^2s^2C^2 + RSc + 3R^2s^2C^2 + 4RSC + 1}{s^3C^3} \right] - \frac{2R^3sC + R^2}{sC}$$

$$= \frac{3R^3s^3C^3(K+1) + s^2R^2C^2(4K+7) + SRC(K+4) + 1 - (2R^3s^3C^3 + R^2s^2C^2)}{s^3C^3}$$

$$= \frac{3R^3s^3C^3(K+1) - 2R^3s^3C^3 + s^2R^2C^2(4K+7) - R^2s^2C^2 + SRC(K+5) + 1}{s^3C^3}$$

$$\frac{21 + R^3 S^3 C^3 (3K + 1) + S^2 R^2 C^2 (4K + 6) + SRC (K + 5)}{S^3 C^3}$$

$$\Delta I_3 = \begin{bmatrix} (K+1)R + \frac{1}{sC} & -R & -h_{fe} I_{bK} R \\ -R & 2R + \frac{1}{sC} & 0 \\ 0 & -R & 0 \end{bmatrix}$$

$$= \left[(K+1)R + \frac{1}{sC} \right] \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} + R \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} - h_{fe} I_{bK} R$$

$$(R^2 = 0)$$

$$\Delta I_3 = -h_{fe} I_{bK} R^3$$

$$I_3 = \frac{\Delta I_3}{\Delta} = \frac{-h_{fe} I_{bK} R^3 S^3 C^3}{(3K+1)R^3 S^3 C^3 + (4K+6)S^2 R^2 C^2 + (K+5)SRC + 1}$$

I_3 = output current of the feedback circuit

I_b = Input current of the amplifier

$I_c = h_{fe} I_b$ = input current of the feedback circuit.

$$\beta = \frac{\text{output of feedback ckt}}{\text{Input of feedback ckt}}$$

$$= \frac{I_3}{h_{fe} I_b}$$

$A = \frac{\text{Output of Amplifier circuit}}{\text{Input to Amplifier ckt}}$

$$= \frac{h_{fe} I_b}{I_b} = h_{fe}$$

$$A\beta = \frac{h_{fe} I_3}{h_{fe} I_b} = \frac{I_3}{I_b}$$

$$A\beta = \frac{I_3}{I_b} = \frac{-h_{fe} K R^3 s^3 C^3}{(3K+1)R^3 C^3 s^3 + (4K+6)R^2 s^2 C^2 + (K+5)R s C + 1}$$

Sub $s = j\omega$, $s^2 = (j\omega)^2 = j^2 \omega^2 = -\omega^2$

$$s^3 = (j\omega)^3 = j^2 \cdot j\omega^3 = -j\omega^3$$

$$A\beta = \frac{I_3}{I_6} = \frac{-k_{fe} \cdot KR^3 (-j\omega^3) C^3}{(3K+1) R^3 C^3 (-j\omega^3) + (4K+6) R^2 \omega^2 C^2 + (K+5) (j\omega) RC + 1}$$

$$= \frac{+k_{fe} jKR^3 C^3 \omega^3}{-j(3K+1) R^3 C^3 \omega^3 - (4K+6) R^2 \omega^2 C^2 + j(K+5) \omega RC + 1}$$

$$= \frac{k_{fe} jKR^3 C^3 \omega^3}{[1 - (\omega^2 C^2 R^2)(4K+6)] + j(\omega RC K + j\omega RC - 3K\omega^3 R^3 C^3 - \omega^3 C^3 R^3)}$$

$$A\beta = \frac{k_{fe} jKR^3 C^3 \omega^3}{- [1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] + j[\omega RC K + j\omega RC - 3K\omega^3 C^3 R^3 - \omega^3 C^3 R^3]}$$

$$A\beta = \frac{k_{fe} jKR^3 C^3 \omega^3}{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] + j\omega [RC K + SRC - 3K\omega^2 C^3 R^3 - \omega^2 C^3 R^3]}$$

Dividing Numerator and denominator by $j\omega^3 R^3 C^3$

$$A\beta = \frac{k_{fe}}{\frac{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2]}{-j\omega^3 R^3 C^3} - \frac{j\omega [3K\omega^2 C^3 R^3 + \omega^2 R^3 C^3 - SRC - KRC]}{-j\omega^3 R^3 C^3}}$$

At resonating frequency

$$\beta = \frac{\omega^2 RC [3RC]}{[1 - \omega^2 R^2 C^2]^2 + \omega^2 [3RC]^2}$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

$$\beta = \frac{3 RC^2}{R^2 C^2}$$

$$= \frac{[1 - \frac{1}{R^2 C^2} R^2 C^2]^2 + \frac{1}{R^2 C^2} \times 9 R^2 C^2}{9}$$

$$= \frac{3}{9} = \frac{1}{3}$$

$$\beta = \frac{1}{3}$$

$$|A\beta| \geq 1$$

$$A \geq \frac{1}{\beta} \Rightarrow A \geq \frac{1}{1/3} \Rightarrow A \geq 3$$

$$\boxed{A \geq 3}$$


Suppose $R_1 \neq R_2$; $C_1 \neq C_2$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$\beta = \frac{C_1 R_2}{R_1 C_1 + R_2 C_2 + C_1 R_2}$$

$$A\beta \geq 1$$
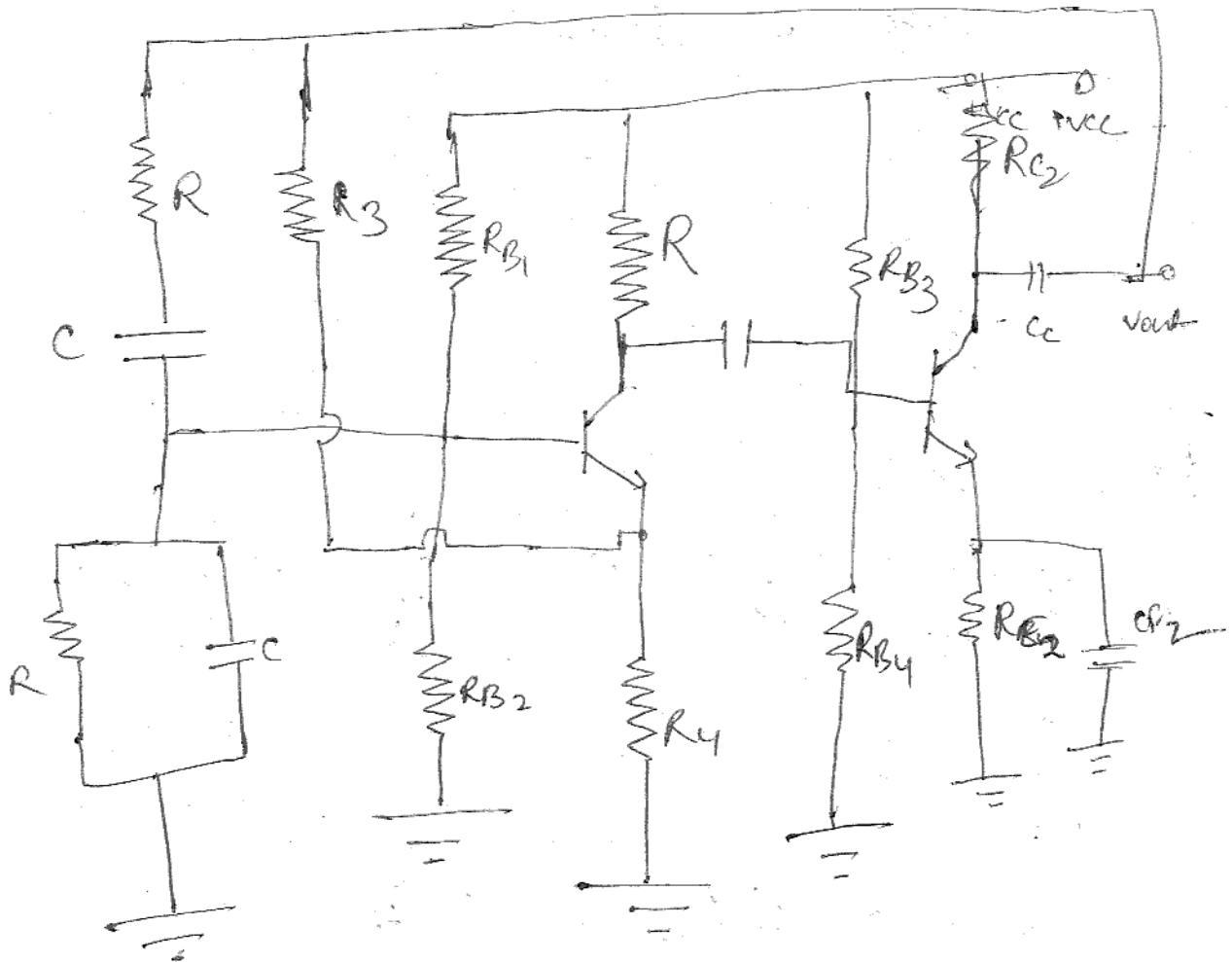
$$A \geq \frac{R_1 C_1 + R_2 C_2 + C_1 R_2}{C_1 R_2}$$



In this circuit two stage common emitter transistor amplifier is used. Each stage contributes 180° phase shift hence the total phase shift due to amplifier stage becomes 360° which is necessary as per the oscillator conditions.

The bridge consists of R and C in series and R & C in parallel, R_3 & R_4 .

The feedback is applied from the collector of Q_2 through the coupling capacitor to the bridge circuit.


The resistance R_4 shows the dual purpose of emitter resistance of the transistor Q_1 and also the element of the Wien Bridge.

The two stage amplifier provides a gain much more than 3 and it is necessary to reduce it. To reduce the gain -ve feedback is used without bypassing resistance R_4 .


The negative feedback can accomplish the gain stability and can control the output magnitude. The -ve feedback also reduces the distortion and therefore output obtained is pure sinusoidal in nature. The amplitude stability can be improved using a non-

linear resistor for R_f . Due to this the loop gain depends on the amplitude of the oscillation. Increase in the amplitude of the oscillation, increases the current through non linear resistance which results into an increase in the value of non-linear resistance R_f .

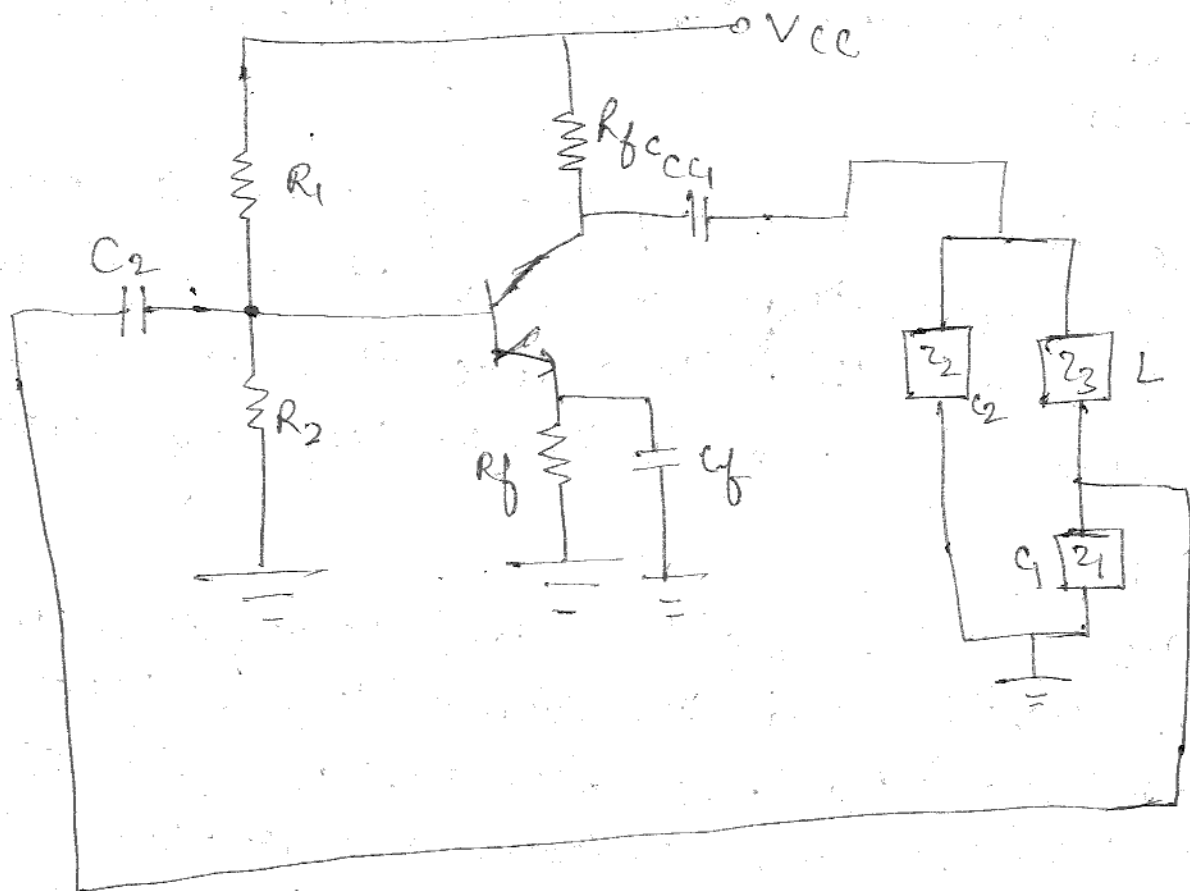When this value increases, a greater amount of -ve feedback is applied. This induces the loop gain & hence signal amplitude gets reduced & controlled.




TRANSISTORISED COLPITTS OSCILLATOR

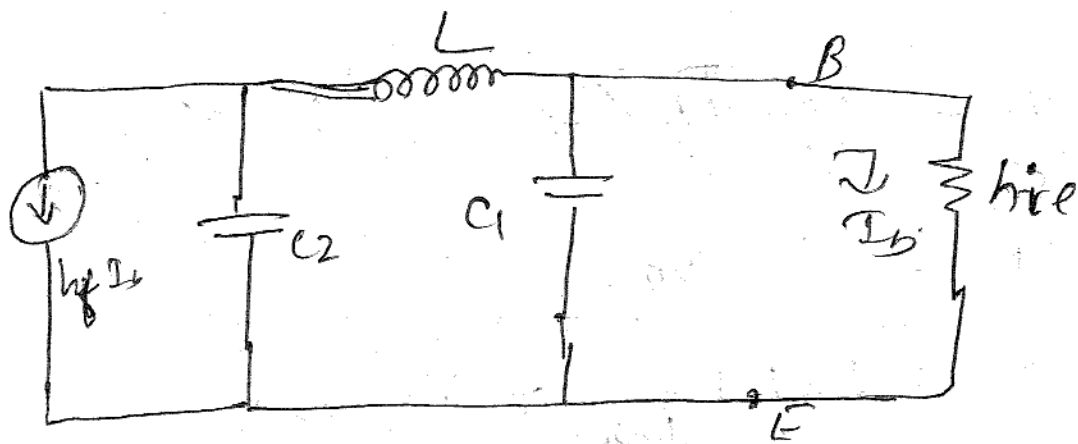

The O/P current I_c which is $h_f I_b$ acts as i/p to the feedback network while the base current I_b acts as the O/P current of the tank circuit, flowing through the input impedance of the amplifier h_{ie} . The equivalent circuit of the tank circuit is shown in fig.

Converting the current source into voltage source we get the equivalent circuit as shown in fig.

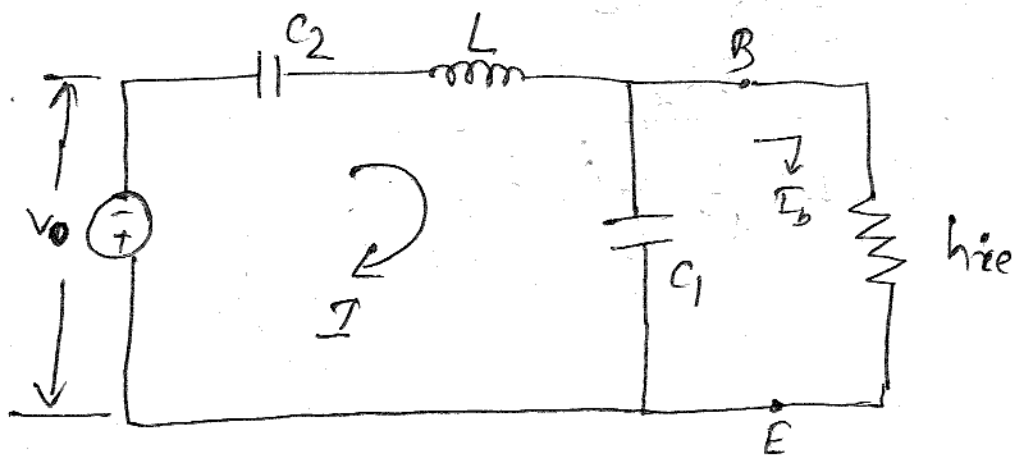Converting the Norton's equivalent to Thevenin's we get



$$V_o = h_{fe} I_b X_{C_2} = h_{fe} I_b \frac{1}{j\omega C_2}$$

$$I = \frac{-V_o}{j\omega L + \frac{1}{j\omega C_2} + X_{C_1} \parallel h_{ie}}$$

$$X_{C_1} \parallel h_{ie} = \frac{1}{\frac{1}{h_{ie}} + j\omega C_1}$$

$$I = \frac{-h_{fe} I_b}{j\omega C_2} \frac{1}{h_{ie} + \frac{1}{j\omega C_1}}$$

$$I = \frac{-h_{fe} I_b}{j\omega C_2} \frac{h_{ie}}{h_{ie} + \frac{1}{j\omega C_1}}$$

$$I = \frac{-h_{fe} I_b}{j\omega C_2} \frac{h_{ie}}{h_{ie} + \frac{1}{j\omega C_1}}$$

$$I = \frac{-h_{fe} I_b}{j\omega C_2} \frac{h_{ie}}{h_{ie} + \frac{1}{j\omega C_1}}$$

Replacing $j\omega$ by s

$$I = \frac{-h_{fe} I_b}{s C_2} \frac{h_{ie}}{h_{ie} + \frac{1}{s C_1}}$$

$$I = \frac{-h_{fe} I_b}{s C_2} \frac{h_{ie}}{h_{ie} + \frac{1}{s C_1}}$$

$$\underline{I} = \frac{-hfe I_b}{sC_2}$$

$$\left(sL + \frac{1}{sC_2} \right) + \frac{hie}{hiesc_1 + 1}$$

$$= \frac{-hfe I_b / sC_2}{\left(\frac{s^2 LC_2 + 1}{sC_2} \right) + \frac{hie}{hiesc_1 + 1}}$$

$$= \frac{-hfe I_b (1 + hiesc_1)}{(s^2 LC_2 + 1)(hiesc_1 + 1) + hiesc_2}$$

$$= \frac{-hfe I_b (1 + sc_1 hie)}{1 + hiesc_1 + s^3 LC_1 C_2 hie + s^2 LC_2 + hiesc_2}$$

$$\underline{I} = \frac{-hfe I_b (1 + sc_1 hie)}{s^3 LC_1 C_2 hie + s^2 LC_2 + hies(c_1 + c_2) + 1} \quad \text{--- (1)}$$

$$I_b = \frac{I x c_1}{x c_1 + hie} = \frac{I / sc_1}{\frac{1}{sc_1} + hie}$$

$$= \frac{I / sc_1}{\frac{1 + sc_1 hie}{sc_1}}$$

$$I_b = \frac{I}{1 + sc_1 hie} \quad \text{--- (2)}$$

Sub ① in ②

$$I_b = -h_{fe} I_b (1 + sL_1 h_{ie})$$

$$\frac{I_b}{(1 + sL_1 h_{ie})} = \frac{s^3 L_1 C_2 h_{ie} + s^2 L C_2 + s h_{ie} (C_1 + C_2) + 1}{(1 + sL_1 h_{ie})}$$

$$\cancel{I_b} = -h_{fe} \cancel{I_b}$$

$$s^3 L_1 C_2 h_{ie} + s^2 L C_2 + s h_{ie} (C_1 + C_2) + 1$$

$$s^3 L_1 C_2 h_{ie} + s^2 L C_2 + h_{ie} s (C_1 + C_2) + 1 = -h_{fe}$$

$$-h_{fe} = -j\omega^3 L_1 C_2 h_{ie} - \omega^2 L C_2 + j\omega h_{ie} (C_1 + C_2) + 1$$

imaginary part will be zero

$$-j\omega^3 L_1 C_2 h_{ie} + j\omega h_{ie} (C_1 + C_2) = 0$$

$$-\omega^3 L_1 C_2 h_{ie} + \omega h_{ie} (C_1 + C_2) = 0$$

$$+\omega h_{ie} (-\omega^2 L_1 C_2 + C_1 + C_2) = 0$$

$$h_{ie} \neq 0$$

$$-\omega^2 L_1 C_2 \neq C_1 + C_2 = 0$$

$$C_1 + C_2 = \omega^2 L_1 C_2$$

$$\omega^2 = \frac{C_1 + C_2}{LC_1 C_2}$$

$$\omega^2 = \frac{1}{L \frac{C_1 C_2}{C_1 + C_2}} = \frac{1}{L C_{eq}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\omega = \frac{1}{\sqrt{L C_{eq}}}$$

$$2\pi f = \frac{1}{\sqrt{L C_{eq}}}$$

$$f = \frac{1}{2\pi \sqrt{L C_{eq}}}$$

For Real part

$$I = \frac{-V_{in}}{1 + s^2 L C_2}$$

$$I = \frac{-V_{in}}{1 - \omega^2 L C_2}$$

$$= \frac{-V_{in}}{1 - \frac{1}{K C_{eq}} K C_2}$$


$$= \frac{-V_{in}}{1 - \left(\frac{C_1 + C_2}{C_1 C_2}\right) C_2}$$

$$= \frac{-\omega f_e}{1 - 1 - \frac{C_2}{C_1}}$$

$$1 = \frac{\omega f_e}{\frac{C_2}{C_1}}$$



$$\boxed{\omega f_e = \frac{C_2}{C_1}}$$

Clap Oscillator

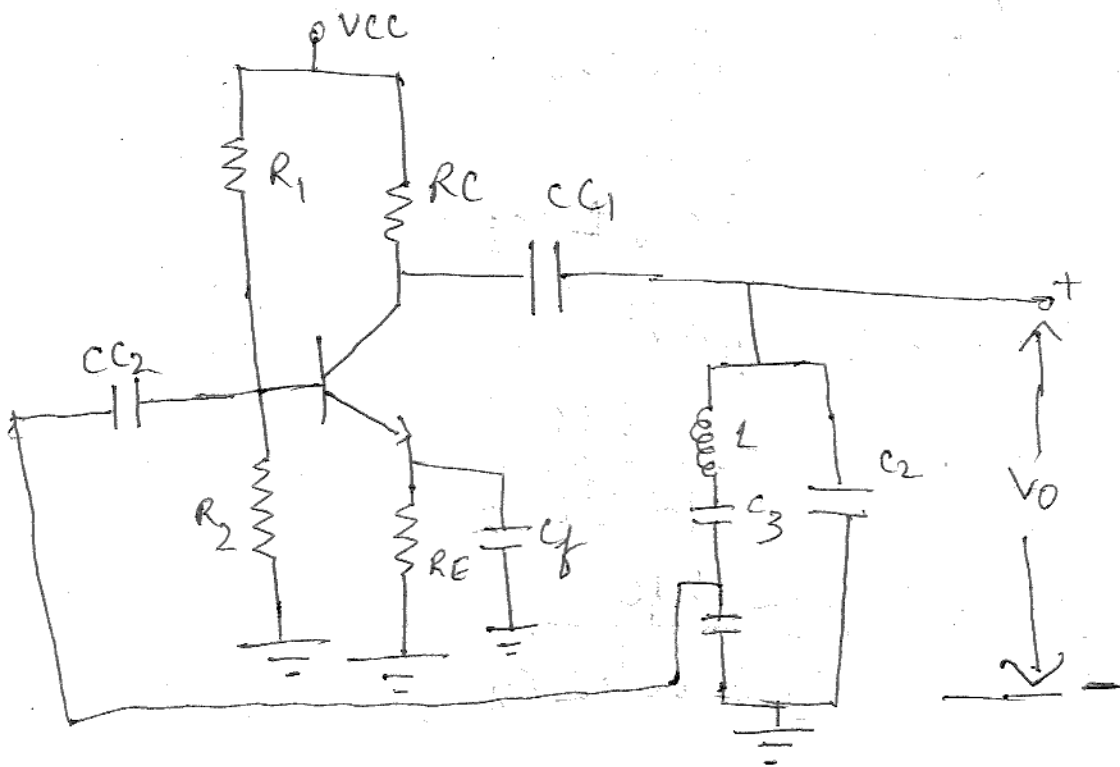

Derivation of frequency of oscillation

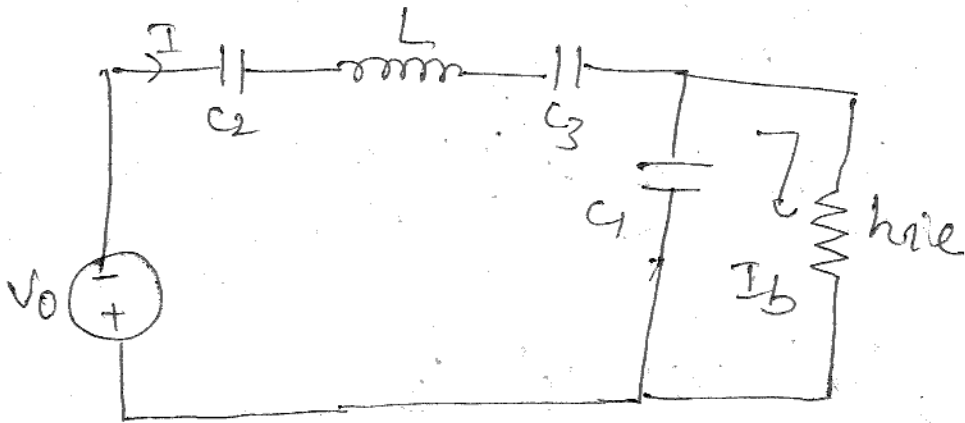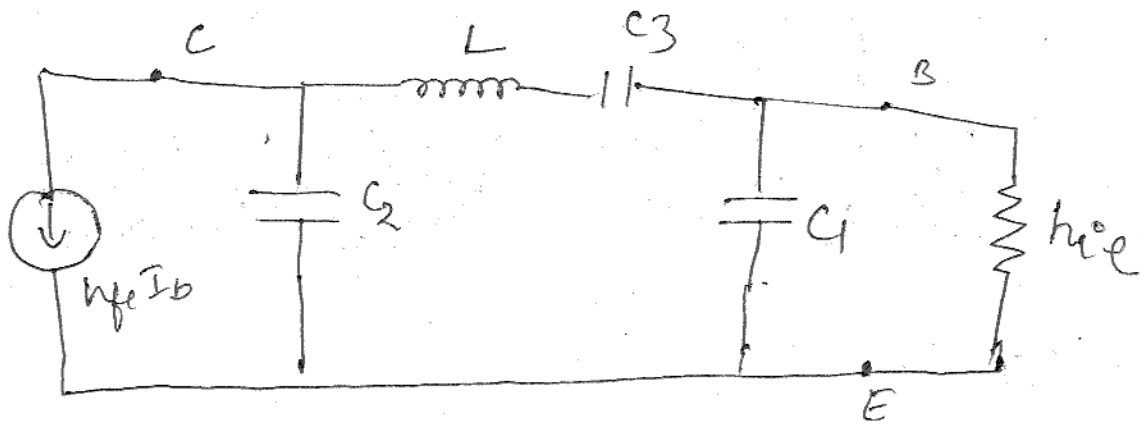Advantage of C_3 is that it can be kept variable, as frequency is dependent on C_3 , it can be varied at desired range.



$$V_0 = h_{fe} I_B \times X_{C_2} = h_{fe} I_B \frac{1}{j\omega C_2}$$

$$I = \frac{-V_0}{[X_{C_2} + X_L + X_{C_3}] + [X_{C_1} \parallel h_{ie}]}$$

$$X_{C_2} + X_L + X_{C_3} = \frac{1}{j\omega C_2} + \frac{1}{j\omega C_3} + j\omega L$$

$$X_{C_1} \parallel h_{ie} = \frac{1}{\frac{1}{j\omega C_1} + h_{ie}}$$

$$I = \frac{-h_{fe} I_B / j\omega C_2}{\left[\frac{1}{j\omega C_2} + \frac{1}{j\omega C_3} + j\omega L \right] + \left[\frac{h_{ie}}{1 + j\omega C_1 h_{ie}} \right]}$$

$$= \frac{-h_{fe} I_b}{}$$

$$\left[\frac{j\omega C_2}{j\omega C_2} + \frac{j\omega C_2}{j\omega C_3} + \frac{j\omega L_2}{j\omega C_2} \right] + \left[\frac{h_{fe} j\omega C_2}{1 + j\omega C_1 h_{ie}} \right]$$

Put $j\omega = s$

$$= \frac{-h_{fe} I_b}{}$$

$$\left[1 + \frac{C_2}{C_3} + s^2 L_2 C_2 \right] + \left[\frac{h_{fe} s C_2}{1 + s C_1 h_{ie}} \right]$$

$$= \frac{-h_{fe} I_b [1 + s C_1 h_{ie}] C_3}{}$$

$$(1 + s C_1 h_{ie}) [C_3 + C_2 + s^2 L_2 C_2 C_3] + (h_{fe} s C_2) C_3$$

$$= \frac{-h_{fe} I_b C_3 (1 + s C_1 h_{ie})}{}$$

$$C_3 + C_2 + s^2 L_2 C_2 C_3 + s C_1 C_3 h_{ie} + s C_1 C_2 h_{ie} + s^3 C_1 C_2 C_3 L_2 h_{ie} + h_{fe} s C_2 C_3$$

$$I_2 = \frac{-h_{fe} I_b C_3 (1 + s C_1 h_{ie})}{}$$

$$s^3 C_1 C_2 C_3 L_2 h_{ie} + s^2 L_2 C_2 C_3 + (C_1 C_3 h_{ie} + C_1 C_2 h_{ie} + C_3 h_{ie}) s + C_3 + C_2$$

$$I_b = \frac{I \times C_1}{X_{C_1} + h_{ie}} = \frac{I}{s C_1 + h_{ie}}$$

$$I_b = \frac{I}{1 + h_{fe} s C_1}$$

$$I_b = \frac{-h_{fe} I_b C_3 (1 + h_{fe} s C_1)}{[s^3 h_{fe} C_1 C_2 C_3 L + s^2 L C_2 C_3 + h_{fe} s (C_1 C_3 + C_1 C_2 + C_2 C_3) + (C_2 + C_3)] [1 + h_{fe} s C_1]}$$

$$I = \frac{-h_{fe} C_3}{[s^3 h_{fe} C_1 C_2 C_3 L + s^2 L C_2 C_3 + h_{fe} s (C_1 C_3 + C_1 C_2 + C_2 C_3) + (C_2 + C_3)]}$$

$$s^3 = -j\omega^3, \quad s^2 = -\omega^2, \quad s = j\omega$$

$$I = \frac{-h_{fe} C_3}{-j\omega^3 h_{fe} C_1 C_2 C_3 L + -\omega^2 L C_2 C_3 + h_{fe} j\omega (C_1 C_3 + C_1 C_2 + C_2 C_3) + (C_2 + C_3)}$$

Taking imaginary part as zero.

$$-\omega^3 h_{fe} C_1 C_2 C_3 L + h_{fe} j\omega (C_1 C_3 + C_1 C_2 + C_2 C_3) = 0$$

$$h_{fe} [-\omega^2 C_1 C_2 C_3 L + C_1 C_3 + C_1 C_2 + C_2 C_3] = 0$$

$$h_{fe} \neq 0$$

$$-\omega^2 C_1 C_2 C_3 L + C_1 C_3 + C_1 C_2 + C_2 C_3 = 0$$

$$C_1 C_3 + C_1 C_2 + C_2 C_3 = \omega^2 C_1 C_2 C_3 L$$

$$\omega^2 = \frac{C_1 C_3 + C_1 C_2 + C_2 C_3}{C_1 C_2 C_3 L}$$

$$\omega^2 = \frac{1}{LC_{eq}}$$

$$C_{eq} = \frac{C_1 C_2 C_3}{C_1 C_2 + C_2 C_3 + C_1 C_3}$$

$$\omega = \frac{1}{\sqrt{LC_{eq}}}$$


$$2\pi f = \frac{1}{\sqrt{LC_{eq}}}$$

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

This is the required frequency of Clap oscillator.

18/7/11

Negative Resistance oscillator

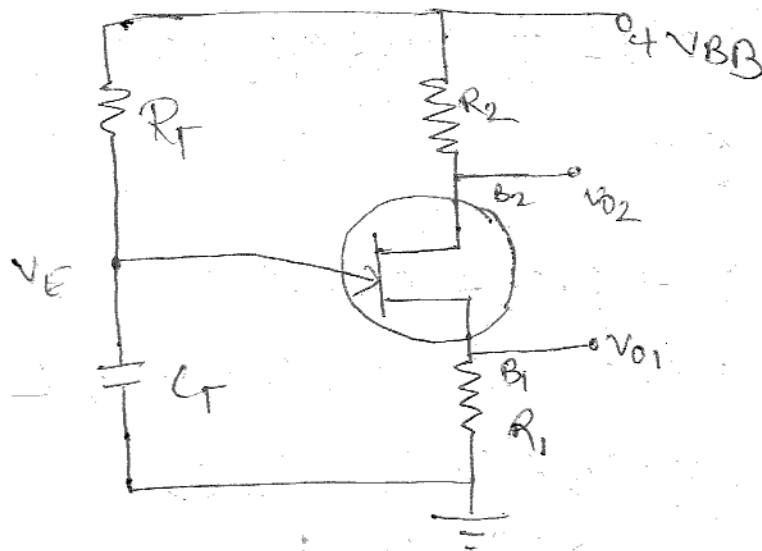

$$V_P = \eta V_{BB} + V_D$$

$\eta \rightarrow$ Stand-off ratio

$V_D \rightarrow$ cut-in voltage of diode.

$$V_{CC}(t) = V_v + V_{BB} [1 - e^{-t/R_T C_T}]$$

$$V_{CC}(t) = V_P \text{ at } t = T$$

$$V_P = V_v + V_{BB} [1 - e^{-T/R_T C_T}]$$

$$\eta (V_{BB} + V_D) = V_v + V_{BB} [1 - e^{-T/R_T C_T}]$$

$$\eta = [1 - e^{-T/R_T C_T}]$$


$$1 - \eta = e^{-T/R_T C_T}$$

$$\frac{-T}{R_T C_T} \ln e = \ln(1 - \eta)$$

$$\frac{T}{R_T C_T} = \frac{\ln\left(\frac{1}{1 - \eta}\right)}{\ln e}$$

$$T = R_T C_T \ln\left(\frac{1}{1 - \eta}\right)$$
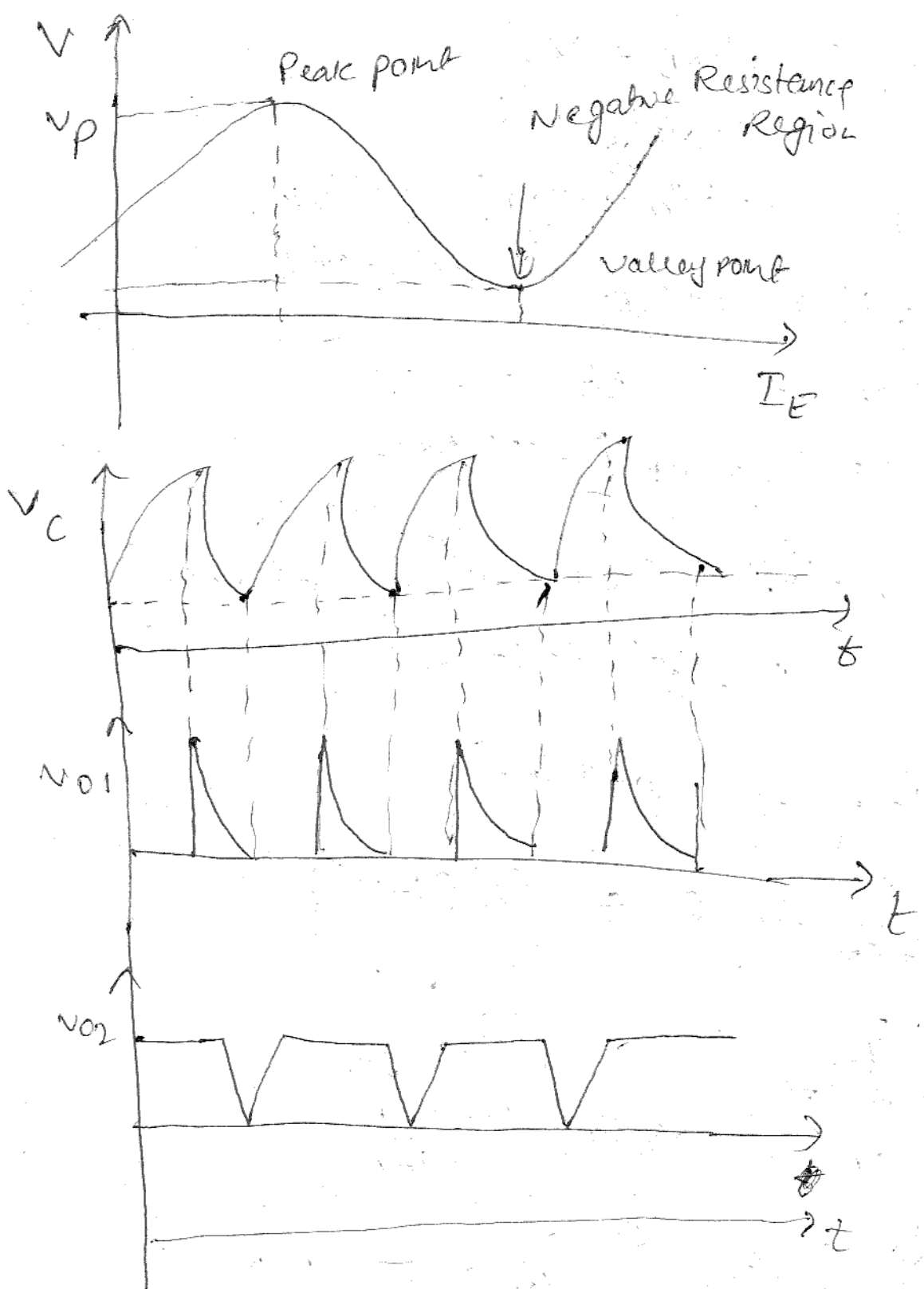
$$f_0 = \frac{1}{T} = \frac{1}{R_T C_T \ln\left(\frac{1}{1 - \eta}\right)}$$



Q. In a certain oscillator circuit the gain of the amplifier is $A = \frac{-16 \times 10^6}{j\omega}$ and the feedback factor of the feedback

Now is $\beta = \frac{10^3}{[2 \times 10^3 + j\omega]^2}$ verify the Book

Use the criterion for the Sustained Oscillation
Also find the frequency at which circuit will oscillate.

Solⁿ

$$A\beta = \frac{-16 \times 10^6 \cdot 10^3}{j\omega [2 \times 10^3 + j\omega]^2}$$

$$= \frac{-16 \times 10^9}{j\omega [4 \times 10^6 + j^2 \omega^2 + 4 \times 10^3 j\omega]}$$

$$= \frac{-16 \times 10^9}{4 \times 10^6 j\omega + j^3 \omega^3 + 4 \times 10^3 j^2 \omega^2}$$

$$A\beta = \frac{-16 \times 10^9}{4 \times 10^6 j\omega - j\omega^3 - 4 \times 10^3 \omega^2}$$

Now equating imaginary part to zero

$$4 \times 10^6 j\omega - j\omega^3 = 0$$

$$j\omega (4 \times 10^6 - \omega^2) = 0$$

$$4 \times 10^6 \omega = \omega^3$$

$$\omega^2 = 4 \times 10^6$$

$$\omega = 2 \times 10^3$$

ω

$$\begin{aligned}
 A\beta &= \frac{-16 \times 10^9}{4 \times 10^6 \times 2 \times 10^3 j - j(2 \times 10^3)^3 - 4 \times 10^3 \omega^2} \\
 &= \frac{-16 \times 10^9}{8 \times 10^9 j - 8 \times 10^9 j - 4 \times 10^3 \times (2 \times 10^3)^2} \\
 &= \frac{-16 \times 10^9}{8 \times 10^6 - 4 \times 4 \times 10^3 \times 10^6} \\
 &= \frac{-16 \times 10^9}{-16 \times 10^9}
 \end{aligned}$$

$$A\beta = 1$$

Barkhausen criterion satisfied