
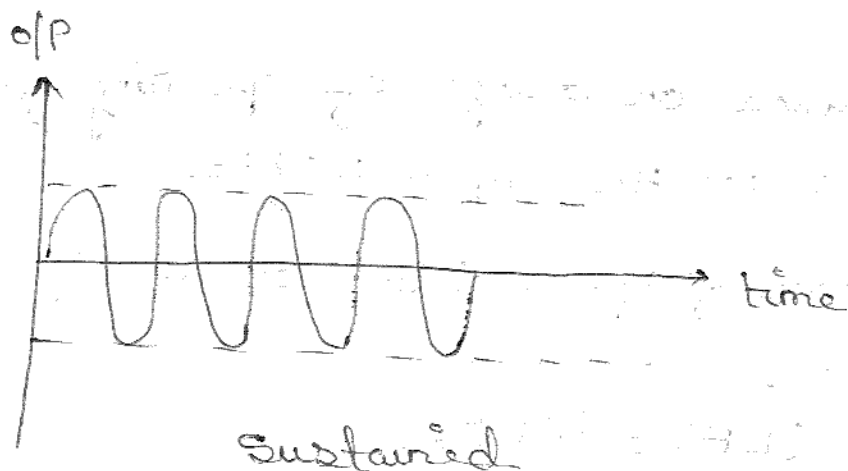
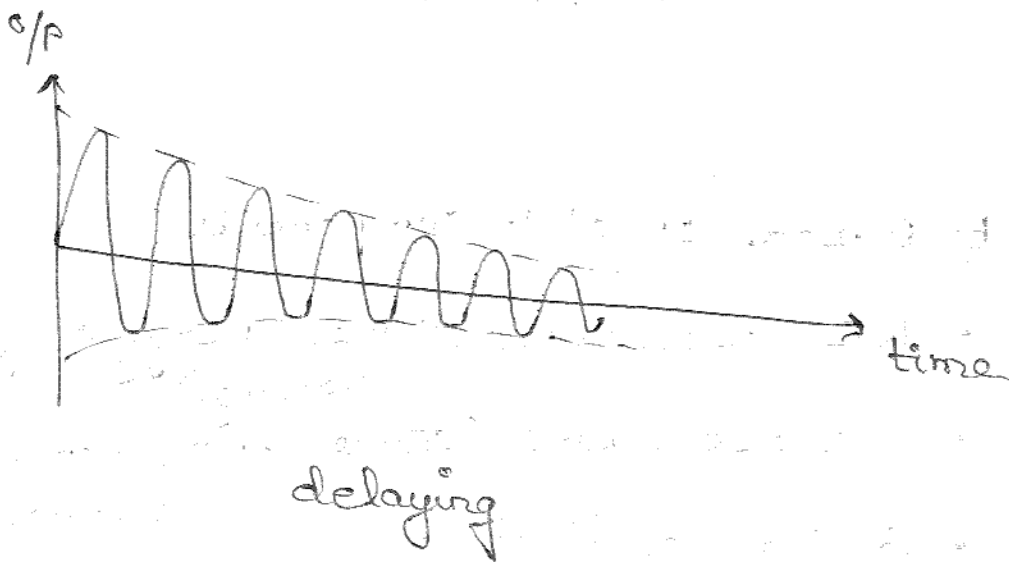


11.7.11

### \* Oscillators

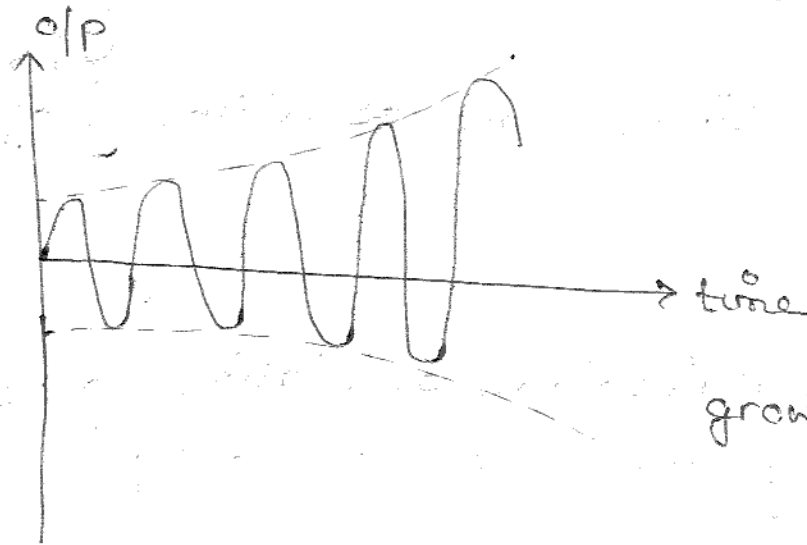

## → Classification of oscillators

- Sinusoidal oscillators
  - Non-sinusoidal oscillators
- } based on O/P wave.

→ The sinusoidal oscillators generates purely sine wave at the o/p.

→ Non-sinusoidal oscillators generates saw-tooth, triangular.

### b) Based on ckt components

- RC oscillators (stores energy in form of voltage)
- LC oscillators (stores energy in form of current)
- Crystal oscillators

### c) Based on range of operating freq.

- (20-100)Hz upto 20KHz

audio freq. oscillator or low freq. osci.

(LF) oscillator

- (200 to 300) Hz to GHz

High freq or Radio freq (RF) oscillators


d) Based on feedback

- Non-feedback oscillator -


which uses -ve resistance region of characteristic of device (UJT relaxation osci).

12.7.11

- RC phase shift oscillator

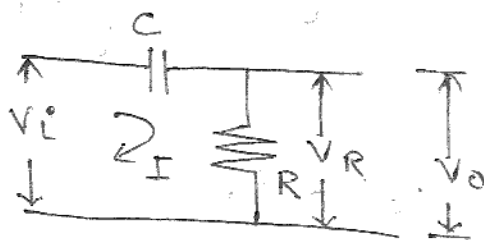

ckt

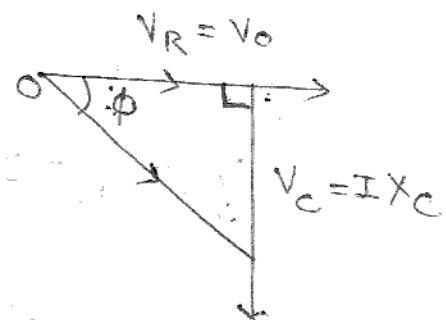

phasor diagram

~~Basically the ckt consist of~~

capacitor C and R is connected in series and

$$X_C = \frac{1}{2\pi f C}$$

$$\text{Total impedance} = R - jX_C$$

$$= R - j \left( \frac{1}{2\pi f c} \right) \Omega$$

$$= |Z| \angle -\phi^\circ \Omega$$

$$\text{Current } I = \frac{V_i \angle 0^\circ}{|Z| \angle -\phi^\circ} = \frac{V_i \angle \phi_i}{|Z| \angle -\phi_i}$$

where,

$$|Z| = \sqrt{R^2 + (X_c)^2}$$


$$\phi = \tan^{-1} \left( \frac{X_c}{R} \right)$$

$I$  leads input voltage  $V_i$  by angle  $\phi$


$$V_o = V_R = IR \quad ; \quad V_c = IX_c$$

$V_R$  is in phase with  $I$  i.e. current while drop  $V_c$  lags current  $I$  by  $90^\circ$  ( $I_c$  leads  $V_c$  by  $90^\circ$ ).

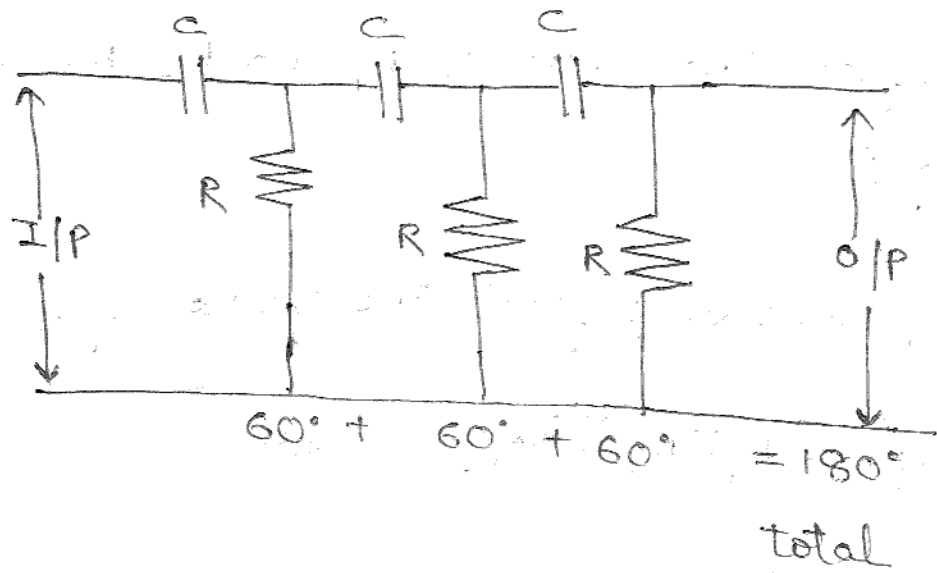By using proper values of  $R$  and  $c$  the  $\angle \phi$  is adjusted in practice equal to  $60^\circ$



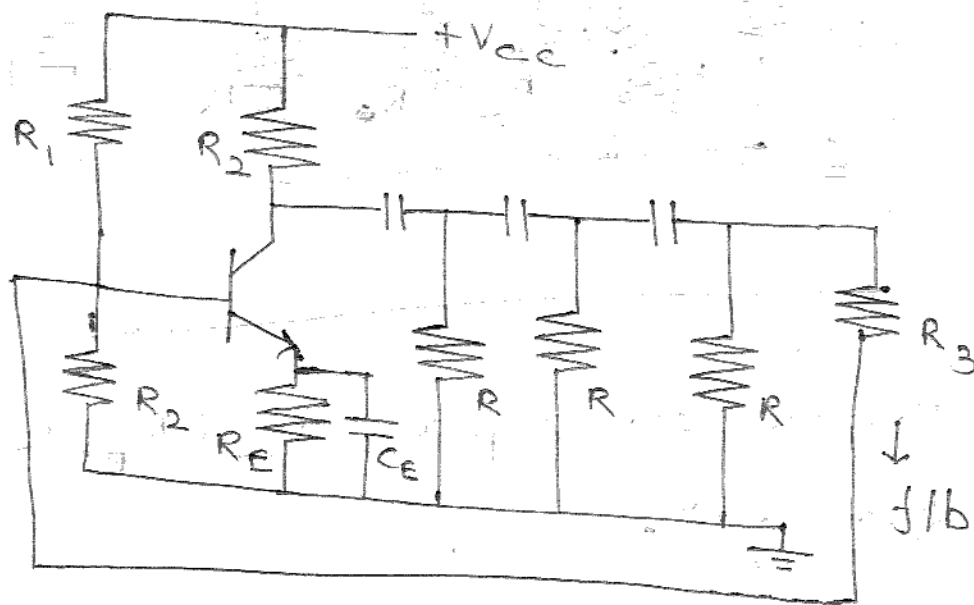- Transistorised RC phase shift oscillator



The o/p of a f/b n/w gets loaded due to the low i/p impedance ( $h_{ie}$ ) of a transistor.

$$R = h_{ie} + R_3 \quad \text{--- (1)}$$


Neglect the value of  $R_1$  and  $R_2$  we get eq (1)

If we not neglect the value of  $R_1, R_2$

$$R_L' = R_1 \parallel R_2 \parallel h_{ie} \quad \text{--- (1a)}$$

$$R_L' + R_3 = R \quad \text{--- (1b)}$$


# Derivation of freq of oscillation

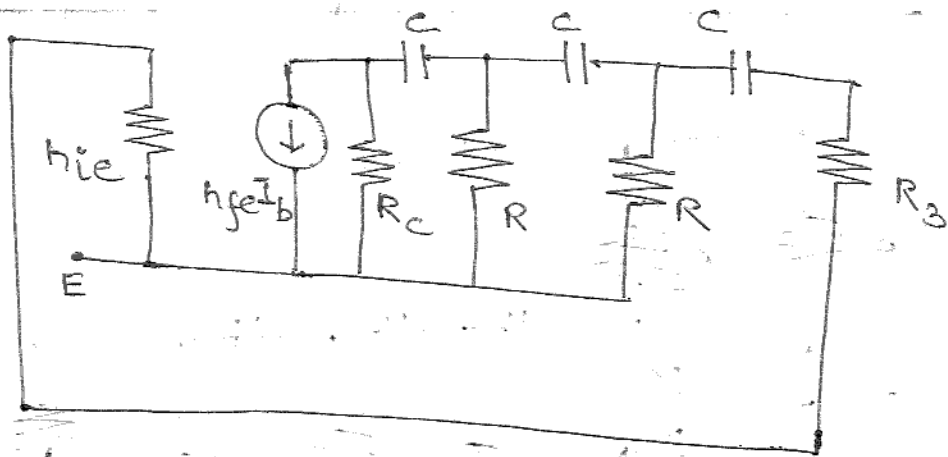

Now we can replace  $h_{ie} + R_E$  as  $R$  from eq (1).

Similarly we can replace the current source  $h_{fe} I_b$  by its equivalent voltage source

$$K = \frac{R_c}{R}$$

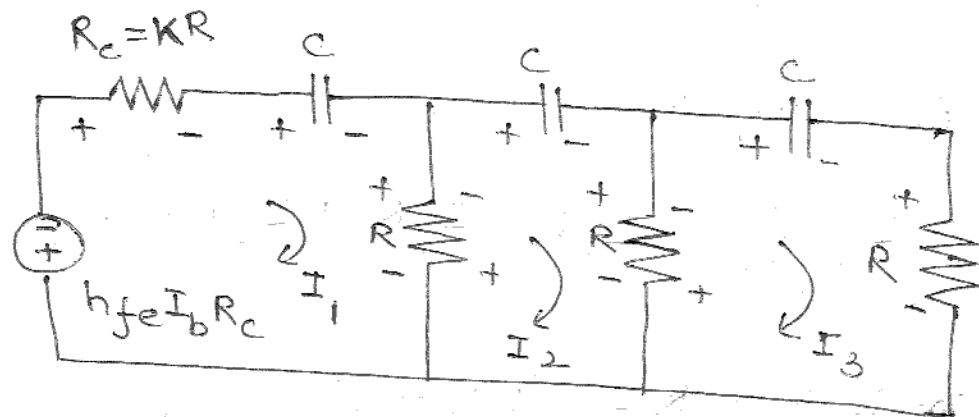

by applying KVL to loop 1

$$-I_1 R_c - I_1 \frac{1}{j\omega C} - I_1 R - h_{fe} I_b R_c = 0$$

$$+ I_2 R$$

Replace  $R_c$  by  $KR$  and  $j\omega$  by  $s$

$$-I_1 KR - I_1 \frac{1}{sC} + I_1 R - h_{fe} I_b KR = 0$$

$$+ I_2 R$$

$$I_1 \left[ (K+1)R + \frac{1}{sC} \right] - I_2 R = -h_{fe} I_b KR \quad \text{--- (2)}$$

for loop 2

$$-\frac{1}{j\omega C} I_2 - I_2 R - I_2 R + I_1 R + I_3 R = 0$$

$$-\frac{1}{sC} I_2 - I_2 R - I_2 R + I_1 R + I_3 R = 0$$

$$-I_2 \left( \frac{1}{sC} + R + R \right) + I_1 R + I_3 R = 0$$

$$I_1 R + I_2 \left[ \frac{1}{sC} + 2R \right] - I_3 R = 0 \quad \text{--- (3)}$$

13.7.11

For loop 3

$$-I_3 \frac{1}{j\omega C} - I_3 R - I_3 R + I_2 R = 0$$

$$-I_2 R + I_3 \left[ 2R + \frac{1}{sC} \right] = 0 \quad \text{--- (4)}$$

using cramer's rule we can solve for  $I_3$

$$\begin{vmatrix} (k+1)R + \frac{1}{sC} & -R & 0 \\ R & \frac{1}{sC} + 2R & -R \\ 0 & -R & 2R + \frac{1}{sC} \end{vmatrix}$$

$$D = (k+1)R + \frac{1}{sC} \left\{ \left( \frac{1}{sC} + 2R \right) \left( 2R + \frac{1}{sC} \right) - R^2 \right\}$$

$$+ R \left\{ (R) \left( 2R + \frac{1}{sC} \right) - 0 \right\}$$

$$D = (k+1)R + \frac{1}{sC} \left\{ \frac{1}{s^2 C^2} + 2 \times 2R \times \frac{1}{sC} + 4R^2 - R^2 \right\}$$

$$+ R \left\{ 2R^2 + \frac{R}{sC} \right\}$$

$$= kR + R + \frac{1}{sC} \left\{ \frac{1}{s^2 C^2} + \frac{4R}{sC} + 3R^2 \right\}$$



$$+ 2R^3 + \frac{R^2}{SC}$$

$$D = \frac{KR}{S^2C^2} + \frac{4KR^2}{SC} + \frac{3R^2}{1} + \frac{R}{S^2C^2} + \frac{4R^2}{SC} \\ + 3R^3 + \frac{1}{S^3C^3} + \frac{4R}{S^2C^2} + \frac{3R^2}{SC} + 2R^3 + \frac{R^2}{SC}$$

$$D = \frac{R}{S^2C^2} [K+1+4] + \frac{R^2}{SC} [4K+4+4]$$

$$+ \frac{1}{S^3C^3} + 3R^2 + 5R^3$$

$$= \frac{R}{S^2C^2} [K+5] + \frac{R^2}{SC} [4K+8] + \frac{1}{S^3C^3}$$

$$+ 3R^2 + 5R^3$$

$$= \frac{RK+5R}{S^2C^2} + \frac{4KR^2+8R^2}{SC} + \frac{1}{S^3C^3} + 3R^2$$

$$+ 5R^3$$

$$= \frac{S^3C^3R^3[3K+1] + S^2C^2R^2[4K+6] + SRC[5+K]}{S^3C^3}$$

(5)

$$\Delta_3 = \begin{vmatrix} (k+1)R + \frac{1}{sC} & -R & -h_{fe} I_b KR \\ R & \frac{1}{sC} + 2R & 0 \\ 0 & -R & 0 \end{vmatrix}$$

$$\Delta_3 = (k+1)R + \frac{1}{sC} \{0\} + R \{0\} \\ - h_{fe} I_b KR \{-R^2 - 0\}$$

$$= -h_{fe} I_b KR^3 \quad \text{--- (6)}$$

$$\Delta_2 = \begin{vmatrix} (k+1)R + \frac{1}{sC} & -h_{fe} I_b KR & 0 \\ R & 0 & -R \\ 0 & 0 & 2R + \frac{1}{sC} \end{vmatrix}$$

$$= (k+1)R + \frac{1}{sC} \times 0 - \{-h_{fe} I_b KR\} \left\{ R \left( 2R + \frac{1}{sC} \right) \right. \\ \left. - 0 \right\}$$

$$= h_{fe} I_b KR \left\{ 2R^2 + \frac{R}{sC} \right\}$$

$$= 2h_{fe} I_b KR^3 + \frac{h_{fe} I_b KR^2}{sC}$$

$$D_2 = \frac{2h_{fe}I_b KR^3 SC + h_{fe}I_b KR^2}{SC}$$

$$D_2 = \frac{h_{fe}I_b KR^2 [2SCR + 1]}{SC}$$

$$D_1 = \begin{bmatrix} -h_{fe}I_b KR & -R & 0 \\ 0 & \frac{1}{SC} + 2R & -R \\ 0 & -R & 2R + \frac{1}{SC} \end{bmatrix}$$

$$= -h_{fe}I_b KR \left\{ \left( \frac{1}{SC + 2R} \right)^2 - R^2 \right\}$$

$$+ R \{ 0 - 0 \}$$

$$= -h_{fe}I_b KR \left\{ \frac{1}{SC^2 + 4RSC + 4R^2} - R^2 \right\}$$

$$= -h_{fe}I_b KR \left\{ \frac{1 - R^2 \{ SC^2 + 4RSC + 4R^2 \}}{SC^2 + 4RSC + 4R^2} \right\}$$

$$= -h_{fe}I_b KR \left\{ \frac{1 - SC^2 R^2 - 4R^3 SC - 4R^4}{SC^2 + 4RSC + 4R^2} \right\}$$

15.7.11

$$I_3 = \frac{-KR^3 h_{fe} I_b s^3 c^3}{s^3 c^3 R^3 [3K+1] + s^2 c^2 R^2 [4K+6] + s c R [5K+1] + 1}$$

→ (7)

Here,

$I_3$  = o/p current of f/b ckt

$I_b$  = I/P current of amp

$I_c = h_{fe} \cdot I_b$  = I/P current of f/b ckt

$$\beta = \frac{\text{o/p f/b ckt}}{\text{I/P f/b ckt}}$$

$$A = \frac{\text{o/p of amp ckt}}{\text{I/P of amp ckt}}$$

$$A\beta = \frac{I_3}{h_{fe} I_b} \times \frac{h_{fe}}{1} = \frac{I_3}{I_b} \quad \text{--- (8)}$$

using eqn (8)

$$A\beta = \frac{-KR^3 h_{fe} s^3 c^3}{s^3 c^3 R^3 [3K+1] + s^2 c^2 R^2 [4K+6] + s c R [5K+1] + 1}$$

→ (9)

Subst  $s = j\omega$  and  $s^2 = -\omega^2$ ;  $s^3 = -j\omega^3$   
 in eq (9)

$$A\beta = \frac{-KR^3 h_{fe} (-j\omega^3) C^3}{(-j\omega^3) C^3 R^3 [3K+1] + (-\omega^2) C^2 R^2 [4K+6] + (j\omega) CR [5K+1] + 1}$$

$$A\beta = \frac{KR^3 h_{fe} j\omega^3 C^3}{-j\omega^3 C^3 R^3 (3K+1) - \omega^2 C^2 R^2 (4K+6) + j\omega CR(5K+1) + 1}$$

Separate real and imaginary part

$$A\beta = \frac{-j\omega^3 R^3 C^3 h_{fe} K}{[1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2] - j\omega [3K\omega^2 R^2 C^3 + \omega^2 R^3 C^3 - 5RC - KRC]}$$

Dividing num and deno. by  $-j\omega^3 C^3 R^3$

$$A\beta = \frac{Kh_{fe}}{\left[ \frac{1 - 4K\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2}{-j\omega^3 R^3 C^3} \right] - \left[ \frac{j\omega [3K\omega^2 R^2 C^3 + \omega^2 R^3 C^3 - 5RC - KRC]}{-j\omega^3 R^3 C^3} \right]}$$

Replacing  $-\frac{1}{j} = j$  in above equation

$$A\beta = \frac{khfe}{j \left\{ \frac{1}{\omega^3 R^3 C^3} - \frac{4K}{\omega RC} - \frac{6}{\omega RC} \right\} + \left\{ (3K+1) - \frac{5}{\omega^2 R^2 C^2} - \frac{K}{\omega^2 R^2 C^2} \right\}}$$

Replacing  $\frac{1}{\omega RC} = \alpha$  for simplification

$$A\beta = \frac{khfe}{[3K+1-5\alpha^2-K\alpha^2] + j[\alpha^3-4K\alpha-6\alpha]} \quad \text{--- (10)}$$

As per Barkhausen criterion  $\angle A\beta = 0^\circ$

$$\alpha^3 - 4K\alpha - 6\alpha = 0$$

$$\alpha(\alpha^2 - 4K - 6) = 0$$

$$\alpha^2 = 4K + 6$$

$$\alpha = \sqrt{4K + 6}$$

$$\alpha = \frac{1}{\omega RC} ; \omega = \frac{1}{RC\sqrt{4K+6}}$$

$$\omega = \frac{1}{2\pi f} ; f = \frac{1}{2\pi\sqrt{4K+6}} \quad \text{--- (11)}$$

Here,  $f$  = freq. of oscillation at which  $\angle A\beta = 0^\circ$


and

$$|A\beta| = 1$$
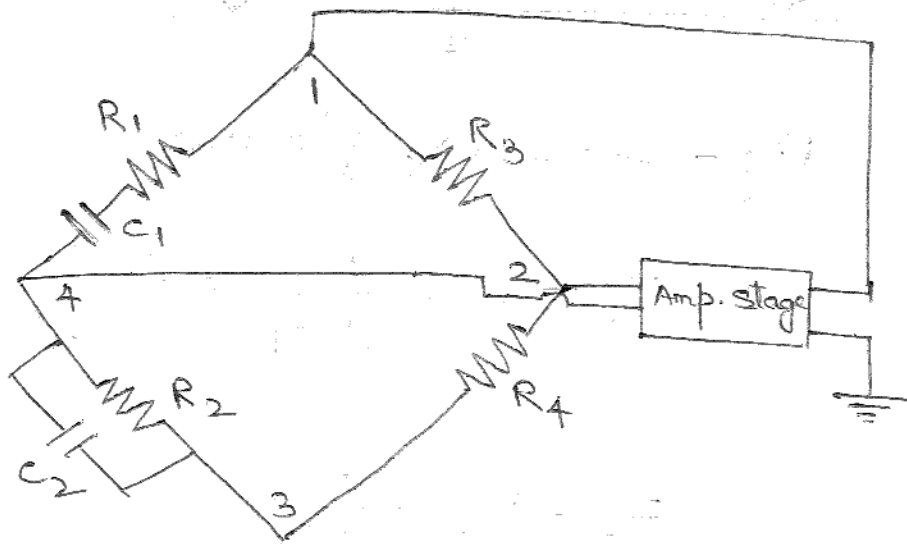
## # Wein Bridge Oscillator

→ Generally in an oscillator amplifier stage introduces  $180^\circ$  phase shift and f/b introduces additional  $180^\circ$  to obtain phase shift of  $360^\circ$ .

→ The Wein bridge oscillator uses a non-inverting amp and hence does not provide any phase shift during the amplifier stage.



I lead by  $V$   $90^\circ$

I lag by  $V$

The output of amplifier is applied b/w the terminal 1 and 3 which is the i/p to the feedback network. while the i/p is supplied from diagonal terminal 2 and 4 which the o/p is from feedback.

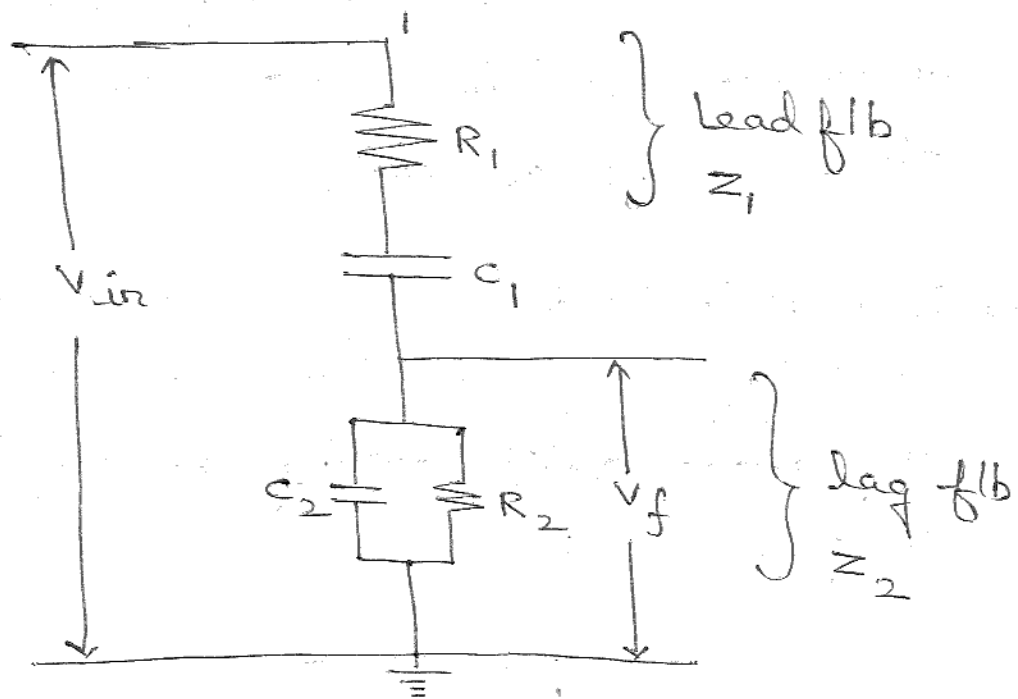


Fig - Lead-lag flb ckt

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + R_1 j\omega C_1}{j\omega C_1}$$


$$Z_2 = R_2 \parallel \frac{1}{j\omega C_2}$$

$$= \frac{R_2 / j\omega C_2}{R_2 j\omega C_2 + 1} = \frac{R_2}{1 + j\omega R_2 C_2} \quad \text{--- (1)}$$


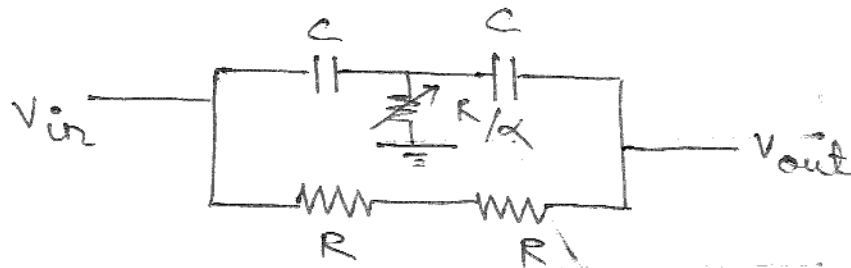
## # Twin T-oscillator

- RC n/w or RC oscillator
- $-90^\circ$  to  $90^\circ$





$$f = f_r$$

- The twin T oscillator is basically lead-lag circuit whose phase angle varies b/w  $+90^\circ$  to  $-90^\circ$ .
- At  $f = f_r$ , its phase angle is  $0^\circ$  and it does not introduce any phase shift.
- Equation for its resonating freq. is same as that of Wien bridge ckt.

$$f_r = \frac{1}{2\pi RC}$$

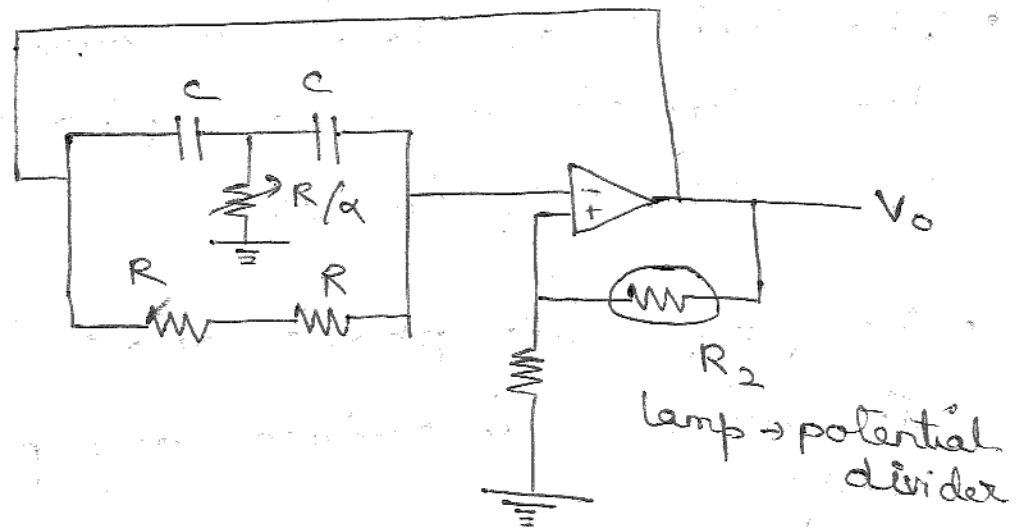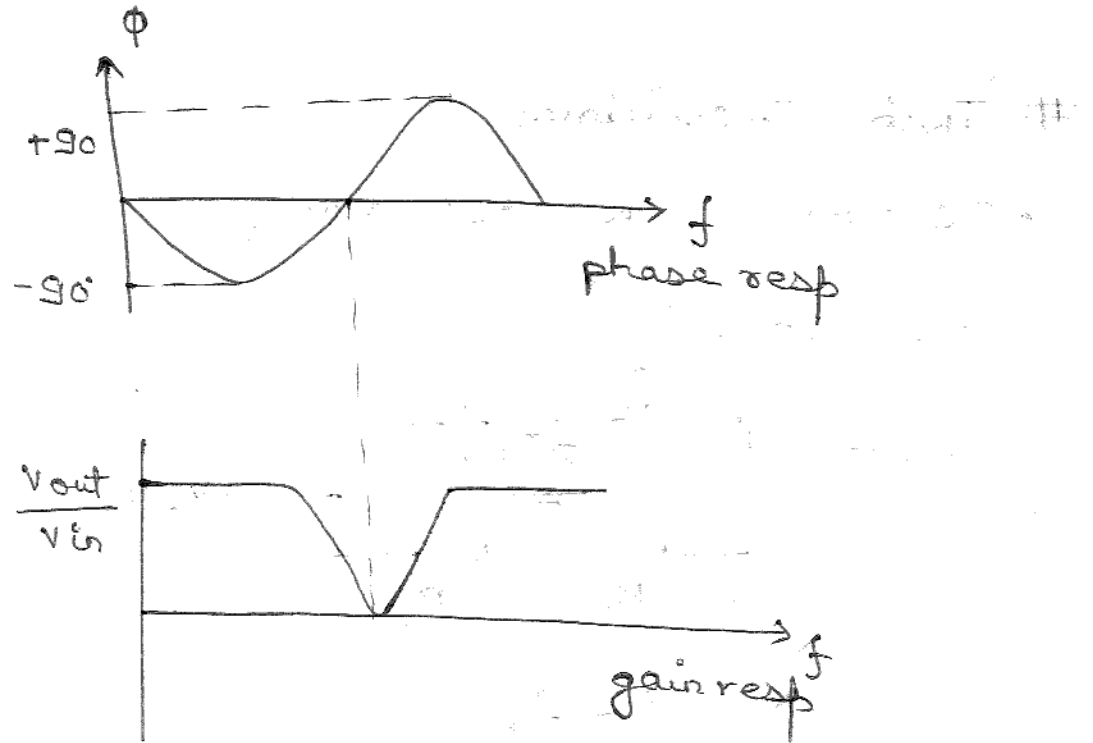- Twin-T filter is a combination of low pass and high pass filter.



- The -ve f/b to the inverting iff is given through Twin-T filter
- $R_2$  of the potential divider is lamp.
- -ve f/b is given through Twin-T filter.

• When power is given to the circuit lamp resistance  $R_2$  will be low and the feedback of the circuit will be max. (Act as a osc).

• The oscillation growing on  $R_2$  will be increased and the feedback will decrease.

• Oscillation freq. near the Notch freq  $\frac{R}{2}$  of the twin T filter is kept variable.

• Only at  $f_0$ , the -ve f/b is negligible and +ve f/b through  $R_1$  and  $R_2$  allows the circuit to oscillate.

• The oscillator is rarely used compared to RC and Wein bridge because it operates only at one frequency.

## # LC oscillator

Two types

- Hartley osc.
- Colpitts osc.


→ 'L' and 'C' as components

→ It is also called tank circuit

→ It is 20 KHz to few GHz

→ RF oscillator ckt (radio freq).

- LC tank circuit

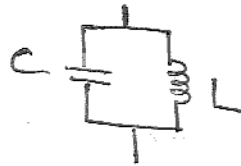


LC tank circuit used along with transistor amplifier can be used to obtain oscillators called LC oscillators. Due to the supply of energy which is lost oscillation get maintain hence called sustained oscillation or undamped oscillation.

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

Based on reactances  $X_1$ ,  $X_2$  and  $X_3$

	$X_1$	$X_2$	$X_3$
Hartley osci	L	L	C
Colpitt osci	C	C	L

→ Hartley oscillator

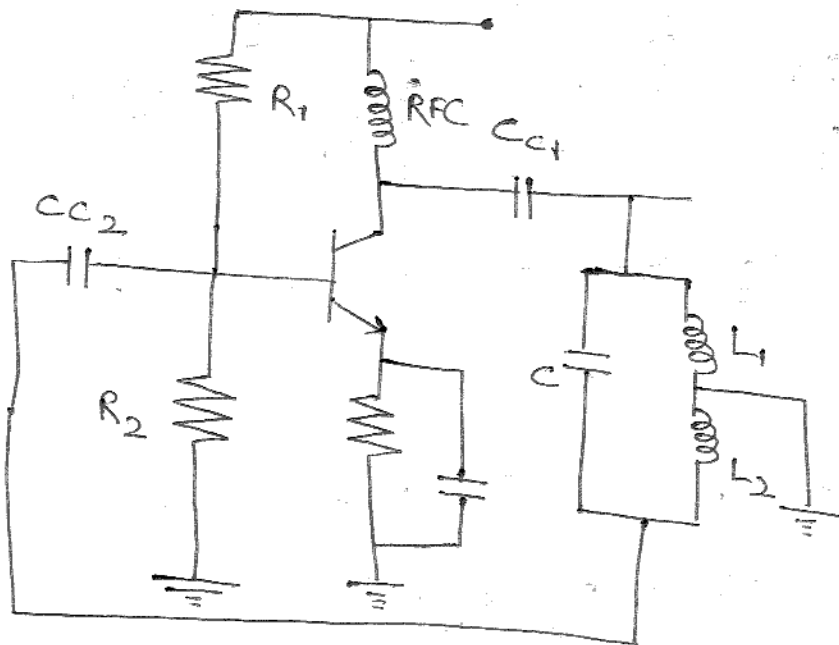


- RFC is the radio freq choke its reactance value is very high for high frequency (open ckt) while for dc condition tends to zero reactance.
- Due to RFC the isolation between AC and DC operation is achieved.

- LC rfn gives the phase shift of  $180^\circ$   
CE amp provides addition  $180^\circ$ .

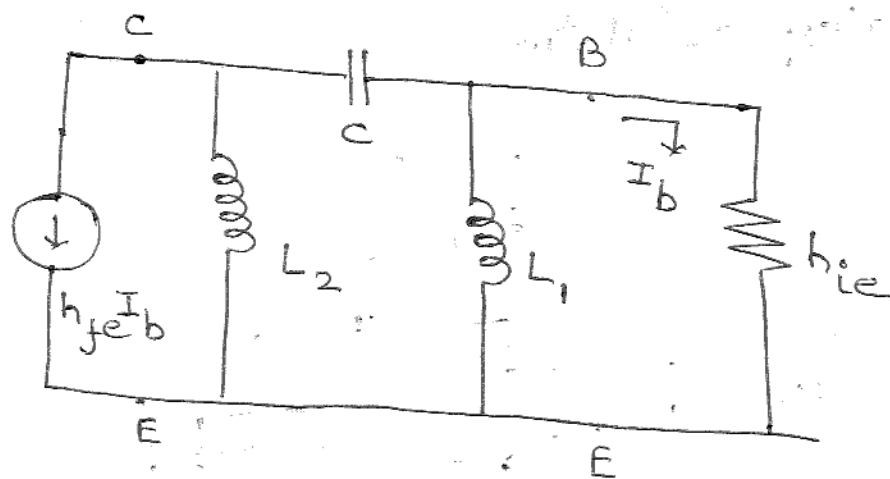
20.7.11

\* Derivation for Freq of osc of Hartley Osc



- The op current which is the collector current is  $h_{fe} I_b$ .
- Capacitor  $C$  is b/w base and collector and inductor  $L_1$  is b/w base and emitter while the inductor  $L_2$  is b/w collector to emitter.

equivalent ckt of the above figure

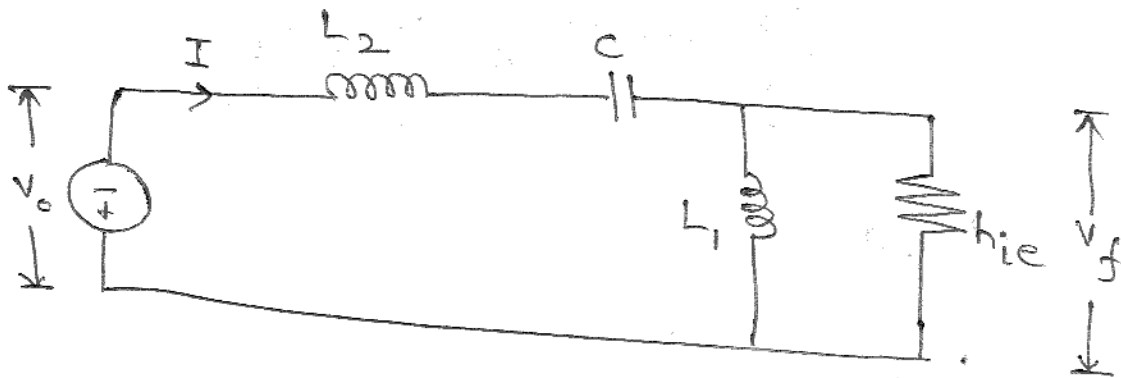

$$V_o = h_{fe} I_b \cdot X_{L_2} = h_{fe} I_b j\omega L_2 \quad \text{--- (1)}$$

Now  $L_1$  and  $h_{ie}$  are connected in parallel.  
So, the total current  $I$  is drawn from the supply is

$$I = \frac{-V_o}{[X_{L_2} + X_C] + [X_{L_1} \parallel h_{ie}]} \quad \text{--- (2)}$$

$$X_{L_2} + X_C = j\omega L_2 + \frac{1}{j\omega C}$$

$$X_{L_1} \parallel h_{ie} = j\omega L_1 \parallel h_{ie}$$

$$= \frac{j\omega L_1 h_{ie}}{j\omega L_1 + h_{ie}}$$

Subst in eq (2) we get

$$I = \frac{-V_o}{\frac{j\omega^2 L_2 C + 1}{j\omega C} + \frac{j\omega L_1 h_{ie}}{j\omega L_1 + h_{ie}}}$$

Replace  $j\omega$  by 's'

$$I = \frac{-V_o}{\frac{s^2 L_2 C + 1}{sC} + \frac{sL_1 h_{ie}}{sL_1 + h_{ie}}}$$

$$I = \frac{-h_{fe} I_b s L_2}{\frac{(s^2 L_2 C + 1)(sL_1 + h_{ie}) + (sL_1 h_{ie} sC)}{sC(sL_1 + h_{ie})}}$$

$$I = \frac{-(h_{fe} I_b s L_2)(s^2 C L_1 + s C h_{ie})}{(s^2 L_2 C + 1)(sL_1 + h_{ie}) + s^2 L_1 C h_{ie}}$$

$$I = \frac{-h_{fe} I_b s^3 L_1 L_2 C - h_{fe} I_b s^2 L_2 C h_{ie}}{s^3 L_2 C L_1 + s^2 L_2 C h_{ie} + sL_1 + h_{ie} + s^2 L_1 C h_{ie}}$$

$$I = \frac{-s^2 h_{fe} I_b L_2 C (sL_1 + h_{ie})}{s^3 L_1 L_2 C + s^2 C h_{ie} (L_1 + L_2) + sL_1 + h_{ie}}$$

— (3)



A/c to current division in parallel ckt

$$I_b = ?$$

$$I_b = I \times \frac{X_{L_1}}{X_{L_1} + h_{ie}}$$

$$= I \times \frac{j\omega L_1}{j\omega L_1 + h_{ie}}$$

$$I_b = I \times \frac{sL_1}{sL_1 + h_{ie}} \quad \text{--- (4)}$$

subt (3) in (4)

$$I_b = \frac{-s^2 h_{fe} I_b L_2 C (sL_1 + h_{ie}) sL_1}{[s^3 L_1 L_2 C + s^2 C h_{ie} (L_1 + L_2) + sL_1 + h_{ie}] [sL_1 + h_{ie}]}$$

$$\frac{I_b}{I_b} = \frac{-s^3 h_{fe} L_1 L_2 C (sL_1 + h_{ie})}{s^3 L_1 L_2 C + s^2 C h_{ie} (L_1 + L_2) + sL_1 + h_{ie}}$$

$$1 = \frac{-s^3 h_{fe} C L_1 L_2}{s^3 L_1 L_2 C + s^2 C h_{ie} (L_1 + L_2) + sL_1 + h_{ie}}$$

--- (5)

$$\text{sub } s = j\omega, s^2 = -\omega^2, s^3 = -j\omega^3 \text{ in eq (5)}$$

$$I = \frac{j\omega^3 h_{fe} C L_1 L_2}{-j\omega^3 L_1 L_2 C - \omega^2 h_{ie} (L_1 + L_2) + j\omega L_1 + h_{ie}} \quad \text{--- (6)}$$

$$I = \frac{j\omega^3 h_{fe} C L_1 L_2}{[h_{ie} - \omega^2 h_{ie} (L_1 + L_2)] + j\omega L_1 (1 - \omega^2 L_2 C)} \quad \text{--- (6)}$$

Rationalising the RHS of above eq (6)

$$I = \frac{j\omega^3 h_{fe} C L_1 L_2}{[h_{ie} - \omega^2 h_{ie} (L_1 + L_2)] + j\omega L_1 (1 - \omega^2 L_2 C)} \times \frac{[h_{ie} - \omega^2 h_{ie} (L_1 + L_2)] - j\omega L_1 (1 - \omega^2 L_2 C)}{[h_{ie} - \omega^2 h_{ie} (L_1 + L_2)] - j\omega L_1 (1 - \omega^2 L_2 C)}$$

$$I = \frac{j\omega^3 h_{fe} C L_1 L_2 [h_{ie} - \omega^2 h_{ie} (L_1 + L_2)] \frac{\omega^4 h_{fe} C^2 L_1 L_2}{(1 - \omega^2 L_2 C)^2}}{\{h_{ie} - \omega^2 h_{ie} (L_1 + L_2)\} + \omega^2 L_1^2 (1 - \omega^2 L_2 C)^2} \quad \text{--- (7)}$$

5) To satisfy this eq, the imaginary part of

$$\text{RHS} = 0$$

$$\omega^2 h_{fe} L_1 L_2 C [h_{ie} e^{-\omega^2 h_{ie} C (L_1 + L_2)}] = 0$$

$$\omega^2 h_{fe} L_1 L_2 [1 - \omega^2 C (L_1 + L_2)] = 0$$

$$1 - \omega^2 C (L_1 + L_2) = 0$$

$$\omega^2 = \frac{1}{C(L_1 + L_2)}$$

$$4\pi^2 f^2 = \frac{1}{C(L_1 + L_2)}$$


$$f^2 = \frac{1}{4\pi^2 C(L_1 + L_2)}$$

$$f = \frac{1}{2\pi \sqrt{(L_1 + L_2) C}}$$

22.07.11  
cssss

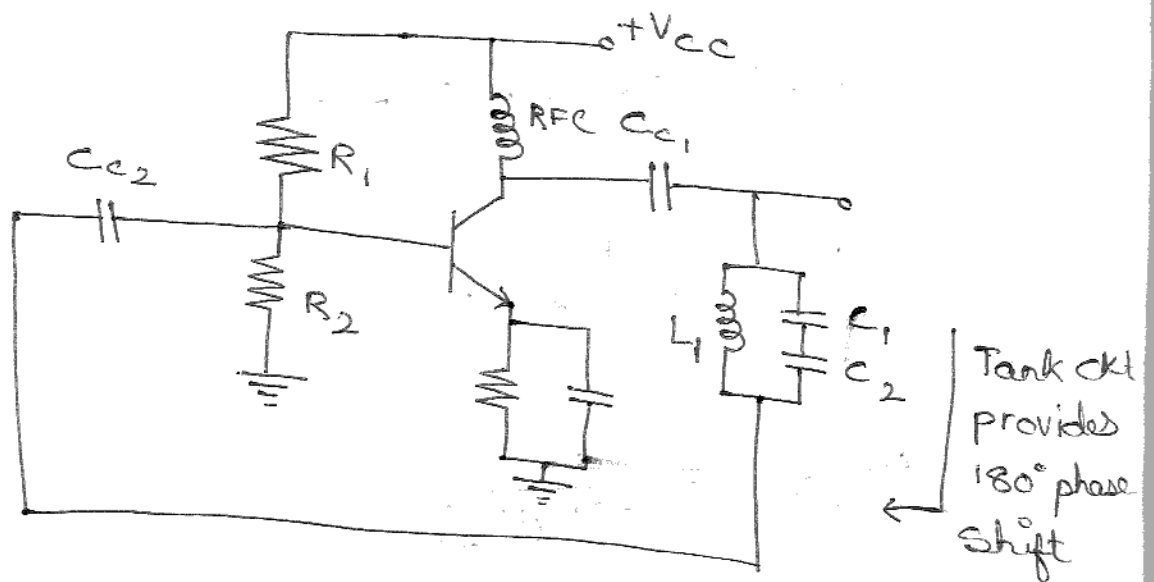
### \* Colpits Oscillator


LC oscillators which uses two capacitive reactances and one inductive reactance in the feedback (tank ckt).



→ Derivation of freq. oscillation :

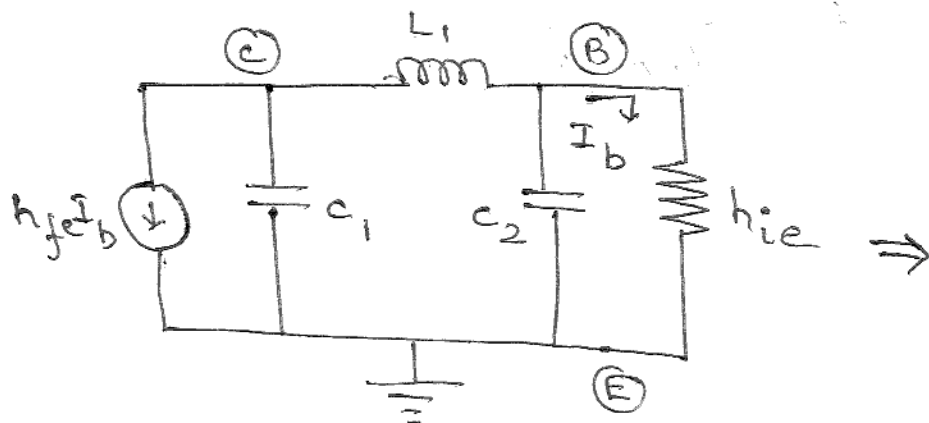The basic ckt is same as the transistor used hartley osc. except tank circuit.



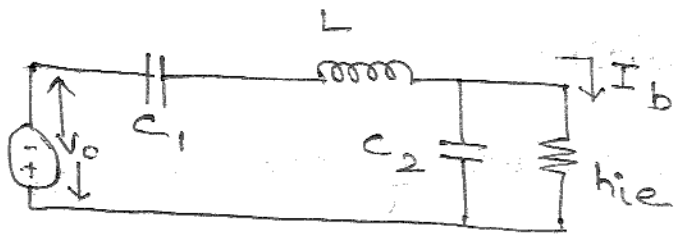

$$V_0 = h_{fe} I_b X_{C_2} = h_{fe} I_b \times \frac{1}{j\omega C_2} \quad \text{--- (1)}$$

$$I = \frac{-V_0}{[X_{C_2} + X_{C_1}] + [X_{C_1} \parallel h_{ie}]} \quad \text{--- (2)}$$

$$\omega = \frac{1}{\sqrt{L \left[ \frac{C_1 C_2}{C_1 + C_2} \right]}}$$

$$f = \frac{1}{2\pi \sqrt{L C_{eq}}}$$

where

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

## \* Crystal oscillator

- Crystals are naturally occurred or synthetically manufactured exhibiting the piezo electric effect.
- Under the influence of mechanically pressure the voltage gets generated across the opposite face of crystal.
- Crystal oscillator gets generate AC voltage which is used in watches, communication transmitters and receivers.
- Piezo electric materials are quartz, rochelle salt, fowmaline.

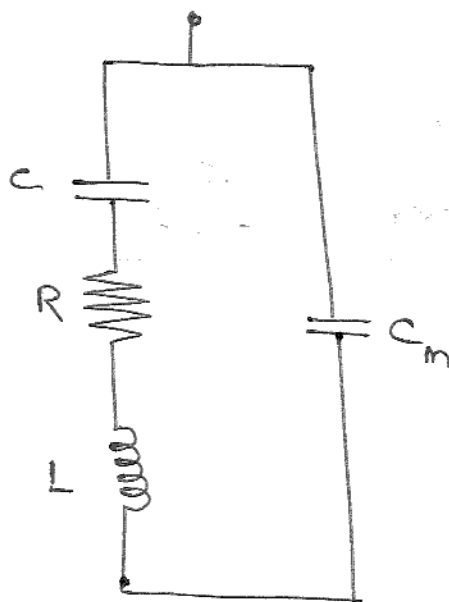


Fig. AC eq ckt of crystal

- The crystal material (Rochelle salt) which is mostly used in microphones associated with tape recorder, head set, loud speakers.
- Quartz is inexpensive and easily available in nature.
- When the crystal is not vibrating it is equivalent to a capacitance due to the mechanical mounting of crystal.
- When it is vibrating there are internal frictional losses which are denoted by  $R$  while mass of crystal which is the indication of inertia force (inductor).