

28/06/2011

① feedback Amplifiers

The portion of o/p is fed back to the ~~the~~ input

- i) +ve f/b
- ii) -ve f/b

+ve f/b: In +ve f/b, the ^{sample} output signal_n is going to ~~fed back~~ be in phase with the ip signal.

-ve f/b: The ^{sample} f/b signal_n is going to 180° out of phase.

-ve f/b results in decrease voltage gain for which the no. of ~~co~~ circuits & features are improved.

+ve f/b ~~rise~~ rise the ckt. to the oscillator.

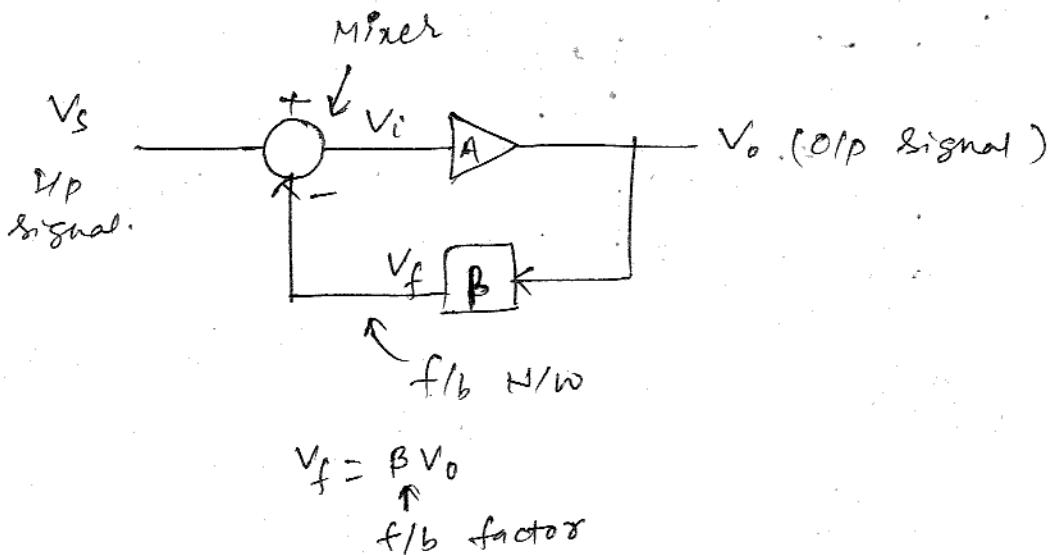


Fig. Block diagram of f/b Amplifier

while, it results in overall voltage gain, the no. of improvements are obtained.

- i) Higher i/p impedance of the circuit!
- ii) Better stabilized voltage gain.
- iii) Improved frequency response
- iv) Lower o/p impedance.
- v) Reduced noise.
- vi) More linear operation.

F/b Connection types

- i) voltage series f/b.
- ii) current " " "
- iii) voltage shunt f/b.
- iv) current " " "

- series f/b connections tend to increase the i/p resistance,
- shunt f/b connections tend to decrease the i/p resistance.

- voltage f/b decreases the o/p impedance

- current f/b increases the o/p impedance.

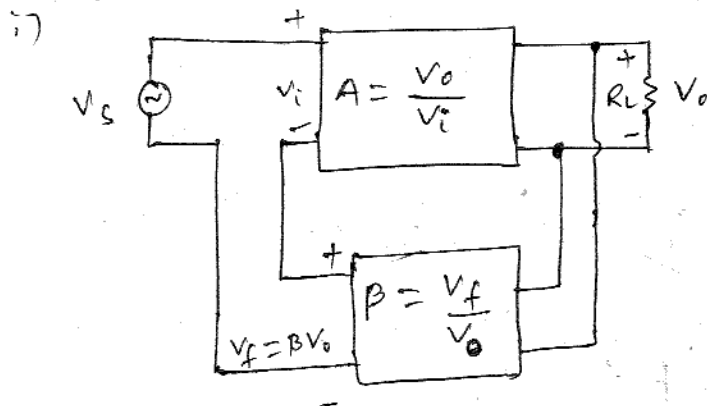


Fig. voltage series f/b

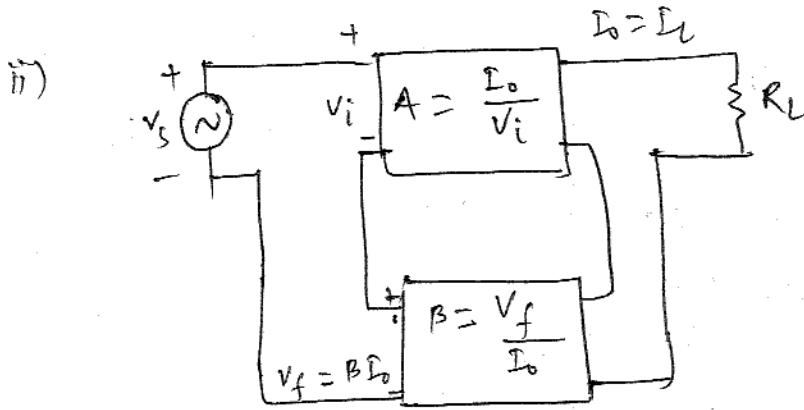
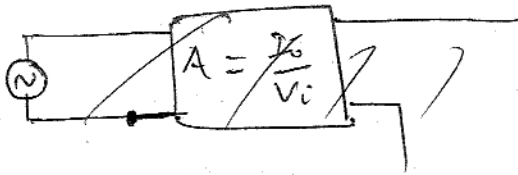


Fig. current series f/b

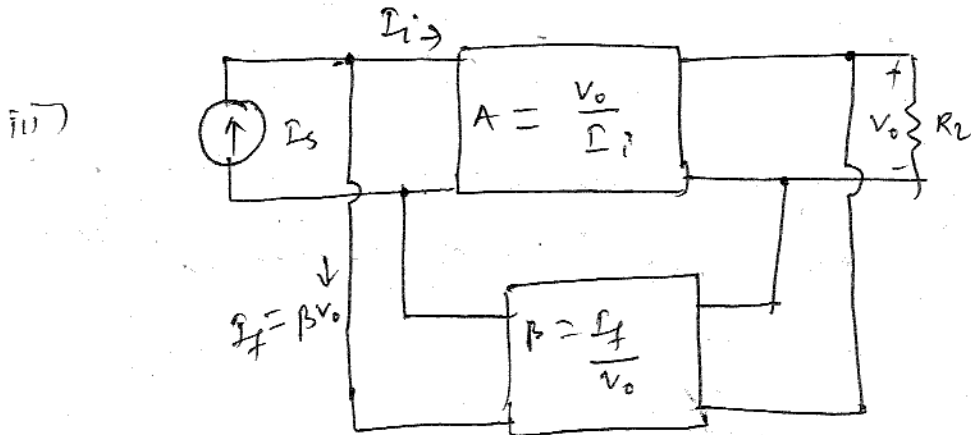



Fig. voltage shunt f/b

21/08/11

Amplifiers based on magnitude of V_p and O/p Resistance relating to source and load impedance.

- i) voltage amplifier.
- ii) current "
- (iii) Trans Conductance amplifier
- iv) Trans resistance "

i) voltage amplifier

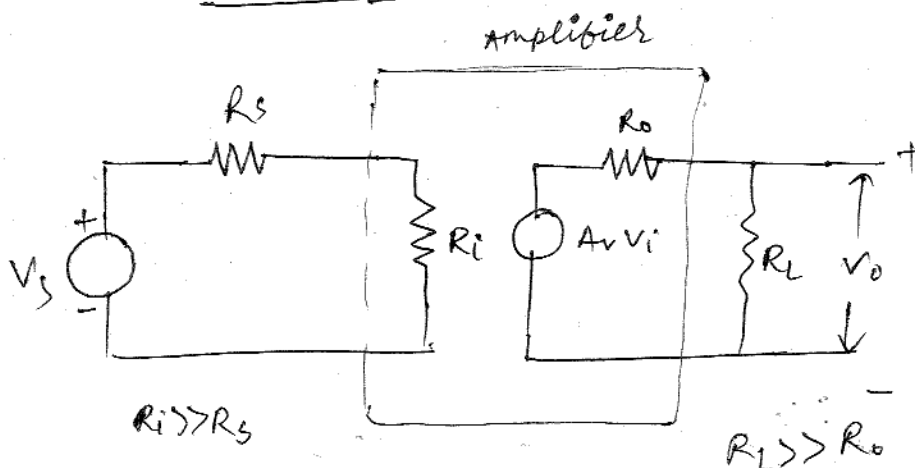

- if amplifier ~~is~~ R_i is large compare with source R Resistance (R_s)

then,

$$V_i = V_s$$


- if external load (R_L) is large compared with O/p resistance (R_o) of the amplifier

then $V_o = A_v V_i \approx A_v V_s$

Such amplifier provides a voltage O/p ~~is~~ $V_o \propto V_i$ and the proportionality factor does not depend on source and load resistance.

- An ideal amp. must have infinite i/p resistance and zero o/p resistance.


ii) Current Amplifier

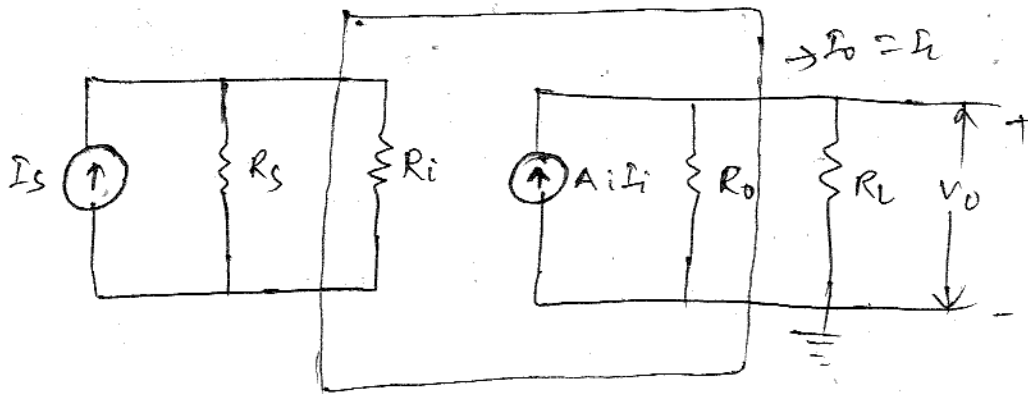


$$R_i \rightarrow 0$$
$$R_i \ll R_s$$

$$R_o \rightarrow \infty$$
$$R_L \ll R_o$$

iii) Trans Conductance amplifier

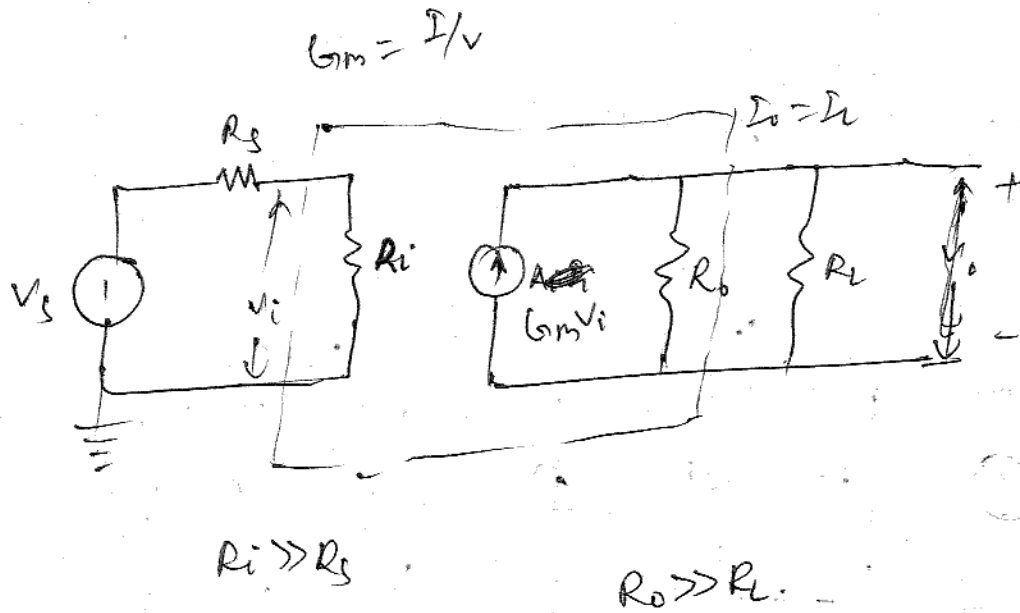


iv) Trans Resistance

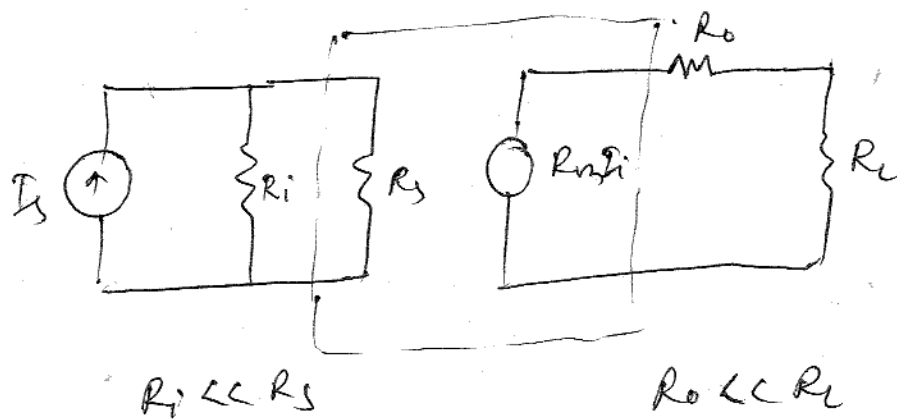

22-06/11

current series f/b

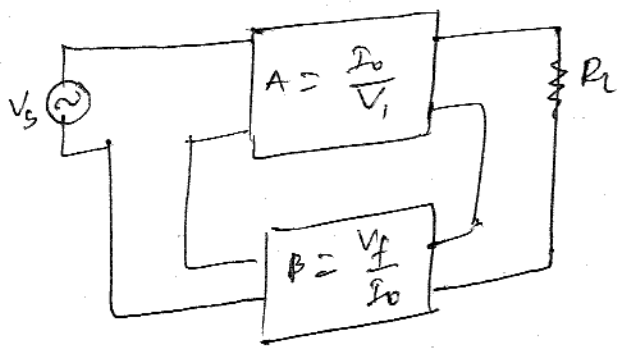


Transconductance

$$V_f = \beta I_o$$

voltage shunt f/b


Transresistance

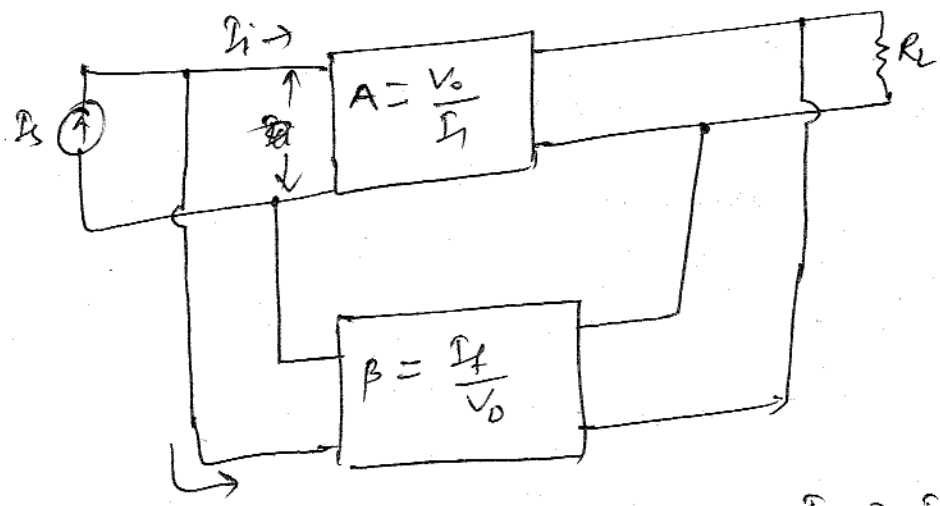

$$I_f = \beta V_o$$

$$I_i = I_s - I_f$$

current shunt f/b

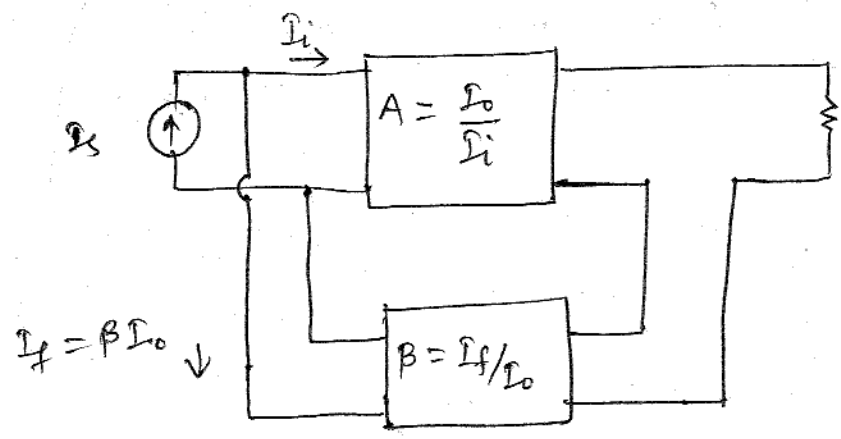

$$I_f = \beta I_o \downarrow$$

Gain for voltage series f/b amp.

* If there is no f/b signal then

$$A = \frac{V_o}{V_s} \quad (\because \text{refer to diagram})$$

$$= \frac{V_o}{V_i}$$

* If V_f (f/b) is connected in series with the i/p then (\because -ve f/b)

$$V_i = V_s - V_f$$

$$V_o = A V_i$$

$$= A (V_s - V_f)$$

$$= A V_s - A V_f$$

$$\therefore V_o = A V_s - A B V_o$$

$$V_o + A B V_o = A V_s$$

$$V_o (1 + A B) = A V_s$$

$$V_o = \frac{A V_s}{1 + A B}$$

$$\boxed{\frac{V_o}{V_s} = \frac{A}{1 + A B}}$$

$$A = \frac{A V_s / (1 + A B)}{V_i} = \frac{A V_s}{V_i (1 + A B)}$$

$$A = \frac{A V_s}{V_i (1 + A B)}$$

$$V_i + A B V_i = V_s$$

$$A B V_i = V_s - V_i$$

$$A = \frac{V_s - V_i}{V_i}$$

voltage shunt ffb

$$A_f = \frac{V_o}{I_s} = \frac{A I_i}{I_i + I_f}$$

$$[\because I_i = I_s - I_f]$$

$$= \frac{A I_i}{I_i + \beta V_o} = \frac{A I_i}{I_i + \beta A I_i}$$

$$A_f = \frac{A I_i}{I_i (1 + \beta A)}$$

$$\therefore A_f = \frac{A}{1 + \beta A}$$

$$\text{Loop Gain} = -\beta A \quad (\because \text{-ve ffb})$$

Distortion ffb

If β is made up of reactive components, the reactance of this component will change with the frequency changing the β .

As a result, gain will also change with frequency.

In tuned amplifiers, ffb network is designed such that at tuned frequency $\beta = 0$ and at other frequency, $\beta = \infty$. As a result, amplifier provides high gain for signal at tuned frequency and relatively reject all other frequencies.

Noise and Non-linear distortion


signal feedback reduces the amount of noise signal and non-linear distortion. The factor '1 + βA ' reduces both input noise and resulting non-linear distortion for considerable improvement.

23/06/11.

Input resistance

- If f/b signal is added to the input in series due to the applied voltage, it increases the input resistance.
- f/b signal - in shunt - with applied voltage \Rightarrow input resistance decreases.

Voltage series feedback amplifier

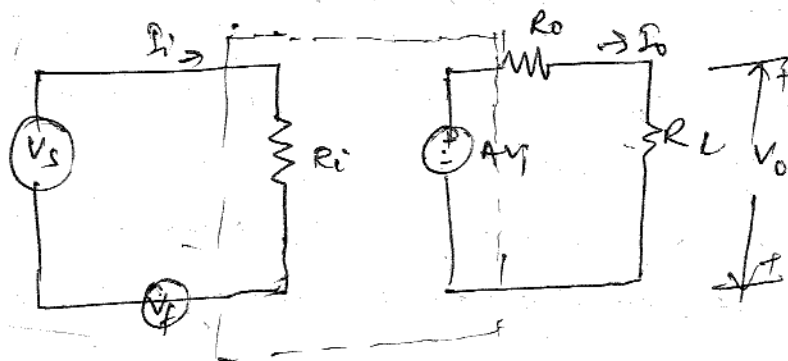

$$R_{if} = \frac{V_f}{I_i}$$

$$V_f = \beta V_o$$

Applying KVL to the i_p side,

$$V_s - I_i R_i - V_f = 0$$

$$V_s = I_i R_i + V_f$$

o/p voltage, $V_o = \frac{A V_i \cdot R_L}{R_o + R_L}$

$V_o = A V_i$

$\left(\therefore A_V = \frac{A R_L}{R_o + R_L} \right)$

Sub. the value of V_o in (1)

$V_s = I_i R_i + \beta A V_i$

$V_s = I_i R_i + \beta A V_i$


$\frac{V_s}{I_i} = R_i + \beta A V_i$

$\frac{V_s}{I_i} = R_i (1 + \beta A V)$

o/p Resistance

→ The -ve f/b which samples the o/p voltage tends to decrease the o/p resistance, which samples the o/p current tends to increase o/p resistance.

→ ~~The -ve f/b which~~

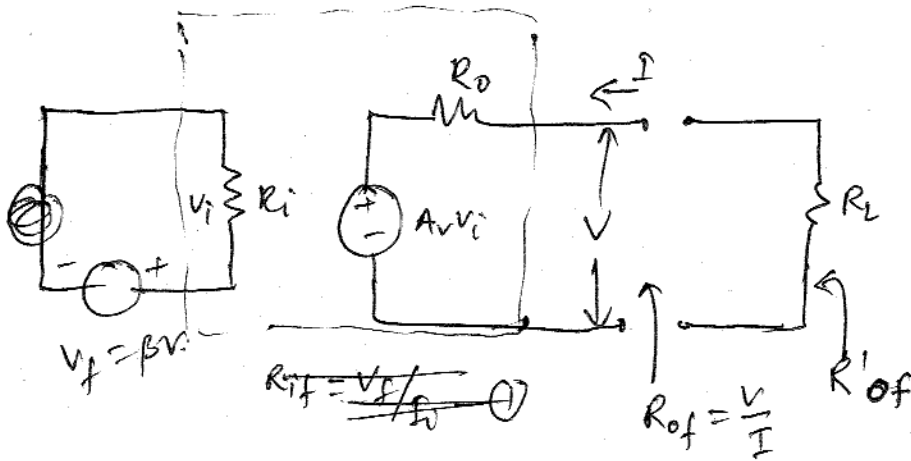

$A V_i + I R_o - V = 0$

$I = \frac{V - A V_i}{R_o} \quad \text{--- (1)}$

o/p voltage,

$V_i = -V_f = -\beta V \cdot \left[\because V_s = 0 \right] \quad \text{--- (2)}$

Sub ② in ①

$$I = \frac{V + A_v \beta V}{R_o}$$

$$I = \frac{V(1 + \beta A_v)}{R_o}$$

$$\boxed{\frac{V}{I} = \frac{R_o}{1 + \beta A_v}}$$

$$\text{So, } R_{of} = \frac{R_o}{1 + \beta A_v}$$

$$R_{of}' = R_{of} \parallel R_L$$

$$= \frac{R_{of} R_L}{R_{of} + R_L}$$

$$\boxed{\frac{\frac{R_o}{1 + \beta A_v} \cdot R_L}{\frac{R_o}{1 + \beta A_v} + R_L}}$$

2/56/11

Desensitivity


The fractional change in amplification with the feedback, divided by fractional change in amplification without feedback ~~or~~ ^{or} transfer gain.

$$\boxed{\text{Sensitivity} = \frac{1}{1 + \beta A}}$$

Reciprocal of sensitivity is called desensitivity.

$$D = 1 + \beta A$$

current series feedback amplifier

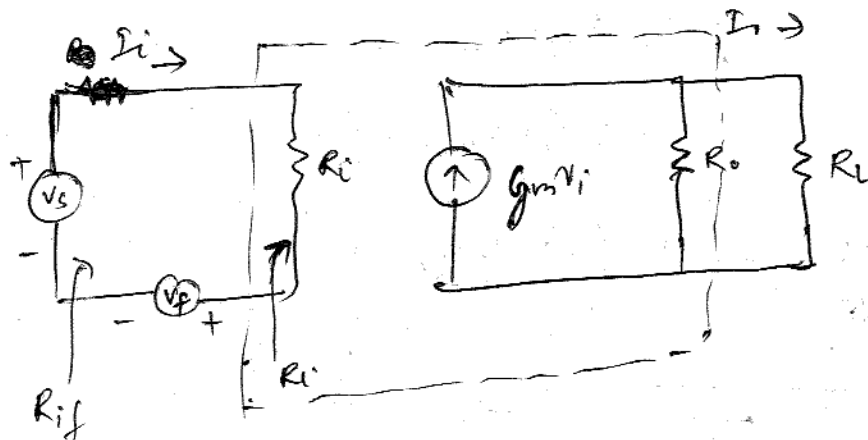

$$V_f = \beta V_o \quad V_f = \beta I_o$$

$$R_{if} = \frac{V_s}{I_i}$$

Applying KVL in the i/p side.

$$V_s - I_i R_i - V_f = 0 \Rightarrow V_s - I_i R_i = \beta I_o \quad (1)$$

$$\frac{V_s - V_f}{R_i} = I_i \quad (4)$$

$$I_o = \frac{g_m V_i \times R_o}{R_o + R_L} = G_m V_i \quad (2)$$

where the small G_m represents transconductance without feedback.

G_m represents transconductance with f/b taking R_i in account.

Now, sub.

from (1) & (2)

$$V_s - I_i R_i = \beta G_m V_i$$

$$V_s = \beta G_m I_i R_i + I_i R_i$$

$$V_s = I_i R_i (\beta G_m + 1)$$

$$R_{if} = \frac{V_s}{I_i} = R_i (1 + \beta G_m)$$

$$\therefore \text{f/b resistance } (R_{if}) = R_i (1 + \beta G_m)$$

Step-1 Methods for analysing the f/b amplifier.

i) Identify topology (type of f/b).

a) To find the input circuit type of sampling n/w.

i) By shorting the o/p i.e. $V=0$, if f/b signal become zero. Then we can say, this is voltage sampling.

ii) By opening the output loop

ie. $I=0$, the f/b signal become zero.

Then it is said as current sampling.

b) To find the type of mixing network.

→ If the f/b signal is subtracted from the externally applied voltage signal as a voltage in the input loop, then it is said that it is series mixing.

→ If the f/b signal is subtracted from the externally applied signal as a current in the i/p loop, then it can be said as shunt mixing.

⊗ Thus, by ~~determining~~ determining the ~~and~~ type of sampling n/w & mixing n/w, the type of f/b can be determined.

Step-2: Find the input circuit.

- i) For voltage sampling ^{make} ~~make~~ $V=0$ by shorting
ii) " current " $I=0$ by opening
the o/p loop.

Step-3: Find the o/p circuit.

- i) For series mixing, make $I=0$ by opening the i/p loop.
ii) For shunt mixing, make $V=0$ by shorting the i/p loop.

step-4: Replace each device by its h-parameter model.

step-5: Find the open loop gain.

step-6: Indicate S_f and S_o in the ckt. and find out β .

step-7: Find A_f , R_{id} , R_{of} , R'_{of} (R_i included).