

$$= \frac{h_{fe} R R^3 j\omega^3 C^3}{1 - \omega^2 C^2 R^2 (4R + 6) + j\omega RC (5 + 10) - j\omega^3 C^3 R^3 (5R + 1)}$$

$$= \frac{j\omega^3 R^3 C^3 h_{fe}}{(1 - 4R\omega^2 C^2 R^2 - 6\omega^2 C^2 R^2) - j\omega [3R\omega^2 R^3 C^3 + \omega^2 R^3 C^3 - 5RC - 10R]}$$

Divide nr & dr by $(-j\omega^3 R^3 C^3)$
we get -

$$= \frac{kh_{fe}}{\left(\frac{-1}{\omega^3 R^3 C^3} + \frac{4R}{\omega RC} - \frac{6j}{\omega RC} \right)}$$

$$AB = \frac{kh_{fe}}{j \left(\frac{1}{\omega^3 R^3 C^3} - \frac{4R}{\omega RC} - \frac{6}{\omega RC} \right) + (3R + 1) \frac{-5}{\omega^2 R^2 C^2} - \frac{R}{\omega^2 C^2 R}}$$

Condition: -
(i) $AB = 1$

Barkhausen Criteria

& (ii) $AB = 0^\circ$ or 180°

J.S.
18/07/11

$$\theta = -\tan^{-1} \left(\frac{\text{Imaginary part}}{\text{Real part}} \right)$$

$$= -\tan^{-1} \left(\frac{I.P.}{R.P.} \right) = 0$$

\Rightarrow Imaginary part = 0

$$\Rightarrow \frac{1}{\omega^3 R^3 C^3} - \frac{4k}{\omega R C} - \frac{6}{\omega R C} = 0$$

Substitute, $\frac{1}{\omega R C} = a$

$$\Rightarrow \frac{a^3}{\omega^3} - \frac{4k}{\omega} - \frac{6}{\omega} = 0$$

$$\Rightarrow a^3 - 4ak - 6a = 0$$

$$\Rightarrow a(a^2 - 4k - 6) = 0$$

$$\boxed{a=0} \text{ or, } a^2 - 4k - 6 = 0$$

$$a = \pm \sqrt{4k+6}$$

$$\Rightarrow \frac{1}{\omega R C} = \sqrt{4k+6}$$

$$\Rightarrow \frac{1}{2\pi f R C} = \sqrt{4k+6}$$

$$\Rightarrow \boxed{f = \frac{1}{2\pi R C \sqrt{4k+6}}}$$

When $AB = 1$

$$\Rightarrow \frac{k h_{fe}}{3k + 1 - 5\alpha^2 - k\alpha^2} = 1$$

$$\Rightarrow k h_{fe} = 3k + 1 - 5\alpha^2 - k\alpha^2 \quad \text{--- (1)}$$

$$\text{Sub } \alpha = \sqrt{4k+6} \text{ in (1)}$$

$$\begin{aligned} k h_{fe} &= 3k + 1 - 5(4k+6) - k(4k+6) \\ &= 3k + 1 - 20k - 30 - 4k^2 - 6k \end{aligned}$$

$$k h_{fe} = -4k^2 - 23k - 29$$

$$\boxed{k h_{fe} = -4k^2 - 23k - 29}$$



$$\therefore \left| \frac{k h_{fe}}{3k + 1 - 5\alpha^2 - k\alpha^2} \right| = 1$$

$$\Rightarrow \frac{k h_{fe}}{4k^2 + 23k + 29} = 1$$

$$\Rightarrow \boxed{k h_{fe} = \frac{4k^2 + 23k + 29}{k}}$$

Wien Bridge Oscillator

frequency sensitive arms

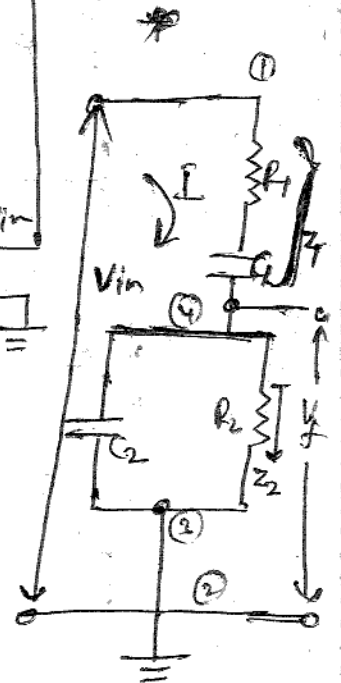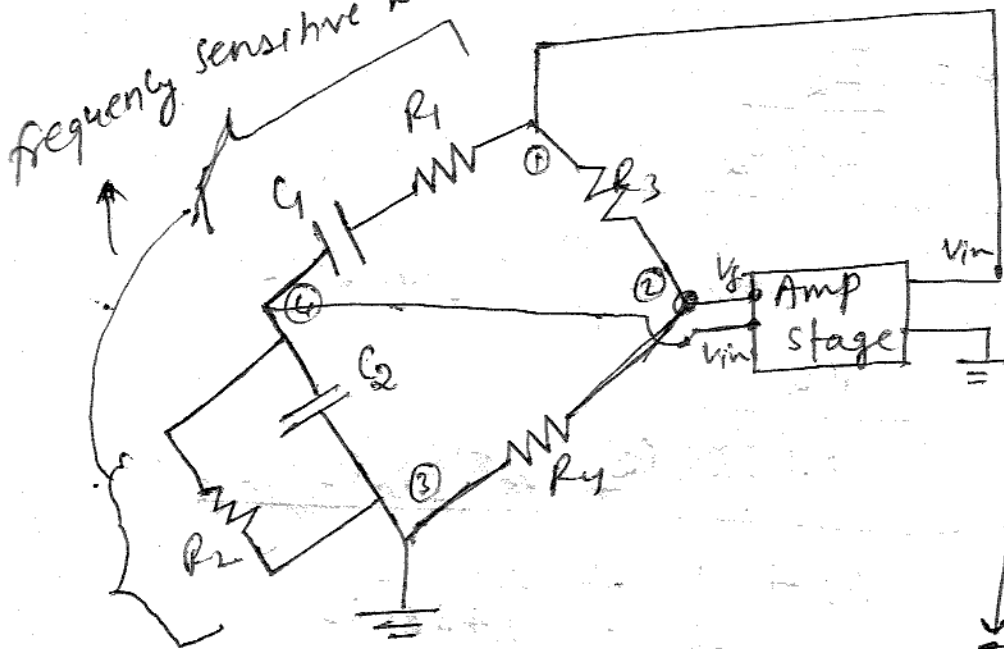

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = R_1 + \frac{1}{sC_1}$$

$$Z_2 = \frac{R_2 \times \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{\frac{R_2}{j\omega C_2}}{\frac{R_2 j\omega C_2 + 1}{j\omega C_2}} = \frac{R_2}{1 + R_2 j\omega C_2}$$

Ice

Ves

Ro

$$I = \frac{V_{in}}{Z_1 + Z_2}$$

$$V_f = I Z_2$$

$$\text{and } \beta = \frac{V_f}{V_{in}}$$

$$\Rightarrow V_f = \left(\frac{V_{in}}{Z_1 + Z_2} \right) Z_2$$

$$\Rightarrow \frac{V_f}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

$$\beta = \frac{V_f}{v_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

$$\beta = \frac{Z_2}{Z_1 + Z_2}$$

$$\beta = \frac{R_2}{1 + sR_2C_2}$$

$$R_1 + \frac{1}{sC_1} + \frac{R_2}{1 + sR_2C_2}$$

$$= \frac{R_2}{1 + sR_2C_2}$$

$$\frac{(sC_1)(1 + sR_2C_2)R_1 + (1 + sR_2C_2) + R_2(sC_1)}{(sC_1)(1 + sR_2C_2)}$$

$$= \frac{R_2}{\cancel{(1 + sR_2C_2)}} \times \frac{\cancel{(sC_1)(1 + sR_2C_2)}}{(sC_1)(1 + sR_2C_2)R_1 + (1 + sR_2C_2) + R_2sC_1}$$

$$= R_2 sC_1$$

$$\frac{R_2 sC_1}{(sC_1)(1 + sR_2C_2)R_1 + (1 + sR_2C_2) + R_2sC_1}$$

$$= \frac{R_2 s C_1}{s C_1 R_1 + s^2 R_2 R_1 C_1 C_2 + 1 + s R_2 C_2 + R_2 s C_1}$$

$$\beta = \frac{R_2 s C_1}{s^2 [R_2 R_1 C_1 C_2] + s [R_2 C_2 + R_1 C_1 + R_2 C_1] + 1}$$

$$\beta = \frac{R_2 j\omega C_1}{j^2 \omega^2 [R_1 R_2 C_1 C_2] + j\omega [R_2 C_2 + R_1 C_1 + R_2 C_1] + 1}$$

$$= \frac{R_2 j\omega C_1}{1 - \omega^2 [R_1 R_2 C_1 C_2] + j\omega [R_2 C_2 + R_1 C_1 + R_2 C_1]}$$

$$= \frac{R_2 j\omega C_1}{1 - \omega^2 (R_1 R_2 C_1 C_2) + j\omega (R_2 C_2 + R_1 C_1 + R_2 C_1)}$$

$$= \frac{R_2 j\omega C_1}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + j\omega (R_2 C_2 + R_1 C_1 + R_2 C_1)}$$

$$= \frac{R_2 j\omega C_1}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + j\omega (R_2 C_2 + R_1 C_1 + R_2 C_1)} \times \frac{1 - \omega^2 (R_1 R_2 C_1 C_2)}{1 - \omega^2 (R_1 R_2 C_1 C_2)} \quad \text{--- (1)}$$

$$= \frac{R_2 j\omega C_1 (1 - \omega^2 (R_1 R_2 C_1 C_2))}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + j\omega (R_2 C_2 + R_1 C_1 + R_2 C_1)}$$

$$= \frac{R_2 j \omega C_1}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + j \omega (R_2 C_2 + R_1 C_1 + R_2 C_1)} \times \frac{[1 - \omega^2 R_1 R_2 C_1 C_2] - j \omega [R_2 C_2 + R_1 C_1 + R_2 C_1]}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + j \omega (R_2 C_2 + R_1 C_1 + R_2 C_1)}$$

$$= \frac{R_2 j \omega C_1 \{ [1 - \omega^2 R_1 R_2 C_1 C_2] - j \omega [R_2 C_2 + R_1 C_1 + R_2 C_1] \}}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + j \omega (R_2 C_2 + R_1 C_1 + R_2 C_1)}$$

$$(1 - \omega^2 R_1 R_2 C_1 C_2) + \omega^2 (R_2 C_2 + R_1 C_1 + R_2 C_1)$$

$$= \frac{R_2 j \omega C_1 \{ (1 - \omega^2 R_1 R_2 C_1 C_2) - j \omega (R_2 C_2 + R_1 C_1 + R_2 C_1) \}}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + j \omega (R_2 C_2 + R_1 C_1 + R_2 C_1)}$$

$$1 - \omega^2 R_1 R_2 C_1 C_2 + \omega^2 R_2 C_2 + \omega^2 R_1 C_1 + \omega^2 R_2 C_1$$

$$= \frac{R_2 j \omega C_1 (1 - \omega^2 R_1 R_2 C_1 C_2) + R_2 \omega^2 C_1 (R_2 C_2 + R_1 C_1 + R_2 C_1)}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + \omega^2 (R_2 C_2 + R_1 C_1 + R_2 C_1)^2}$$

$$\text{--- (2) ---}$$

∴ Imaginary part = 0

$$\Rightarrow \frac{R_2 j \omega C_1 (1 - \omega^2 R_1 R_2 C_1 C_2)}{[1 - \omega^2 (R_1 R_2 C_1 C_2)] + \omega^2 (R_2 C_2 + R_1 C_1 + R_2 C_1)^2} = 0$$

$$\Rightarrow R_2 j \omega C_1 (1 - \omega^2 R_1 R_2 C_1 C_2) = 0$$

$$0 [R_2 G + R_2 G]$$

$$\Rightarrow I = \omega^2 R_1 R_2 G G$$

$$\omega = \frac{1}{\sqrt{R_1 R_2 G G}}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 G G}}$$

When, $R_1 = R_2 = R$ & $G = G = C$

$$f = \frac{1}{2\pi \sqrt{R^2 C^2}} = \frac{1}{2\pi RC}$$

Sub $f = \frac{1}{2\pi RC}$, $\omega = \frac{1}{RC}$, $R_1 = R_2 = R$
 $G = C = C$

in (2)

$$= RC \left(\frac{1}{RC} \right)^2 \left(1 - \frac{1}{R^2 C^2} \cdot R^2 C^2 \right) + \frac{RC}{R^2 C^2} \cdot (RC + RC + RC)$$

$$\left(1 - \frac{1}{R^2 C^2} R^2 C^2 \right) + \frac{1}{RC} (RC + RC + RC)$$

$$= \frac{\frac{1}{RC} (3RC)}{\frac{1}{RC} (3RC)} = \frac{3}{3} = \frac{3 \times RC}{3} = RC$$

$$\beta = R \frac{1}{R^2 C^2} \cdot \left(1 - \frac{1}{R^2 C^2}\right) + R C \frac{1}{R^2 C^2} (3RC)$$

$$\frac{\left(1 - \frac{1}{R^2 C^2}\right) + \frac{1}{R^2 C^2} (3RC)}{9RC^2}$$

$$= \frac{3}{9RC^2} = \frac{1}{3}$$

$$= \frac{3}{9} = \frac{1}{3}$$

$$\boxed{\beta = 1/3}$$

$$|AB| = 1$$

$$A\left(\frac{1}{3}\right) = 1$$



$$\Rightarrow \boxed{A = 3}$$

21/7/14

R.C)


Twin-T Oscillator

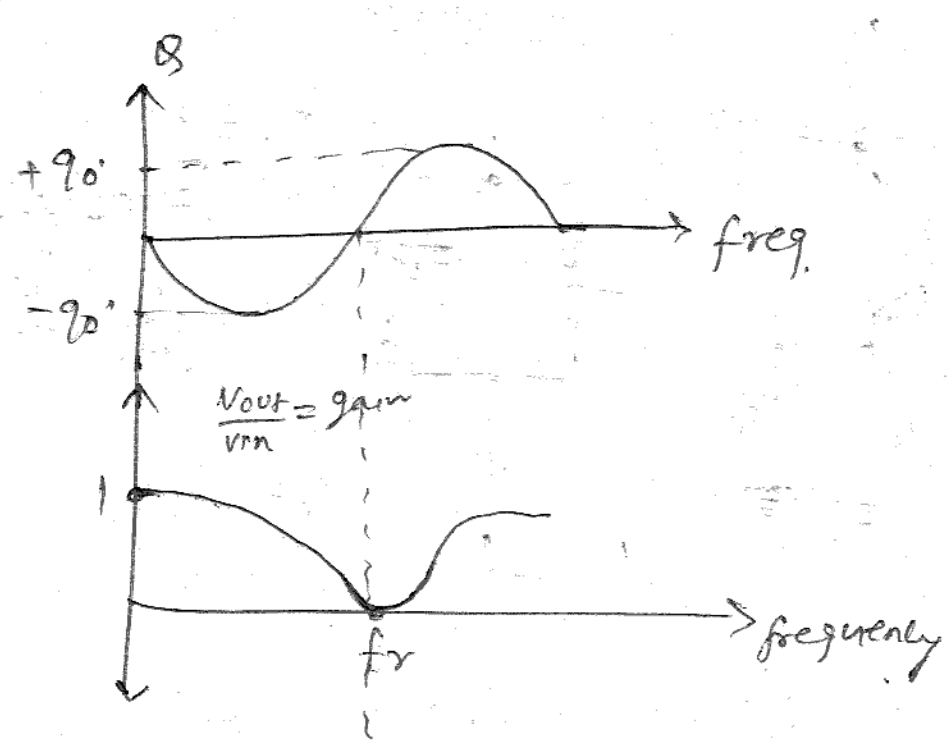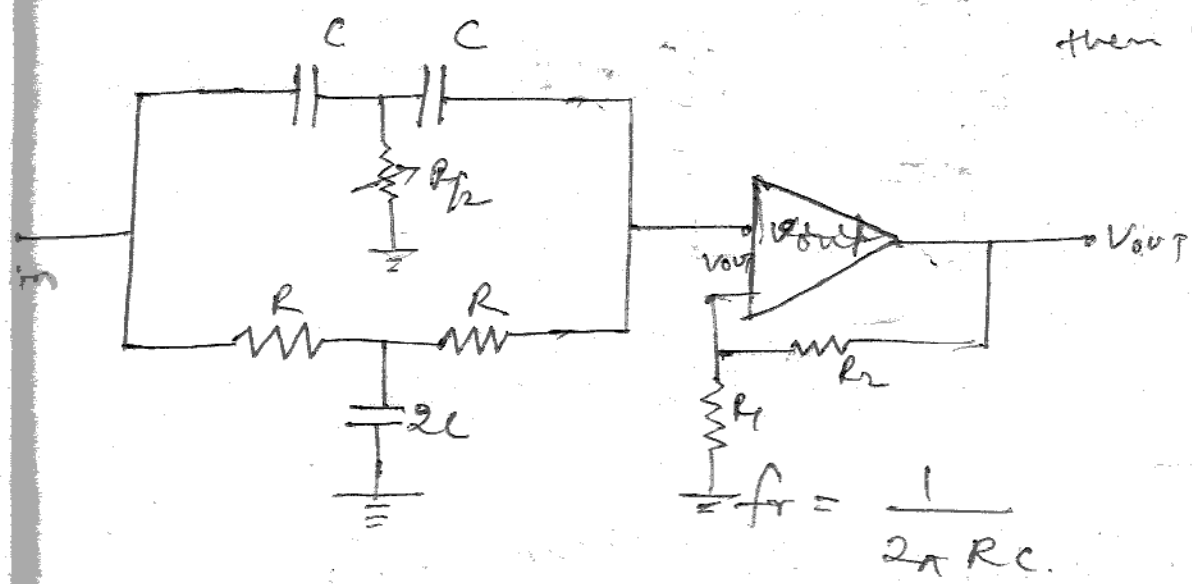If first capacitor & then resistor is connected then HPF.




Band stop filter or Band elimination filter.
Notch filter.

LC-oscillator

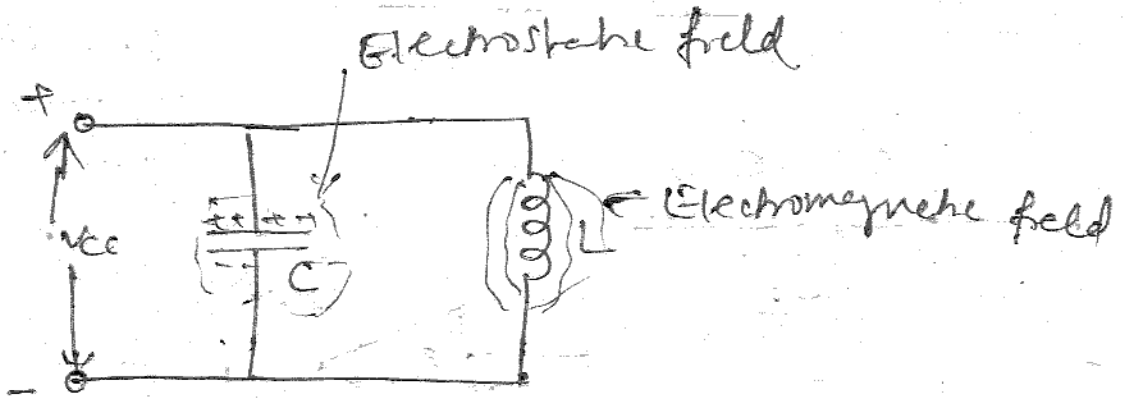

26/7/11


Colpitts oscillator

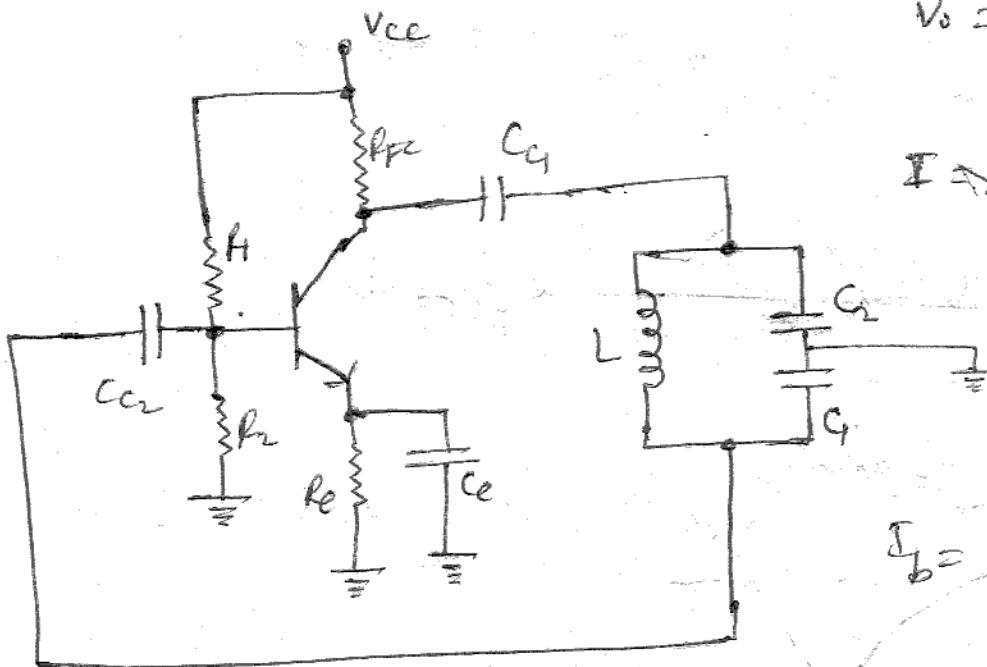


$$V_o = h_{fe} I_b \cdot \frac{1}{j\omega C_2}$$

$$I = \frac{V_o}{R} = -h_{fe} I_b \cdot \frac{1}{j\omega C_2} \cdot \frac{1}{1 + j\omega L}$$

$$I_b =$$

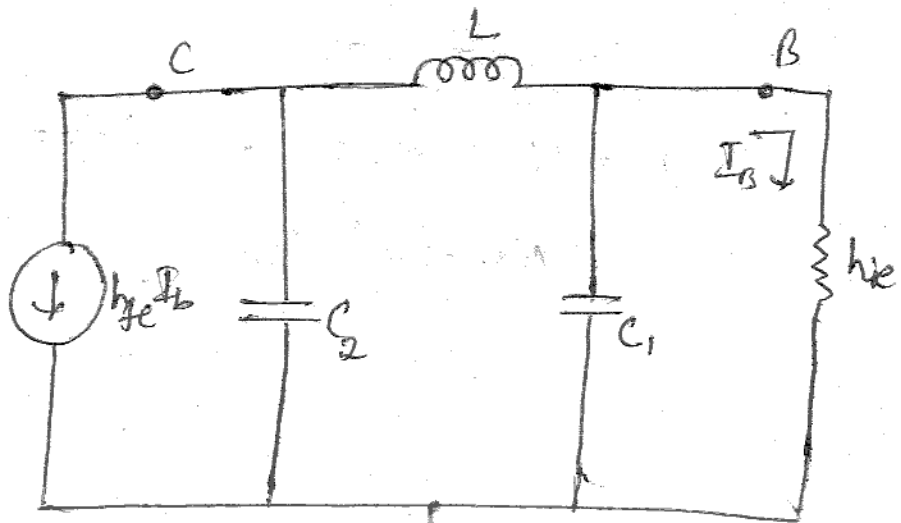

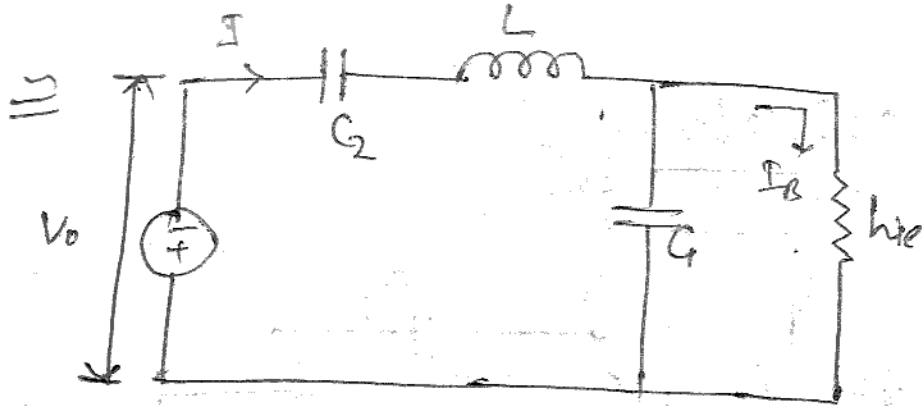

$$I = \frac{V_0}{R} = -h_{fe} I_b \cdot \frac{1}{j\omega C_2}$$

$$\left(\frac{1}{j\omega C_2} + j\omega L \right) + \left(\frac{\frac{1}{j\omega C_4} \cdot h_{ie}}{\frac{1}{j\omega C_4} + h_{ie}} \right)$$

Substitute $s = j\omega$.

$$I = -h_{fe} I_b (1 + s C_4 h_{ie})$$

$$s^3 L C_4 C_2 h_{ie} + s^2 L C_2 + s h_{ie} (C_1 + C_2) + 1$$

$$I_b = \frac{I \cdot \frac{1}{j\omega C_4}}{\frac{1}{j\omega C_4} + h_{ie}}$$




Sub $j\omega = s$, and simplifying we get

$$I_b = \frac{I}{1 + s h_{ie} C_4}$$

Then sub I in I_b .

**

Clapp's Oscillator

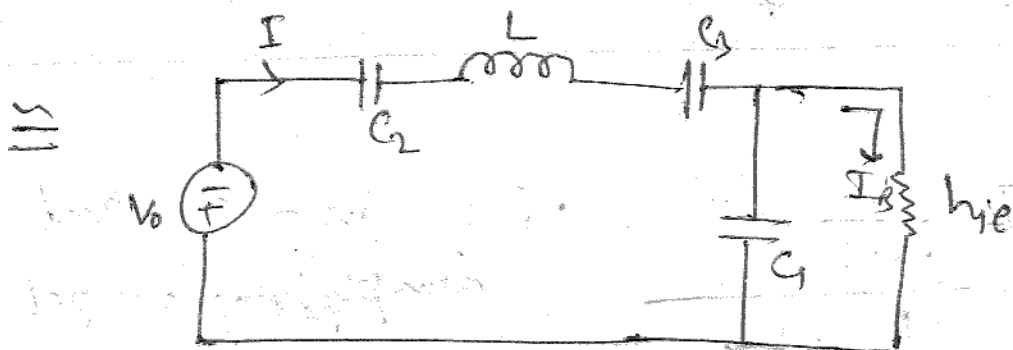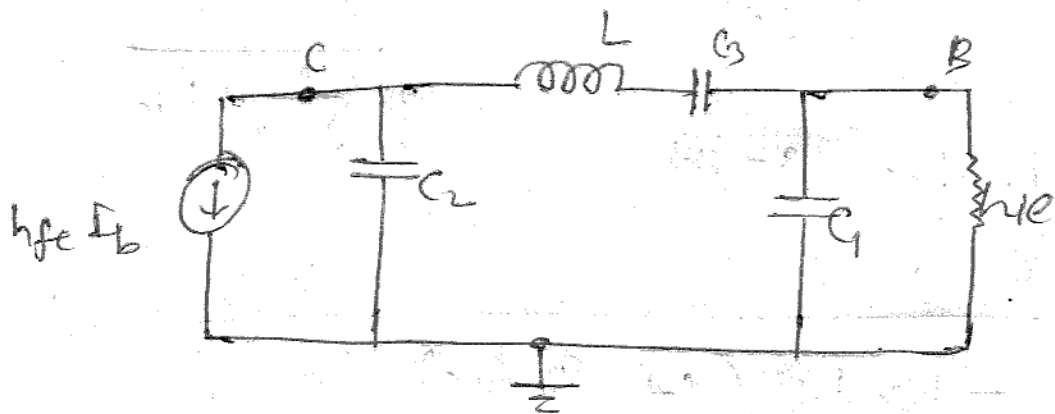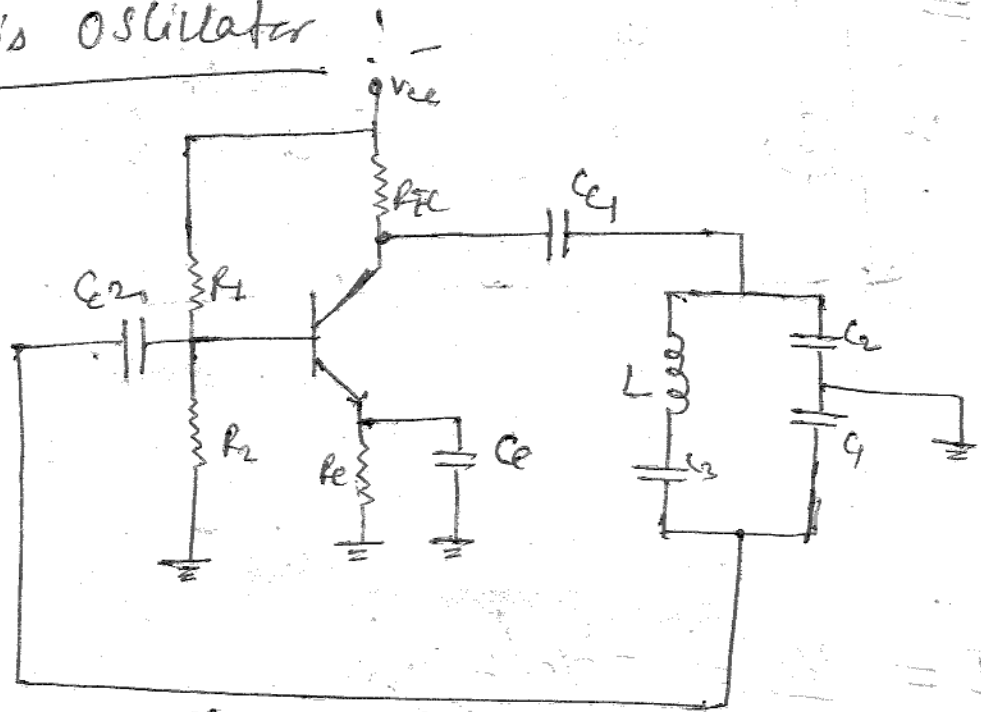

$$V_o = h_{fe} I_b \cdot \frac{1}{j\omega C_2}$$

$$I = \frac{V_o}{R} = h_{fe} I_b \cdot \frac{1}{j\omega C_2}$$

$$\textcircled{I_b} \left(\frac{1}{j\omega C_2} + j\omega L_1 + \frac{1}{j\omega C_3} \right) + \frac{j\omega C_4 h_{fe}}{\frac{1}{j\omega C_4} + h_{fe}}$$

Sub $j\omega = s$, in above eqⁿ,

$$I = \frac{-h_{fe} I_b C_3 (1 + s C_4 h_{fe})}{s^3 L_1 C_2 C_3 h_{fe} + s^2 L_1 C_2 C_3 + s h_{fe} (C_2 C_3 + C_4 C_2 + C_4 C_3) + C_2 + C_3}$$

Sub I in eqⁿ

$$I_b = \frac{I \times \frac{1}{j\omega C_4}}{\frac{1}{j\omega C_4} + h_{fe}} = \frac{I}{1 + s h_{fe} C_4}$$

Sub I in eqⁿ, we get,

$$\Rightarrow \frac{I}{1 + s h_{fe} C_4} = -h_{fe} I$$

$$1 = \frac{-h_{fe} C_3}{C_2 + C_3 - \omega^2 L_1 C_2 C_3 + j\omega h_{fe} (C_4 C_2 + C_4 C_3 + C_4) - \omega^2 L_1 C_2 C_3}$$

$$I.P = 0$$

$$C_1 C_2 + C_2 C_3 + C_3 C_1 - \omega^2 L C_1 C_2 C_3 = 0$$

$$\omega = \sqrt{\frac{C_1 C_2 + C_2 C_3 + C_3 C_1}{L C_1 C_2 C_3}}$$

$$\omega = \frac{1}{\sqrt{L C_{eqiv}}}$$

$$f = \frac{1}{2\pi \sqrt{L C_{eqiv}}}$$

FCS

Sub I_b in I , we get.

$$I_b = \frac{I}{1 + s h_{ie} C_1}$$

$$\frac{V_o}{I} = \frac{-h_{fe} I_b (1 + s C_1 h_{ie})}{(1 + s h_{ie} C_1) [s^3 L C_1 C_2 h_{ie} + s^2 L C_2 + s h_{ie} (C_1 + C_2) + 1]}$$

$$\Rightarrow 1 = \frac{-h_{fe} (1 + s C_1 h_{ie})}{s^3 L C_1 C_2 h_{ie} + s^2 L C_2 + s h_{ie} (C_1 + C_2) + 1}$$

Sub $s = j\omega$,

$$1 = \frac{-h_{fe} (1 + j\omega C_1 h_{ie})}{1 - \omega^2 L C_2 + j\omega h_{ie} [C_1 + C_2 - \omega^2 L C_1 C_2]}$$

$$1 = \frac{-h_{fe}}{1 - \omega^2 L C_2 + j\omega h_{ie} [C_1 + C_2 - \omega^2 L C_1 C_2]}$$

$$1 - \omega^2 L C_2 + j\omega h_{ie} [C_1 + C_2 - \omega^2 L C_1 C_2]$$

\therefore for $\theta = 0$

$\Rightarrow \theta = \frac{\pi}{2}$

Imaginary part

$$= \frac{\text{Imag part}}{\text{Real part}}$$

\Rightarrow Imaginary part = 0

$$[C_1 + C_2 - \omega^2 L C_1 C_2] = 0$$


$$\omega = \sqrt{\frac{C_1 + C_2}{L C_1 C_2}} = \sqrt{\frac{1}{L C_{eq} \omega}}$$

$$\therefore \frac{C_1 C_2}{C_1 + C_2} = C_{eq}$$

∴ frequency for Colpitts oscillator

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$




Hartley oscillator

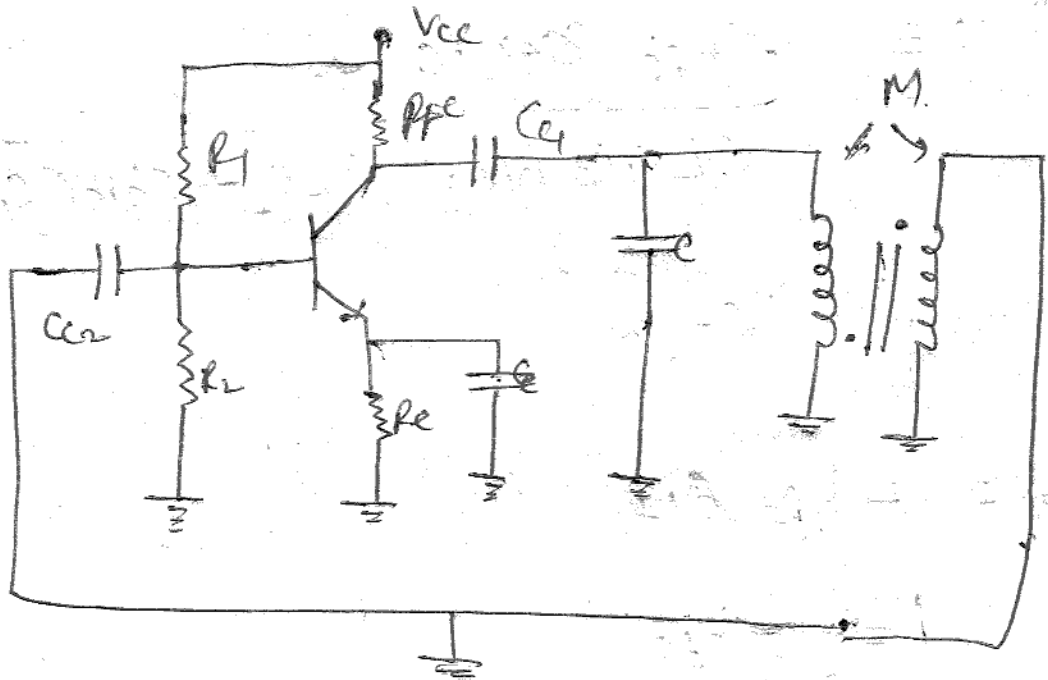

FCN

4/8/11

Negative Resistance Oscillator using UJT

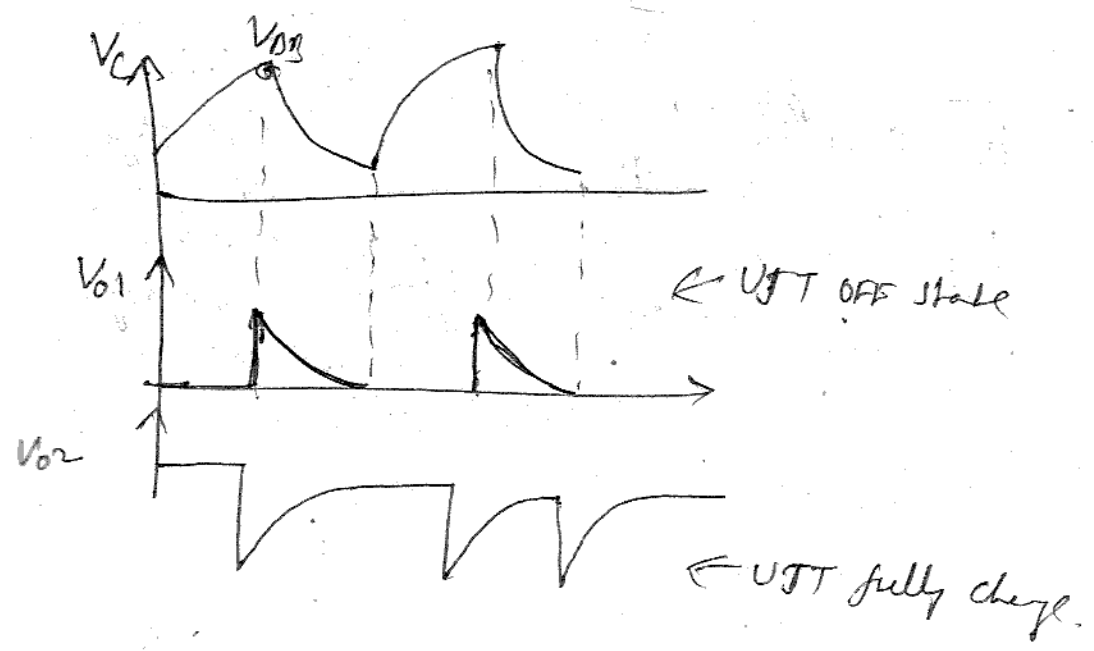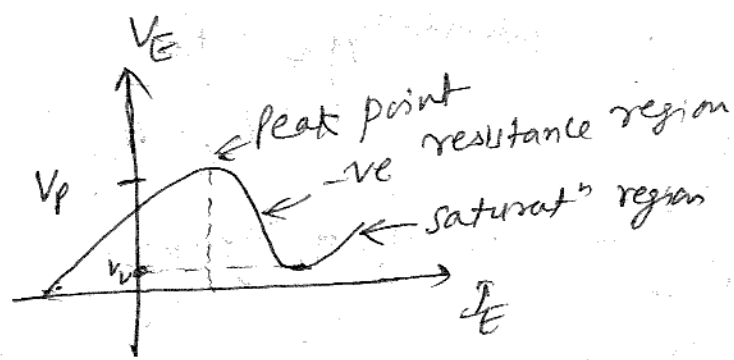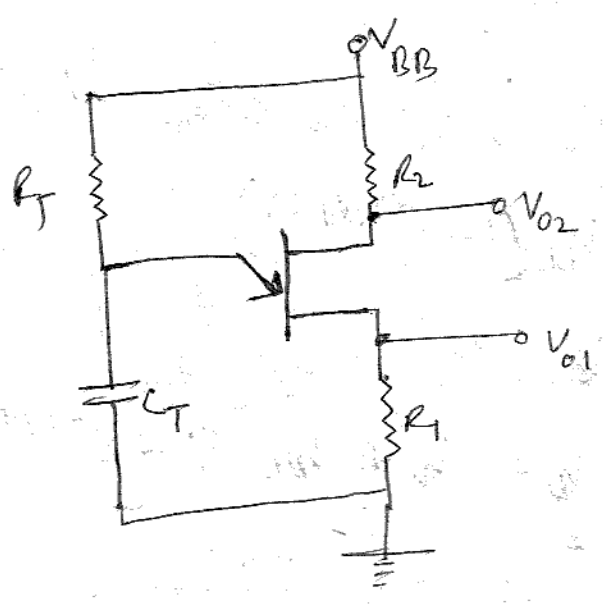

$$V_p = \eta V_{BB} + V_D$$

↑
intrinsic stand off ratio

$V_D \leftarrow$ Diode Cut in Voltage.

Capacitor voltage, $V_C = V_V + V_{BB} (1 - e^{-t})$

$$V_C = V_V + V_{BB} (1 - e^{-t/R_T C_T})$$

When, $V_C = V_p$, at $t = T$

$$\eta V_{BB} + V_D = V_V + V_{BB} (1 - e^{-T/R_T C_T})$$

V_D & $V_V \rightarrow$ small

$$\eta = 1 - e^{-T/R_T C_T}$$

$$\Rightarrow e^{-T/R_T C_T} = 1 - \eta$$

where $\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$

$$\Rightarrow \frac{T}{R_T C_T} = \ln \left(\frac{1}{1 - \eta} \right)$$



R_{B1} = Base resistance of UJT.

$$\Rightarrow T = R_T C_T \ln \left(\frac{1}{1 - \eta} \right)$$

$$T = R_T C_T \ln \left(\frac{1}{1 - \eta} \right)$$

$$f = \frac{1}{T} = \frac{1}{R_T C_T \ln \left(\frac{1}{1 - \eta} \right)}$$

V_V = Valley voltage or minimum voltage.

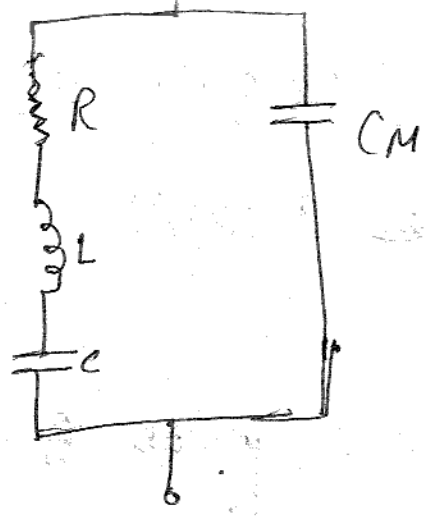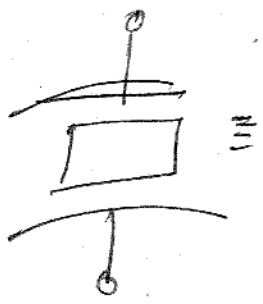

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

⇒ frequency stability

$f \propto \frac{1}{\text{thickness}}$

Rochelle Crystal

piezo oscillator
Million oscillator

→ Piezoelectric prop ↑
mechanical strength ↓

Tormaline Crystal


→ Piezo ↑
mechanical ↑

Quartz Crystal

Piezoelectric
mechanical strength

RC-phase
wein
Karlby.
Cant Colpits.

Analysis
i/p resistance
↓
o/p

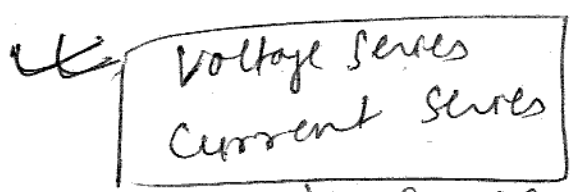

i/p & o/p


Analysis

Steps of Analysis

11/8/14

USE OF LOGIC GATE

→ as linear amplifier


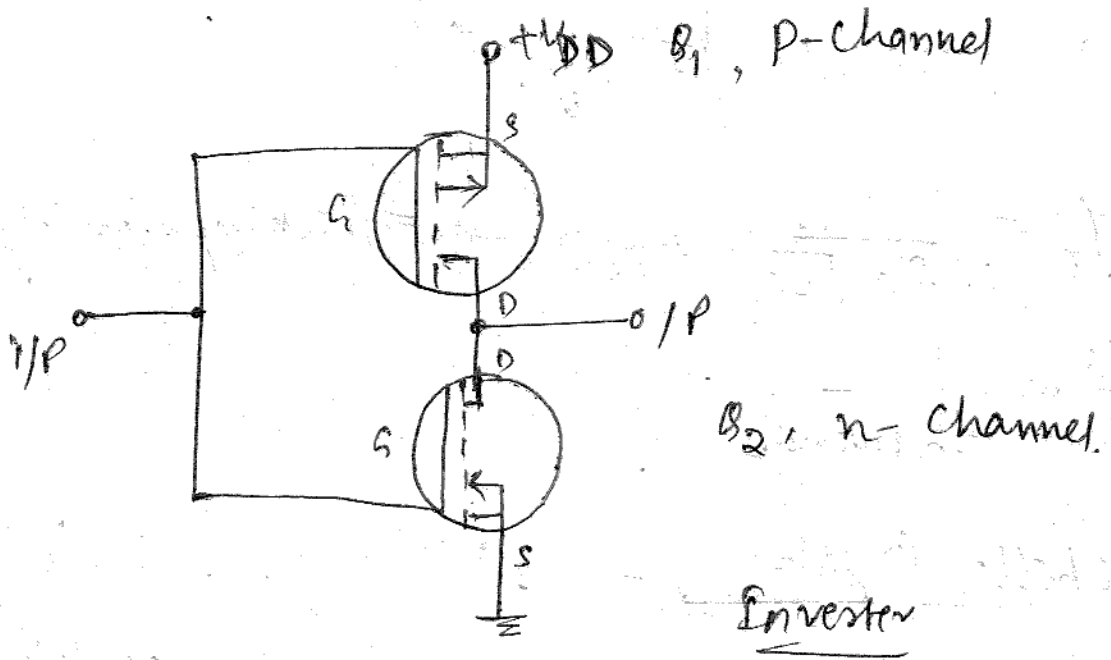


FCU

oscillator & clock Gen

eg } P channel ON when $i/p = 0$
N " ON when $i/p = 1$

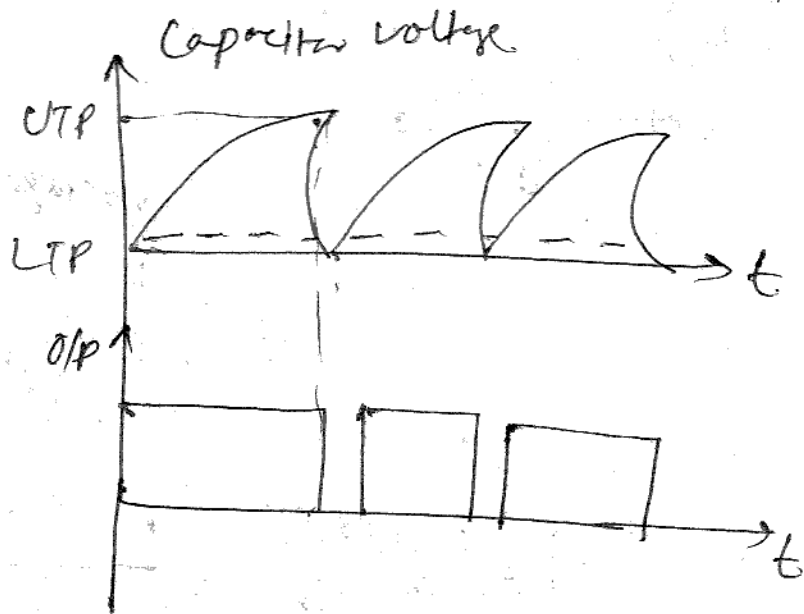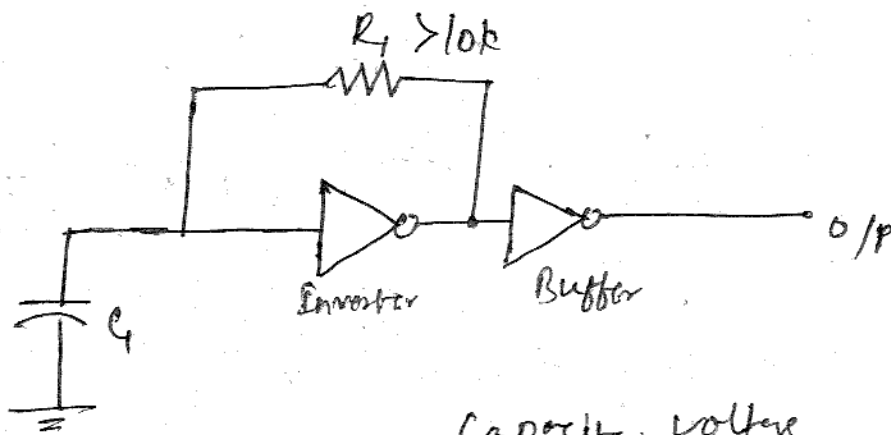Oscillator & Clock generator Circuits using logic gates :-




when $0/p = 0$
when $0/p = 1$

12/8/11


UNIT 3 TUNED AMPLIFIER

Tuned circuit:- as Tanked circuit

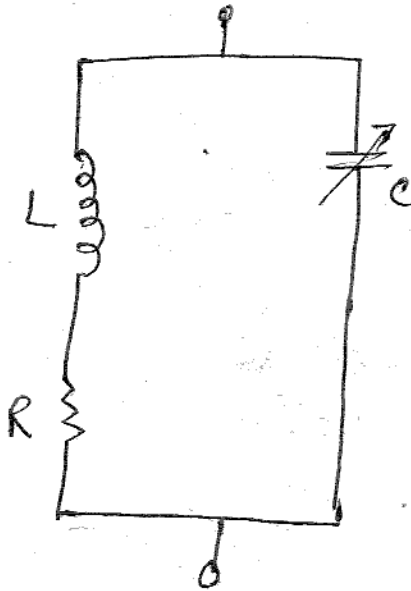

$$\text{frequency, } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$X_C = X_L, \text{ at resonance}$$

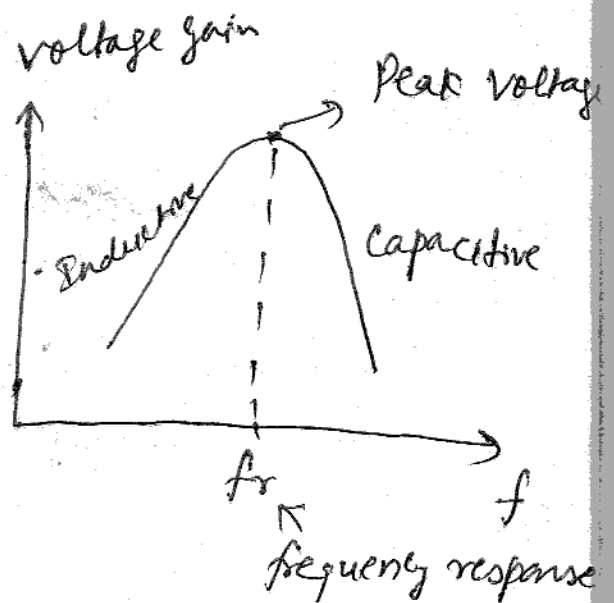

$f_r =$ tuned freq
or
resonant
freq.


Coil losses:-

- ① Copper loss \Rightarrow DC Resistance $\propto \frac{1}{f}$
- ② Eddy current loss \Rightarrow due to current flow within the core caused by inductⁿ \propto frequency
- ③ Hysteresis loss \propto area enclosed by the hysteresis loop \propto frequency


Quality factor = $\frac{\text{Reactance}}{\text{Resistance}} = Q$

Dissipation factor, $D = \frac{1}{Q} \Rightarrow$ Dissipation within the Component

Series:-

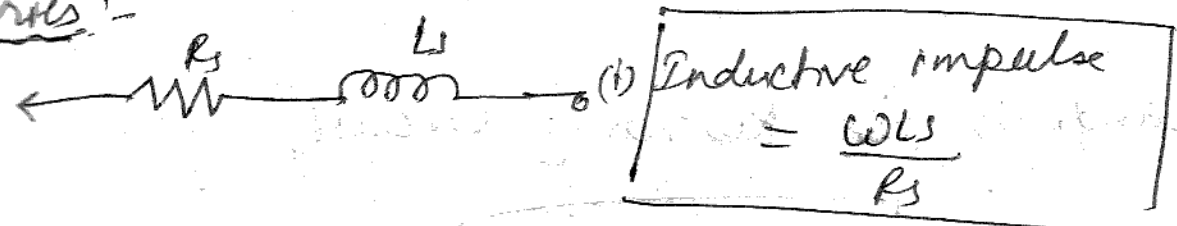

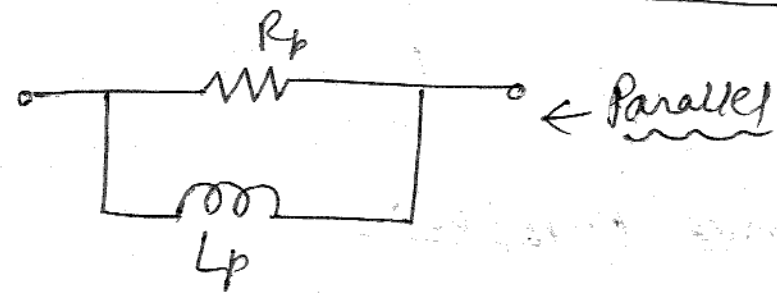(ii) Inductive admittance = $\frac{R_p}{\omega L_p}$




Quality factor, $Q = \frac{1}{D} = \frac{\omega L_s}{R_s} = \frac{R_p}{\omega L_p}$

Loaded Q & unloaded Q.

$Q_u = \frac{\omega L}{R_o}$

$Q_L = \frac{\omega L}{R_c}$

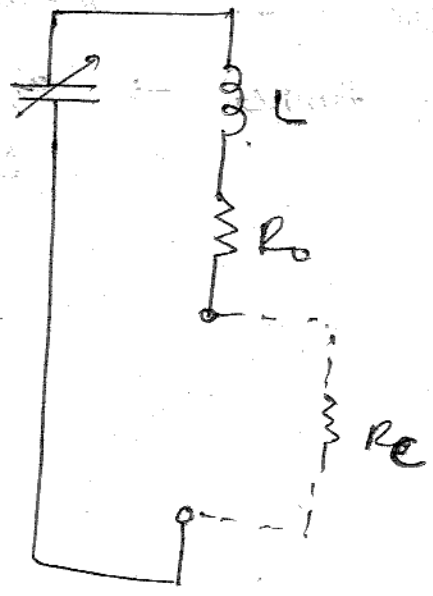

Q factor
resonance

peak voltage

capacitive

f
frequency response

flow

Efficiency for the tanked circuit:

$\eta = \frac{P_{out}}{P_{in}}$

$$\eta = \frac{P_u}{P_u + P_L}$$

Bandwidth for Resonance Circuit,

$$B.W. = \frac{f_r}{Q_L}$$

16/8/4

Types of Tuned Amplifier:



- (i) Single Tuned
- (ii) Double Tuned
- (iii) Stagger Tuned amplifier

Single Tuned \rightarrow 1 tanked ckt

Double " \rightarrow 2 tanked ckt


Stagger Tuned \rightarrow Two single tuned ckt are connected together

Single Tunned Amplifier :-

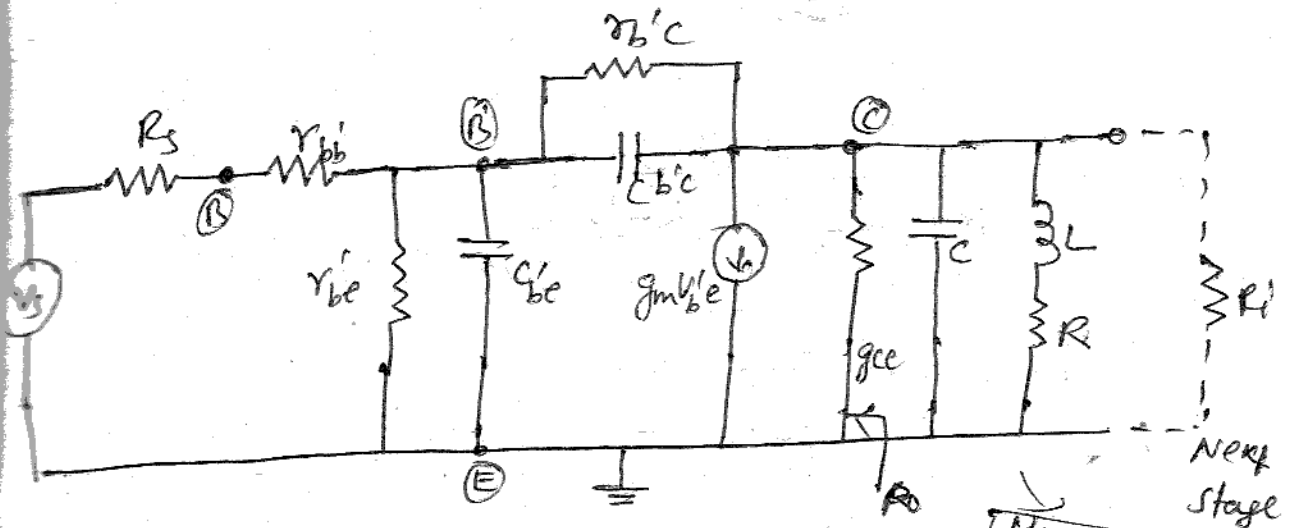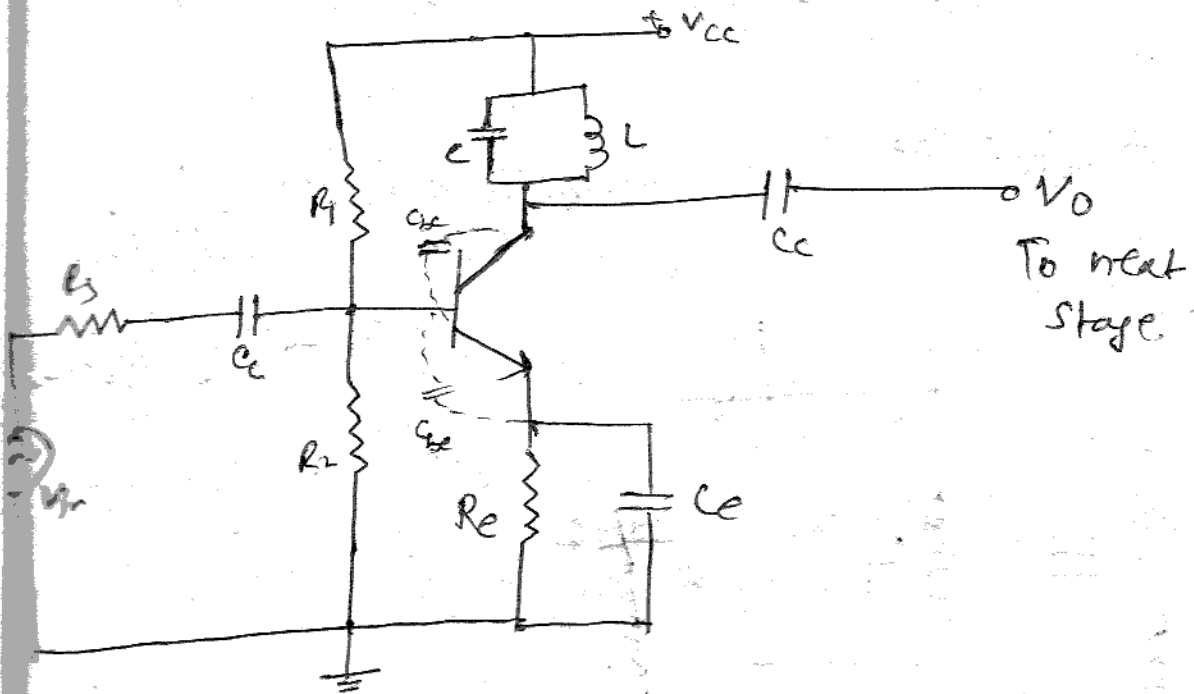

\downarrow
 Pure,
 $g_{ce} = R_0$

Simplified Ckt using millers theorem,

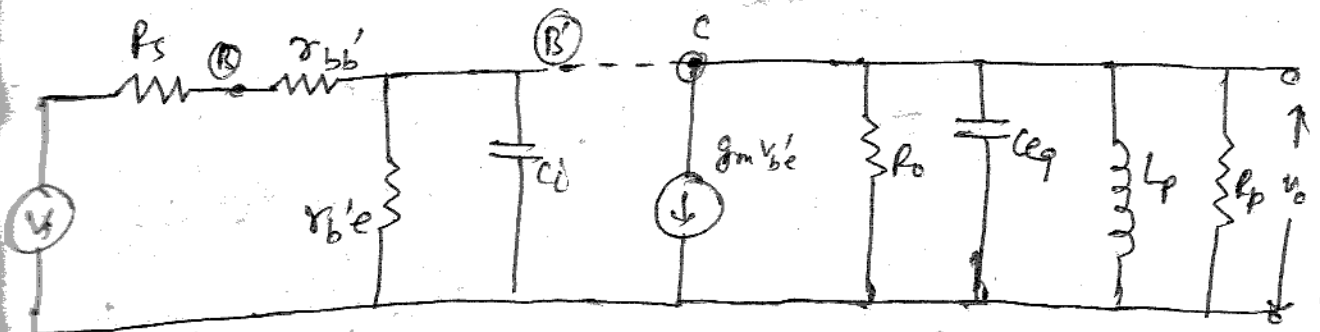


Ckt are

$$C_i = C_{b'e} + C_{b'c}(1-A) \quad \& \quad C_{e'g} = C_{b'c} \left(\frac{A'}{A} \right) + C$$

$$\& \quad g_{ce} = R_o$$

$$\text{Admittance } z, \quad Y = \frac{1}{R + j\omega L}$$
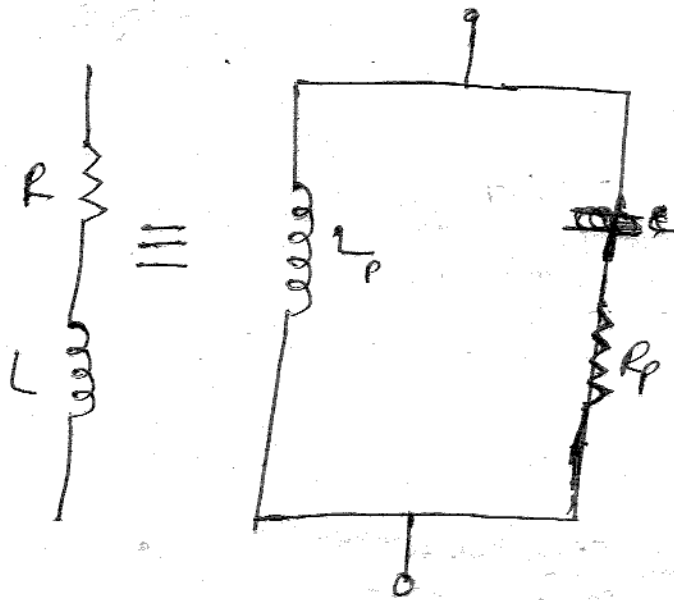
$$\div \text{ '2 x by } (R - j\omega L)$$



$$Y = \frac{1}{R + j\omega L} \times \frac{R - j\omega L}{R - j\omega L}$$

$$Y = \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

$$Y = \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega L}{R^2 + \omega^2 L^2}$$

$$= \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega^2 L}{(R^2 + \omega^2 L^2)\omega}$$

[x & ÷ by ω in 2nd term]

$$= \frac{R}{R^2 + \omega^2 L^2} + \frac{\omega^2 L}{j\omega(R^2 + \omega^2 L^2)}$$

$$\frac{A'}{A} + C$$

$$= \frac{1}{R_p} + \frac{1}{j\omega L_p}$$

where, $R_p = \frac{R^2 + \omega^2 L^2}{R}$

$$L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L}$$

Resonant freq, $f_r = \frac{1}{2\pi \sqrt{L_p C_{equiv}}}$

Quality factor, $Q = \frac{\text{Reactance}}{\text{Resistance}} = \frac{\omega L}{R}$

At resonance,

$$Q_r = \frac{\omega_r L}{R}$$

$$R_p = \frac{R^2 + \omega^2 L^2}{R} = R + \frac{\omega^2 L^2}{R}$$

Here neglect $R \because R \ll \frac{\omega^2 L^2}{R}$

$$R_p = \frac{\omega^2 L^2}{R}$$

$$L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L} = \frac{R^2}{\omega^2 L} + L$$


Since $\omega^2 L$ is higher, and in denominator.

So, neglecting, $\frac{R^2}{\omega^2 L}$ in above eqⁿ

$$L_p \equiv L$$


$$R_p =$$

18/8/11

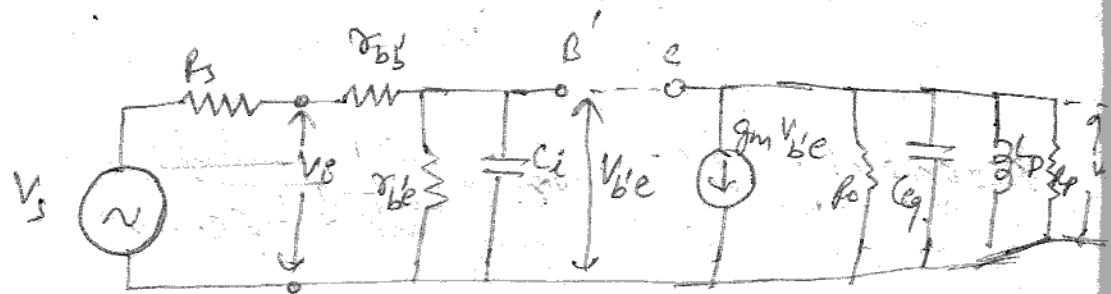

Hybrid model of single tuned amplifier

O/P
equiv. circ

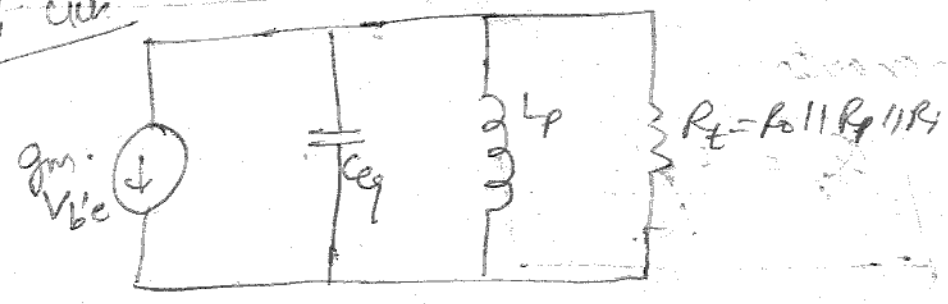

Effective Q-factor, Q_{eff} is susceptance of L or C

Conductance of shunt resistance R_L

~~Voltage gain~~

$$Q_{eff} = \frac{1}{\omega L} \cdot \frac{1}{R_L}$$

for inductance

$$Q_{eff} = \frac{R_L}{\omega L}$$

at resonance freq, $Q_{eff} \equiv \frac{R_L}{\omega L}$

for capacitance,

$$R_{eff} = \frac{R_t}{\omega_r C}$$

$$R_{eff} = \frac{1/\omega_r C}{1/R_t} = \frac{\omega_r C}{1/R_t} = \omega_r C R_t$$

Voltage gain -

$$A_v = \frac{V_o}{V_i}$$

$$\Rightarrow V_o = g_m V_{be} \times R_t$$

Admittance

$$V_o = g_m V_{be} Z$$

$$\text{Admittance } Y = \frac{1}{Z} = \frac{1}{C_{eq}} + \frac{1}{L_p} + \frac{1}{R_t}$$

$$Y = \frac{1}{j\omega C_{eq}} + \frac{1}{j\omega L_p} + \frac{1}{R_t}$$

$$Y = j\omega C_{eq} + \frac{1}{j\omega L_p} + \frac{1}{R_t}$$

$$Y = \frac{1}{R_t} \left[j R_t \omega C_{eq} + \frac{R_t}{j\omega L_p} + 1 \right]$$

$$= \frac{1}{R_t} \left[\frac{j\omega \cdot \omega_r R_t C_{eq}}{\omega_r} + \frac{\omega_r R_t}{j\omega_r \omega L_p} + \frac{\omega_r}{\omega_r} \right]$$

$$= \frac{1}{R_t} \left[1 + \frac{j\omega_r}{\omega} \cdot R_{eff} + \frac{j\omega}{\omega_r} \cdot R_{eff} \right]$$

$$= \frac{1}{R_t} \left[1 + Q_{eff} \left(\frac{j\omega_r}{\omega} + j \frac{\omega}{\omega_r} \right) \right]$$

$$= \frac{1}{R_t} \left[1 + Q_{eff} \left(\frac{\omega_r^2 + \omega^2}{\omega \cdot \omega_r} \right) \right]$$

$$= \frac{1}{R_t} \left[1 + Q_{eff} \left(\frac{\omega_r}{\omega} - \frac{\omega}{\omega_r} \right) \right]$$

$$= \frac{1}{R_t} \left[1 + j Q_{eff} \left(\frac{\omega}{\omega_r} - \frac{\omega_r}{\omega} \right) \right] \quad \text{--- (1)}$$

Variation in resonant freq,

$$\delta = \frac{\omega_r - \omega}{\omega_r} = \frac{\omega - \omega_r}{\omega_r}$$

$$\delta = \frac{\omega}{\omega_r} - 1$$

$$\Rightarrow \frac{\omega}{\omega_r} = \delta + 1 \quad \text{Sub in (1)}$$

\Rightarrow

$$Y = \frac{1}{R_t} \left[1 + j Q_{eff} \left(\delta + 1 - \frac{1}{\delta + 1} \right) \right]$$

$$= \frac{1}{R_t} \left[1 + j Q_{eff} \left(\frac{(\delta + 1)^2 - 1}{\delta + 1} \right) \right]$$

$$= \frac{1}{R_t} \left[1 + j Q_{eff} \left(\frac{\delta^2 + 1 + 2\delta - 1}{\delta + 1} \right) \right]$$

$$= \frac{1}{R_t} \left[1 + j Q_{\text{eff}} \left(\frac{s^2 + 2\delta}{s+1} \right) \right]$$

$$Y = \frac{1}{R_t} \left[1 + j Q_{\text{eff}} \frac{\delta (s+2)}{(s+1)} \right]$$

$$Y = \frac{1}{R_t} \left[1 + j Q_{\text{eff}} \frac{(s^2 + 2\delta)}{(s+1)} \right]$$

$$Z = \frac{R_t}{1 + j Q_{\text{eff}} \left(\frac{s^2 + 2\delta}{s+1} \right)}$$

$$Z = \frac{R_t}{1 + j Q_{\text{eff}} \frac{2\delta \left(\frac{s+1}{2} \right)}{s+1}}$$

assuming variation is very less

so neglect $\left(\frac{s+1}{2} \right)$ & $(s+1)$

$$\text{So, } Z = \frac{R_t}{1 + j Q_{\text{eff}} 2\delta}$$

do, at, resonant freq. $\omega_c = \omega_r$

\Rightarrow so C, L & L is cancelled

$$\Rightarrow Z = R_t$$

$$V_o = g_m V_{b'e} Z$$

$$V_o = g_m V_{b'e} R_t$$

at resonant.

$$Z = R_t$$

$$V_{b'e} = \frac{V_o r_{b'e}}{r_{b'b'} + r_{b'e}}$$

By voltage divider rule

$$\therefore V_o = g_m V_{b'e} Z$$

$$= g_m \frac{V_i r_{b'e}}{r_{b'b'} + r_{b'e}} Z$$

$$V_o = \frac{g_m V_i r_{b'e}}{r_{b'b'} + r_{b'e}} \cdot \frac{R_t}{1 + j 2\pi f C_{eff}}$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m r_{b'e} \times R_t}{(r_{b'b'} + r_{b'e})(1 + j 2\pi f C_{eff})}$$

At resonant freq,

$$(A_v)_{at\ res} = \frac{V_o}{V_i} = \frac{-g_m r_{b'e} R_t}{(r_{b'b'} + r_{b'e})}$$

at res
 $Z = R_t$

$$\boxed{\frac{A_v}{(A_v)_{reson}} = \frac{1}{1 + j 2\delta \theta_{eff}}}$$

$$\left| \frac{A_v}{(A_v)_{reson}} \right| = \frac{1}{\sqrt{1^2 + (2\delta \theta_{eff})^2}}$$

$$\boxed{\left| \frac{A_v}{(A_v)_{res}} \right| = \frac{1}{\sqrt{1 + 4\delta^2 \theta_{eff}^2}}}$$

$$\angle \frac{A_v}{(A_v)_{res}} = -\tan^{-1} \frac{2\delta \theta_{eff}}{1}$$

$$\boxed{\phi = -\tan^{-1}(2\delta \theta_{eff})}$$

At f_L , freq drops by 3dB, so

$$\left| \frac{A_v}{(A_v)_{reson}} \right| = \frac{1}{\sqrt{1 + (2\delta \theta_{eff})^2}} = \frac{1}{\sqrt{2}}$$

Square both sides.

$$3dB = 0.707 = \frac{1}{\sqrt{2}}$$

$$1 + (2\delta \theta_{eff})^2 = 2$$

$$2\delta \theta_{eff} (2\delta \theta_{eff})^2 = 1$$

$$\Rightarrow \underline{\underline{\delta = \frac{1}{\sqrt{2\theta_{eff}}}}}$$

$$\Rightarrow 2\delta \theta_{eff} = 1$$

t.
R_o

Alloy
den
le

eff)

res
= k_t

$$\Rightarrow \boxed{f = \frac{1}{2 \ell_{\text{eff}}}}$$

$$\text{B.W} = \omega_2 - \omega_1$$

$$\Delta \omega = (\omega_2 - \omega_r) + (\omega_r - \omega_1)$$

~~*~~ multiply & div by ω_r

$$\Delta \omega = \left(\frac{\omega_2 - \omega_r}{\omega_r} + \frac{\omega_r - \omega_1}{\omega_r} \right) \omega_r$$

$$\Rightarrow \Delta \omega = (f + f) \omega_r$$

$$\Delta \omega = 2 f \omega_r$$

$$\text{sub } f = \frac{1}{2 \ell_{\text{eff}}}$$

$$\Delta \omega = 2 \times \frac{1}{2 \ell_{\text{eff}}} \times \omega_r = \frac{\omega_r}{\ell_{\text{eff}}}$$

$$\Delta \omega = \frac{\omega_r}{\omega_r \ell_{\text{eff}} R_t} = \frac{1}{R_t \ell_{\text{eff}}}$$

$$\boxed{\Delta f = \frac{1}{2\pi \ell_{\text{eff}} R_t}}$$

$$\Delta \omega = \frac{\omega_r}{R_t / \omega_r L} = \frac{\omega_r^2 L}{R_t}$$

$$\boxed{\Delta f = \frac{\omega^2 L}{2\pi R_t}}$$

$$\boxed{\Delta f = \frac{f_r}{Q_{eff}}} \quad \leftarrow \text{Bandwidth} = \frac{f_r}{Q_{eff}}$$

9/8/11

Effect of Cascading Single Tuned Amplifier
on B.W.

→ to have high overall gain

$$\left| \frac{A_v}{A_{v(\text{resonance})}} \right| = \frac{1}{\sqrt{1 + (2sQ_{eff})^2}}$$

Relative gain for n-stage cascaded amplifier,

$$\left| \frac{A_v}{A_{v(\text{resonance})}} \right|^n = \left[\frac{1}{\sqrt{1 + (2sQ_{eff})^2}} \right]^n = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \frac{1}{[1 + (2sQ_{eff})^2]^{n/2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow [1 + (2sQ_{eff})^2]^{n/2} = (2)^{1/2}$$

$$\Rightarrow [1 + (2sQ_{eff})^2]^{n/2} = (2)^{1/2}$$

$$\Rightarrow \frac{1}{[1 + (2sQ_{eff})^2]}$$

$$\frac{1}{1 + 2(sQ_{eff})^2}$$

$$\Rightarrow 1 + (2sQ_{eff})^2 = 2^{1/n}$$

$$(2\delta B_{eff})^2 = 2^{1/m} - 1$$

$$\Rightarrow 2\delta B_{eff} = \pm \sqrt{2^{1/m} - 1}$$

$$\Rightarrow 2\delta B_{eff} = \pm \sqrt{2^{1/m} - 1}$$

Sub, $\delta = \frac{\omega - \omega_r}{\omega_r} = \frac{f - f_r}{f_r}$


$$\Rightarrow 2 \frac{\omega - \omega_r}{\omega_r} B_{eff} = \pm \sqrt{2^{1/m} - 1}$$

$$\Rightarrow 2 \frac{f - f_r}{f_r} \cdot B_{eff} = \pm \sqrt{2^{1/m} - 1}$$

$$\Rightarrow \frac{f - f_r}{f_r} = \pm \frac{\sqrt{2^{1/m} - 1}}{2 B_{eff}} \quad \text{--- (3)}$$

$f_1 \rightarrow$ lower cut off frequency

$f_2 \rightarrow$ higher cut off freq.

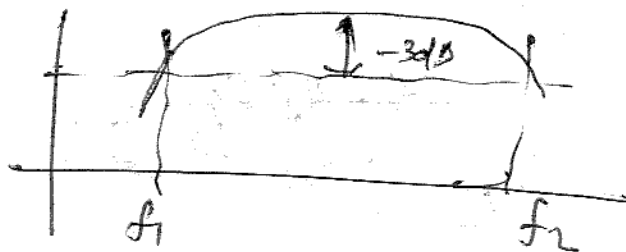

at lower cut off freq, eqn (3) becomes

$$f_1 - f_r = \pm \frac{f_r \sqrt{2^{1/m} - 1}}{2 Q_{eff}}$$

at higher cut off freq.

$$f_2 - f_r = \pm \frac{f_r \sqrt{2^{1/m} - 1}}{2 Q_{eff}}$$

$$\text{Bandwidth} = f_2 - f_1$$

$$= (f_2 - f_r) + (f_r - f_1)$$

$$= \pm \frac{f_r \sqrt{2^{1/m} - 1}}{2 Q_{eff}} + \pm \frac{f_r \sqrt{2^{1/m} - 1}}{2 Q_{eff}}$$

$$= \pm \frac{2 f_r \sqrt{2^{1/m} - 1}}{2 Q_{eff}}$$

$$= \pm \frac{f_r \sqrt{2^{1/m} - 1}}{Q_{eff}}$$


$$\text{B.W} = \pm \frac{f_r \sqrt{2^{1/m} - 1}}{Q_{eff}}$$


(3)

f_r
 B_{eff} = Bandwidth of Single tuned amplifier

$$BW_n = BW_1 \sqrt{2^{1/n} - 1}$$

CLASS C Tunned Amplifier

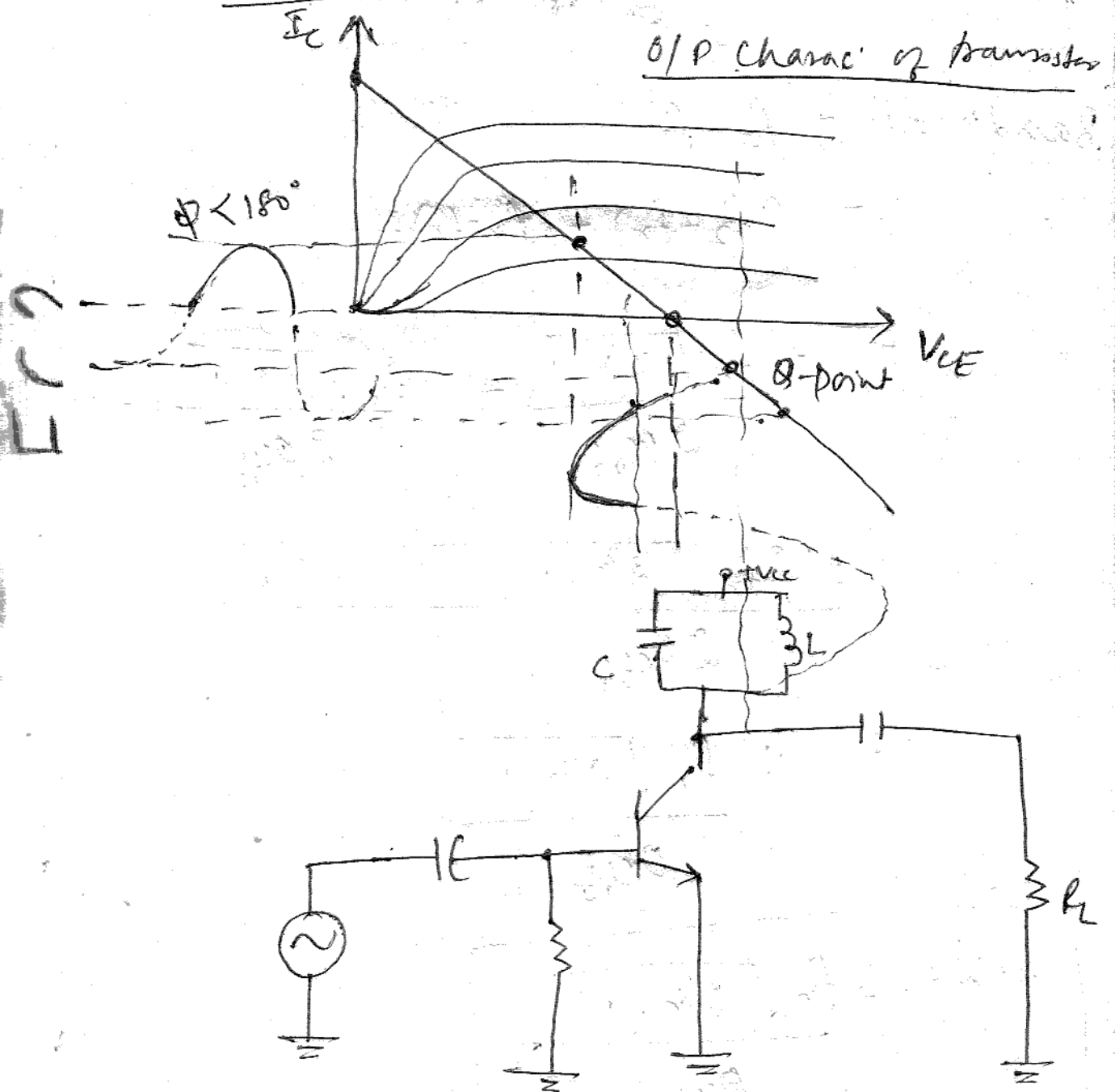

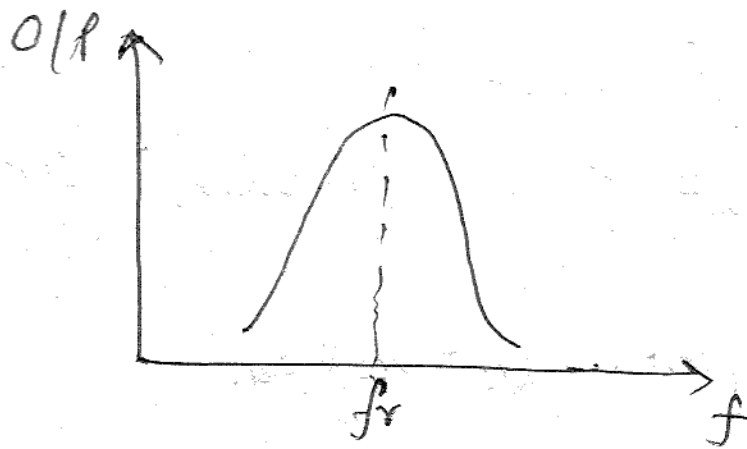


$$f = \frac{1}{2\pi\sqrt{LC}}, \quad \text{Power gain} = \frac{P_{out}}{P_{in}}$$

$$P_{out} = \frac{V_{rms}^2}{R_L}; \quad V_{rms} = \frac{V_{pp}}{2\sqrt{2}}$$

$$P_{out} = \frac{(V_{pp}/2\sqrt{2})^2}{R_L} = \frac{V_{pp}^2}{8R_L}$$

Ac Collector Resistance
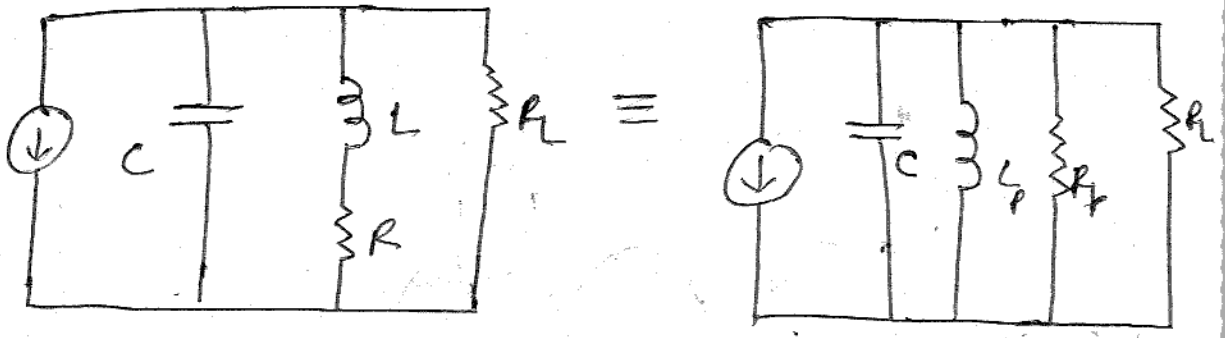
$$Q = \frac{X_L}{R} = \frac{\omega_r L}{R}$$



$$R_p = Q^2 \omega_r L$$

$$r_c = R_p || R_L \Rightarrow \text{ac Collector Resist.}$$

$$Q = \frac{r_c}{\omega_r L}$$

Power dissipation :-

$$(V_{pp})_{max} = 2V_{cc}, \quad P_{(max)} = \frac{V_{pp}^2}{40\%}$$

Dc i/p power, $P_{dc} = V_{cc} \times I_{dc}$

$$\Rightarrow \eta = \frac{P_{out}}{P_{dc}} = \frac{P_{out}}{V_{cc} \times I_{dc}}$$


$$B.W = f_2 - f_1 = \frac{f_r}{Q}$$

22/10/11
Double
tuned
Amplifier

23/8/11


Stagger tuned Amplifier

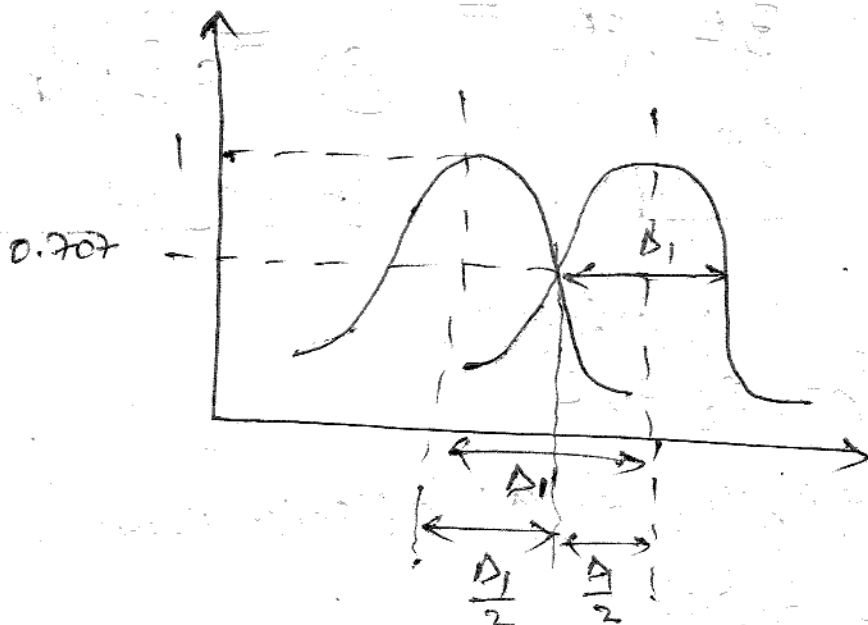→ Resonant frequency are spaced separated equal to Bandwidth.



Response of individual stages

2
p max
40%

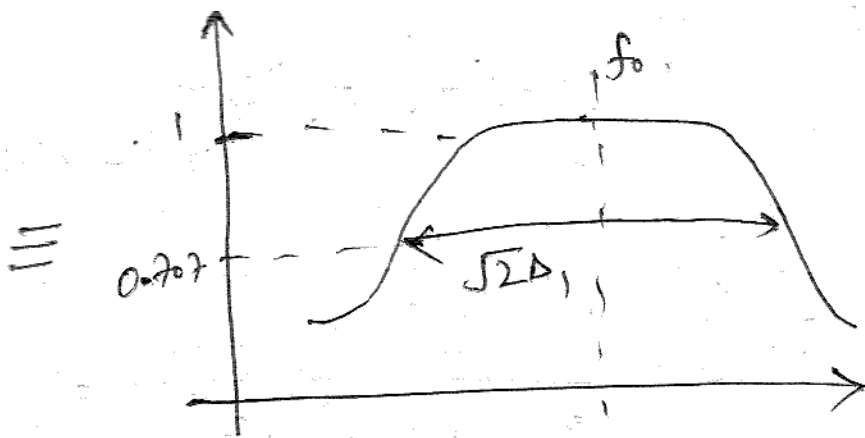

Overall response of staggered pair,

1/4
le
red
paper

Analysis:-

$$\frac{A_v}{A_v(\text{resonance})} = \frac{1}{1 + 2j\delta\omega} = \frac{1}{1 + jX}$$

$$f_{m1} = f_r + \delta \quad \& \quad f_{m2} = f_r - \delta$$

$$\frac{A_v}{A_v(\text{reso})_1} = \frac{1}{1 + j(X+1)} \quad \& \quad \frac{A_v}{A_v(\text{reso})_2} = \frac{1}{1 + j(X-1)}$$

$$\frac{A_v}{A_v(\text{cascaded})} = \frac{A_v}{A_v(\text{reso})_1} \times \frac{A_v}{A_v(\text{reso})_2}$$

$$= \frac{1}{1 + j(X+1)} \times \frac{1}{1 + j(X-1)}$$

$$= \frac{1}{[1 + j(X+1)][1 + j(X-1)]}$$

$$= \frac{1}{[1 + jX + j][1 + jX - j]}$$

$$= \frac{1}{(1+j\omega - j + j\omega - \omega^2 + \omega + j\omega - \omega + 1)}$$

$$\frac{A_v}{A_v(\text{cascaded})} = \frac{1}{2 + 2j\omega - \omega^2}$$

~~Instability of tuned Amplifier & Neutral~~

Separately real & imaginary parts, we get.

FCO

$$\frac{A_v}{A_v(\text{cascaded})} = \frac{1}{(2 - \omega^2) + 2j\omega}$$

$$\left| \frac{A_v}{A_v(\text{cascaded})} \right| = \frac{1}{\sqrt{(2 - \omega^2)^2 + 4\omega^2}}$$

$$= \frac{1}{\sqrt{4 + \omega^4 - 4\omega^2 + 4\omega^2}} = \frac{1}{\sqrt{\omega^4 + 4}}$$

$$\left| \frac{A_v}{A_v(\text{cascaded})} \right| = \frac{1}{\sqrt{x^4 + 4}}$$

$$x = 280 \text{eff}$$


$$\left| \frac{A_v}{A_v(\text{cascaded})} \right| = \frac{1}{\sqrt{(280 \text{eff})^4 + 4}}$$

$$= \frac{1}{\sqrt{16 \cdot 8^4 \cdot \text{eff}^4 + 4}}$$

$$= \frac{1}{2 \sqrt{(4 \cdot 8^4 \cdot \text{eff}^4 + 1)}}$$

Instability of tuned Amplifier & Neutralization techniques

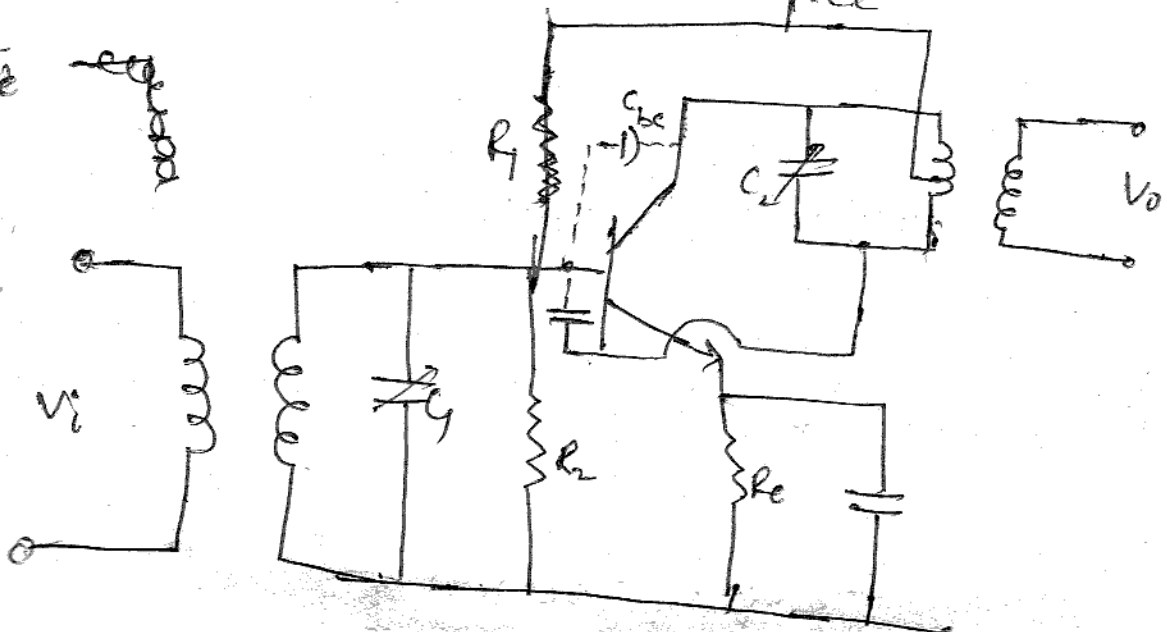⇒ resonant freq o/p voltage is not stable.



Neutralization technique

(i)

(ii) Neurodysme

FC9

