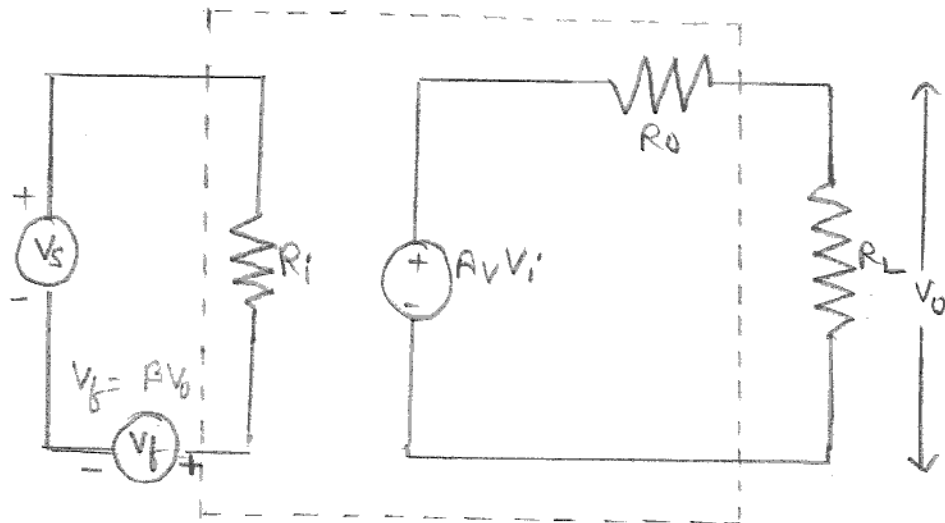


# Voltage Series Feedback Amplifier

## Input Resistance



The voltage series feedback topology with amplifier is replaced by Thevenin's model and  $A_v$  represents the open circuit voltage gain taking  $R_s$  into account

I/P resistance with f/b

$$R_{if} = \frac{V_s}{I_i} \quad \text{--- (1)}$$

Applying KVL to the i/p side

$$\begin{aligned} V_s &= I_i R_i + V_f \\ &= I_i R_i + \beta V_o \end{aligned}$$

o/p voltage  $V_o$  is given as

$$V_o = \frac{A_v V_i R_L}{R_o + R_L}$$
$$= A_v I_i R_i$$
$$V_o = A_v V_i \quad \text{--- (3)}$$

where,

$A_v$  = open ckt voltage gain without feedback.  
= voltage gain with f/b with  $R_L$  into account.

Sub  $V_o$  from eq<sup>n</sup> (3) in eq<sup>n</sup> (2)

$$V_s = I_i R_i + \beta V_o$$

$$V_s = I_i R_i + \beta A_v V_i$$

$$= V_i + \beta A_v V_i$$

$$= V_i (1 + \beta A_v)$$

$$V_s = I_i R_i (1 + \beta A_v)$$

dividing both sides by  $I_i$

$$\frac{V_s}{I_i} = R_i (1 + \beta A_v)$$


$$\boxed{R_{if} = R_i (1 + \beta A_v)}$$

Here,


$$R_{if} = \frac{V_s}{I_i}$$
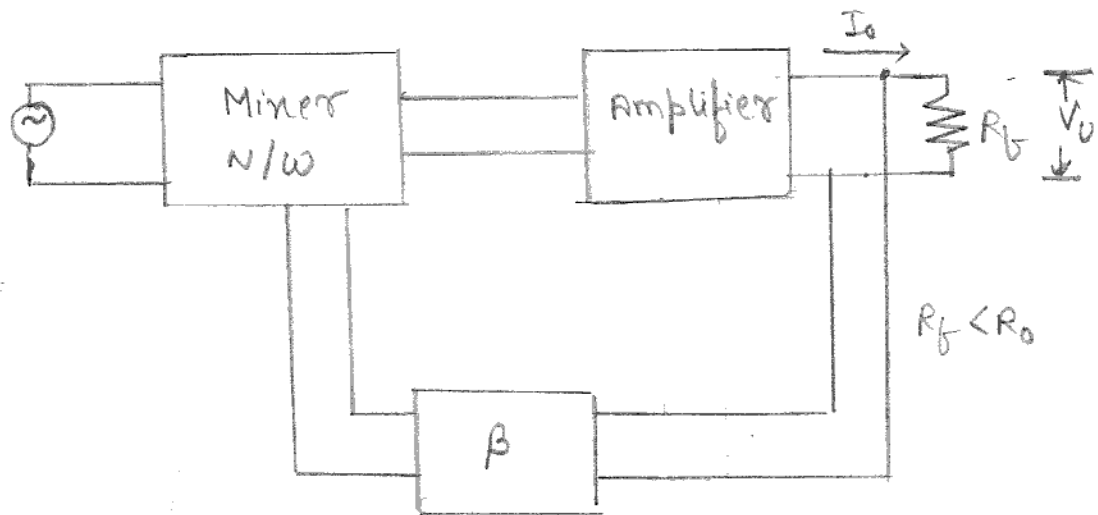
## Output resistance :-

The -ve f/b which samples the o/p voltage regardless of how this o/p signal is return to the i/p



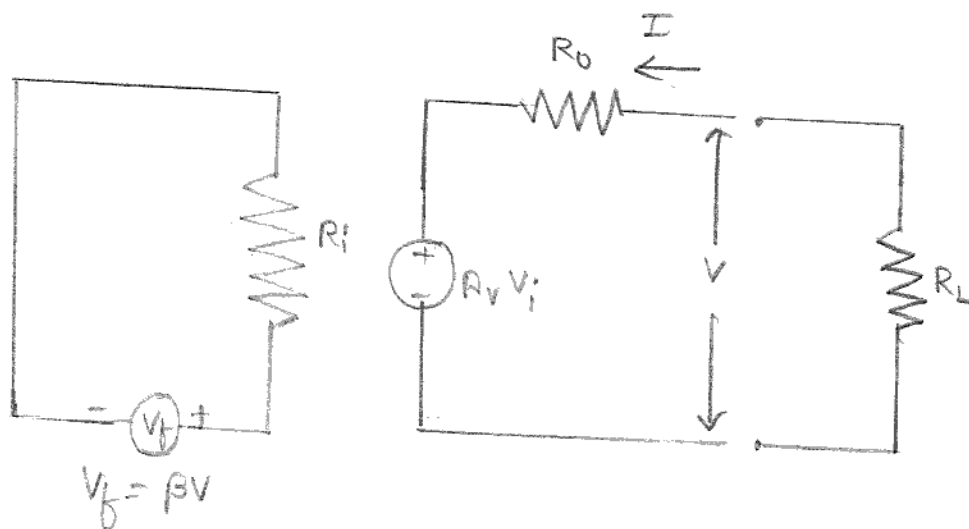In -ve f/b which is used in the f/b amplifier tends to increase the o/p resistance.



In this topology o/p resistance can be measured by shorting the i/p source  $V_s = 0$ . The o/p terminal with  $R_L$  is connected.

Applying KVL to o/p side

$$A_v V_i + I R_o - V = 0$$

$$I R_o = V - A_v V_i$$

$$I = \frac{V - A_v V_i}{R_o} \quad \text{--- (1)}$$

i/p voltage

$$V_i = -V_f = -\beta V \quad \text{--- (2)}$$

Sub.  $V_i$  from eqn (2) to eqn (1)

$$I = \frac{V + A_v \beta V}{R_o}$$

$$I = \frac{V(1 + A_v \beta)}{R_o}$$

$$R_{of} = \frac{V}{I} = \frac{R_o}{1 + A_v \beta}$$

where,

$A_v$  = open loop gain without taking  $R_L$  into account.

$$R_{of}' = R_{of} \parallel R_L$$

$$R_{of}' = \frac{R_{of} R_L}{R_{of} + R_L} \quad \text{--- (3)}$$

Sub  $R_{of}$  in eqn (3)

$$R_{of}' = \frac{\frac{R_o}{1+A_v\beta} R_L}{\frac{R_o}{1+A_v\beta} + R_L}$$

$$R_{of}' = \frac{R_o R_L}{R_o + R_L(1+A_v\beta)}$$

Divide numerator and denominator by  $(R_o + R_L)$

$$R_{of}' = \frac{\frac{R_o R_L}{R_o + R_L}}{\frac{R_o + R_L(1+A_v\beta)}{R_o + R_L}}$$

Put  $\frac{R_o R_L}{R_o + R_L} = R_L'$

&  $\frac{A_v R_L}{R_o + R_L} = A_v$

$$R_{of}' = \frac{R_L'}{1+\beta A_v}$$

Here,

$A_v =$  open loop voltage gain taking  $R_L$  into account.

# Analysing Methodology of feedback Amplifier

## Introduction:-

The analysis of feedback amplifier is very important to accurately model the behaviour of an amplifier. The analysis involves amplifier characteristics, overall gain, return ratio, frequency response, input and output impedance.

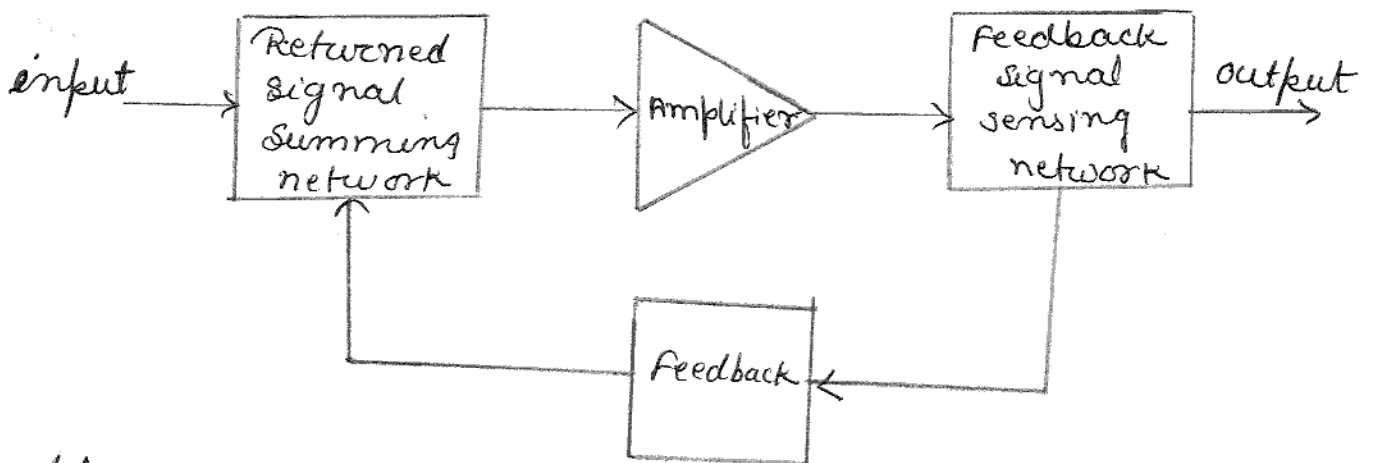


fig :- Ideal block diagram of the feedback system.

It is usually based on modeling the internal amplifier and feedback n/w by two-ports

To analysis the feedback amplifier it is necessary to go through the following steps:-

1) Identify Topology ie type of feedback:-

To find the type of sampling n/w

i) By shorting the o/p i.e.  $V_o = 0$  if feedback signal becomes zero then it is called as voltage shunt sampling.

ii) By opening the o/p loop  $I = 0$  with f/b signal = 0 then it is called as current shunt sampling.

2) To find out the type of mixing signal:-

i) If the feedback signal is subtracted from the externally applied voltage in the input loop, it is called as series mixing.

ii) If the feedback signal is subtracted from the externally applied current in the input loop, it is called as shunt mixing.

3) To find the input circuit :-

i) For voltage sampling make  $V=0$  by shorting the o/p.

ii) For current sampling make  $I=0$  by opening the o/p.

4) To find the o/p circuit :-

i) For series mixing make  $I=0$  by opening the I/P loop.

ii) For shunt mixing make  $V=0$  by shorting the input.

5) Replace each active device by its h-parameter model at low frequency.

6) Find the open loop gain i.e. without feedback of the amplifier.

7) Indicate  $x_f$  and  $x_o$  on the circuit and evaluate  $\beta = \frac{V_f}{V_o} = \frac{x_f}{x_o}$

8) From  $A \text{ \& } \beta$  find  $A_f$  or  $A_m$ ,  $R_{of}$ ,  $R_{if}$  and  $R_{of}'$ .