
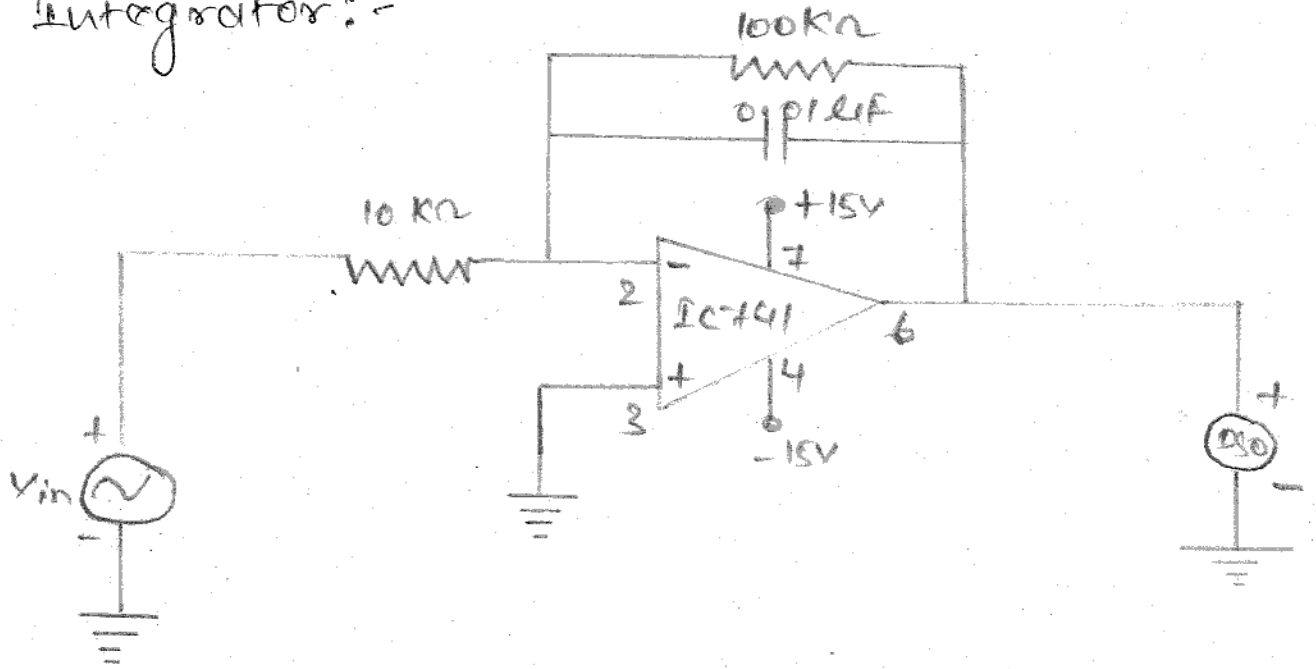


CIRCUIT DIAGRAM

Integrator :-

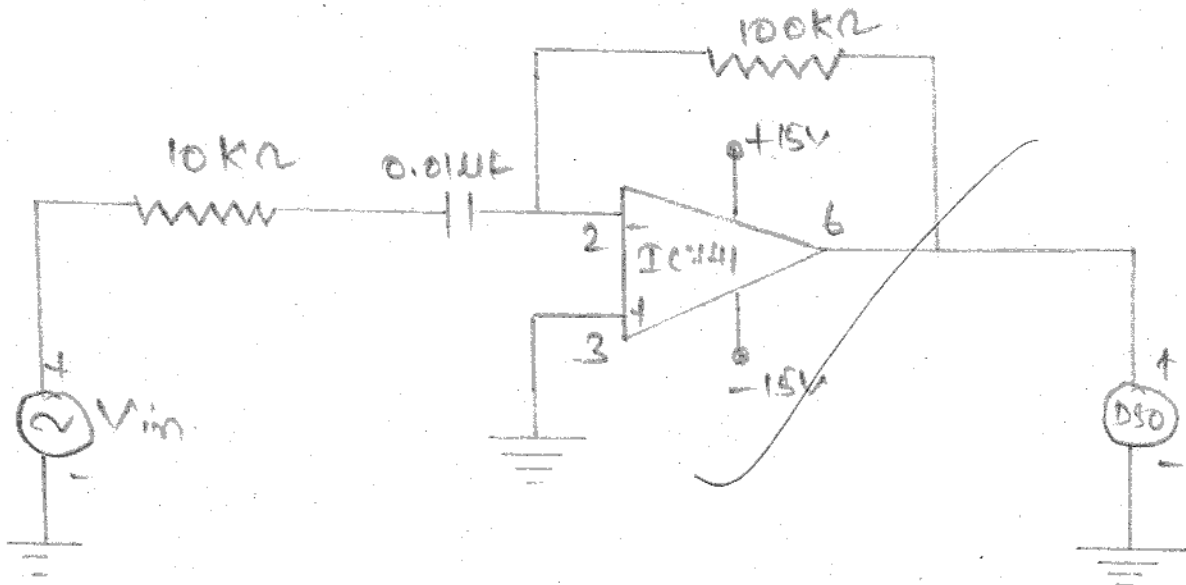

Differentiator :-



Expt No: 2

Date: 15.07.2011

INTEGRATOR AND DIFFERENTIATOR USING OP-AMP


AIM:- To study the operation of integrator and differentiator using operational amplifier

APPARATUS REQUIRED:-

S.No	Components	Range	Quantity
1.	IC 741	—	1
2.	Resistor	10 k Ω	1
		100 k Ω	1
3.	Dual power supply	$\pm 15V$	1
4.	Capacitor	0.01 μF	1
5.	Function generator	—	1
6.	DSO	—	1
7.	Probes	—	2
8.	Connecting wires	—	As reqd.

MODEL GRAPH

Integrator

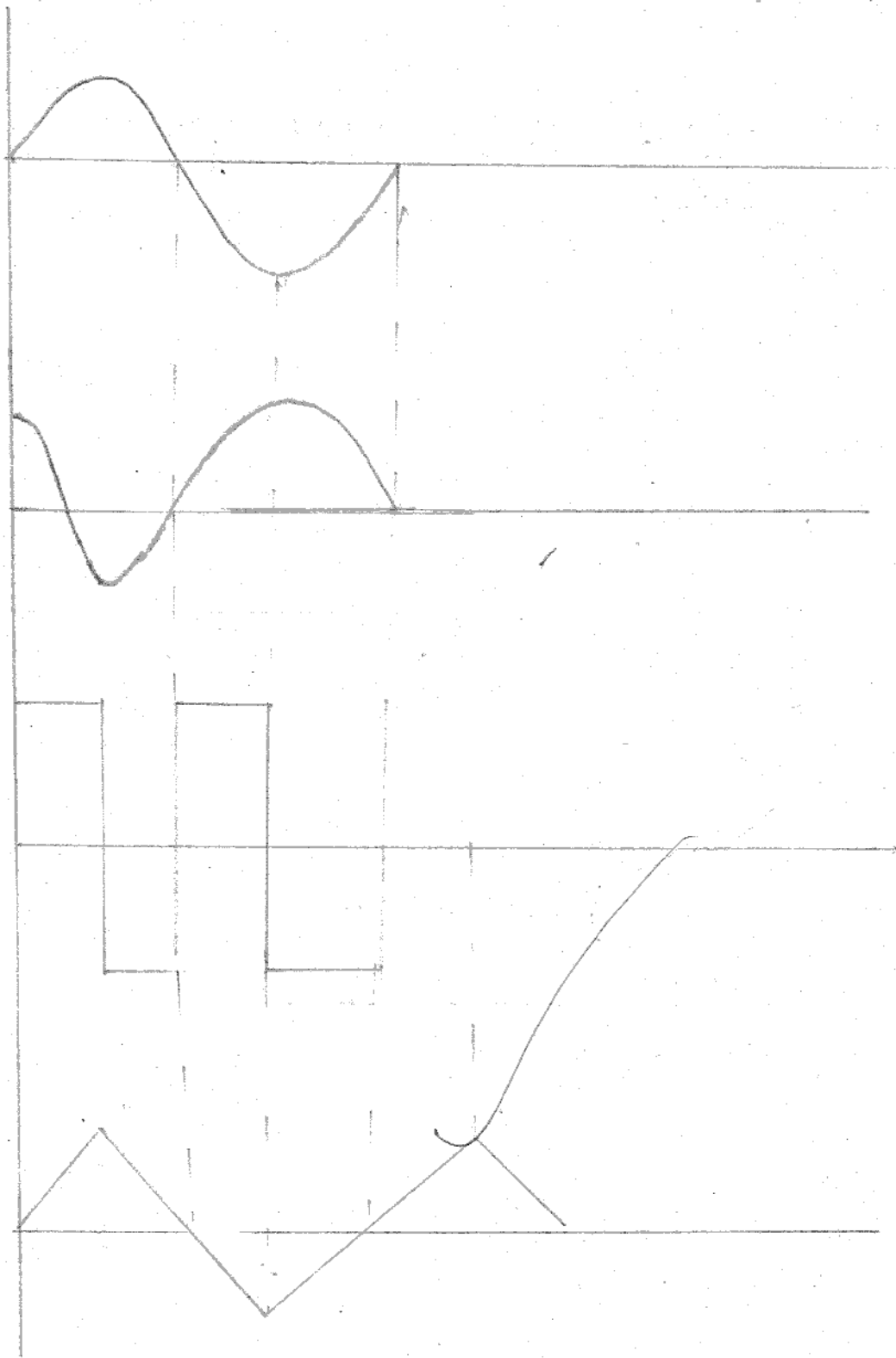

THEORY :-

INTEGRATED AMPLIFIER :- The circuit provides an output voltage which is proportional to the time signal of input. It is the integrated amplifier.

DIFFERENTIATOR :- The differentiator contains capacitor in the simplest circuit of operational amplifier. This circuit performs the mathematical operation of differential [i.e. the output waveform is the derivative of input waveform]

$$V_o = -R_f \left(\frac{C_f}{dt} \right)$$

PROCEDURE :-**INTEGRATOR :-**

→ Connections are given as per the circuit diagram

→ The sine wave input is given from the function generators.

→ The cosine wave output is obtained because of inverting differentiator

→ The square wave input is given and output is triangular wave.


TABULAR COLUMN INTEGRATOR

Waveform	Amplitude (V)		Time (ms)	
	Input	Output	Input	Output
Square wave	1.58V	1.98V	995μs	995μs
Sine wave	1.18V	2.93V	995μs	995μs


DIFFERENTIATOR:

Waveform	Amplitude (V)		Time Period (ms)	
	Input	Output	Input	Output
Sine wave	1.54V	7.52V	1KHz	995Hz
Square wave	14.7V	19.01V	1KHz	995Hz

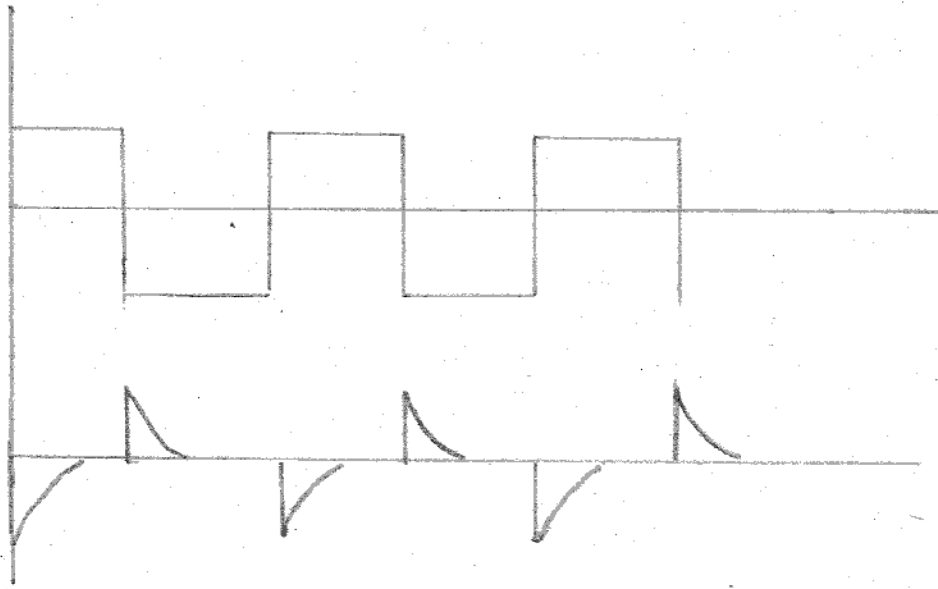a) Input and output for square wave input




b) Input and Output for sine wave input

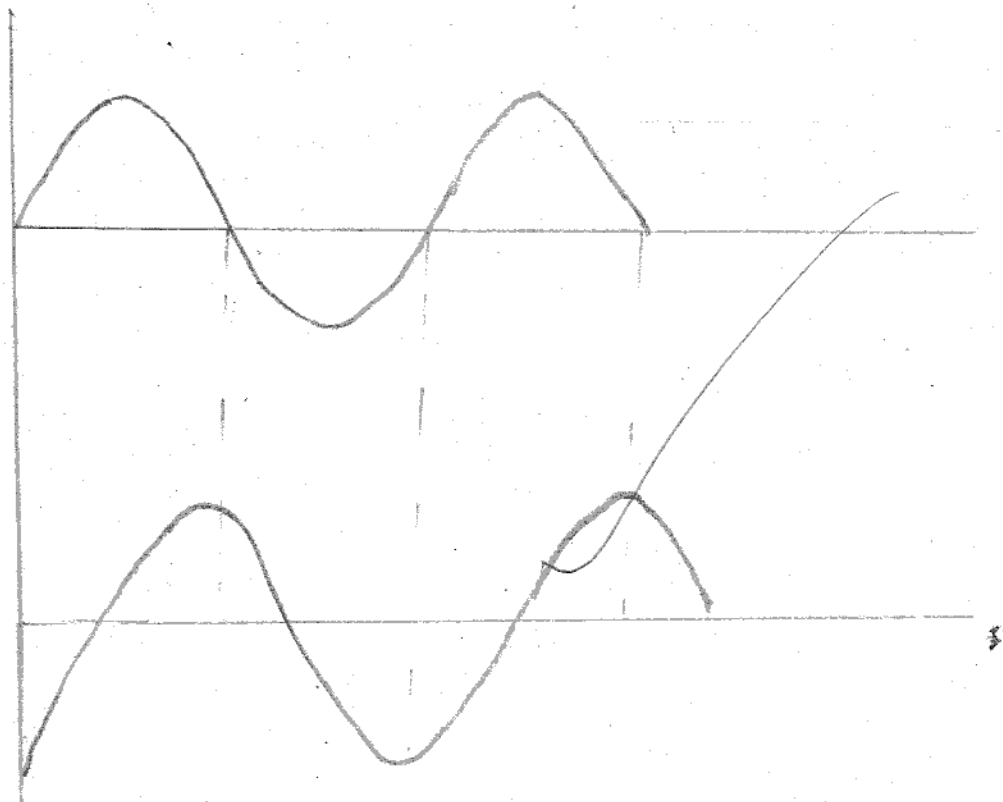


~~Page No. 111~~
*RESULT:-

Thus the study of operation of
Integrator and differentiator using
op-amp has been completed.

Circuit Diagram WITH FEEDBACK

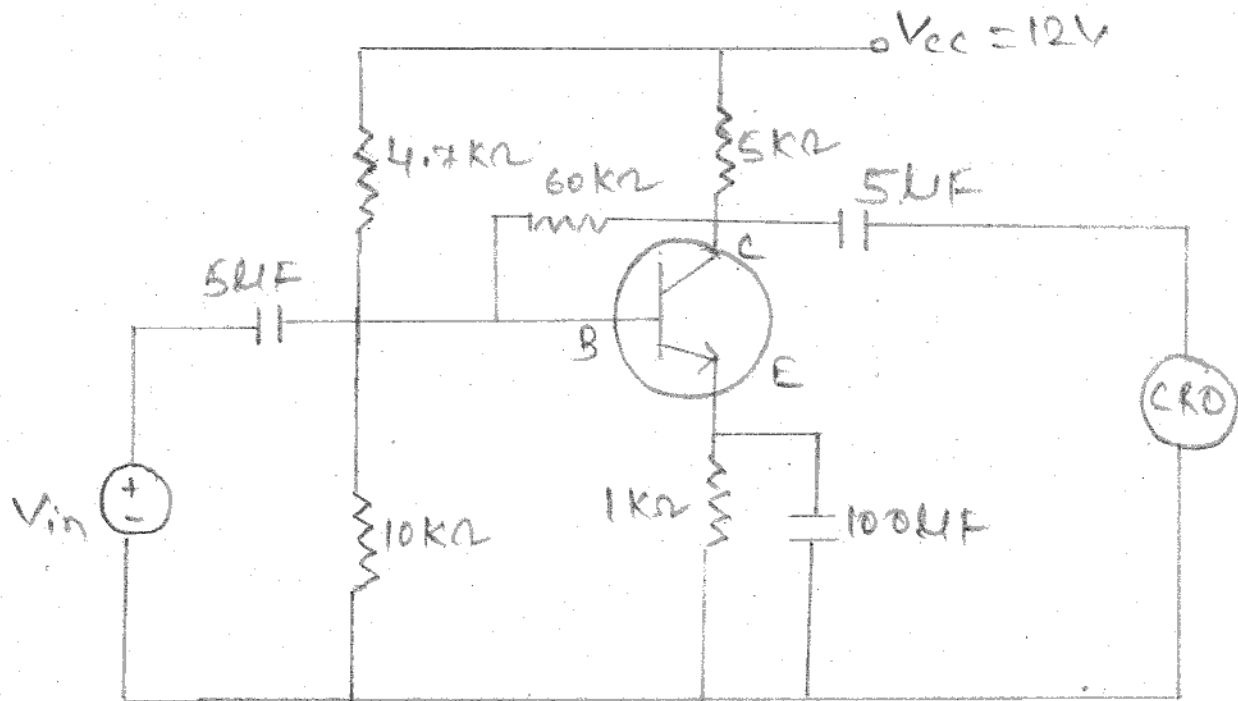

WITHOUT FEEDBACK

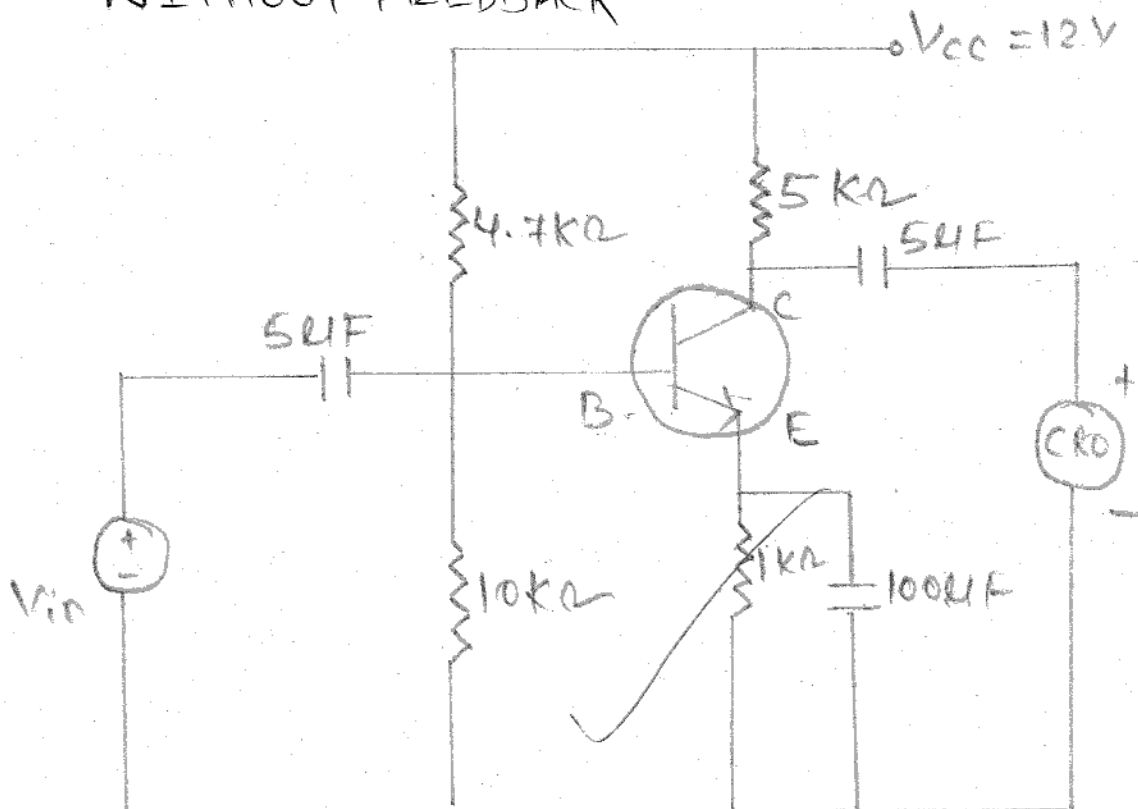

EXPT NO : 5

DATE : 15.7.2011


VOLTAGE SHUNT FEEDBACK AMPLIFIER

AIM:- To design and study frequency response of voltage shunt feedback amplifier

APPARATUS REQUIRED:

S.NO	COMPONENTS	RANGE	QTY.
1.	Resistor	4.7K Ω	1
		5K Ω	1
		1K Ω , 10K Ω	1, 1
		60K Ω	1
2.	Capacitor	5 μ F	2
		100 μ F	1
3.	Transistor	BC 547	1
4.	DSO	(0-30) MHz	1
5.	F.G	(0-30) MHz	1
6.	Power Supply	(0-15) V	1
7.	Bread Board	—	1
8.	Connecting wire	—	As reqd.

MODEL GRAPH

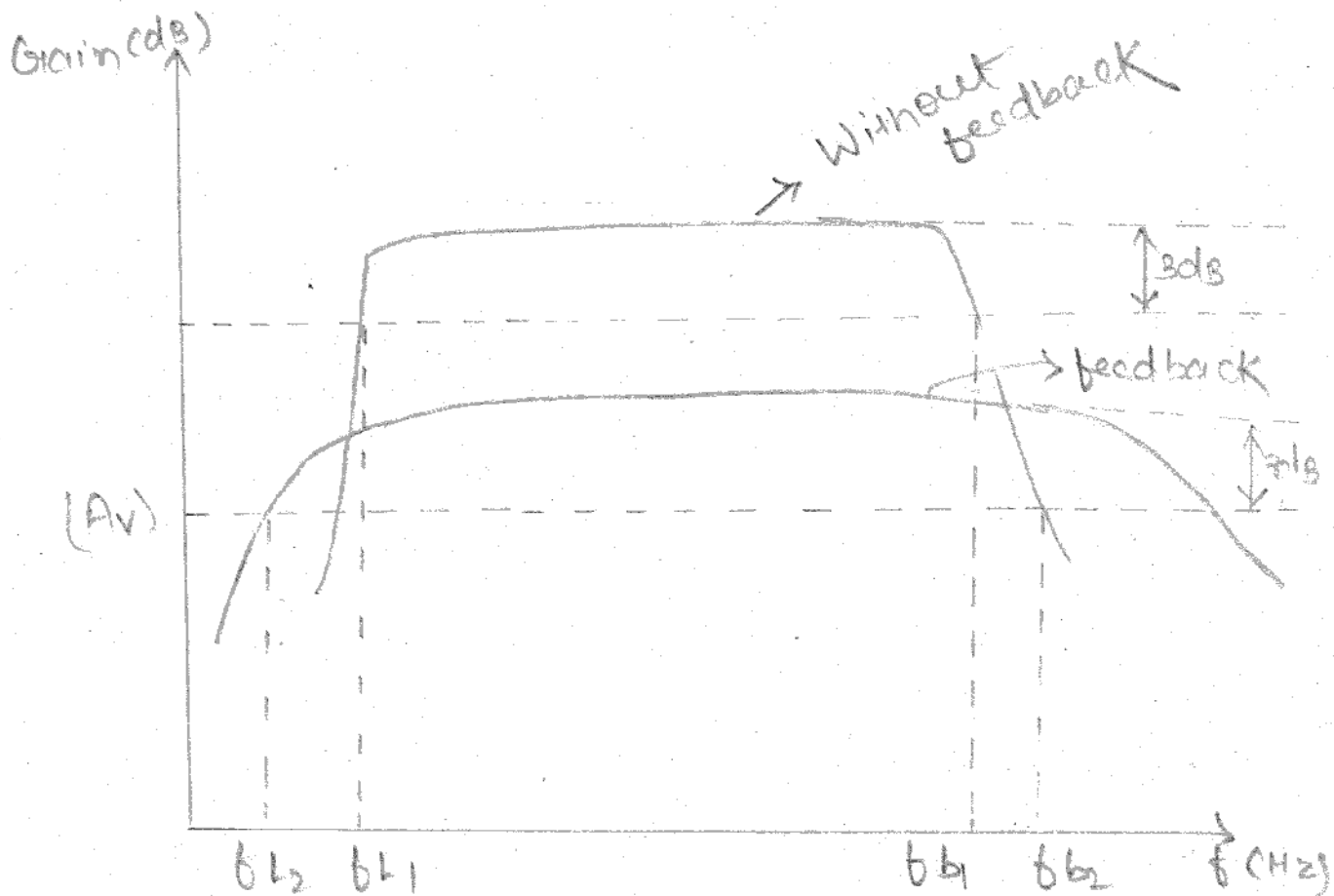

Q. Design Procedure

$$A_{vF} = 100, A_v = 250, V_{CC} = 12\text{V}, I_C = 1\text{mA}$$

(i) Selection of R_C & R_E :-

$$V_{CC} = I_C (R_C + R_E) + V_{CE} \quad (V_{CE} = V_{CC}/2) = 6\text{V}$$

$$R_E + R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{12 - 6}{10^{-3}} = 6\text{k}\Omega$$

$$V_{RE} = I_C \cdot R_E$$

$$V_{RE} = 0.1 \quad V_{CE} = 0.1 \times 12 = 1.2\text{V}$$

$$R_E = \frac{V_{RE}}{I_C} = \frac{1.2}{1\text{mA}} = 1.2\text{k}\Omega$$

THEORY:-

In a feedback amplifiers the output voltage or current is sampled by means of sampling network and this sampled signal is applied to the input through a two port network. Referred as feedback amplifiers.

In a shunt feedback a resistor R_f is placed between collector and R_f is placed between collector and base, the feedback signal is proportional to the output voltage V_o .

PROCEDURE

- ① Connection are given as per the circuit diagram
- ② Set $V_{cc} = 10V$, set input voltage using A.f oscillator
- ③ By varying A.f oscillator take from output frequency oscillator voltage for different frequency.
- ④ Calculate gain in dB
- ⑤ Plot the gain vs frequency curve in Semilog Sheet.

TABULAR COLUMN
With feedback

S.No	Frequency (Hz)	V_o (Volts)	Gain = $20 \log \frac{V_o}{V_{in}}$ (dB)
1	1	1.15	1.21
2	1.5	1.20	1.58
3	2	1.25	1.93
4	2.5	1.50	3.52
5	3	1.50	3.52
6	3.3	1.50	3.52
7	3.8	1.50	3.52
8	4.4	1.50	3.52
9	4.5	1.50	3.52
10	5	1.50	3.52
11	5.5	1.3	2.27
12	6	1.26	2.00
13	6.5	1.25	1.21
14	6.7	1.13	1.06

Choose $R_E = 1k\Omega$, $R_1 + R_2 = 6k\Omega$, $R_C = 6 - 1.2 = 4.8k\Omega$

Choose $R_C = 5k\Omega$

Selection of R_1 and R_2

$$V_{R2} = V_{BE} + I_E R_E = 0.7 + 1.2 \times 1 = 1.9V$$

$$V_{R1} = 12 - 1.9 = 10.1V$$

$$\frac{V_{R1}}{V_{R2}} = \frac{12}{1.9} = 5.3 = \frac{R_1}{R_2}$$

Assume $R_2 = 10k\Omega$

WITHOUT FEEDBACK

S.No	Frequency (Hz)	V_o (Volts)	Gain $= 20 \log \frac{V_o}{V_{in}}$
1.	150	17.03	24.62
2.	160	18.40	25.29
3.	170	19.40	25.75
4.	175	20.20	26.10
5.	180	20.20	26.10
6.	185	20.20	26.10
7.	190	20.20	26.10
8.	195	20.20	26.10
9.	200	20.20	26.10
10.	210	19.8	25.93
11.	215	19.2	25.66
12.	220	18.4	25.29
13.	230	17.3	25.00

$R_1 = 5.3 \times 10 = 53 \text{ k}\Omega$ Choose $R_1 = 47 \text{ k}\Omega$

Selection Capacitance C_E

$V_{cc} < 0.1 R_E$

$\frac{1}{2\pi f C_E} \leq 0.1 R_E$

$C_E > \frac{1}{2 \times 3.14 \times 10.1 \times 10^3} \quad C_E > 31.81 \mu\text{F}$

Assume C_f and $C_c = 5 \mu\text{F}$

Selection of R_E :-

$A_{vB} = -\frac{R_E}{R_S} \quad R_S = 600 \Omega$

$R_E = R_S \times A_{vB} = 600 \times 100 = 60 \text{ k}\Omega$

~~Ref~~
22/11
RESULT:-


The voltage shunt feedback amplifier is designed and studied its performance

$$\text{B.W without feedback} = 3.5 \text{ KHZ}$$


$$\text{B.W with feedback} = 5.6 \text{ KHZ}$$

Circuit diagram:-

LOW PASS FILTER:-

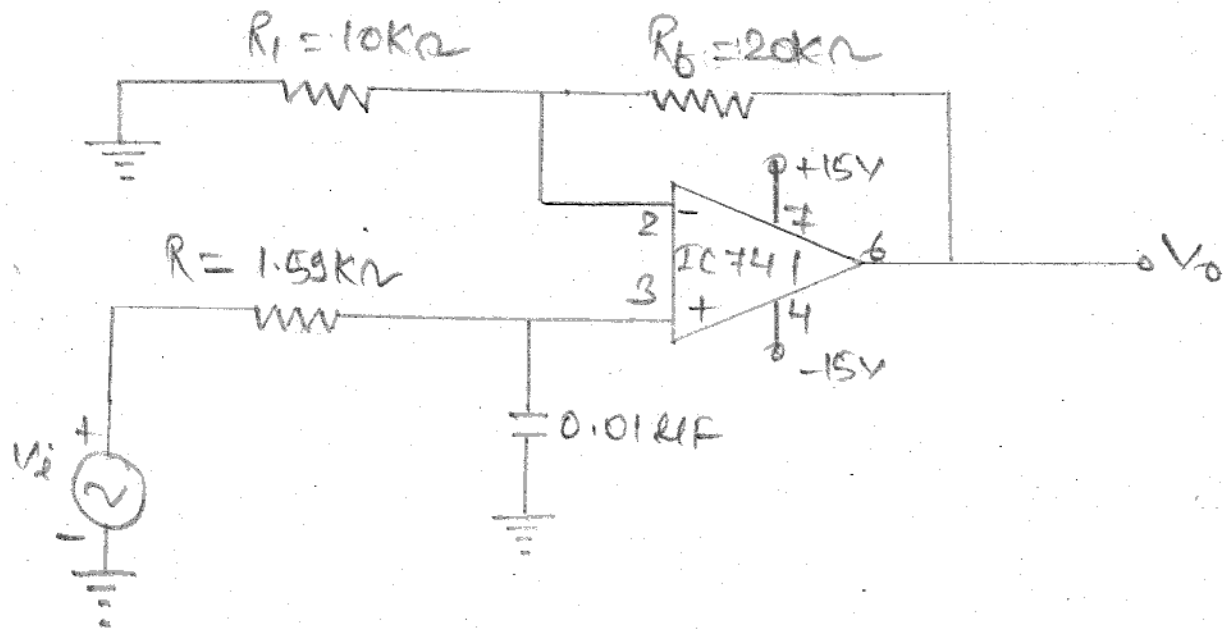

BAND PASS FILTER:-

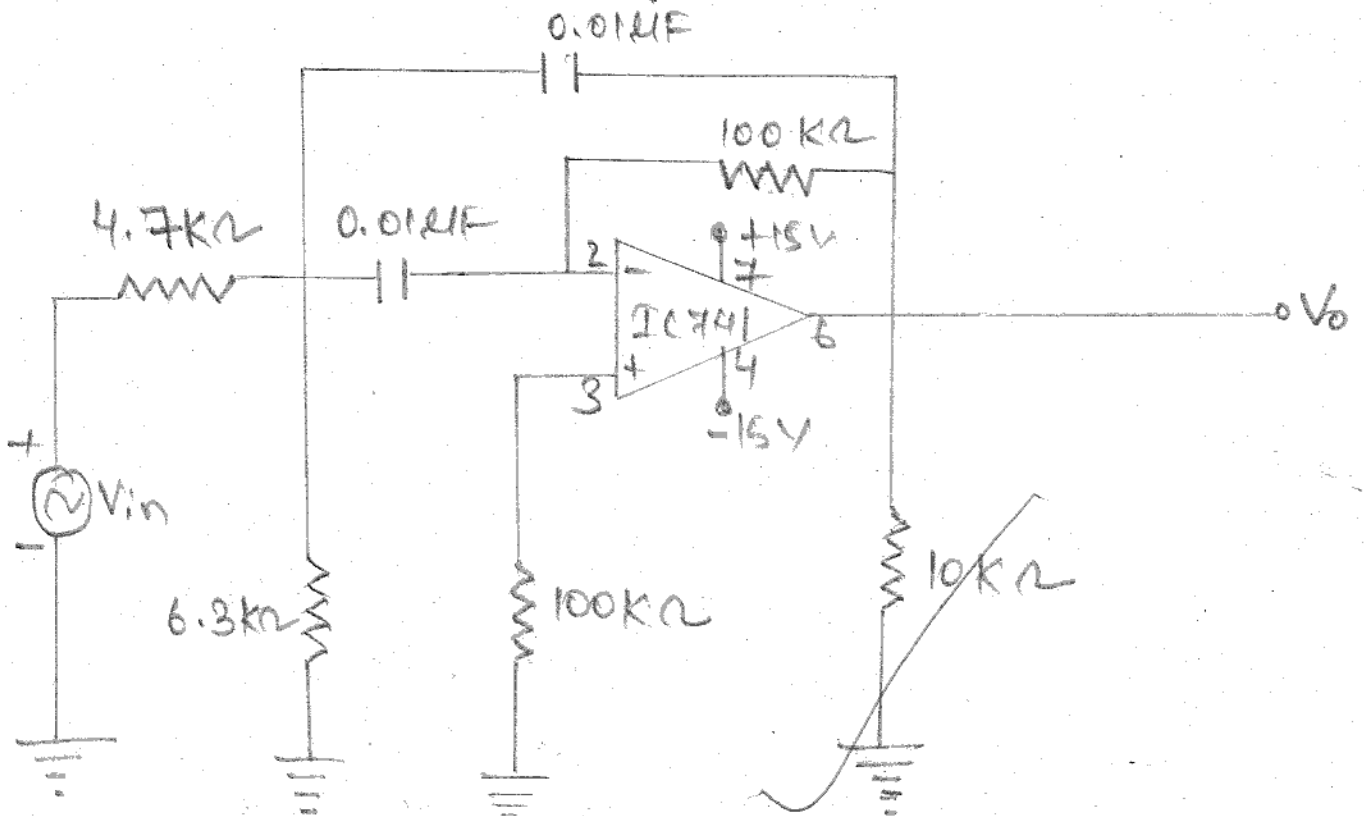

Exp No - 6

DATE - 22.7.2011


LOW PASS FILTER AND BAND PASS FILTER:-

AIM:- To design a low pass filter and Band Pass filter using operational Amplifier

APPARATUS REQUIRED:-


Sl. No	Components	Range	Quantity
1.	IC 741	—	1
2.	Resistor	4.7k Ω , 100k Ω , 10k Ω , 1.5k Ω , 6.3k Ω	1 each 1 each
		20k Ω , 10k Ω , 100k Ω	1 each
3.	Capacitor	0.1 μ F, 0.01 μ F	1 each
4.	Function generator	(0-30) MHz	1
5.	Power Supply	15 V	1
6.	CRO	(0-25) MHz	1
7.	Bread Board	—	1
8.	Connecting wires	—	As req.

PIN DIAGRAM

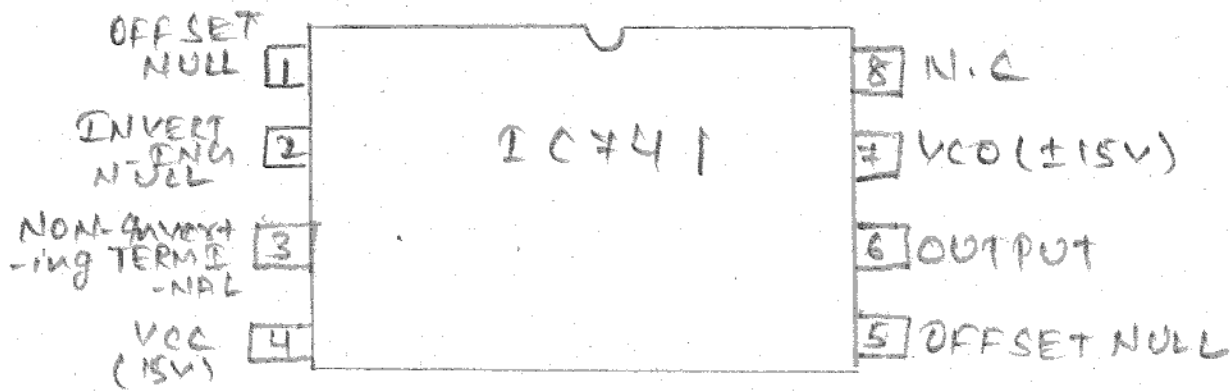


MODEL GRAPH

LOW PASS FILTER :-

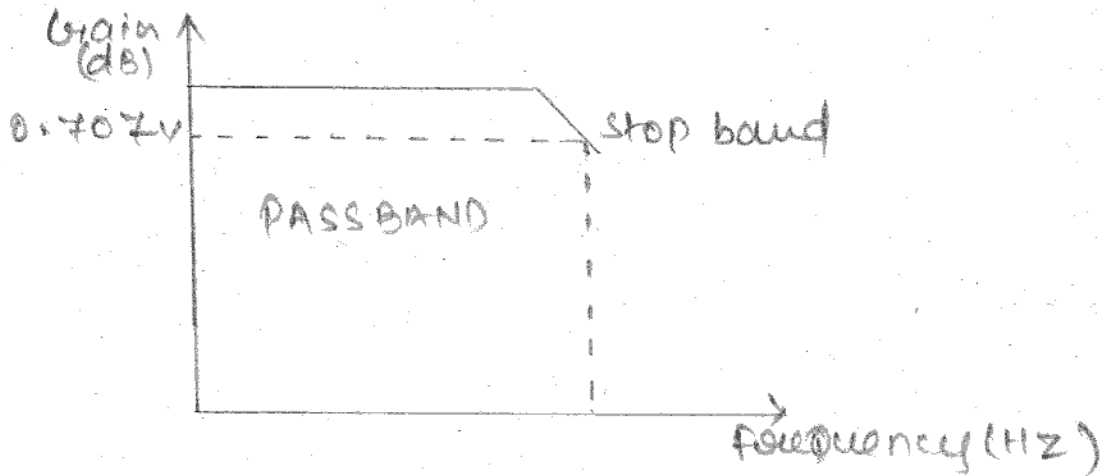

BAND PASS FILTER :-

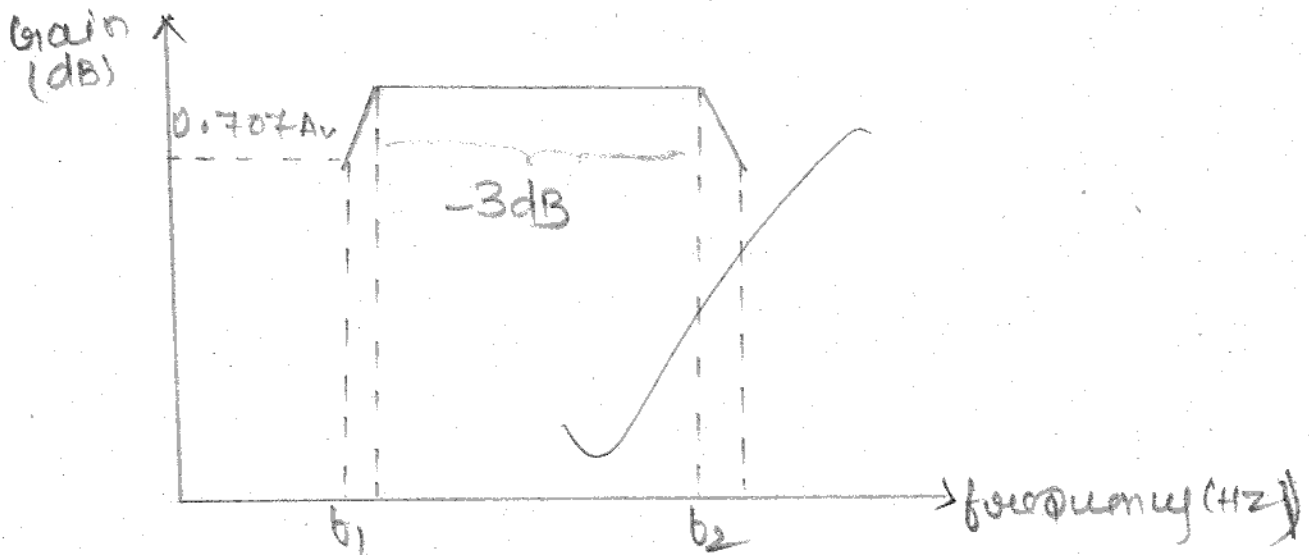

THEORY :-

LOW PASS FILTER

The low pass filter not only removes the high frequency components and noise, but also controls the dynamic characteristics of the PLL. These characteristics include capture and lock range, bandwidth and transient response. If filter bandwidth is reduced, the response time increases. However, reducing the bandwidth of the filter also reduces the capture range of the PLL.

BAND PASS FILTER

There are two types of bandpass filters which are classified as per the figure of merit or quality factor Q .

(i) Narrow band pass filter ($Q > 10$)

(ii) Wide band pass filter ($Q < 10$)

(i) Narrow band pass filter :- The important parameters in a band pass filter (BPF) are upper and lower cut-off frequencies (f_u and f_L), the band width (BW).

TABULAR COLUMN
Low pass filter:-

Sl. No	Frequency (Hz)	Op voltage (V _o)	V _o /V _i (V)	Gain = 20 log V _o /V _i (dB)
1.	100 Hz	4.11	4.11	12.27
2.	200 Hz	4.11	4.11	12.27
3.	400 Hz	4.11	4.11	12.27
4.	500 Hz	4.11	4.11	12.27
5.	600 Hz	4.11	4.11	12.27
6.	700 Hz	4.11	4.11	12.27
7.	800 Hz	4.11	4.11	12.27
8.	900 Hz	4.11	4.11	12.27
9.	1 KHz	4.11	4.11	12.27
10.	1.7 KHz	3.09	3.09	9.79
11.	2 KHz	2.09	2.09	6.40
12.	3 KHz	1.85	1.85	5.34
13.	4 KHz	1.33	1.33	2.47
14.	5 KHz	1.05	1.05	0.42
15.	6 KHz	0.69	0.69	-3.22
16.	7 KHz	0.42	0.42	-7.53
17.	8 KHz	0.24	0.24	-12.39

Design Procedure

$$f_c = 1 \text{ KHz} \quad A_t = 10 \quad Q = 3$$

$$\text{Let } C_1 = C_2 = 0.01 \mu\text{F}$$

$$R_1 = \frac{Q}{2\pi f_c A_t} = \frac{3}{2\pi \times 1000 \times 0.01 \times 10^{-6} \times 10}$$

$$R_1 = 4.77 \text{ K}\Omega$$

(ii) Wide band pass filter

→ A wide band-pass filter can be formed by HPF and LPF section. If the HPF and LPF are of the first order, then the band pass filter (BPF) will have a roll-off rate of 20dB/decade.

PROCEDURE:-

- (i) Connections are given as per the circuit diagram.
- (ii) connect the dual supply voltage of +15V and -15V.
- (iii) As input voltage in the range of millivolt is set for a particular frequency then by keeping the voltage control and varying the frequency various output voltage are obtained.
- (iv) From the observed reading the gain is calculated in decibel.

BAND PASS FILTER

Sl. No	Frequency (KHz)	Output V _o (V)	V _o /V _i (V)	Gain = 20 log V _o /V _i (dB)
1.	1 KHz	4.25	4.25	12.56
2.	2 KHz	4.54	4.54	13.14
3.	3 KHz	4.85	4.85	13.71
4.	4 KHz	5.17	5.17	14.26
5.	5 KHz	5.46	5.46	14.74
6.	6 KHz	5.67	5.67	15.07
7.	7 KHz	5.85	5.85	15.34
8.	8 KHz	5.95	5.95	15.44
9.	9 KHz	6	6	15.56
10.	10 KHz	6	6	15.56
11.	11 KHz	5.91	5.91	15.43
12.	12 KHz	5.75	5.75	15.19
13.	13 KHz	5.47	5.47	14.75
14.	14 KHz	5.14	5.14	14.21
15.	15 KHz	4.74	4.74	13.51
16.	16 KHz	4.35	4.35	12.76
17.	17 KHz	4.04	4.04	12.12
18.	18 KHz	3.67	3.67	11.29
20.	20 KHz	3.23	3.23	10.08



$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_0)} = 8.97$$

$$R_3 = \frac{Q}{\pi f_c C} = \frac{3}{\pi \times 10^3 \times 0.01 \times 10^{-6}} = 95.5 \text{ k}\Omega$$

Hence, $R_1 = 4.7 \text{ k}\Omega$, $R_2 = 6.2 \text{ k}\Omega$ & $R_3 = 100 \text{ k}\Omega$

~~Result~~
RESULT:- Thus the low pass filter and high pass filter are designed and the frequency response of those filter was obtained.

PIN DIAGRAM

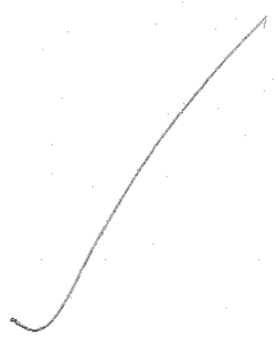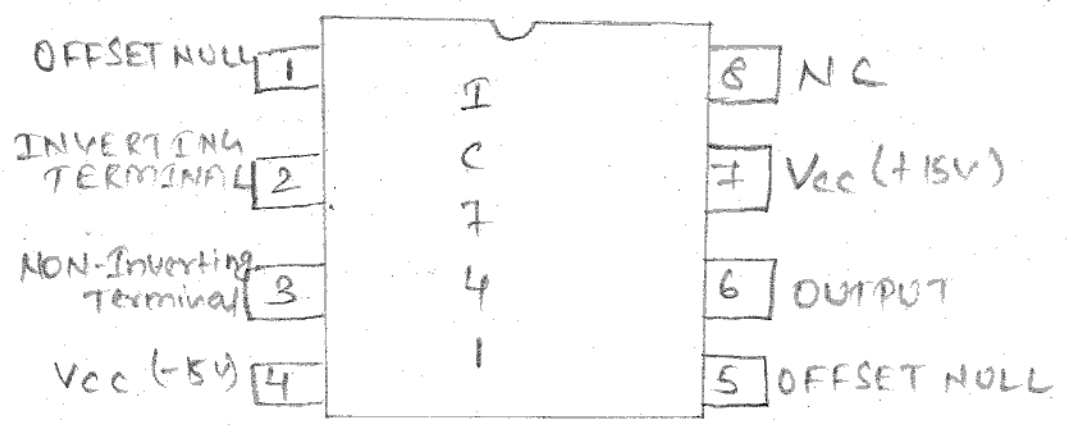

EXPT. No: 7

DATE: 12.8.2011


INSTRUMENTATION AMPLIFIER

AIM: To design an instrumentation amplifier and calculate the output.

APPARATUS REQUIRED:-

S.No	Components	Range	Quantity
1	op. Amp	IC 741	3
2.	Resistor	1 k Ω	4
		5 k Ω	2
3.	Variable resistor	± 1.5 k Ω	1
4.	RPS	± 15 V	1
5.	DSO	(0-30) MHz	1
6.	Bread Board	-	1
7.	Connecting wires	-	As per
8.	Probes	-	2

Circuit Diagram

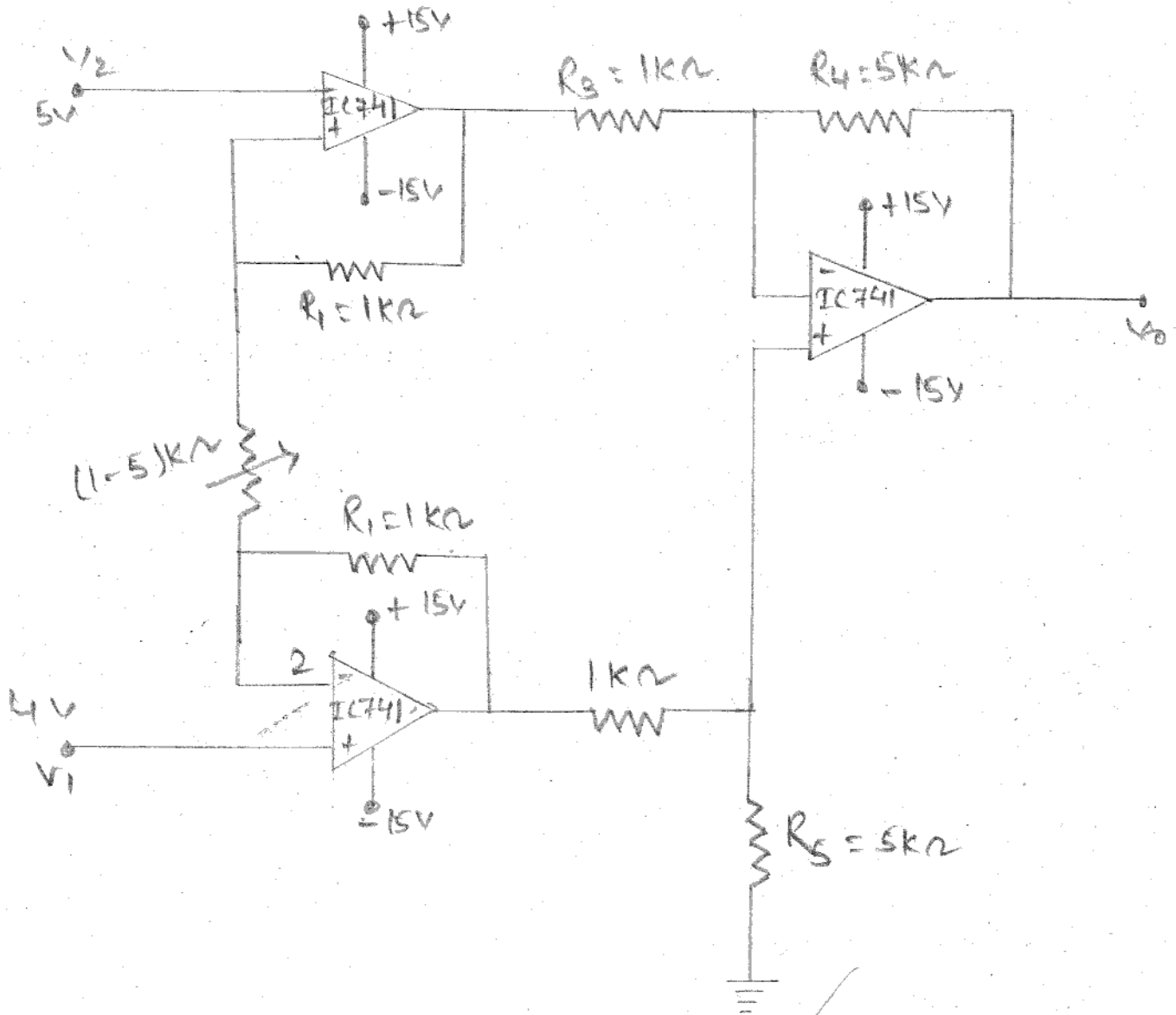

THEORY

Instrumentation amplifier is intentional for precise low level signal amplifier where low noise, low thermal and time drift, high input resistance and accurate closed loop gain are required. Instrumentation amplifier IC's such as ICL7605, IA725 are extensive. So general purpose amplifier can be employed in the differential mode to amplify low level output signal is the major frequency function of instrumentation amplifier.

$$V_1' = R' R + V_1$$

$$V_1 = \frac{R'}{R} (V_1 - V_2) + V_1$$

$$V_2' = -\frac{R'}{R} (V_1 - V_2) + V_2$$

TABULAR COLUMN

S.No	V_1 (V)	V_2 (V)	R (k Ω)	V_1' (V)	V_2' (V)	Theoretical output (V)	Practical output (V)
1.	4	5	1K	2.75	6.05	15V	14.46
2.	4	5	2K	3.3	5.5	8.30V	10.18
3.	4	5	3K	3.4	5.3	7V	8.36
4.	4	5	4K	3.5	5.2	7.5V	7.5

Theoretical Calculation

$$V_1 = 5V \quad V_2 = 4V \quad R = 1k\Omega$$

$$V_1' = \frac{R'}{R} (V_1 - V_2) + V_1$$

$$= \frac{1 \times 10^3}{1 \times 10^3} (1) + 5$$

$$V_1' = 6V$$

$$V_2' = -\frac{R'}{R} (V_1 - V_2) + V_2$$

$$= -\frac{1 \times 10^3}{1 \times 10^3} (1) + 4$$

$$V_2' = 3V$$

PROCEDURE

→ Connection are given as per the circuit diagram

→ The input V_1 and V_2 are given

→ The output voltage reading are noted.

→ The graph is plotted.

$$V_0 = (V_1' - V_2') \times 5$$
$$= 3 \times 5$$

$$V_0 = 15V$$

$$V_1 = 5V$$

$$V_1' = \frac{R'}{R} (V_1 - V_2) + R$$
$$= \frac{1 \times 10^3}{3.3 \times 10^3} \times (1) + 5$$

$$V_1' = 5.2V$$

$$V_2' = -\frac{R'}{R} (V_1 - V_2) + V_2$$
$$= -\frac{1 \times 10^3}{5 \times 10^3} + 4$$

$$V_2' = 3.8V$$


$$V_0 = (V_1' - V_2') \times 5$$

$$V_0 = 7V$$


~~Result~~

RESULT: Thus the instrumentation amplifier circuit was constructed and output gain was calculated.

Circuit Diagram Astable Multivibrator

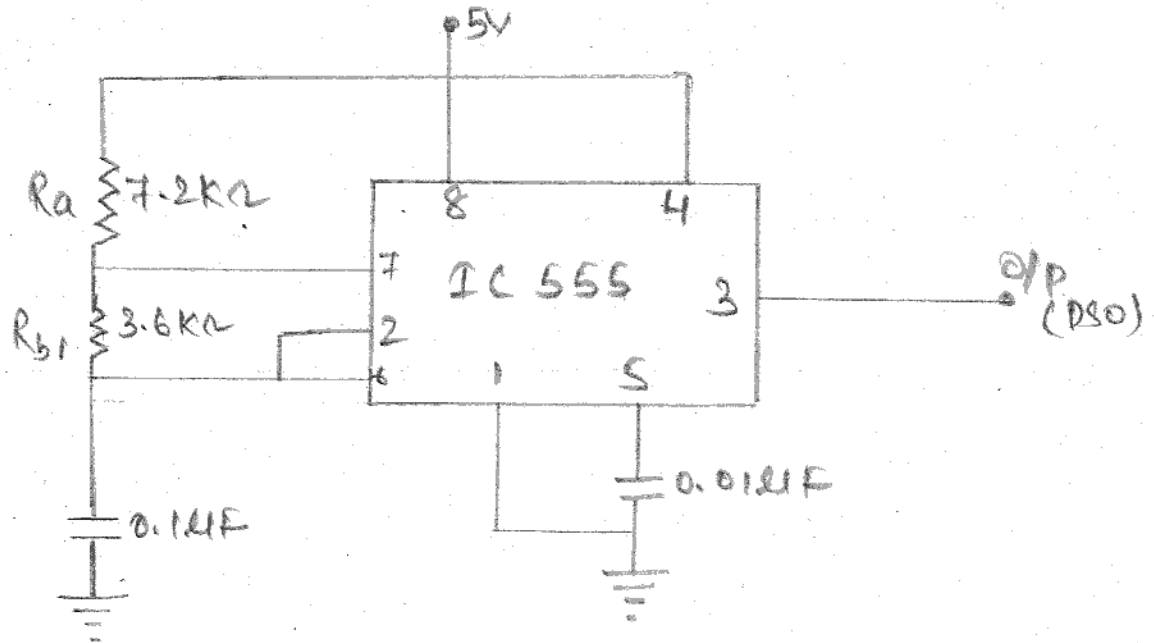

MODEL GRAPH

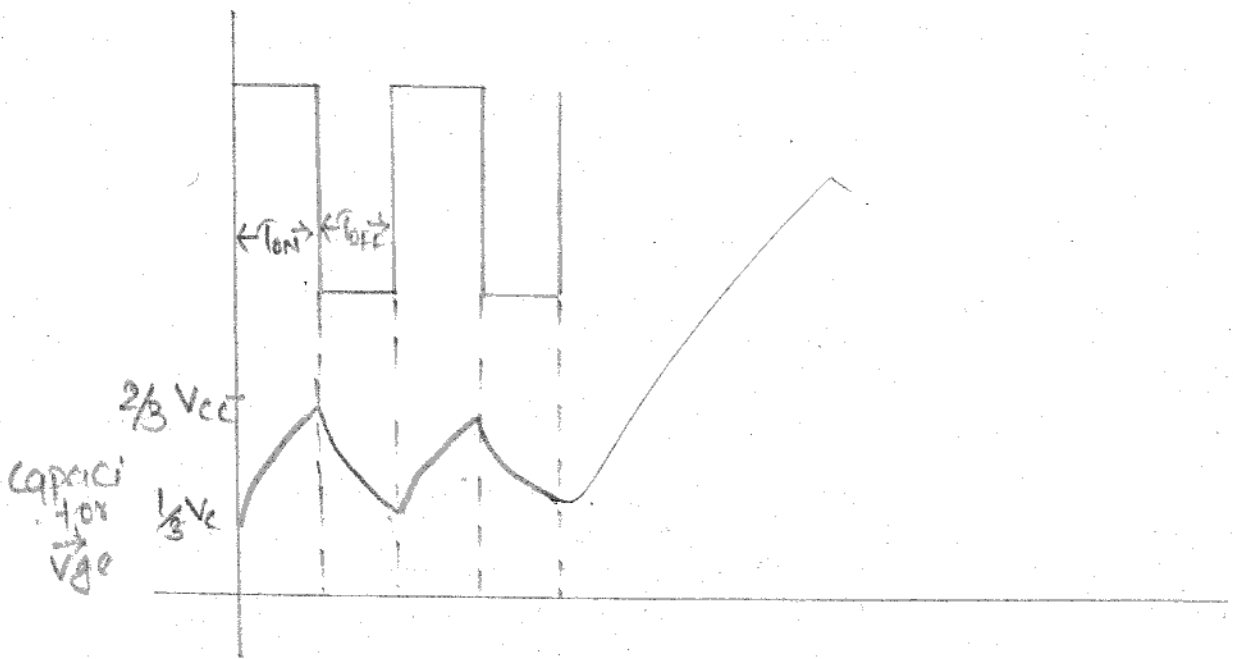

Exp. No : 8

DATE : 19.8.2011

MULTIVIBRATOR USING IC555 TIMER

AIM: To design and construct multivibrator using IC555 timer

APPARATUS REQUIRED

S.NO	COMPONENT	Range	Qty.
1.	Timer	IC555	1
2.	Resistor	7.2 k Ω	1
		3.6 k Ω	1
		91 k Ω	1
3.	Capacitor	0.1 μ F	1
		0.01 μ F	1
4.	Fixed power supply	$\pm 5V$	1
5.	DSO	(0-30) MHz	1
6.	Bread Board	-	1
7.	Connecting wires	-	As reqd.


TABULAR COLUMN : (SQUARE WAVE)

Amplitude	T _{ON} (ms)		T _{OFF} (ms)		Freq (Hz)	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical
4.44V	0.55ms 0.55ms	800μs	0.25ms	260μs	1KHz	925.9 Hz

Capacitor V_{ge}

Amplitude	charge	discharge	frequency.
4.78V	820μs	260μs	925.9 Hz


PIN DIAGRAM

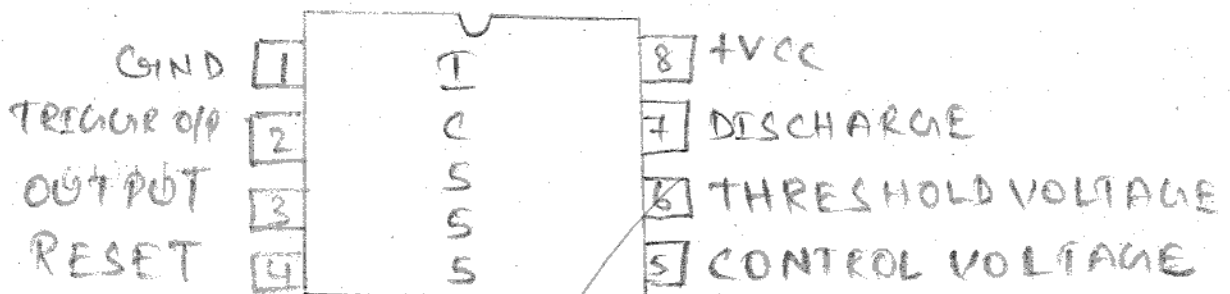


THEORY:-

The electronic circuit which is used to generate the non-sinusoidal wave form are called multivibrator. The monostable multivibrator has only one stable state the other state is unstable called as quasi stable. When an external trigger pulse is applied to circuit, the circuit goes to quasi stable state from its normal state after some time interval, the circuit is automatically return to the stable state. The circuit is used to generate the rectangular wave and hence can be used as to gate other circuit. The time between the transistor from quasi stable state can be predetermined and hence it can be used to introduced time delay with the help of best transistor.

MONOSTABLE

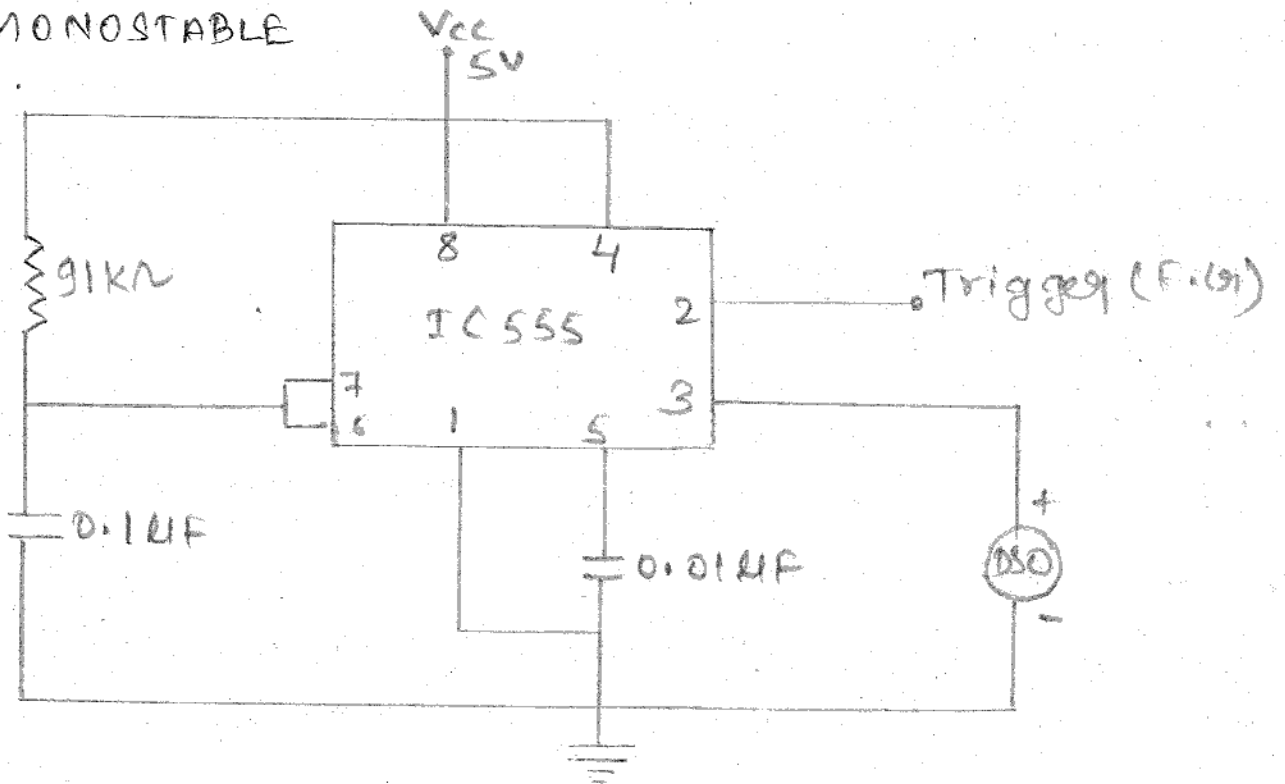

MODEL GRAPH

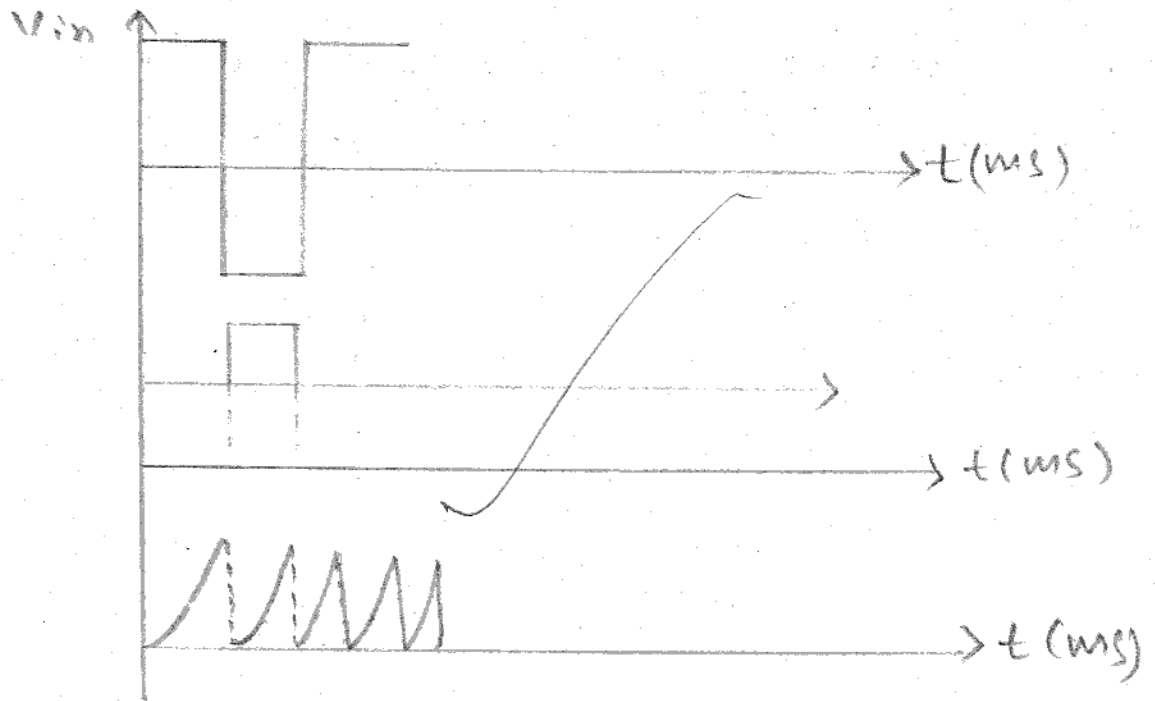

PROCEDURE:-

- ① Connect the circuit as per the circuit diagram.
- ② Apply the trigger signal
- ③ Observe the i/p and o/p waveform using DSO
- ④ Draw the required graph.

TABULAR COLUMN

	Amplitude	Time period (ms)		Freq.
		T _{ON}	T _{OFF}	
i/p	3.60	560 μs	480 μs	1 KHz
o/p	4.48		520 μs	
Capacitor vxg	1.58	10 μs	220 μs	1 KHz

Design procedure

A stable multivibrator

$$f = 1 \text{ KHz} \quad D = 75\% = 0.75$$

$$f = \frac{1.44}{(R_A + 2R_B)C} \text{ Hz}$$

$$\Rightarrow 1 \times 10^3 = \frac{1.44}{(R_A + 2R_B)C}$$

$$\therefore (R_A + 2R_B)C = 1.44 \times 10^{-3} \text{ --- (1)}$$

$$\% D = \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

$$\Rightarrow R_A + 2R_B = 1.33 (R_A + R_B)$$

$$\Rightarrow 0.66 R_B = 1.33 R_A$$

$$R_B = 0.5 R_A \text{ --- (2)}$$

Choose $C = 0.1 \mu F$

$$(R_A + 2R_B) \times 0.1 \times 10^{-6} = 1.44 \times 10^{-3}$$

$$R_A + 2R_B = 14400 \text{ --- (3)}$$

Substitute (2) in (3)

$$R_A + 2(0.5R_A) = 14400$$

$$R_A = 7.2 \text{ k}\Omega$$

$$R_B = 3.6 \text{ k}\Omega \quad C = 0.1 \mu F$$

monostable multivibrator

pulse width $\omega = 10 \text{ ms}$

The pulse width is given by $\omega = 1.1 R_C$

$$10 \times 10^{-3} = 1.1 R_C$$

$$R_C = 9.09 \times 10^3 \Omega$$

Choose $C = 0.1 \mu F$

$$R = \frac{9.09 \times 10^3}{C}$$


$$= \frac{9.09 \times 10^3}{0.1 \times 10^{-6}}$$

$$= 90.90 \text{ k}\Omega$$

$$R = 91 \text{ k}\Omega$$

~~Result~~
RESULT: Thus a multivibrator is designed and constructed using IC 555 timer.

CIRCUIT DIAGRAM

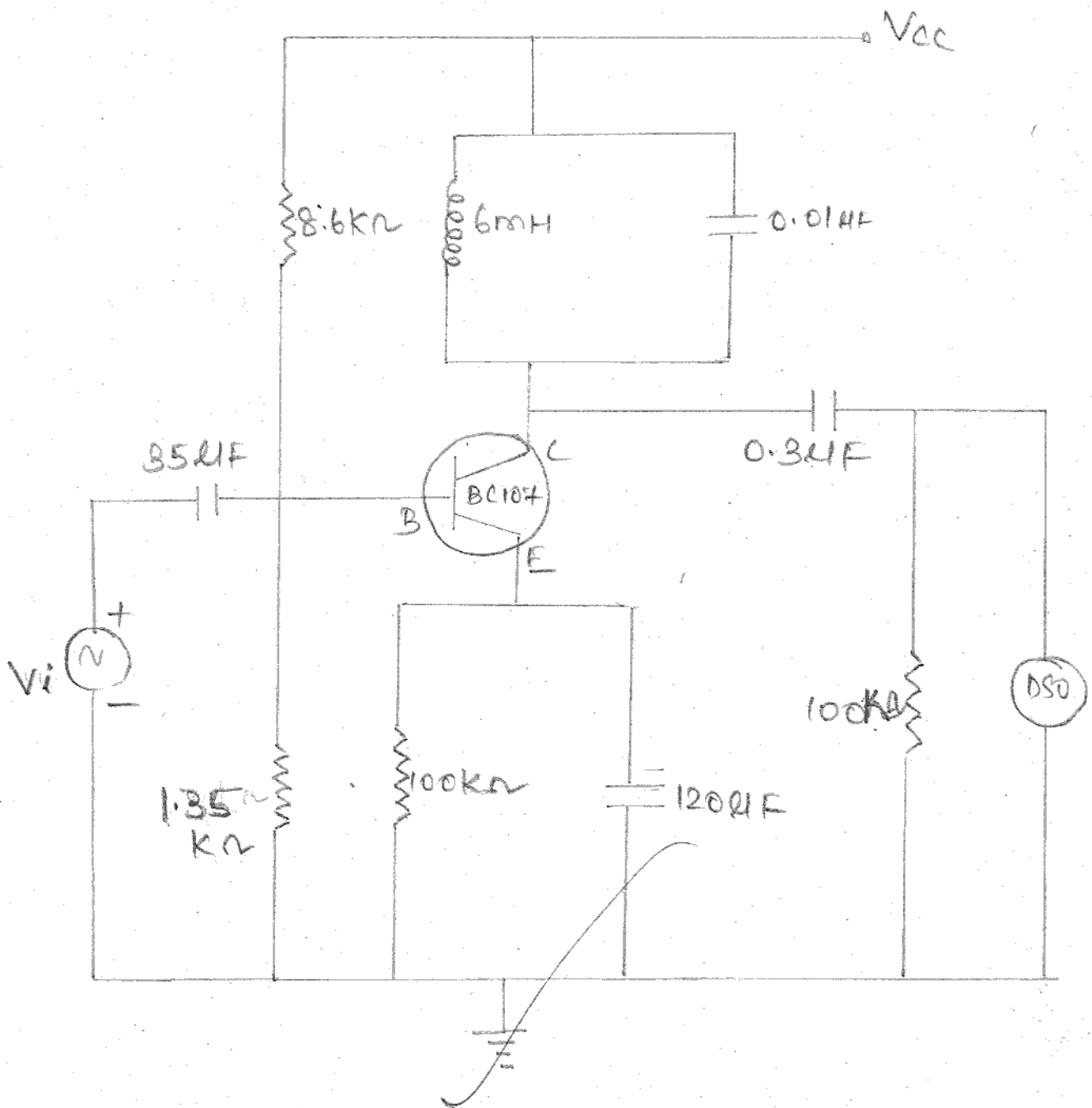

Exp. No - 11

DATE: 9.9.11

CLASS A SINGLE TUNED AMPLIFIER

AIM: To design a single tuned amplifier and to draw its frequency response.

APPARATUS REQUIRED:

S.No	COMPONENT	RANGE	QUANTITY
1.	Resistor	8.56K	1
		1.35K	1
		10K	1
		100K	1
2.	Capacitor	33 μ F	1
		120 μ F	1
		0.3 μ F	1
		0.01 μ F	1
3.	RPS	(0-30)V	1
4.	Transistor	BC107	1
5.	DSO	(0-30)MHz	1
6.	F.G	(0-10)MHz	1

DESIGN PROCEDURE:

$$V_{CC} = 20V, \beta = 150, f = 50\text{Hz}, I_C = 20\text{mA}$$

$$R_{iC} = 4\text{k}\Omega$$

$$I_E = I_C = 20\text{mA}$$

$$V_{CE} = V_{CC}/2 = 20/2 = 10V$$

$$V_E = V_{CC}/10 = 20/10 = 2V$$

$$V_B = V_{BE} + V_E = 0.7 + 2 = 2.7$$

$$I_2 = I_C/10 = \frac{20 \times 10^{-3}}{10} = 2\text{mA}$$

$$R_2 = V_B / I_2 = 2.7 / 2 \times 10^{-3} = 1.35\text{k}\Omega$$

$$R_1 = \left(\frac{V_{CC} - V_B}{I_2} \right) = \frac{20 - 2.7}{20 \times 10^{-3}} = 8.05\text{k}\Omega$$

$$Z_{in} = R_B \parallel R_{iC}$$

$$R_B = R_1 \parallel R_2 = (8.05 \parallel 1.35)\text{k} = 1.16\text{k}\Omega$$

$$= 904\Omega$$

$$X_{12} = \frac{904}{10} = 90.4\Omega$$

$$C_{in} = \frac{1}{2\pi f X_{in}} = \frac{1}{2\pi \times 50 \times 90.4} = 35.2\mu\text{F}$$

$$C_o = \frac{1}{2\pi f (R_C/10)} = \frac{1}{2\pi \times 50 \times 10 \times 10^3} = 0.318\mu\text{F}$$

or $R_C = 100\text{k}\Omega$

$$X_{CE} = \frac{g_{iE}}{1+\beta} = \frac{4 \times 10^3}{1+150} = 20.49\Omega$$

$$= 0.138\mu\text{F}$$

$$C_E = \frac{1}{2\pi f X_{CE}} = 120\mu\text{F}$$

7. Bread Board

-



1

8. Connecting
Wires

-

As required.

MODEL GRAPH

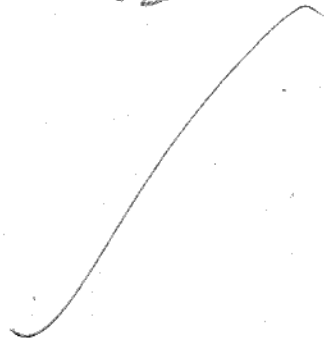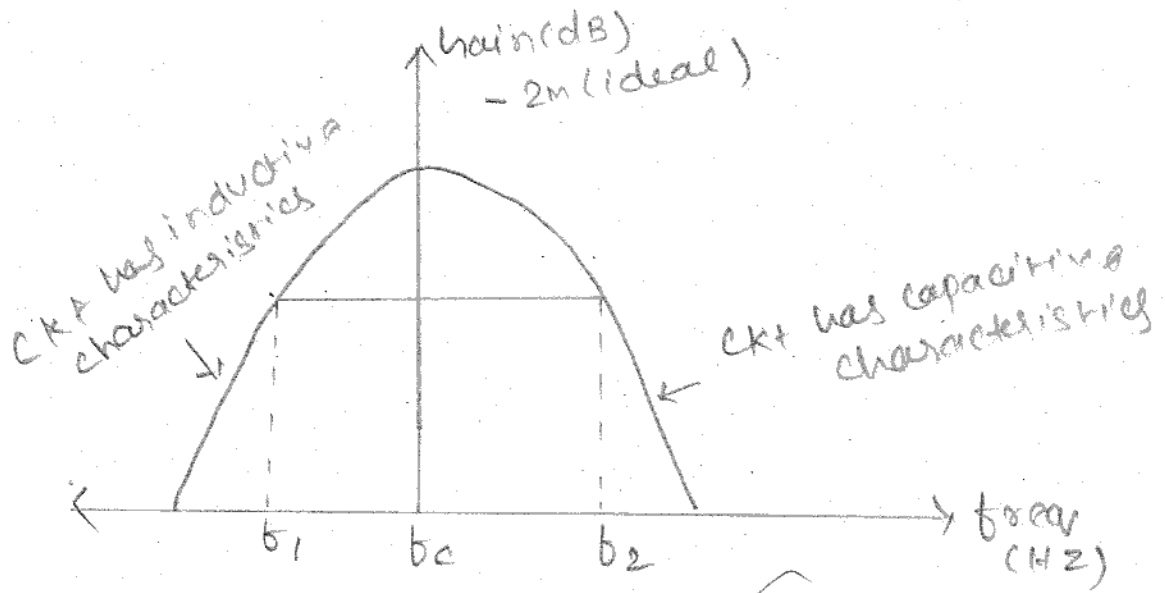

THEORY:-

The single tuned amplifier selecting the range of frequency. The resistance load replaced by the tank circuit. The tuned amplifier gives response only at particular frequency at which the Q/P is almost zero. The resistance R_1 & R_2 provide potential dividing bias. R_3 and C_{ce} provides the thermal stabilization. Thus it fixes up the operating point.

TABULATION


$$V_{in} = 1V$$

S.No	Frequency (Hz)	O/P Voltage (V)	Gain $= 20 \log (V_o/V_i)$ (dB)
1.	200 Hz	1.35 kV	2.60
2.	500 Hz	3.09 kV	9.79
3.	800 Hz	4.67 kV	13.38
4.	1 kHz	6.26 kV	15.93
5.	2 kHz	8 kV	18.06
6.	5 kHz	9 kV	19.08
7.	10 kHz	9.42 kV	19.48
8.	11 kHz	9.50 kV	19.55
9.	12 kHz	9.42 kV	19.48
10	100 kHz	8.64 kV	18.73
11	120 kHz	8.22 kV	18.29
12	130 kHz	7.35 kV	17.29
13	200 kHz	6.44 kV	16.17
14	230 kHz	5.54 kV	14.87
15	600 kHz	3.70 kV	11.50
	1 MHz	1.53 kV	8.69

SEMI-LOG PAPER (5 CYCLES X 100)

Frequency

Gain (dB)

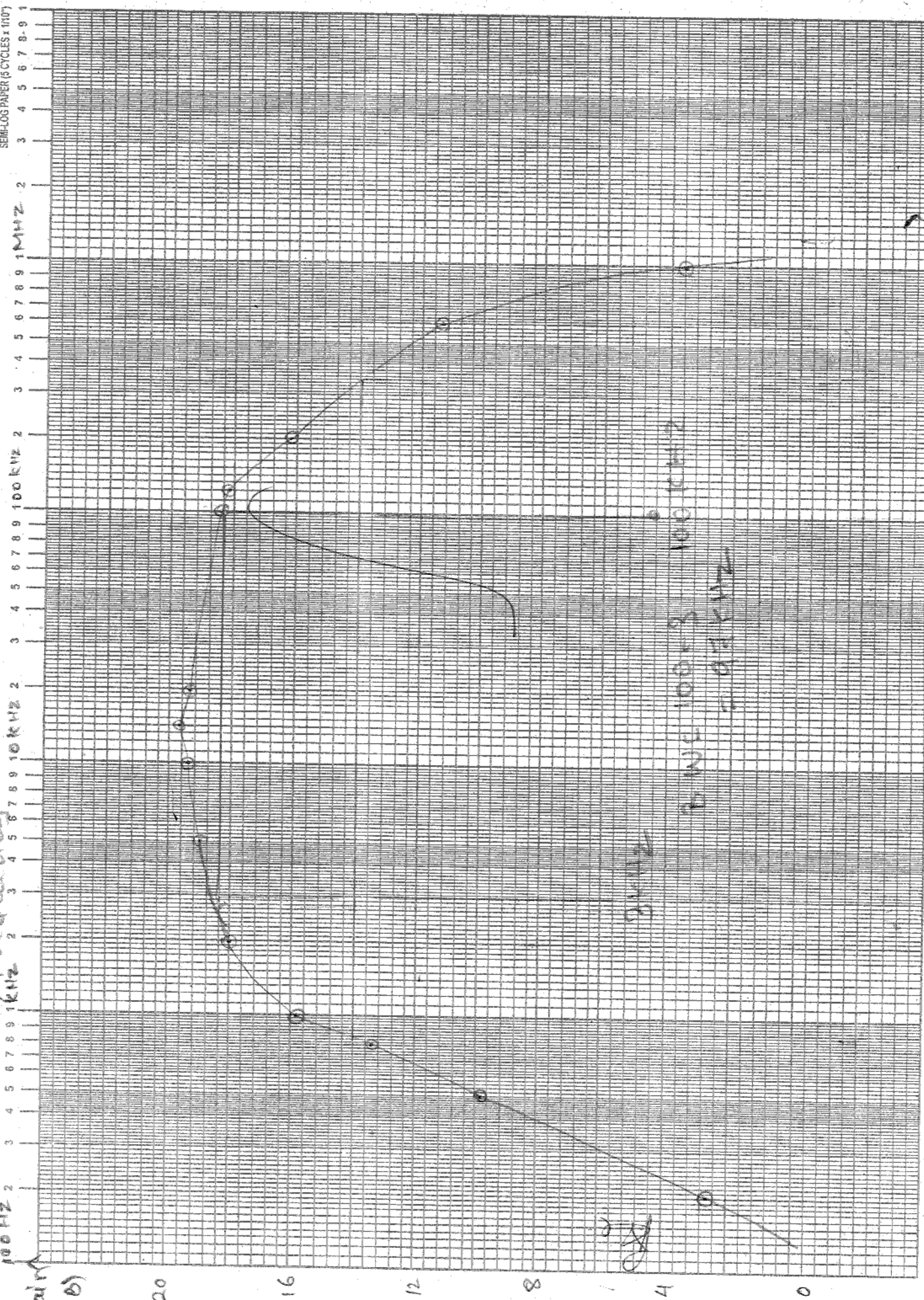

PROCEDURE :-

- (1) Connections are given as per the circuit diagram
- (2) By varying frequency amplitude is noted down.
- (3) Gain is calculated in dB.
- (4) Frequency response curve is plotted.

~~AC~~
~~20/11/17~~


~~AC~~
~~20/11/17~~

RESULT:- This Class A tuned amplifier is designed and frequency response is plotted.

THEORETICAL FREQUENCY: 20 KHZ


PRACTICAL FREQUENCY: ~~10-48 KHZ~~
97 KHZ

PIN DIAGRAM

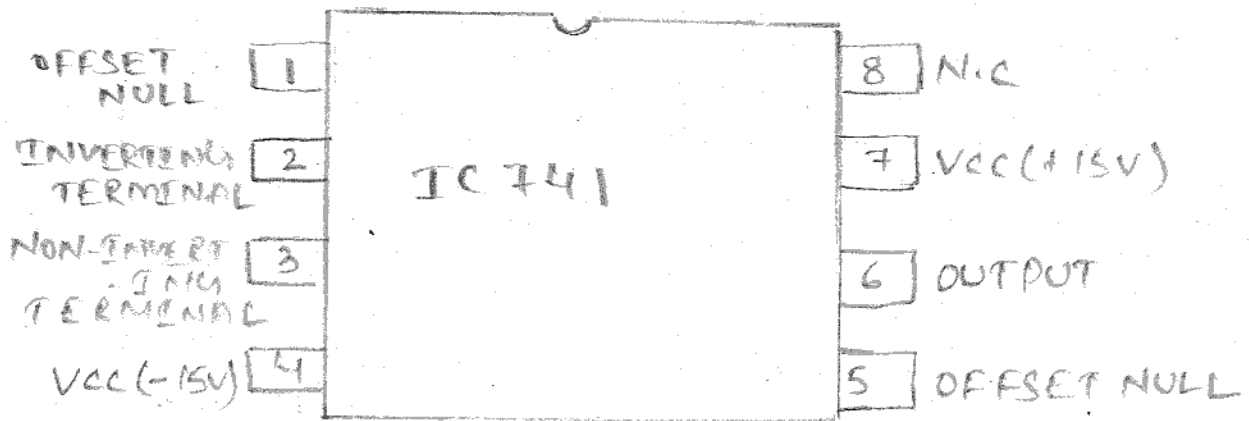

CIRCUIT DIAGRAM:

INVERTING COMPARATOR:

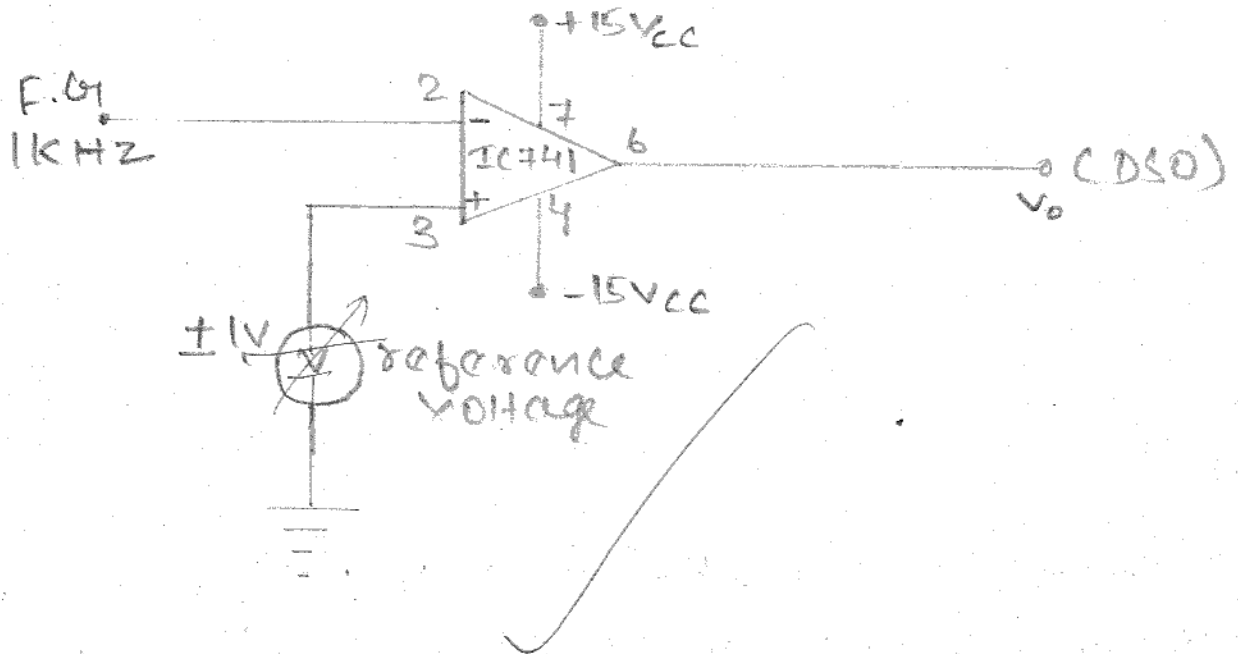

EXPT No - 12

DATE : 10.9.2011



INVERTING AND NON-INVERTING COMPARATOR

AIM: To study and compare the operation of the comparator circuits using operational amplifier IC741

APPARATUS REQUIRED:-

S.No	COMPONENTS	Range	Quantity
1.	OP-AMP	IC741	1
2.	Power Supply	(0-30)V	1
3.	Variable power	$\pm 1V$	1
4.	DSO	(0-30)MHz	1
5.	Function generator	-	1
6.	Bread Board	-	1
7.	Connecting wires and probes	-	1

NON-INVERTING COMPARATOR:

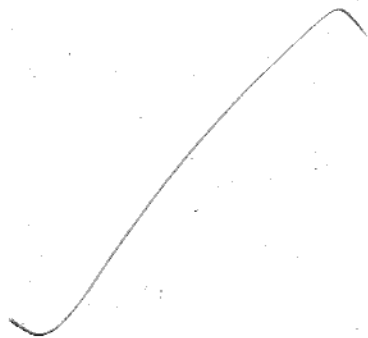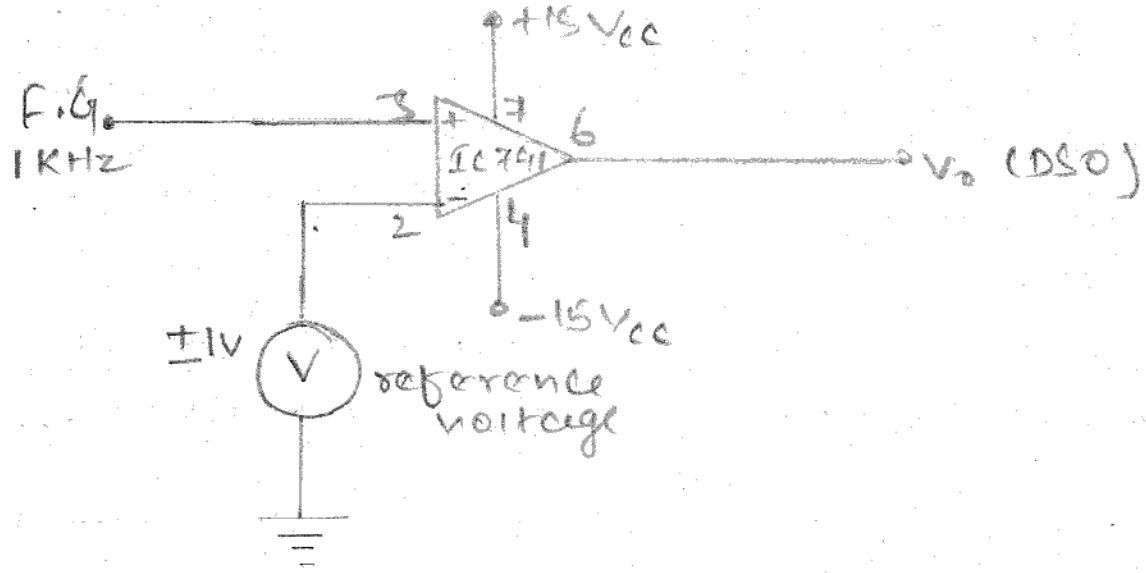

THEORY:

INVERTING COMPARATOR: In inverting comparator a fixed, V_{ref} is given at the non-inverting terminal, while the time varying signal is given to inverting input terminal. When input s/d $V_i < V_{ref}$, the output is at $+V_{sat}$ and when $V_i > V_{ref}$, the output is at $-V_{sat}$.

NON-INVERTING COMPARATOR: In non-inverting comparator a fixed V_{ref} is given at a negative input terminal and time varying signal is given at positive terminal. When the input signal $V_i < V_{ref}$ the output voltage $-V_{sat}$ and v_o goes to $+V_{sat}$ for the condition $V_i > V_{ref}$.

TABULAR COLUMN

INVERTING COMPARATOR :-

S.No	$V_{ref}(V)$	Amplitude (V)		$T_{ON}(ms)$	$T_{OFF}(ms)$	T.(ms)
		V_{in}	V_{out}			
1.	+1V	5V	27.6V	720 μ S	280 μ S	1ms
2.	-1V	5V	27.6V	400 μ S	600 μ S	1ms

NON INVERTING COMPARATOR :-

S.No	$V_{ref}(V)$	Amplitude (V)		$T_{ON}(ms)$	$T_{OFF}(ms)$	T(ms)
		V_{in}	V_{out}			
1.	+1V	5V	27.6V	320 μ S	700 μ S	1ms
2.	-1V	5V	27.6V	600 μ S	380 μ S	1ms







$V_{ref} = +1 \text{ Volt}$

$V_{ref} = -1 \text{ Volt}$

Scale

X-axis = 1 unit = .25 μs

Y-axis = 1 unit = 1 Volt

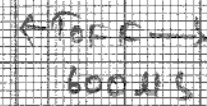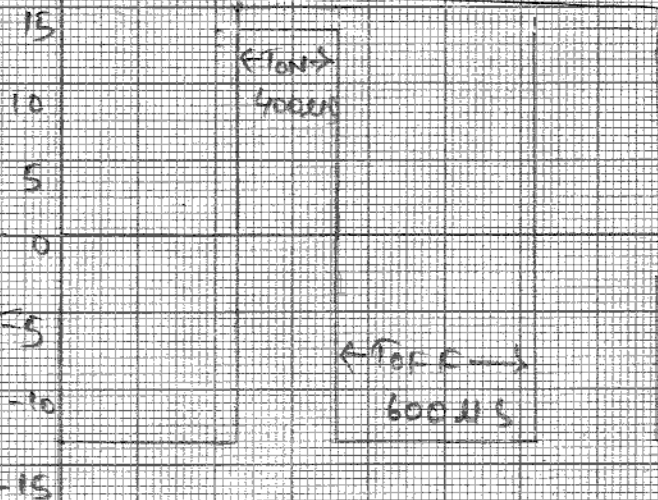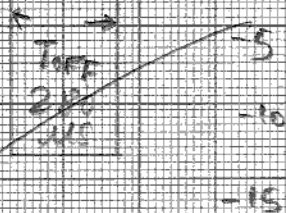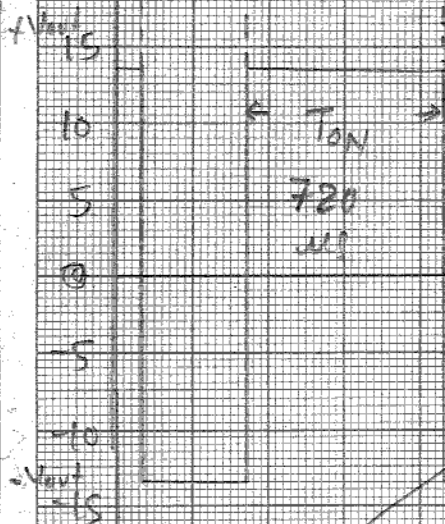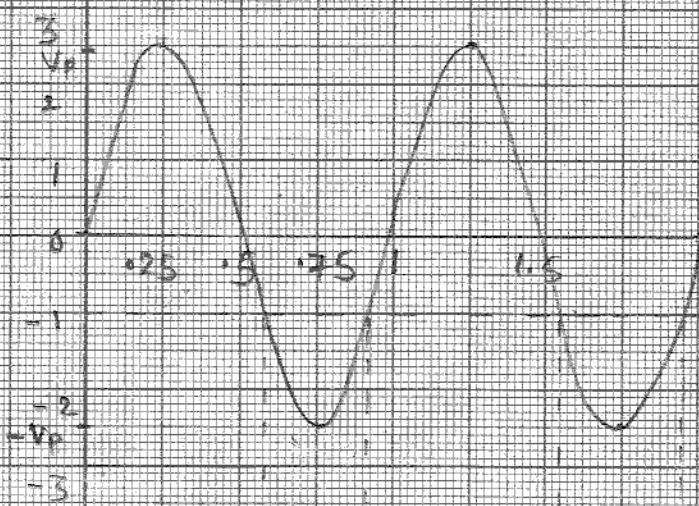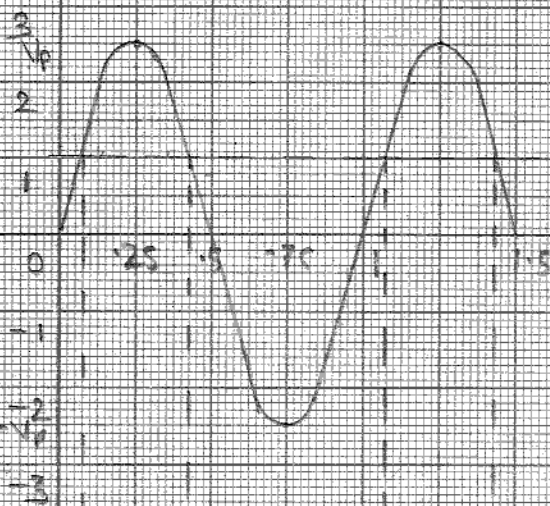

Scale

X-axis = $T_{ON} = 7000 \mu\text{s}$

$T_{OFF} = 2000 \mu\text{s}$

Y-axis = 1 unit = 5 Volt

Scale

X-axis = $T_{ON} = 1000 \mu\text{s}$

$T_{OFF} = 600 \mu\text{s}$

Y-axis = 1 unit = 5 Volt

PROCEDURE:-

INVERTING COMPARATOR:-


- connections are given as per the circuit diagram
- The input voltage V_{in} is set during function generator
- observe the output and input waveform using DSO
- The graph is drawn.

NON INVERTING COMPARATOR:-


- connections are given as per the circuit diagram
- The input voltage V_{in} is set using function generator
- observe the input and output waveform using DSO
- The graph is drawn.





MODEL GRAPH :-

INVERTING COMPARATOR :-

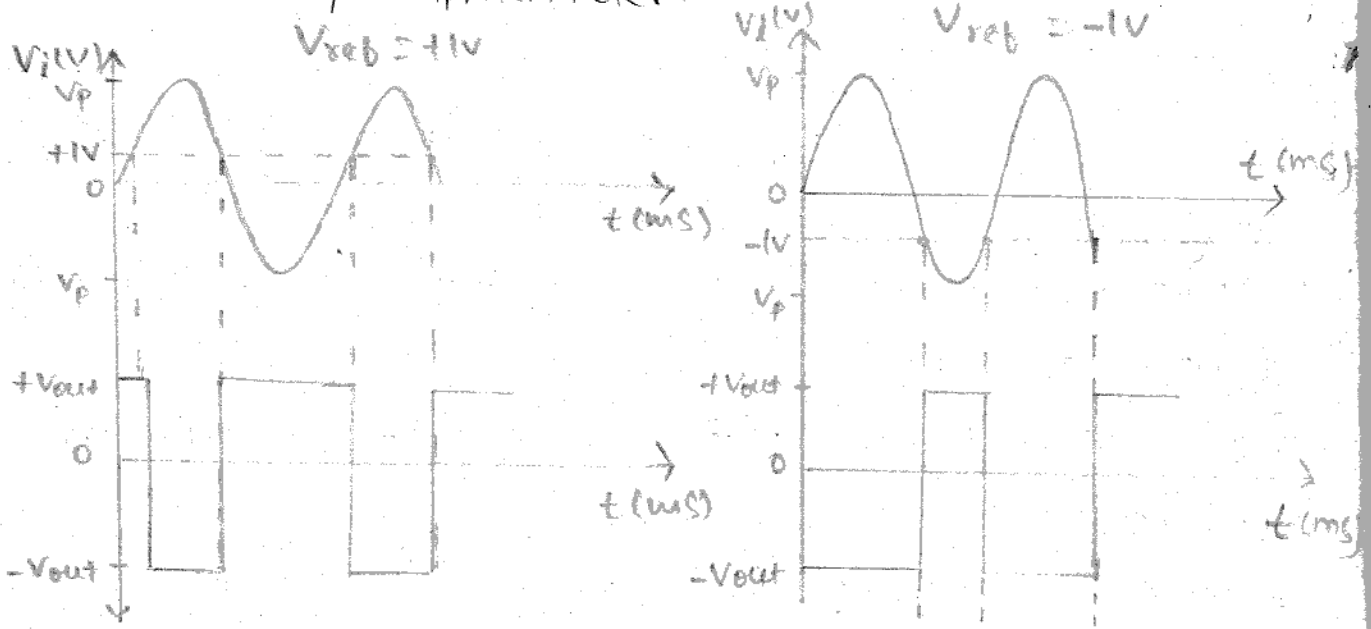


NON-INVERTING COMPARATOR

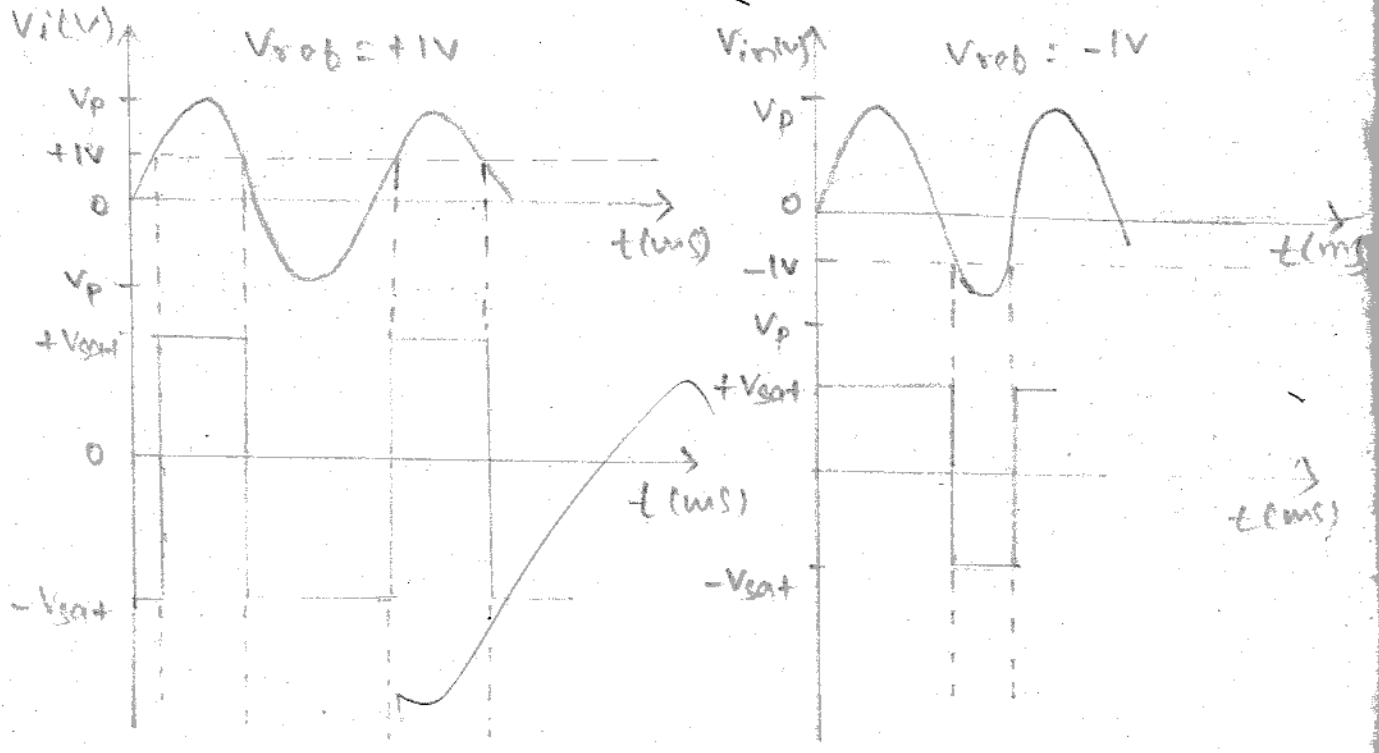

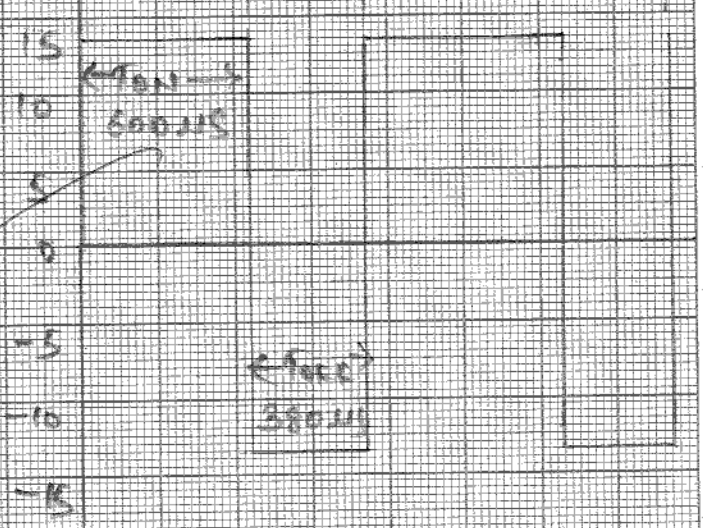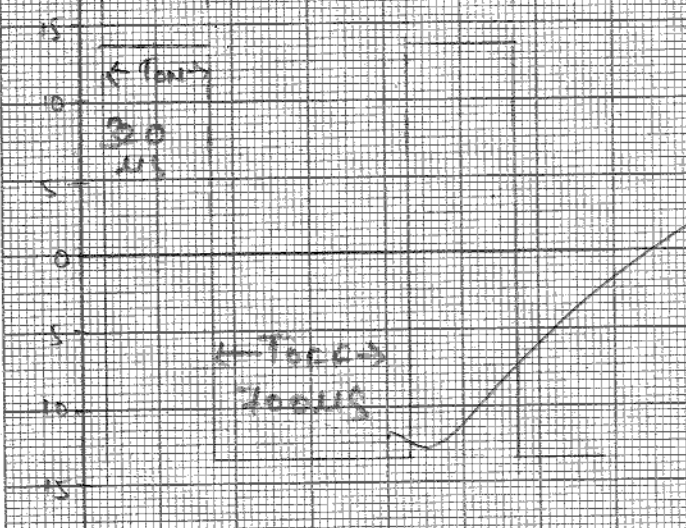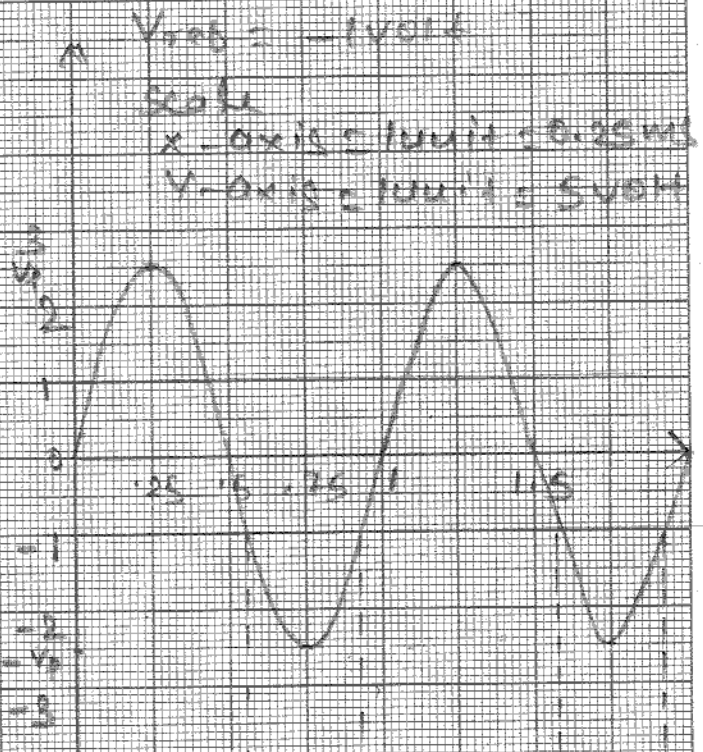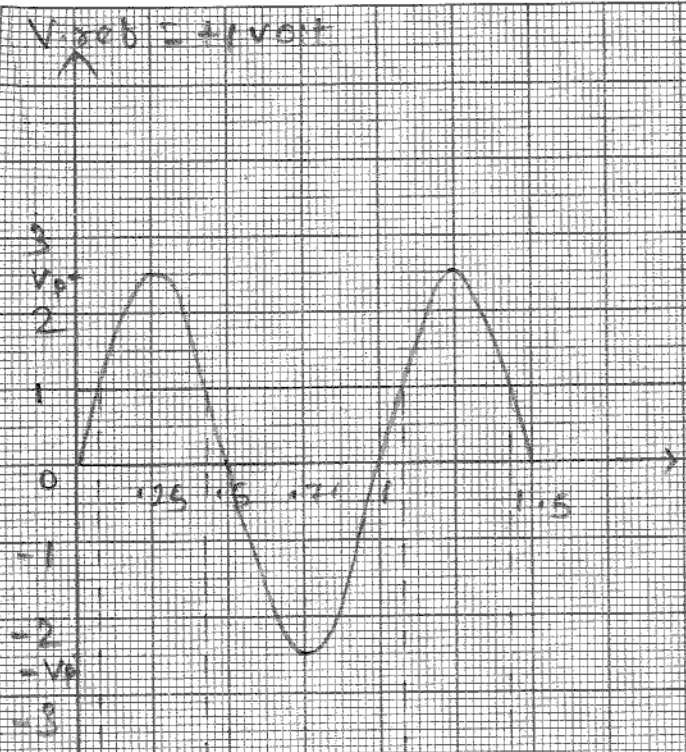


~~Result~~
RESULT: That the inverting and non-inverting
comparator is constructed and tested using
op-amp.

PIN DIAGRAM :-

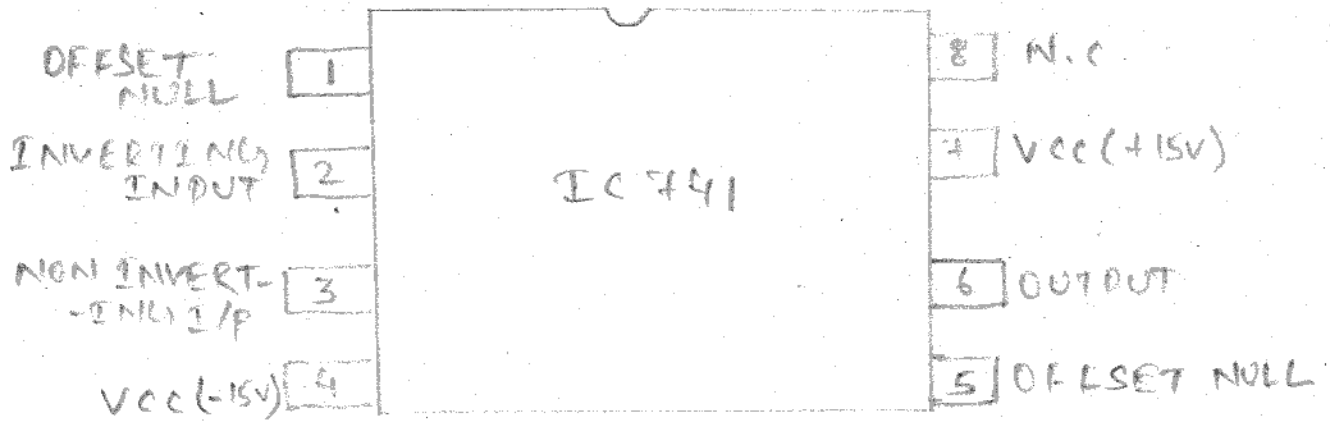

CIRCUIT DIAGRAM :-

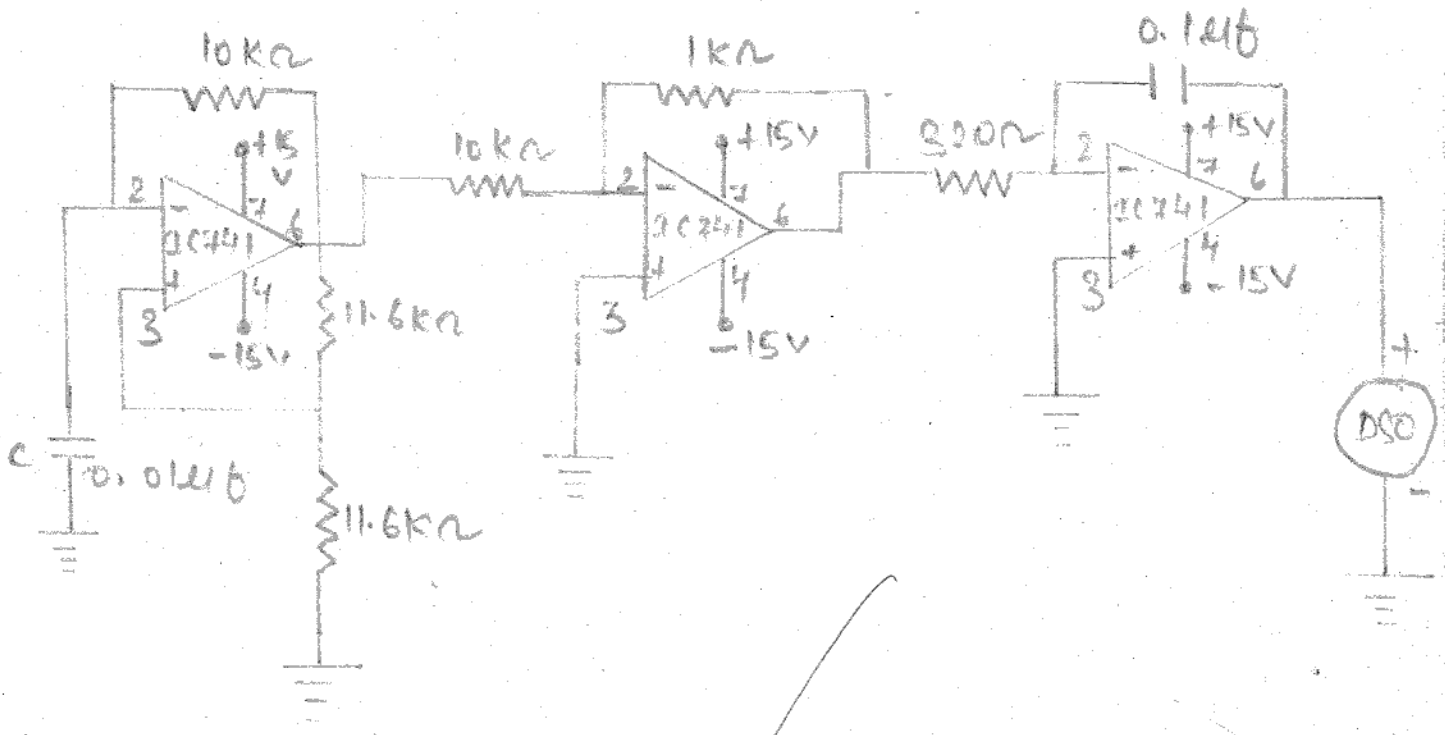

EXPT No : 13

DATE : 15.9.11

WAVEFORM GENERATOR

AIM: To construct a waveform generator and generate the square and triangular waveforms.

APPARATUS REQUIRED:-




S. No	COMPONENTS	RANGE	QUANTITY
1.	OP-AMP	IC 741	3
2.	Resistor	10K Ω	3
		1K Ω	1
		11.6K Ω	1
		320 Ω	1
3.	Capacitor	0.01 μ F	1
		0.1 μ F	1
4.	Fixed power supp	(0-15)V	1
5.	DSO	(0-30)MHz	1
6.	Bread Board	-	1
7.	Connecting wires	-	As reqd.

TABULAR COLUMN

	Amplitude (V)	Time Period (ms)	
		T _{ON}	T _{OFF}
Astable op-amp I	2.5 V	8.4 ms	11.2 ms
De-amplifier op-amp II	2.5 V	8.4 ms	11.2 ms
Integrator op-amp	1.8 V	9.62 ms	11.2 ms

Waveform Generator

Amplitude (V)

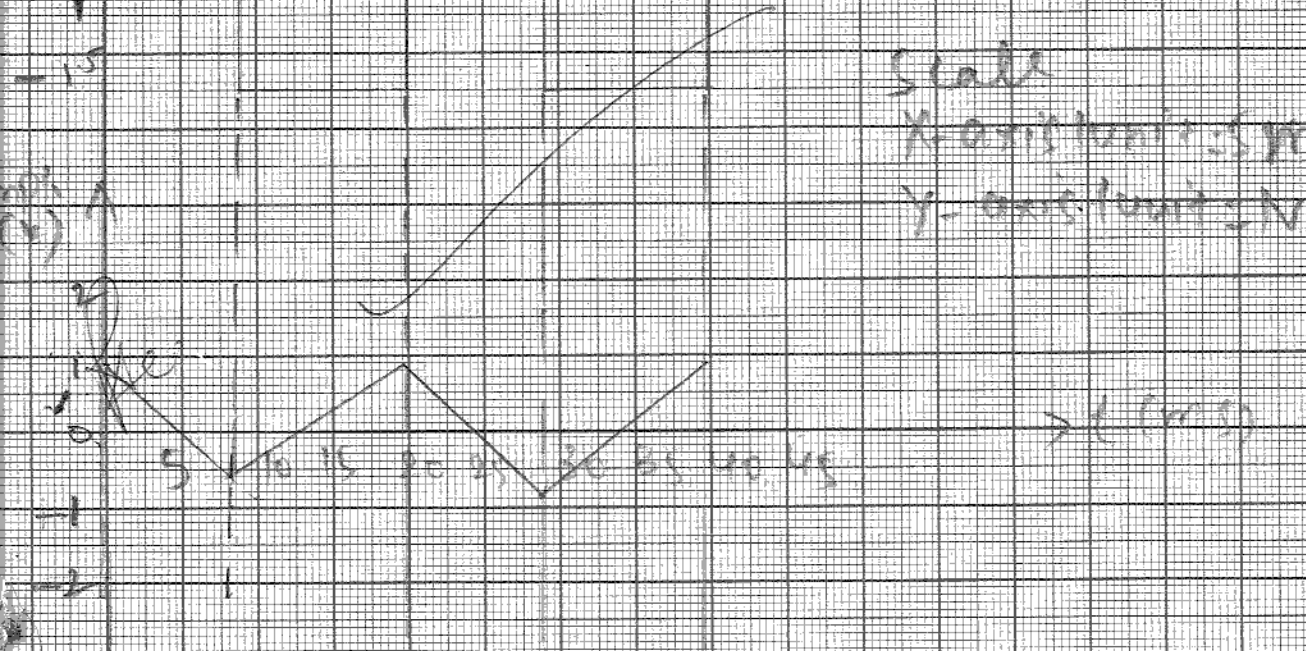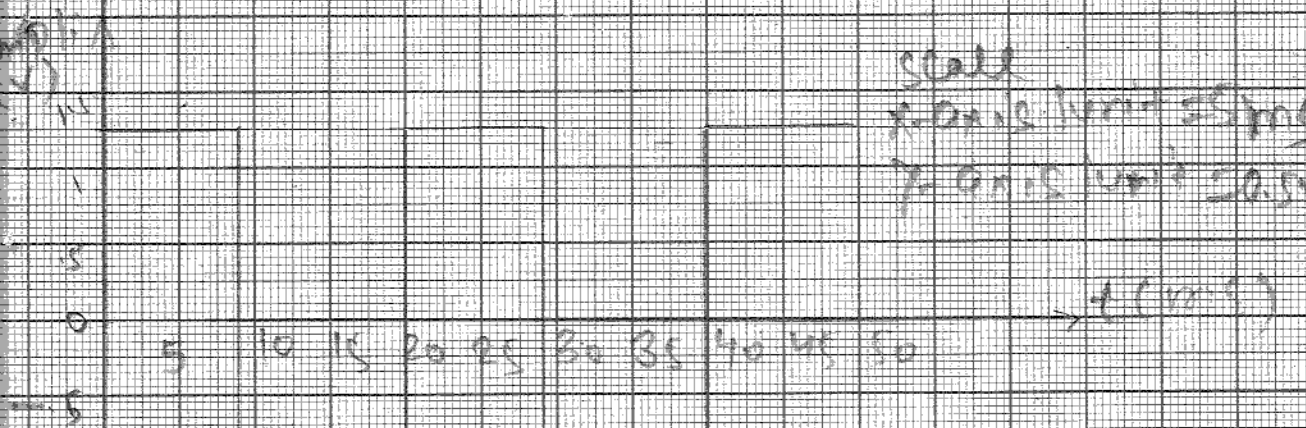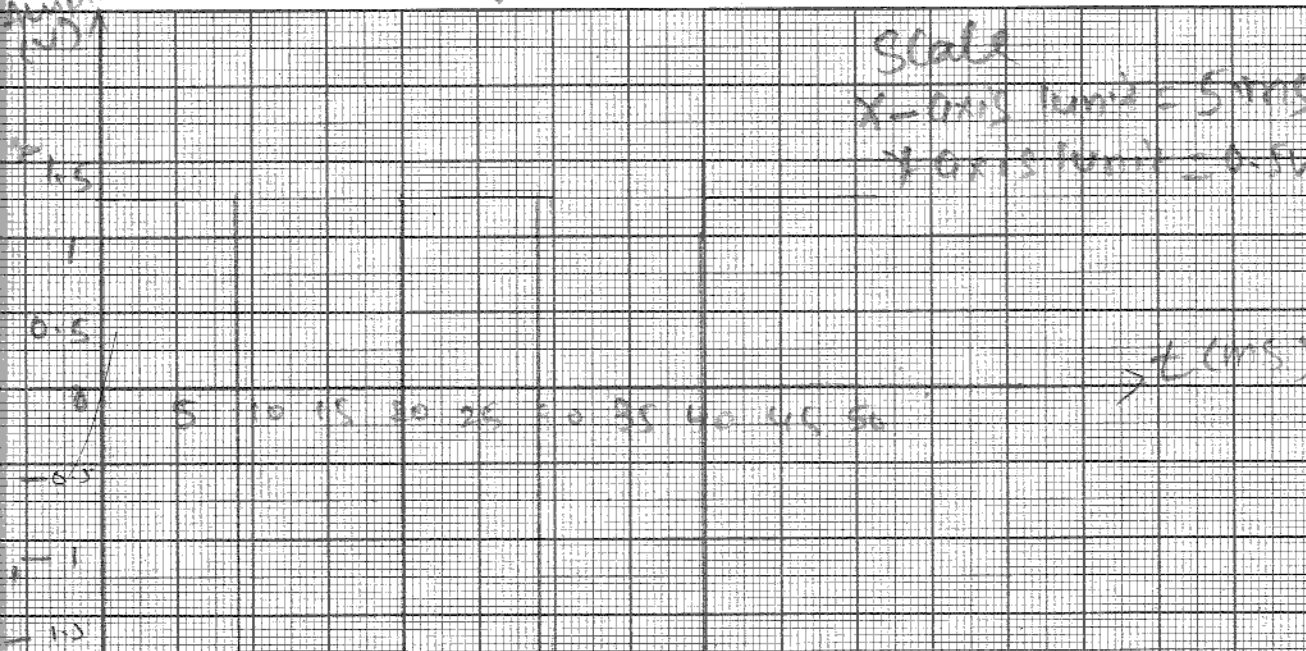


THEORY:-

An integrator can produce triangular waveform when its input is square wave. This means that a triangular wave generator can be found by simply connecting an integrator to square wave generator. The frequency of square wave and triangular wave are same. The frequency of triangular wave generator is limited of slow rate of op-amp. So, high slow rate of op-amp should be used for generation of relatively higher frequencies.

PROCEDURE:-

- (1) Connections are given as per the circuit diagram
- (2) Check the output of first op-amp, it should be a square wave.
- (3) Take the reading of frequencies
- (4) Take the reading of triangular wave at output and draw the respective graph

MODEL GRAPH

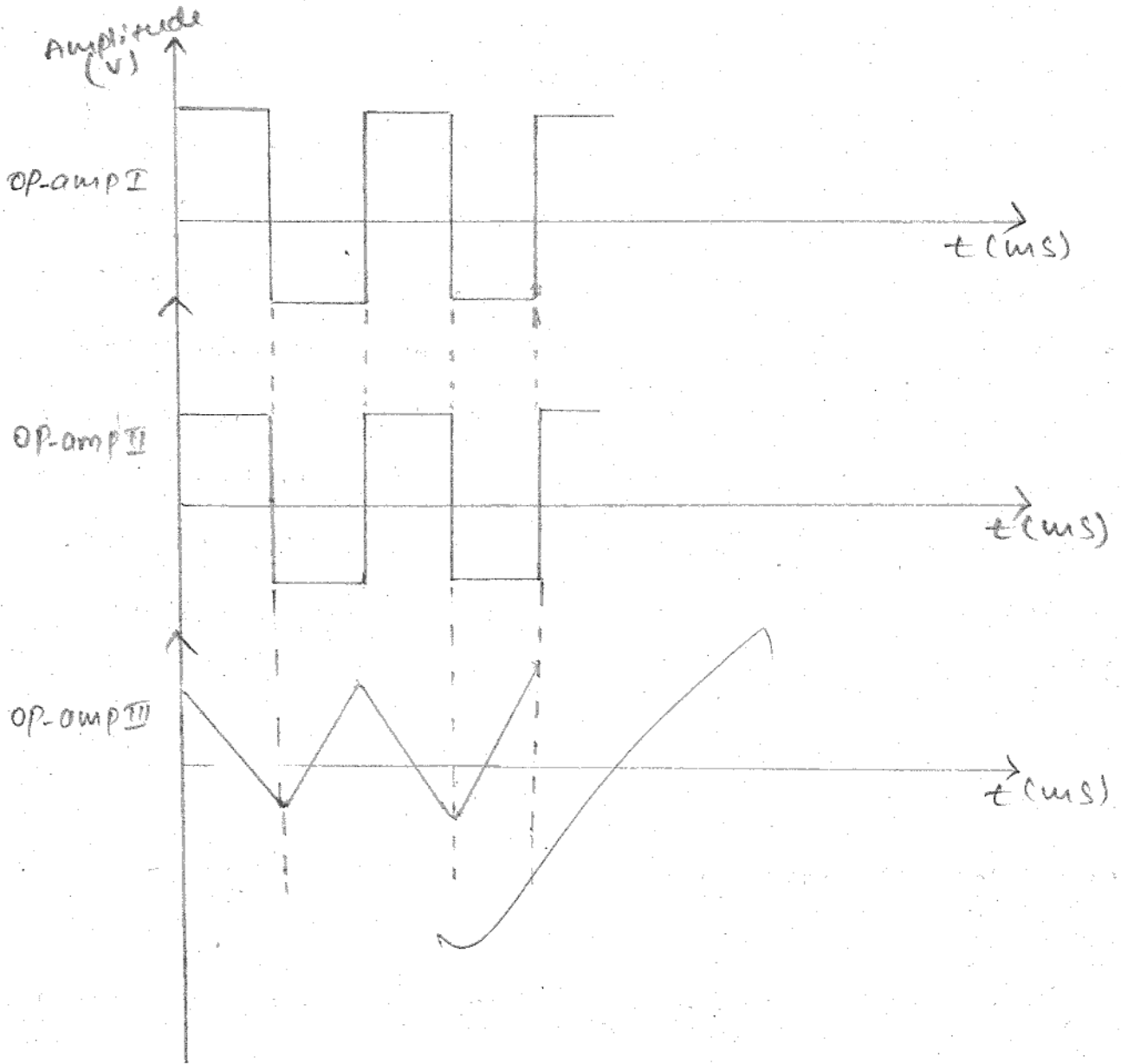

~~Result~~ :- Thus the waveform generator is constructed and triangular waveform is generated and output is verified