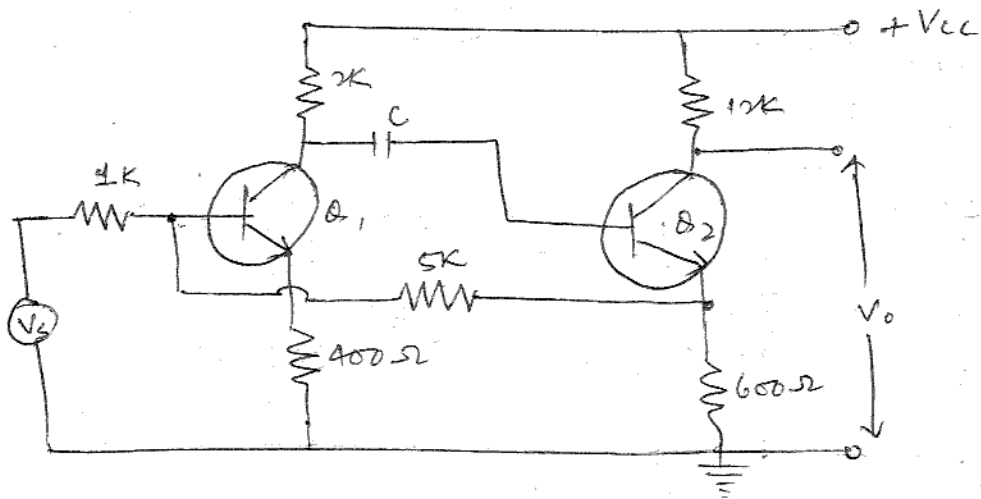


Ⓕ solution!




Step-1: Identify topology.

- The feedback is given from emitter of Q_2 to the base of Q_1 .
- If $I_o = 0$, the I_b current through $5K$ resistor is zero, hence it is current sampling.
- As I_b signal ~~signal~~ is mixed in shunt with i_p , the amplifier is current shunt I_b amplifier.

Step-2 & Step-3

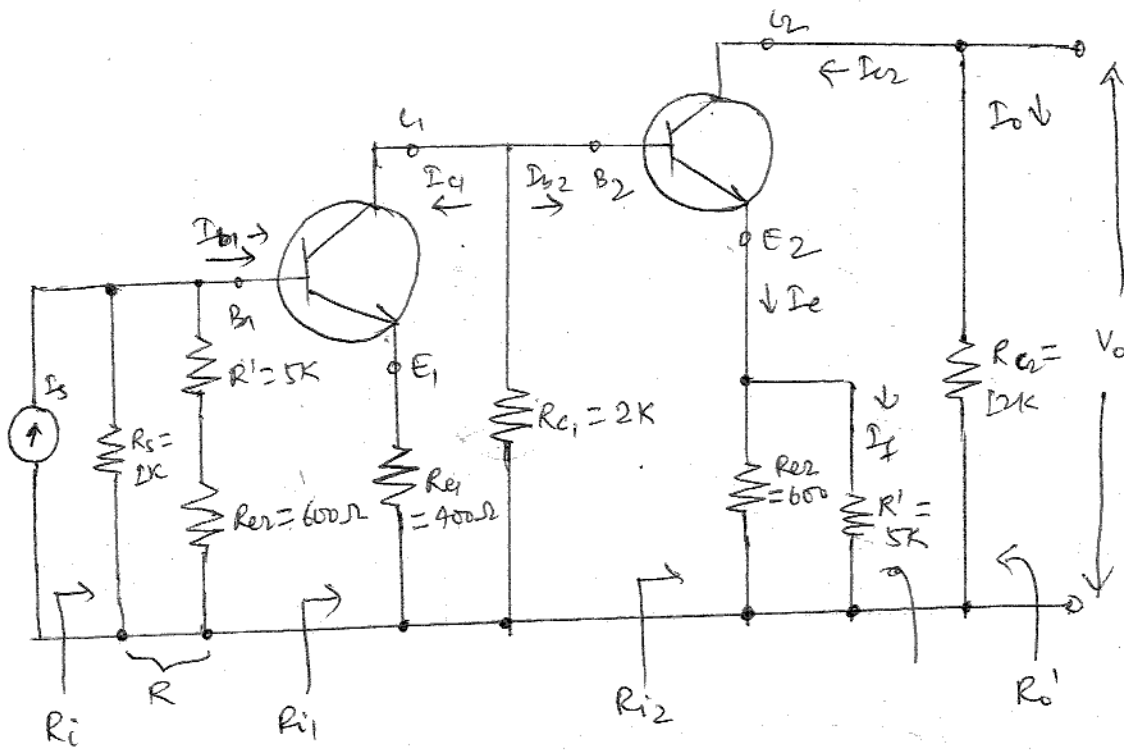- The i_p ckt of an amplifier, without I_b is obtained by opening the o/p loop of the emitter of Q_2 ($I_o = 0$).
- This places R' ($5K$) in series with R_e (600Ω) from base to emitter of Q_1 .
- The o/p ckt. is found by shorting the i_p node, i.e. making $V_i = 0$. This places R' ($5K$) in parallel with R_e . The resultant equivalent ckt. can be drawn as,



Step-4 : To find open circuit transfer gain.

$$A_v = \frac{V_o}{I_s} = \frac{-I_{c2}}{I_s}$$

$$A_v = \frac{-I_{c2}}{I_s} = \frac{-I_{c2}}{I_{b2}} \cdot \frac{I_{b2}}{I_{c1}} \cdot \frac{I_{c1}}{I_{b1}} \cdot \frac{I_{b1}}{I_s} \quad \text{--- (1)}$$

We know that,

$$\left. \begin{aligned} \frac{-I_{c2}}{I_{b2}} = A_{v2} = -h_{fe} = -50 \\ \frac{I_{c1}}{I_{b1}} = A_{v1} = h_{fe} = 50 \end{aligned} \right\} \text{--- (2)}$$

from above fig

$$\frac{I_{b2}}{I_{c1}} = \frac{-R_{c1}}{R_{c1} + R_{i2}} = \frac{-2K}{2K + \left[\frac{0.6 \times 5}{0.6 + 5} \right]} \quad \left[\because R_{i2} = R_{e2} || R_4 \right]$$

$$= \frac{-2K}{2K + 0.52} \quad \text{--- (3)}$$

$$R_{i2} = h_{ie} + (1 + h_{fe}) \left(\frac{0.6 \parallel 5}{0.6 + 5} \right)$$

$$= h_{ie} + 51 \times \left(\frac{0.6 \times 5}{0.6 + 5} \right)$$

$$= 1.5 + 51 \times 0.536$$

$$R_{i2} = 28.82 \text{ k}\Omega$$

$$\therefore \frac{I_{b2}}{I_{c1}} = \frac{-2}{2 + 28.82} = -0.0649$$

$$\therefore \boxed{\frac{I_{b2}}{I_{c1}} = -0.0649}$$

Again,

$$\frac{I_{b1}}{I_{b2}} = \frac{R}{R + R_{i1}}$$

$$R = 1 + (51 \parallel 0.6) \quad R = 211.56$$

$$= \frac{1 + 3}{5.6} \quad = \frac{5.6}{6.6} = 0.848$$

$$\& R_{i1} = h_{ie} + (1 + h_{fe}) \times R_{e1}$$

$$= 1.5 + 51 \times 0.4$$

$$= 21.9$$

$$\therefore \frac{I_{b1}}{I_{b2}} = \frac{0.848}{0.848 + 21.9} = 0.0372$$

$$\boxed{\frac{I_{b1}}{I_{b2}} = 0.0372}$$

$$\therefore A_v = (-50) \times (-0.0649) \times 50 \times (0.0372) = 6.0357$$

$$\boxed{A_v = 6} \quad //$$

$$R_{i2} = R_{i1} \parallel R'$$

Step-5: To Calculate β

$$\beta = \frac{I_f}{I_o} = \frac{R_{eq}}{R_{eq} + R_1} = \frac{0.6}{0.6 + 5} = 0.107$$

$$\boxed{\beta = 0.107}$$

Step-6: To Calculate D , A_{if} , A_{vf} , β_{if} , R_{of}

$$D = 1 + \beta A_1$$

$$= 1 + 0.107 \times 6$$

$$\boxed{D = 1.642}$$

$$A_{if} = \frac{A_1}{D} = \frac{6}{1.642} = \boxed{3.654}$$

$$A_{vf} = \frac{V_o}{V_s} = \frac{-\beta_{if} R_{eq}}{\beta_s R_s} = \frac{A_{if} R_{eq}}{R_s}$$

$$= \frac{3.654 \times 12}{1}$$

$$= \boxed{43.848}$$

$$R_i = R_1 \parallel R_{i1}$$

$$= 0.848 \parallel 21.9$$

$$= \frac{0.848 \times 21.9}{22.748}$$

$$= 0.81638 \text{ k}\Omega$$

$$\boxed{R_i = 816.38 \Omega}$$

$$R_{sf} = \frac{R_i}{\beta} = \frac{816.38}{1.642} = \boxed{497.186 \Omega}$$


$$R_o = \infty$$

$$\boxed{R_{of} = R_o \beta = \infty}$$

$$R_o' = R_o \parallel R_{ez} = \infty \parallel 12k = \boxed{12k}$$

$$R_{of}' = R_o' \frac{1 + \beta A_v}{1 + \beta A_v} = R_o' = \boxed{12k}$$

② Soln :

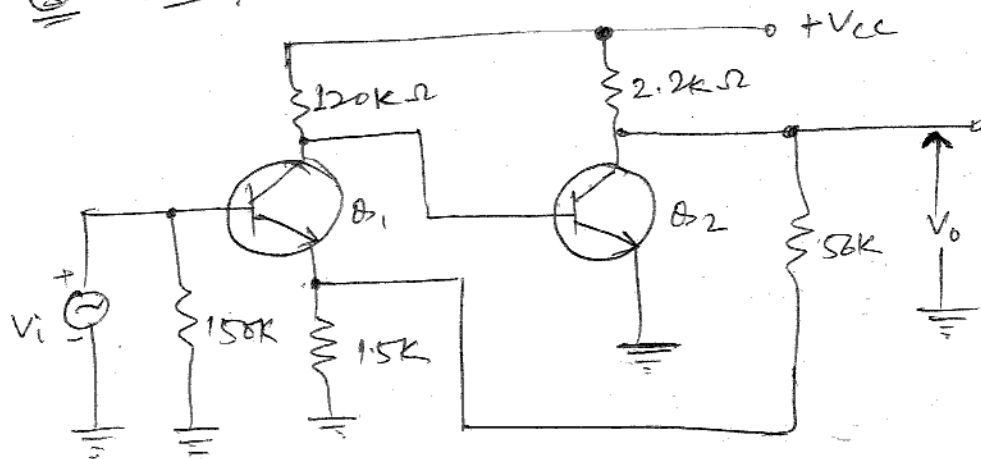


Step-I : Identify topology.

- The f/b voltage is applied across $15k$, which is in series with the i/p signal.
- Hence, f/b is voltage series feedback.

Step-II : To find the i/p and o/p circuit.

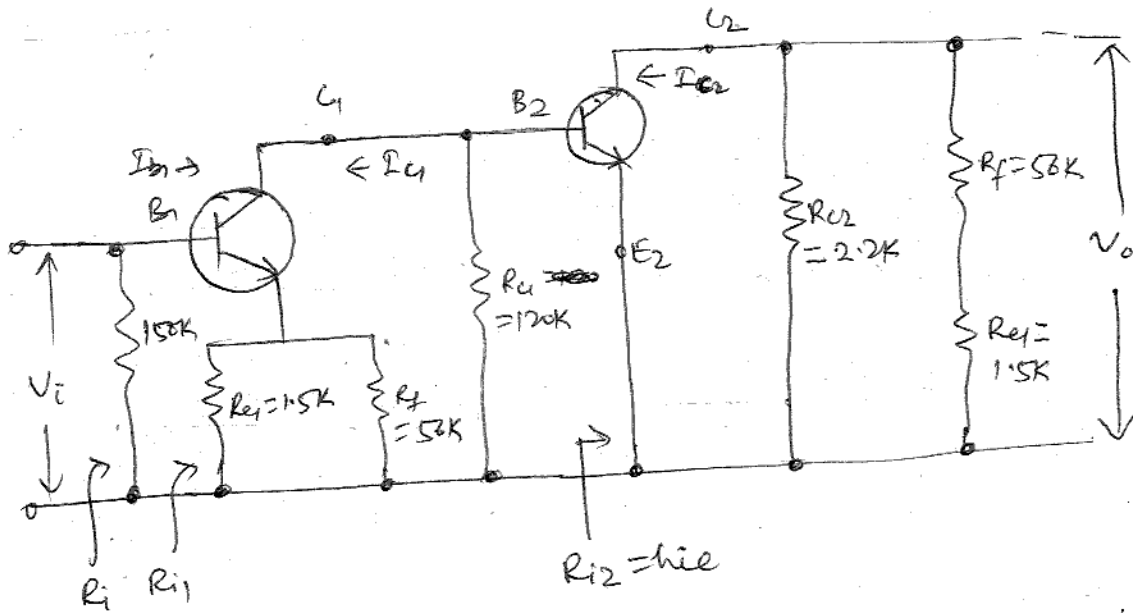- To find the i/p circuit, set $V_o = 0$, which gives parallel combⁿ of R_{e1} with R_f at E_2 .
- To find o/p ckt, set $I_i = 0$ by opening the i/p node, E_1 at emitter of Q_1 , which gives the series combination of R_f and R_{e1} across the o/p . The resultant R_o is given below.



Step-4: Find the open loop voltage gain (A_v)

$$\begin{aligned} R_{L2} &= R_{C2} \parallel (R_f + R_{E1}) \\ (\text{loop 2}) &= 2.2 \parallel 57.5 \\ &= \frac{2.2 \times 57.5}{59.7} \end{aligned}$$

$$R_{L2} = 2.12 \text{ K}$$

Since, $\omega_{oe} R_{L2} = 10^{-6} \times 2.119 \text{ K} < 0.1$

\therefore The approximate analysis can be used as

$$A_{i2} = -h_{fe} = -200$$

$$R_{i2} = h_{ie} = 2 \text{ k}\Omega$$

$$A_{v2} = \frac{A_{i2} R_{L2}}{R_{i2}} = \frac{-200 \times 2.12}{2}$$

$$A_{v2} = -212$$

$$R_{u1} = R_{C1} \parallel R_{i2} = 120 \parallel 2 = \frac{120 \times 2}{122}$$

$$R_{u1} = 1.967 \text{ K}$$

since, $h_{fe} = 10^{-6} \times 1.967 < 0.1$.

$$\therefore A_{i1} = -h_{fe} = -200$$

$$R_{i2} = h_{ie} + (1+h_{fe}) R_e$$

$$= 2 + (1+200)(1.5 \parallel 50)$$

$$= 2 + 201 \times \frac{1.5 \times 50}{57.5}$$

$$= 2 + 293.63$$

$$\boxed{R_{i1} = 295.63 \text{ K}}$$

$$A_{v1} = \frac{A_{i1} R_{e1}}{R_{i1}} = \frac{-200 \times 1.967}{295.63}$$

$$\boxed{A_{v1} = -1.33}$$

Now, the overall gain without feedback is

$$A_v = A_{v1} \times A_{v2} \\ = (-1.33) (-212)$$


$$\boxed{A_v = 282}$$

Step-5: Calculate β .

$$\beta = \frac{V_f}{V_o} = \frac{2 \times 1.5 \text{ K}}{2(50 \text{ K} + 1.5 \text{ K})}$$

$$\beta \approx \frac{1.5}{57.5}$$

$$\boxed{\beta = 0.026}$$

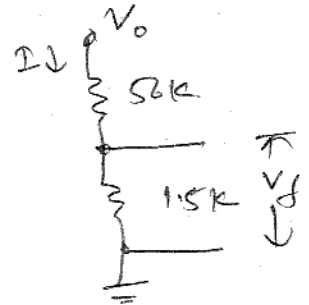

Step-6: To calculate D , A_{vf} , R_{if} , R_{of}

$$D = 1 + \beta A_v \\ = 1 + (0.026) 281.82$$

$$D = 8.327$$

$$A_{vf} = \frac{A_v}{D} = \frac{282}{8.327} = 33.86 //$$

$$R_i = R \parallel R_{ii} \\ = 150 \parallel (1.5 \parallel 56) \\ = 150 \parallel \left(\frac{1.5 \times 56}{1.5 + 56} \right) = 150 \parallel$$

$$= 150 \parallel 295.63$$

$$= \frac{150 \times 295.63}{150 + 295.63} = \frac{44344.5}{445.63}$$

$$R_i = 99.5K$$

$$R_{if} = R_i \times D \\ = 99.5 \times 8.327$$

$$R_{if} = 828.53K //$$

$$R_o = \frac{1}{\text{Loc}} = \frac{1}{10^{-6}} = 10^6 = 1M\Omega //$$

$$R_{of} = \frac{R_o}{D} = \frac{10^6}{8.327} = 120K\Omega //$$


$$R_o' = R_o \parallel R_{o2} \parallel (R_f + R_{e1}) = R_o \parallel R_{o2}$$

$$= 1M \parallel 2.119K = 1000 \parallel 2.119K$$

$$= \frac{1000 \times 2.119}{1000 + 2.119} = 2.1145K //$$

$$R_{of}' = \frac{R_o'}{D} = \frac{2.1145}{8.327} = 254\Omega //$$

9) Soln:

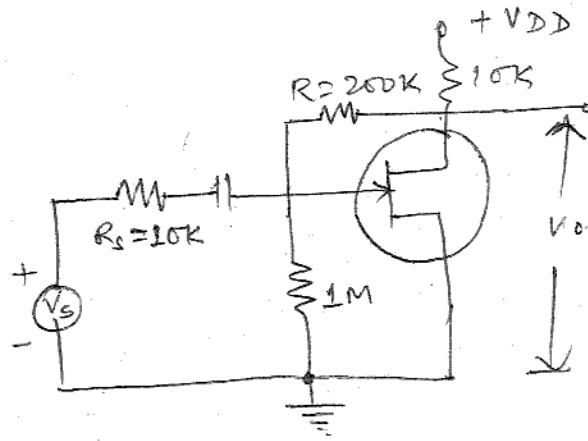


Step I: To identify the topology.


- By making $V_o = 0$, feedback current becomes zero. Hence, it is a voltage sampling. The f_b is fed in shunt with the i_p signal & thus the topology is voltage shunt feedback.

Step-II & Step-III: To find the i_p & o_p ckt.

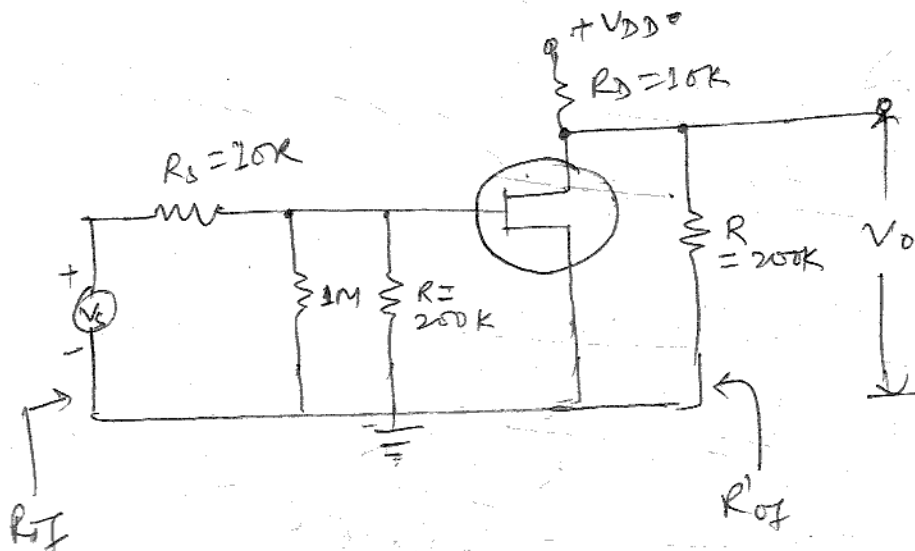- To find the i_p circuit, set $V_o = 0$. This places resistor R across the i_p .
- To find o_p ckt, set $V_i = 0$. This places resistor R' across the o_p . The resultant ckt is shown as,



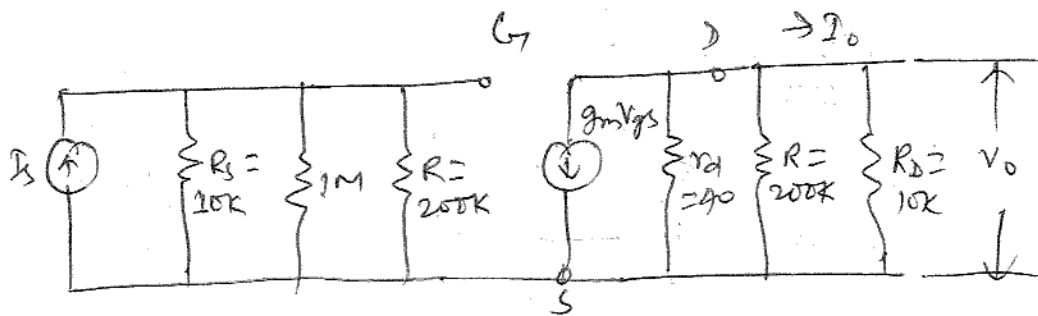Step-4: By replacing FET with its equivalent ckt.



Step-5: To find open loop transresistance

$$R_m = \frac{V_o}{I_s} = \frac{-g_m V_{gs} R_{eff}}{I_s}$$

$$\text{where } R_{eff} = r_d \parallel R \parallel R_D = 40 \parallel 200 \parallel 10 \\ = 7.69 \text{ K}\Omega$$

$$\begin{aligned} \& V_{gs} = I_s R_i \\ &= I_s (R_s \parallel 1M \parallel 200K) \\ &= I_s (10K \parallel 1M \parallel 200K) \\ &= 9.43 \times 10^3 I_s \end{aligned}$$

$$\begin{aligned} \therefore R_m &= \frac{-g_m \times 9.43 \times 10^3 I_s \times 7.69 \times 10^3}{I_s} \\ &= -2.5 \times 10^{-3} \times 9.43 \times 10^3 \times 7.69 \times 10^3 \end{aligned}$$

$$\boxed{R_m = -181.29 \text{ K}}$$

Step-6: To calculate β .

$$\beta = \frac{I_f}{I_o} = \frac{V_i - V_o}{V_o R} = -\frac{1}{R} \quad (\because V_o > V_i)$$

$$= \frac{-1}{200 \times 10^3} = \boxed{-5 \times 10^{-6}}$$

Step-7: To calculate D , A_{mf} , A_{vf} , R_{of} & R_{of}' .

$$D = 1 + \beta R_m$$

$$= 1 + (-5 \times 10^{-6}) (-181.29)$$

$$\boxed{D = 1.9}$$

$$R_{mf} = \frac{R_m}{D} = \frac{-181.29}{1.9} = \boxed{95 \text{K}}$$

$$\Rightarrow A_{vf} = \frac{V_o}{V_s} = \frac{V_o}{\beta R_s} = \frac{R_{mf}}{R_s} \quad \left(R_{mf} = \frac{V_o}{I_s} \right)$$

$$\begin{aligned} R_i &= \cancel{9.43 \times 10^3} \quad R_s \parallel R_1 \parallel R_2 = \cancel{100 \parallel 100} \\ &= 0.07 \parallel 1 \parallel 0.2 = 0.07 \parallel \left(\frac{1 \times 0.2}{1 + 0.2} \right) \\ &= (0.07 \parallel 0.267) \\ &= \frac{\cancel{0.01837}}{0.277} \end{aligned}$$

$$R_i = 9.43 \times 10^3 \Omega, \quad R_{if} = \frac{R_i}{D} = \frac{9.43 \times 10^3}{1.9}$$

$$\boxed{R_{if} = 4.963 \Omega}$$

$$R_o' = R_{of} = r_d \parallel R_1 \parallel R_2$$


$$= 40 \text{K} \parallel 200 \text{K} \parallel 20 \text{K}$$

$$= \boxed{7.69 \text{K} \Omega}$$

$$R_{of} = \frac{R_o'}{D} = \frac{7.69 \times 10^3}{1.9} = \boxed{4 \text{K} \Omega}$$

$$R_{of}' = \frac{R_{of}}{D} = \frac{4}{1.9} = \boxed{2.1 \text{K} \Omega}$$

(16) Soln:

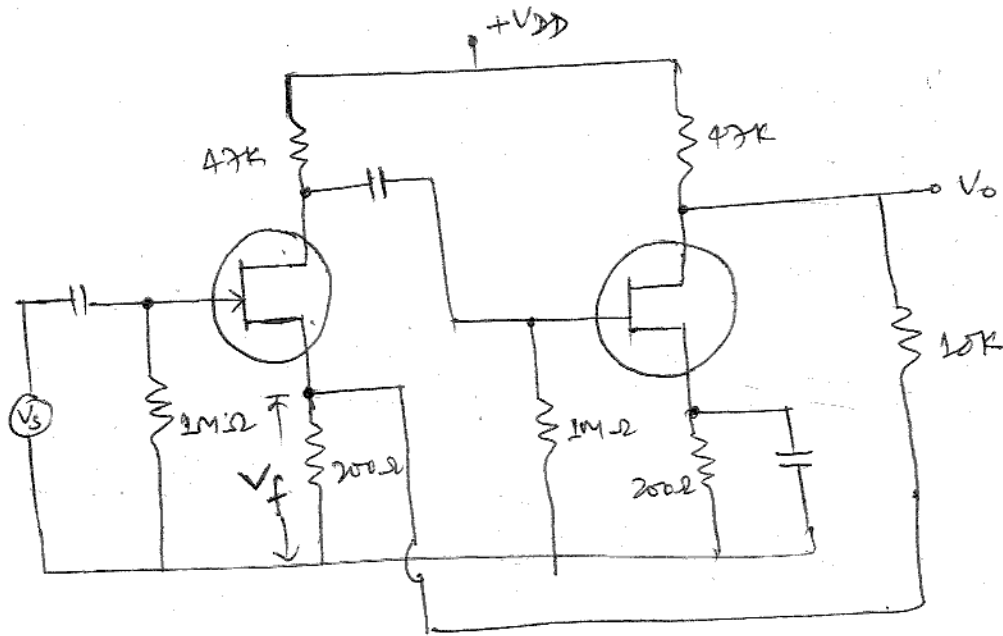


Step-2. To identify topology.


- By shorting o/p voltage ($V_o = 0$), V_f becomes zero & hence it.
- The f/b voltage is applied in series with the i/p voltage hence the topology is voltage series f/b .

Step-2 & Step-3. To find the i/p & o/p ckt.

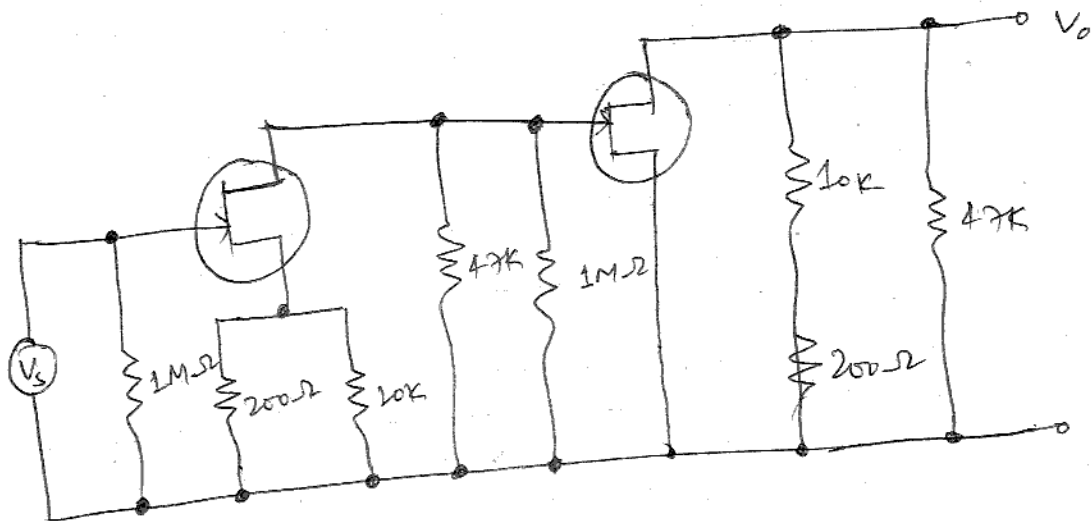- = To find the i/p ckt, set $V_o = 0$, where, $10K\Omega$ will be in parallel with 200Ω at first source.
- To find the o/p ckt, set $V_s = 0$, where, $10K\Omega$ and 200Ω are in series across the o/p .
The resultant ckt. diagram becomes:



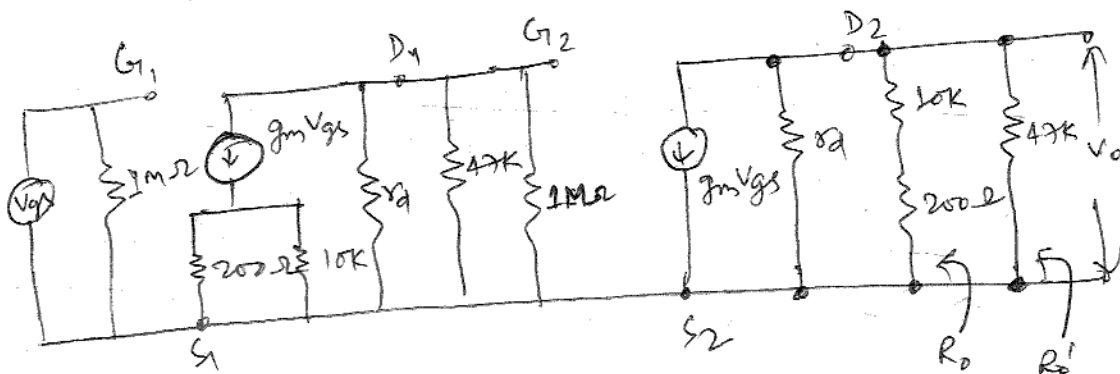Step-4: Replacing FET with its equivalent ckt.



Step-5: To find open loop transfer gain.

$$A_v = \frac{V_o}{V_s} = A_{v1} A_{v2}$$

$$A_{v2} = \frac{-\mu R_{L2}}{R_{in2} + r_d}$$

$$\text{Where } R_{in2} = (10K + 0.2K) \parallel 47K \\ = 8.38K$$

$$\therefore A_{v2} = \frac{-40 \times 8.38 \times 10^3}{8.38 \times 10^3 + 0 \times 10^3} = \boxed{-18.237}$$

$$A_{v1} = \frac{-\mu R_{\text{deff}}}{r_d + R_{\text{deff}} + (1+\mu)R_s}$$

$$\text{where } R_{\text{deff}} = R_D \parallel R_{G2} = 47k \parallel 1M\Omega \\ = 44.89k\Omega$$

$$\therefore A_{v1} = \frac{-40 \times 44.89 \times 10^3}{10 \times 10^3 + 44.89 \times 10^3 + (1+40)(10k \parallel 10.2)} \\ = -28.59$$

$$A_v = -28.59 \times (-18.237)$$

$$\Rightarrow \boxed{A_v = 521.39}$$

$$\text{Step-6: } \beta = \frac{V_f}{V_o} = \frac{200}{10 \times 10^3} = 0.02$$

Step-7:

$$\Rightarrow D = 1 + \beta A_v = 1 + 0.02 \times 521.39 = \boxed{11.42}$$

$$\Rightarrow A_{vf} = \frac{A_v}{D} = \frac{521.39}{11.42} = \boxed{45.62}$$

$$R_i = R_{G1} = 1M\Omega$$

$$\Rightarrow R_{if} = R_i \times D = 1 \times 11.42 = \boxed{11.42 M\Omega}$$


$$R_o = r_d = \boxed{10k\Omega}$$

$$\Rightarrow R_{of} = \frac{R_o}{D} = \frac{10}{11.42} = \boxed{0.8756 k\Omega}$$


$$R_o' = r_d \parallel R_2 = 10k \parallel 8.38k = \boxed{4.559 k\Omega}$$

$$\Rightarrow R_{of}' = \frac{R_o'}{D} = \frac{4.559 k\Omega}{11.42} = \boxed{0.399 k\Omega}$$

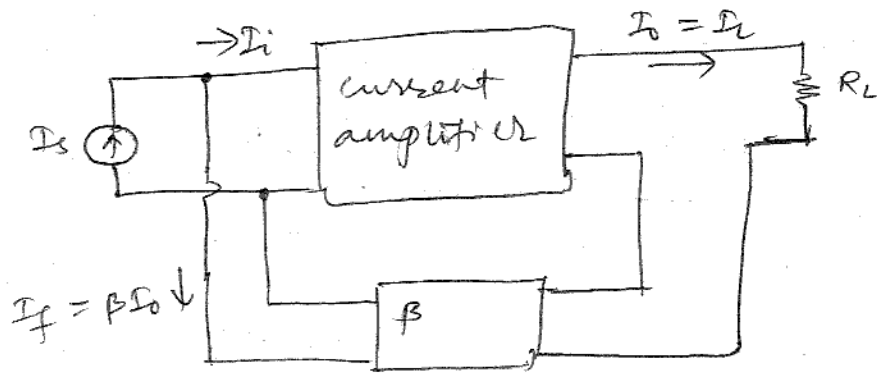⑥ effect of negative feedback on i_p & o_p resistance of current shunt ff amplifier.



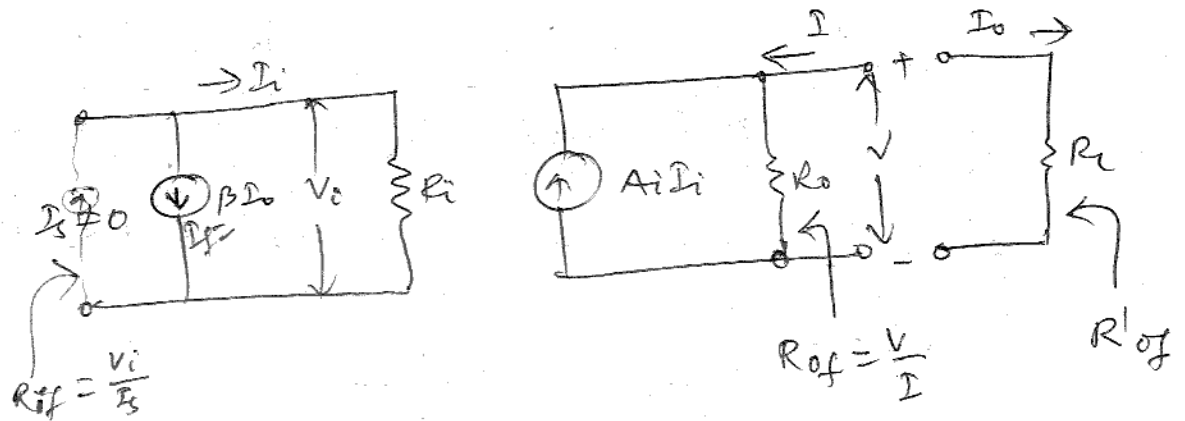to z current amplifier with current shunt-feedback.



In this topology, the o_p resistance can be measured by open circuiting the i_p source $I_s = 0$, and looking into the o_p terminals, with R_L disconnected, as shown in above fig.

Applying the KCL to the o_p node, we get,

$$I = \frac{V}{R_o} - A_i I_i \quad \text{--- (1)}$$

The i_p current is given as,

$$I_i = -I_f = -\beta I_o \quad (\because I_s = 0)$$

$$\boxed{I_o = \beta I} \quad (\because I = 0) \quad \text{--- (2)}$$

Solving eqn ① & ②.

$$I = \frac{V}{R_o} - A_i \beta I$$

$$I(1 + A_i \beta) = \frac{V}{R_o}$$

$$R_{of} = \frac{V}{I} = \frac{R_o(1 + A_i \beta)}{1} \quad \text{--- ③}$$

open loop current gain
without taking R_L in
account.

$$R_{of}' = R_{of} \parallel R_L$$

$$= R_o(1 + A_i \beta) \parallel R_L$$

$$= \frac{R_o(1 + \beta A_i) \cdot R_L}{R_o(1 + \beta A_i) + R_L} = \frac{R_o R_L}{R_o + R_L + \beta A_i R_o}$$

Dividing num. & den. by $R_o + R_L$, we get

$$R_{of}' = \frac{R_o R_L (1 + \beta A_i)}{R_o + R_L} \cdot \frac{1}{1 + \frac{\beta A_i R_o}{R_o + R_L}}$$

$$R_{of}' = \frac{R_o (1 + \beta A_i)}{(1 + \beta A_i)} \quad \text{--- ④}$$

$$\therefore R_o' = \frac{R_o R_L}{R_o + R_L} \quad \& \quad A_i = \frac{A_i R_o}{R_o + R_L}$$

Here, A_i is the open loop ^{current} gain taking R_L in account.

gain with feedback = $A_{if} = \frac{A_i}{1 + \beta A_i} \rightarrow$ decreases.

i/p resistance (R_{if}) = $\frac{R_i}{1 + \beta A_i} \rightarrow$ decreases

o/p resistance (R_{of}) = $R_o (1 + \beta G_m) \rightarrow$ increases.
 stability & frequency response \rightarrow improves & increase

frequency distortion \rightarrow reduces.

noise & non-linear distortion \rightarrow reduces.

Applying KCL to the i/p node, we get,

$$I_s = I_i + I_f$$

$$= I_i + \beta I_o \quad \text{--- (1)}$$

o/p current (I_o) = $\frac{A_i I_i R_o}{R_o + R_L}$

$V_o = I R$
 $V/R = I$

= $A_2 I_i$ --- (2) sub in (1)

where,

$$A_2 = \frac{A_i R_o}{R_o + R_L}$$

$$I_s = I_i + \beta (A_2 I_i)$$

$$= I_i (1 + \beta A_2)$$

The i/p resistance with f/b is given as,

$$R_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i (1 + \beta A_2)}$$

$$\therefore R_{if} = \frac{R_i}{(1 + \beta A_2)}$$