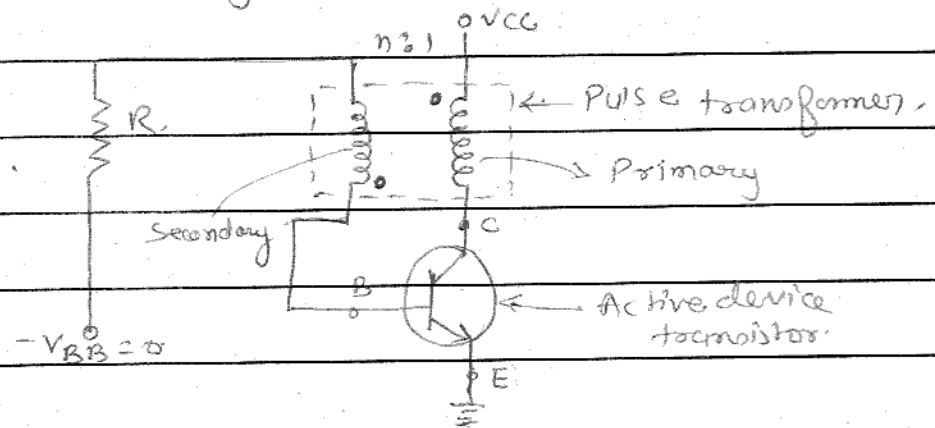


Q1. Explain with suitable diagram the performance of Monostable blocking Oscillator.

Solⁿ

A monostable blocking Oscillator using base timing is also called a triggered transistor blocking Oscillator.



One winding of the pulse transformer is in the collector circuit while the other is in the base circuit. The number of turns of transformer winding in base circuit is n -times the number of turns of transformer winding in the collector circuit.

A pulse transformer is basically a transformer which accepts the pulse at one winding and tries to produce a similar pulse at the other winding. It can produce inverted pulse of that applied to one winding if winding polarities are properly designed.

A resistance R is used in series with the base of transistor, which controls the timing i.e. pulse duration. Hence the circuit is called base timing blocking Oscillator. The pulse width can be varied in the range from nanosecond to microsecond. The pulse width depends on resistance R , other pulse transformer parameters and the circuit


Parameters to operate the circuit, a triggering signal is required to the collector momentarily (short time)

In the quiescent state, the transistor is off. The cut-in base-emitter voltage at room temp^r for germanium transistor is 0.1 V, while for a silicon transistor it is 0.5 V. Thus if a small voltage pulse gets applied to the collector, then as the turns ratio of the pulse transformer is $n:1$, it can produce a large signal which is enough to start the operation of circuit, such a small voltage pulse may be noise voltage or noise pulse. Thus unintentionally circuit may get triggered. In order to avoid such false triggering, at increased temp^r V_{BE} is applied to the base, keeping base-emitter junction reverse biased. But the magnitude of V_{BE} is of the order of few tenths of a volt and hence $|V_{BE}| < |V_{CC}|$.

Operation: Let a triggering signal is applied momentarily to the collector of transistor Q₁ such that collector voltage level reduces suddenly. The pulse transformer windings polarities are designed such that the voltage applied at the primary (collector) produce inverted signal at the secondary. The phase dots on the transformer indicate such a voltage inversion.

When this voltage is more than the cut-in voltage of the transistor, it starts conducting drawing current from the supply. This increases the collector current. Due to this drop across transformer winding in collector increases. This further lowers collector potential and increases base potential. This draws more collector current resulting further decrease in collector potential.

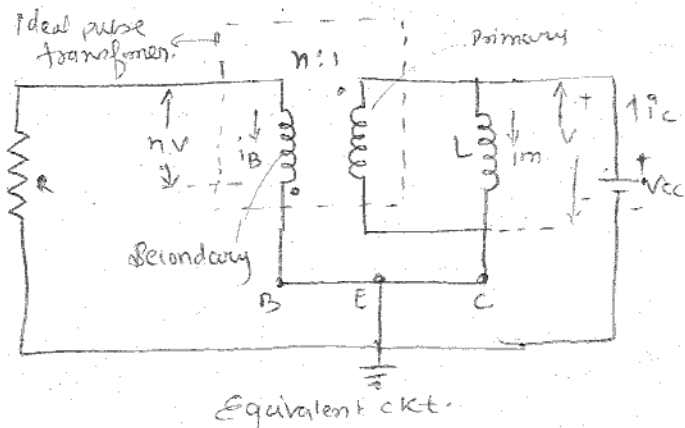
This cumulative action happens very quickly and time period required for the transistor to enter saturation from its off state, can be ignored.




Equivalent ckt.

The equivalent ckt of the pulse transformer neglecting resistance and shunt capacitance. The only important parameter is the shunt magnetising inductance L . The transformer is ideal. The leakage inductance σ of the winding also can be neglected. Similarly for the transistor the saturation voltage levels $V_{BE(sat)}$ and $V_{CE(sat)}$ are very small.

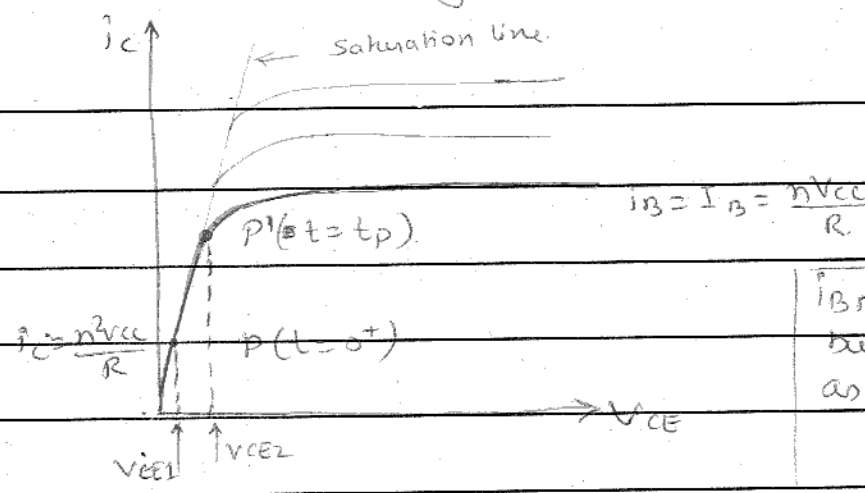Compared to V_{CC} and hence can be neglected -




Thus on the collector characteristics, the point P moves along the constant I_B characteristics to P' as shown in the fig. So operating point moves up the curve from P to P'. It can be noted that the corresponding change in V_{CE} is from V_{CE1} to V_{CE2} . Due to increased V_{CE} , the transformer primary voltage drop reduces. Due to increased V_{CE} , the transformer primary voltage drop reduces. Due to transformer enters into active region from saturation region. This can be observed from the characteristics. As base current reduces the collector current reduces which further reduces transformer primary voltage level and gain base current further reduces. As the loop gain exceeds unity in the active region this action is regenerative.

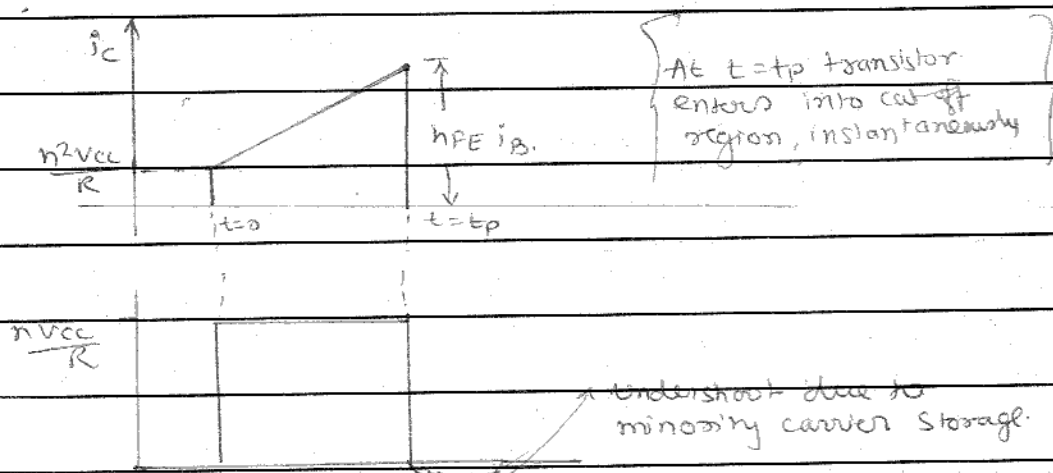

Sheet No.

Q2 a) Explain how sawtooth waveforms are generated using UJT.

5/23

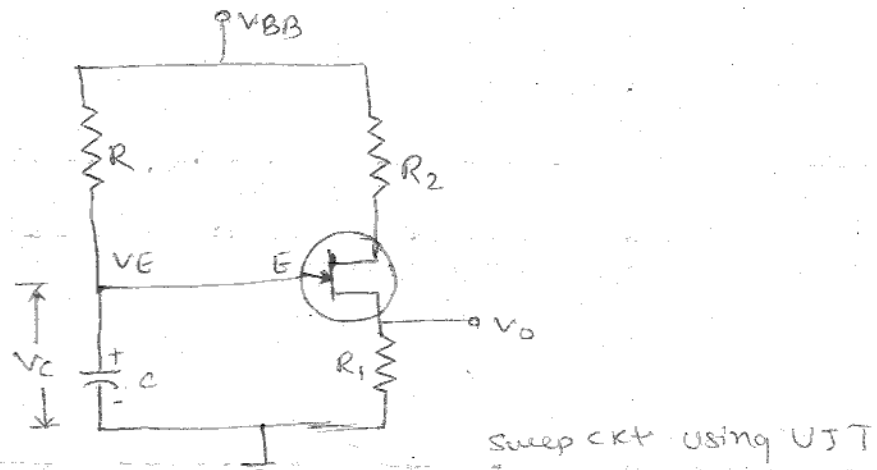

The exponential sweep ckt is used in which mechanical switch is used in parallel with the capacitor C. Many devices such as transistor, UJT, PET can be used as a switch. In this section, we will see how a UJT can be used as a switch to obtain the sweep voltage.

Operation.

Capacitor C gets charged through the resistance R towards supply voltage V_{BB} . As long as the capacitor voltage is less than peak voltage V_p , the emitter appears as an open circuit.

$$V_p = \eta V_{BB} + V_D \quad \text{--- (1)}$$

where


η = stand off ratio of UJT

V_D = cut-in voltage of diode.

When the capacitor voltage V_c exceeds the voltage V_p the UJT fires (switch ON). The capacitor starts discharging through $R_1 + R_B$, where R_B internal base resistance. As R_B is assumed negligible and hence capacitor discharge through R_1 .

Due to the design of R_1 , this discharge is very fast, and it produces a pulse across R_1 when the capacitor voltage falls below V_v . i.e. $V_{ce} = V_E = V_v$. the UJT gets turned OFF. The capacitor starts charging again.

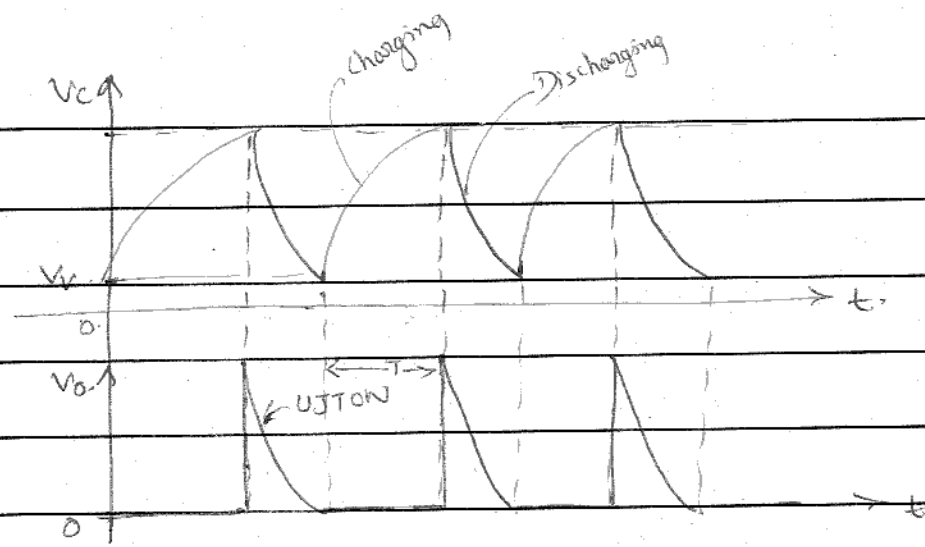The discharge time of the pulse is controlled by time constant CR_1 , while the charging time is controlled by time constant RC . The waveforms are shown in fig.



There is voltage drop across R_2 and voltage V_D across R_1 when UJT fires. The charging eqⁿ of the capacitor is given by,

$$V_c(t) = V_r + V_{BB} \cdot [1 - e^{-t/RC}] \quad \text{--- (2)}$$

But $V_c(t) = V_p$, at $t = T$

$$V_p = V_r + V_{BB} [1 - e^{-T/RC}] \quad \text{--- (3)}$$

Substituting value of V_p from eqⁿ (3) in eqⁿ (1) we have

$$\eta V_{BB} + V_D = V_r + V_{BB} [1 - e^{-T/RC}] \quad \text{--- (4)}$$

Neglecting V_D and V_r to get approximate relation for T

$$\eta = 1 - e^{-T/RC}$$


$$T = T_c = T_s = RC \ln \left[\frac{1}{1-\eta} \right] \quad \text{--- (5)}$$

$$f_0 = \frac{1}{T} = \frac{1}{RC \ln \left[\frac{1}{1-\eta} \right]} \quad \text{--- (6)}$$

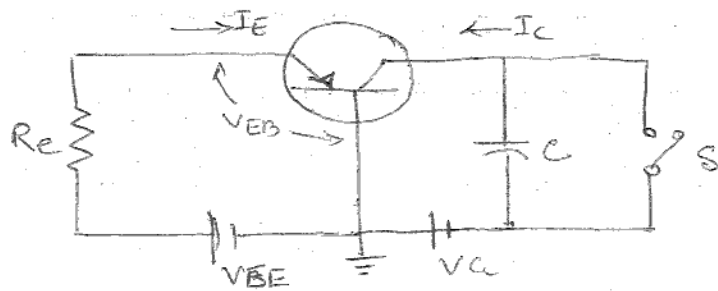Q.2b) Discuss about linearization using constant current sources

In a common base configuration, the collector current of the transistor is almost constant with fixed emitter current.

except for very small values of collector-to-Base voltage. This characteristics of common base configuration can be used to generate linear sweep by causing a constant current to flow into a capacitor.




Looking at the fig. the emitter current I_E can be given as

$$I_E = \frac{V_{EE} - V_{EB}}{R_e} \quad \text{--- (1)}$$

If we assume that V_{EB} remains constant with time after the switch S is opened, then the collector current will also be constant because $I_C = h_{fb} I_E \approx -\alpha I_E$. As a result, the capacitor C will charge linearly with time.

Fig (b) show h-parameter equivalent ckt. Here the transistor is replaced by its C_B hybrid parameters. Sweep voltage is represented by V_s and the effective input signal V_i is given as $V_i = V_{EE} - V_r \equiv V_i$. The V_r is the emitter threshold bias which brings the transistor just to the point of conduction.

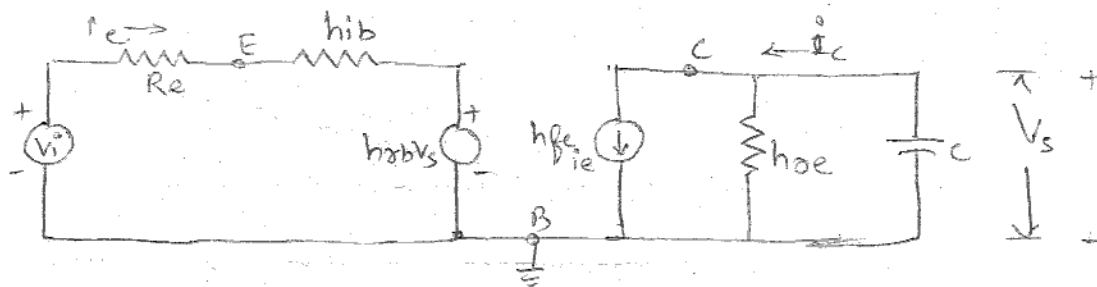

By applying KVL to the i/p ckt and KCL to o/p node.

$$V_i = i_e (R_e + h_{ib}) + h_{fb} V_s = V_i \quad \text{--- (2)}$$

$$i_c = i_e h_{fb} + h_{ob} V_s = -C \frac{dV_s}{dt} \quad \text{--- (3)}$$

Considering initial condition $V_s = 0$ at $t=0$, the Eqⁿ becomes

$$V_s = \frac{\alpha \tau V_i}{C (R_e + h_{ib})} (1 - e^{-t/\tau})$$

where $\alpha = -h_{fb}$, $V_i = V_{EE} - V_r$ and.

$$\frac{1}{\tau} = \frac{1}{C} \left(h_{ob} + \frac{\alpha h_{rb}}{R_e + h_{ib}} \right) \quad \text{--- (4)}$$

Expanding the exponential term into a power series in t/τ and retaining only the first term, we get.

$$V_s = \frac{\alpha V_i t}{C(R_e + h_{ib})} \quad \text{--- (5)}$$

$$= \frac{\alpha i_e t}{C} \quad \therefore i_e = \frac{V_i}{(R_e + h_{ib})}$$

$$= \frac{i_c t}{C} \quad \therefore i_c = \alpha i_e \quad \text{--- (6)}$$

The sweep amp. V_s can be obtained by substituting $t = T_s$ in eqn (6) as.

$$V_s = \frac{\alpha V_i T_s}{C(R_e + h_{ib})} \quad \text{--- (7)}$$

$$\therefore T_s = \frac{V_s C (R_e + h_{ib})}{\alpha V_i} \quad \text{--- (8)}$$

We know that, the Slope error given by ~~eqn (8)~~ ~~forms~~

$$e_s = T_s / \tau$$

$$e_s = \frac{V_s C (R_e + h_{ib})}{\alpha \tau V_i} \quad \text{--- (9)}$$

Substituting expression for τ from eqn (4) we have.

$$e_s = \frac{V_s C (R_e + h_{ib})}{\alpha V_i} \times \frac{1}{C} \left(\frac{h_{ob} + \alpha h_{rb}}{R_e + h_{ib}} \right)$$

$$e_s = \frac{V_s}{V_i} \left[\frac{h_{ob} (R_e + h_{ib}) + h_{rb}}{\alpha} \right] \quad \text{--- (10)}$$

* Slope Error: The first term in eqⁿ (10) represents the slope error introduced due to the fact that the collector current is not precisely constant due to shunting effect of h_{ob} even for constant emitter current.

* Change in the emitter current: In the h-parameter equivalent ckt shown in fig. (b) the generator $h_{ob} V_s$ represents the variation of the collector voltage on the $1/p$ circuit and it causes the change in emitter current as the sweep forms. The second term in the eqⁿ results from this change in emitter current.



* Effect of loading: If a load R_L is placed across C, then this resistance appears in parallel with $1/h_{ob}$ in fig. (b). Hence, the eqⁿ (10) h_{ob} must be replaced by $h_{ob} + 1/R_L$. This replacement gives serious in the slope error. Therefore the ckt should not be loaded appreciably to deteriorate linearity.

* Deterioration of linearity: To avoid this deterioration of linearity the sweep voltage must be applied to the load by means of an emitter follower.

* Effect of Temp^r: We know that the transistor ckt are temp^r dependent. The variation in transistor parameters does not affect the sweep junction linearly but does not make the sweep rate a fⁿ of temp^r. The emitter jⁿ voltage V_{EB} for a fixed current decreases about $2mV/^\circ C$. Hence from eqⁿ (10) the sweep speed $|I_c|/C = \alpha I_E/C$ increases with temp^r.

Q3 With a neat Diagram explain the Operation of Bootstrap Circuit (571)

Vol 13

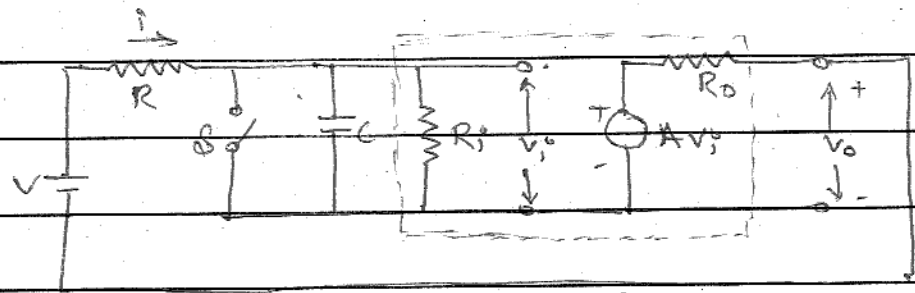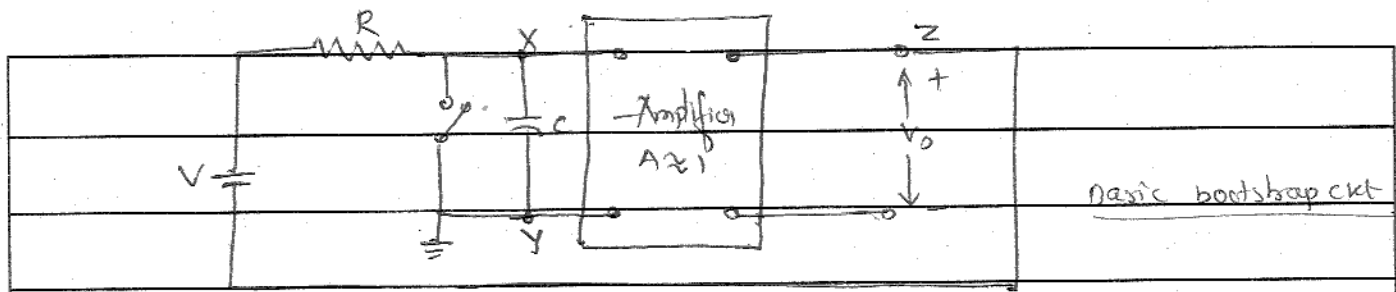


Looking

$$V_i = iR + AV_i - iR_o = 0$$

Q4 Draw the circuit diagram of monostable transistor blocking oscillator with emitter timing. Explain its operation with equivalent ckt during pulse formation.


Solⁿ

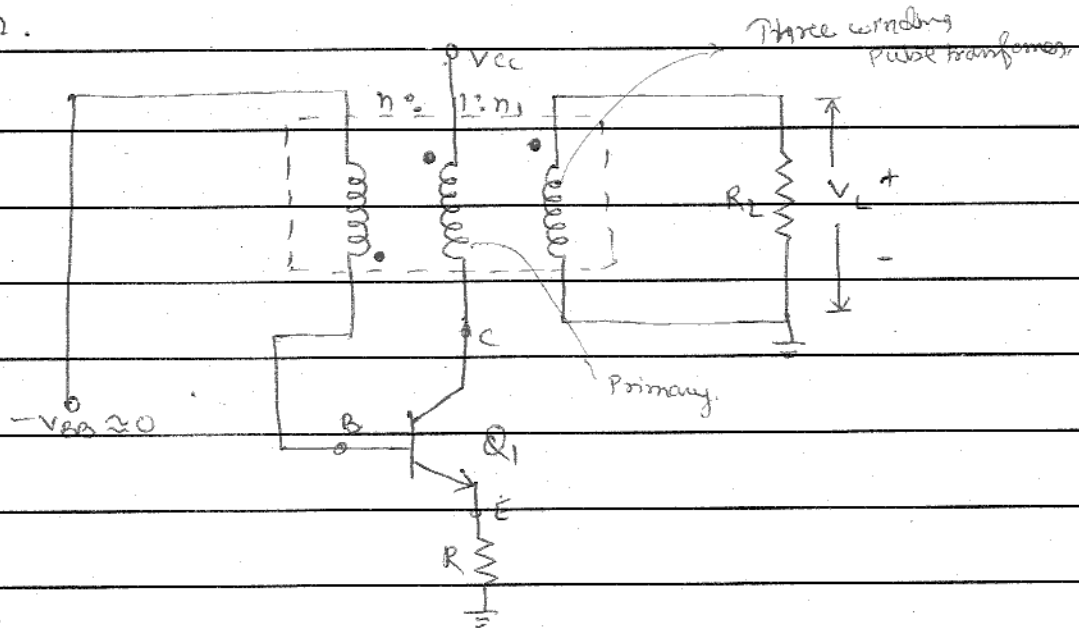

The circuit is also called triggered transistor blocking oscillator using emitter timing. This uses a resistance in the emitter circuit which controls the pulse width. The pulse transformer used is a three winding transformer. One winding is in the collector circuit which is primary winding. The second winding is in the base circuit which has n times as many turns as the collector winding. A load resistance R_L is connected across third winding which has n_1 times as many turns as the collector winding. The resistance R_L acts as load and also helps in improving damping. The base and collector windings must produce polarity inversion indicated by dots, while relative direction of third winding can be arbitrary. The circuit diagram of emitter timing ckt is shown.

x



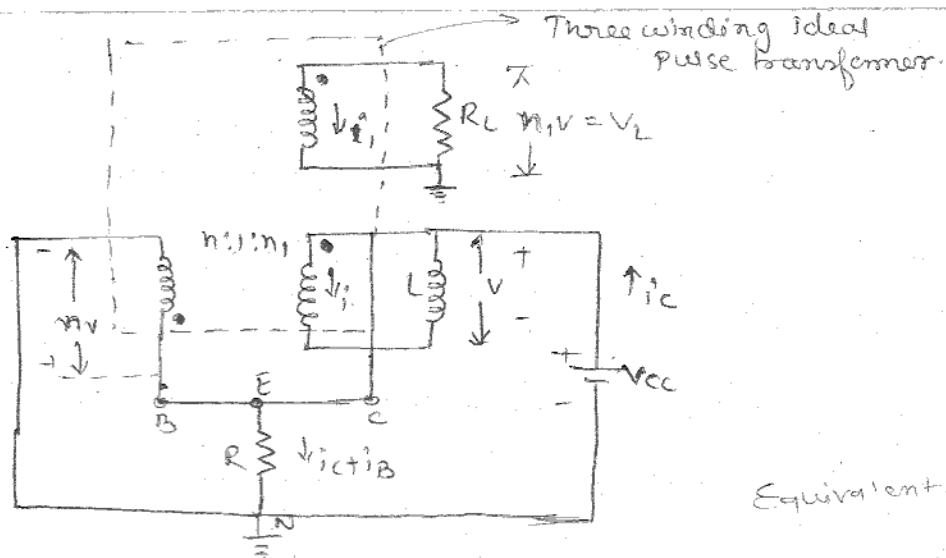
Some basic operation of the ckt is that of base timing circuit.






Assuming ideal transformer, neglecting leakage inductance, capacitance and winding resistance and neglecting transistor saturation voltages, the equivalent ckt can be shown in the fig.

For simplicity of analysis assume no. of turns of primary of transformer which is in collector circuit be 1. proportionally the number of turns of winding in base ckt. is n_2 and that of winding used to connect R_L is n_3 .

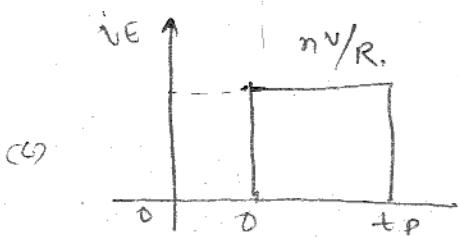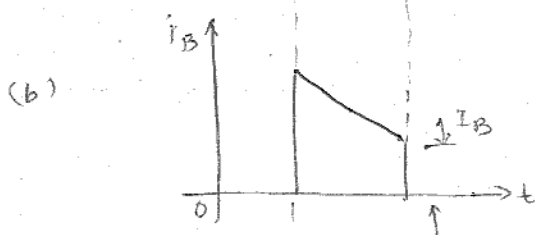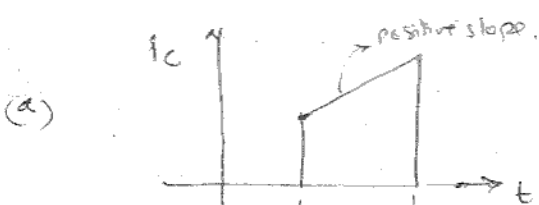Now V be the voltage across the primary collector winding, when transistor is in saturation. The corresponding voltage across secondary winding in base circuit is $n_2 V$. And due to phase inversion polarities of V and $n_2 V$ are opposite. The voltage across the resistance R_L is $n_3 V$ and the polarity is same as that of V .




Current waveforms

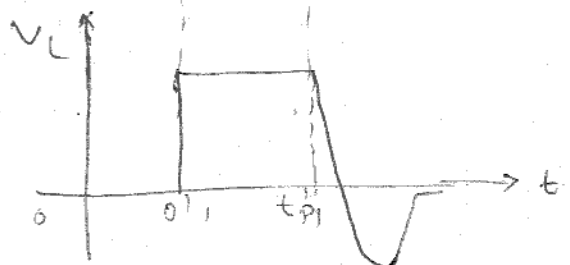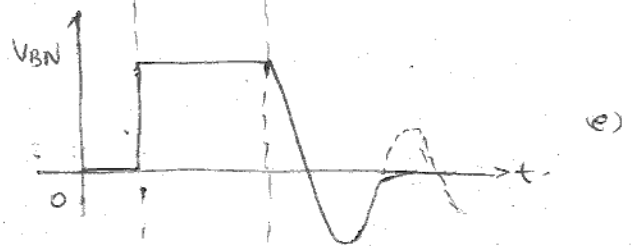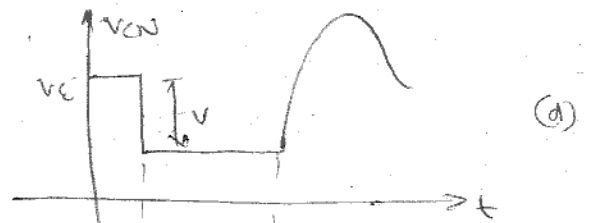


Voltage waveforms

Q5 Explain the basic principles of miller sawtooth generator circuit with the help of neat diagram.

Soln

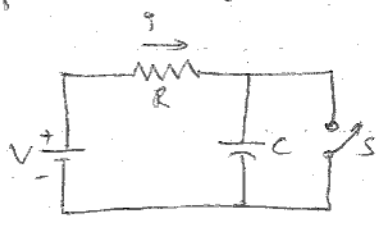

(a) Exponential charging of capacitor

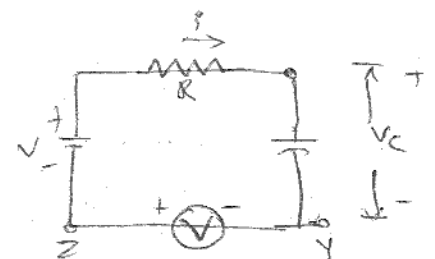

(b) Constant current charging of capacitor

The basic sweep circuit in which S opens to form the sweep. If we introduced an auxiliary variable generator V and if V is always kept equal to the voltage drop across C, the charging current will be kept constant at $i = V/R$ and perfect linearity can be achieved.


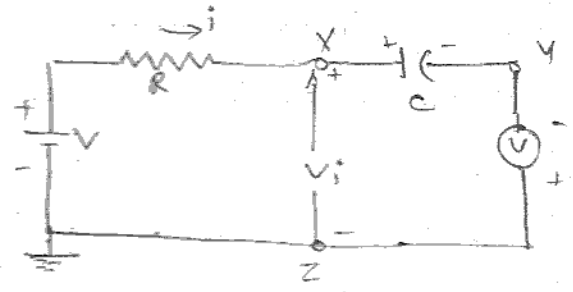


Fig (c) Point Z is grounded.

Let us consider the circuit in Fig (b) with its Z-terminal grounded as in Fig (c). With this ckt, linear sweep will appear between terminals Y and grounded (Z terminal) and it will increase in the negative direction. Let us now replace the auxiliary variable generator by an amplifier with output terminal YZ and input terminal XZ as shown in Fig (d). Since we have assumed that the magnitude of the voltage V equals the voltage V_c across the capacitor at every instant of time, then the i/p V_i to the amplifier is zero. We can say that point X behaves as a virtual ground. With this situation if we want to obtain finite output, the amplifier gain A should ideally be infinite. Such a need of amplifier can be satisfied by using operational

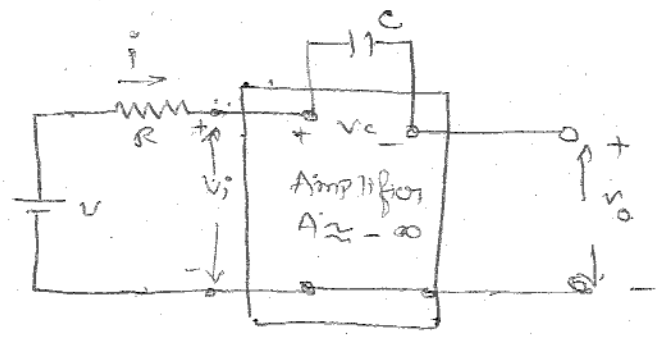

amplifier and ckt is recognized as the operational integrator amplifier. It is customarily referred to as a Miller integrator or Miller Sweep.

Figure 1 shows the Miller circuit with its equivalent ckt. R_i represents input impedance of the amplifier, A represents open circuit voltage gain and R_o is the o/p resistance. Here, switch is added at the closing of which the time-base waveform will start.


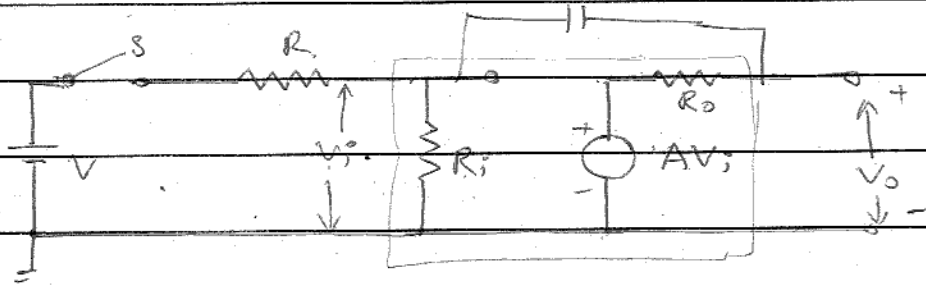


Figure 2 shows the Miller circuit with i/p circuit replaced by Thevenin's Equivalent. The i/p circuit components V , R and R_i are replaced by V' and R' as follows

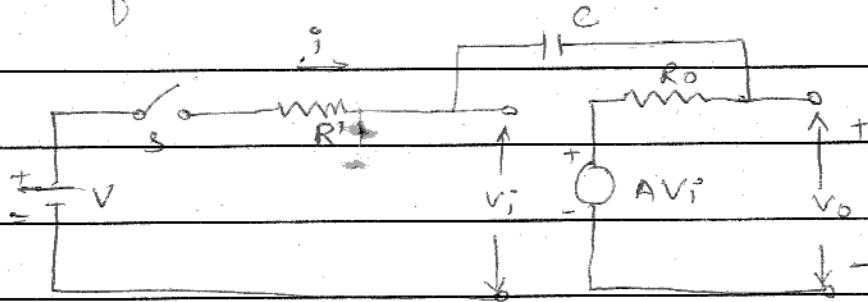

$$V' = \frac{VR_i}{R_i + R} = \frac{V}{1 + R/R_i} \quad \text{and} \quad \text{--- (1)}$$

$$R' = \frac{R_i R}{R_i + R} \quad \text{--- (2)}$$

Let us assume that at $t = 0^+$ voltage across capacitor is zero. Then neglecting R_o we can write:

$$V_i - AV_i = V_i(1 - A) = 0$$

$$V_i = AV_i = 0$$

Since R_o is neglected $AV_i = V_o$

$$V_i = AV_i = V_o = 0$$