

SCHMITT TRIGGER:-

Design:-

Given $V_{CC} = 12V$ $U_{TP} = 5V$ $L_{TP} = 3V$

$I_C = 2mA$ $I_B = 0.01 I_C$ $h_{FE}(\text{min}) = 100$

Calculation of R_E :-

$$U_{TP} = V_{B_2} = 5V$$

Voltage across R_E is $V_E = V_{B_2} - V_{BE}$
 $= 5 - 0.7 = 4.3V$

$$V_E = 4.3V$$

$$I_E = I_C = 2mA$$

$$R_E = \frac{V_E}{I_E} = \frac{4.3}{2 \times 10^{-3}} = 2.15k\Omega$$

$$R_E = 2.15k\Omega$$

Calculation of R_{C_2} :-

Taking Q_2 as saturated, $V_{CE}(\text{sat}) = 0.2V$

$$I_C R_{C_2} = V_{CC} - V_E - V_{CE}(\text{sat})$$
$$= 12 - 4.3 - 0.2 = 7.5V$$

$$R_{C2} = \frac{7.5}{I_{C2}} = \frac{7.5}{2 \times 10^{-3}}$$

$$R_{C2} = 3.75 \text{ k}\Omega$$

Calculation of R_2 !

$$I_2 = \frac{I_{C2}}{10} = 0.1 \times 2 \times 10^{-3}$$

$$I_2 = 0.2 \text{ mA}$$

$$R_2 = \frac{V_{B2}}{I_2} = \frac{5}{0.2 \times 10^{-3}}$$

$$R_2 = 25 \text{ k}\Omega$$

Calculation of R_{C1} , R_1 and R_B

$$I_{B2} = \frac{I_{C2}}{\beta_{\text{eff}}(\text{min})} = \frac{2 \times 10^{-3}}{100}$$

$$I_{B2} = 2 \times 10^{-5} = 20 \times 10^{-6} \text{ A}$$

$$I_{B2} = 20 \mu\text{A}$$

$$I_1 = I_2 + I_{B2} = 0.2 \times 10^{-3} + 2 \times 10^{-6} \text{ (2)}$$

$$= 2.2 \times 10^{-4} \text{ A}$$

$$I_1 = 0.22 \text{ mA}$$

$$I_1 = \frac{V_{CC} - V_{B2}}{R_{C1} + R_{B1}} = \frac{12 - 5}{R_{C1} + R_{B1}} = 0.22 \times 10^{-3}$$

$$R_{C1} + R_{B1} = \frac{7}{0.22 \times 10^{-3}} = 31.8 \text{ k}\Omega$$

$$R_{C1} + R_{B1} = 31.8 \text{ k}\Omega$$


II) Q_1 is ON, $V_i = \text{LTP}$ $V_{B2} = 3 \text{ V}$.

$$I_1 = \frac{V_{B2}}{R_2} = \frac{3 \text{ V}}{25 \times 10^3} = 0.12 \text{ mA}$$

$$I_1 = 0.12 \text{ mA}$$

$$I_{C1} = I_E = \frac{V_{B1} - V_{BE}}{R_{E1}} = \frac{3 - 0.7}{2.15 \times 10^3}$$

$$I_{C1} = I_E = 1.07 \text{ mA} //$$

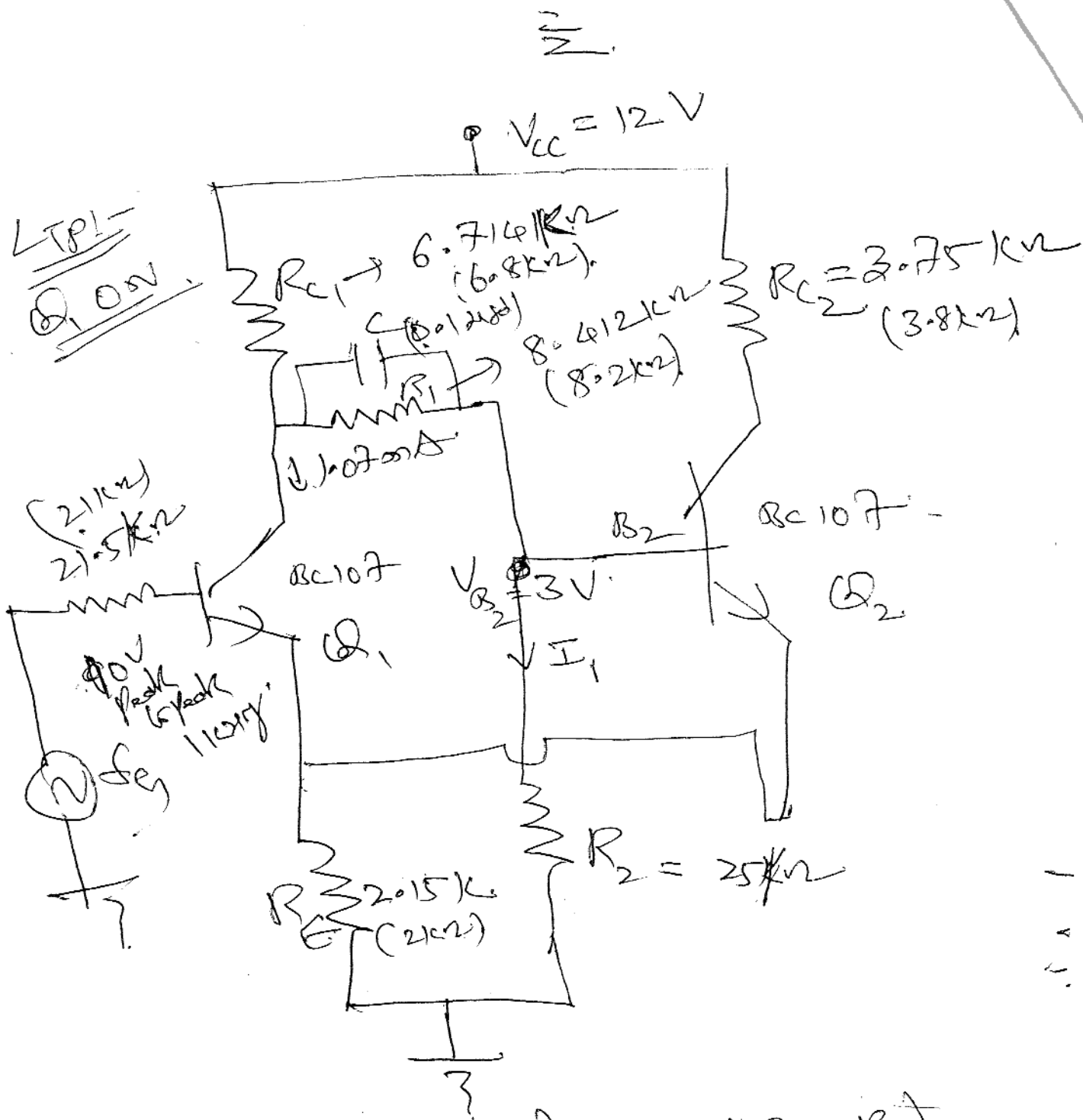

$$V_{CC} = R_{C1} (I_{C1} + I_1) + I_1 (R_1 + R_2)$$

$$V_{CC} = R_{C1} (I_{C1} + I_1) + I_1 (R_1 + R_2)$$

$$R_{C1} = \frac{V_{CC} - I_1 (R_1 + R_2)}{I_{C1} + I_1}$$

$$R_{C_1} = \frac{12 - (0.12 \text{ mA})(R_1 + 25 \text{ k}\Omega)}{(1.07 + 0.12) \text{ mA}}$$

$$R_{C_1} + R_1 = 31.8 \text{ k}\Omega$$

$$1.19 \times 10^{-3} R_{C_1} = 12 - 0.12 \times 10^{-3} R_1 - 3$$

$$1.19 \times 10^{-3} R_{C_1} + 0.12 \times 10^{-3} R_1 = 9$$

$$R_{C_1} + R_1 = 31.8 \times 10^3$$

$$1.19 \times 10^{-3} R_{C_1} + 1.19 \times 10^{-3} R_1 = 37.842$$

$$1.19 \times 10^{-3} R_{C_1} + 0.12 \times 10^{-3} R_1 = 9$$

$$1.07 \times 10^{-3} R_1 = 9$$

$$\therefore R_1 = \frac{9}{1.07 \times 10^{-3}} = 8.4112 \text{ k}\Omega$$

$$\therefore R_1 = 8.4112 \text{ k}\Omega$$

$$R_{C_1} = \frac{9 - 0.12 \times 10^{-3} \times 8.4112 \times 10^3}{1.19 \times 10^{-3}}$$

$$= \frac{9 - 1.0093}{1.19 \times 10^{-3}} = \underline{\underline{6.714 \text{ k}\Omega}}$$

$$R_{C_1} = 6.714 \text{ k}\Omega$$

VAMU
A U I T, PA 140000R.

D. OF G.C.T

FEET

PERIODICAL TEST-1. TIMES OVER REMAIN

Sub: Hospital Management — FEET SIZE 12 BOLD
Time: 2 hrs.

Sem: VII. ————— max marks: 50

Year/Branch: IV / B.P.G. ————— Date:

PART-A (7 x 2 = 14 Marks)

(Answer all the questions)

PART-B (3 x 12 = 36 Marks)

(Answer any three)


4) RC PHASE SHIFT OSCILLATOR:-

4.1 Aim:-

To design a RC phase shift oscillator and to find the frequency of oscillation.

4.2 Apparatus Required:-


Sl no.	Apparatus Required	Range	Quantity
1.	Resistors	68K 12K 4.7K 1K 3.3K	1 1 3 1 1
2.	Power supply	0-20V	1
3.	Transistor	BC107	1
4.	Capacitors	50nF	1
5.	CRO		1
6.	Bread Board. & S		1

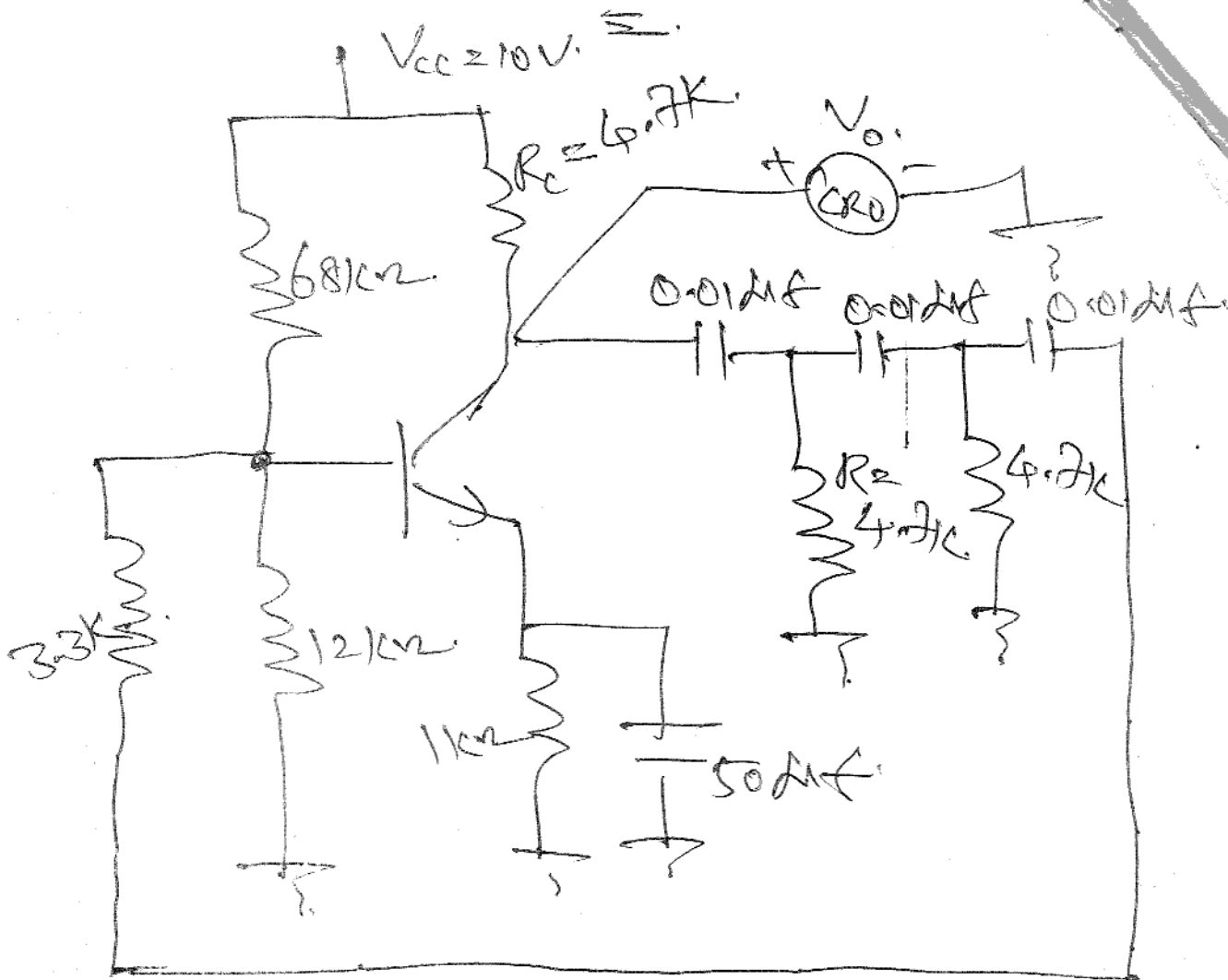

Tabulations :-

Amplitude volts	Time Period (T_0) (ms)

Wave Graph :-

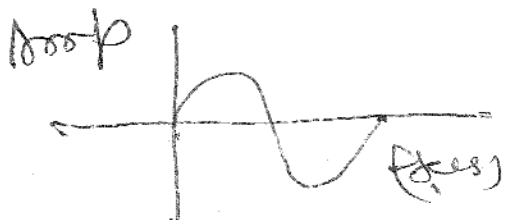

Calculations :-

Frequency :-
 $f = \frac{1}{T_0}$

4.3. Design specifications!

$$V_{CC} = 10V \quad I_{CQ} = 1mA \quad \beta = 345$$

$$f = 11kHz \quad C = 0.01\mu F \quad A_V = 29.$$

$$h_{ie} = 1.1k \quad S = 11.$$

Calculation of R_B and R_C !

$$V_{CG} = \frac{V_{CC}}{2} = \frac{10}{2} = 5V.$$

$$V_B = \frac{10}{10} = 1V.$$

$$I_{CG} = 1mA \quad \boxed{R_B = 1k\Omega}$$

$$V_{CC} = I_C R_C + V_{CG} + I_B R_B$$

$$10 = (1 \times 10^{-3}) R_C + 5 + 1.$$

$$\frac{4}{1 \times 10^{-3}} = R_C \quad \therefore R_C = 4k\Omega.$$

$$\boxed{R_C = 4.7k\Omega}$$

Calculation of R in the feedback network:-

$$f = 1.0479$$

$$f = \frac{1}{2\pi RC \sqrt{4k+6}}$$

$$k = 1$$

$$\therefore f = \frac{1}{2\pi RC \sqrt{10}}$$

$$\therefore R = \frac{1}{2\pi (1 \times 10^3) (0.01 \times 10^{-6}) \sqrt{10}}$$

$$R =$$

$$R_c = kR$$

$$k = 1$$

$$R_c = R$$

$$\therefore R = 4.7k$$

(Q-3)

To find R_3 :-

$$R_3 + I_{ie} = R.$$

$$R_3 = R - I_{ie}.$$

$$= 4.7k - 1.01k = 3.6k.$$

$$\boxed{R_3 = 3.3k\Omega}$$

Calculation of R_1 and R_2 :-

$$V_{BQ3} = \frac{V_{CC}R_2}{R_1 + R_2}.$$

$$V_{BE} = V_B - V_E.$$

$$\therefore V_B = V_{BE} + V_E = 0.7 + 1 = 1.7V.$$

$$\boxed{V_{BQ3} \approx 1.5V}$$

$$\beta = 1 + \frac{R_{B3}}{R_E}$$

$$(11-1) = \frac{R_B}{R_E} \quad \therefore R_B = 10 R_E$$

$$R_B = 10 \times 1K$$

$$\boxed{R_B = 10K}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2} = 10K$$

$$V_{BB} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_{BB}}{V_{CC}} = \frac{1.5}{10} = 0.15$$

$$10K = R_1 (0.15) \quad \therefore R_1 = \frac{10K}{0.15}$$

$$R_1 = 66.67K$$

$$\boxed{\therefore R_1 = 68K\Omega}$$

$\frac{2}{2}$

(4-4)

$$\frac{R_1 R_2}{R_1 + R_2} = 10K$$

$$\frac{10K}{68K} = \frac{R_2}{R_1 + R_2}$$

$$\frac{68K(R_2)}{R_1 + R_2} = 10K$$

$$\frac{68K}{10K} = \frac{R_1 + R_2}{R_2}$$

$$6.8 = 1 + \frac{R_1}{R_2}$$

$$\therefore \frac{R_1}{R_2} = 5.8$$

$$\therefore R_2 = \frac{R_1}{5.8} = \frac{68K}{5.8} = \underline{\underline{11.72K}}$$

$$\therefore R_2 = 12K \Omega$$

$$X_{CG} = \frac{h_{ie}}{1 + \beta} = \frac{1.01 \times 10^3}{1 + 365}$$

$$X_{CG} = 3.18 \Omega$$

$$C_G = \frac{1}{2\pi f X_{CG}}$$

$$= \frac{1}{2\pi (1 \times 10^3) (3.18)}$$

$$f = 50 \text{ kHz}$$

Result:-

Rc phase shift Oscillator is designed and the practical frequency is observed as _____.

HARTLEY OSCILLATOR

Aim:-

To design and Construct a Hartley Oscillator at the given operating frequency.

Apparatus required:-

<u>Sl. No.</u>	<u>Apparatus</u>	<u>Range</u>	<u>Quantity</u>
1.	Resistors	100k 22k 2k 1k	1. 1. 1. 1.
2.	RPS	(0-30)V	1.
3.	Transistor	BC107	1
4.	Capacitors	3.2mF 0.1μF 0.01μF	1 1 2
5.	Inductor	10mH	2
6.	CRO	30MHz	1.
7.	Bread Board.		1.

Q-3 Design Example:-

Design of feedback network:-

Given $L_1 = L_2 = 10\text{mH}$, $f = 20\text{kHz}$
 $V_{CC} = 12\text{V}$, $I_C = 3\text{mA}$, $S = 12$.

$$f = \frac{1}{2\pi \sqrt{(L_1 + L_2)C}}$$

$$\sqrt{C} = \frac{1}{2\pi \sqrt{L_1 + L_2} \cdot f}$$

$$C = \frac{1}{4\pi^2 (L_1 + L_2) f^2}$$
$$= \frac{1}{4\pi^2 (20 \times 10^{-3}) (20 \times 10^3)^2}$$

$$C = 3.2 \text{ nano farad}$$

Amplifier design - ²

(i) selection of R_C .

Gain formula is:

$$A_V = - \frac{\beta_{FE} R_{C_{eff}}}{h_{ie}}$$

Assume $V_{CE} = \frac{V_{CC}}{2} = \frac{12}{2} = 6V$.

$$V_G = I_G R_G = \frac{V_{CC}}{10} = \frac{12}{10} = 1.2V$$

$$V_{CC} = I_C R_C + V_{CE} + I_G R_G$$

$$R_C = \frac{V_{CC} - V_{CE} - I_G R_G}{I_C}$$

$$= \frac{12 - 6 - 1.2}{3 \times 10^{-3}}$$

$$R_C = 1.6 k\Omega$$

$$\boxed{R_C \approx 2 k\Omega}$$

(ii) Selection of R_G :-

$$I_E = I_G = 3 \text{ mA}$$

$$R_G = \frac{V_G}{I_G}$$

$$\boxed{R_G = 1 \text{ k}\Omega}$$

$$R_G = \frac{1.2}{3 \times 10^{-3}} = 400 \Omega \approx 1 \text{ k}\Omega$$

(iii) Selection of R_1 & R_2 :-

$$S = 1 + \frac{R_B}{R_G} = 12$$

$$\frac{R_B}{R_G} = 11 \quad R_B = (11)(R_G) = 11 \text{ k}\Omega$$

$$\boxed{R_B = 11 \text{ k}\Omega}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_B}{V_{CC}} = \frac{1.9}{12} = \underline{\underline{0.1583}}$$

$$V_{BE} = V_B - V_G$$

$$\begin{aligned} V_B &= V_{BE} + V_G \\ &= 0.7 + 1.2 \\ &= 1.9 \text{ V} \end{aligned}$$

$\frac{2}{2}$

$$11k = R_1 \cdot (0.1583)$$

$$R_1 = \frac{11k}{0.1583} = 69.49.$$

$$\therefore R_1 = 100k\Omega$$

$$\frac{R_2}{100k + R_2} = 0.1583$$

$$\frac{100k}{R_2} + 1 = \frac{1}{0.1583}$$

$$\frac{100k}{R_2} = 5.3171$$

$$R_2 = \frac{100k}{5.3171}$$

$$R_2 = 18.8k \quad R_2 = 22k\Omega$$

(ii) Output Capacitance (C_0):-

$$X_{C_0} = \frac{R_c}{10} = \frac{2 \times 10^3}{10} = 200\Omega$$

$$\frac{1}{2\pi f C_0} = 200 \quad \therefore C_0 = \frac{1}{(2)(3.14)(20 \times 10^3)(200)}$$

$$C_0 = 0.039 \times 10^{-6} \text{ farad}$$

$$C_0 = 0.01 \mu\text{fd}$$

2

(V) Input Capacitance (C_{in}): -

$$X_{C_{in}} = \frac{R_B}{10} = \frac{11 \times 10^3}{10} = 1.1 \text{ k}\Omega$$

$$\frac{1}{2\pi f C_{in}} = 1.1 \times 10^3$$

$$C_{in} = \frac{1}{2\pi (20 \times 10^3) (1.1 \times 10^3)}$$

$$C_{in} = 0.007 = 0.01 \mu\text{F} \\ \text{1 microfarad.}$$


(VI) Bypass Capacitance (C_F): -

$$X_{C_F} = \frac{R_E}{10} = \frac{1 \times 10^3}{10} = 100 \Omega$$

$$\frac{1}{2\pi f C_F} = 100$$

$$C_F = \frac{1}{2\pi (20 \times 10^3) (100)}$$
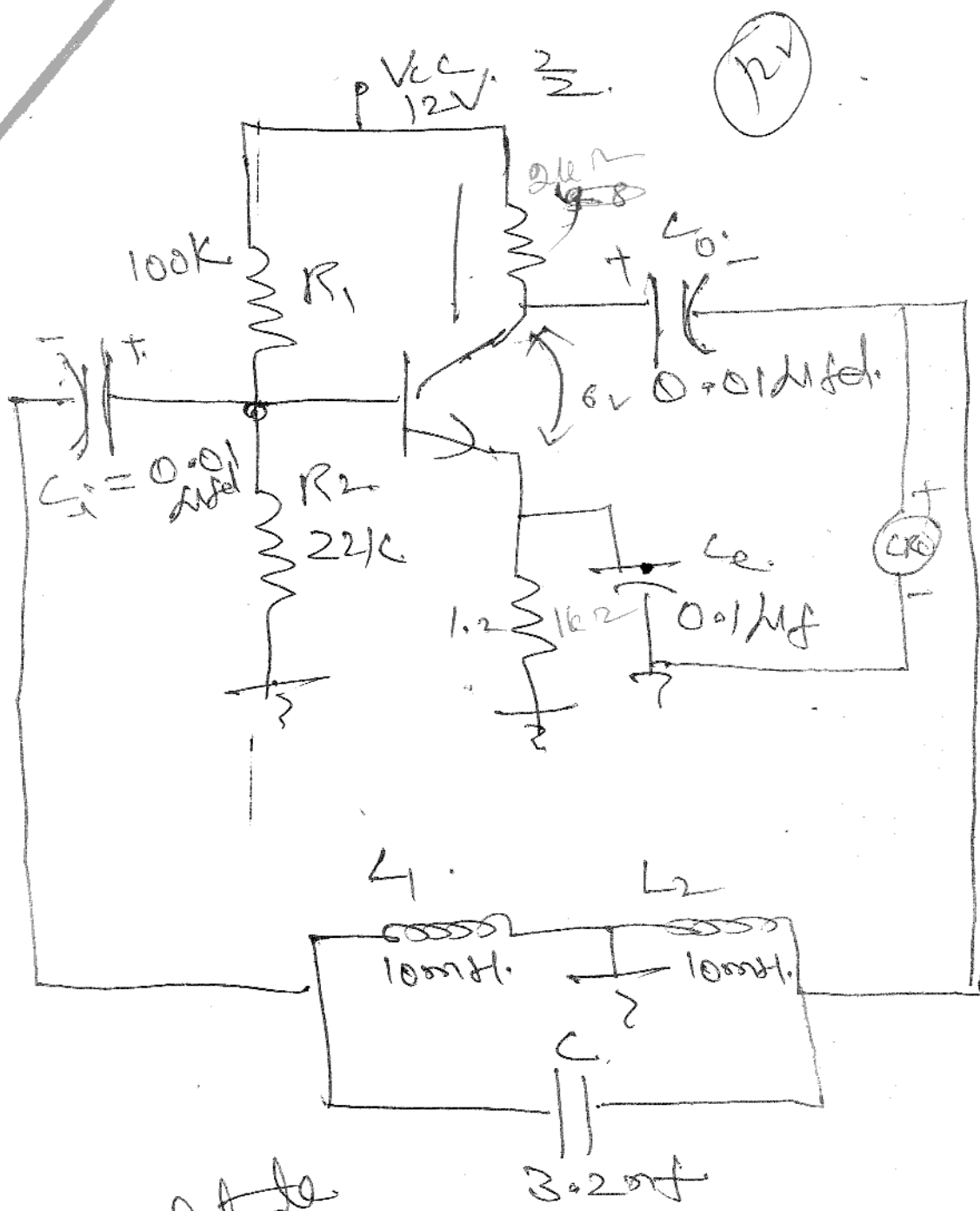
$$C_F = 0.079 \mu\text{F} = 0.1 \mu\text{F}$$



12V

Vcc 12V

100k

R1

2k

Co

C1 = 0.01

R2 22k

6V 0.01 microfarad

1.2k

Ce

0.01 microfarad

L1


L2

100mH

100mH

C 3.2mF

Amplitude

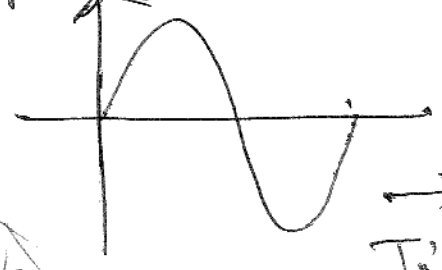

Time (msec)

2.30
6.62
1.13
10.15

Vce 9.5V
Vbe 1.4V
Vce 9.9V
11.80

Graph from

Tabulation:-

Amplitude	Time in sec	Frequency (Hz)

Result:-

The Hartley oscillator is designed and constructed for the given frequency:

Theoretical
Frequency:

Practical Frequency:

COLPITT OSCILLATOR! -Aim! -


To design and construct a Colpitt oscillator at the given operating frequency.

Theory is same as Hartley.

Apparatus required! -

S.No.	Apparatus	Range	Quantity
1.	Resistors	2k Ω	1
		1k Ω	1
		100k Ω	1
		22k Ω	1
2.	RPS	0-30V	1.
3.	Transistor	BC107	1.
4.	Capacitors	0.1 μ F	1
		0.01 μ F	1.
5.	Inductor	10mH	1.
6.	CRO	30MHz	1.
7.	Breadboard		1

Am. 11/11

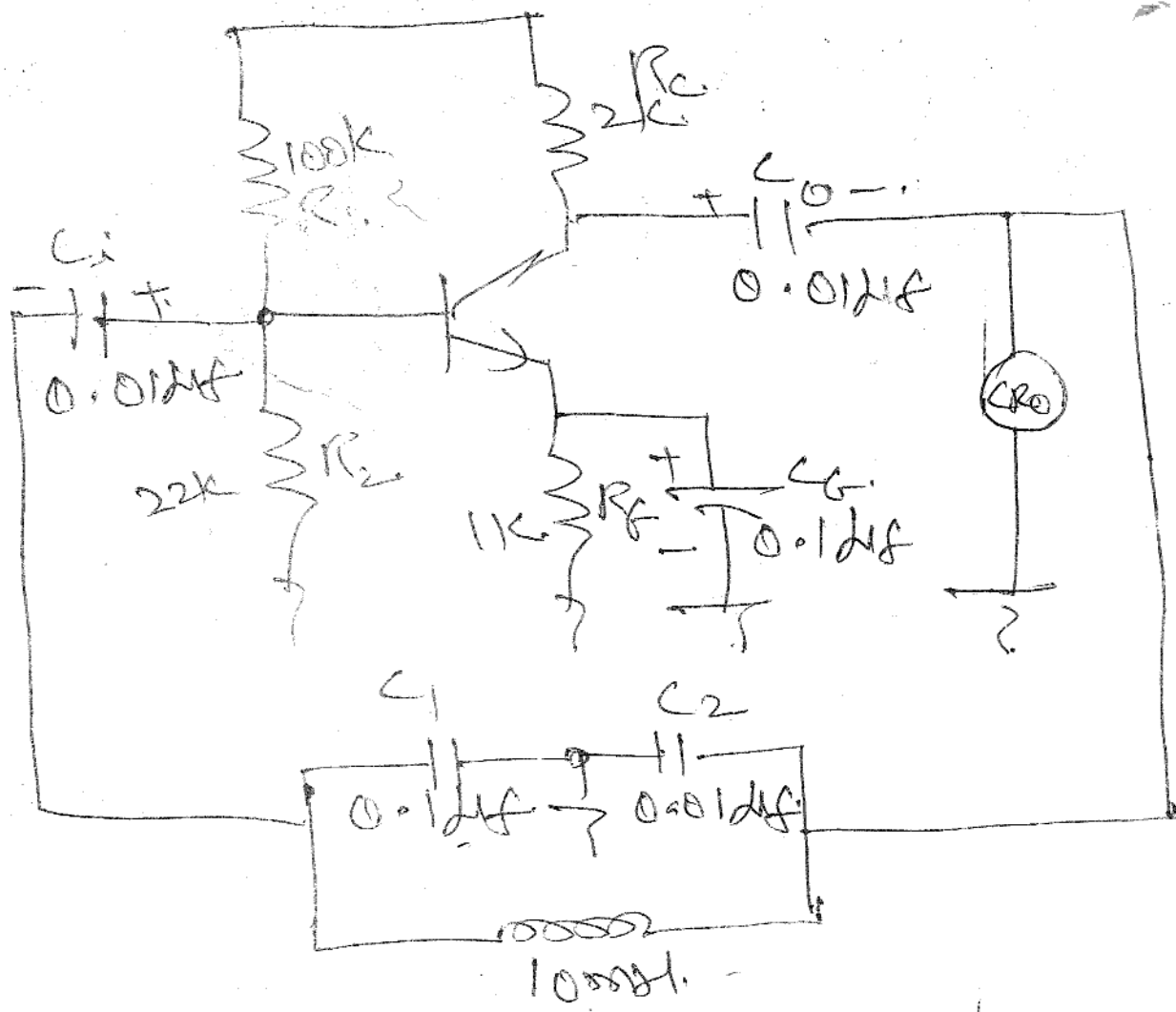

Model Graph

