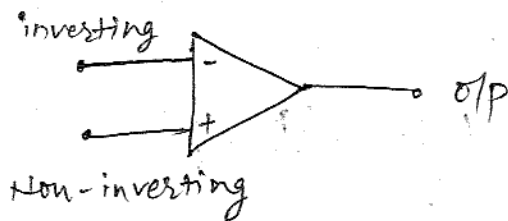


UNIT-1

Applications of op-amplifier

op-amp: symbol $\left\{ \begin{array}{l} \rightarrow \text{Linear} \\ \rightarrow \text{Non-linear} \end{array} \right.$




Offset voltage - External applying voltage.


Packages

1. Metal can
2. Dip (Dual ^{inline} in ~~package~~ package)
3. Flat

PIN diagram $+5V$ to $\pm 20V$.

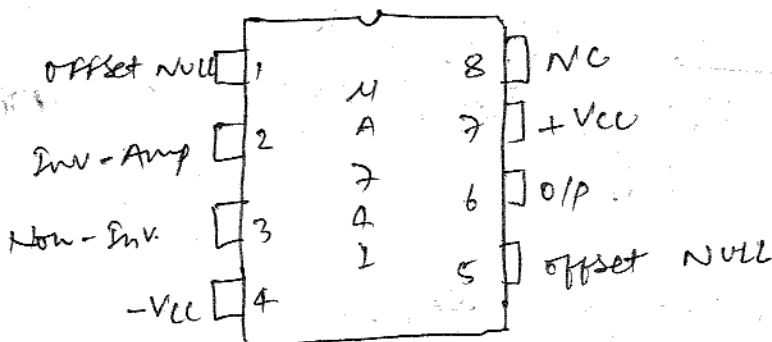


Characteristics:

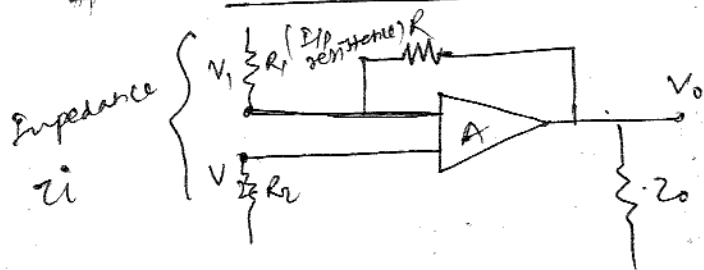

AOL (open loop gain)

Acl (closed loop gain)

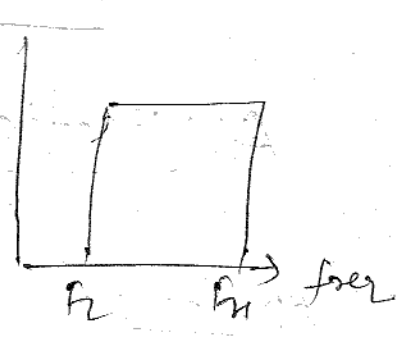


$B.W = f_H - f_L$

ii) Input offset voltage (V_{iOFF})

Linear - Inverting, Non-inverting, voltage follower, adder, subtractor, differentiator, integrator, instrumentation amplifier

Non-linear : eg. RPS

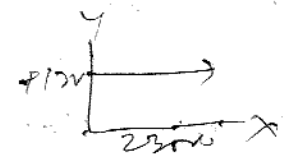


~~12V~~ $V_m = 230V$ but setting 12V

Precision Rectifier: log amplifier, audio-log amplifier, Comparator, Schmitt trigger, Schmitt trigger.

LM 745 - provides only +5V.

Inverting amplifier:

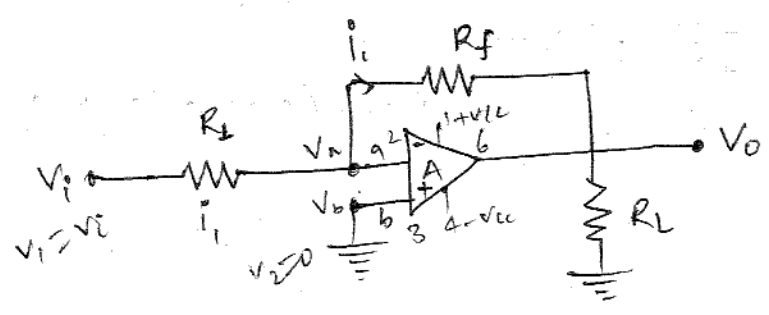

Ckt.

~~ACL~~ = ~~ACL~~ For ACL

Applying KCL,

$$i_1 = \frac{V_i}{R_1} \quad \text{--- (1)}$$

$$V_b = V_a = 0 \quad \text{--- (2)}$$

$$i_1 = \frac{V_a - V_o}{R_f} \quad \text{--- (3)}$$

From (1), (2) & (3)

$$\frac{V_i}{R_1} = \frac{-V_o}{R_f}$$

$$V_o = -\frac{V_i R_f}{R_1}$$

$$\frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

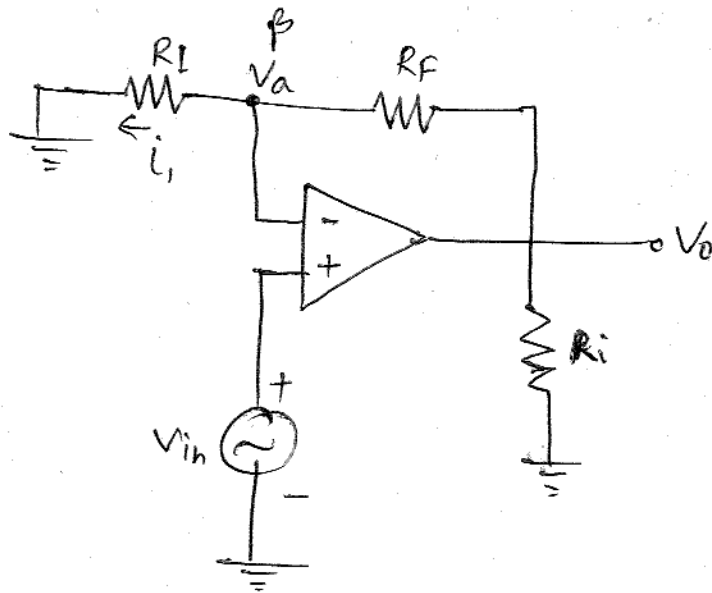
$$\frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

(Prob. 1) Design an amplifier circuit with the gain of -10 with the ~~ip~~ ~~res~~ resistance $R_1 = 10 \text{ k}\Omega$.

$$ACL = \frac{V_o}{V_i} = -10$$

$$R_f = -\frac{V_o}{V_i} \times R_1 = -\left(\frac{-10}{1}\right) \times 10 = 100 \text{ k}\Omega$$

24/06/11.

Non-Inverting AmplifierApplying KCL

$$\frac{V_i - V_a}{R_l} = \frac{V_o - V_i}{R_f}$$

$$\frac{V_i}{R_l} = \frac{V_o - V_i}{R_f} \quad [\because V_a = 0]$$

$$\frac{V_i}{R_l} + \frac{V_i}{R_f} = \frac{V_o}{R_f}$$

$$V_i \left(\frac{1}{R_l} + \frac{1}{R_f} \right) = \frac{V_o}{R_f}$$

$$\frac{V_o}{V_i} = R_f \left(\frac{1}{R_l} + \frac{1}{R_f} \right)$$


$$\frac{V_o}{V_i} = R_f \left(\frac{R_f + R_l}{R_l R_f} \right)$$

$$\frac{V_o}{V_i} = \frac{R_l + R_f}{R_l}$$

$$V_o = \left(\frac{R_l + R_f}{R_l} \right) V_i$$

$$\beta = \frac{R_l}{R_l + R_f}$$

Integrator

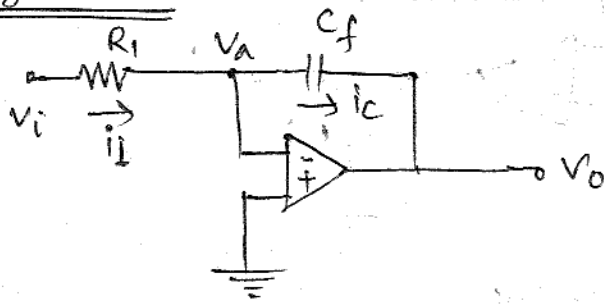

Applying KCL in the ckt:

$$\frac{V_i - V_a}{R_i} = \frac{C \frac{d(V_a - V_o)}{dt}}$$

$$\therefore \frac{V_i}{R_i} = -C \frac{dV_o}{dt} \quad \left[\because V_a = 0 \right]$$

Now, taking integration, on both sides

$$\int \frac{V_i}{R_i} dt = -C \int \frac{dV_o}{dt}$$

$$\int \frac{V_i}{R_i} dt = -CV_o$$


$$V_o = -\frac{1}{R_i C_f} \int V_i dt$$

Applications:

- 1] Analog to digital converter.
- 2] Analog computer.
- 3] RAM generator.
- 4] Frequency response of capacitor.

Q) Consider a practical integrated ckt for the component values $R_i = 10k\Omega$, $R_f = 100k\Omega$, $C_f = 10\mu F$. Determine the lower frequency limit of integration and the response of the ~~input~~ input.

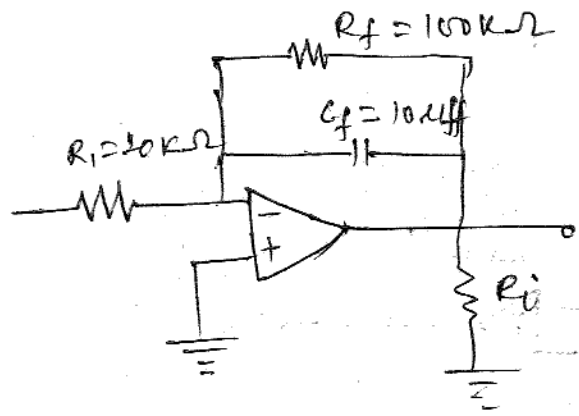- i) sine wave
- ii) step & D/P
- iii) square wave.




1] sine wave input

For the i/p of one voltage peak value,
the o/p is,


$$V_o = \frac{1}{R_i C_f} \int V_i(t) dt$$
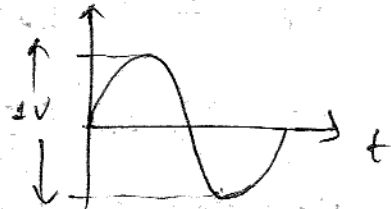
$$= \frac{1}{10 \times 10^3 \times 10 \times 10^{-6}}$$



25/06/11

Differentiator

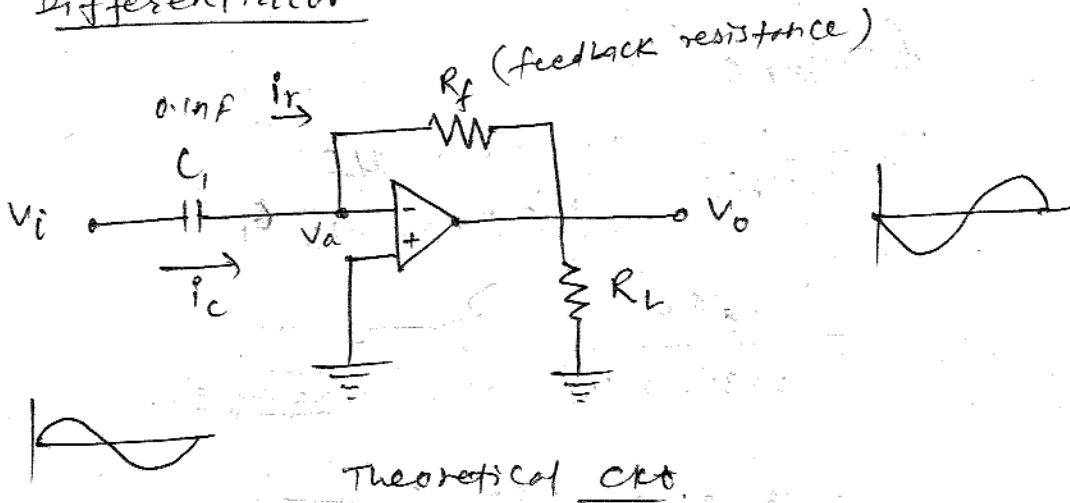

Applying KCL,

$$V = IR$$

$$i_c = i_r$$

$$C \frac{dv_i}{dt} = \frac{V_o - V_a}{R_f} \quad [\because V_a = 0]$$

$$C \frac{d(V_a - V_i)}{dt} = \frac{V_o}{R_f}$$

$$-C \frac{dV_i}{dt} = \frac{V_o}{R_f}$$

$$\therefore V_o = -R_f C \frac{dV_i}{dt}$$

Q: design an op-amp diff that will differentiate i/p signal with $f_{max} = 100 \text{ Hz}$.

i) draw the o/p waveform for a sine wave 2V peak at 100 Hz applied to the differentiator.

Soln:

we know,

$$f = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi f C} \quad \left[\because C = 0.1 \mu\text{F} \right]$$

$$\left[C = 0.1 \times 10^{-6} \text{ F} \right]$$

$$= \frac{10^6}{2 \times 3.14 \times 100 \times 0.1} = \frac{10^9}{628}$$

$$= 1592.35 \times 10^3$$

$$= 15.9 \times 10^3$$

$$\boxed{R = 15.9 \text{ K}\Omega}$$

again,

$$f = 10 \text{ kHz}$$

$$= 10 \times 1000 \text{ Hz}$$

$$f = 1 \text{ kHz}$$


$$f = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi R_1 C_1}$$

$$R_1 = \frac{10^6}{2\pi \times 1000 \times 0.1 \times 10^{-6}} = \frac{10^6}{628}$$

$$= 1592.35$$

$$= 1.59235 \times 10^3$$

$$\boxed{R_1 = 1.59 \text{ K}\Omega}$$

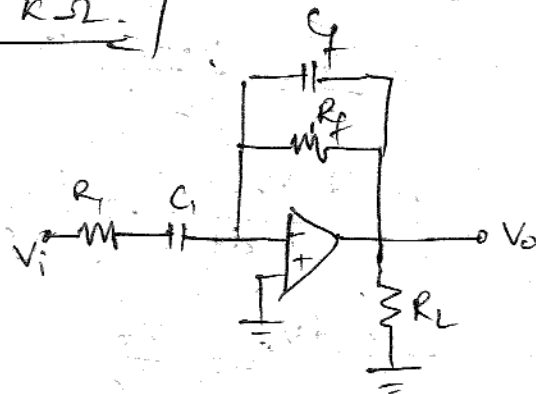

Practical ckt.


$$R_1 C_1 = R_f C_f$$

$$(1.5 \times 10^3)(0.1 \mu\text{F}) = (15.9 \times 10^3) C_f$$

$$C_f = 0.01 \mu\text{F}$$

$$V_o = -R_f C_f \frac{dV_i}{dt} \quad \text{--- (1)}$$
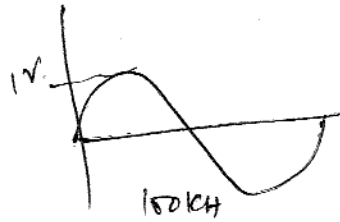
$$= -(15.9 \times 10^3)(0.1 \mu\text{F}) \frac{d \sin 200\pi t}{dt}$$



$$= -15.9 \times 10^3 \times 0.1 \times 10^{-6} \cos 200\pi t$$

$$1 \sin(2\pi \times 10^4) t$$

$$= -1.59 \times 10^{-3} \cos 200\pi t \times 200\pi$$

$$= -0.99852 \cos 200\pi t$$

$$= -0.999 \cos 2\pi \times 10^4 t$$

$$V_o = 1 \cos 2\pi \times 10^4 t$$