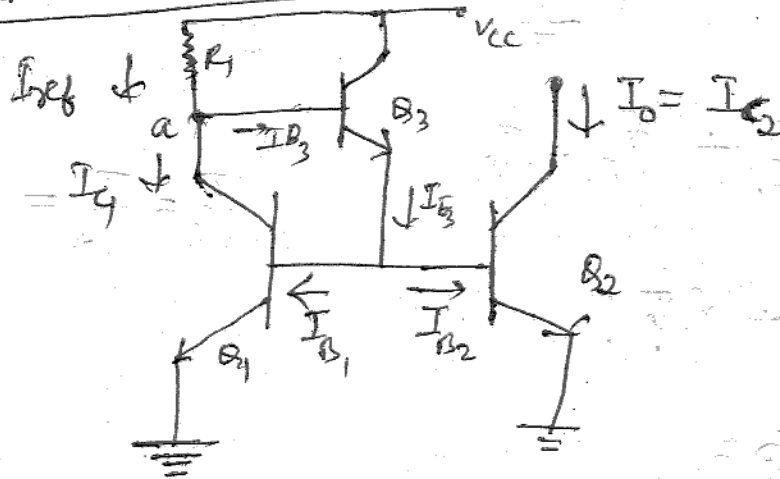


$$I_{ref} = I_C = \frac{V_{CC}}{R}$$

~~25/10/11~~

30/6/11 :-

CURRENT SOURCE WITH GAIN



To find I_o :

Apply KCL at node a

$$I_{ref} = I_q + I_{B3}$$

$$I_{ref} = I_q + \frac{I_{E3}}{\beta}$$

$$I_{B3} = \frac{I_{E3}}{1+\beta}$$

$$\beta = \frac{I_C}{I_B} \quad \text{--- (1)}$$

$$\alpha = \frac{I_C}{I_E} \quad \text{--- (2)}$$

from (1),

$$I_B = \frac{I_C}{\beta}$$

from

$$I_C = \alpha I_E$$

$$\therefore I_B = \frac{I_C}{\beta}$$

$$= \frac{\alpha I_E}{\beta}$$

$$\left[\because \alpha = \frac{\beta}{1+\beta} \right]$$

$$= \frac{\beta}{1+\beta} \left(\frac{I_E}{\beta} \right)$$

$$I_B = \frac{I_E}{1+\beta}$$

$$\Rightarrow I_{B3} = \frac{I_{E3}}{1+\beta}$$

$$I_{ref} = I_{C1} + I_{B3}$$

$$= I_{C1} + \frac{I_{E3}}{\beta}$$

$$= I_{C1} + \alpha \frac{I_E}{\beta}$$

$$I_{ref} = I_{C1} + \frac{\beta}{1+\beta} \cdot \frac{I_E}{\beta}$$

$$I_{ref} = I_{C1} + \frac{I_E}{1+\beta}$$

It consist of Transistor Q₁ & Q₂ with and identical bases connected, collector current are equal

$$I_{E3} = I_{B1} + I_{B2}$$

$$\therefore I_{B1} = I_{B2} = I_B$$

$$\Rightarrow I_{E3} = 2I_B$$

$$\therefore I_{ref} = I_{C1} + \frac{2I_B}{1+\beta}$$

$$\therefore I_B = \frac{I_C}{\beta}$$

$$I_{ref} = I_{C1} + \frac{2}{1+\beta} \cdot \frac{I_C}{\beta}$$

$$I_{C1} = I_{C2} = I_0$$

$$\frac{I_C}{\beta}$$


$$= I_0 \left[1 + \frac{2}{\beta(1+\beta)} \right]$$

$$I_{ref} = I_0 \left[1 + \frac{2}{\beta(1+\beta)} \right]$$

Conclusion :- O/P Current I_o is independent of β . If $\beta \ll 1$.

O/P Current is approximately equal to I_o
 $\Rightarrow I_o = I_{ref}$

WILSON CURRENT SOURCE :-

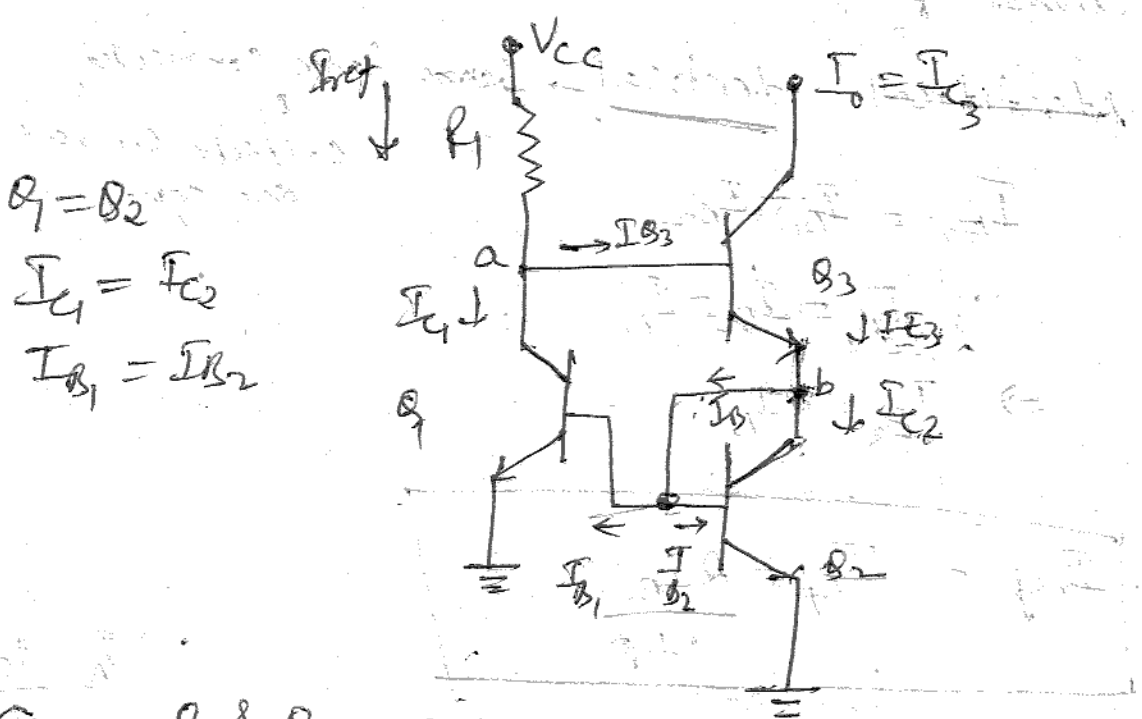

$Q_1 = Q_2$
 $I_{C1} = I_{C2}$
 $I_{B1} = I_{B2}$

Since Q_1 & Q_2 are identical.

Apply KCL at 'a'

$I_{ref} = I_{C1} + I_{B3}$

$I_{B3} = \frac{I_{C1}}{\beta}$

$$I_{ref} = I_{C1} + \frac{I_{C1}}{\beta}$$

$$I_{ref} = I_{C1} \left(1 + \frac{1}{\beta} \right)$$

$$I_{out} = \frac{I_1 + \alpha I_2}{\beta}$$

Apply KCL at node B,

$$I_{B1} = I_{B2} = I_B$$

$$I_{E3} = I_{C2} + I_{B1} + I_{B2}$$

$$= I_{C2} + 2I_B$$

$$= I_{C2} + \frac{2I_C}{\beta}$$

from B3

$$I_{E3} = I_{C3} + I_{B3}$$

$$= I_{C3} + \frac{I_{C3}}{\beta} = I_{C3} \left(1 + \frac{1}{\beta} \right)$$

$$\Rightarrow I_{C2} + \frac{2I_C}{\beta} = I_{C3} \left(1 + \frac{1}{\beta} \right)$$

$$\therefore I_{C3} = I_0$$

$$\Rightarrow I_{C2} + \frac{2I_C}{\beta} = I_0 \left(1 + \frac{1}{\beta} \right)$$

$$\Rightarrow I_C \left(1 + \frac{2}{\beta} \right) = I_0 \left(1 + \frac{1}{\beta} \right)$$

$$\Rightarrow I_C = \frac{I_0 \left(1 + \frac{1}{\beta} \right)}{1 + \frac{2}{\beta}}$$

$$I_C = \frac{I_0 \left(\frac{\beta+1}{\beta} \right)}{\frac{2+\beta}{\beta}}$$

$$I_C = I_0 \left(\frac{1+\beta}{2+\beta} \right)$$

$$I_C = \frac{V_{CC} - V_{BE}}{R}$$

$$I_C = I_E = I_B$$

$$I_C = I_E$$

$$I_C = I_E$$

$$I_C = I_E$$

$$I_C = I_E$$

$$I_C = I_E$$

$$I_C = I_E$$

$$(I_C) = I_E = I_B$$

$$(I_C) = I_E = I_B$$

$$I_C = I_E$$