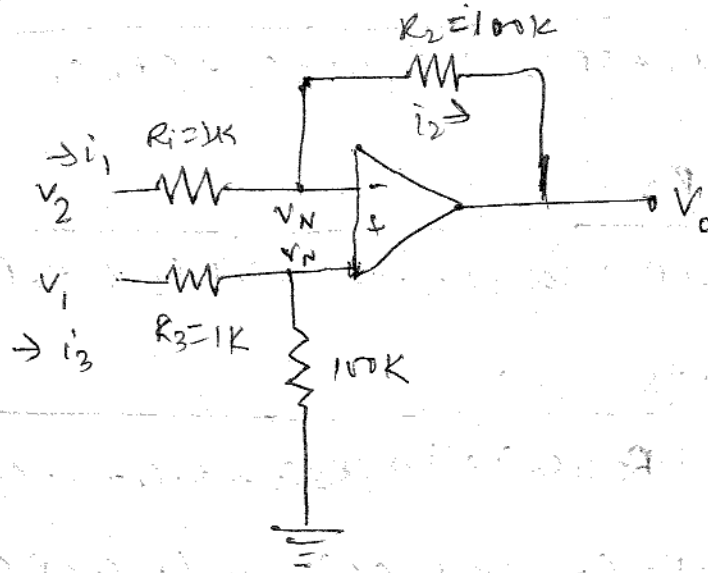


04/07/11. Basic differential amplifier



$$\frac{V_2 - V_N}{R_1} = -\frac{V_N - V_0}{R_2}$$

$$\frac{V_2}{R_1} - \frac{V_N}{R_1} = \frac{V_N}{R_2} - \frac{V_0}{R_2}$$

$$\frac{V_2}{R_1} - \frac{V_N}{R_1} - \frac{V_N}{R_2} = -\frac{V_0}{R_2}$$

$$\frac{V_2}{R_1} - V_N \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = -\frac{V_0}{R_2} \quad \text{--- (1)}$$

$$\frac{V_1 - V_N}{R_3} = \frac{V_N - 0}{R_4}$$


$$\frac{V_1}{R_3} - V_N \left( \frac{1}{R_3} + \frac{1}{R_4} \right) = 0 \quad \text{--- (2)}$$

$$\frac{V_2}{R_1} - V_N \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_1}{R_3} + V_N \left( \frac{1}{R_3} + \frac{1}{R_4} \right) = \frac{V_0}{R_2}$$


$$\frac{V_1}{R_3} - \frac{V_2}{R_1} = \frac{V_0}{R_2}$$

$$\Rightarrow \boxed{V_0 = R_2/R_1 (V_1 - V_2)}$$

# Instrumentation Amplifier

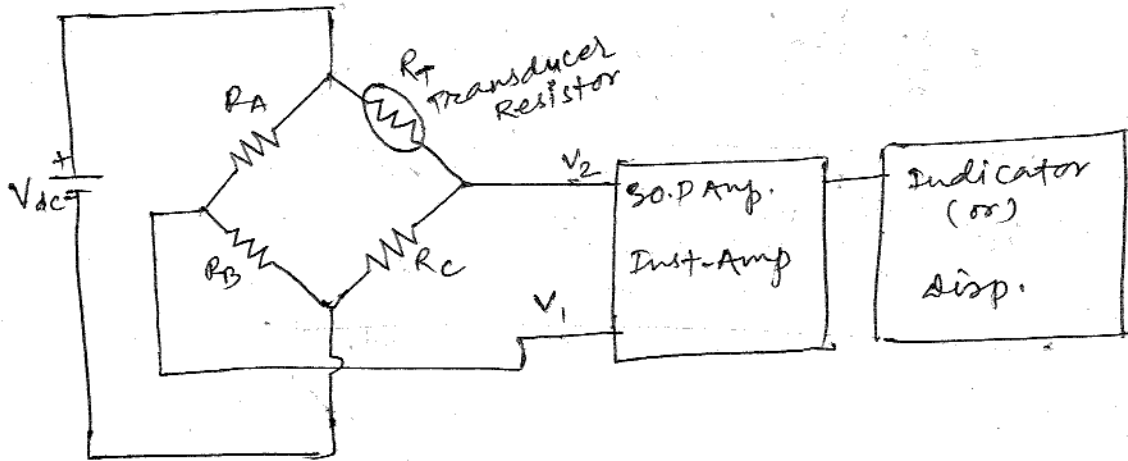

## Circuit Design:

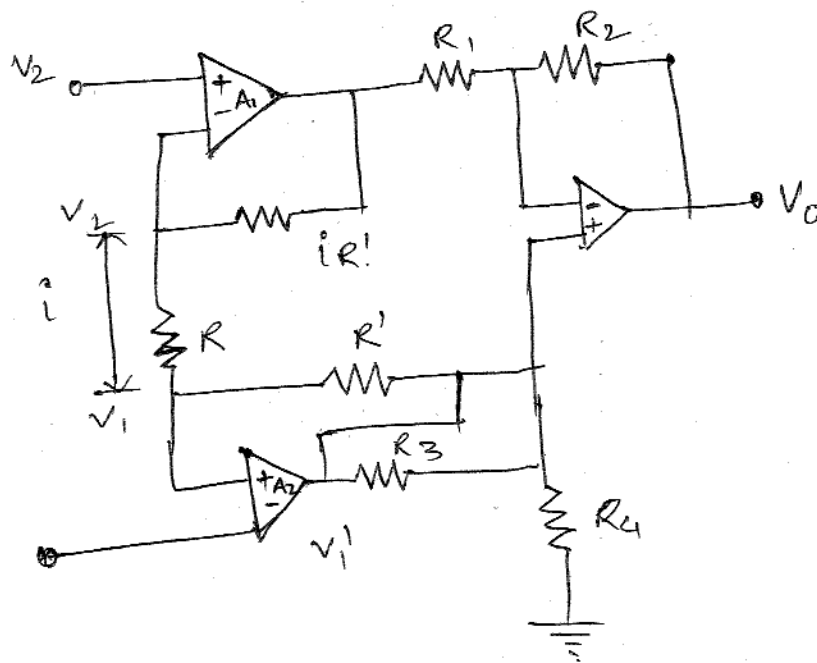

$$V_0 = R_2/R_1 (V_1 - V_2)$$

$$V_0 = R_2/R_1 (V_1' - V_2')$$

$$V_1' = DR' + V_1$$

$$V_2' = DR' + V_2$$

$$V_1' = \left( \frac{V_1 - V_2}{R} \right) R' + V_1$$

$$V_2' = - \left( \frac{V_1 - V_2}{R} \right) R' + V_2$$

$$V_0 = \frac{R_2}{R_1} \left[ \frac{V_1 - V_2}{R} \right] R' + (V_1 - V_2) + \left( \frac{V_1 - V_2}{R} \right) R'$$


$$= \frac{R_2}{R_1} \left[ \frac{2R'}{R} (V_1 - V_2) + (V_1 - V_2) \right]$$

$$V_0 = \frac{R_2}{R_1} \left[ \left( \frac{2R'}{R} + 1 \right) (V_1 - V_2) \right]$$

08/04/2011

## Filters

### 1. First order low pass filter

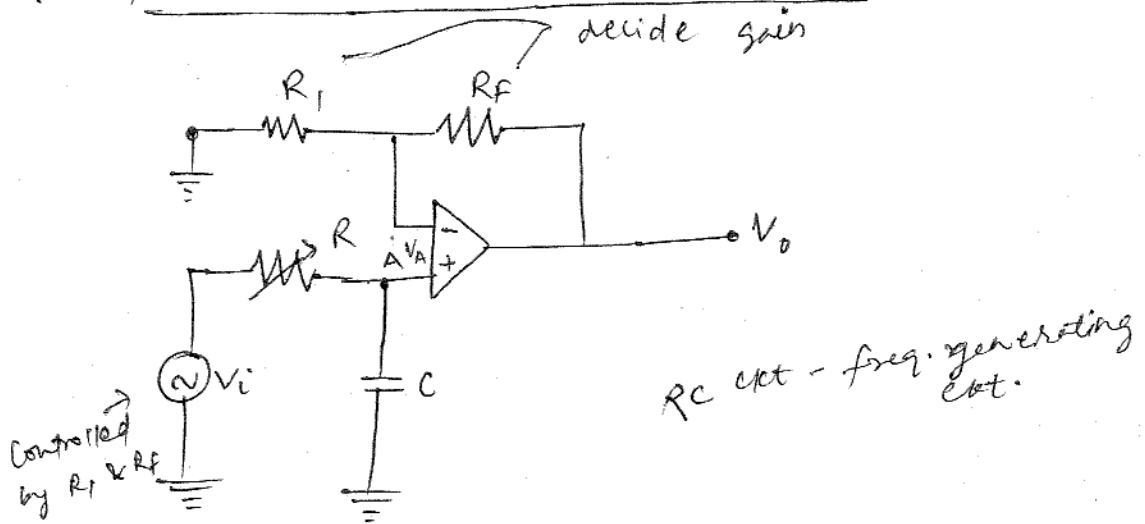

Total impedance of C,

$$X_c = -jX_c = \frac{1}{j2\pi f_c}$$

$$[-j = -j \times j / j = 1/j]$$

$$X_c = -jX_c = \frac{1}{2\pi f_c}$$

$$V_A = \frac{-jX_c}{R - jX_c} \cdot V_{in}$$

$$[X_c = 1/2\pi f_c]$$

$$V_A = \left[ \frac{-j/2\pi f_c}{R - j/2\pi f_c} \right] V_{in}$$

$$V_A = \left[ \frac{-j}{R2\pi f_c - j} \right] V_{in}$$

$$= \frac{V_{in}/j}{jR2\pi f_c + 1}$$

$$V_A = \frac{V_{in}}{1 + j2\pi R f_c}$$

$$V_A = \frac{V_{in}}{1 + j(f/f_c)}$$

$$f_c = \frac{1}{2\pi RC} \quad f_c = \frac{1}{2\pi RC} \rightarrow \text{cut-off frequency.}$$

$f \rightarrow$  operating frequency.

$$V_o = \left[ 1 + \frac{R_f}{R_i} \right] V_{in} = \left( 1 + \frac{R_f}{R_i} \right) \cdot \frac{V_{in}}{1 + j(f/f_c)}$$


$$\frac{V_o}{V_{in}} = 1 + \frac{R_f}{R_i}$$

$$\frac{V_o}{V_{in}} = \frac{A}{1 + j(f/f_c)}$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A}{\sqrt{1 + (f/f_c)^2}}$$

i)  $f < f_c$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_f}{\sqrt{1 + (0)}} = A_f$$

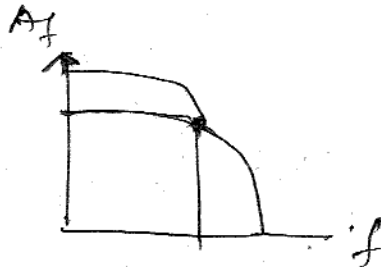

$$\left| \frac{V_o}{V_{in}} \right| = A_f$$

ii)  $f = f_c$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_f}{\sqrt{2}} = 0.707 A_f$$

$$\text{iii) } f > f_c$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_f}{1 + f/f_c} = \frac{A_f}{\infty} = 0$$

$$\therefore \boxed{\frac{V_o}{V_{in}} = 0}$$

Q1] Design a low pass filter at a cut-off frequency 15.9 kHz with a pass band gain 1.5 dB.

$$C = 0.001 \mu\text{F}$$

$$f_c = 15.9 \text{ kHz}$$

$$A_f = 1.5 \text{ dB}$$

$$f_c = \frac{1}{2\pi RC}$$

$$15.9 = \frac{1}{2\pi R \times 0.001}$$

$$R = \frac{1}{2\pi \times 0.001} = \frac{1}{0.0099} = 10 \text{ k}\Omega$$

$$\boxed{R = 10 \text{ k}\Omega}$$

$$A_f = 1 + \frac{R_f}{R_i}$$

$$1.5 = 1 + \frac{R_f}{10} = \frac{10 + R_f}{10}$$

$$15 - 10 = R_f$$

$$\therefore \boxed{R_f = 5 \text{ k}\Omega}$$

Hence  $\boxed{f_c = f}$  ( $\because$  for low pass filter).