

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

Assume

$$R_1 = R_2, \quad C_1 = C_2$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

$$\omega = \frac{1}{\sqrt{R^2 C^2}} = \frac{1}{RC}$$


$$2\pi f = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$

J.S.  
01/07/11

## FILTERS


Low pass filters :-

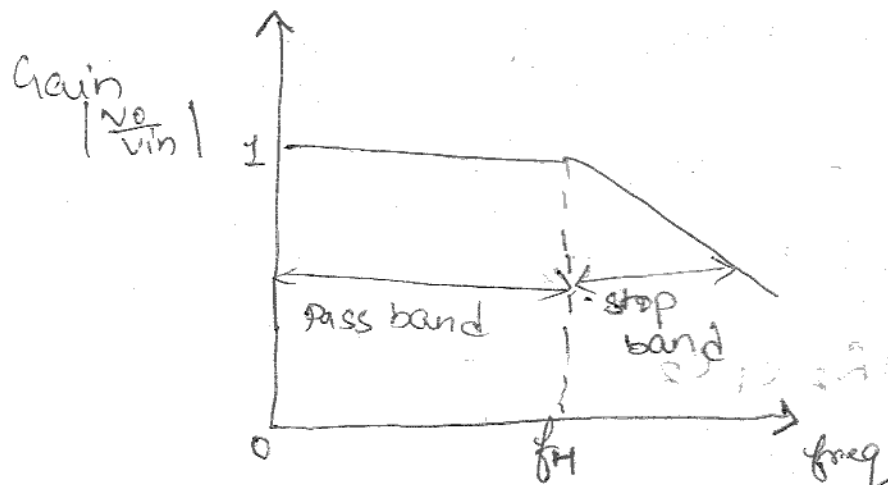

- First order Butterworth LPF.
- Second " " " " " "

First order LP Butterworth filter:-

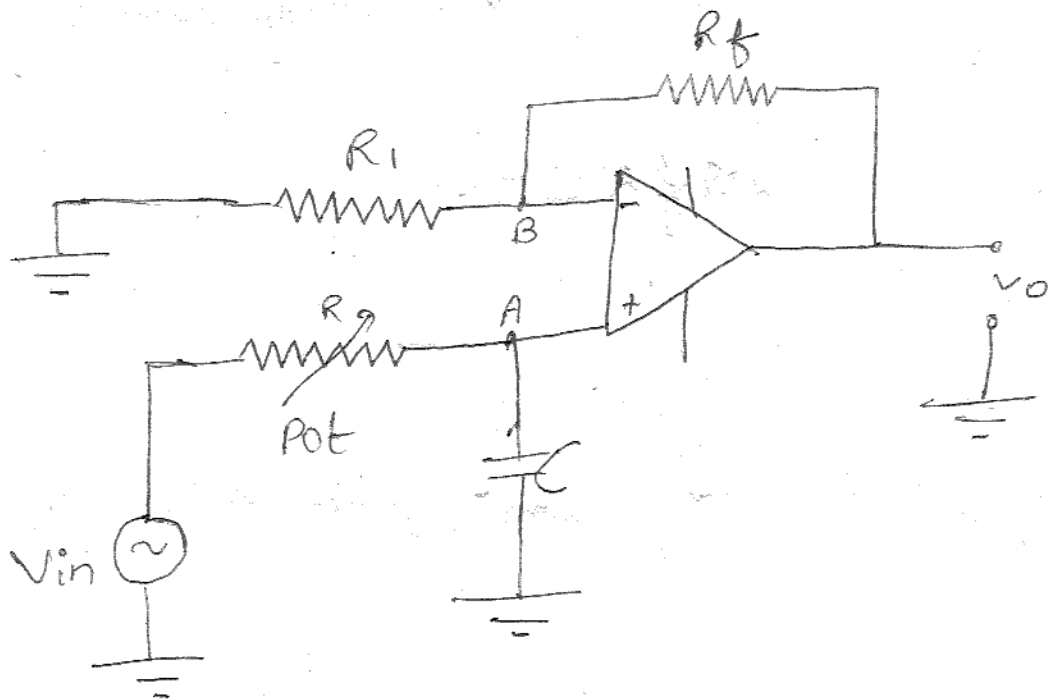It is realized by an AC circuit used with an op-amp in an non-inverting configuration. This is also called one pole LP Butterworth filter. The resistance  $R_f$  and  $R_i$  decides the gain of the filter in the Pass band.



Analysis

The impedance of the capacitor  $X_c$  is

$-jX_c$

where  $X_c = \frac{1}{2\pi f c}$

By using potential divider Rule, the voltage at the non-inverting input terminal A, across the capacitor C is given by

$$V_A = \frac{-jX_C \cdot V_{in}}{R - jX_C}$$

$$= \frac{-j}{2\pi f C} \cdot V_{in}$$

$$R - \frac{j}{2\pi f C}$$

$$= \frac{-j}{2\pi f R C - j} V_{in}$$

$$= \frac{V_{in}}{1 - \frac{2\pi f R C}{j}}$$

$$= \frac{V_{in}}{1 + j2\pi f R C}$$

But,  $-j = \frac{1}{j}$ ,  $\frac{1}{j} = j$

$$V_A = \frac{V_{in}}{1 + j2\pi f R C}$$

Since the op-amp is in the non-inverting configuration,

le,  
ng  
spectator

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_{in}$$

$$= \left(1 + \frac{R_f}{R_1}\right) \frac{V_{in}}{1 + 2\pi f RC}$$

$$\frac{V_o}{V_{in}} = \frac{\left(1 + \frac{R_f}{R_1}\right)}{1 + 2\pi f RC}$$

$$\frac{V_o}{V_{in}} = \frac{A_f}{1 + 2\pi f RC}$$

where  $A_f$  is the gain of the  
Passband frequency and  $f_H = \frac{1}{2\pi RC}$   
high cutoff frequency of the filter  
and  $f \rightarrow$  operating frequency.

$\frac{V_o}{V_{in}}$  is the transfer function of  
the filter and can be expressed  
in the polar form as  $\frac{V_o}{V_{in}}$


$$\frac{V_o}{V_{in}} = \left| \frac{V_o}{V_{in}} \right| \angle \phi$$

where


$$\frac{V_o}{V_{in}} = \frac{A_f}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

$$\text{and } \phi = -\tan^{-1}\left(\frac{f}{f_H}\right)$$

Second order Butterworth LPF :-

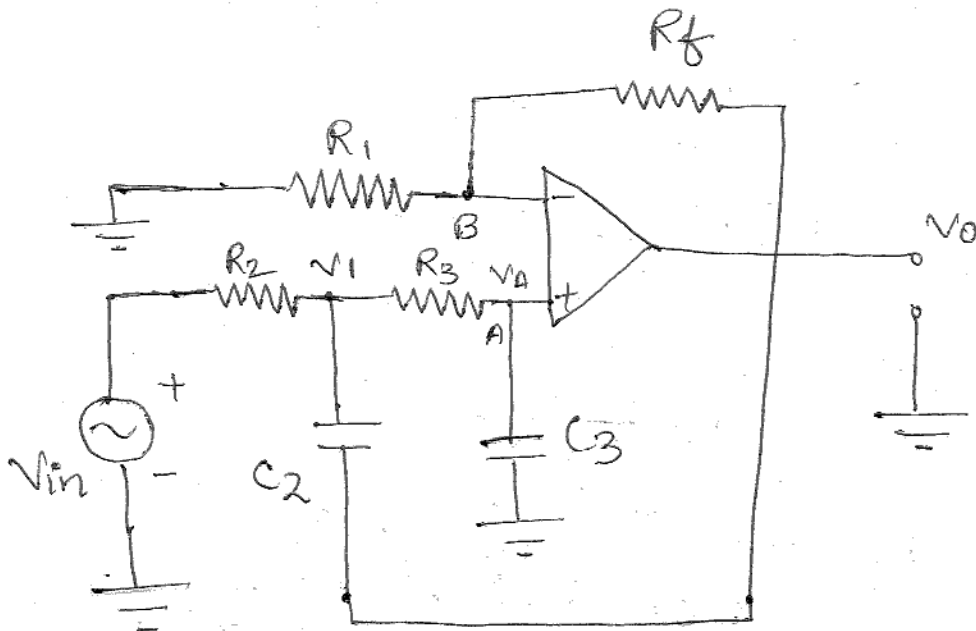

Analysis :-

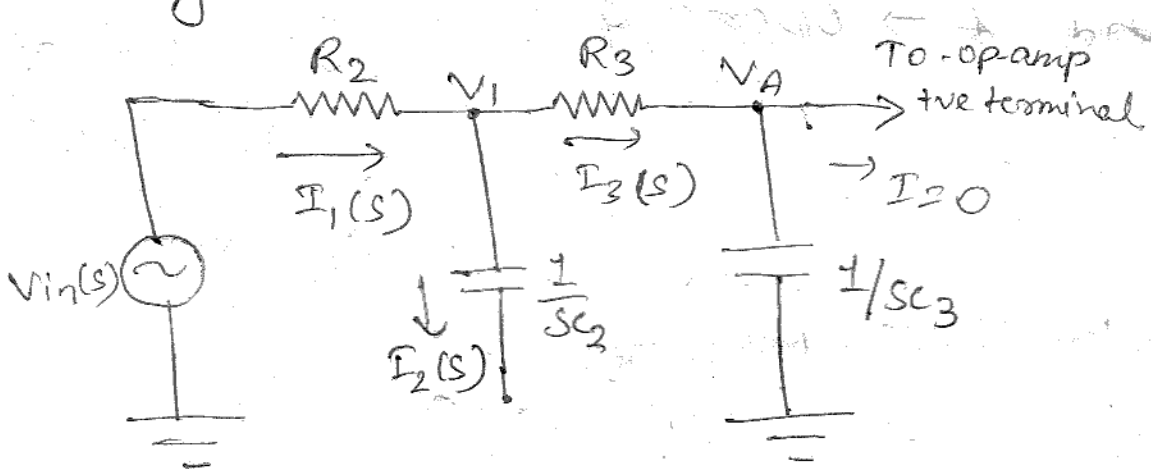

$$\text{At } \omega, \quad I_1 = I_2 + I_3 \quad \text{--- (1)}$$

$$\frac{V_{in} - V_1}{R_2} = \frac{V_1 - V_0}{1/sC_2} + \frac{V_1 - V_A}{R_3} \quad \text{--- (2)}$$

using potential divider rule,

$$V_A = V_1 \left[ \frac{1/sC_3}{R_3 + 1/sC_3} \right]$$

$$V_A = V_1 \left[ \frac{1/sC_3}{1 + sR_3C_3} \right]$$

$$V_1 = V_A (1 + sR_3C_3) \quad \text{--- (3)}$$

Sub  $V_1$  in (2)

$$\frac{V_{in} - V_A(1 + sR_3C_3)}{R_2} = \frac{V_A(1 + sR_3C_3) - V_O}{1/sC_2} + \frac{V_A(1 + sR_3C_3) - V_A}{R_3}$$

$$\Rightarrow \frac{V_{in}}{R_2} - \frac{V_A(1 + sR_3C_3)}{R_2} = \frac{V_A(1 + sR_3C_3)}{1/sC_2} - \frac{V_O}{1/sC_2} + \frac{V_A(1 + sR_3C_3)}{R_3} - \frac{V_A}{R_3}$$

$$\Rightarrow \frac{V_{in}}{R_2} + \frac{V_O}{1/sC_2} = \frac{V_A(1 + sR_3C_3)}{1/sC_2} + \frac{V_A(1 + sR_3C_3)}{R_3} + \frac{V_A(1 + sR_3C_3)}{R_2} - \frac{V_A}{R_3}$$

$$\Rightarrow \frac{V_{in}}{R_2} + V_O(sC_2) = V_A \left[ \frac{1 + sR_3C_3}{1/sC_2} + \frac{1 + sR_3C_3}{R_3} + \frac{1 + sR_3C_3}{R_2} - \frac{1}{R_3} \right]$$

$$= V_A \frac{R_3 (1 + sR_3 C_3) + sC_2 R_2 R_3 (1 + sR_3 C_3) + R_2 (1 + sR_3 C_3) - R_2}{R_2 R_3}$$

$$V_{in} R_3 + V_o (sC_2) R_2 R_3 = V_A [R_3 (1 + sR_3 C_3) + sC_2 R_2 R_3 (1 + sR_3 C_3) + R_2 (1 + sR_3 C_3) - R_2]$$

$$V_A = \frac{V_{in} R_3 + V_o (sC_2) R_2 R_3}{[R_3 (1 + sR_3 C_3) + sC_2 R_2 R_3 (1 + sR_3 C_3) + R_2 (1 + sR_3 C_3) - R_2]}$$

$$V_A = \frac{V_{in} R_3 + V_o (sC_2) R_2 R_3}{(1 + sR_3 C_3) [R_3 + sC_2 R_2 R_3 + R_2] - R_2}$$

For op-amp in the non-inverting configuration

$$A_F = 1 + \frac{R_f}{R_1}$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_A$$

$$V_o = A_F \frac{V_{in} R_3 + V_o sC_2 R_2 R_3}{(1 + sR_3 C_3) [R_3 + sC_2 R_2 R_3 + R_2] - R_2}$$

$$\frac{A_F R_3 V_{in}}{(1 + S R_3 C_3) [R_3 + S C_2 R_2 R_3 + R_2] - R_2} = V_0 \left[ \frac{1 - A_F S R_2 C_2 R_3}{(1 + S R_3 C_3) [R_3 + S C_2 R_2 R_3 + R_2] - R_2} \right]$$

$$A_F R_3 V_{in} = V_0 \left[ (1 + S R_3 C_3) (R_3 + S C_2 R_2 R_3 + R_2) - R_2 - A_F S R_2 C_2 R_3 \right]$$

$$\frac{V_0}{V_{in}} = \frac{A_F R_3}{\left[ (1 + S R_3 C_3) (R_3 + S C_2 R_2 R_3 + R_2) - R_2 - A_F S R_2 C_2 R_3 \right]}$$

$$= \frac{A_F R_3}{R_3 + S C_2 R_2 R_3 + R_2 + S R_3^2 C_3 + S^2 R_3^2 C_2 R_2 C_3 + S R_3 C_3 R_2 - R_2 - A_F S R_2 C_2 R_3}$$

$$= \frac{A_F R_3}{R_3 + S C_2 R_2 R_3 + R_2 + S R_3^2 C_3 + S^2 R_3^2 C_2 R_2 C_3 + S R_3 C_3 R_2 - R_2 - A_F S R_2 C_2 R_3}$$

$$= \frac{A_F R_3}{1 + S C_2 R_2 + \frac{R_2}{R_3} + S R_3^2 C_3 + S^2 R_3^2 C_2 R_2 C_3 + S C_3 R_2 - \frac{R_2}{R_3} - A_F S R_2 C_2}$$

$$= \frac{A_F R_3}{1 + S C_2 R_2 + \frac{R_2}{R_3} + S R_3^2 C_3 + S^2 R_3^2 C_2 R_2 C_3 + S C_3 R_2 - \frac{R_2}{R_3} - A_F S R_2 C_2}$$

$$= \frac{A_F R_3}{1 + R_2 C_2 S + R_3 C_3 S + S^2 R_2 R_3 C_2 C_3 + S C_3 R_2 - A_F S R_2 C_2}$$

$$= \frac{A_F R_3}{1 + R_2 C_2 S + R_3 C_3 S + S^2 R_2 R_3 C_2 C_3 + S C_3 R_2 - A_F S R_2 C_2}$$

$$\frac{V_0}{V_{in}} = \frac{A_F R_3}{S^2 R_2 R_3 C_2 C_3 + S (R_2 C_2 + R_3 C_3 + C_3 R_2 - A_F R_2 C_2) + 1}$$

$$\frac{V_0}{V_{in}} = \frac{A_F R_3}{S^2 R_2 R_3 C_2 C_3 + S (R_2 C_2 + R_3 C_3 + C_3 R_2 - A_F R_2 C_2) + 1}$$



$$\frac{V_o}{V_{in}} = \frac{A F}{s^2 + \frac{s(R_2 C_2 + R_3 C_3 + R_2 C_3 - A F R_2 C_2)}{R_2 C_2 R_3 C_3} + \frac{1}{R_2 C_2 R_3 C_3}} \quad (4)$$

∴ the gain of the filter has an order of 2. It is said to be second order filter.

Then, the transfer function of the II order system is

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A}{s^2 + 2\zeta \omega_n s + \omega_n^2} \quad (5)$$

Comparing eqn<sup>n</sup> (4) & (5)

$$\omega_n^2 = \frac{1}{R_2 R_3 C_2 C_3}$$

In the case of filters, this equation is based upon the cutoff frequency.

$$\omega_n = \frac{1}{\sqrt{R_2 R_3 C_2 C_3}}$$

Since we are finding the higher cutoff frequency

$$\omega_H = \frac{1}{\sqrt{R_2 R_3 C_2 C_3}}$$

(4)

$$2\pi f_H = \frac{1}{\sqrt{R_2 R_3 C_2 C_3}}$$

$$f_H = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$

$$\frac{1}{R_2 C_2 R_3 C_3}$$

an second

In the polar form

order

$$\left| \frac{V_O}{V_{in}} \right| < \phi$$

(5)

where,

$$\left| \frac{V_O}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + \left(\frac{f}{f_H}\right)^4}}$$

where  $A_F$  is gain of the filter in Pass band.

$f$  is input frequency and  $f_H$  is high cutoff frequency.

equation  
ency.


### Band pass filters :-

A combination of high pass & low pass filter is called Band pass filter.

A Band pass filter is basically a frequency selector, it allows a particular band of frequency to pass by thus the passband is between the two frequencies  $f_1$  and  $f_2$ .

mes

where  $f_H > f_L$

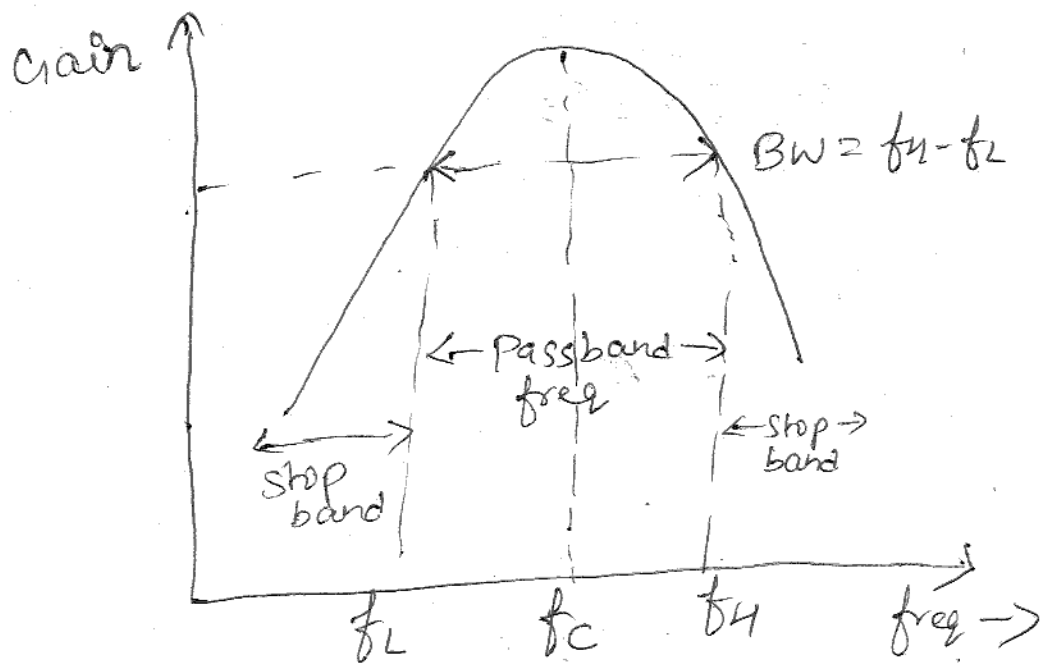


There are two types of band pass filters classified based on the figure of merits (or) quality factor ( $Q$ ) =  $\frac{f_0}{BW}$


→ Wide BPF  $\Rightarrow Q < 10$

→ Narrow BPF  $\Rightarrow Q > 10$

8/7/11

Narrow Band pass filter :-

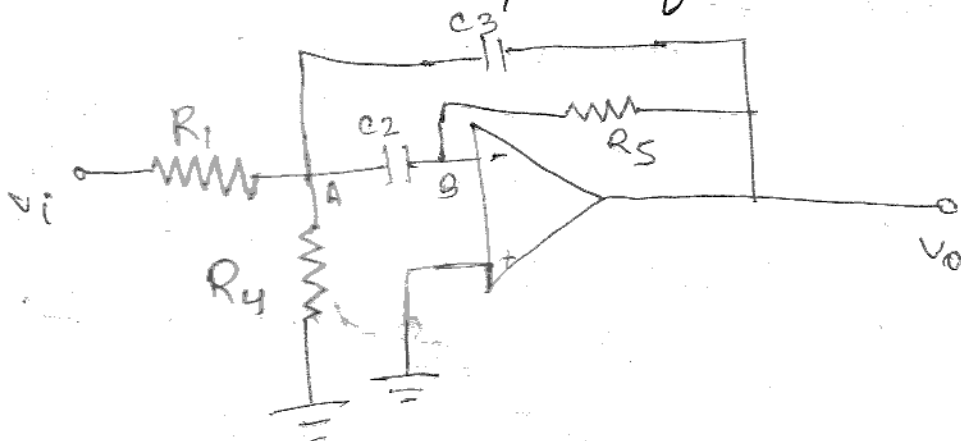

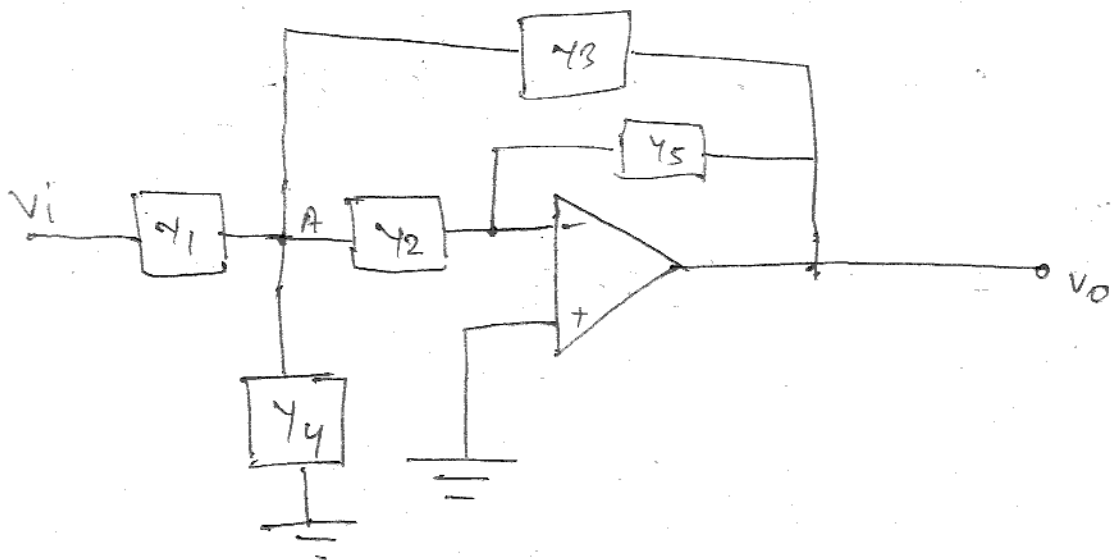

At node 'A'

$$V_i Y_1 + V_o Y_3 = V_A (Y_1 + Y_2 + Y_3 + Y_4) \quad \text{--- (1)}$$

At node 'B'

Assume,  $V_B = 0$

$$V_A Y_2 + V_o Y_5 = 0$$

$$V_A = \frac{-V_o Y_5}{Y_2} \quad \text{--- (2)}$$

Sub eqn (2) in (1)

$$V_i Y_1 + V_o Y_3 = \frac{-V_o Y_5}{Y_2} (Y_1 + Y_2 + Y_3 + Y_4)$$

$$V_i Y_1 = \frac{-V_o Y_5 (Y_1 + Y_2 + Y_3 + Y_4) - V_o Y_3}{Y_2}$$

$$V_i Y_1 = -V_o \left[ \frac{Y_5 Y_1 + Y_5 Y_2 + Y_5 Y_3 + Y_5 Y_4 + Y_2 Y_3}{Y_2} \right]$$

filters  
resists.

$$\frac{V_o}{V_i} = \frac{-Y_1 Y_2}{[Y_5 Y_1 + Y_5 Y_2 + Y_5 Y_3 + Y_5 Y_4 + Y_2 Y_3]} \quad \text{--- (3)}$$

Assume

$$Y_1 = G_1, \quad Y_2 = sC_2, \quad Y_3 = sC_3,$$

$$Y_4 = G_4, \quad Y_5 = G_5.$$

Sub the values in eqn (3)  
Hence the transfer function is given by

$$\frac{V_o(s)}{V_i(s)} = - \frac{G_1 s C_2}{[G_5 G_1 + G_5 s C_2 + G_5 s C_3 + G_5 G_4 + s^2 C_2 C_3]}$$

$$= - \frac{s C_1 C_2}{G_5 C_1 + G_5 s C_2 + G_5 s C_3 + G_5 G_4 + s^2 C_2 C_3}$$

$$= \frac{- s C_1 C_2}{s^2 C_2 C_3 + s(C_2 + C_3) G_5 + G_5(G_1 + G_4)} \quad \text{--- (4)}$$

Dividing num & deno by  $sC_2$


$$\frac{V_o(s)}{V_i(s)} = \frac{- C_1}{s C_3 + \frac{(C_2 + C_3) G_5}{s C_2} + \frac{G_5(G_1 + G_4)}{s C_2}}$$

--- (5)

③ The transfer function is equivalent to the gain of the given RLC circuit with the band pass filter.

Gain Exp of this ckt is,
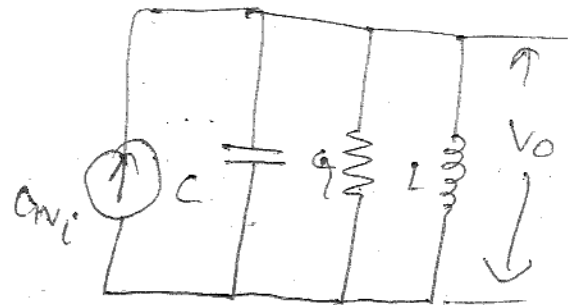
$$\frac{V_o(s)}{V_i(s)} = -\frac{G'}{Y}$$



$$= \frac{-G'}{sC + G + \frac{1}{sL}} \quad \text{--- ⑥}$$

By comparing ⑤ & ⑥

$$G' = G_1, \quad C = C_3, \quad G = \frac{G_5(C_2 + C_3)}{C_2},$$

$$L = \frac{C_2}{G_5(G_1 + G_4)}$$

At the resonant condition the circuit has a unity power factor

i.e. the imaginary part equal to zero.

Thus the resonant frequency  $\omega_0$  is given by

$$\omega_0^2 = \frac{1}{LC}$$

⑤

$$Z = \frac{1}{\frac{C_2 \cdot C_3}{G_5 (G_1 + G_4)}}$$

$$\omega_0^2 = \frac{G_5 (G_1 + G_4)}{C_2 C_3}$$

The gain at the resonance is

$$\frac{V_o}{V_i} = -\frac{G_1'}{G_1} = -\frac{G_1}{G_5 (G_2 + G_3)} \quad \text{--- (7)}$$

$$= -\frac{G_1 C_2}{G_5 (C_2 + C_3)}$$

$$= -\frac{\cancel{R_5}}{R_5}$$

$$= -\frac{R_5 C_2}{R_1 (C_2 + C_3)} \quad \text{--- (8)}$$

Quality factor :-

$$Q = \frac{\omega_0 L}{R} = \omega_0 R C = \frac{\omega_0 C}{G}$$

$$Q = \frac{\omega_0 C_3 C_2}{G_5 (C_2 + C_3)} \quad \text{--- (9)}$$

$$BW = \frac{1}{\phi} = \frac{\omega_0}{2\pi Q_0}$$

$$= \frac{G_5 (G_1 + G_4)}{C_2 C_3} \cdot \frac{\omega_0 / C_3 C_2}{G_5 (C_2 + C_3)}$$

$$= \frac{\cancel{\omega_0} G_5 (C_2 + C_3)}{2\pi \cancel{\omega_0} C_3 C_2}$$

$$BW = \frac{G_5 (C_2 + C_3)}{2\pi C_3 C_2}$$

Assume  $C_2 = C_3 = C$

$$BW = \frac{G_5 \times C}{2\pi \times C^2} = \frac{G_5}{\pi C}$$

$$= \frac{\frac{1}{R_5}}{\pi C} = \frac{1}{\pi R_5 C}$$

$$BW = \frac{1}{\pi R_5 C}$$