


12/7/11

## COMPARATOR

A comparator is a circuit which compares a signal voltage applied at one input of the op-amp with a known voltage at the other input and produce either a higher or low voltage in the output depending on which I/P is high.

### Types of comparators

1. Non-Inverting Comparator :-

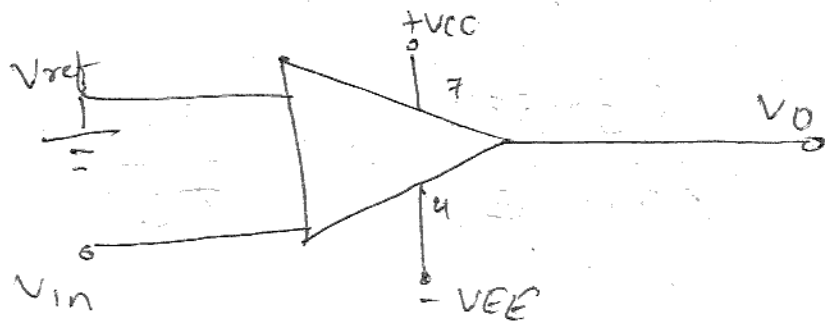


$$V_{in} > V_{ref} \Rightarrow O/P + V_{sat} = +V_{CC}$$

$$V_{in} < V_{ref} \Rightarrow O/P - V_{sat} = -V_{EE}$$

Thus the two possible output levels of the comparator are  $+V_{sat}$  or  $-V_{sat}$  indicating whether the I/P voltage is greater than or less than the ref. voltage. Such type of comparator in which operation is at

Saturation level is called saturating level of comparator.


Output waveform

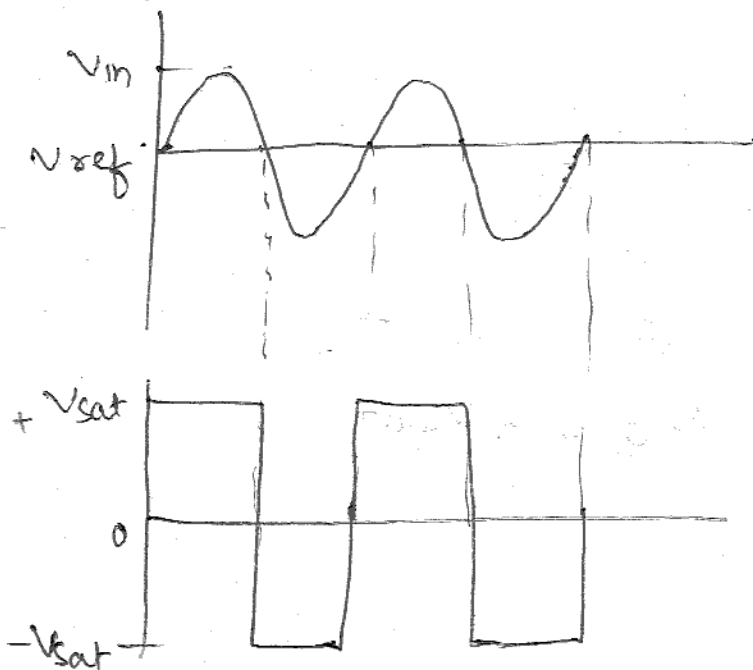

The op-amp differential voltage gain  $A_{OL}$  is very large.  $\pm V_{sat}$  i.e. the saturation voltage levels of op-amp are mentioned and hence ~~by~~  $V_{sat}$  by knowing  $V_{sat}$  and differential voltage gain we can determine the minimum input voltage level required to saturate is


$$V_{in}(\min) = \frac{V_{sat}}{A_{OL}}$$

## 2. Inverting Comparator

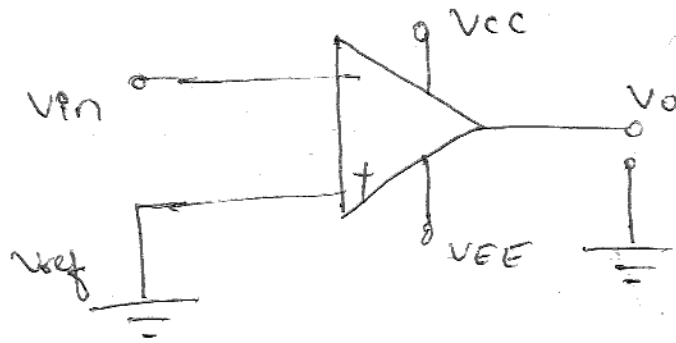

$$V_{in} < V_{ref} \Rightarrow V_o = +V_{sat}$$
$$V_{in} > V_{ref} \Rightarrow V_o = -V_{sat}$$

O/P waveform

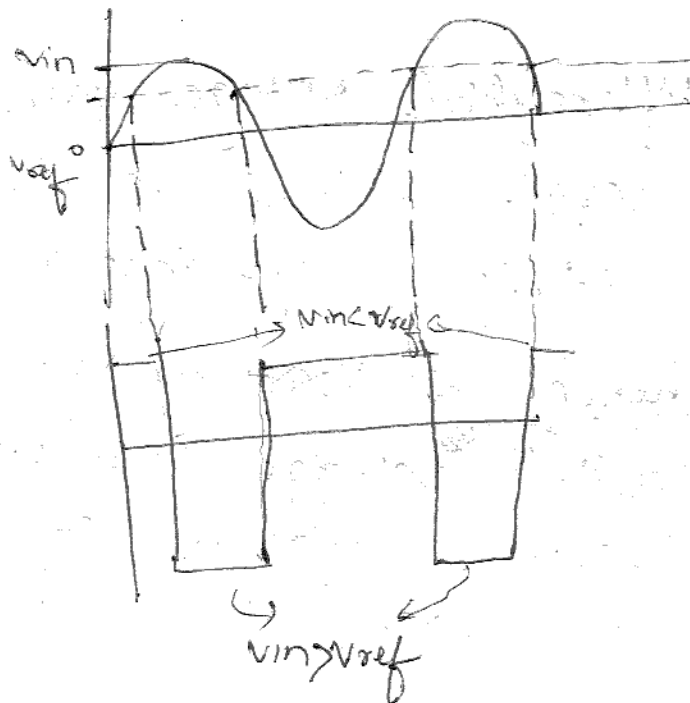


So when  $V_{in} < V_{ref}$ , the O/P voltage  $V_o$  is at  $+V_{sat}$  because the voltage at the inverting O/P is less than at the non-inverting O/P and when  $V_{in} > V_{ref}$ , the O/P

non investing i/p becomes -ve with respect to the investing i/p and so  $V_o$  goes to  $-V_{sat}$ .

## Applications of Comparators

1. Zero crossing detector,
2. Time Marker generator,
3. Phase detector.
4. Window detector.
5. Pulse generator.
6. Level detector.
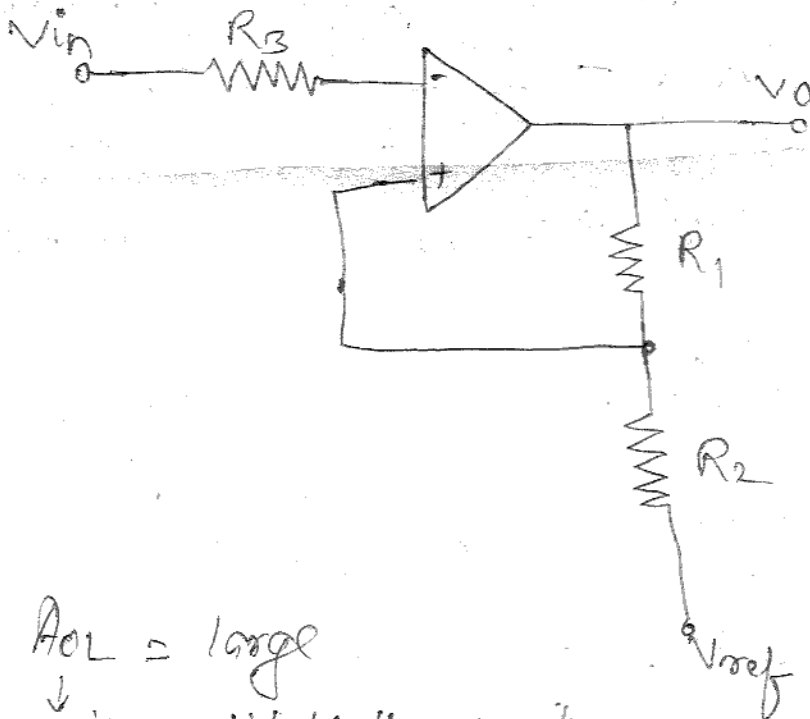
## Schmitt Trigger (Regenerative comparator)



$A_{OL} = \text{large}$

↓  
noise → disturbs the circuit

to remove noise we provide positive feedback.

-  $\beta A_{OL} = 1$  which gives  $A_{VF} > 1$   
 For as  $A_{OL}$  can't be maintained at constant value, so

$$A_{VF} > 1$$

This gives rise to a phenomenon called "hysteresis".

$$\text{Hysteresis width} = V_{UT} - V_{LT}$$

$V_{UT} \rightarrow$  upper threshold voltage"  
 $V_{LT} \rightarrow$  lower " " "

$$V_H = V_{UT} - V_{LT}$$


$$V_{UT} = V_{ref} + \frac{R_2}{R_1 + R_2} (V_{sat} - V_{ref})$$

As long as  $V_i < V_{UT}$ , the  $V_o$  remains at  $+V_{sat}$

$$V_{LT} = V_{ref} - \frac{R_2}{R_1 + R_2} (V_{sat} + V_{ref})$$

When  $V_i > V_{UT}$ , the  $V_o$  switches to  $-V_{sat}$

O/P waveform

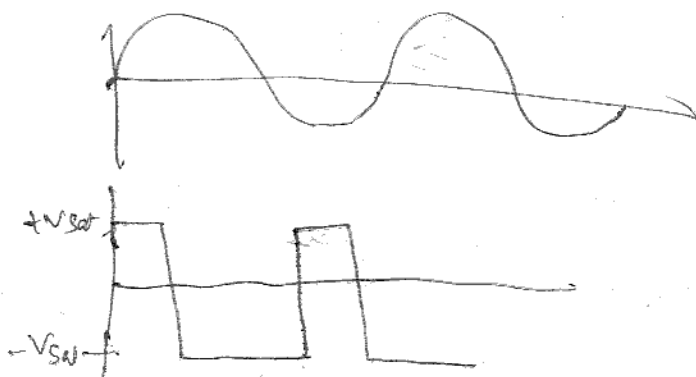

Hysteresis width ~~width~~  $V_H = V_{UT} - V_{LT}$

$$= \cancel{V_{ref}} + \frac{R_2}{R_1 + R_2} (V_{sat} - V_{ref}) -$$

$$\cancel{V_{ref}} + \frac{R_2}{R_1 + R_2} (V_{sat} + V_{ref})$$

$$= \frac{R_2}{R_1 + R_2} [V_{sat} - \cancel{V_{ref}} + V_{sat} + \cancel{V_{ref}}]$$

$$V_H = \frac{2R_2}{R_1 + R_2} \cdot V_{sat}$$

If PK-PK input signal  $V_i$  is smaller than  $V_H$ , then the Schmitt trigger circuit having a threshold voltage could never reset itself.


If  $V_{ref}$  is chosen at 0V then

$$V_{UT} = - - V_{LT} = + \frac{R_2}{R_1 + R_2} \cdot V_{sat}$$

# PRECISION RECTIFIERS :-

- Half wave Rectifier
- Full wave Rectifier

## Half wave Rectifier

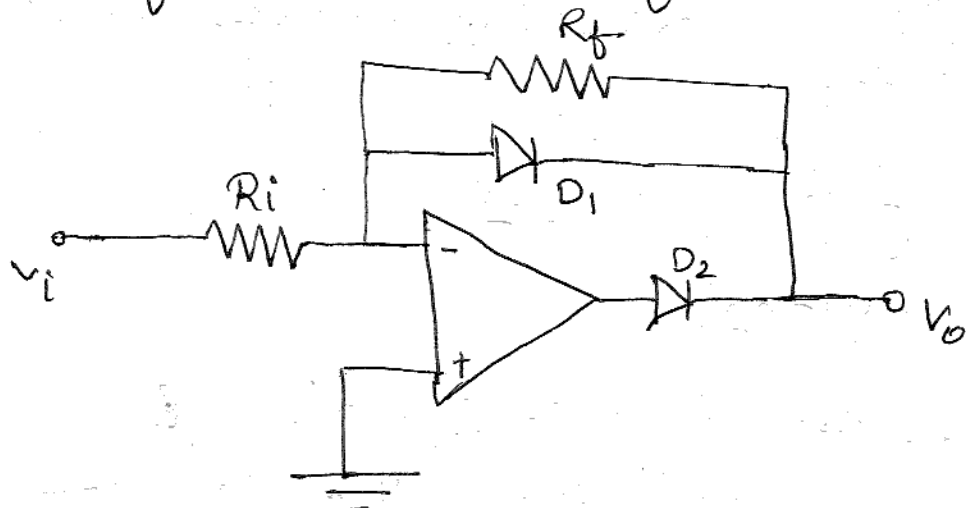

Case 1 :-

→  $V_i$  is positive i.e.  $V_i > 0$

$D_1$  - ON → conducts

$D_2$  - OFF → Reverse bias

$V_o$  → zero


Case 2 :-

→  $V_i$  is -ve i.e.  $V_i < 0$


$D_1$  - OFF

$D_2$  - ON

Case 2:

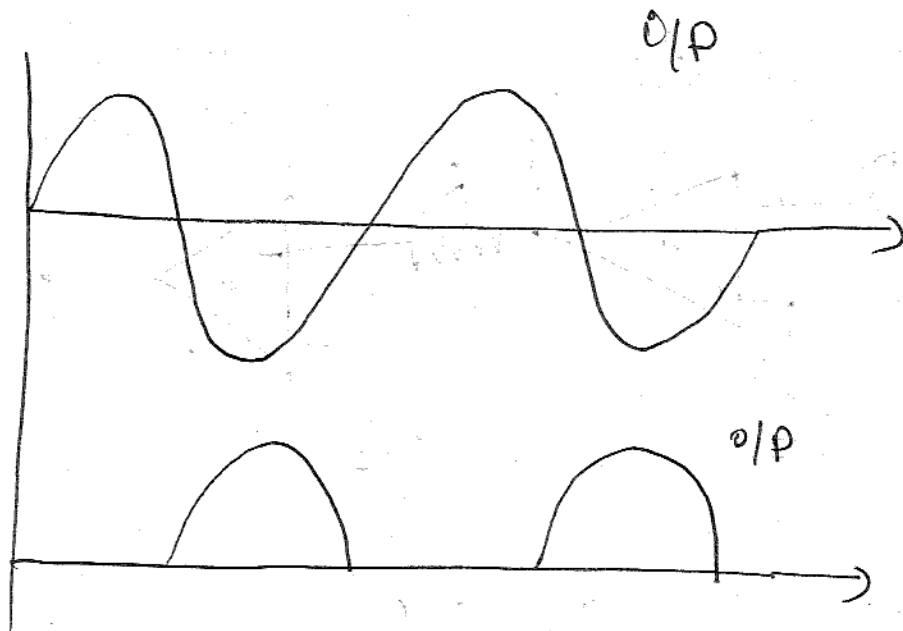

## FULL WAVE RECTIFIER

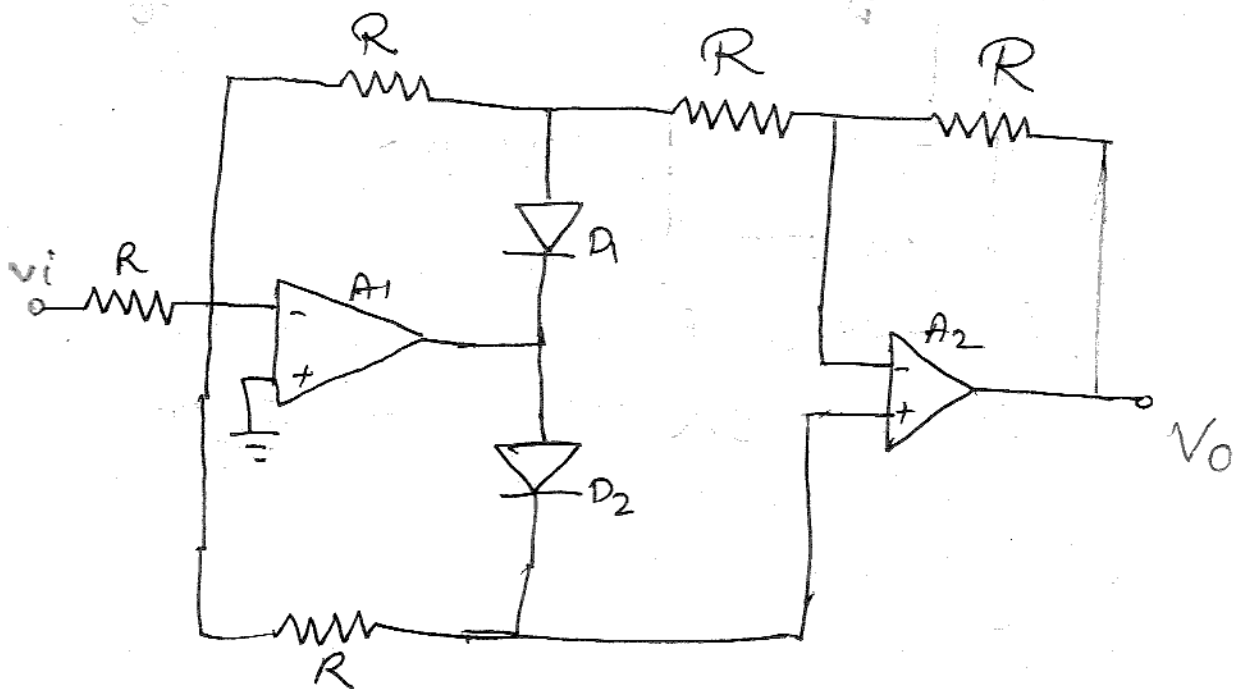


Case 1:

$$V_i > 0$$


$D_1$  - ON,  $D_2$  - OFF

$A_1$  &  $A_2$  acts as inverters.



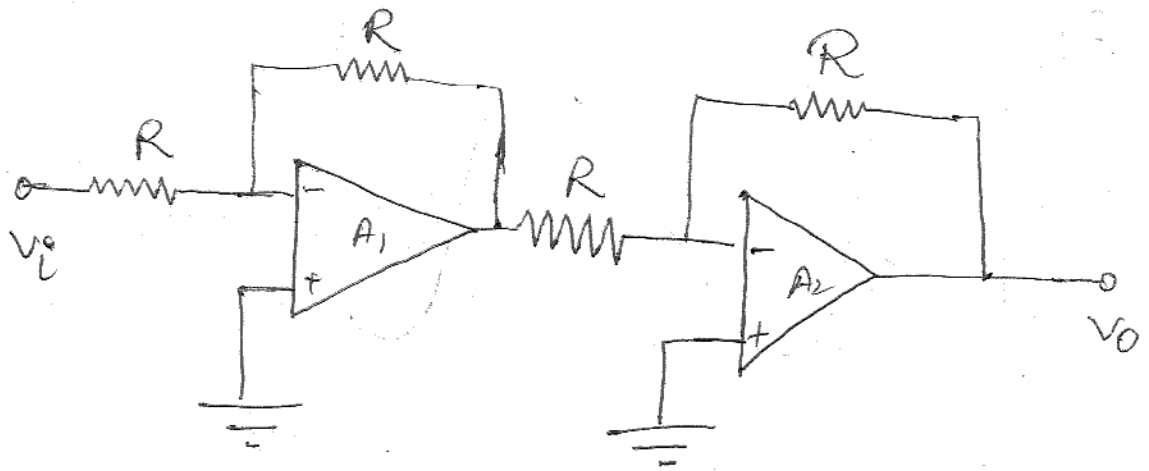

Case (ii)  $V_i < 0$

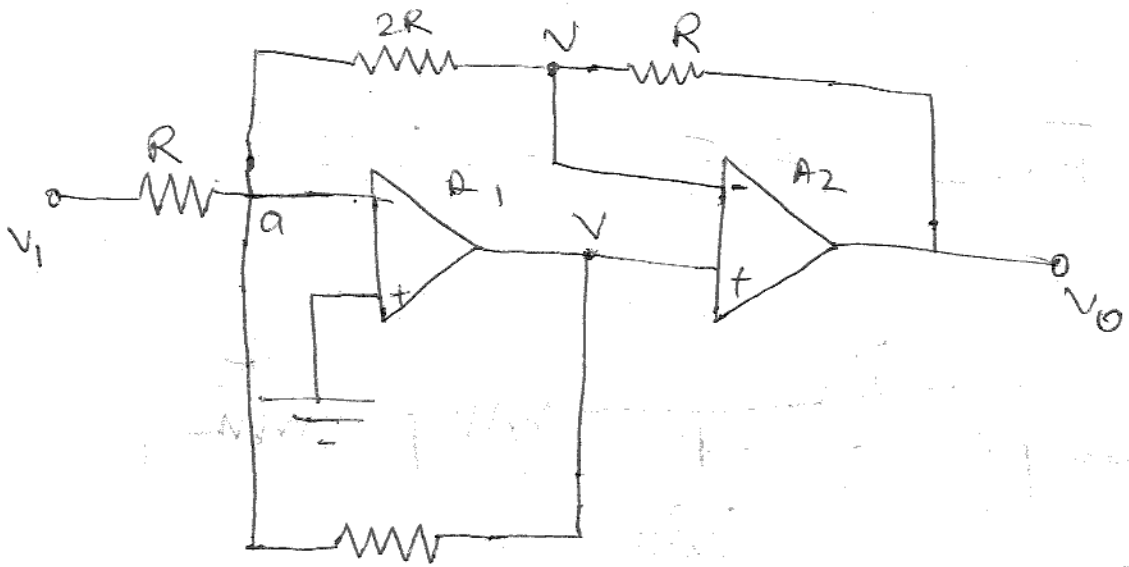

$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$

using node 'a'

$$\frac{V_i}{R} + \frac{V}{2R} + \frac{V}{R} = 0$$


$$V = -\frac{2}{3} V_i$$

$$V_o = \text{Gain} (V_i)$$

$$= \left(1 + \frac{R_f}{R_i}\right) \left(-\frac{2}{3} V_i\right)$$

$$V_o \equiv -\frac{2}{3} \left(1 + \frac{R_f}{R_i}\right) V_i$$

Waveform

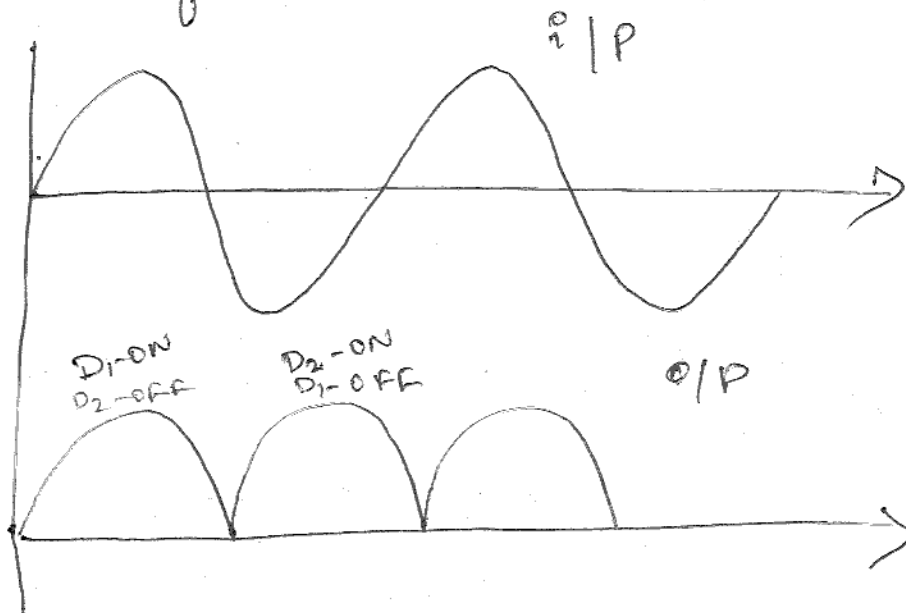

## Monostable Multivibrator

$$V_0 = V_{fi} + (V_{in} - V_{fi}) e^{-t/RC}$$

$$V_{fi} = -V_{sat} \quad V_{in} = V_D$$

$$V_0 = -\beta V_{sat}$$

$$\Rightarrow -\beta V_{sat} = -V_{sat} + (V_D + V_{sat}) e^{-t/RC}$$

$$\Rightarrow V_{sat} - \beta V_{sat} = (V_D + V_{sat}) e^{-t/RC}$$

$$V_{sat}(1-\beta) = (V_D + V_{sat}) e^{-t/RC}$$

$$\frac{V_{sat}(1-\beta)}{V_D + V_{sat}} = e^{-t/RC}$$

$$\Rightarrow \frac{(1-\beta)}{\left(1 + \frac{V_D}{V_{sat}}\right)} = e^{-t/RC}$$

$$\ln\left(\frac{1-\beta}{1 + \frac{V_D}{V_{sat}}}\right) = -t/RC$$

$$RC \ln\left(\frac{1-\beta}{1 + \frac{V_D}{V_{sat}}}\right) = -t$$

$$T = RC \ln\left(\frac{1 + \frac{V_D}{V_{sat}}}{1-\beta}\right)$$

Application

→ Pulse detection.