

As the gain of integrator \downarrow , with freq \uparrow ,
 the integrator act will not have frequency
 as differentiator

(ii) At low frequency, gain becomes ∞ ,

J.S.
 19107111

~~20/7/11~~

27/7/14

V-I Converter (Transconductance Amplifier)

(i) floating load.

(ii) Grounded load.


$$V_i \rightarrow I/P$$

$$I_o \rightarrow O/P$$

$$I = \frac{V}{R} = \left(\frac{1}{R}\right) V$$

\uparrow Conductance.


Floating load :-

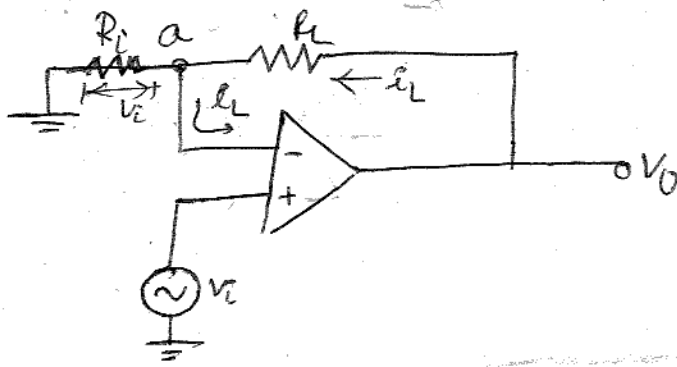

Since op-amp is said to be ideal,

$$V_i = R_i i_i$$

$$i_i = \frac{V_i}{R_i}$$

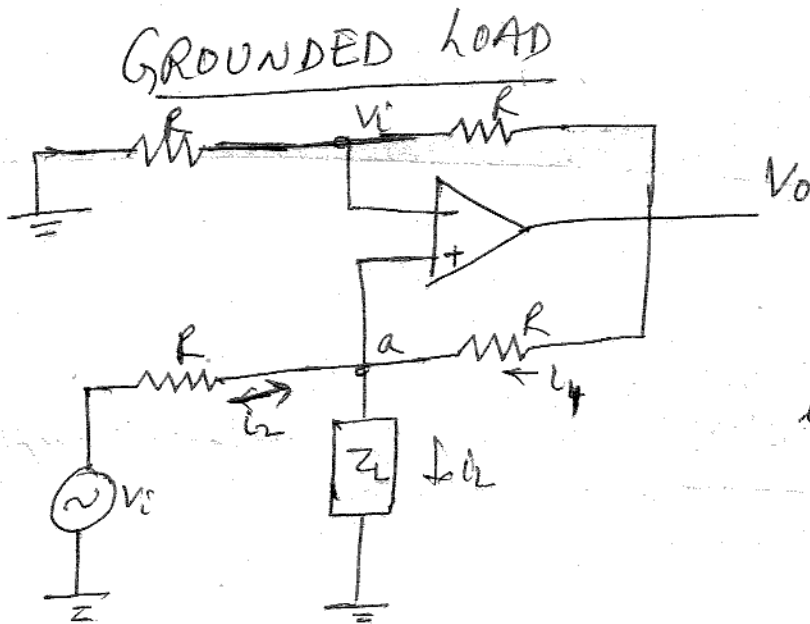

$$i_L = i_1 + i_2$$

$V_i \rightarrow i_1$
 \hookrightarrow load current

Apply KCL at node 'a',

$$i_1 = i_2 + i_L$$

$$\frac{V_o - V_a}{R} = \frac{V_i}{R} + \frac{V_a}{Z_L}$$

$$\Rightarrow \frac{V_o}{R} = \left[\frac{V_i}{R} + \frac{V_a}{Z_L} + \frac{V_a}{R} \right]$$

$$V_o = \left[V_i + \frac{V_a R}{Z_L} + V_a \right]$$

gain of non inverting terminal

$$= 1 + \frac{R_f}{R_a} = 1 + \frac{R}{R} = 2$$

$$V_o = \text{gain}(V_i)$$

$$\Rightarrow V_i + V_a + \frac{V_a(R)}{Z_L} = 2[V_i]$$

Apply KCL at node a.

$$i_1 + i_2 = i_L$$

$$i_L \equiv \frac{V_o - V_a}{R} + \frac{V_i - V_a}{R}$$

$$i_L R = V_o - V_a + V_i - V_a = V_o + V_i - 2V_a$$

$$\Rightarrow \boxed{2V_a = V_o + V_i - i_L R}$$

gain of non-inverting terminal

$$= 1 + \frac{R_f}{R} = 1 + R/R = 2$$

$$V_o = \text{gain}(\text{i/p voltage})$$

$$= 2V_a$$

$$V_o = V_o + V_i - i_L R$$


$$\Rightarrow V_i = i_L R \Rightarrow \boxed{i_L = \frac{V_i}{R}}$$

As i/p impedance of non-inverting amplifier is very high, this ckt has the advantage of drawing a very little current from the source.

Applications :-

- (i) LED,
- (ii) ZENER DIODE TESTER

COMPARATOR :-

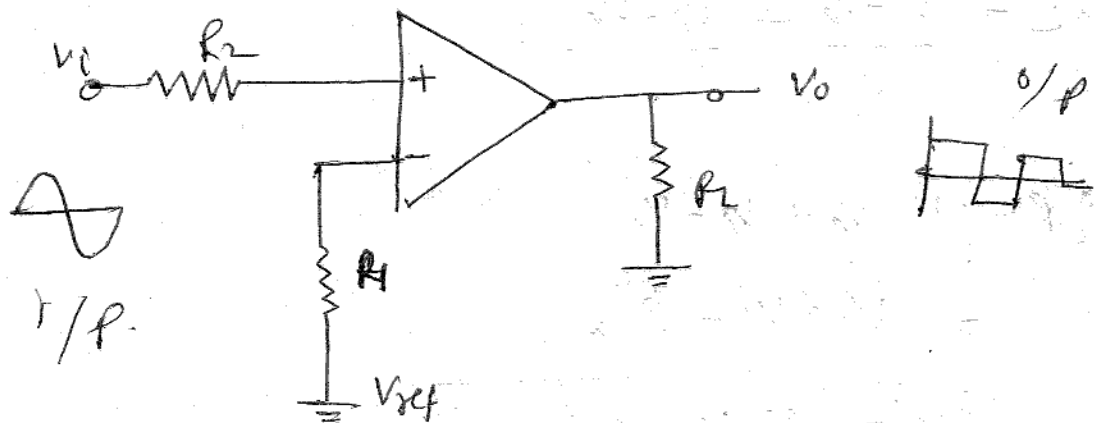


$v_i \rightarrow$ Varying w.r to time

$v_{ref} =$ Constant voltage


WAVEFORM :-

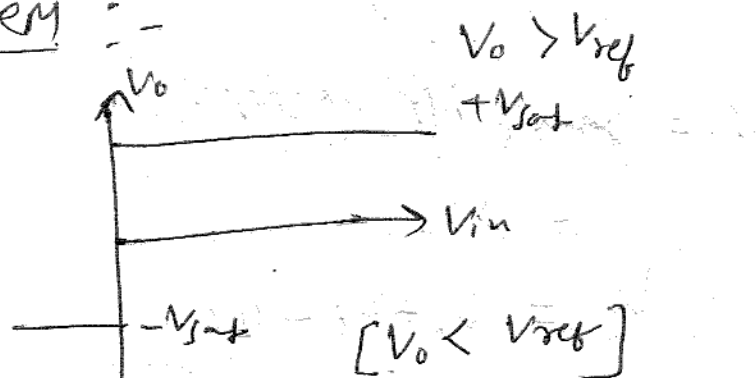always
i/p is Sin wave
o/p is Square wave





ideal comparator


Non-Inverting

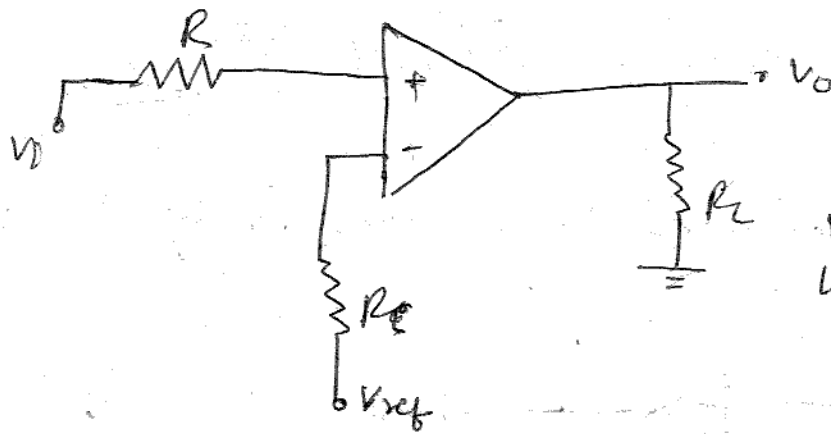

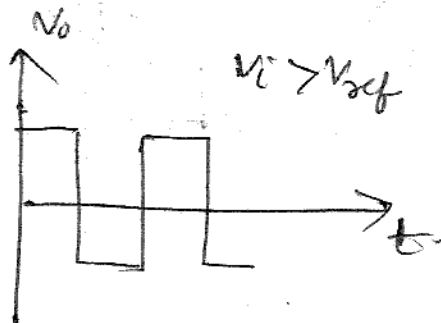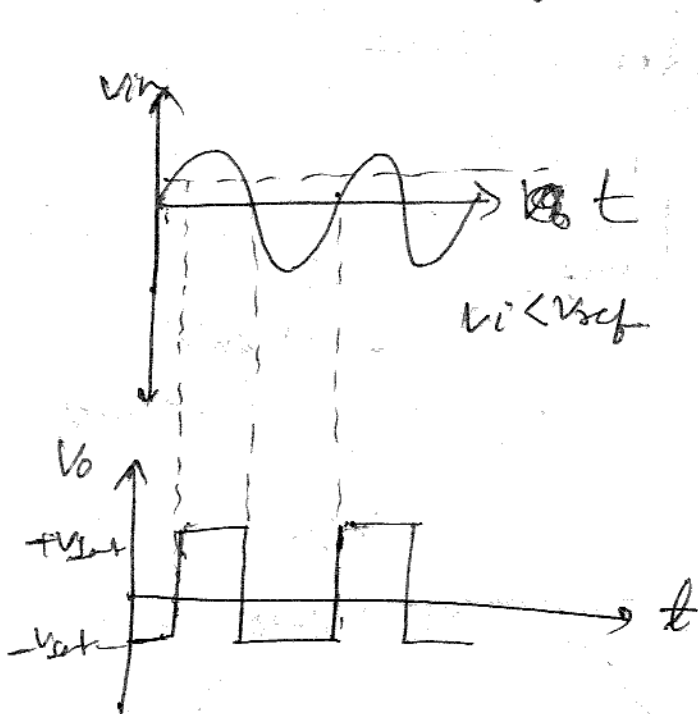o/p when $V_i < V_{ref}$
 $V_o = -V_{sat}$



Inverting Comparasator



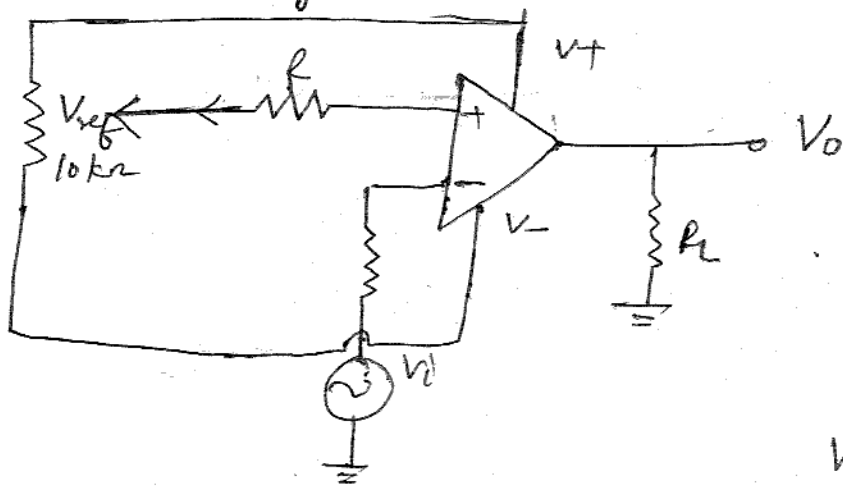


$V_i < V_{ref}$
 $V_o = +V_{sat}$
 $V_i > V_{ref}$
 $V_o = -V_{sat}$



Regenerative Comparator :-

→ also known as Schmitt Trigger

→ Converts sine wave to square wave

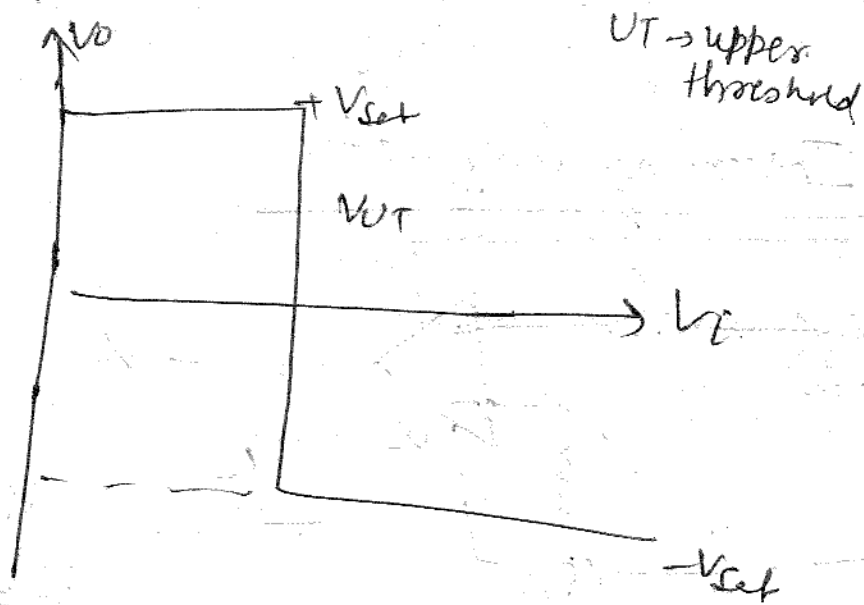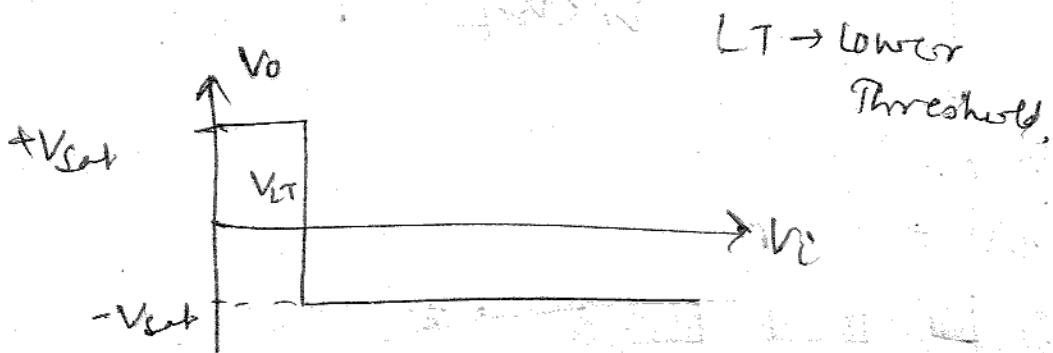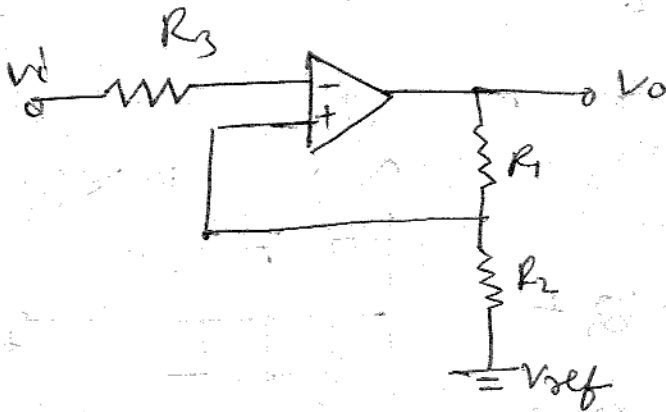

Triangular wave generation

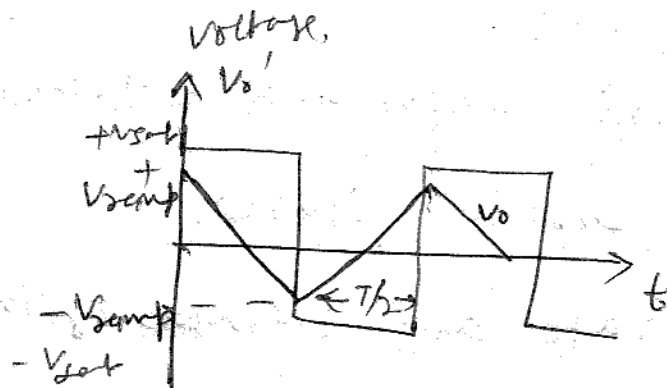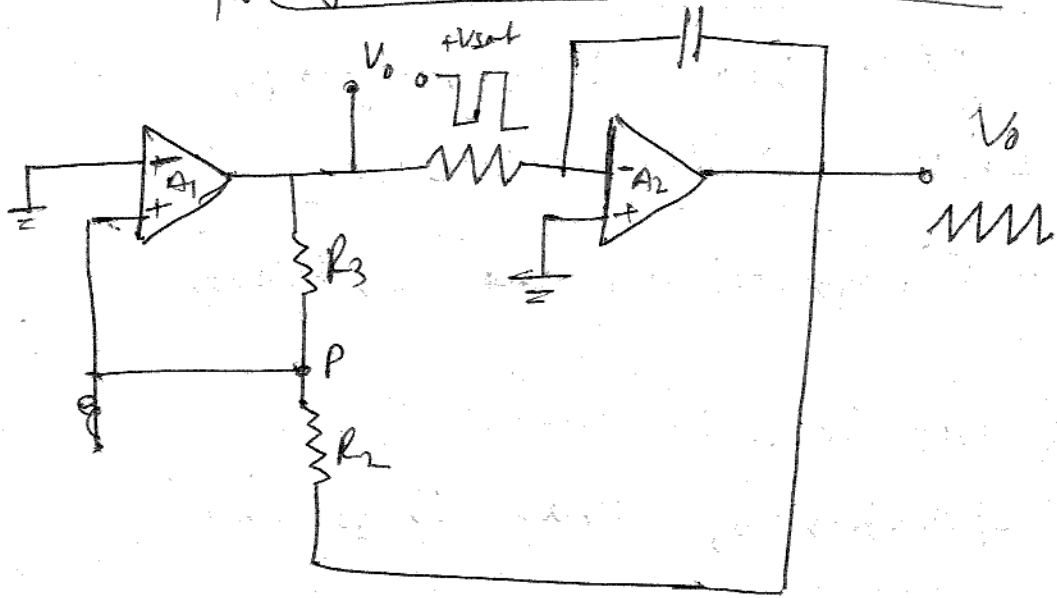

3/8/14

Important Q

① R-C phase shift oscillator
→ ~~Wheatstone Bridge~~ oscillator

→ ② Differentiator and Integrator

③ Wilson Current Source.

④ operation of phase shift base differential amplifier.

⑤ Frequency Compensation techniques.

⑥ Wobler Current Source.

⑦ slew rate and methods of improving slew rate.

⑧ Voltage to Current Converter.

⑨ Triangular wave generator.

⑩ Schmitt Trigger, and Comparator.


Precision Diode Rectifier (PDR)

Diode (Cut in volt) ≈ 0.6 volt

Ideal voltage operates only above the cut in voltage.

\Rightarrow ~~RRP~~ PDR can operate below 0.6 V.

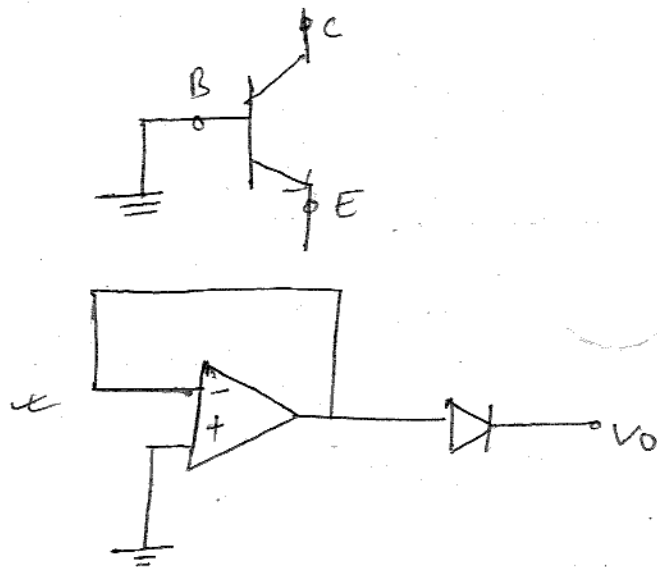\Rightarrow process to make transistor as a diode.




This ckt is also called Precision diode by connecting a diode in the feedback path of an op-amp. This ckt is capable of rectifying i/p signal of millivolts.

Types of Rectifier

- (i) Half wave
- (ii) full wave

Half wave rectifier :-

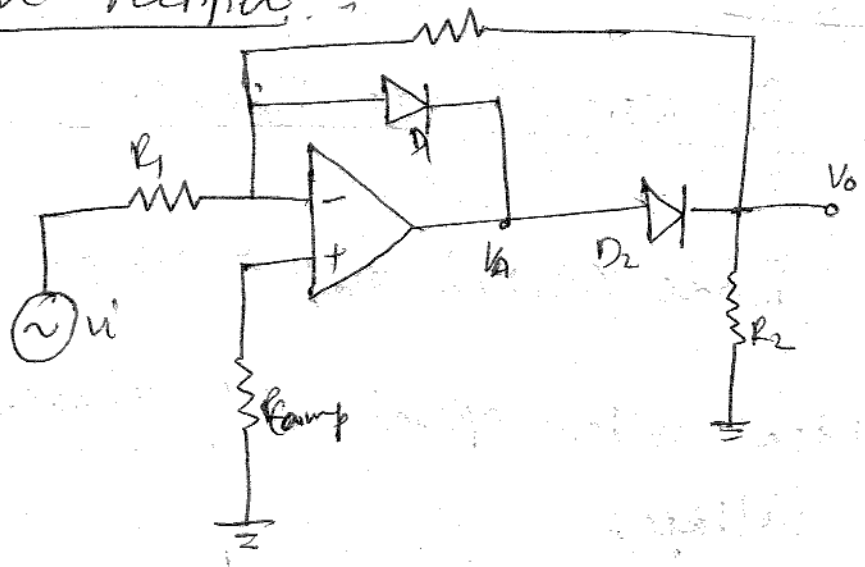


Analysis :-

$$V_i > 0V$$

\rightarrow +ve

$D_1 \rightarrow$ Conduct

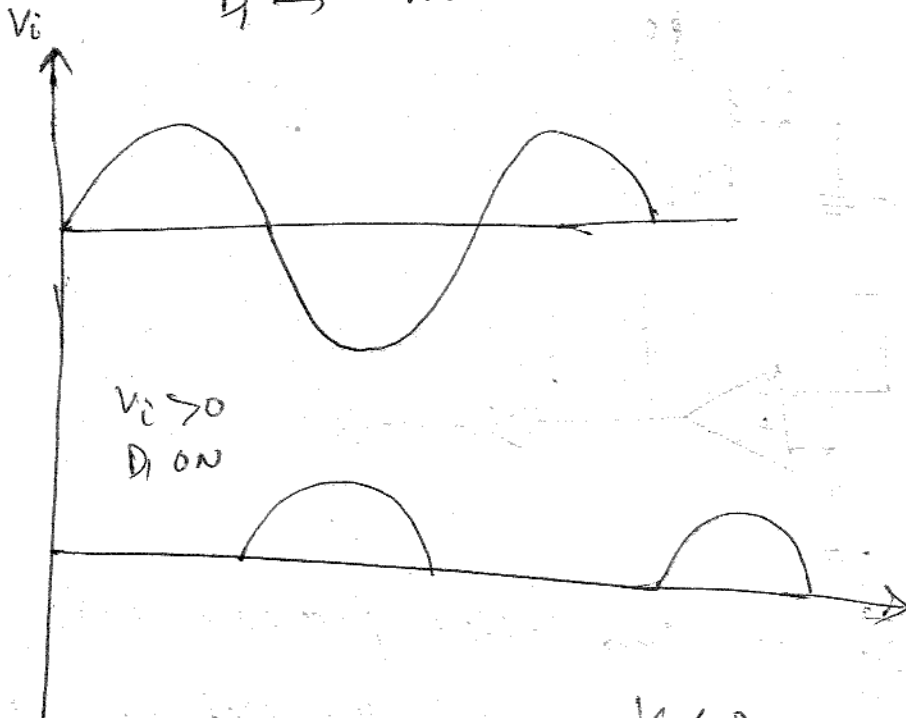

$V_i > 0$
 D_1 ON


$$V_i < 0$$

$D_1 \rightarrow$ OFF

$D_2 \rightarrow$ ON

$V_o \rightarrow$ ON

Full wave Rectifier

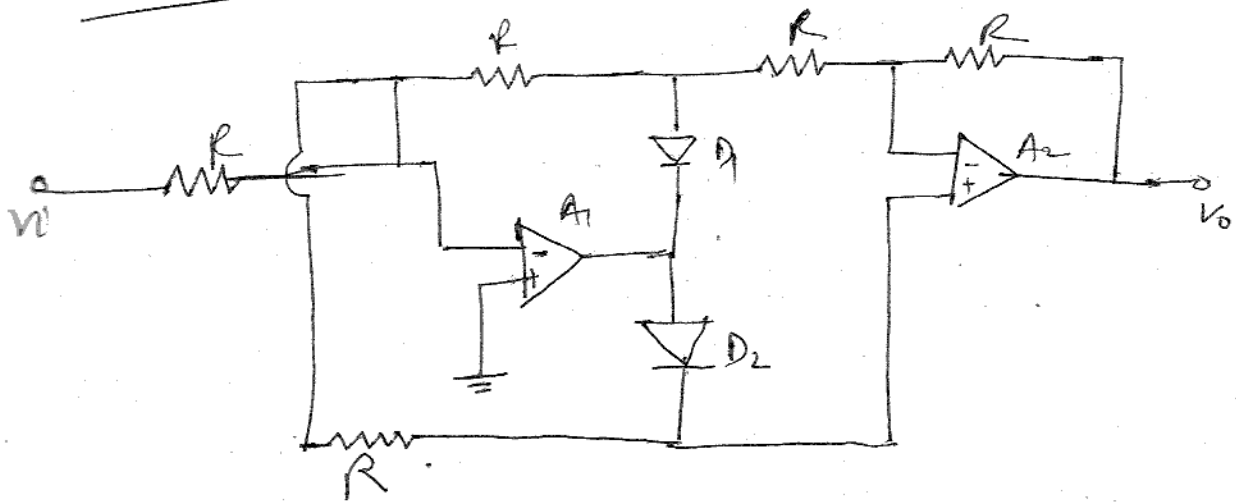


Both the op-amps act as inverters and
O/P voltage $V_o = 1/p$ voltage V_i .

Op on :-

$$V_i > 0$$

$$D_1 \rightarrow ON$$

$$D_2 \rightarrow OFF$$

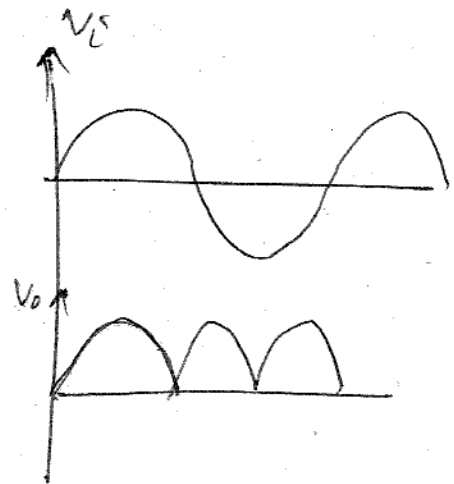


10/8/12

FILTERS


Types:-
LPF
HPF
BPF

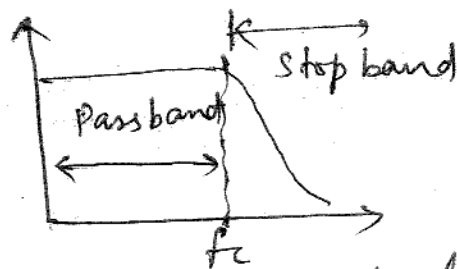A filter is a circuit that processes the signal based on frequency dependent characteristics, the manner in which the behaviour of the filter varies frequency, is known as frequency response.




LPF: it allows only lower freq. which is lower than ~~cut off~~ f_c .

HPF:-

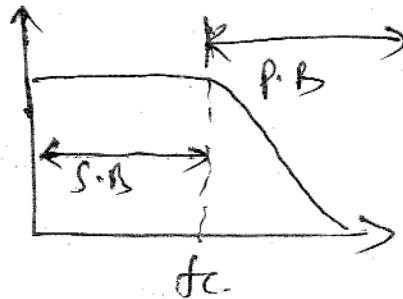


BPF:-

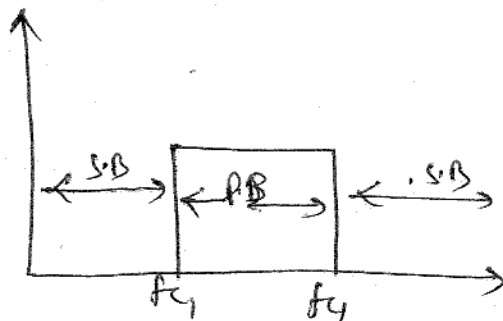

BPF:- it allows only particular range of frequency.

First order LPF

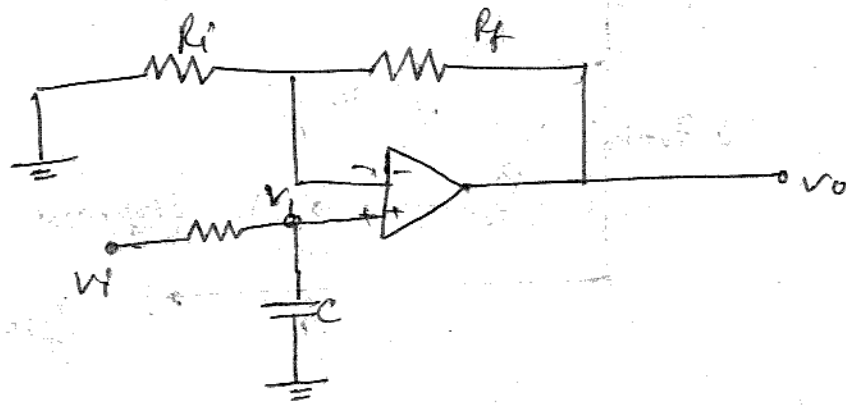

First order filter :- Consist of single RC n/w^k,
Connected to non-inverting terminal.
 R_i & R_f determines the gain of the filter
in pass band.

Voltage at C

voltage across capacitor, $V_1(s) = \frac{1/sC}{R+1/s} V_i(s)$

$$\Rightarrow \left| \frac{V_1(s)}{V_i(s)} = \frac{1}{1+sCR} \right|$$


Gain of OP-amp :- $\left| \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i} \right|$

now

$$\frac{V_o}{V_i} = \frac{V_o}{V_1} \times \frac{V_1}{V_i} = \left(1 + \frac{R_f}{R_i} \right) \left(\frac{1}{1+sCR} \right)$$

$$\Rightarrow \left| \frac{V_o}{V_i} = \left(A_{OL} \cdot \frac{1}{1+sCR} \right) \right| \quad \therefore A_{OL} = 1 + \frac{R_f}{R_i}$$

Frequency Response :-

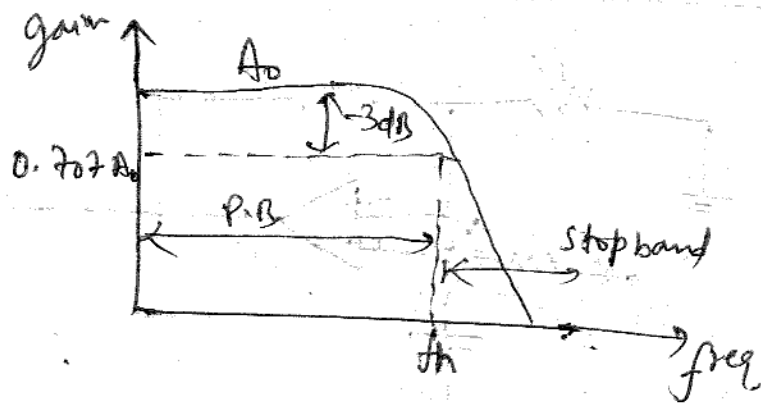

$$\frac{V_o(s)}{V_i(s)} = \frac{A_0}{1+sCR} \Rightarrow H(s) = \frac{A_0}{1+sCR}$$

Put $s = j\omega$

$$\Rightarrow H(j\omega) = \frac{A_0}{1+j\omega CR}$$

$$\frac{L}{RC} = \omega_c$$

Substitute $\frac{1}{RC} = \omega_c$

$$\Rightarrow H(j\omega) = \frac{A_0}{1+j\omega/\omega_c}$$

$$H(j\omega) = \frac{A_0}{1+(f/f_h)}$$

$f_h \rightarrow$ cut off frequency.

If $f < f_h \rightarrow$ Pass Band

$f = f_h \Rightarrow$ gain = $0.707 A_0$


$$V_1 Y_1 = V_A Y_1 - V_A Y_2 + V_B Y_2 - V_A Y_3 + V_C Y_3$$

$$\Rightarrow V_1 Y_1 = V_A (Y_1 - Y_2 - Y_3)$$

$$+ V_B Y_2$$

$$+ V_C Y_3$$

Second order LPF (Sallen Key filter)

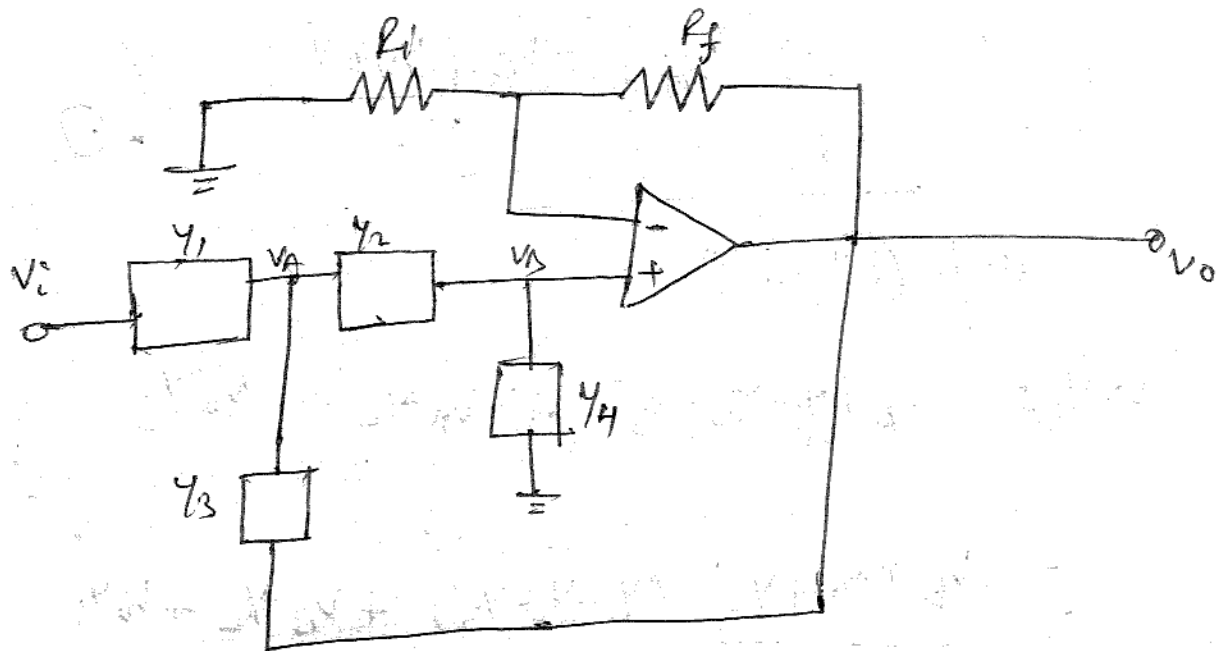

An improved version filter responds can be obtained by using 2nd order active filter. It consists of 2 RC pairs, and has a slope of -40dB .

Gain $A = \frac{V_o}{V_B} = 1 + \frac{R_f}{R_i}$

Apply KCL at node 'A',

$$(V_i - V_A)Y_1 + (V_A - V_B)Y_2 + (V_A - V_o)Y_3 = 0$$

$$\Rightarrow V_i Y_1 = V_A(Y_1 + Y_2 + Y_3) - V_B Y_2 - V_o Y_3 \quad \text{--- (1)}$$

$$V_i Y_1 = V_A Y_1 - V_A Y_2 - V_A Y_3 + V_B Y_2 + V_o Y_3$$

$$V_i Y_1 = V_A (Y_1 - Y_2 - Y_3) + V_B Y_2 + V_o Y_3$$

Apply KCL at 'B',

$$V_B(Y_4) + (V_B - V_A)Y_2 = 0$$

$$V_B(Y_4 + Y_2) = V_A Y_2$$

$$\boxed{V_A = \frac{V_B(Y_4 + Y_2)}{Y_2}} \quad \text{--- (2)}$$

Sub (2) in (1),

$$V_0 Y_1 = V_A(Y_1 - Y_2 - Y_3) + V_B Y_2 + V_0 Y_3$$

$$= \frac{V_B(Y_4 + Y_2)(Y_1 - Y_2 - Y_3) + V_B Y_2 + V_0 Y_3}{Y_2}$$

$$= V_B \left[\frac{(Y_4 + Y_2)(Y_1 - Y_2 - Y_3) + Y_2}{Y_2} \right] + V_0 Y_3$$

$$= V_B \left\{ \frac{Y_1 Y_4 - Y_2 Y_4 - Y_3 Y_4 + Y_1 Y_2 - Y_2^2 - Y_2 Y_3 + Y_2^2}{Y_2} \right\} + V_0 Y_3$$

$$= V_B \left\{ \frac{Y_1 Y_4 - Y_2 Y_4 - Y_3 Y_4 + Y_1 Y_2 - Y_2 Y_3}{Y_2} \right\} + V_0 Y_3$$

Apply KCL at node A

$$(V_A - V_i) Y_1 + (V_B - V_A) Y_2 + (V_0 - V_A) Y_3 = 0$$

Sub ② in ①,


$$V_i Y_1 = \frac{V_B}{Y_2} (Y_2 + Y_4) (Y_1 + Y_2 + Y_3) - V_0 Y_3 - V_0 Y_2$$

we get $\frac{V_0}{V_B} = A$

$$\Rightarrow V_0 = A V_B$$

$$\frac{V_0}{V_i} = \frac{A Y_1 Y_2}{Y_1 Y_2 + Y_4 (Y_1 + Y_2 + Y_3) + Y_3 Y_3 (1-A)}$$

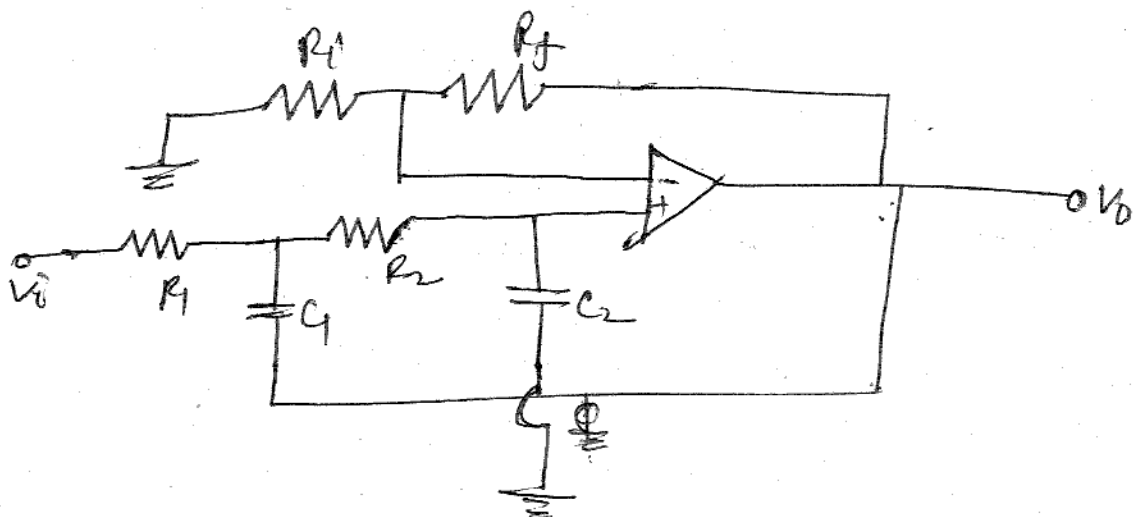
To make it a 2nd order filter,
as low pass filter choose $Y_1 = Y_2 = \frac{1}{R}$
and $Y_3 = Y_4 = sC$



$$\frac{V_o(s)}{V_i(s)} = \frac{A}{1 + s^2 C^2 R^2 + sCR(3-A)}$$


$$H(s) = \frac{A}{1 + s^2 C^2 R^2 + sCR(3-A)}$$

damping coefficient $\alpha = 3-A$

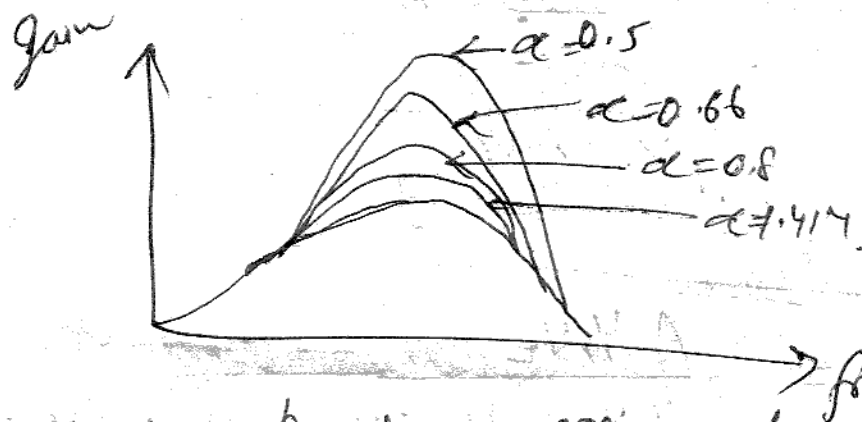


The flattest passband occurs for damping coefficient of $\alpha = 1.414$, this is called Butterworth filter, audio filters are usually Butterworth filter.

Band Pass filter

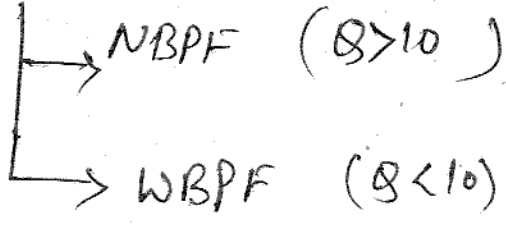

Narrow BPF → Path Narrow
 wideband BPF → wide.

Quality Filter :-
$$Q = \frac{f_0}{BW}$$

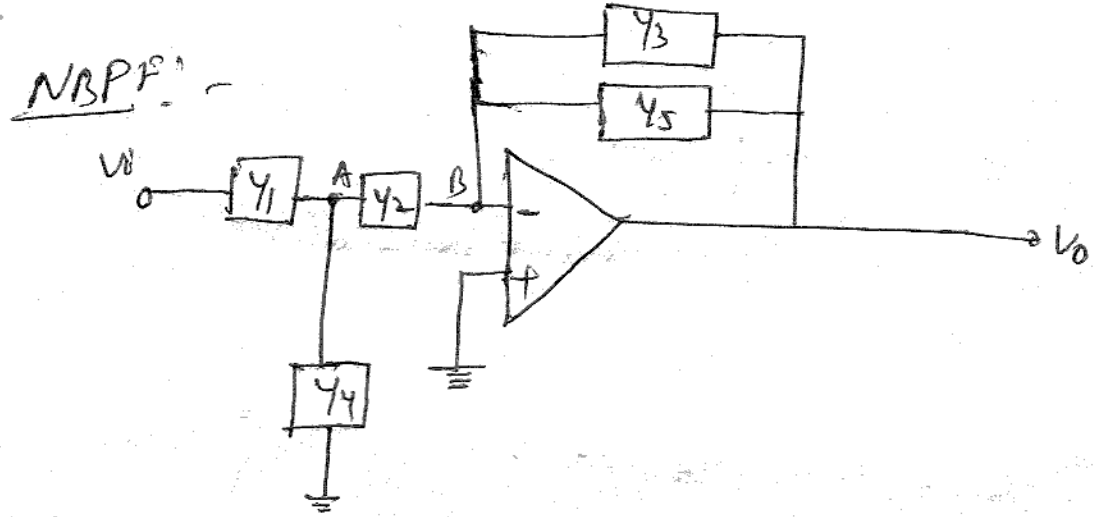

Apply KCL at node A,

$$V_A Y_1 = (V_A - V_B) Y_2 + V_A Y_4$$

$$V_A Y_1 = V_A (Y_2 + Y_4)$$

$\therefore V_B = 0$ at ground potential,
 $\therefore V_B$ is ground potential,

apply KCL at node B,

$$(V_A - V_B) Y_2 = (V_B - V_0) Y_5 + (V_B - V_0) Y_3$$

$$[V_B = 0]$$

$$V_A Y_2 = V_B Y_5 - V_0 Y_5 + V_B Y_3 - V_0 Y_3$$

$$V_0 (y_5 + y_3) = V_B (y_5 + y_3) - V_A y_2$$

$$V_0 = -V_A y_2 / (y_5 + y_3) \quad (2)$$

$$\frac{V_0}{V_i} = \frac{-y_1 y_2}{(y_3 + y_5)(y_2 + y_4)}$$

for,


to be band pass filter (narrow), put $y_1 = G_1$,

$$y_2 = S C_2, \quad y_3 = S G_3, \quad y_4 = G_4$$

$$y_5 = G_5$$


Wide band pass filter :- It is formed

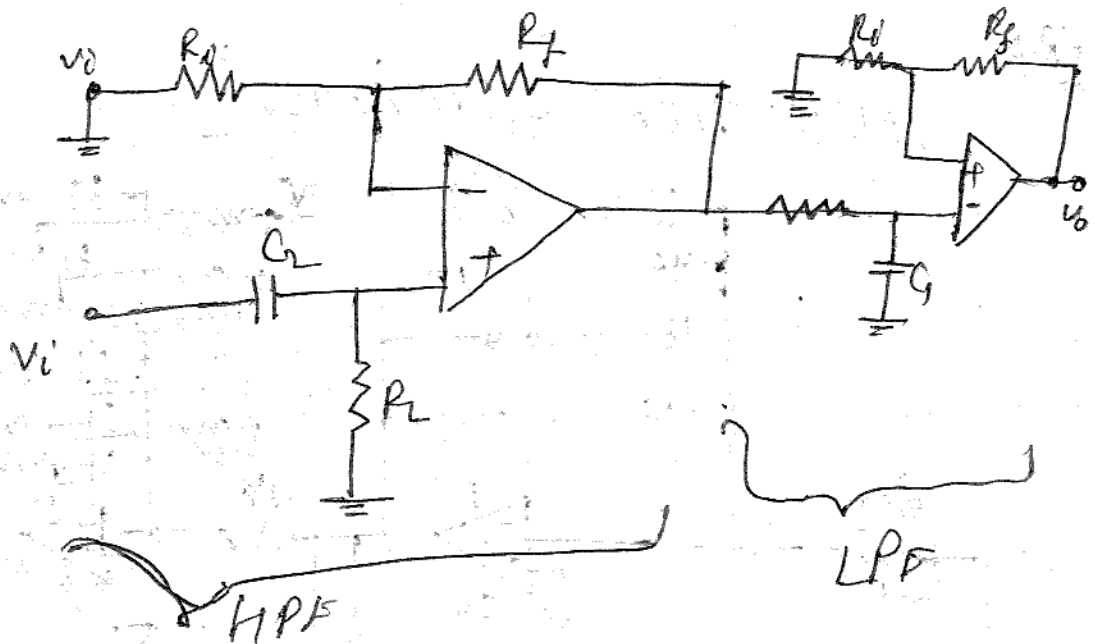by cascading high pass filter with low pass filter



11/8/14

Band Pass filter

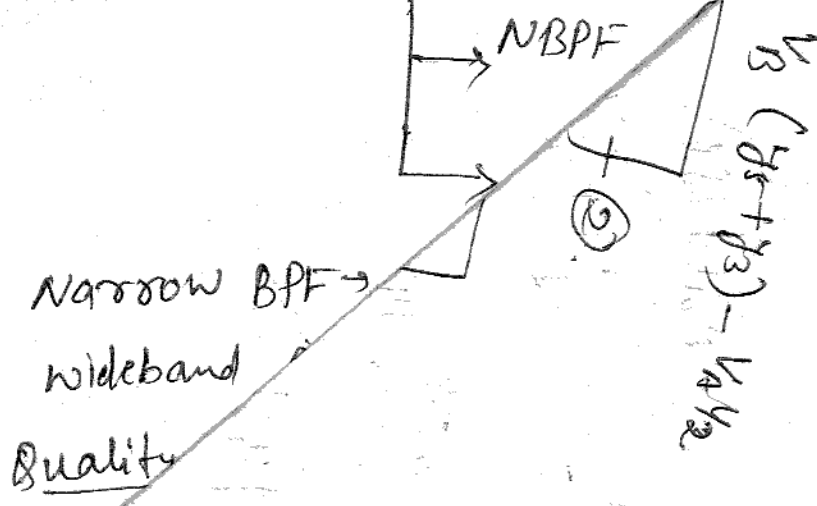


$A_o = A_{o1} \times A_{o2}$

the of Band pass, ... voltage gain
 gain of low pass filter and high pass filter
 the product of

$$\left| \frac{V_o}{V_i} \right| = \left| \frac{A_o (f/f_c)}{R_f \sqrt{1+(f/f_c)^2} \sqrt{1+(f/f_c)^2}} \right|$$

11/8/14



FUNCTION GENERATOR

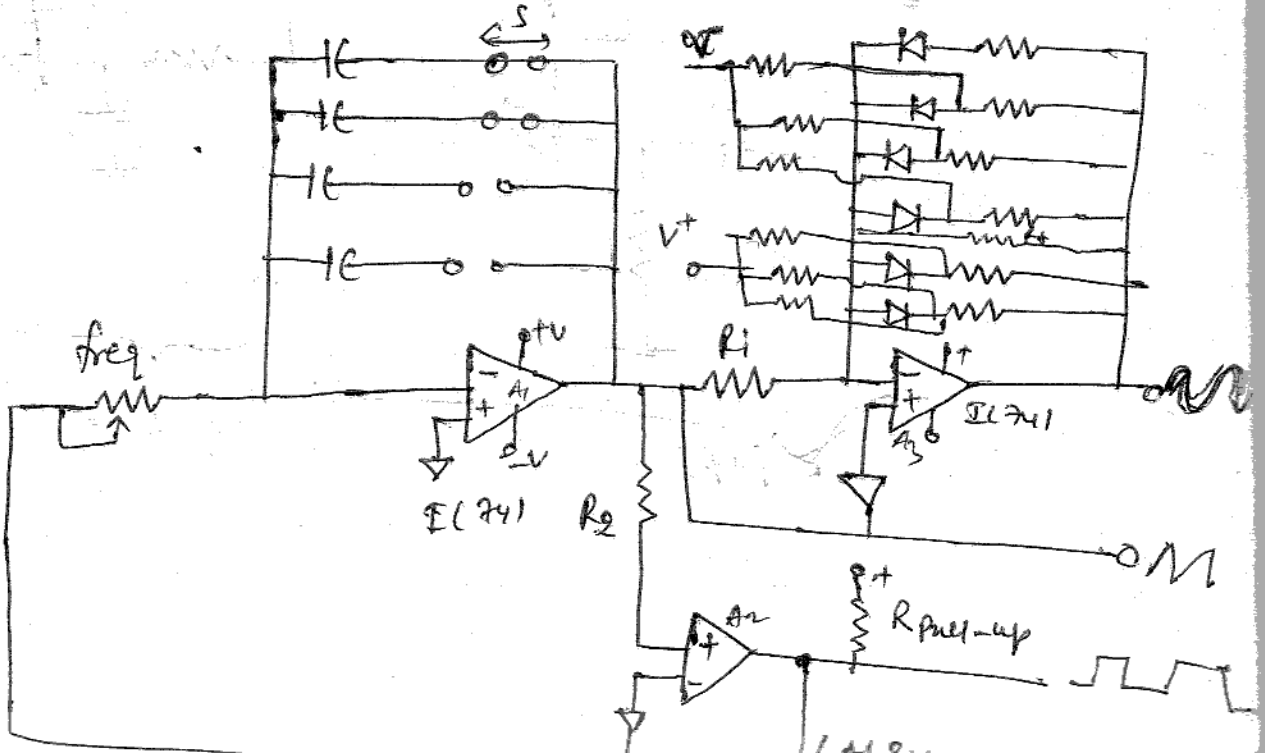

LM311 represents Comparator

A_1 acts as integrator

A_3 act as sine wave shaper.

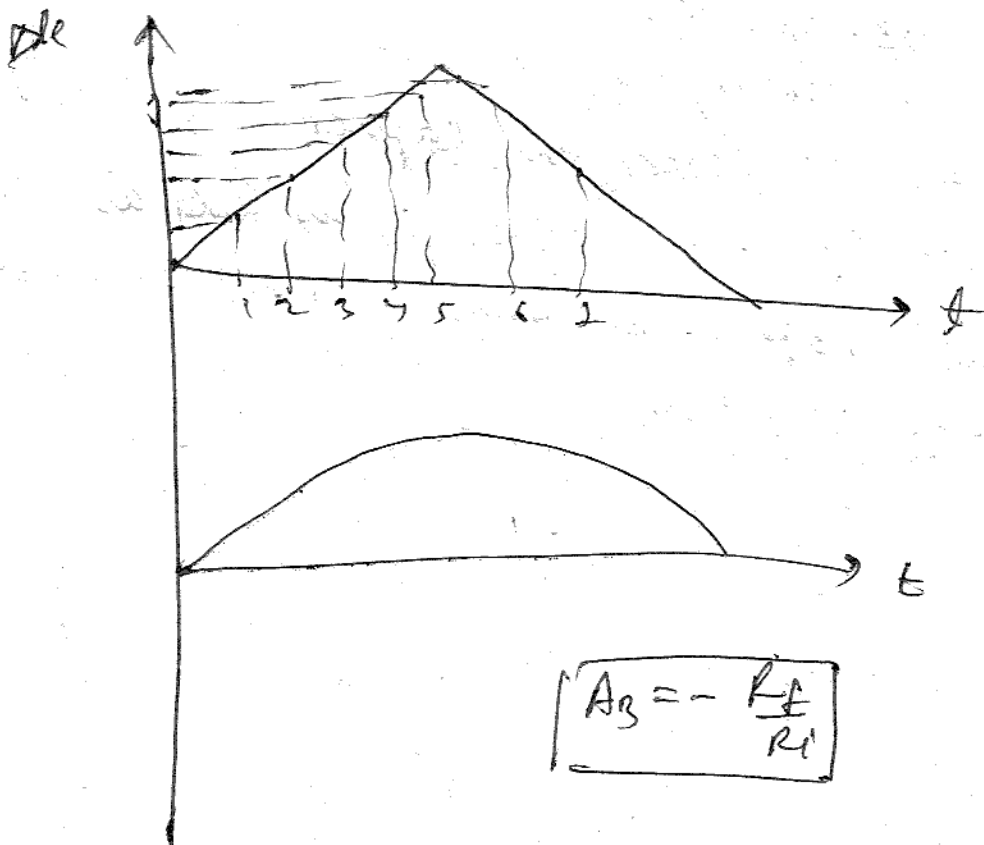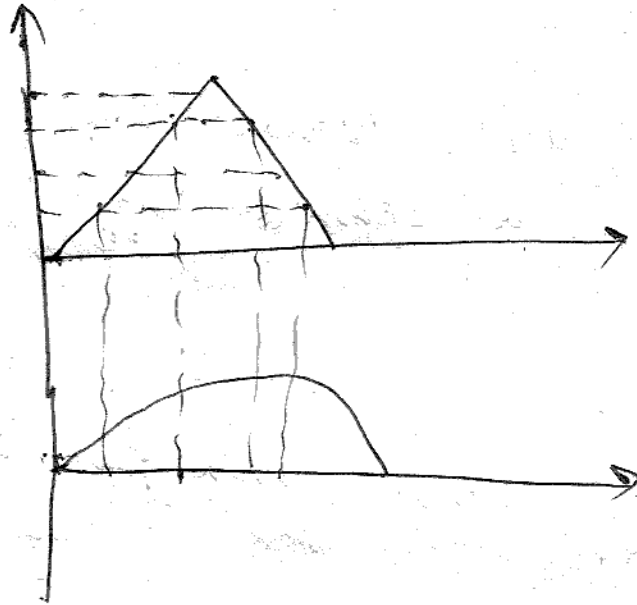

Function generator produces three types of waveforms, it is possible to achieve the frequency from very low value (0.01 Hz to 10 MHz) without significant distortion.

⇒ op-amp A_2 produces square waveform as it is used as a Schmitt trigger, or Comparator.

⇒ LM311 represents a high speed Comparator to produce square wave with fast rise & fall time.


⇒ The op-amp A_1 is used as integrator to produce triangular waveform.

⇒ Switch S selects the capacitor & operating frequency. A_3 (op-amp) is used as sine shaper it shapes triangular wave into sine waveform.

17/8/14

UNIT 3

Phase Locked loop

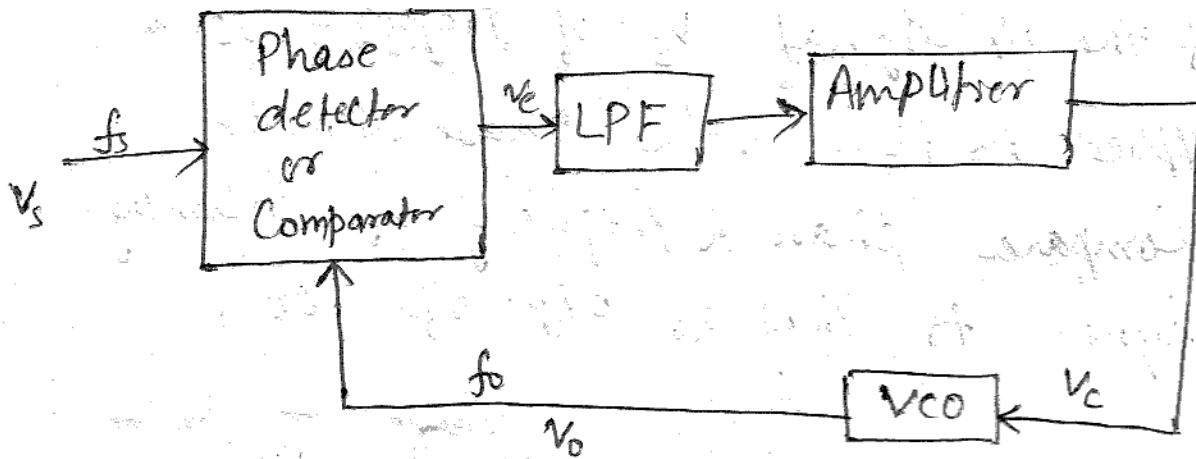

(1) Phase detector or Comparator

O/P $\rightarrow (f_s + f_o)$ or $(f_s - f_o)$

LPF \rightarrow It filters the high freq & allows the low freq $(f_s - f_o)$

$V_c \rightarrow$ dc voltage

$$V_o \propto V_c$$

Lock in range: - when $f_s = f_o$, then PLL is said to be locked.

Capture range: - range of freq $f_o = f_s$.

\Rightarrow VCO (Voltage Controlled oscillator), is a free running multivibrator & operates at a set frequency f_o called free running frequency.


The frequency deviation is directly proportional to V_c Controlled Voltage & hence it is called ~~the~~ VCO.

If the i/p signal V_s of frequency f_s is applied to PLL, the phase detector compares phase & frequency of incoming signal, to that of o/p of VCO.



Locked in Range :- Once the PLL is locked it can track the frequency in the incoming signal, the range of frequency over which the PLL can maintain is known as lock in range.

Captured Range :- The range of frequencies over which the PLL can acquire lock called as capture range.

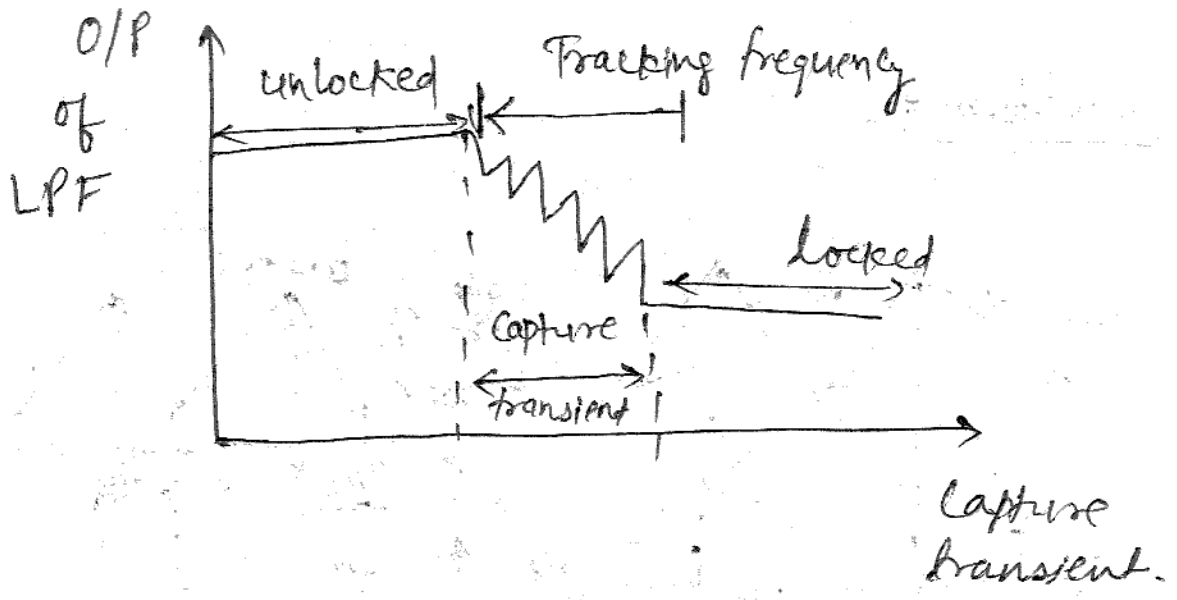Pull-in time :- The total time taken by the PLL to establish lock




Voltage Controlled Oscillator

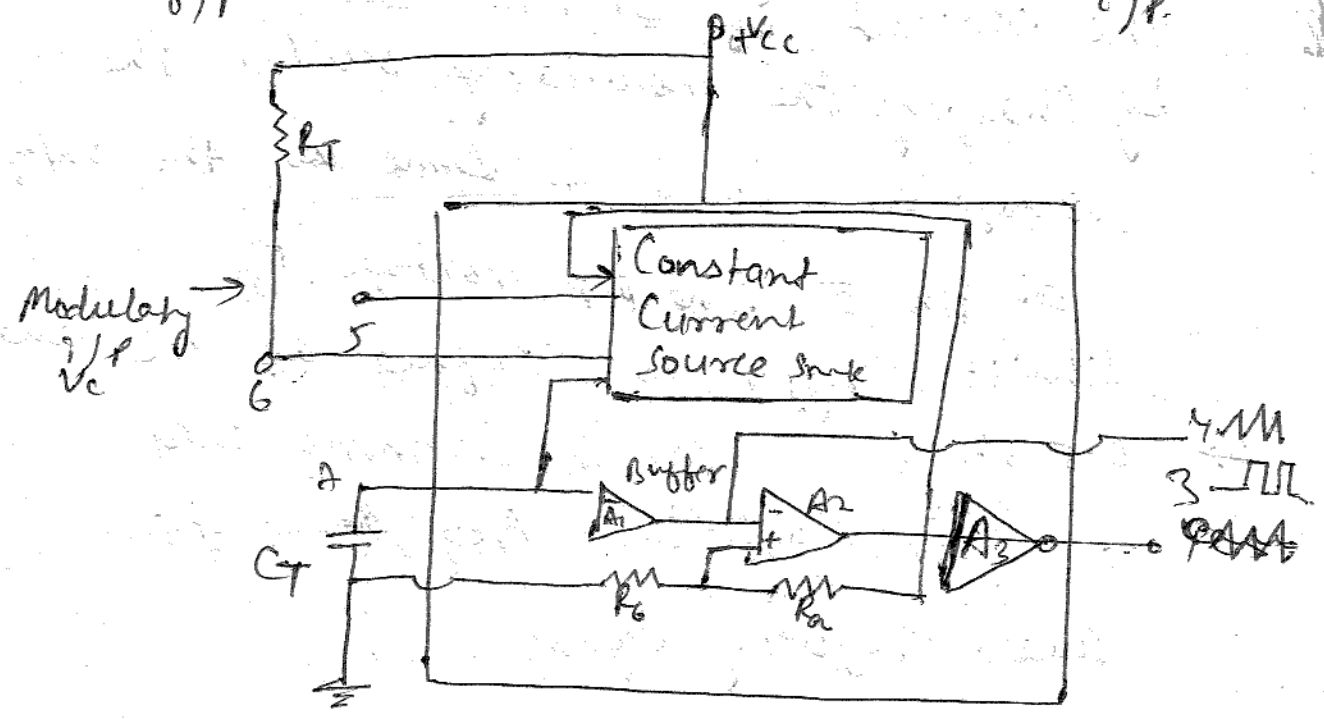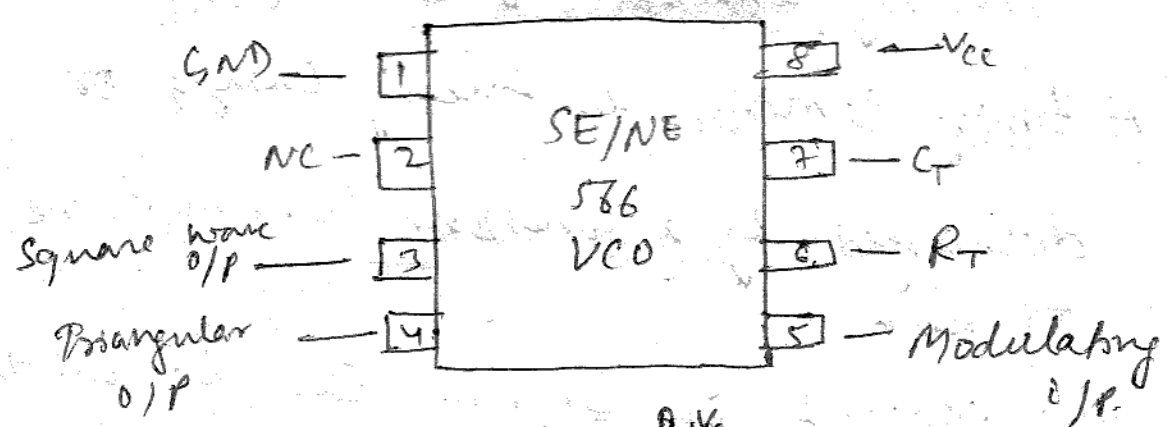

Block Diagram of VCO
 $A_2 \rightarrow$ Schmitt Trigger
 $A_3 \rightarrow$ inverter

$R_T, C_T \rightarrow$ ext timing. R & C.

Waveform :-

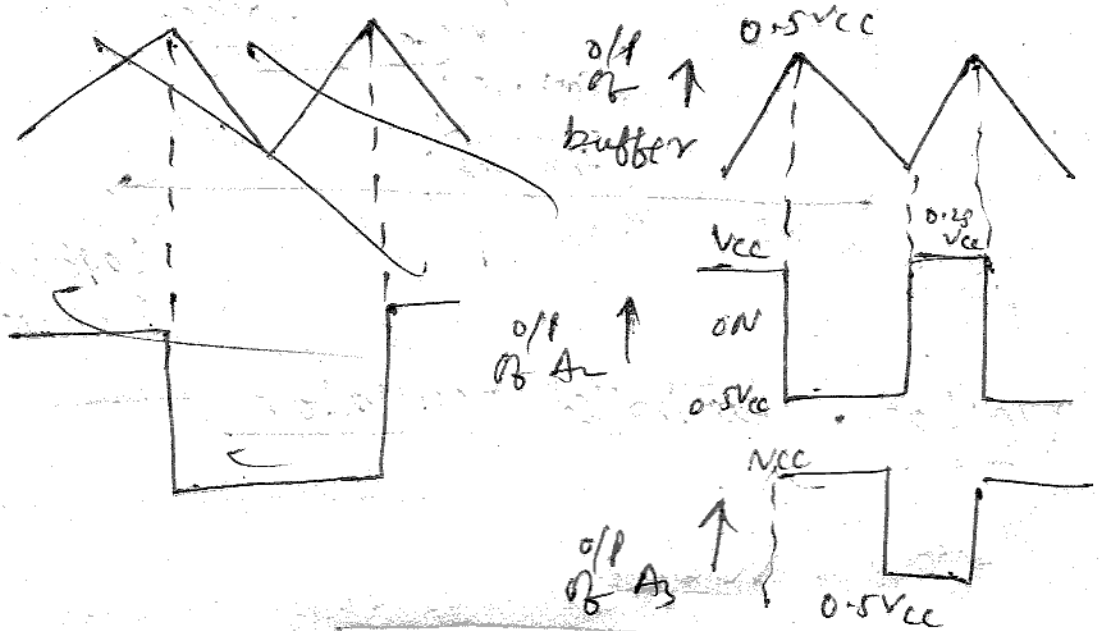

A timing capacitor is linearly charged or discharged by a constant current source or sink.

The amount of current can be controlled by changing the modulating voltage. The voltage at pin 6 is same as the voltage at pin 5. The o/p voltage of Schmitt Trigger is designed as V_{cc} and $0.5V_{cc}$. VCO is commonly used in converting low freq signal to audio frequency signal.

O/P freq of V_{ce} :-

$$f_o(0)$$

$$\frac{\Delta V}{\Delta t} = i / C_T, \quad \boxed{\Delta V \approx 0.25 V_{ce}}$$

The o/p freqⁿ is calculated by change in voltage with time.

ΔV varies from $0.25 V_{ce}$ to $0.5 V_{ce}$.

$$\Delta t = \frac{0.25 V_{ce} C_T}{i}$$

Time period of Δ wave is $2\Delta t$

$$\boxed{T = \frac{0.5 V_{ce} C_T}{i}}$$

also, $\boxed{\frac{i}{C_T} = \frac{0.25 V_{ce}}{\Delta t}}$

$$f_o = \frac{1}{T} \quad \boxed{f_o = \frac{i}{0.5 V_{ce} C_T}}$$

$$i = \frac{V_{ce} - V_c}{R_T}$$

$$\boxed{f_o = \frac{V_{ce} - V_c}{0.5 V_{ce} R_T C_T}}$$

The o/p frequency of V_{ce} can be changed either by R_T , C_T or modulating i/p V_c

Modulating $\frac{3}{8}$, $V_c = \frac{7V_{cc}}{8}$

$$f_o = \frac{V_{cc} - \frac{7V_{cc}}{8}}{0.5 V_{cc} R_T C_T}$$

$$= \frac{V_{cc}}{4 V_{cc} R_T C_T}$$


$$f_o = \frac{1}{4 R_T C_T}$$

Important parameter of V_{CO} is Voltage to frequency conversion factor. It is represented by (K_V)

$$K_V = \frac{\Delta f_o}{\Delta V_c}$$

18/8/14

Closed Loop Analysis of PLL

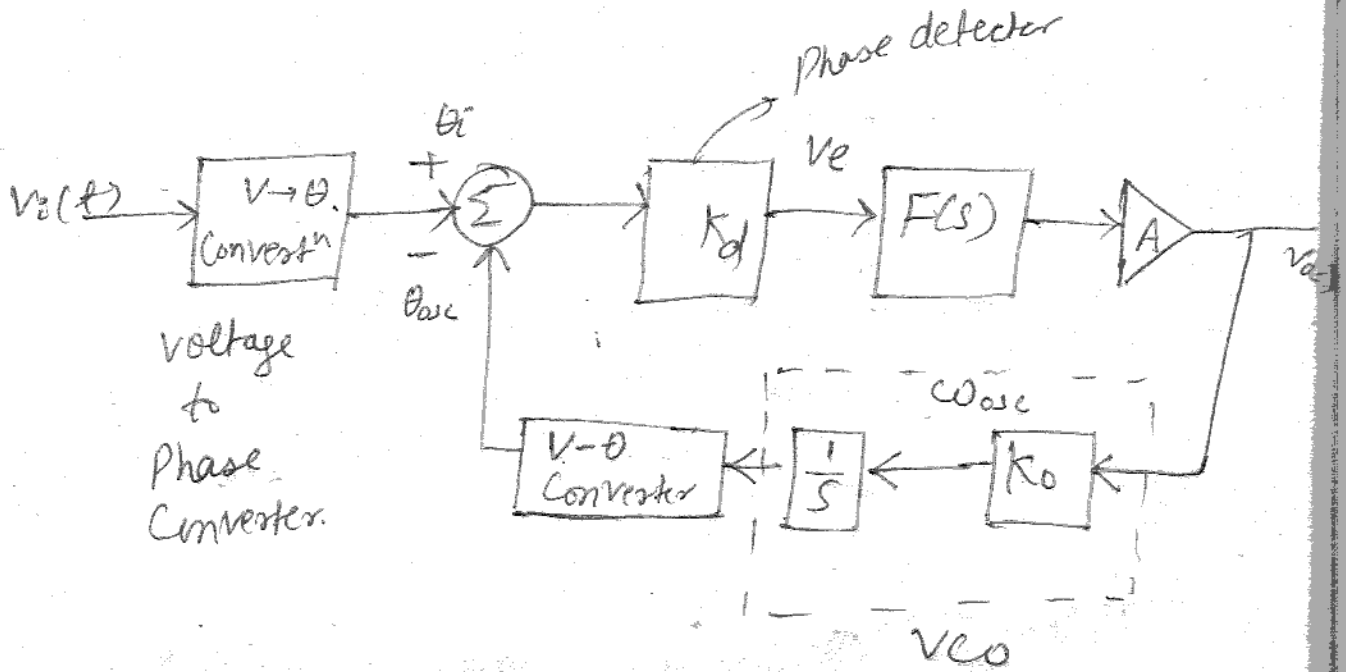

$$\frac{V_o(t)}{\theta_{os}(t)} = \frac{G(s)}{1 + G(s) \cdot H(s)} \quad \text{eqn ①}$$

$$V_i(t) = \sin(\omega t + \theta_i)$$

$$V_e = K_d (\theta_i - \theta_{osc})$$

$$\omega_{osc} \leftrightarrow \theta_{osc}$$

$$\omega_{osc} = \frac{d\theta_{osc}}{dt}$$

$$\theta_{osc} = \int_0^t \omega_{osc}(t) dt$$

In s-domain eqn ① becomes

$$\frac{V_o(s)}{\theta_{os}(s)} = \frac{K_d A f(s)}{1 + K_d A f(s) \cdot \frac{K_o}{s}}$$

Consider $H(s) = 1$

$$\frac{V_o(s)}{\theta_{os}(s)} = \frac{A k_d}{1 + k_d A k_o / s}$$

$$\frac{V_o(s)}{\theta_{os}(s)} = \frac{s A k_d}{s + k_d A k_o}$$

This is the response w.r.t. VCO freq.
o/p. Considering phase of o/p signal.

$$\frac{V_o(s)}{\theta_{os}(s)} = \frac{s A k_d}{s + k_d A k_o}$$

$$\frac{V_o(s)}{\omega_{osc}(s)} = \frac{A k_d}{s + k_d A k_o}$$

$k_v = k_d A k_o$


$$\frac{V_o(s)}{\omega_{osc}(s)} = \frac{A k_v}{s + k_v} \cdot \frac{1}{k_o}$$

k_v is known as trap Bandwidth
It is the effective bandwidth at
which the capture range are
dependent upon k_v . As $k_v \downarrow$,
capture time \uparrow , and capture range \downarrow
Therefore interference rejection
improves

Applications of PLL


- (i) AM detection
- (ii) FM detection
- (iii) FSK detection
- (iv) Frequency synthesizing.

AM detection

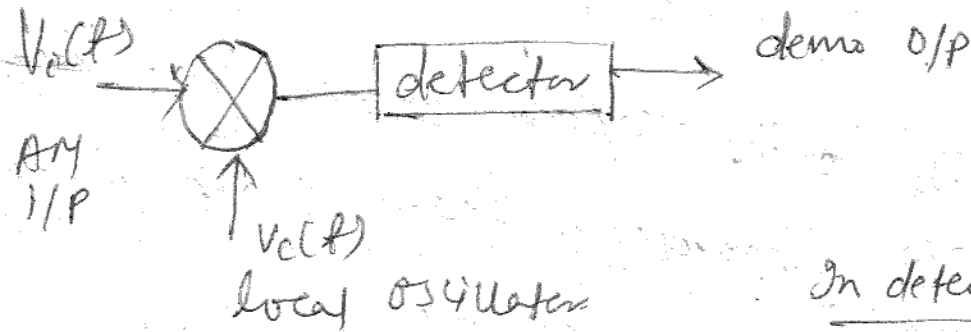

In detector we have LPF demod.

AM detection using PLL

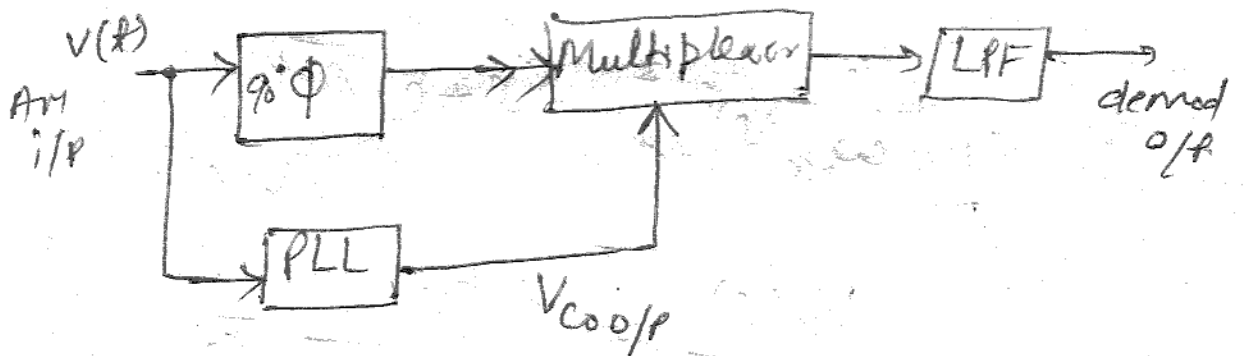

→ When PLL is locked o/p freq from V_{CO} is 90° phase shifted w.r.t i/p frequency.

$$V(t) = A \sin(\omega_c t + \theta) \\ = A \sin(\omega_c t - \theta)$$

Carrier freq :- $V_{CO} o/p = V_c \sin(\omega_c - \theta)$

→ PLL is locked to carrier freq. which has the same value as carrier

but ~~an~~ unmodulated is applied as one i/p to the multiplier

under carrier multiplication
90° phase shift & multiplier o/p will be
off of high frequency signal. LPF
allows only lower frequency signal
and this signal is the demodulated

o/p.

This AM detector exhibits the high
degree of selectivity due to that

PLL responds selectively to carrier
frequency, which are very close to VCO


o/p. Therefore higher degree of
noise immunity is achieved

19/8/11

FREQUENCY SYNTHESIZER

$f_R \rightarrow$ Ref. freq.

PLL

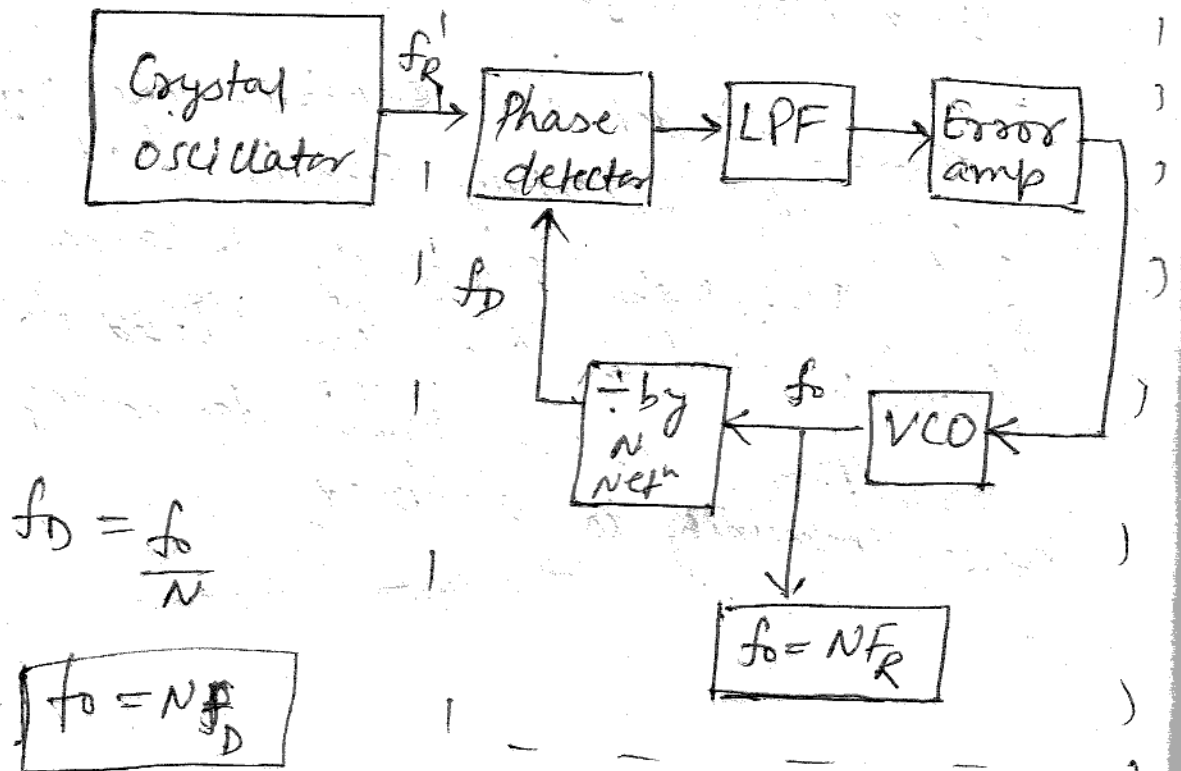

$$f_D = \frac{f_0}{N}$$


$$f_0 = N f_D$$

$$f_0 = N f_R$$

When $179 \text{ freq} = \text{VCO freq}$, PLL is said to be locked.

~~Using~~
 \rightarrow PLL can be used as the base is for freq. synthesizer that can produce, pre-determined freq. from a single crystal oscillator, under locked condition. O/p freq of VCO is N times of reference frequency, therefore it is possible to obtain multiples of reference freq.


(1) FM detection.

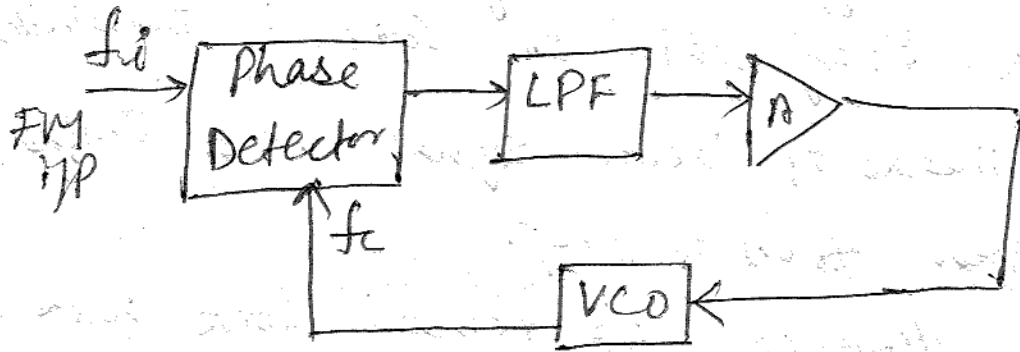

PLL is locked with input FM signal then VCO freq. will be equal to instantaneous freq of FM signal.

O/P \rightarrow inst value of FM signal.
 The Controlled voltage of VCO is a linear function of freq deviation, of instantaneous signal. Hence FM signal is demodulated without any distortion.

FSK Detection

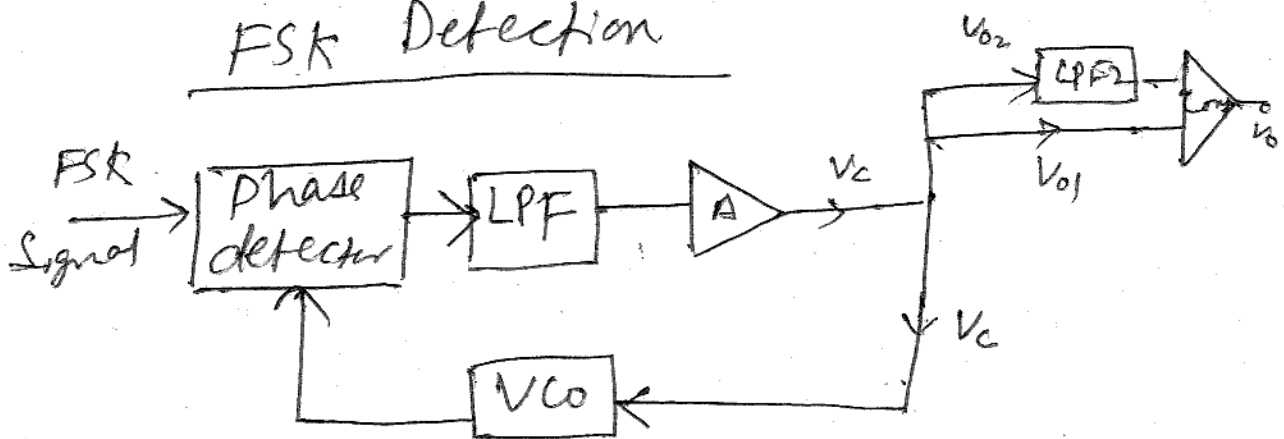

i/p \rightarrow binary 0's & 1's.

Carrier \rightarrow

FSK o/p \rightarrow

Binary data is varied according to the carrier signal

FSK is a type of Frequency modulation in which binary data or code is transmitted by means of carrier signal i.e. is shifted between two set of freq.

PLL is designed to remain lock with FSK signal for both freq. The Comparator is used to compare this two set of frequencies & produces the o/p which is the demodulated FSK.