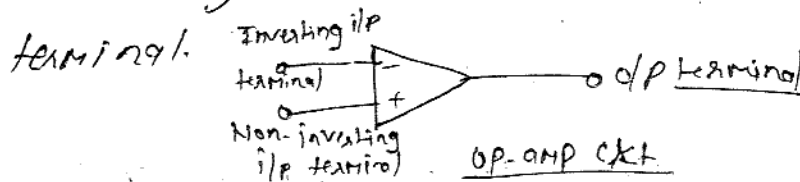


# LIC

## UNIT - 4

1) The operational amplifier is a multi-terminal device which internally is quite complex. op-amp's performance can be completely described by its terminal characteristics.

The circuit of op-amp is a triangle. It has two input terminal and one output terminal. The terminal with  $(-)$  sign is called inverting i/p terminal and the terminal with  $(+)$  sign is called the non-inverting input terminal.




### Characteristics

- (i) Open loop voltage gain,  $A_{OL} = \infty$
- (ii) Input impedance,  $R_i = \infty$
- (iii) Output impedance,  $R_o = 0$
- (iv) Bandwidth,  $BW = \infty$
- (v) Zero offset, i.e.  $v_o = 0$  when  $v_1 = v_2 = 0$

2) The common terminal of the  $V^+$  and  $V^-$  sources is connected to a reference point on ground. The common point of the two supplies must be grounded, otherwise twice

The supply voltage will get applied and it may damage the op-amp.

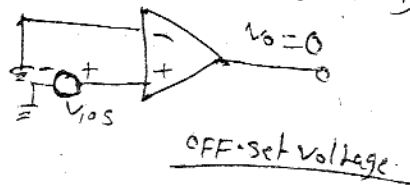- (4) In spite of the use of the compensating techniques, it is found that the output voltage may still not be zero with zero input voltage. This is due to unavoidable imbalances inside the op-amp and one may have to apply a small voltage at the input terminal to make op voltage zero. This voltage is called input offset voltage.



- (5) Bias current compensation will work if both bias currents  $I_B^+$  and  $I_B^-$  are equal. Since the input transistors cannot be made identical, there will always be some small difference b/w  $I_B^+$  and  $I_B^-$ . This difference is called the offset current  $I_{OS}$  and can be written as

$$|I_{OS}| = |I_B^+ - I_B^-|$$

The absolute value sign indicates that there is no way to predict which of the bias currents will be larger.

Even with bias current compensation offset current will produce an output voltage when the i/p voltage  $V_i$  is zero.

and


(6) The relative sensitivity of an op-amp to a difference signal as compared to a common-mode signal is called common-mode rejection ratio (CMRR) and gives the figure of merit  $\rho$  for the differential amplifier amplifier. So, CMRR is given by

$$\rho = \left| \frac{A_{DM}}{A_{CM}} \right|$$

and is usually expressed in decibels (dB).

(7) <sup>(4)</sup> A constant current source makes use of the fact that for a transistor in the active mode of operation, the collector voltage. Transistor  $Q_1$  and  $Q_2$  are matched as the circuit is fabricated using IC technology.

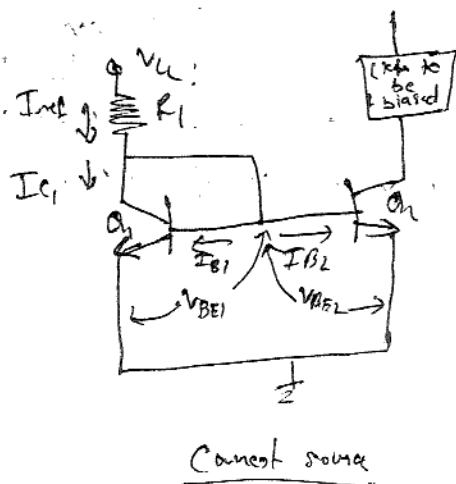(8) <sup>(4)</sup> above and the bases and emitter of  $Q_1$  and  $Q_2$  are tied together and thus have same  $V_{BE}$ . In addition, transistor  $Q_1$  is connected as a diode by shorting its collector to base.



(9) (1) The value of the Resistance, required is sufficiently high and can not be fabricated economically in IC circuit.

(2) Widlar current source is suitable for low value of currents.

(10) It is a rate of change of o/p voltage with respect to time.



$$S = \frac{\Delta V_o}{\Delta t} \text{ V/ms}$$

It is cause due to limited charging rate of compensating capacitor

$$C = I/V$$

Stew rate whose max. internal capacitor charging current is known

$$\frac{dV_c}{dt} = I/C$$

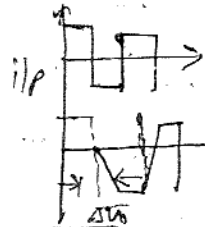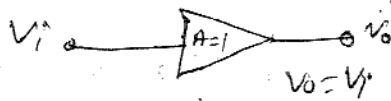

$$S = \frac{\Delta V}{\Delta t}$$

Ideally slew rate should be infinite for better performance of op-amp.

(11)

(12) In band suitable i.e.

Two types

(i) Ext


Dominant compen

(13) A

s/w on a gain the s/w to

Type


(11)

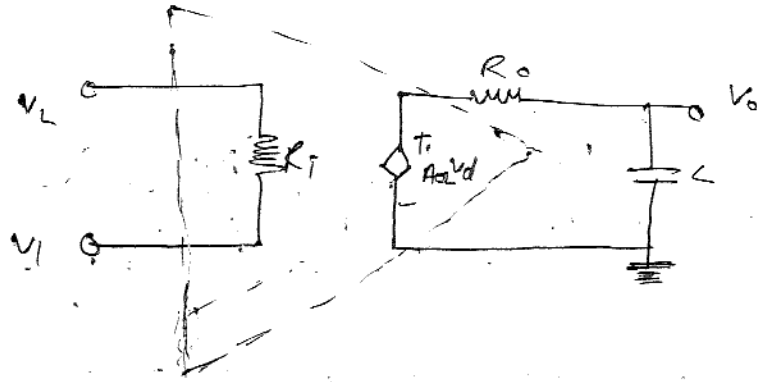

(12) In application where one desires large bandwidth and lower closed loop gain, suitable compensation techniques are used i.e. frequency compensation.


Two types of F.C

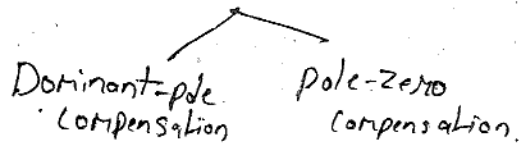- (i) External compensation
- (ii) Internal compensation.




(13) A circuit that amplifies the difference b/w two signal is called a difference or differential amplifier. It is provide high gain to the difference mode signal and cancel the common mode signal. it is able to suppress any Undesired noise which is common to both of the input terminals.

TYPE

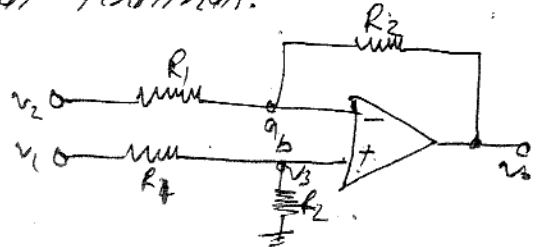

(17)

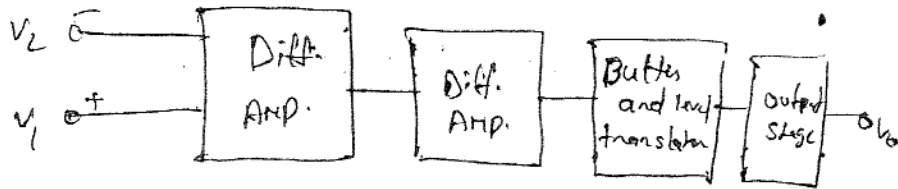

(18) 741, 741C, 741A, 741E, 741S, 741SC.

741 - Military grade op-amp

741C - Commercial grade op-amp

741A - Improved version of 741

741E - Improved version of 741C

741S - Military grade op-amp with high slew-rate.



741SC - Commercial grade op-amp with high slew-rate.

(19) The open circuit voltage gain of an op-amp should be as large as possible and this is achieved by cascading gain stages. However, this increases the phase shift too and amplification becomes more ~~affected~~ susceptible to breaking out into oscillations.

(19)  $R_E$  is replaced by a constant current transistor circuit in which  $R_1$ ,  $R_2$  and  $R_3$  can be adjusted to give the same quiescent condition for the transistor  $Q_1$  and  $Q_2$ . The modified circuit presents a very high effective emitter resistance  $R_E$  even for very small values of  $R_3$ .
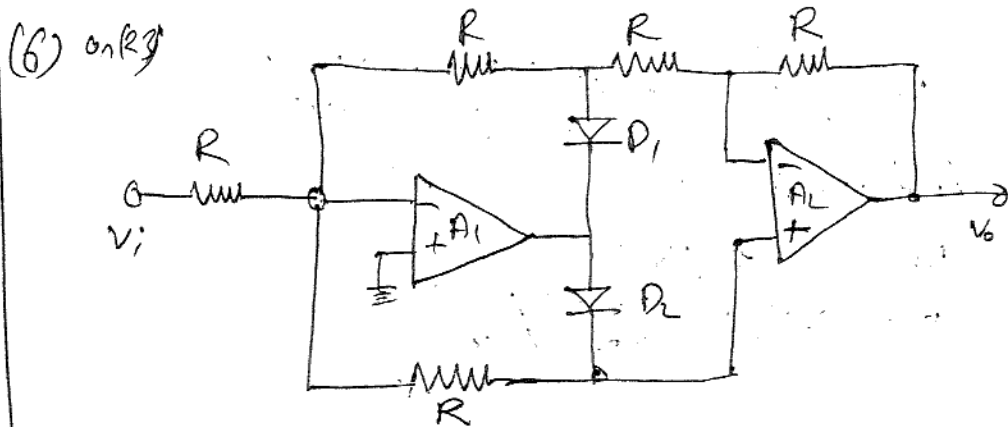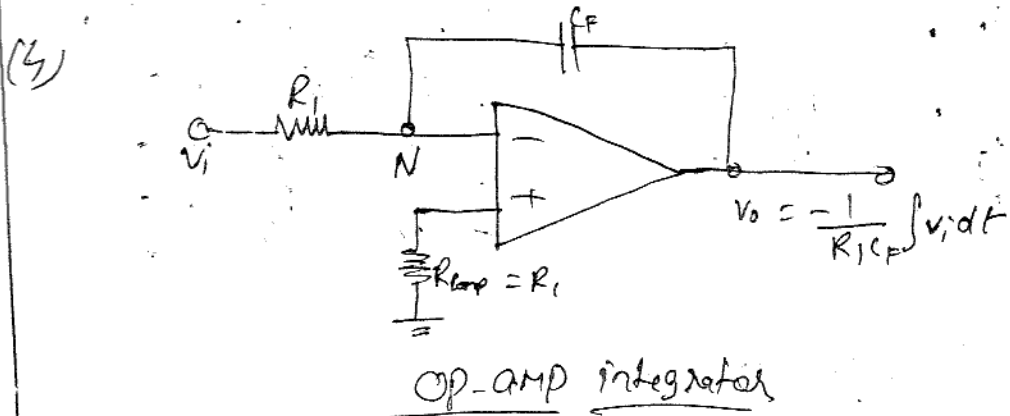
## UNIT-2

- ① Characteristics of Instrumentation Amplifier.
- ① high gain accuracy
  - ② high CMRR
  - ③ high gain stability with low temperature coefficient
  - ④ low dc offset
  - ⑤ low output impedance





(25) ① Monostable Multivibrator has one stable state and the other is quasi stable state.

In astable Multivibrator both the states are quasi stable.

② The circuit is useful for generating single output pulse of adjustable time duration in response to a triggering signal

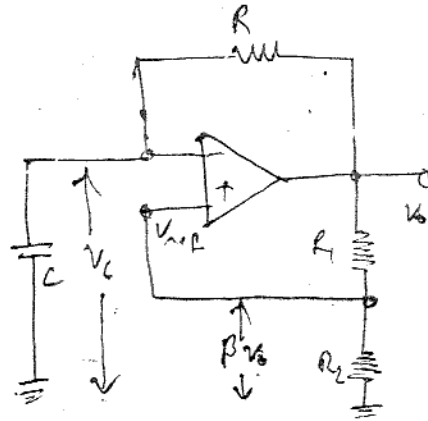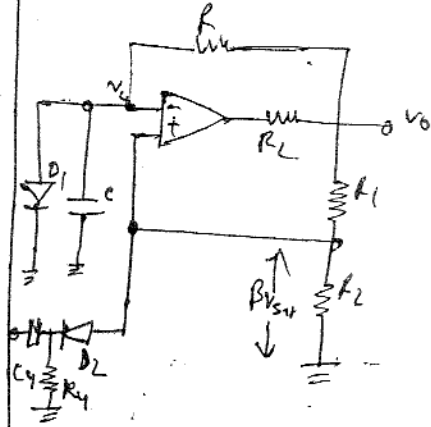The principal of generation of square wave output is to force an op-amp to operate in the saturation region.



(24) Log amplifier —

$$V_o = \frac{kT}{q} \ln\left(\frac{V_i}{V_{ref}}\right)$$

$$V_{o\text{comp}} = \left(1 + \frac{R_2}{R_{TC}}\right) \frac{kT}{q} \ln\left(\frac{V_i}{V_{ref}}\right)$$

Anti-log amplifier

$$V_o = V_{ref} (10^{k'V_i})$$

$$k' = 0.4343 \left(\frac{q}{kT}\right) \left(\frac{R_{TC}}{R_2 + R_{TC}}\right)$$

(22) Multivibrator — The electronic circuit which is used to generate the non-sinusoidal waveform are called multivibrator.

types


Monostable multivibrator

Astable " "




of  
to  
operate  
region.

(21)

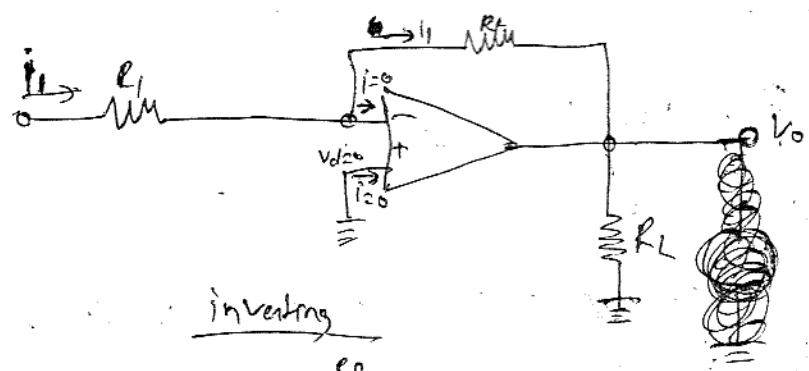


inverting

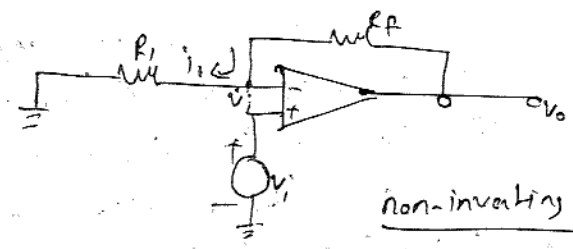

non-inverting

(20) (i) The function such as  $\ln x$ ,  $\log x$  or  $\sin x$  can be performed continuously with log-amps. Log-amp can easily perform this function.

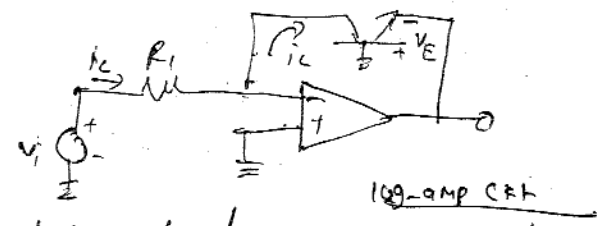(ii) Log-amp can also be used to compress the dynamic range of a signal.




log-amp CRT

(19) Application of precision diode


- (i) Half-wave rectifier
- (ii) Full - " "
- (iii) Peak value detector
- (iv) Clipper
- (v) Clamper.

(18) The circuit acts like a voltage follower for input  $V_i$  and the output  $V_o$  follow the input voltage  $V_i$  during the positive half cycle. When  $V_i$  is negative or less than  $V_{T/AOL}$ , the Diode D is off and no current is delivered to the load  $R_L$  except for small bias current of the op-amp and the reverse saturation current of the diode, it's called precision diode.

circuit  
sinusoidal

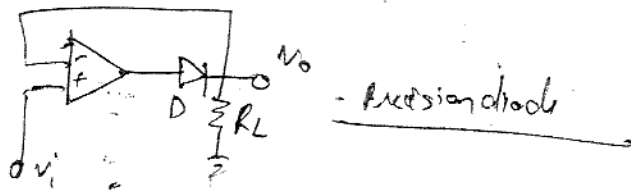

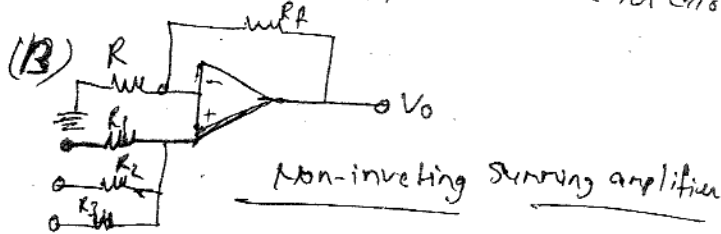- (11) - The op-amp is used in non-inverting mode
- The i/p impedance of a non-inverting amplifier is very high, this circuit has the advantage of drawing very little current from the source.
  - A V to I converter is used for low voltage dc and Vc voltmeter, LED and Zener diode tester.





Equation - 
$$V_o = \left(1 + \frac{R_F}{R}\right) \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}\right)$$

(14) 
$$V_o = V_{o1} + V_{o2} + V_{o3} + V_{o4}$$

$$= -V_1 + V_2 + V_3 + V_4$$

$$= (V_3 + V_4) - (V_1 + V_2)$$

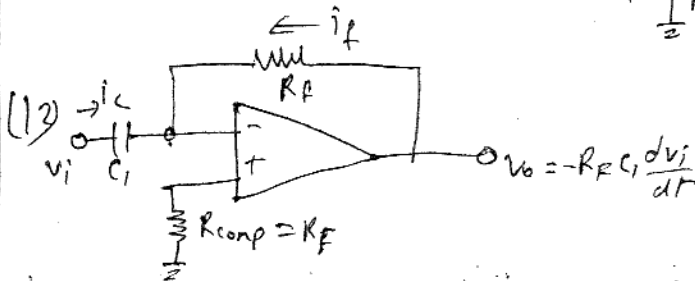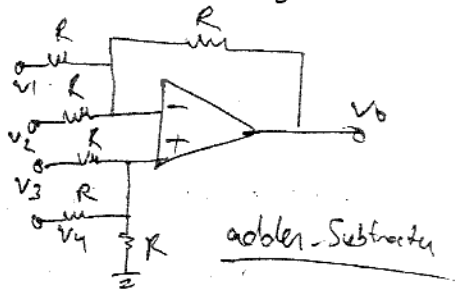

- (8) (i) At high frequency, a differentiator may become unstable and break into oscillation.
- (ii) The input impedance ( $Z_{in}$ ) decrease with the increase in frequency, thereby making the circuit sensitive to high frequency noise.

### (15) Application of linear op-amp

- The output signal varies with the input signal in a linear manner.
- Some of the linear applications - adder, subtractor, voltage to current converter and current to voltage converter, instrumentation amplifier, analog computation, power amplifiers.

### (16) Application of non-linear op-amp

- Rectifier, peak detector, clipper, clamper, sample and hold circuit, log and antilog amplifier, multiplier.
- Non-linear ckt are very useful in industrial instrumentation, communication and general signal processing.

mode  
amplifier  
advantage  
ee  
dc

rectifier

oscillation.  
making  
noise



## Precision Diode Rectifier

Cut in voltage of diode  $\approx 0.6\text{V}$

Ideal diode cannot operate below cut in voltage


But precision diode rectifier can operate below the cut in voltage i.e. in millivolt

To make transistor to an diode

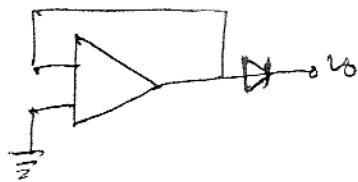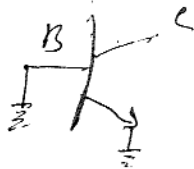

This circuit is called precision diode by connecting a diode in the feedback path of an op-amp & this circuit is capable of rectifying input signal of millivolt.

## Half Wave Rectifier

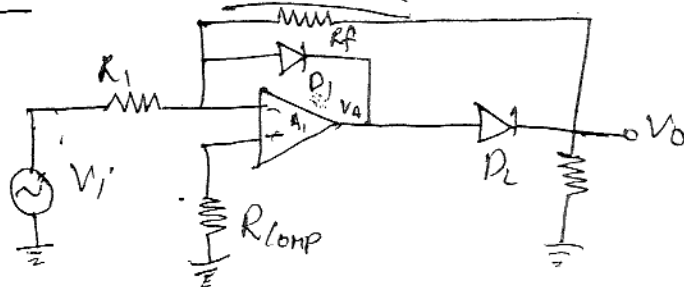

## Analysis

$$V_i > 0V$$

$\rightarrow +ve$

$D_1 \rightarrow \text{conducts}$

$D_2 \rightarrow \text{OFF}$


$$V_o = 0$$

$$V_i < 0V$$


$D_1 \rightarrow \text{OFF}$

$D_2 \rightarrow \text{ON}$

$V_o \rightarrow \text{ON}$

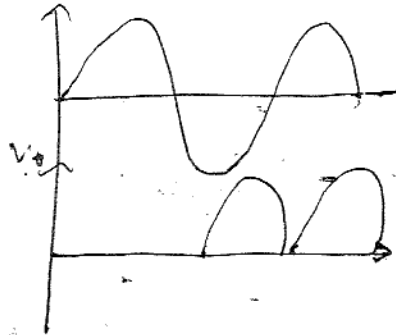

## Full wave rectifier

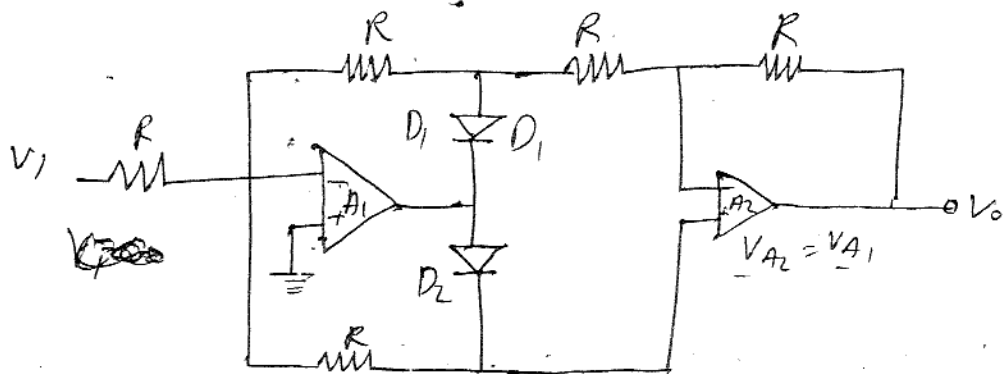

Both op-amp act as inverter so the o/p voltage  $V_o = \text{input voltage}$ .


When

$$V_i > 0$$

$D_1 \rightarrow \text{ON}$

$D_2 \rightarrow \text{OFF}$


$$V_o = V_i$$

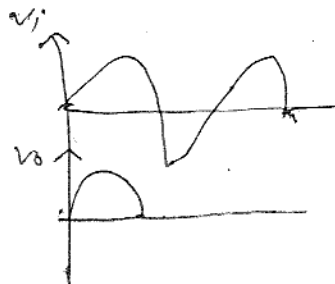

*Practical*

# UNIT-3

## PLL (Phase Locked Loop)

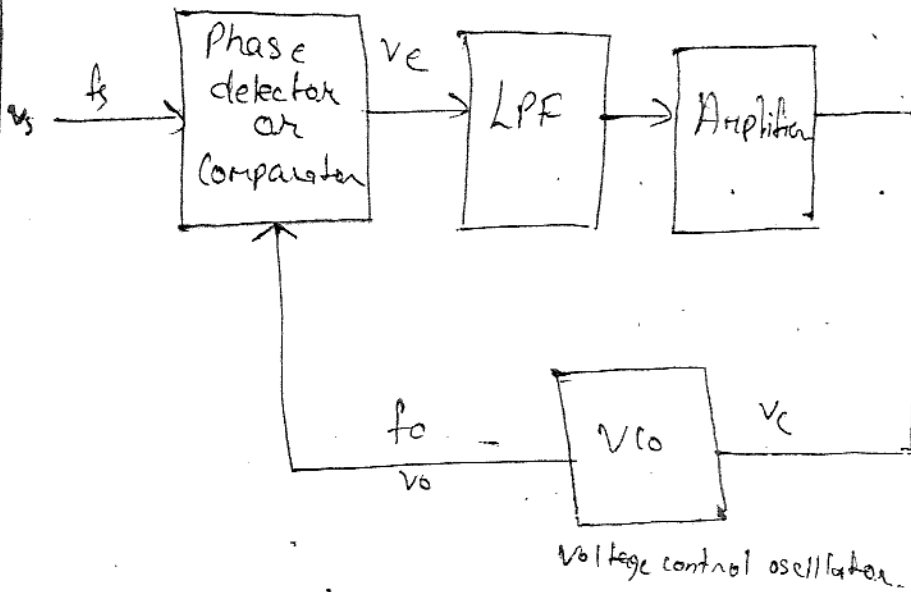

(i) Phase detector / comparator

$$O/P \rightarrow (f_s + f_o) (f_s - f_o)$$

$(f_s + f_o) \rightarrow$  It filters the high frequency

$v_c \rightarrow$  dc voltage

$$[V_{oc} \propto v_c]$$

Basic term in PLL

$\rightarrow$  Lock-in range  $\rightarrow f_s = f_o$

## UNIT-3

(2) <sup>and (1)</sup> The range of frequency over which the PLL can maintain lock with the incoming signal is called the lock range. The lock range is usually expressed as a percentage of  $f_0$ , the VCO frequency.

(4) A parameter of importance for VCO is voltage to frequency conversion factor  $k_v$  and is defined as

$$k_v = \frac{\Delta f_0}{\Delta V_c}$$

Here  $\Delta V_c$  is the modulation voltage required to produce the frequency shift  $\Delta f_0$  for a VCO.

(6) The range of frequencies over which the PLL can acquire lock with an input signal is called the capture range. This parameter is also expressed as percentage of  $f_0$ .



### (7) Application of PLL

- (1) Frequency multiplication/Division.
- (2) Frequency Translation.
- (3) AM detection
- (4) FM demodulation
- (5) FSK demodulator.

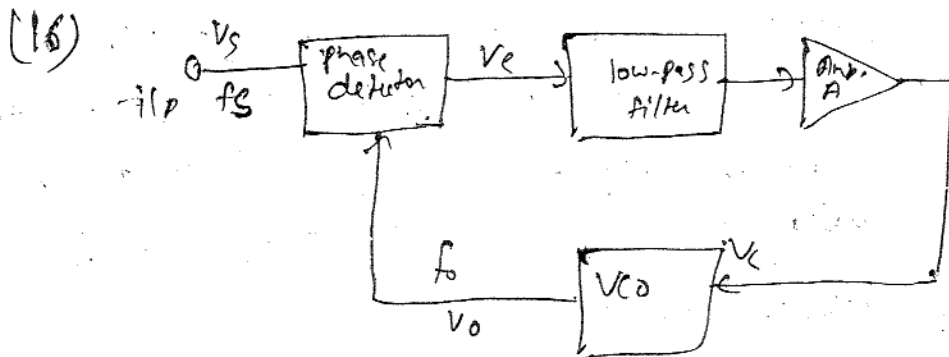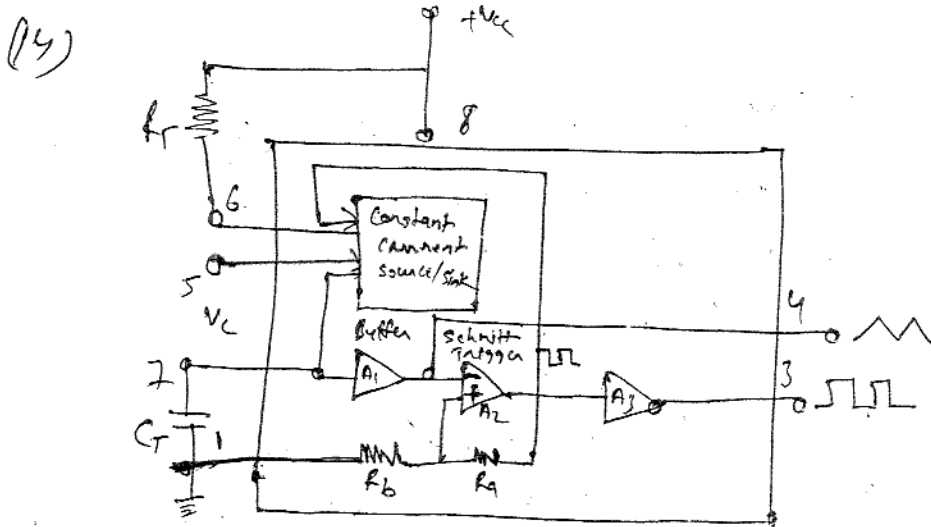(8) <sup>and (2)</sup> The VCO is a free running multivibrator and operates at a set frequency  $f_0$  called free running frequency. This frequency

is determined by an external timing capacitor and an external resistor. It can also be shifted to either side by applying a dc control voltage  $V_c$  to an appropriate terminal of the IC.

The frequency deviation is directly proportional to the dc control voltage and hence it is called a VCO.



(17) three stages


- ① Free running ② capture ③ locked or tracking

(18) Phase detector

- ① Analog P.D ② Digital P.D.



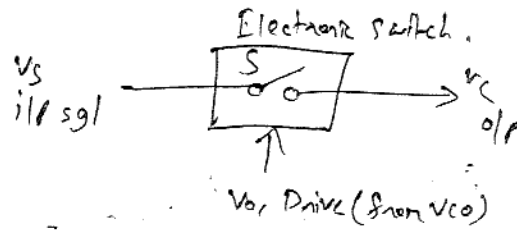(18) Switch type phase detector is used in analog phase detector. An electronic switch  $S$  is opened and closed by signal coming from VCO. The input signal is, therefore chopped at a repetition rate determined by VCO frequency. i.e. the switch is only dependent on VCO.




(20) Two problems

- ① The output voltage  $v_e$  is proportional to the input signal amplitude  $v_s$ . This is undesirable since it makes phase detector gain and the loop gain dependent on the input signal amplitude.
- ② The o/p is proportional to  $\cos \phi$  and not proportional to  $\phi$  making it non-linear.

RC ladder filter


(25)

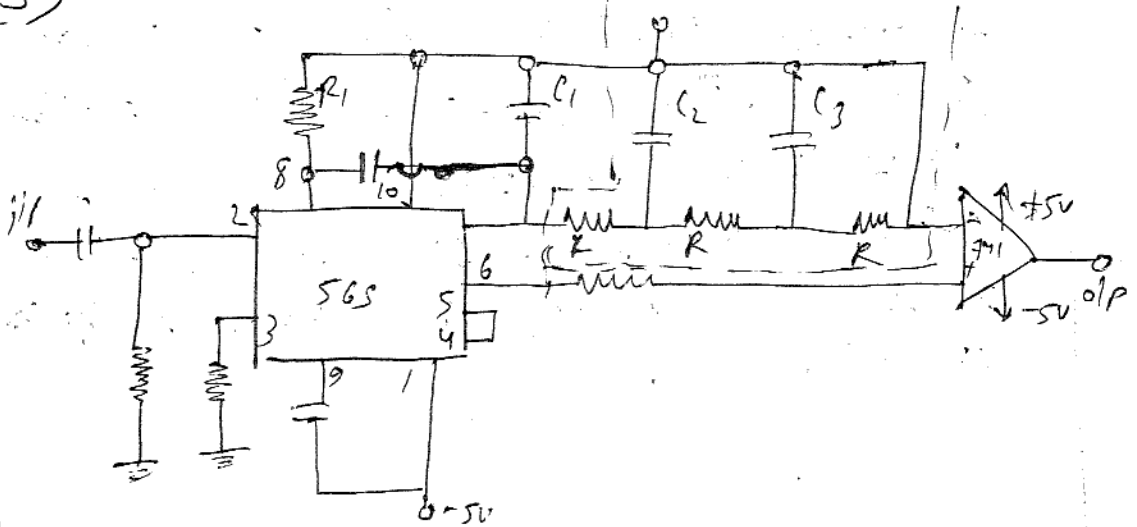

1 or tracking

(23) In order to increase the ability of lock-in range, large capture range is required. A large capture range will make the PLL more susceptible to noise and undesired signal.


(24)

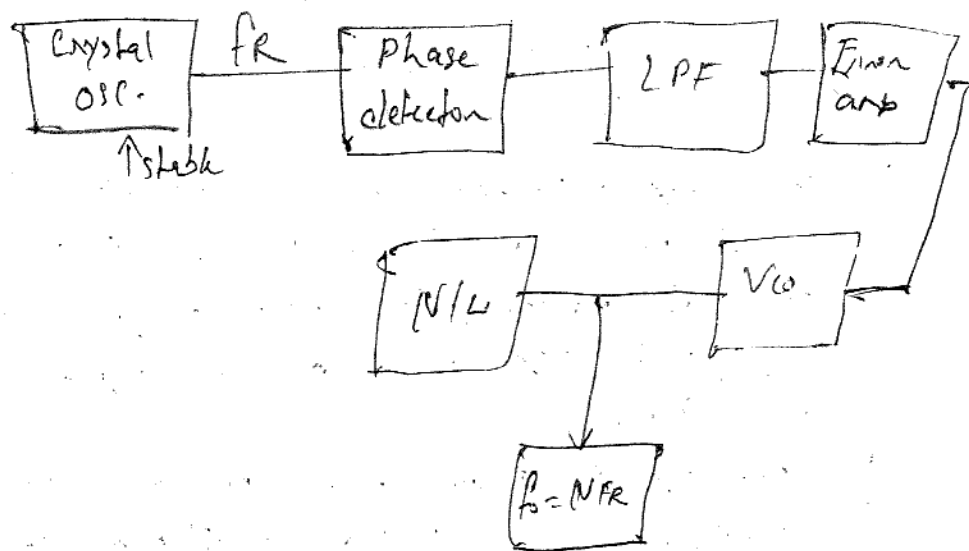

PLL can be used as the base is for frequency synthesizer that can produce precise frequencies from a single oscillator. Under locked condition, the frequency of VCO is  $n$  times the reference frequency. Therefore, it is possible to obtain multiples of reference frequency.
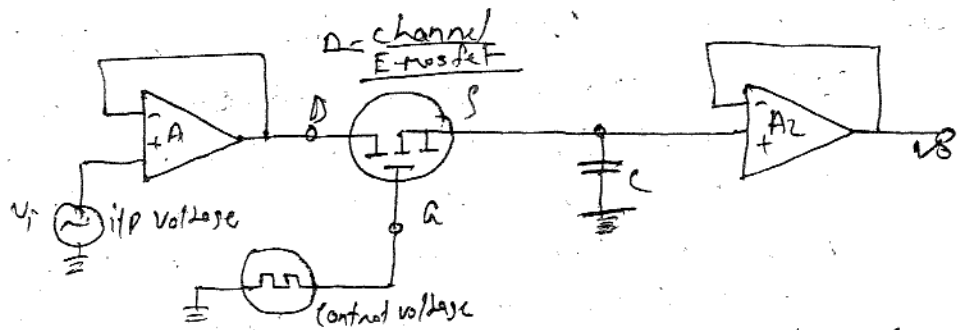
## UNIT-4

- ① A sample and hold circuit samples an input signal and holds on to its last sampled value until the input is sampled again. This type of circuit is very useful in digital interfacing and analog to digital and pulse code modulation systems.



- ② The D/A converter is to convert digital signal into analog signal and hence the function of DAC is exactly opposite to that of ADC. The D/A converter is usually operated at the same frequency as the ADC. The o/p of a D/A converter is commonly a staircase. This staircase like digital o/p is passed through a smoothing filter to reduce the effect of quantization noise.

### classified

- ① Weighted Resistor DAC ② R2R ladder DAC ③ Multiplying DAC's ④ Monolithic DAC

- ③ 8-op-amp comparators are required to build an  $n$  bit flash type A/D converter. A small amount of hysteresis is built into the comparator to resolve any problems that

might occur if both inputs were of equal voltage.

(4) R-2R ladder N/W DAC is better than weighted resistor DAC because a wide range of resistor are required in binary weighted resistor type DAC but in R-2R ladder type DAC only two values of resistor are required.

(5) Monolithic DAC consisting of R-2R ladder, switches and the feedback ~~resistor~~ resistor are available for 8, 10, 12, 14 and 16 bit resolution from various manufacturers. A monolithic DAC is the one whose analog o/p increases for an increase in digital i/p. If a DAC has to be monotonic, the error should be less than  $\pm(1/2)LSB$  at each o/p.

(6) The most important dynamic parameter is the settling time. It represents the time it takes for the o/p to settle within a specified band  $\pm(1/2)LSB$  of its final value following a code change at the input. It depends upon the switching time of the logic circuitry due to internal parasitic capacitance and inductance.

(7) The successive approximation technique uses a very efficient code search strategy to complete n-bit conversion in just n-clock periods. An eight bit converter would.

required eight clock pulses to obtain a digital o/p. circuit uses SAR to find the required value of each bit by trial and error.

(13) Weighted Resistor DAC is the simplest DAC

→ The op-amp is connected in inverting mode, it can also be connected in non-inverting mode.

→ The op-amp is simply working as a current to voltage converter.

→ The polarity of the reference voltage is chosen in accordance with the type of the switch used.

(19) Integrating type converters are

(i) charge balancing ADC.

(ii) Dual slope ADC.

(20) Integrating type ADCs perform conversion in an indirect manner by first changing the analog input signal to a linear function of time or frequency and then to a digital code. The two most widely used integrating type converters are -

(i) charge balancing ADC

(ii) Dual slope ADC.

(7) (a) Digital interfacing (b) Analog to digital

converter circuits (c) Pulse modulating system.

(d) In reset-stabilised op-amp. (e) In analog demultiplexers.

R. (1) The primary use of the sample and hold circuit to hold the sampled analog input voltage constant during conversion time of A/D converter.

(2) In case of multichannel ADCs, synchronization can be achieved by sampling signals from all channels at the same time.

(3) It also reduces the crosstalk in the multiplexer.


### (15) Parameter of ADC

- (1) Resolution, (2) Quantization error
- (3) Conversion time.

### Parameter of DAC


- (1) Resolution, (2) Accuracy (3) Monotonicity
- (4) Conversion time (5) settling time (6) stability.

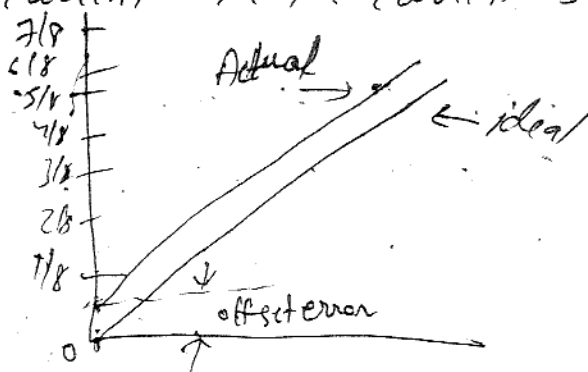(24) Offset error - The offset error is defined as the non zero level of the o/p voltage when all inputs are zero. It is due to the presence of offset voltage in op-amp and leakage current in the current switches.




(25) S  
C  
U  
W  
SP

(21) 9  
an  
94  
or

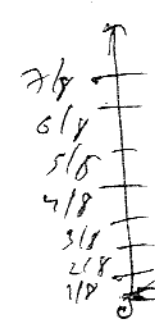

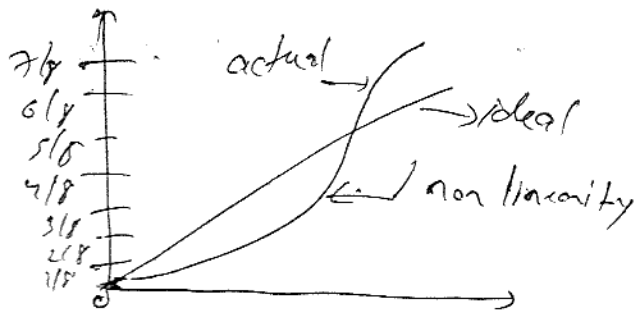Linearity error - The error is defined as the amount by which the actual o/p differs from the ideal straight line o/p. It is mainly due to the errors in the current source resistor value.



(25) Suppose the binary o/p is 011 for all values of  $V_i$  b/w  $V_q$  and  $\frac{1}{2}V$ . There is an unavoidable about the exact value of  $V_i$  when the o/p is 011. This uncertainty is specified as quantization error. Its value is  $\pm \frac{1}{2} \text{LSB}$ .

it is given as,

$$Q.E = \frac{V_{FS}}{(2^n - 1)2}$$

(21) It is a time required for conversion of analog signal into its digital equivalent. It is also called as setting time. It depends on the response time of the switches and the o/p of the amplifier in DAC and in ADC is depends upon the conversion techniques and the propagation delay of the circuit components.

(22) It is a comparison of actual o/p voltage with expected o/p. It is expressed in percentage. Ideally, the accuracy of DAC should be, at worst,  $\pm 1/2$  of its LSB. If the full scale o/p voltage is 10.2V then for an 8-bit DAC accuracy can be given as—

$$\text{Accuracy} = \frac{V_{FS}}{(2^n - 1)2} = \frac{10.2}{255 \times 2} = 2.0 \mu\text{V}$$

### (18) Single slope

- 1) It consists of a ramp generator and BCD or binary counters.
- 2) The analog input voltage  $V_{in}$  is applied to the positive terminal of the comparator.

### Dual slope

- 1) It consists of ramp generator, comparator, binary counter, D latch and reference voltage.
- 2) Ramp generator input is switched b/w the analog input voltage  $V_i$  and a negative reference voltage,  $-V_{REF}$ .



## UNIT-5

(2) The o/p of rectifier and filter circuit consists of ripples. The ripple is equivalent to periodic changes in input voltage. Due to the negative feedback, the ripple voltage gets attenuated by large amount. The factor by which it gets reduced is  $1+AB$ . Mathematically the o/p ripple of a voltage regulator is given by -

$$V_r(\text{out}) = \frac{V_r(\text{in})}{1+AB}$$

(3<sup>or(6)</sup>) Switching regulators operate the power transistor as a high frequency on/off switch, so that the power transistor does not conduct current continuously. This gives improved efficiency over series regulator.

(5) Two packages - (1) 8-pin circular style  
(2) TO-99 can or 8-pin mini DIP  
or as 14-pin DIP.


(7) line regulation - It is defined as the change in the o/p voltage for a given change in the i/p voltage. It is expressed as a percentage of o/p voltage or in millivolts.

(10.) (i) 555 is a monolithic timer device which can be used to produce accurate & highly stable time delay. It can be used to produce time delay ~~of several~~ of  $\mu\text{s}$  to several ms.

(ii) It has 2 basic operating mode - astable & monostable.

(iii) Available in 3 packages - 8 pin metal can, 8-pin mini DIP, 14 pin DIP. 14 pin package is IC 555 & 556.

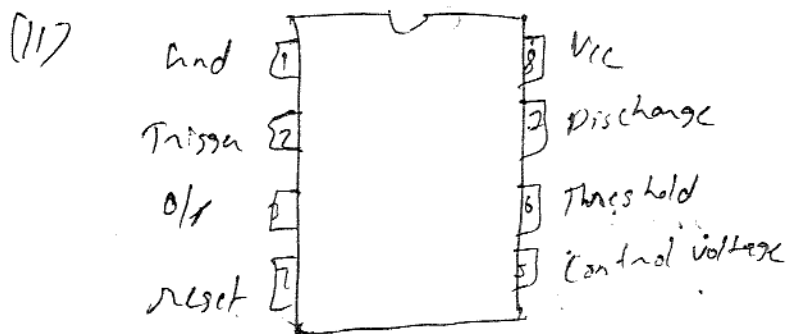(iv) It is compatible with TTL, CMOS & op-amp.



(22) On very high value of resistors can be easily simulated using small value capacitors of the order of  $10\ \mu\text{F}$ .

(i) The switched capacitor filters require no external reactive components like inductors and capacitors.

(ii) Accuracy is very high.

(iii) Overall cost of the system is low.

(iv) Due to good temperature char., the system have good temperature stability.

circuit  
equivalent

Due  
to  
factor  
rather  
regulator

1  
2  
dog  
to  
4/9 to

mini DIP

the change  
in the  
percentage

(23) The power amplifiers are classified by their classes of operation. The class of operation represents the amount of the o/p signal varies over one cycle of operation for a full cycle of input signal.

For an amplifier, a quiescent point (Q point) is fixed by selecting the proper d.c. biasing to the transistor used. The position of the Q point on the load line decides the class of operation.


→ (i) Class A amplifier.

(ii) " B " "

(iii) " C " "

(iv) " AB " "

(24)

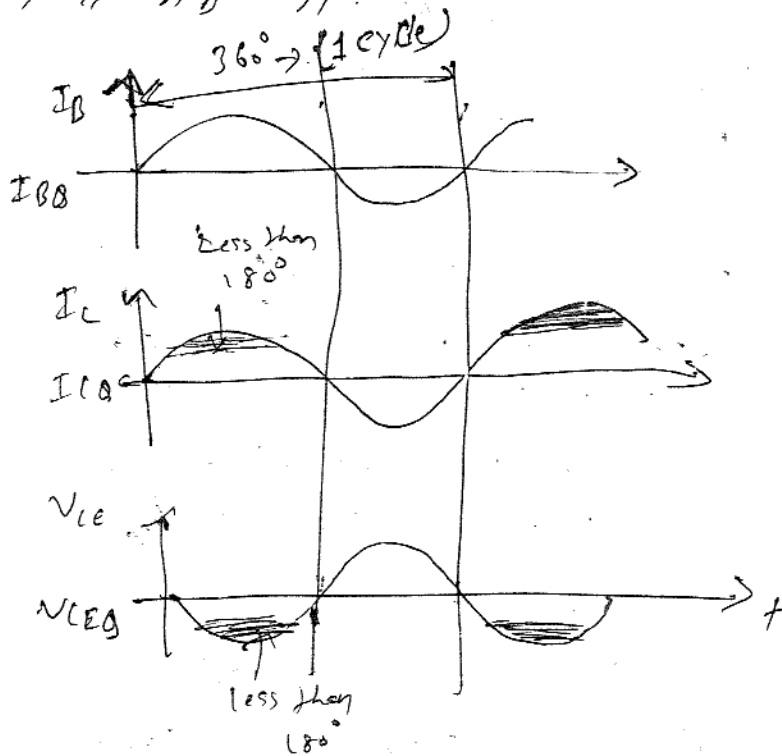

(21)

(18)

(16)

Advant

(1)

(2)

(3)

(4)

(5)

(21) Types of voltage regulator

(1) Series regulator

(2) Switching "

~~(20)~~

(18) Duty cycle - Generally the charging time constant is greater than the discharging time constant hence at the o/p, the waveform is not symmetric. The high o/p remains for longer period than low o/p. The ratio of high o/p period and low o/p period is given by a mathematical parameter called duty cycle. It is defined as the ratio of ON time i.e. high o/p to the total time of one cycle.

$$D = \frac{W}{T}$$

(16) The combined package of a LED and a photodiode is called an optocoupler. It is also called an optoisolator or an optically coupled isolator.

#### Advantage

- (1) The response times of optocouplers is so small that they can be used to transmit data in the megahertz range.
- (2) Capable of wide band signal transmission.
- (3) Easy interfacing with logic device.
- (4) Compact and light weight.
- (5) Much faster than isolation transformers and relays.

classified

the

amount

of cycle

of input

resistor

the

used,

the load

(12) Or FSK Generator

(13) Pulse Position Modulation

(12) An isolation amplifier is an amplifier that offers an ohmic or electrical isolation b/w its input and output terminals. Isolation amplifiers are often used when there is a very large common-mode voltage difference b/w the input and output sides of the device. The isolation in the isolation amplifiers is achieved by use of transformer or by use of optically coupled devices.

ANKUR

202