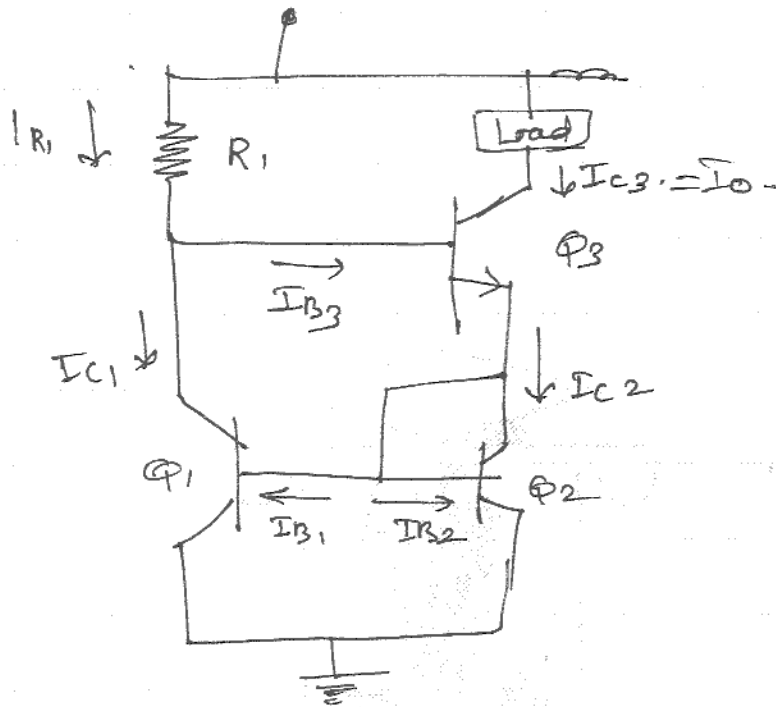


Wilson Current Source:

→ It provides constant current source.



Assumption:

→ All transistors have the same current gain β .

→ Q_1 & Q_2 are matched. so collector current are equal.

$$\therefore I_{C1} = I_{C2} = (I_C) \text{ and } I_{B1} = I_{B2} = I_B \quad \text{--- (1)}$$

Base current of Q_3 is given by

$$I_{B3} = \frac{I_{C3}}{\beta} \quad \text{--- (2)}$$

and Emitter current

$$I_{E3} = \left(\frac{\beta + 1}{\beta} \right) I_{C3} \quad \text{--- (3)}$$

From the cut,

$$I_{E3} = I_{C2} + I_{B1} + I_{B2} \quad \text{--- (4)}$$

Substitute for I_{C2} , I_{B1} from (1) to (4).

$$I_{E3} = I_C + 2I_B \quad \text{--- (5)}$$

$$I_{E3} = I_C \left(1 + \frac{2}{\beta} \right) \quad \text{--- (6)}$$

Substitute for I_{E3} from (3).

$$\left(\frac{\beta+1}{\beta} \right) I_{C3} = I_C \left(1 + \frac{2}{\beta} \right)$$

Rearranging,

$$I_C = \left(\frac{\beta+1}{\beta+2} \right) I_{C3} \quad \text{--- (7)}$$

Current through R_1 is given by,

$$I_{R1} = I_{C1} + I_{B3} \quad \text{--- (8)}$$

$$\text{But } I_{C1} = I_{C2} = I_C$$

Substitute for I_C from (7) in (8) and since,

$$I_{R1} = \left(\frac{\beta+1}{\beta+2} \right) I_{C3} + \frac{I_{C3}}{\beta} \quad \text{--- (9)}$$

$$I_{R1} = \left(\frac{\beta+1}{\beta+2} + \frac{1}{\beta} \right) I_{C3} \quad \text{--- (10)}$$

Finally,

$$I_{C3} = \frac{I_{R1}}{1 + \frac{2}{\beta(\beta+2)}} \quad \text{--- (11)}$$

From the above eqn,

$$\frac{2}{\beta(\beta+2)} \ll 1, \quad I_{C3} \approx I_{R1}$$

And the o/p current,

$$I_{C3} \approx I_{R1} = \frac{V_{CC} - 1.4}{R_1}$$

O/P current depends only on V_{CC} and R_1