

Summary 368
 Review Questions 369
 Problems 369
 Procedure 370

pendix-I—PSPICE Tutorial 373
 References 376
pendix-II—Answer to Selected Problems 377
uggested Readings 379
lex 381

1

INTEGRATED CIRCUIT FABRICATION

1.1 INTRODUCTION

We are going through a period of micro-electronic revolution. For a common person, the role of electronics is limited to audio-visual gadgets like radio and television, but the truth is, today the growth of any industry like communication, control, instrumentation or computer, is dependent upon electronics to a great extent. And integrated circuits are electronics.

The integrated circuit or IC is a miniature, low cost electronic circuit consisting of active and passive components that are irreparably joined together on a single crystal chip of silicon. Most of the components used in ICs are not similar to conventional components in appearance although they perform similar electrical functions. In this chapter, we describe the basic processes used in the fabrication of integrated circuits. Both bipolar and MOS fabrication are treated. These circuits naturally offer a number of distinct advantages over those made by interconnecting discrete components. These may be listed as follows:

1. Miniaturization and hence increased equipment density
2. Cost reduction due to batch processing
3. Increased system reliability due to elimination of soldered joints
4. Improved functional performance (as it is possible to fabricate even complex circuits for better characteristics)
5. Matched devices
6. Increased operating speeds (due to the absence of parasitic capacitance effect)
7. Reduction in power consumption.

1.2 CLASSIFICATION

Integrated circuits offer a wide range of applications and could be broadly classified as:

- Digital ICs
- Linear ICs

Based upon the above requirements, two distinctly different IC technology namely, Monolithic technology and Hybrid technology have been developed.

In monolithic integrated circuits, all circuit components, both active and passive elements and their interconnections are manufactured into or on top of a single chip of silicon. The

monolithic circuit is ideal for applications where identical circuits are required in very large quantities and hence provides lowest per-unit cost and highest order of reliability. In hybrid circuits, separate component parts are attached to a ceramic substrate and interconnected by means of either metallization pattern or wire bonds. This technology is more adaptable to small quantity custom circuits. Based upon the active devices used, ICs can be classified as bipolar (using BJT) and unipolar (using FET). Bipolar and unipolar ICs may further be classified depending upon the isolation technique or type of FET used as in Fig. 1.1.

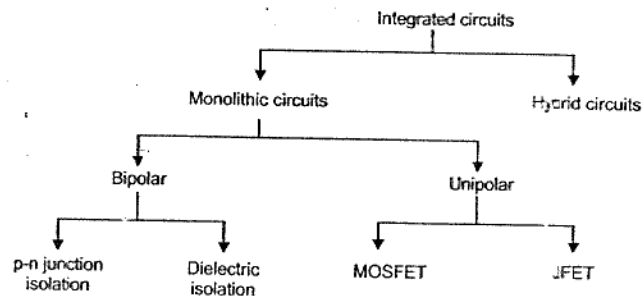


Fig. 1.1 Classification of ICs

1.3 IC CHIP SIZE AND CIRCUIT COMPLEXITY

Up until the-1950s, the electronic device technology was dominated by the vacuum tube. The present-day electronics is the result of the invention of the transistor in 1947. The invention of the transistor by William B. Shockley, Walter H. Brattain and John Bardeen of Bell Telephone Laboratories was followed by the development of the Integrated Circuit (IC). The concept of IC was introduced at the beginning of 1960 by both Texas Instruments and Fairchild Semiconductors. Since that time, the size and complexity of ICs have increased rapidly as shown by the brief chronology.

Invention of transistor (Ge)		1947
Development of Silicon transistor		1955-1959
Silicon Planar Technology	Junction transistor diode	1959
First ICs, Small Scale Integration (SSI)	3 to 30 gates/chip approx. or 100 transistors/chip (Logic gates, Flip-flops)	1960-1965
Medium Scale Integration (MSI)	30 to 300 gates/chip or 100 to 1000 transistors/chip (Counters, Multiplexers, Adders)	1965-1970
Large Scale Integration (LSI)	300 to 3000 gates/chip or 1000-20,000 transistors/chip (8 bit microprocessors, ROM, RAM)	1970-1980
Very Large Scale Integration (VLSI)	More than 3000 gates/chip or 20,000-10,00,000 transistors/chip (16 and 32 bit microprocessors)	1980-1990
Ultra Large Scale Integration (ULSI)	$10^6 - 10^7$ transistors/chip (Special processors, Virtual reality) machines, Smart sensors	1990-2000
Quantum-Scale Integration (QSI)	$> 10^7$ transistors/chip	

Over the years, the device density has increased together with some increase in the chip area. Figure 1.2 (a, b, c) show small (SSI), medium (MSI) and large (LSI or VLSI) IC chip size. The chip areas range from 1 mm^2 (1600 mil²) for the SSI chip to 1 cm^2 (1,60,000 mil²) for the LSI chip.

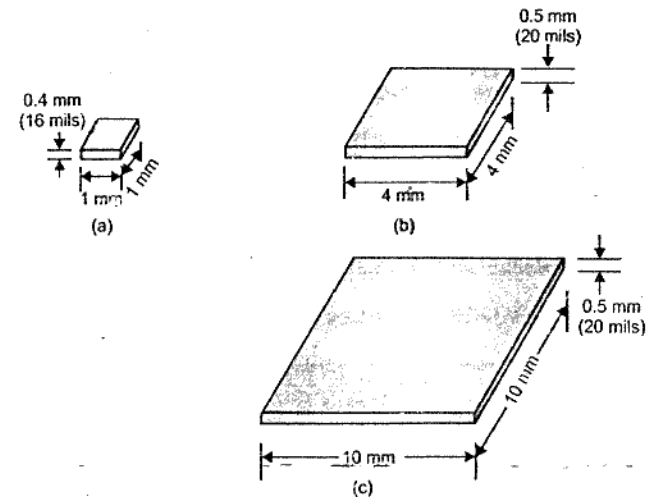


Fig. 1.2 Integrated circuit chips (a) SSI chip (b) MSI chip (c) LSI or VLSI chip

1.4 FUNDAMENTALS OF MONOLITHIC IC TECHNOLOGY

A monolithic circuit, literally speaking, means a circuit fabricated from a single stone or a single crystal. The origin of the word 'monolithic' is from the Greek word *monos* meaning 'single' and *lithos* meaning 'stone'. So monolithic integrated circuits are, in fact, made in a single piece of single crystal silicon.

The most significant advantage of integrated circuit of reducing the cost of production of electronic circuits due to batch production can be easily visualized by a simple example. A standard 10 cm diameter wafer can be divided into approximately 8000 rectangular chips of sides 1 mm. Each IC chip may contain as few as tens of components to several thousand components. And if 10 such wafers are processed in one batch, we can make 80,000 ICs simultaneously. Many chips so produced will be faulty due to imperfection in the manufacturing process. Even if the yield (percentage of fault free chips/wafer) is only 20 per cent, it can be seen that 16,000 good chips are produced in a single batch.

The fabrication of discrete devices such as transistor, diode or an integrated circuit in general can be done by the same technology. The various processes usually take place through a single plane and therefore, the technology is referred to as planar technology. A simple circuit of Fig. 1.3 when fabricated by silicon planar technology will have the cross-sectional view shown in Fig. 1.4.

$$1 \text{ mil} = 0.001 \text{ in} = 25.4 \mu\text{m} = 0.0254 \text{ mm}$$

 


Fig. 1.3 A typical circuit

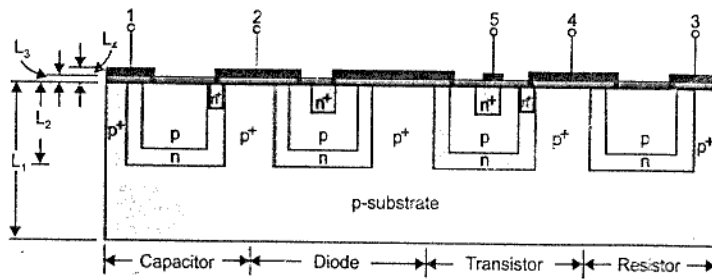


Fig. 1.4 Complete cross-sectional view of the circuit in Fig. 1.3 when transformed into monolithic form

An IC in general, consists of four distinct layers, as follows:

- Layer No. 1** is a *p*-type silicon substrate upon which the integrated circuit is fabricated. (~ 400 μm)
- Layer No. 2** is a thin *n*-type material grown as a single crystal extension of the substrate using epitaxial deposition technique. All active and passive components are fabricated within this layer using selective diffusion of impurities. (~ 5–25 μm)
- Layer No. 3** is a very thin SiO_2 layer for preventing diffusion of impurities wherever not required using photolithographic technique. (0.02–2 μm)
- Layer No. 4** is an aluminium layer used for obtaining interconnection between components. (~ 1 μm)

It may be pointed out that the drawings showing the cross-sectional view in this chapter are never scale drawings, but are distorted for the particular emphasis required.

1.5 BASIC PLANAR PROCESSES

The basic processes used to fabricate ICs using silicon planar technology can be categorised as follows:

1. Silicon wafer (substrate) preparation
2. Epitaxial growth
3. Oxidation
4. Photolithography
5. Diffusion
6. Ion implantation
7. Isolation techniques

8. Metallization
 9. Assembly processing and packaging
- We shall now describe these processes in detail.

1.5.1 Silicon Wafer Preparation

The following steps are used in the preparation of Si-wafers:

1. Crystal growth and doping
2. Ingot trimming and grinding
3. Ingot slicing
4. Wafer polishing and etching
5. Wafer cleaning

The starting material for crystal growth is highly purified (99.99999) polycrystalline silicon. The Czochralski crystal growth process is the most often used for producing single crystal silicon ingots. The polycrystalline silicon together with an appropriate amount of dopant is put in a quartz crucible and is then placed in a furnace. The material is then heated to a temperature in excess of the silicon melting point of 1420°C . A small single crystal rod of silicon called a *seed crystal* is then dipped into the silicon-melt and slowly pulled out as shown in Fig. 1.5. As the seed crystal is pulled out of the melt, it brings with it a solidified mass of silicon with the same crystalline structure as that of seed crystal. During the crystal pulling process, the seed crystal and the crucible are rotated in opposite directions in order to produce ingots of circular cross-section. The diameter of the ingot is controlled by the pulling rate and the melt temperature. Ingot diameter of about 10 to 15 cm is common and ingot length is generally of the order of 100 cm.

Next the top and bottom portions of the ingot are cut off and the ingot surface is ground to produce an exact diameter ($D = 10, 12.5, 15$ cm). The ingot is also ground flat slightly along the length to get a reference plane. The ingot is then sliced using a stainless steel saw blade with industrial diamonds embedded into the inner diameter cutting edge. This produces circular wafers or slices as shown in Fig. 1.6. The orientation flat portion serves as a useful reference plane for the various processes described later. The silicon wafers so obtained have very rough surface due to slicing operation. These wafers undergo a number of polishing steps to produce a flat surface. Then one side of the wafer is given a final mirror-smooth highly polished finish, whereas the other

 
 


Fig. 1.5 Czochralski crystal growth

Fig. 1.6 Silicon wafer, $D = 10, 12.5, 15$ cm showing flat orientation


side is simply lapped on an abrasive lapping machine to obtain an acceptable degree of flatness. Finally, the wafers are thoroughly rinsed and dried. A raw cut slice of thickness 23–40 mils produces wafers of 16–32 mils thickness after all the polishing steps.

These silicon wafers will contain several hundred rectangular chips, each one containing a complete integrated circuit. After all the IC fabrication processes are complete, these wafers are sawed into 100 to 8000 rectangular chips having side of 10 to 1 mm. Each chip is a single IC and may contain hundreds of components. The wafer thickness therefore is so chosen that it is possible to separate chips without breaking and at the same time, it gives sufficient mechanical strength to the IC chip.

 1.5.2 Epitaxial Growth

The word epitaxy is derived from Greek word *epi* meaning 'upon' and the past tense of the word *teino* meaning 'arranged'. So, one could describe epitaxy as, arranging atoms in single crystal fashion upon a single crystal substrate, so that the resulting layer is an extension of the substrate crystal structure.

The basic chemical reaction used for the epitaxial growth of pure silicon is the hydrogen reduction of silicon tetrachloride.



Mostly, epitaxial films with specific impurity concentration are required. This is accomplished by introducing phosphine (PH_3) for the *n*-type and bi-borane (B_2H_6) for *p*-type doping into the silicon-tetrachloride hydrogen gas stream.

The process is carried out in a reaction chamber consisting of a long cylindrical quartz tube encircled by an RF induction coil. Figure 1.7 shows the diagrammatic representation of the system used. The silicon wafers are placed on a rectangular graphite rod called a *boat*. This boat is then placed in the reaction chamber where the graphite is heated inductively to a temperature 1200°C. The various gases required for the growth of desired epitaxial layers are introduced into the system through a control console.

 


Fig. 1.7 A diagrammatic representation of a system for growing silicon epitaxial films

1.5.3 Oxidation

SiO_2 has the property of preventing the diffusion of almost all impurities through it. It serves two very important purposes.

1. SiO_2 is an extremely hard protective coating and is unaffected by almost all reagents except hydrofluoric acid. Thus, it stands against any contamination.
2. By selective etching SiO_2 , diffusion of impurities through carefully defined windows in the SiO_2 can be accomplished to fabricate various components.

The silicon wafers are stacked up in a quartz boat and then inserted into quartz furnace tube. The Si-wafers are raised to a high temperature in the range of 950 to 1115°C and at the same time, exposed to a gas containing O_2 or H_2O or both. The chemical reaction is



This oxidation process is called *thermal oxidation* because high temperature is used to grow the oxide layer. The thickness of the film is governed by time, temperature and the moisture content. The thickness of oxide layer is usually in the order of 0.02 to 2 μm .

1.5.4 Photolithography

With the help of photolithography, it has become possible to produce microscopically small circuit and device patterns on Si-wafers. As many as 10,000 transistors can be fabricated on a 1 cm \times 1 cm chip. The conventional photolithographic process uses ultraviolet light exposure and device dimension or line width as small as 2 μm can be obtained. However, with the advent of latest technology using X-ray or electron beam lithographic techniques, it has become possible to produce device dimension down to sub-micron range (<1 μm).

Photolithography involves two processes, namely:

Making of a photographic mask

Photo etching

The making of a photographic mask involves the following sequence of operations—first the preparation of initial artwork and secondly, its reduction. The initial layout or artwork of an IC is normally done at a scale several hundred times larger than the final dimensions of the finished monolithic circuit. This is because, for a tiny chip, larger the artwork, more accurate is the final mask. For example, it is often required to make an opening of width about 1 mil (25 μm). Obviously, this cannot be managed by any draftsman even with his thinnest of sketch pens. So the drawings are made magnified and often by a factor of 500. With this magnification, it is easy to see that a width of one mil is magnified to a width of 500 mils, that is, about 1.2 cm. Therefore, for a finished monolithic chip of area 50 mils \times 50 mils, the artwork will be made on an area of about 60 cm \times 60 cm.

This initial layout is then decomposed into several mask layers, each corresponding to a process step in the fabrication schedule, e.g., a mask for base diffusion, another for collector diffusion, another for metallization and so on.

For photographic purpose, artwork should not contain any line drawings but must be of alternate clear and opaque regions. This is accomplished by the use of clear Mylar coated with a sheet of red photographically opaque mylar (trade name-Rubylith). The red layer can be easily peeled off thus exposing clear areas with a knife edge from the regions where impurities have to be diffused. The artwork is usually produced on a precision drafting machine, known as *coordinatograph*. The coordinatograph has a cutting head that can be

positioned accurately and moved along two perpendicular axes. The coordinatograph outlines the pattern cutting through the red mylar without damaging the clear layer underneath.

This rubylith pattern of individual mask is photographed and then reduced in steps by a factor of 5 or 10 several times to finally obtain the exact image size. The final image also must be repeated many times in a matrix array, so that many ICs will be produced in one process. The photo repeating is done with a step and repeat camera. This is an imaging device with a photographic plate on a movable platform. Between exposure, the plate is moved in equal steps so that successive images form in an array. When the exposed plate is developed, it becomes a master mask. The masks, actually used in IC processing are made by contact printing from the master. These working masks wear out with use and are replaced as required.

Photo-etching is used for the removal of SiO_2 from desired regions so that the desired impurities can be diffused. The wafer is coated with a film of photosensitive emulsion (Kodak Photoresist KPR). The thickness of the film is in the range of 5000–10000 Å as shown in Fig. 1.8 (a). The mask negative of the desired pattern) as prepared by steps described earlier is placed over the photoresist coated wafer as shown in Fig. 1.8 (b). This is now exposed to ultraviolet light, so that KPR becomes polymerized beneath the transparent regions of the mask. The mask is then removed and the wafer is developed using a chemical (trichloroethylene) which dissolves the unexposed/unpolymerized regions on the photoresist and leaves the pattern as shown in Fig. 1.8 (c). The polymerized photoresist is next fixed or cured, so that it becomes immune to certain chemicals called *etchants* used in subsequent processing steps. The chip is immersed in the etching solution of hydrofluoric acid, which removes the SiO_2 from the areas which are not protected by KPR as shown in Fig. 1.8 (d). After diffusion of impurities, the photoresist is removed with a chemical solvent (hot H_2SO_4) and mechanical abrasion.

 


Fig. 1.8 Various steps for photo-etching

The etching process described is a wet etching process and the chemical reagents used are in liquid form. A new process used these days is a dry etching process called *plasma etching*. A major advantage of the dry etching process is that it is possible to achieve smaller line openings ($\leq 1 \mu\text{m}$) compared to wet process. Complete description of the plasma etching process is beyond the scope of this book.

X-Ray and Electron Beam Lithography

With conventional ultraviolet (UV) photolithography process in which the UV wavelengths used are in the range, 0.3 to 0.4 μm , the minimum device dimensions or line widths are

limited by diffraction effects to around five wavelengths or about 2 μm . This is what puts an upper limit on the IC device density using UV photolithography.

With the advent of X-ray and electron beam lithography techniques, it has become possible to produce device dimensions down to submicron range ($< 1 \mu\text{m}$). This is due to much shorter wavelengths involved. With these techniques, MOSFET with gate length as small as 0.25 μm have been made. The cost of X-ray or electron beam equipment is very high and the exposure time is very much longer than UV photolithography. So this becomes a very expensive process and is used only when very small device dimensions ($\leq 1 \mu\text{m}$) are needed.

1.5.5 Diffusion

Another important process in the fabrication of monolithic ICs is the diffusion of impurities in the silicon chip. This uses a high temperature furnace having a flat temperature profile over a useful length (about 20" length). A quartz boat containing about 20 cleaned wafers is pushed into the hot zone with temperature maintained at about a 1000°C. Impurities to be diffused are rarely used in their elemental forms. Normally, compounds such as B_2O_3 (Boron oxide), BCl_3 (Boron chloride) are used for Boron and P_2O_5 (Phosphorous pentoxide) and POCl_3 (Phosphorous oxychloride) are used as sources of Phosphorous. A carrier gas, such as dry oxygen or nitrogen is normally used for sweeping the impurity to the high temperature zone. The depth of diffusion depends upon the time of diffusion which normally extends to 2 hours.

The diffusion of impurities normally takes place both laterally as well as vertically. Therefore, the actual junction profiles will be curved as shown in Fig. 1.9. However, for the sake of simplicity, lateral diffusion will be omitted in all the drawings.

 


Fig. 1.9 The cross-section of an npn transistor showing curved junction profiles as a result of lateral diffusion

1.5.6 Ion Implantation

Ion implantation is the other technique used to introduce impurities into a silicon wafer. In this process, silicon wafers are placed in a vacuum chamber and are scanned by a beam of high-energy dopant ions (borons for p-type and phosphorus for n-type) as shown in Fig. 1.10. These ions are accelerated by energies between 20 kV to 250 kV. As the ions strike the silicon wafers, they penetrate some small distance into the wafer. The depth of penetration of any particular type of ion increases with increasing accelerating voltage. Ion implantation technique has two important advantages.

1. It is performed at low temperatures. Therefore, previously diffused regions have a lesser tendency for lateral spreading.

2. In diffusion process, temperature has to be controlled over a large area inside the oven, whereas in ion implantation technique, accelerating potential and the beam current are electrically controlled from outside.

 


Fig. 1.10 Ion implantation system

5.7 Isolation Techniques

Since a number of components are fabricated on the same IC chip, it becomes necessary to provide electrical isolation between different components and interconnections. Various types of isolation techniques have been developed. However, we shall discuss here only two commonly used techniques, namely:

- p-n* junction isolation
- Dielectric isolation

p-n Junction Isolation

In this isolation technique, p^+ type impurities are selectively diffused into the n -type epitaxial layer so as to reach p -type substrate as shown in Fig. 1.11 (a). This produces islands surrounded by p -type moats. It can be seen that these regions are separated by two back-to-back $p-n$ junction diodes. If the p -type substrate material is held at the most negative potential in the circuit, the diodes will be reverse biased providing electric isolation between these islands. The different components are fabricated in these isolation islands. The concentration of the

 


Fig. 1.11 (a) *p-n* junction isolation

acceptor atoms in the region between isolation islands is usually kept much higher (p^+) than the p -type substrate. This prevents the depletion region of the reverse biased diode from penetrating more into p^+ region and possibly connecting the isolation islands.

There is, however, one undesirable by-product of this isolation process. It is the presence of a transition capacitance at the isolating $p-n$ junctions, resulting in an inevitable capacitor coupling between the components and the substrate. These parasitic capacitances limit the performance of the circuit at high frequencies. But being economical, this technique is commonly used for general purpose ICs.

Dielectric Isolation

Here a layer of solid dielectric such as silicon dioxide or ruby completely surrounds each component, thereby producing isolation, both electrical and physical. This isolating dielectric layer is thick enough so that its associated capacitance is negligible. Also, it is possible to fabricate both *pnp* and *nnp* transistor within the same silicon substrate. Since this method requires additional fabrication steps, it becomes more expensive. The technique is mostly used for fabricating professional grade ICs required for specialised applications viz, aerospace and military, where higher cost is justified by superior performance. Figure 1.11 (b) shows such a structure.

 


Fig. 1.11 (b) Dielectric isolation

1.5.8 Metallization

The purpose of this process is to produce a thin metal film layer that will serve to make interconnections of the various components on the chip. Aluminium is usually used for the metallization of most ICs as it offers several advantages.

1. It is relatively a good conductor.
2. It is easy to deposit aluminium films using vacuum deposition.
3. Aluminium makes good mechanical bonds with silicon.
4. Aluminium forms low resistance, non-rectifying (i.e., ohmic) contact with p -type silicon and the heavily doped n -type silicon.

The film thickness of about $1 \mu\text{m}$ and conduction width of about 2 to $25 \mu\text{m}$ are commonly used. The process takes place in a vacuum evaporation chamber as shown in Fig. 1.12. The pressure in the chamber is reduced to the range of 10^{-5} to 10^{-7} torr (1 atmosphere = 760 torr = 760 mm Hg). The material to be evaporated is placed in a resistance heated tungsten coil or basket. A very high power density electron beam is focussed at the surface of the material to be evaporated. This heats up the material to very high temperature and

it starts vaporising. These vapours travel in straight line paths. The evaporated molecules hit the substrate and condense there to form a thin film coating.

After the thin film metallization is done, the film is patterned to produce the required interconnections and bonding pad configuration. This is done by photolithographic process and aluminium is etched away from unwanted places by using etchants like phosphoric acid (H_3PO_4).

1.5.9 Assembly Processing and Packaging

Each of the wafer processed contains several hundred chips, each being a complete circuit. So, these chips must be separated and individually packaged. A common method called *scribing and cleaving* used for separation makes use of a diamond tipped tool to cut lines into the surface of the wafer along the rectangular grid separating the individual chips. Then the wafer is fractured along the scribe lines and the individual chips are physically separated. Each chip is then mounted on a ceramic wafer and attached to a suitable package.

There are three different package configurations available:

1. Metal can package
2. Ceramic flat package
3. Dual-in-line (ceramic or plastic type) package.

The metal can packages are available in 8, 10 or 12 leads, whereas the flat or dual-in-line package is commonly available in 8, 14 or 16 leads, but even 24 or 36 or 42 leads are also available for special circuits. Ceramic packages, whether of flat type or dual-in-line are costly due to fabrication process, but have the advantage of best hermetic sealing. Most of the general

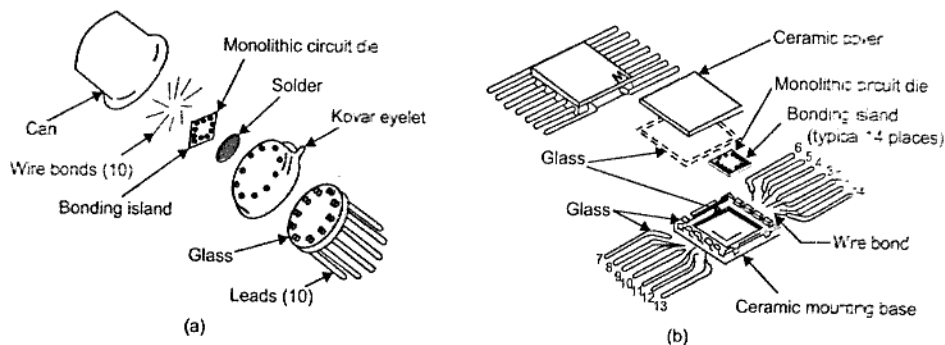


Fig. 1.13 Exploded view of (a) TO-5 metal can package (b) 14-lead version of the flat package, showing the various components as well as the completed flat package

 


Fig. 1.12 Vacuum evaporation for metallization

purpose ICs are dual-in-line plastic packages due to economy. Figures 1.13 (a) and (b) shows the exploded view of TO-5 metal can and flat package respectively.

1.6 FABRICATION OF A TYPICAL CIRCUIT

We shall here show the various steps utilized in converting the circuit of Fig. 1.3 into the monolithic IC of Fig. 1.4.

Step-1: Wafer Preparation

Refer Fig. 1.14 (a). The starting material called the substrate is a *p*-type silicon wafer prepared as discussed in Sec. 1.5.1. The wafers are usually of 10-cm diameter and 0.4 mm ($\sim 400 \mu\text{m}$) thickness. The resistivity is approximately $10 \Omega\text{-cm}$ corresponding to concentration of acceptor atom, $N_A = 1.4 \times 10^{15} \text{ atoms/cm}^3$.

Step-2: Epitaxial Growth

An *n*-type epitaxial film ($5\text{--}25 \mu\text{m}$) is grown on the *p*-type substrate as shown in Fig. 1.14 (b). This ultimately becomes the collector region of the transistor, or an element of the diode and diffused capacitor associated with the circuit. So, in general it can be said that all active and passive components are fabricated within this layer. The resistivity of *n*-epitaxial layer is of the order of 0.1 to $0.5 \Omega\text{-cm}$.

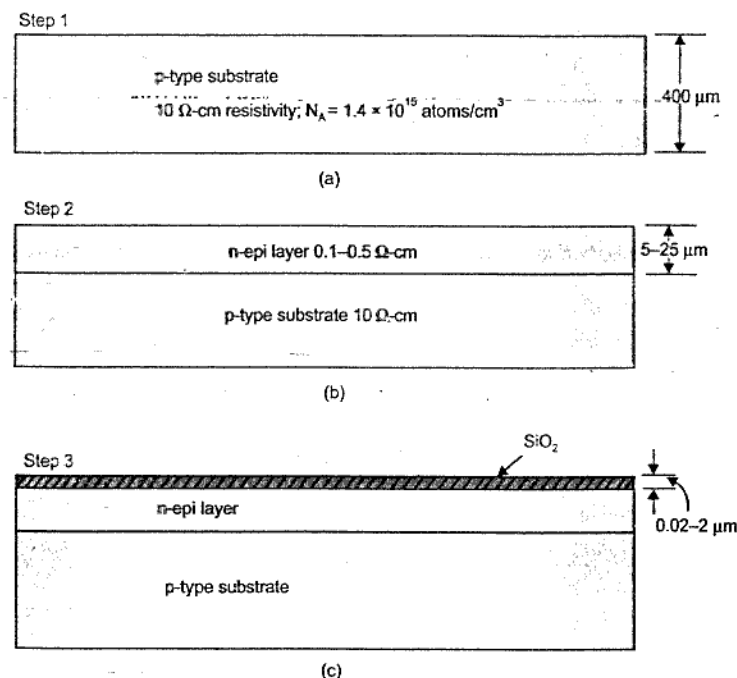


Fig. 1.14 Contd.

 


Fig. 1.14 (a-e) Steps in the fabrication of the circuit shown in Fig. 1.3

Step 3: Oxidation

Refer Fig. 1.14 (c). A SiO_2 layer of thickness of the order of 0.02 to 2 μm is grown on the n -epitaxial layer.

Step 4: Isolation Diffusion

In the circuit of Fig. 1.3, four components have to be fabricated, so we require four islands which are isolated. For this, SiO_2 is removed from five different places using photolithographic technique. Refer Fig. 1.14 (d). The wafer is next subjected to heavy p -type diffusion for a long time interval so that p -type impurities penetrate the n -type epitaxial layer and reach the p -type substrate. The area under the SiO_2 are n -type islands that are completely surrounded by p -type moats. As long as the pn junctions between the isolation islands are held at reverse bias, that is, the p -type substrate is held at a negative potential with respect to the n -type isolation islands, these regions are electrically isolated from each other by two back-to-back diodes, providing the desired isolation.

The concentration of acceptor atoms ($N_A = 5 \times 10^{20} \text{ cm}^{-3}$) in the region between isolation islands is generally kept higher than p -type substrate for which $N_A = 1.4 \times 10^{16} \text{ atoms/cm}^3$. This ensures that the depletion region of the reverse biased diode will not extend into p^+ region to the extent of electrically connecting the two isolation islands. There will, however, be a significant amount of barrier or transition capacitance present as a by product of the isolation diffusion. The top view of the isolation islands is depicted in Fig. 1.14 (e).

Step 5: Base Diffusion

Refer to Fig. 1.14 (f). A new layer of SiO_2 is grown over the entire wafer and a new pattern of openings is formed using photolithographic technique. Now, p -type impurities, such as

boron, are diffused through the openings into the islands of n -type epitaxial silicon. The depth of this diffusion must be controlled so that it does not penetrate through n -layer into the substrate. This diffusion is utilized to form base region, of the transistor, resistor, the anode of the diode and junction capacitor.

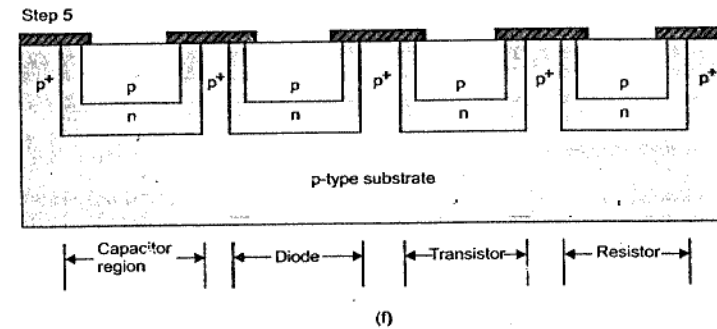


Fig. 1.14 (f)

Step 6: Emitter Diffusion

Refer to Fig. 1.14 (g). A new layer of SiO_2 is again grown over the entire wafer and selectively etched to open a new set of windows and n -type impurity (phosphorus) is diffused through them. This forms transistor emitter and cathode region of diode.

Windows (W_1 , W_2 etc.) are also etched into n -region where contact is to be made to the n -type layer. Heavy concentration of phosphorus (n^+) is diffused into these regions simultaneously with the emitter diffusion. The reason for using heavily-doped n -regions can be explained as follows:

Aluminium, normally used for making interconnections, is a p -type impurity in silicon, and can produce an unwanted rectifying contact with the lightly-doped n -material. However, heavy concentration of phosphorus ($\sim 2 \times 10^{20} \text{ cm}^{-3}$) doping causes a high degree of damage to the Si-lattice at the surface, thus effectively making it semi-metallic. This n^+ layer thus makes a good ohmic contact with the Al-layer. The top view corresponding to Fig. 1.14 (g) is shown in Fig. 1.14 (h).

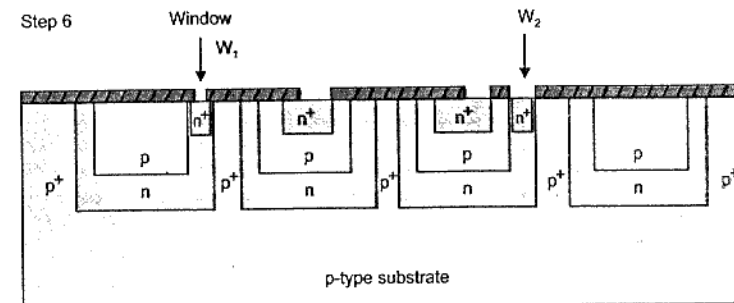


Fig. 1.14 (g)


 


Fig. 1.14 (h)


Step 7: Aluminium Metallization

Now the IC chip is complete with all the active and passive devices and only interconnections between the various components have to be made in accordance with the circuit in Fig. 1.3. The chip is further subjected to the process of the formation of a new SiO_2 layer and masked etching to open a new set of windows at the points where contacts have to be made.

Now, a thin even coating of aluminium is vacuum-deposited over the entire surface of the wafer. The interconnection pattern between the components is then formed by photo-resist techniques. The undesired aluminium areas are etched away leaving a pattern of interconnections between transistor, resistor, diode and capacitor as shown by the cross-sectional and top view in Fig. 1.14 (i) and Fig. 1.14 (j), respectively.

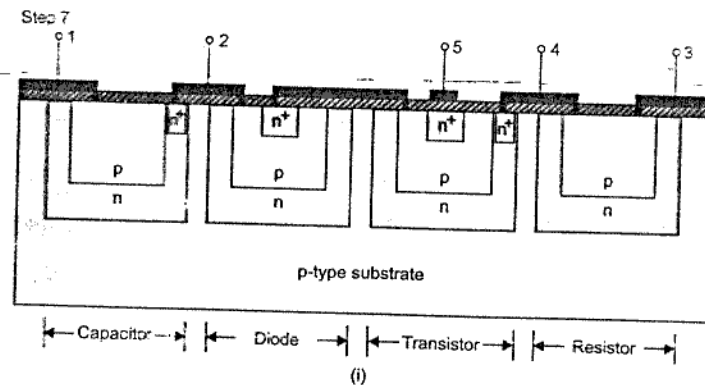

(i)

 

(j)

Fig. 1.14 (i, j)

17 ACTIVE AND PASSIVE COMPONENTS OF ICs

Now the reader is familiar with the basic technology involved in the fabrication of ICs. More light will be thrown on the various devices which constitute a monolithic circuit. These include:

1. Transistors
2. Diodes
3. Resistors
4. Capacitors
5. Inductors.

1.7.1 Monolithic Transistors

Figure 1.15 (a) shows the cross-sectional view of an IC transistor. Let us compare it with the conventional discrete transistor also fabricated using planar technology and shown in Fig. 1.15 (b).

 


Fig. 1.15 Cross-section of (a) Monolithic integrated circuit transistor, (b) A discrete planar epitaxial transistor

The most striking feature in the two structures is that in the IC transistor, collector contact is on the top whereas in the discrete transistor it is at the bottom. In IC transistor collector contact has to be taken from the top because collector is isolated from the substrate and the next isolation island by reverse-biased diodes. This structural difference makes integrated transistor poorer than discrete transistor in two ways:

- (i) Collector contact being at the top increases the collector current path, thereby increasing the collector series resistance and hence $V_{CE(sat)}$ of the device.
- (ii) In the integrated transistor, additional parasitic capacitance appears between collector and substrate is held at negative potential. However, these shortcomings of the integrated transistors can be overlooked on account of a number of advantages inherent in integrated technology. In this, circuit performance is highly improved as matched transistors can be obtained for example to be used in difference amplifiers. Integrated transistors spaced within 30 mils can have V_{BE} matching better than 5 mV and a match of ± 10 per cent.

Use of 'Buried n^+ Layer' to Reduce Collector Series Resistance

The higher collector series resistance of an integrated transistor can be easily reduced by a process known as 'buried layer' shown in Fig. 1.16. In this, a heavily-doped n^+ region is sandwiched between the n -type epitaxial collector and p -type substrate. This buried region provides a low resistivity current path from the active collector region (n -type layer) to the collector contact (n^+ contact layer). In effect, the n^+ layer shunts the n -layer of collector region with respect to the flow of the current thus effectively reducing the collector resistance.

 


Fig. 1.16 Use of "buried n^+ layer" to reduce collector series resistance

pnp Transistor

pnp transistors in integrated circuits are fabricated in one of the following three ways:

- (i) Vertical or substrate pnp (ii) Lateral pnp (iii) Triple diffused pnp.

Vertical pnp Transistor

The p -type substrate itself is used as p -collector, n -epitaxial layer for the base and the next p -diffusion (base in n p n structure) as the emitter region. This type of pnp transistor has the limitation that collector has to be held at a fixed negative potential, as substrate is to be held at the most negative potential in the circuit for providing good isolation.

Lateral pnp Transistor

This is the most common form of an integrated pnp transistor which can be fabricated simultaneously with the npn transistor and requires no additional masking or diffusion step. The n -type epi layer is used as the base of the pnp transistor. During the p -type base diffusion for the npn transistor, two adjacent p -regions are diffused to form emitter and collector regions of the lateral pnp transistor as shown in Fig. 1.17.

 


Fig. 1.17 A pnp lateral transistor

Triple Diffused pnp Transistor

To a standard npn transistor, an extra p -type diffusion is added after the n -diffusion, it is quite possible to obtain a pnp transistor and is known as triple diffused pnp transistor. However, the usefulness of such a structure is limited due to additional fabrication steps required and serious design considerations.

Comparison of npn and pnp IC Transistors

In general, npn transistors are preferred in integrated circuits compared to pnp transistors due to a variety of reasons.

1. A vertical pnp transistor has the disadvantage that its collector has to be held at a fixed negative voltage.
2. Lateral pnp transistor has inferior characteristic as the base width is usually larger controlled by lateral diffusion of p -type impurities and photographic limitations during mask making and alignment. Therefore, pnp transistor normally gives current gain as low as 1.5 to 30 compared to 50 to 300 for the npn transistor. With improved technology, however, it has now been possible to increase the gain to 100.
3. We know that collector region is heated during base and emitter diffusions, so the diffusion coefficient of the collector impurities should be as small as possible to avoid the movement of the collector junction. Since n -type impurities have smaller diffusion constant than p -type impurities, the n -type collector moves very little while p -type moves appreciably. This makes the npn transistor superior in performance with relatively easier process control.

Multi-emitter Transistor

In many applications such as transistor-transistor logic (TTL), we need multi-emitter transistor of the type shown in Fig. 1.18 (a). The cross-sectional view of such a transistor is shown in Fig. 1.18 (b) where n^+ emitter is diffused at three places in the p -type base. Thus, it is possible to save chip area and enhance component density of an IC.

 


Fig. 1.18 (a) Multi-emitter transistor, (b) Cross-sectional view of a multi-emitter transistor

The Schottky Transistor

In digital circuits, many times it is desired that the switching should be very fast. This can be achieved if the transistor is prevented from entering into saturation. Figure 1.19 (a) shows such an arrangement where a Schottky diode (Sec. 1.7.2) is used as a clamp between the base and collector.

If base current is increased to saturate the transistor, the voltage at the collector drops thereby making diode D conduct. As soon as diode D conducts, the base to collector voltage drops to about 0.4 V which is less than the cut-in voltage for Si-base to collector junction (≈ 0.5 V), so that the transistor does not enter into saturation.

Figure 1.19 (b, c) shows the cross-sectional view of a Schottky transistor, and its symbol. A Schottky diode is formed between base and collector by allowing Al-metallization for the base lead to make contact with the *n*-type collector region. This is discussed in detail in Sec. 1.7.2.

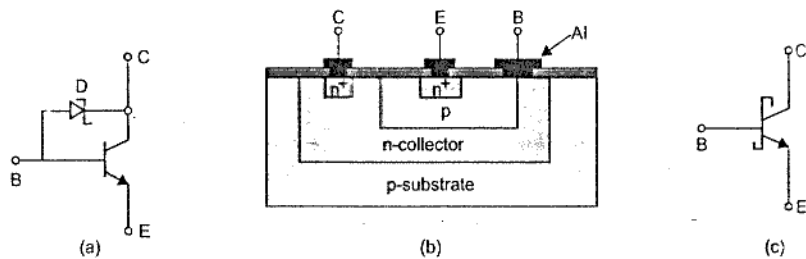


Fig. 1.19 (a) A transistor with a Schottky-barrier diode clamped between base and collector to prevent saturation, (b) Cross-section of a Schottky-barrier transistor, (c) Symbolic representation

1.7.2 Monolithic Diodes

Diodes find extensive use in integrated circuits, especially in digital applications. Figure 1.20 shows five different possible connections by which a transistor could be utilized as a diode. These configurations have slightly different characteristics as depicted in Table 1.1 and the choice of the diode depends upon the application and circuit performance desired.

 


Fig. 1.20 Cross-section of various diode structures

Table 1.1 Summary of typical values for various diode connections

Characteristic	(a) $V_{CE} = 0$	(b) $V_{CE} = 0$	(c) $V_{EB} = 0$	(d) $I_C = 0$	(e) $I_E = 0$
Breakdown voltage in volts	7	7	55	7	55
Storage time, in sec	9	100	53	56	85
Forward voltage in volts	.85	.92	.94	.96	.95

It can be seen that diode 'a' is most useful for getting high speed diode to be used in digital integrated circuit due to its lowest storage time and lowest forward voltage drop. Diodes 'b' and 'd' can be utilized as a stored charge device as this feature gives a high speed turn-off of the transistor. Diode 'c' and 'e' have the advantage of highest breakdown voltage.

Schottky Barrier Diode

Metal to semiconductor junctions can be ohmic as well as rectifying. The ohmic contact is used when a lead is to be attached to a semiconductor device. And a rectifying contact called a metal semiconductor diode (also called Schottky barrier diode), has characteristics very similar to an ordinary *pn* diode.

As already mentioned aluminium is a *p*-type impurity in silicon. So when it is used to make a contact with *n*-type Si, it is essential that contact is ohmic and no *pn* junction is formed. This is done by making *n*⁻ diffusions in the *n* regions near the surface where Al is deposited. On the other hand, if Al is deposited directly upon the *n*-type Si, a metal semiconductor diode is formed. It is found that such a metal semiconductor diode has essentially the same type of V-I characteristics as an ordinary *pn* junction, though the physical mechanism is very different and complicated.

Figure 1.21 (a) shows two contacts, where contact 1 is a Schottky barrier and contact 2 is an ohmic contact. The symbolic representation of a schottky diode is shown in Fig. 1.21 (b). The contact potential between the semiconductor and the metal creates a barrier to the flow of conduction electrons from semiconductor to metal. Forward biasing the junction lowers this barrier and permits electron flow from semiconductor to metal where electrons are abundant. Note that the majority carrier electrons carry current in a Schottky diode. On the other hand, in a *pn* junction diode, current is due to minority carriers and such a diode

 


Fig. 1.21 (a) A Schottky diode, (b) Symbol for metal semiconductor diode

shows a substantial time delay from *on* to *off*, as the minority carriers stored in the junction have to be totally removed. In this sense, Schottky diode exhibit negligible storage time, since electrons from the *n*-type Si enter the Al almost right at the contact surface, where they mix with the free electrons and are not stored.

Another significant advantage of this type of diode is that it has less forward voltage ($V_f \approx 0.3V$) when compared to that of *pn* diode ($V_f = 0.6V$). Thus it can be used for more ideal clamping, or as detectors in high frequency and microwave ICs.

1.7.3 Integrated Resistors

The basic technique for obtaining a resistor in integrated circuit is by utilising the bulk resistance of a defined volume of semiconductor region. Four different methods are available for fabricating integrated resistors, namely:

- Diffused Resistor
- Epitaxial Resistor
- Pinched Resistor
- Thin Film Resistor

Diffused Resistor

In this method, resistor is formed in one of the isolated regions of epitaxial layer during base or emitter diffusion, common to bipolar transistor fabrication. As no extra fabricating steps are required, this type of resistor is very economical. However, a severe limitation is the small range of resistances possible.

The value of the resistance depends upon the surface geometry i.e., length, width and upon the diffused impurity profile. In this context, a very useful quantity sheet resistance is defined as diffused layers are very thin.

Sheet Resistance R_s

Consider the square $L \times L$ of a material of resistivity ρ , thickness t , and cross-sectional area $A = L \times t$ shown in Fig. 1.22 (a). The resistance of this sheet of material can be written as

$$R_s = \frac{\rho L}{L \times t} = \frac{\rho}{t} \text{ (ohms per square)}$$

This quantity R_s is independent of the size of the square and mainly depends upon the diffusion characteristic of the material. Now consider Fig. 1.22 (b, c) which shows a base resistor and the emitter resistor. The resistance for these resistors can be expressed in terms of the sheet resistance R_s and the surface dimensions L and W .

$$\text{Now } R = \rho \frac{L}{W \times t}$$

$$\text{or, } R = R_s \frac{L}{W}$$

where the ratio L/W is called the aspect ratio of the surface geometry and is, therefore, the effective number of square contained in the resistor. The base resistor in the range of 20Ω to $300 \text{ k}\Omega$ can be easily fabricated due to medium resistivity, $200 \Omega/\text{square}$ *p*-type base region. However, the sheet resistance of the emitter diffusion is of the order of $5 \Omega/\text{sq}$. only. So, emitter resistors are usually in the range of 10 to $1 \text{ k}\Omega$.

 


Fig. 1.22 (a) Sheet resistance (b) Base resistor (c) Emitter resistor (d) Top view showing dimensions for a 4000Ω diffused resistor

Example

Design a 4 kΩ diffused resistor.

The sheet resistance of *p*-type diffusion is 200 ohm/sq.

$$\text{Then } \frac{L}{W} = \frac{R}{R_s} = \frac{4 \times 10^3}{200} = 20$$

So, a 4 kΩ resistor can be fabricated by using a pattern of 20 mils long by 1 mil wide as shown by the top view in Fig. 1.22 (d).

Epitaxial Resistor

Large value of resistance than possible by base or emitter resistor can be achieved by using *n*-epitaxial collector region as shown in Fig. 1.23 (a). Sheet resistance of epitaxial layer in the order of 1 to 10 kΩ/square, can be obtained.

 


Fig. 1.23 (a) Epitaxial resistor

Pinched Resistor

The sheet resistivity of a semiconductor region can be increased by reducing its effective cross-sectional area. In a pinched resistor, this technique is used to achieve a high value of sheet resistance from the ordinary base diffused resistor.

 


Fig. 1.23 (b) Cross-sectional view of a pinch resistor

A pinched base diffused resistor is shown in Fig. 1.23 (b). It can give resistances of the order of mega-ohm in a reasonably small area. In this structure, no current can flow through the *n*-type material (dark region) due to the diode at contact 2 in the reverse direction. Only

a small reverse saturation current can flow through *n*-material. So, by creating this *n*-type region the effective cross-sectional area for the conduction path has been reduced and thus resistance between 1 and 2 increases.

Thin Film Resistor

Vapour thin film deposition techniques as discussed in Sec. 1.5.8 can also be used for the fabrication of IC resistors. In this, a very thin metallic film usually of Nichrome (NiCr) of thickness less than 1 μm is vapour deposited on the SiO₂ layer. Using masked etching, desired geometry of this thin film is achieved to obtain suitable values of resistors. The ohmic contacts are made using Al metallization and usual masked etching techniques. Nichrome resistors are available with typical sheet resistance values of 40 to 400 Ω/square depending upon film thickness, so that resistance in the range of 20 to 50 kΩ can be easily obtained. Figure 1.23 (c) shows the cross-sectional view of such a resistor. These thin film resistors have three distinct advantages over the diffused resistors.

1. Thin film resistors have lesser and smaller parasitic components and hence their high frequency behaviour is better.
2. The values of thin-film resistors can be easily adjusted even after fabrication by cutting a part of the resistor with a laser beam (Laser trimming).
3. Thin film resistors have low temperature coefficient, thereby making them more stable.

 


Fig. 1.23 (c) Cross-section of a thin film resistor

Higher values of thin film resistors have been obtained by depositing Tantalum over SiO₂ layer. The main disadvantage of thin film resistors is the additional process steps required in their fabrication.

1.7.4 Integrated Capacitors

Two commonly used methods for obtaining integrated capacitors are as follows:

- (1) Junction capacitor
- (2) MOS and thin film capacitor

Junction Capacitor

It is possible to use the junction capacitance of a reverse biased diode as an element in monolithic ICs. Figure 1.24 shows the cross-sectional view of a junction monolithic capacitor and its equivalent circuit. It can be seen that there are two junctions in this type of diffused capacitor. Junction *J*₂, if reverse biased, will produce the desired capacitance. However, a parasitic capacitance *C*₁ is inevitable due to the junction *J*₁ between *n*-type epitaxial layer and the substrate. Also a series resistance results due to the bulk resistance of the *n*-region. In the equivalent circuit, two diodes are the idealized diodes of the two junctions. The

 


Fig. 1.24 (a) Junction-type IC capacitor, (b) Equivalent circuit

substrate must be held at the most negative point in the circuit, to minimize C_1 . The value of the capacitance C_2 will depend upon the area of the junction, impurity concentration of the n -type epitaxial layer and the voltage across the junction. It can be seen that the capacitor C_2 is polarised and is obtained only when the junction J_2 is reverse biased.

MOS and Thin Film Capacitor

A commonly used capacitor is the metal-oxide semiconductor capacitor for which the cross-sectional view and equivalent circuit is shown in Fig. 1.25. It is basically a parallel plate capacitor with SiO_2 as the dielectric. The heavily doped n^+ -region formed during the emitter diffusion forms the lower plate and the thin film of aluminium metallization forms the upper plate of the capacitor with SiO_2 as the dielectric. As shown in the equivalent circuit, the parasitic effects consist of a small series resistance R due to n^+ region, a collector substrate junction J_1 , and its associated capacitance C_1 .

 


Fig. 1.25 (a) Structure and (b) Equivalent circuit of a MOS capacitor

This type of capacitor has the advantage of being nonpolar, that is, it does not matter which of the plates is positive or negative. Nor is it a function of the voltage applied, thus giving more circuit flexibility. Silicon Nitride (Si_3N_4) can also be used as dielectric layer. Silicon Nitride offers a higher value of capacitance because of higher dielectric constant value, but requires extra processing steps.

Thin film capacitor structures which use thin dielectric film layer between two metal layers are also in use. Although such a capacitor structure is almost free from substrate

parasitics, it requires a number of additional masking and deposition steps beyond the basic MOS structure. In such a structure, either aluminium or tantalum is used as capacitor plates and aluminium oxide (Al_2O_3) or tantalum oxide (Ta_2O_5) as the dielectric material. Ta_2O_5 is particularly preferred for large value capacitors. One basic serious disadvantage of thin film capacitor is that it fails when the voltage rating exceeds due to breakdown of the dielectric. This is a destructive and irreversible failure mechanism and may require over-voltage protection.

1.7.5 Integrated Inductors

Inductors, transformers and chokes are the missing link in the chain of IC components. IC devices are essentially two dimensional as the depth dimension is usually very small (~1 to 10 μm) compared to the lateral dimensions. IC inductors can be made in the form of a flat metallic thin film spirals by successive deposition of conduction patterns. Very small values of inductance of the order of nano-henry with low quality factor can be only obtained. For any reasonable inductance value, a three-dimensional coil structure is needed to obtain a large number of turns.

Most circuit designers go to great lengths to avoid the use of inductors or otherwise simulate them by using RC active networks. In applications such as RF and IF circuits, where inductors cannot be avoided, inductors external to the IC-package are used. However, in thin-film hybrid microwave integrated circuit (MIC), thin-film inductor spirals are used giving upto 250 nH.

1.8 FABRICATION OF FET

Unipolar monolithic ICs use JFET or MOSFET as an active device. The fabrication technique of JFET, MCFET and CMOS is discussed.

1.8.1 JFET Fabrication

The structure of an n -channel JFET is shown in Fig. 1.26. The basic processes used are the same as in BJT fabrication. The epitaxial layer which formed the collector of the BJT is used as the n -channel of the JFET. The p^+ gate is formed in the n -channel by the process of diffusion or ion-implantation. The n^+ regions have been formed under the drain and source contact regions to provide good ohmic contact.

 


Fig. 1.26 n-channel JFET structure

1.8.2 MOSFET Fabrication

Two types of MOSFET devices are available, such as, enhancement type and depletion type. The cross-sectional view of n -channel aluminium gate enhancement MOSFET is shown in Fig. 1.27. In this structure, the metallic gate G is separated from the semiconductor channel by the insulating SiO_2 layer. The insulating layer of silicon dioxide gives an extremely high input resistance (10^{16} to $10^{18} \Omega$) for the MOSFET.

 


Fig. 1.27 n -channel MOSFET

The value of V_T , the threshold voltage for MOSFET fabricated by this technique is typically 3 to 6 V and power supply voltage of 12V is used for the drain supply. This large voltage is not compatible with the $\pm 5V$ supply used in digital ICs. A number of techniques have been developed to lower the magnitude of V_T which leads to improved device performance.

Use of Silicon Nitride (Si_3N_4)

It has been found that Si_3N_4 has superior masking properties compared to SiO_2 . The Si_3N_4 is sandwiched between two SiO_2 layers and provides the necessary barrier to prevent impurities penetrating through the SiO_2 layer. The dielectric constant of Si_3N_4 is 7.5 whereas that of SiO_2 is 4. This increased overall dielectric constant reduces V_T .

Polysilicon Gate

Polycrystalline silicon when doped with phosphorus is conductive and is used as the gate electrode instead of aluminium. This reduces V_T to about 1 to 2V. Such devices are called *silicon gate MOS transistors*. The fabrication of NMOS enhancement device using these improved techniques is shown in Fig. 1.28.

The Si_3N_4 is first coated on the entire surface of a p -type wafer. With the help of a mask, sufficient area is defined to include the source, gate and drain. The Si_3N_4 is next etched away from the surface outside the transistor region. Now p^+ impurities are ion-implanted in the exposed p -substrate. These p^+ regions serve to isolate the various devices. Next a thick SiO_2 layer called *field oxide* is grown over the p^+ regions. The Si_3N_4 region, however, remains unaffected by the oxidation. The structure now is as shown in Fig. 1.28 (a).

The Si_3N_4 is now removed by selective etching and then SiO_2 layer (800 to 1000 Å) is thermally grown over the transistor area as shown in Fig. 1.28 (b).

 


Fig. 1.28 Fabrication of polysilicon gate enhancement NMOS (a) Thick oxide growth and p^+ implantation, (b) Selective etching of Si_3N_4 and thin oxide growth, (c) Deposition of polysilicon gate, (d) Final cross-sectional view showing metalization and interconnection between substrate and source

Polycrystalline silicon commonly known as *polysilicon* is now deposited over the entire wafer. The polysilicon gate is now formed by selective removal of polysilicon as shown in Fig. 1.28 (c).

The n^+ source and drain regions are formed by ion implantation. The field oxide and the polysilicon gate prevent the penetration of dopants below these regions. The thin oxide layer however, allows the penetration of dopants and thus drain and source regions are formed.

After this, the entire wafer is covered with a protective isolating layer usually of SiO_2 . The contact areas (including the body) are next defined using photolithographic process. Finally aluminium is evaporated over the entire wafer and another mask is used to pattern the circuit connections. The final cross-section is shown in Fig. 1.28 (d).

There are two important points to be noticed in this structure.

1. The polysilicon-gate provides self-alignment of the gate with the source and drain. In a conventional metal gate structure of Fig. 1.27, the gate electrode is normally designed to overlap the edges of the source and drain region by about $5 \mu\text{m}$ to avoid any masking errors. This, however, results in small overlap capacitance C_{gs} between gate G and source S and C_{gd} between gate G and drain D . These capacitances are of the order of 1 to 3 pF and lower the speed of operation and increase the power consumption. The silicon gate due to self-aligning property eliminates these capacitances.
2. Another advantage of this structure is that no isolation island is required. This is because drain terminal in an NMOS device is held positive with respect to the source which is tied to the substrate. This cuts off the drain to substrate diode and the source to substrate diode formed due to p^+ region and the current flows only along the channel between D and S . In BJT, the isolation diffusion occupies an extremely large percentage of chip area. With MOSFET, it is possible to get a packaging density twenty times more than that of BJT IC.

1.8.3 Complementary MOSFET (CMOS) Fabrication

It is possible to fabricate NMOS and PMOS enhancement devices on the same silicon chip. These devices are called complementary MOSFETs (abbreviated as CMOS, COS/MOS). The CMOS circuit of Fig. 1.29 (a) when implemented with polysilicon gate FETs, has the cross-sectional view as shown in Fig. 1.29 (b). An n -type 'well' or 'tub' is diffused in the p -type substrate. The PMOS transistor (Q_2) is fabricated within this well. The n -type region forms the substrate or body B_2 for the PMOS transistor. There are two additional steps required in the fabrication of PMOS transistor (Q_2) compared to NMOS transistor (Q_1), such as, the formation of n -region and ion implantation of p -type source and drain regions. The rest of the processes are the same as discussed for NMOS fabrication.

 


Fig. 1.29 (a) CMOS inverter, (b) Cross-section of CMOS IC

It can be seen that B_1 is tied to S_1 and is connected to the lowest voltage (GND) whereas B_2 is tied to S_2 and held at supply voltage V_{DD} . Since B_1 is p -type and B_2 is n -type, both the source substrate diodes (B_1 - S_1 and B_2 - S_2) are reverse biased and thus cut off. Thus, isolation between NMOS and PMOS transistor is automatically achieved.

The circuit of Fig. 1.29 (a) is a CMOS inverter where G_1 is tied to G_2 and D_1 is connected to D_2 . However, we have not shown these connections in the cross-sectional view of Fig. 1.29 (b).

1.9 THIN AND THICK FILM TECHNOLOGY

Film ICs are classified as thick-film and thin-film circuits. Film technology at present can produce only passive components. The use of the term 'Thin Film' has been made in this chapter often, wherever isolation or interconnections have to be made in integrated circuits. Thin-film elements like resistors and capacitors have been discussed earlier also.

Conventional film circuits, both thick and thin, are made by depositing film capacitors and resistors on a passive substrate such as glass or ceramic and subsequently adding pre-fabricated active components to the film structure. Care has to be taken that the film elements and their interconnections are compatible with the rest of the integrated circuit.

Combining films and semiconductor technology, a circuit designer has greater degree of freedom, a wider range of component values and better electrical performance than either technology can provide separately.

Thin films are defined as the ones with thickness varying from 50 Å to 20,000 Å, whereas thick-films vary from 1,25,000 Å (0.5 mil) to 6,25,000 Å (2.5 mils). However, a more fundamental difference between thin film and thick film is not the ultimate thickness, but the technology or the processes used for forming the film. Thick film ICs are made by the process of screen printing, usually silk screening techniques, whereas, the materials used to make thin film are generally deposited on to substrates in a vacuum chamber. Nevertheless, thick-film technology produces cheap and rugged resistors, capacitors and conducting patterns. The processing equipment for thick film circuits is relatively inexpensive and easy to use. Thin film technology provides greater precision in manufacturing but is more costly than thick film technology.

1.9.1 Deposition of Thin Film

Various methods in use for deposition of thin film are:

1. Vacuum evaporation
2. Sputtering
3. Gas plating
4. Electroplating
5. Electroless plating
6. Silk screening

The methods listed above have been used with varying degree of success. In this text however, we limit ourselves to discuss cathode sputtering and plating techniques only.

Vacuum Evaporation

The system used for depositing film using this method has been already discussed in sec. 1.5.8 where the technique has been used for depositing thin aluminium film for taking out contacts from the IC.

Cathode Sputtering

The system used for cathode sputtering is almost identical to that used for vacuum evaporation. The process however is much slower than evaporation, depositing a micron-thick film in minutes to hours, compared to seconds to minutes for evaporation. However, sputtering is superior to vacuum evaporation in the quality of the film produced but sputtering equipment is more costly than most evaporation systems. The process of cathode sputtering is performed at a low pressure (about 10^{-12} torr). The source material (material to be sputtered) is subjected to intense bombardment by the ions of a heavy inert gas such as argon. These gas ions are usually accelerated by making the source material as the cathode of a dc glow discharge. As atoms are ejected from the surface of the cathode, they diffuse away from it through a low pressure gas, depositing as a thin film on a nearby substrate. This sounds crude, but the high energy of the particles landing on the substrate actually results in a very uniform film with good crystal structure and adhesion. The principal parts of a sputtering system are

 


Fig. 1.30 The principal parts of sputtering system

shown in the Fig. 1.30. A potential typically 2 to 5 kV, is applied between the cathode (source material) and anode, and produces a glow discharge that fills the entire interelectrode space, except for a thin region close to the cathode.

Plating Technique

The two types of plating technique used are (i) Electroplating (ii) Electroless plating.

Electroplating uses for typical process of coating an object with one or more layers of different metals. Cathode and anode, in this case substrate and metal, are immersed in an electrolytic solution. When dc is passed through the solution, the positive metal ions migrate from the anode and deposit on the cathode. This method is suitable for making conduction films of gold or copper.

In electroless deposition of thin films, a metal ion in solution is reduced to the free metal and deposited as a metallic coating without the use of an electric current. This process can be used to deposit metals on any substrate such as glass, ceramic, plastic, etc. and films to considerable thickness can be deposited.

1.9.2 Thick-Film Technology

The basic thick film processes are:

- (i) Screen printing
- (ii) Ceramic firing

The process of screen printing patterns is an ancient one. The Egyptians used this technique thousands of years ago to decorate pottery and the walls of buildings and tombs. The same process is used today for production of thick film circuits, though considerably more complicated than simply forcing the ink through the screen as did the equipment used by the Egyptians. The screens used are woven from stainless steel wires to mesh size 320 and mounted on aluminium frame so as to keep the screen under uniform tension. The screen is next coated

with a photo-sensitive emulsion which polymerizes on exposure to light. A mask (negative) of the desired pattern is made and kept on it. After exposure to light, it is developed. The screen becomes clear wherever thick film is to be deposited and blocked by the photoresist elsewhere. The screen is now placed on a substrate and carefully aligned components are deposited on the substrate through screening process. The screening process is carried out by a squeegee driven across the patterned screen at a constant rate. The squeegee forces an ink in the paste form through the openings on the screen. Different types of inks are used for depositing resistors conductors.

The desired physical and electrical properties from the thick films so deposited are now developed by thermal processing usually referred to as firing. It uses a furnace or kiln where temperature varies from 500°C to 1000°C in four to eight separately controlled zones. During the firing process, the organic binders of the thick film paste vaporises and the remaining material fuses with the substrate, thereby, becoming a part of the ceramic structure. However, the structure and dimensions of most thick films are not compatible with monolithic circuits, therefore their use is limited to hybrid structures only.

1.9.3 Surface Mount Technology (SMT)

SMT is one of the advanced achievements in the area of semiconductor technology. This technology improves the product in terms of function, size and quality. It is difficult to automate production line with the use of conventional components. However, with surface mount devices, automation of manufacturing process as well as interconnection methodology can be achieved. The compact size of microcassette recorder, calculators, wrist watches and radios is the result of clever electronic component packing and assembly as a surface mount technology.

Surface mount technology utilizes micro-miniature leaded or leadless components called SMDs which are directly soldered to the specified areas on the PCB/surface without holes. The compact size of SMD components greatly reduce the area in a PCB, thus increasing packaging density. In this technology, both the components as well as conductive paths are installed on the same side of PCB, whereas, in conventional mounting technology, the components are mounted on one side and conductive paths are on the other side of PCB.

1.10 TECHNOLOGY TRENDS

The technology of semiconductor is advancing at a rapid rate. For high-speed and low-noise applications, bipolar technology is used. The heat dissipation in bipolar circuits is large and requires elaborate cooling arrangement. The MOS technology is becoming popular, because, high component density can be achieved. Originally, PMOS devices were used but now NMOS technology is predominant due to high-speed performance. The CMOS technology is now leading NMOS because of extremely low power consumption. The feature size of CMOS is also decreasing rapidly. In 1990s, the minimum feature size for CMOS was 0.5 micron (μm), which reduced to 0.12 μm in the year 2002 and it is predicted that 0.07 μm will be available for production by 2004.

The assembly of the chip is also improving drastically: 120 to 250-pin package are already available. It is predicted that 1000-pin package will be available. The electron-beam photolithographic techniques have been outdated and X-rays are in use exclusively. By

2003–04 new techniques EUV and Scalpel will also be used along with X-ray. The interconnections will also undergo change from aluminium to copper and optical interconnections may soon arrive.

The design styles and design tools are also undergoing rapid evolution. The design tools are sometimes referred to as computer-aided-design (CAD) tools and automatic testing is employed. The programs SPICE for circuit analysis and SUPREME for device fabrication are the two widely used CAD tools. These tools are not used to design ICs but provide necessary information to evaluate a given design. No commercial IC is fabricated without such analysis.

SUMMARY

- An IC is a miniature, low cost electronic circuit fabricated on a single crystal chip of silicon.
- An IC offers increased reliability, improved performance, high speed and lower power consumption.
- ICs may be Linear or Digital.
- Important IC technologies used are Monolithic technology and Hybrid technology.
- The basic processes used in the silicon planar technology are (i) Substrate preparation (ii) Epitaxial growth (iii) SiO_2 growth (iv) Photolithography (v) Diffusion (vi) Metallization
- Order of magnitude for some important quantities:
 - Substrate thickness $\sim 400\text{--}800\ \mu\text{m}$ (16–32 mils)
 - Epitaxial thickness $\sim 5\text{--}20\ \mu\text{m}$
 - Oxide thickness $\sim 0.02\text{--}2\ \mu\text{m}$
 - Al metallization $\sim 1\ \mu\text{m}$
 - Base width (thickness) $\sim 0.7\ \mu\text{m}$
 - Diffusion time = about 2 hours
 - Diffusion temperature = 1000°C
 - Surface area for transistor = 25 mils
 - Wafer diameter = 10; 12.5; 15 cm
 - Chip size: $1\ \text{mm}^2$ (SSI); $16\ \text{mm}^2$ (MSI); $1\ \text{cm}^2$ (LSI)
 - Concentration of acceptor atoms in the p -type substrate
 $N_A = 1.4 \times 10^{15}\ \text{atoms/cm}^3$
 - Concentration of acceptor atoms in isolation islands
 $N_A = 5 \times 10^{20}/\text{cm}^3$
 - Sheet resistance for
 - epitaxial collector region is 1 to 10 $\text{k}\Omega/\text{sq}$.
 - p -type base region is 200 Ω/sq .
 - n -type emitter region is 5 Ω/sq .
- The various components in an IC are provided electrical isolation by fabricating each component in an isolation island. Isolation techniques used are p - n junction isolation and dielectric isolation.
- ICs are available in three packages:
 - TO-5 glass metal package
 - Ceramic flat package
 - Dual-in-line package

- Buried layer is a heavily doped n^+ layer sandwiched between the p -type substrate and n -type epitaxial collector to reduce the collector series resistance of the IC transistor.
- Aluminium used for making interconnections is a p -type impurity in silicon. The formation of a rectifying pn junction is avoided by making n^+ diffusions in the n -regions from where contact is to be made using aluminium. Such contacts are called ohmic.
- The npn transistors are preferred over pnp transistors in ICs.
- A Schottky barrier diode is clamped between base and collector of a transistor to avoid saturation.
- It has not been possible to fabricate high-Q inductors in monolithic ICs. Inductors have to be simulated by RC networks.
- MOSFET occupies very small area and consumes less power. A polysilicon gate MOSFET has advantage over aluminium gate as (i) it lowers V_T , (ii) it reduces capacitances due to self-aligning property.
- Thin and thick film technology is used to make passive components like resistors and capacitors. Films with thickness greater than 0.5 mil are usually made by thick film technology.

REVIEW QUESTIONS

- List the advantages of integrated circuit (IC) over discrete component circuit.
- Classify ICs on the basis of application, device used and chip complexity.
- Name the technology used for the fabrication of transistors or ICs.
- List the basic processes used in the silicon planar technology.
- Explain how silicon wafers are prepared.
- Explain the word "Epitaxy".
- Describe the Epitaxial growth process.
- Explain the importance of SiO_2 layer. How thick is this layer?
- Explain briefly the photolithography process.
- Describe the diffusion process.
- What is ion implantation? Give its advantages.
- Explain the need for making isolation islands.
- Explain the various isolation techniques used in ICs.
- To what voltage is the substrate connected and why?
- Name the different types of IC packages.
- Draw the cross-section of a discrete transistor and an IC transistor and hence compare their performance.
- What is meant by parasitic capacitance?
- Discuss the various ways for fabricating pnp transistor.
- Compare the performance of pnp and npn transistor.
- Explain why "Buried layer" is used.
- Show the cross-sectional structure of a multi-emitter transistor.

- 1.22. What is a Schottky transistor? Draw the cross-sectional view and explain its operation.
- 1.23. Give the various ways for making diodes in ICs.
- 1.24. Explain the operation of a Schottky barrier diode.
- 1.25. What is an ohmic contact?
- 1.26. Give the advantages of Schottky barrier diode over pn junction diode.
- 1.27. Discuss the various methods used for fabricating IC resistors and compare their performance.
- 1.28. Define sheet resistance R_s .
- 1.29. Sketch the cross-section of a junction capacitor and draw its equivalent circuit.
- 1.30. Sketch a MOS capacitor and explain the difference in junction capacitor and MOS capacitor.
- 1.31. What is a thin film capacitor?
- 1.32. Explain why inductors are difficult to fabricate in ICs.
- 1.33. Draw the cross-section of an n -channel MOSFET.
- 1.34. Discuss the various ways for reducing V_T of a MOSFET.
- 1.35. What is the effect of using a polysilicon gate?
- 1.36. Discuss the self-aligning property of a polysilicon gate MOSFET.
- 1.37. Sketch the cross-section of a CMOS transistor.
- 1.38. Discuss the difference between thin films and thick films.
- 1.39. List the various methods used for depositing thin films.
- 1.40. Discuss cathode sputtering.
- 1.41. Describe thick-film technology.

2

OPERATIONAL AMPLIFIER

2.1 INTRODUCTION

Linear integrated circuits are being used in a number of electronic applications such as in fields like audio and radio communication, medical electronics, instrumentation control, etc. An important linear IC is operational amplifier which will be discussed in this chapter.

The operational amplifier (commonly referred to as op-amp) is a multi-terminal device which internally is quite complex. Fortunately, for the ordinary user, it is not necessary to know about the op-amp's internal make-up. The manufacturers have done their job so well that op-amp's performance can be completely described by its terminal characteristics and those of external components that are connected to it. However, for the designer's interest, the electronics of op-amp is described where the various stages of op-amp are discussed. Then some of the FET op-amps are described. The dc and ac characteristics with compensating techniques and the various applications of op-amp are taken up later.

2.2 BASIC INFORMATION OF OP-AMP

Circuit Symbol

The circuit schematic of an op-amp is a triangle as shown in Fig. 2.1. It has two input terminals and one output terminal. The terminal with a (-) sign is called inverting input terminal and the terminal with (+) sign is called the non-inverting input terminal.

 


Fig. 2.1 Op-amp circuit symbol

Packages

There are three popular packages available:

1. The metal can (TO) package
2. The dual-in-line package (DIP)
3. The flat package or flat pack

Op-amp packages may contain single, two (dual) or four (quad) op-amps. Typical packages have 8 terminals (the can and the DIP or MINI DIP), 10 terminals (flatpacks and some cans) and 14 terminals (the DIP and the flat pack). The widely used very popular type, for example $\mu A741$ is a single op-amp and is available as an 8-pin can, an 8-pin DIP, a 10-pin flatpack or a 14-pin DIP. The $\mu A747$ is a dual 741 and comes in either a 10-pin can or a 14-pin DIP. Figure 2.2 shows the various IC packages along with the top view of connection diagram.

OP-AMP Terminals

Op-amps have five basic terminals, that is, two input terminals, one output terminal and two power supply terminals. The significance of other terminals varies with the type of the op-amp.

Refer to the top view of a metal can package ($\mu A741$) in Fig. 2.2 (a). The metal can has eight pins with pin number 8 identified by a tab. The other pins are numbered counter-clockwise from pin 8, beginning with pin 1. Pin 2 is called the inverting input terminal and pin 3 is the non-inverting input terminal, pin 6 is the output terminal and pins 7 and 4 are the power supply terminals labelled as V^+ and V^- respectively. Terminals 1 and 5 are used for dc offset. The pin 8 marked NC indicates 'No Connection'. In case of DIP package of 741 as in Fig. 2.2 (b, c), the top pin on the left of the notch locates pin 1, and the flat pack of Fig. 2.2 (d) has a dot on it for identification. The other pins are numbered counter-clockwise from pin 1. The pin numbers have been illustrated only for some popular op-amps and the user should consult the manufacturer's data sheet before connecting a given op-amp into a circuit.

 


Fig. 2.2 Contd.


 


Fig. 2.2 (a, b, c, d) Various IC packages of $\mu A741$ op-amp along with connection diagrams (top view)

Power Supply Connections

The V^+ and V^- power supply terminals are connected to two dc voltage sources. The V^+ pin is connected to the positive terminal of one source and the V^- pin is connected to the negative terminal of the other source as illustrated in Fig. 2.3 (a) where the two sources are 15 V batteries each. These are typical values, but in general, the power supply voltage may range from about ± 5 V to ± 22 V. The common terminal of the V^+ and V^- sources is connected to a reference point or ground. Some op-amps have a ground terminal, but most do not. The ground is simply a convenient point on the circuit bread-board to which the op-amp is connected through the power supplies. The equivalent representation of Fig. 2.3 (a) is given in Fig. 2.3 (b). The common point of the two supplies must be grounded, otherwise twice the supply voltage will get applied and it may damage the op-amp. Instead of using two power

 

(Fig. 2.3 Contd.)

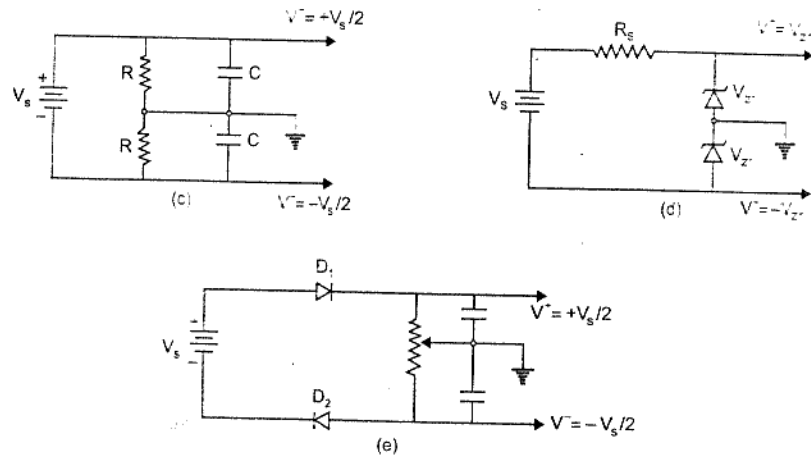


Fig. 2.3 (a) Power supply connections, (b) Circuit symbol showing power supply terminals (c, d, e) Different circuits for obtaining positive and negative supply voltages for op-amp

supplies, one can use a single power supply to obtain V^+ and V^- as shown in circuits of Fig. 2.3 (c, d, e). In Fig. 2.3 (c), resistor R should be greater than $10\text{ k}\Omega$ so that it does not draw more current from the supply V_s . The two capacitors provide decoupling of the power supply and range in value from 0.01 to $10\text{ }\mu\text{F}$. In the circuit of Fig. 2.3 (d), zener diodes are used to give symmetrical supply voltages. The value of the resistor R_s is chosen such that it supplies sufficient current for the zener diodes to operate in the avalanche mode. In Fig. 2.3 (e), potentiometer is used to get equal values of V^+ and V^- . Diodes D_1 and D_2 protect the IC if the positive and negative leads of the supply voltage V_s are accidentally reversed. These diodes can also be connected in the circuits of Fig. 2.3 (c) and 2.3 (d).

Manufacturer's Designation for Linear ICs

Each manufacturer uses a specific code and assigns a specific type number to the ICs produced. For example, 741 an internally compensated op-amp originally manufactured by Fairchild is sold as $\mu\text{A}741$. Here μA represents the identifying initials used by Fairchild. The codes used by some of the well-known manufacturers of linear ICs are:

(1) Fairchild	μA , μAF
(2) National Semiconductor	LM, LH, LF, TBA
(3) Motorola	MC, MFC
(4) RCA	CA, CD
(5) Texas Instruments	SN
(6) Signetics	N/S, NE/SE
(7) Burr-Brown	BB

A number of manufacturers also produce popular ICs of the other manufacturers. For easy use, they usually retain the original type number of the IC alongwith their identifying

initials. For example, Fairchild's original $\mu\text{A}741$ is also manufactured by other manufacturers as follows:

(1) National Semiconductor	LM741
(3) Motorola	MC1741
(4) RCA	CA3741
(5) Texas Instruments	SN52741
(6) Signetics	N5741

It may be noted that the last three digits in each manufacturer's designation are 741. All these op-amps have the same specifications. Since a number of manufacturers produce the same IC, one can refer to such ICs by their type number only and delete manufacturer's identifying initials. For example, $\mu\text{A}741$ or MC1741 may simply be referred as 741.

Some linear ICs are available in different classes such as A, C, E, S and SC. For example 741, 741A, 741C, 741E, 741S and 741SC are different versions of the same op-amp. The main difference of these op-amps are:

741	Military grade op-amp (Operating temperature range -55° to 125°C)	
741C	Commercial grade op-amp (Operating temperature range 0° to $70^\circ/75^\circ\text{C}$)	
741A	Improved version of 741	} Better electrical specifications
741E	Improved version of 741C	
741S	Military grade op-amp with higher slew-rate	
741SC	Commercial grade op-amp with higher slew-rate	

2.3 THE IDEAL OPERATIONAL AMPLIFIER

The schematic symbol of an op-amp is shown in Fig. 2.4 (a). It has two input terminals and one output terminal. Other terminals have not been shown for simplicity. The $-$ and $+$ symbols at the input refer to inverting and non-inverting input terminals respectively, i.e. if $v_1 = 0$, output v_o is 180° out of phase with input signal v_2 . And, when $v_2 = 0$, output v_o will

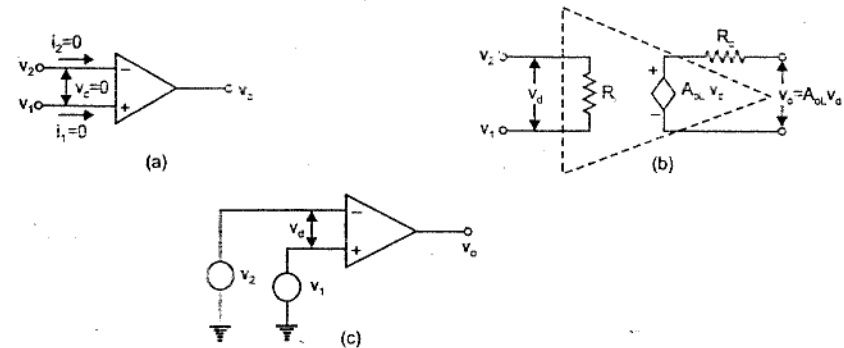


Fig. 2.4 (a) Ideal op-amp, (b) Equivalent circuit of an op-amp (c) Open loop circuit

be in phase with the input signal applied at v_1 . This op-amp is said to be ideal if it has the following characteristics.

Open loop voltage gain,	A_{OL}	=	∞
Input impedance,	R_i	=	∞
Output impedance	R_o	=	0
Bandwidth	BW	=	∞
Zero offset, i.e. $v_o = 0$ when $v_1 = v_2 = 0$.			

It can be seen that

- an ideal op-amp draws no current at both the input terminals i.e., $i_1 = i_2 = 0$. Because of infinite input impedance, any signal source can drive it and there is no loading on the preceding driver stage.
- Since gain is ∞ , the voltage between the inverting and non-inverting terminals, i.e., differential input voltage $v_d = (v_1 - v_2)$ is essentially zero for finite output voltage v_o .
- The output voltage v_o is independent of the current drawn from the output as $R_o = 0$. The output thus can drive an infinite number of other devices.

The above properties can never be realized in practice. However, the use of such an 'Ideal op-amp' model simplifies the mathematics involved in op-amp circuits. There are practical op-amps that can be made to approximate some of these characteristics.

A physical amplifier is not an ideal one. So, the equivalent circuit of an op-amp may be shown in Fig. 2.4 (b) where $A_{OL} \neq \infty$, $R_i \neq \infty$ and $R_o \neq 0$. It can be seen that op-amp is a voltage controlled voltage source and $A_{OL} v_d$ is an equivalent *Thevenin* voltage source and R_o is the *Thevenin* equivalent resistance looking back into the output terminal of an op-amp. The equivalent circuit is useful in analyzing the basic operating principles of op-amp. For the circuit shown in Fig. 2.4 (b), the output voltage is

$$\begin{aligned} v_o &= A_{OL} v_d \\ &= A_{OL} (v_1 - v_2) \end{aligned} \quad (2.1)$$

The equation shows that the op-amp amplifies the difference between the two input voltages.

2.3.1 Open Loop Operation of Op-Amp

The simplest way to use an op-amp is in the open loop mode. Refer to Fig. 2.4 (c) where signals v_1 and v_2 are applied at non-inverting and inverting input terminals respectively. Since the gain is infinite, the output voltage v_o is either at its positive saturation voltage ($+V_{sat}$) or negative saturation voltage ($-V_{sat}$) as $v_1 > v_2$ or $v_2 > v_1$ respectively. The output assumes one of the two possible output states, that is, $+V_{sat}$ or $-V_{sat}$ and the amplifier acts as a switch only. This has a limited number of applications such as voltage comparator, zero crossing detector etc. which are discussed later.

2.3.2 Feedback in Ideal Op-Amp

The utility of an op-amp can be greatly increased by providing negative feedback. The output in this case is not driven into saturation and the circuit behaves in a linear manner.

Two Important Negative Feedback Circuits

There are two basic feedback connections used. In order to understand the operation of these circuits, we make two realistic simplifying assumptions discussed earlier also.

- The current drawn by either of the input terminals (non-inverting and inverting) is negligible.
- The differential input voltage v_d between non-inverting and inverting input terminals is essentially zero.

2.3.3 The Inverting Amplifier

This is perhaps the most widely used of all the op-amp circuits. The circuit is shown in Fig. 2.5 (a). The output voltage v_o is fed back to the inverting input terminal through the $R_f - R_1$ network where R_f is the feedback resistor. Input signal v_i (ac or dc) is applied to the inverting input terminal through R_1 and non-inverting input terminal of op-amp is grounded.

Analysis: For simplicity, assume an ideal op-amp. As $v_d = 0$, node 'a' is at ground potential and the current i_1 through R_1 is

$$i_1 = \frac{v_i}{R_1} \quad (2.2)$$

Also since op-amp draws no current, all the current flowing through R_1 must flow through R_f . The output voltage,

$$v_o = -i_1 R_f = -v_i \frac{R_f}{R_1} \quad (2.3)$$

Hence, the gain of the inverting amplifier (also referred as closed loop gain) is,

$$A_{CL} = \frac{v_o}{v_i} = -\frac{R_f}{R_1} \quad (2.4)$$

Alternatively, the nodal equation at the node 'a' in Fig. 2.5 (a) is

$$\frac{v_a - v_i}{R_1} + \frac{v_a - v_o}{R_f} = 0$$

where v_a is the voltage at node 'a'. Since node 'a' is at virtual ground $v_a = 0$. Therefore, we get,

$$A_{CL} = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$$

 


Fig. 2.5 (a) Inverting amplifier

The negative sign indicates a phase shift of 180° between v_i and v_o . Also since inverting input terminal is at virtual ground, the effective input impedance is R_1 . The value of R_1 should be kept fairly large to avoid loading effect. This however, limits the gain that can be obtained from this circuit. A load resistor R_L is usually put at the output in actual practice

otherwise, the input impedance of the measuring device such as oscilloscope or DVM acts as the load. The calculation of load and output currents is shown in the Example 2.2.

If, however, resistances R_1 and R_f in Fig. 2.5 (a) are replaced by impedances Z_1 and Z_f respectively, then the voltage gain, A_{CL} will be

$$A_{CL} = -\frac{Z_f}{Z_1} \quad (2.5)$$

This expression for the voltage gain will be used in op-amp applications, such as integrator, differentiator etc.

Example 2.1

Design an amplifier with a gain of -10 and input resistance equal to $10 \text{ k}\Omega$.

Solution

Since the gain of the amplifier is negative, an inverting amplifier has to be made.

In Fig. 2.5 (a) choose $R_1 = 10 \text{ k}\Omega$

Then
$$R_f = -A_{CL} R_1 \text{ (from Eq. 2.4)}$$

$$= -(-10) \times 10 \text{ k}\Omega = 100 \text{ k}\Omega$$

Example 2.2

In Fig. 2.5 (b), $R_1 = 10 \text{ k}\Omega$, $R_f = 100 \text{ k}\Omega$, $v_i = 1 \text{ V}$. A load of $25 \text{ k}\Omega$ is connected to the output terminal. Calculate (i) i_1 (ii) v_o (iii) i_L and (iv) total current i_o into the output pin.

Solution

(i)
$$i_1 = \frac{v_i}{R_1} = \frac{1 \text{ V}}{10 \text{ k}\Omega} = 0.1 \text{ mA}$$

(ii)
$$v_o = -\frac{R_f}{R_1} v_i = -\frac{100 \text{ k}\Omega}{10 \text{ k}\Omega} 1 \text{ V} = -10 \text{ V}$$

(iii)
$$i_L = \frac{v_o}{R_L} = \frac{10 \text{ V}}{25 \text{ k}\Omega} = 0.4 \text{ mA}$$

The direction of i_L is shown in Fig. 2.5 (b).

(iv) i_1 as calculated above is 0.1 mA .

Therefore, total current $i_o = i_1 + i_L = 0.1 \text{ mA} + 0.4 \text{ mA} = 0.5 \text{ mA}$. In an inverting amplifier, for a +ive input, output will be -ive, therefore the direction of i_o is as shown in Fig. 2.5 (b).

 


Fig. 2.5 (b) Circuit for Example 2.2

Practical Inverting Amplifier

Equation (2.4) is valid only if the op-amp is an ideal one. For a practical op-amp, the expression for the closed loop voltage gain should be calculated using the low frequency model of Fig. 2.4 (b). The equivalent circuit of a practical inverting amplifier is shown in Fig. 2.6 (a). This circuit can be simplified by replacing the signal source v_i and resistors R_1 and R_f by Thevenin's equivalent as shown in Fig. 2.6 (b) which is analysed to calculate the exact expression for closed loop gain, A_{CL} and input impedance R_{if} .

 
 
 


Fig. 2.6 (a) Equivalent circuit of a practical op-amp inverting amplifier, (b) Simplified circuit by using Thevenin's equivalent (c) Equivalent circuit for computing R_{of}

The input impedance R_{if} of an op-amp is usually much greater than R_1 , so one may assume, $v_{eq} \approx v_i$ and $R_{eq} \approx R_1$.

From the output loop in Fig. 2.6 (b)

$$v_o = iR_o + A_{OL} v_d \quad (2.6)$$

Also
$$v_d + iR_f + v_o = 0 \quad (2.7)$$

Putting the value of v_d from Eq. (2.6) to Eq. (2.7) and simplifying,

$$v_o(1 + A_{OL}) = i(R_o - A_{OL} R_f) \quad (2.8)$$

Also the KVL loop equation gives

$$v_i = i(R_1 + R_f) + v_o \quad (2.9)$$

Putting the value of i from Eq. (2.8) in Eq. (2.9) and solving for closed loop gain $A_{CL} = \frac{v_o}{v_i}$, gives

$$A_{CL} = \frac{v_o}{v_i} = \frac{R_o - A_{OL} R_f}{R_o + R_f + R_1 (1 + A_{OL})} \quad (2.10)$$

It can be seen from Eq. (2.10) that if $A_{OL} \gg 1$ and $A_{OL} R_1 \gg R_o + R_f$, and neglecting R_o ,

$$A_{CL} \cong -\frac{R_f}{R_1}$$

Input Resistance R_{if}

In Fig. 2.6 (b), it can be seen that

$$R_{if} = \frac{v_d}{i}$$

Writing the loop equation and solving for R_{if} ,

$$v_d + i(R_f + R_o) + A_{OL} v_d = 0$$

We obtain

$$R_{if} = \frac{R_f + R_o}{1 + A_{OL}} \quad (2.11)$$

Output Resistance R_{of}

Output impedance R_{of} (without load resistance R_L) is calculated from the open circuit output voltage v_{oc} and short circuit output current i_{sc} . Now consider the circuit shown in Fig. 2.6 (c). Under short circuit conditions at output,

$$i_A = \frac{v_i - 0}{R_1 + R_f} \quad (2.12)$$

$$\text{and, } i_B = \frac{A_{OL} v_d}{R_o} \quad (2.13)$$

$$\text{Since } v_d = -i_A R_f$$

$$\text{So, } i_B = -\frac{A_{OL} i_A R_f}{R_o}$$

Solving for $i_{sc} = i_A + i_B$, we obtain

$$i_{sc} = i_A + i_B = v_i \frac{(R_o - A_{OL} R_f)}{R_o (R_1 + R_f)} \quad (2.14)$$

Since

$$R_{of} = \frac{v_{oc}}{i_{sc}}$$

$$\text{and } A_{CL} = \frac{v_{oc}}{v_i}$$

$$\text{Therefore, } R_{of} = \frac{A_{CL} v_i}{v_i \left[\frac{(R_o - A_{OL} R_f)}{R_o (R_1 + R_f)} \right]} \quad (2.15)$$

Putting the value of A_{CL} from Eq. (2.10), we obtain

$$R_{of} = \frac{R_o (R_1 + R_f)}{R_o + R_f + R_1 (1 + A_{OL})} \quad (2.16)$$

Equation (2.16) may alternatively be written as

$$R_{of} = \frac{\frac{R_o (R_1 + R_f)}{R_o + R_1 + R_f}}{1 + \frac{R_1 A_{OL}}{R_o + R_1 + R_f}} \quad (2.17)$$

It may be seen that numerator consists of a term $R_o \parallel (R_1 + R_f)$ and is therefore smaller than R_o . The output resistance R_{of} (with feedback) is, therefore always less than R_o and for $A_{CL} \rightarrow \infty$, $R_{of} \rightarrow 0$.

2.3.4 The Non-Inverting Amplifier

If a signal (ac or dc) is applied to the non-inverting input terminal and feedback is given as shown in Fig. 2.7 (a), the circuit amplifies without inverting the input signal. Such a circuit is called non-inverting amplifier. It may be noted that it is also a negative feedback system as output is being fed back to the inverting input terminal.

As the differential voltage v_d at the input terminal of op-amp is zero, the voltage at node 'a' in Fig. 2.7 (a) is v_i , same as the input voltage applied to non-inverting input terminal. Now R_f and R_1 forms a potential divider. Hence

$$v_i = \frac{v_o}{R_1 + R_f} R_1 \quad (2.18)$$

as no current flows into the op-amp.

$$\frac{v_o}{v_i} = \frac{R_1 + R_f}{R_1} = 1 + \frac{R_f}{R_1} \quad (2.19)$$

Thus, for non-inverting amplifier the voltage gain,

$$A_{CL} = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1} \quad (2.20)$$

 


Fig. 2.7 (a) Non-inverting amplifier

The gain can be adjusted to unity or more, by proper selection of resistors R_f and R_1 . Compared to the inverting amplifier, the input resistance of the non-inverting amplifier is extremely large ($= \infty$) as the op-amp draws negligible current from the signal source.

Practical Non-Inverting Amplifier

The analysis of a practical non-inverting amplifier can be performed by using the equivalent circuit shown in Fig. 2.7 (b). Writing KCL at the input node,

$$(v_i - v_d) Y_1 + v_d Y_i + (v_i - v_d - v_o) Y_f = 0$$

$$\text{or, } -(Y_1 + Y_i + Y_f) v_d + (Y_i + Y_f) v_i = Y_f v_o \quad (2.21)$$

 


Fig. 2.7 (b) Equivalent circuit of non-inverting amplifier using low frequency model

Similarly at output node, KCL gives

$$(v_i - v_d - v_o) Y_f + (A_{OL} v_d - v_o) Y_o = 0$$

that is,

$$-(Y_f - A_{OL} Y_o) v_d + Y_f v_i = (Y_f + Y_o) v_o \quad (2.22)$$

Now solving Eqs. (2.21) and (2.22) for v_o/v_i , we get

$$A_{CL} = \frac{v_o}{v_i} = \frac{A_{OL} Y_o (Y_1 + Y_f) + Y_f Y_i}{(A_{OL} + 1) Y_o Y_f + (Y_1 + Y_i) (Y_f + Y_o)} \quad (2.23)$$

where all admittances have been taken for simplicity.

If $A_{OL} \rightarrow \infty$, Eq. (2.23) reduces to

$$\begin{aligned} A_{CL} &= \frac{A_{OL} Y_o (Y_1 + Y_f)}{A_{OL} Y_o Y_f} = \frac{Y_1 + Y_f}{Y_f} = 1 + \frac{Y_1}{Y_f} \\ &= 1 + \frac{R_f}{R_1} \end{aligned}$$

which is the same expression as in Eq. (2.20).

2.3.5 Voltage Follower

In the non-inverting amplifier of Fig. 2.7 (a) if $R_f = 0$ and $R_1 = \infty$, we get the modified circuit of Fig. 2.7 (c). From Eq. (2.20) we get,

$$v_o = v_i \quad (2.24)$$

That is, the output voltage is equal to input voltage, both in magnitude and phase. In other words, we can also say that the output voltage follows the input voltage exactly. Hence, the circuit is called a voltage follower. The use of the unity gain circuit lies in the fact that its input impedance is very high (i.e. $M\Omega$ order) and output impedance is zero. Therefore, it draws negligible current from the source. Thus a voltage follower may be used as buffer for impedance matching, that is, to connect a high impedance source to a low impedance load.

 


Fig. 2.7 (c) Voltage follower

Example 2.3

Design an amplifier with a gain of +5 using one op-amp.

Solution

Since the gain is positive, we have to make a non-inverting amplifier. In Fig. 2.7 (a) select $R_1 = 10 \text{ k}\Omega$. Then from Eq. (2.20)

$$A_{CL} = 1 + R_f/R_1$$

$$\text{or, } 5 = 1 + R_f/10 \text{ k}\Omega$$

$$\text{or, } R_f = 4 \times 10 \text{ k}\Omega = 40 \text{ k}\Omega$$

Example 2.4

In the circuit of Fig. 2.7 (a), let $R_1 = 5 \text{ k}\Omega$, $R_f = 20 \text{ k}\Omega$ and $v_i = 1 \text{ V}$. A load resistor of $5 \text{ k}\Omega$ is connected at the output as in Fig. 2.5 (b). Calculate, (i) v_o (ii) A_{CL} (iii) the load current i_L (iv) the output current i_o , indicating proper direction of flow.

Solution

$$(i) v_o = \left(1 + \frac{R_f}{R_1}\right) v_i = \left(1 + \frac{20 \text{ k}\Omega}{5 \text{ k}\Omega}\right) (1 \text{ V}) = 5 \text{ V}$$

$$(ii) A_{CL} = \frac{v_o}{v_i} = \frac{5 \text{ V}}{1 \text{ V}} = 5$$

$$(iii) i_L = \frac{v_o}{R_L} = \frac{5 \text{ V}}{5 \text{ k}\Omega} = 1 \text{ mA}$$

$$(iv) i_o = \frac{v_i}{R_1} = \frac{v_o - v_i}{R_f} = 0.2 \text{ mA}$$

Therefore, $i_o = i_L + i_1 = 1 \text{ mA} + 0.2 \text{ mA} = 1.2 \text{ mA}$

The op-amp output current i_o flows outwards from the output junction.

2.3.6 Differential Amplifier

A circuit that amplifies the difference between two signals is called a difference or differential amplifier. This type of the amplifier is very useful in instrumentation circuits (see section 4.3). A typical circuit is shown in Fig. 2.8. Since, the differential voltage at the input terminals of the op-amp is zero, nodes 'a' and 'b' are at the same potential, designated as v_3 . The nodal equation at 'a' is,

$$\frac{v_3 - v_2}{R_1} + \frac{v_3 - v_o}{R_2} = 0 \quad (2.25)$$

and at 'b' is

$$\frac{v_3 - v_1}{R_1} + \frac{v_3}{R_2} = 0 \quad (2.26)$$

Rearranging, we get

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)v_3 - \frac{v_2}{R_1} = \frac{v_o}{R_2} \quad (2.27)$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)v_3 - \frac{v_1}{R_1} = 0 \quad (2.28)$$

Subtracting Eq. (2.28) from (2.27) we get,

$$\frac{1}{R_1}(v_1 - v_2) = \frac{v_o}{R_2} \quad (2.29)$$

Therefore,

$$v_o = \frac{R_2}{R_1}(v_1 - v_2) \quad (2.30)$$

Such a circuit is very useful in detecting very small differences in signals, since the gain R_2/R_1 can be chosen to be very large. For example, if $R_2 = 100 R_1$, then a small difference $v_1 - v_2$ is amplified 100 times.

Difference-mode and Common-mode Gains

In Eq. (2.30) if $v_1 = v_2$ then $v_o = 0$. That is, the signal common to both inputs gets cancelled and produces no output voltage. This is true for an ideal op-amp, however, a practical op-amp exhibits some small response to the common mode component of the input voltages too. For example, the output v_o will have different value for case (i) with $v_1 = 100 \mu\text{V}$ and $v_2 = 50 \mu\text{V}$ and case (ii) with $v_1 = 1000 \mu\text{V}$ and $v_2 = 950 \mu\text{V}$, even though the difference signal $v_1 - v_2 = 50 \mu\text{V}$ in both the cases. The output voltage depends not only upon the difference signal v_d at the input, but is also affected by the average voltage of the input signals, called the common-mode signal v_{CM} defined as,

$$v_{CM} = \frac{v_1 + v_2}{2}$$

 


Fig. 2.8 A differential amplifier

For differential amplifier, though the circuit is symmetric, but because of the mismatch, the gain at the output with respect to the positive terminal is slightly different in magnitude to that of the negative terminal. So, even with the same voltage applied to both inputs, the output is not zero. The output, therefore, must be expressed as,

$$v_o = A_1 v_1 + A_2 v_2 \quad (2.31)$$

where, A_1 (A_2) is the voltage amplification from input 1 (2) to the output with input 2 (1) grounded. Since $v_{CM} = (v_1 + v_2)/2$ and $v_d = (v_1 - v_2)$,

$$v_1 = v_{CM} + \frac{1}{2}v_d \quad (2.32)$$

and

$$v_2 = v_{CM} - \frac{1}{2}v_d \quad (2.33)$$

Substituting the value of v_1 and v_2 in Eq. (2.31), we get

$$v_o = A_{DM} v_d + A_{CM} v_{CM} \quad (2.34)$$

where,

$$A_{DM} = \frac{1}{2}(A_1 - A_2) \quad (2.35)$$

and

$$A_{CM} = A_1 + A_2 \quad (2.36)$$

The voltage gain for the difference signal is A_{DM} and that for the common-mode signal is A_{CM} .

2.3.7 Common-mode Rejection Ratio

The relative sensitivity of an op-amp to a difference signal as compared to a common-mode signal is called common-mode rejection ratio (CMRR) and gives the figure of merit ρ for the differential amplifier. So, CMRR is given by:

$$\rho = \left| \frac{A_{DM}}{A_{CM}} \right| \quad (2.37)$$

and is usually expressed in decibels (dB). For example, the μA741 op-amp has a minimum CMRR of 70 dB whereas a precision op-amp such as μA725A has a minimum CMRR of 120 dB. Clearly, we should have A_{DM} large A_{CM} should be zero ideally. So, higher the value of CMRR, better is the op-amp.

Example 2.5

In Fig. 2.9 is shown a differential amplifier using ideal op-amp.

- Find the output voltage v_o .
- Show that the output corresponding to common-mode voltage

$$v_{CM} = \frac{(v_1 + v_2)}{2} \text{ is zero if } \frac{R'}{R} = \frac{R_2}{R_1}.$$

Find v_o in this case.

- Find CMRR of the amplifier if $\frac{R'}{R} \neq \frac{R_2}{R_1}$.

 


Fig. 2.9 Circuit of Example 2.5

Solution

The voltage at the non-inverting input terminal is $\frac{R_2}{R_1 + R_2} v_1$. Using principle of superposition and Eqs. (2.4) and (2.20), we have

$$(a) \quad v_o = -\frac{R'}{R} v_2 + \left(\frac{R + R'}{R}\right) \left(\frac{R_2}{R_1 + R_2} v_1\right) \quad (2.38)$$

$$(b) \quad v_{CM} = \frac{1}{2}(v_1 + v_2) \text{ and } v_d = (v_1 - v_2)$$

$$\text{So, } v_1 = v_{CM} + \frac{v_d}{2} \text{ and } v_2 = v_{CM} - \frac{v_d}{2}$$

v_o from Eq. (2.38) is,

$$\begin{aligned} v_o &= -\frac{R'}{R} \left(v_{CM} - \frac{v_d}{2}\right) + \frac{R_2}{R} \frac{R + R'}{R_1 + R_2} \left(v_{CM} + \frac{v_d}{2}\right) \\ &= \left(\frac{R_2}{R} \frac{R + R'}{R_1 + R_2} - \frac{R'}{R}\right) v_{CM} + \left(\frac{R'}{R} + \frac{R_2}{R} \frac{R + R'}{R_1 + R_2}\right) \frac{v_d}{2} \end{aligned} \quad (2.39)$$

Now, if $\frac{R'}{R} = \frac{R_2}{R_1}$, we get,

$$\frac{R'}{R} + 1 = \frac{R_2}{R_1} + 1$$

$$\text{or, } \frac{R' + R}{R} = \frac{R_1 + R_2}{R_1}$$

So, from Eq. (2.39) the term corresponding to v_{CM} is zero, and

$$v_o = \left(\frac{R'}{R} + \frac{R_2}{R_1}\right) \frac{v_d}{2} = \left(\frac{R_2}{R_1}\right) v_d \quad (2.40)$$

$$(c) \quad \text{CMRR} = \frac{A_{DM}}{A_{CM}}$$

From Eq. (2.39), find (i) $A_{DM} = v_o/v_d$ by putting $v_{CM} = 0$

and (ii) $A_{CM} = v_o/v_{CM}$ by putting $v_d = 0$

then we get

$$\text{CMRR} = \frac{R'(R_1 + R_2) + R_2(R + R')}{R'(R_1 + R_2) - R_1(R + R')} \quad (2.41)$$

2.4 OPERATIONAL AMPLIFIER INTERNAL CIRCUIT

Commercial IC op-amps usually consists of four cascaded blocks as shown in Fig. 2.10. The first two stages are cascaded differential amplifiers and are designed to provide high gain and high input resistance. The third stage acts as a buffer as well as a level shifter. The buffer is usually an emitter follower whose input impedance is very high so that it prevents loading of the high gain stage. The level shifter adjusts the d.c. voltages so that output voltage is zero for zero inputs. The adjustment of d.c. level is required as the gain stages are direct coupled. As it is not possible to fabricate large value of capacitors, all IC's are direct coupled usually. The output stage is designed to provide a low output impedance as demanded by the ideal op-amp characteristics. The output voltage should swing symmetrically with respect to ground. To allow such symmetrical swing, the amplifier is provided with both positive and negative supply voltages. Power supply voltages of $\pm 15V$ are common. Additionally, an op-amp generally incorporates circuitry to provide drift compensation and frequency compensation which are discussed in sec. 3.3.3.

 


Fig. 2.10 Block schematic of an op-amp

Before describing the detailed IC circuit, we shall discuss each of the blocks in detail.

2.4.1 Differential Amplifier

The main purpose of the differential amplifier stage is to provide high gain to the difference-mode signal and cancel the common-mode signal. Thus, it is able to suppress any undesired noise which is common to both of the input terminals. The relative sensitivity of an op-amp to a difference signal as compared to common-mode signal is called common-mode rejection ratio (CMRR) and gives the figure of merit of the differential amplifier. The higher the value of CMRR, better is the op-amp. Another requisite of a good op-amp is that it should have high input impedance. In this section, we discuss in detail, the various circuits and their modifications to achieve these characteristics of a good op-amp.

A cascaded direct coupled amplifier can provide high gain down to zero frequency as it has no coupling capacitor. However, such an amplifier suffers from the major problem of drift of the operating point due to temperature dependency of I_{CO} , V_{BE} and h_{FE} of the transistor. This problem can be eliminated by using a balanced or differential amplifier as shown in Fig. 2.11 (a). It may be seen that it is essentially an emitter-coupled differential amplifier. This circuit has low drift on account of symmetrical construction. It can be designed to give high input resistance. It has two input terminals and it may be seen easily that terminal B_2 is the inverting input terminal since transistor Q_2 provides a phase shift of 180° for the output taken at the collector of Q_2 . Obviously, B_1 is the non-inverting input terminal. So, a differential amplifier is well suited to obtain the ideal characteristics of an op-amp as discussed in Sec. 2.3.

A differential amplifier of the type shown in Fig. 2.11 (a) can be used in four different configurations depending upon the number of input signals used and the way output is taken. These four configurations are:

 
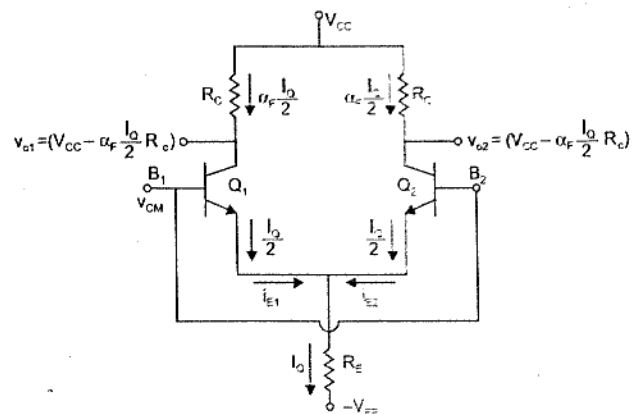


Fig. 2.11 (a) The basic differential amplifier

(i) Differential-input, differential-output or Dual-input balanced-output (ii) Differential-input, single ended-output (iii) Single-input, differential-output (iv) Single-input, single ended-output.

If signal is applied to both the inputs, then it is differential input or Dual input and the difference of signals applied to the two inputs gets amplified. In many applications a single input is only used as we shall see later. Similarly, if output voltage is measured between two collectors then it is a differential output. This is also referred to as a balanced output, as both collectors are at the same d.c. potential w.r.t. ground. We will come across these various configuration as we proceed further.

To understand the working of a differential amplifier first consider the case when both the bases B_1 and B_2 are joined together and connected to a voltage v_{CM} called the common-mode voltage. Thus in Fig. 2.11 (b), $v_1 = v_2 = v_{CM}$. As both the transistors Q_1 and Q_2 are forward-

Fig. 2.11 (b) The differential pair with a common-mode input signal v_{CM}

biased and matched, due to symmetry of the circuit, the current I_Q divides equally through transistors Q_1 and Q_2 , that is, $i_{E1} = i_{E2} = I_Q/2$. The collector currents i_{C1} and i_{C2} through the resistors R_C is $\alpha_F I_Q/2$. The voltage at each of the collectors will be $V_{CC} - \alpha_F \frac{I_Q}{2} R_C$ and, therefore the difference of the voltage between the two collectors ($v_{O1} - v_{O2}$) will be zero. Now, even if the value of v_{CM} is changed, the voltage across the collectors will not change. Thus, the differential pair does not respond to (or rejects) the common-mode input signals. Now, consider the case when the voltage v_2 is made zero and voltage $v_1 = 1$ V (say) as shown in Fig. 2.11 (c). It can be seen that the transistor Q_1 will conduct and transistor Q_2 will be off. The entire current I_Q will now flow through Q_1 . Since Q_1 is on, the voltage at its emitter will be 0.3 V. This will make emitter-base junction of Q_2 reverse-biased and thus Q_2 will be off. The collector voltages will be $v_{O1} = V_{CC} - \alpha_F I_Q R_C$ and $v_{O2} = V_{CC}$.

 


Fig. 2.11 (c) The differential pair with 'large' differential input signal

If, however, $v_1 = -1$ V and $v_2 = 0$ V, it can be seen that Q_1 will be off and the entire current I_Q will flow through Q_2 . The voltage at the common emitter point 'E' will now be -0.7 V which makes Q_1 off and Q_2 on. The collector voltages will be $v_{O1} = V_{CC}$ and $v_{O2} = V_{CC} - \alpha_F I_Q R_C$.

Thus, we see that the differential pair responds only to the difference mode signals and rejects common-mode signals. In the next section, we discuss the transfer characteristics of the circuit to show that a differential pair can be used either as a switch or a linear amplifier.

2.4.2 Transfer Characteristics

In Fig. 2.11 (a) collector currents i_{C1} and i_{C2} for transistors Q_1 and Q_2 biased in the forward-active mode may be given by (neglecting reverse saturation currents of the collector base junction)

$$i_{C1} = \alpha_F I_{ES} e^{v_{BE1}/V_T} \quad (2.42)$$

$$i_{C2} = \alpha_F I_{ES} e^{v_{BE2}/V_T} \quad (2.43)$$

Here, I_{ES} is the reverse saturation current of emitter-base junction and V_T is volts equivalent of temperature.

From Eqs. (2.42) and (2.43), we may write

$$\frac{i_{C1}}{i_{C2}} = e^{(v_{BE1} - v_{BE2})/V_T} \quad (2.44)$$

We may also write KVL for the loop containing two emitter-base junctions as

$$v_1 - v_{BE1} + v_{BE2} - v_2 = 0$$

or

$$v_{BE1} - v_{BE2} = v_1 - v_2 = v_d$$

where, v_d is the difference of two input voltages.

Also in Fig. 2.11 (a)

$$\begin{aligned} I_Q &= i_{E1} + i_{E2} = \frac{i_{C1}}{\alpha_F} + \frac{i_{C2}}{\alpha_F} \\ &= \frac{i_{C1}}{\alpha_F} \left(1 + \frac{i_{C2}}{i_{C1}} \right) \end{aligned} \quad (2.45)$$

Using Eqs. (2.44) and (2.45) and solving for i_{C1} and i_{C2} , gives

$$i_{C1} = \frac{\alpha_F I_Q}{1 + e^{-v_d/V_T}} \quad (2.46)$$

$$i_{C2} = \frac{\alpha_F I_Q}{1 + e^{v_d/V_T}} \quad (2.47)$$

From Eqs. (2.46) and (2.47), the normalised transfer characteristics ($i_{C1}I_Q$ vs v_d/V_T assuming $\alpha_F = 1$) for a differential amplifier are obtained as shown in Fig. 2.12.

 


Fig. 2.12 Normalised transfer characteristics for the differential pair

The following important points are observed from the transfer characteristics:

1. For $v_d > 4V_T$ (~ 100 mV), $i_{C1} = \alpha_F I_Q$ and $i_{C2} = 0$, Hence

$$v_{o1} = V_{CC} - \alpha_F I_Q R_C$$

and

$$v_{o2} = V_{CC}$$

By proper choice of R_C , v_{o1} can be made very small.

2. For $v_d < -4V_T$, $i_{C1} = 0$ and $i_{C2} = \alpha_F I_Q$. Hence $v_{o1} = V_{CC}$ and v_{o2} is negligible. Thus, for $4V_T < v_d < -4V_T$, we can say that a differential amplifier can be made to function as a switch.
3. The differential amplifier functions as a very good limiter for $v_d > \pm 4V_T$.
4. DA can function as an automatic gain control (AGC) by varying I_Q .
5. Between the values $-2V_T \leq v_d \leq 2V_T$, DA functions as a linear amplifier.

2.4.3 Low Frequency Small Signal Analysis of Differential Amplifier

An ideal dual-input balanced-output differential amplifier as shown in Fig. 2.11 (a), should amplify only the differential signal at the two inputs, and reject the signal common to these inputs. As transistors Q_1 and Q_2 are a matched pair of transistors, thus any unwanted signal, such as noise or hum pick up which is common to both the inputs would get rejected. However in a practical case transistors Q_1 and Q_2 are not equally matched and output does appear even when same voltage is applied to the two input terminals. In this section, we will discuss how to compute the small signal differential mode gain, A_{DM} and common-mode gain A_{CM} . These expressions help in finding the figure of merit CMRR of the differential amplifier and hence the ways to improve it.

The a.c. analysis of the differential amplifier can be performed either by using hybrid- π model or h -parameter model. Both the approaches have been dealt with.

Differential-mode Gain, A_{DM}

In Fig. 2.11 (a) for $v_1 = v_2$, the current I_Q divides equally into the two transistors Q_1 and Q_2 because of the symmetry of the circuit. However, if v_1 is now increased by an incremental voltage (small signal) $v_d/2$ and v_2 is decreased by $v_d/2$, it can be seen that the differential amplifier is being fed by differential small signal v_d . The common mode small signal is naturally zero. The collector current i_{C1} will now increase by an incremental current i_c and i_{C2} will decrease by an equal amount. The sum of total currents in transistors Q_1 and Q_2 however remains constant as constrained by the constant current I_Q . As there is no change of current through R_E , the voltage V_E at the common emitter point 'E' remains constant. Thus, for small signal analysis, the common emitter point 'E' can be considered to be at ground potential. Figure 2.13 (a) shows the small signal equivalent circuit of the differential amplifier under the differential input signal conditions described above. It may be noted that for differential amplifier to behave as a linear amplifier, the differential signal $v_d \leq 2V_T$ (that is, v_d should be smaller than about 50 mV) as discussed in the transfer characteristics (section 2.4.2).

 


Fig. 2.13 (a) Differential amplifier with differential input signal v_d

Analysis

(i) Using Hybrid- π Model

Since the performance of two sides of the differential amplifier is identical, we need to analyze only one side of the differential amplifier called differential-half circuit. Figure 2.13 (b) shows a single stage CE transistor amplifier fed by a small signal voltage $v_d/2$ and its a.c. equivalent circuit using hybrid- π model is shown in Fig. 2.13 (c).

From Fig. 2.13 (c),

$$\frac{v_{o1}}{v_d/2} = -g_m R_C$$

$$\text{or } \frac{v_{o1}}{v_d} = -\frac{1}{2} g_m R_C \quad (2.48)$$

 


Fig. 2.13 (b) Differential mode half circuit (c) ac-equivalent circuit using hybrid- π model

Similarly, it can be seen that

$$\frac{v_{o2}}{v_d} = \frac{1}{2} g_m R_C \quad (2.49)$$

The output voltage signal of a differential amplifier can be taken either differentially (i.e. between the two collectors) or single-ended (i.e. between one collector and ground). If the output is taken differentially, then the differential-mode gain, A_{DM} is given by

$$A_{DM} = \frac{v_{o1} - v_{o2}}{v_d} = -g_m R_C \quad (\text{differential-input, differential-output}) \quad (2.50)$$

On the other hand, if output is single-ended, (say between collector of transistor Q_1 and ground), then the differential-mode gain A_{DM} is given by

$$A_{DM} = \frac{v_{o1}}{v_d} = -\frac{1}{2} g_m R_C \quad (\text{differential-input, single-ended output}) \quad (2.51(a))$$

$$\text{and } \frac{v_{o2}}{v_d} = \frac{1}{2} g_m R_C \quad (2.51(b))$$

In the above analysis, we have not included the output resistance r_o of the transistor. If r_o is included, Eq. (2.50) will modify to

$$A_{DM} = -g_m (R_C \parallel r_o)$$

(ii) Using 'h' Parameters

The a.c. equivalent circuit for Fig. 2.13 (b) using approximate h -parameter model is shown in Fig. 2.13 (d).

 


Fig. 2.13 (d) Small signal equivalent circuit of differential half circuit using h -parameter model

From Fig. 2.13 (d),

$$v_{o1} = -i_c R_C = -h_{fe} i_b R_C$$

$$\text{and } \frac{v_d}{2} = i_b h_{ie}$$

Therefore, differential mode gain, A_{DM} is given by

$$A_{DM} = \frac{v_{o1}}{v_d} = -\frac{1}{2} \frac{h_{fe}}{h_{ie}} R_C \quad (\text{Single-ended output}) \quad (2.52 (a))$$

Similarly, we may write

$$A_{DM} = \frac{v_{o2}}{v_d} = \frac{1}{2} \frac{h_{fe}}{h_{ie}} R_C \quad (\text{Single-ended output}) \quad (2.52 (b))$$

If the output is taken differentially between the two collectors, then

$$A_{DM} = \frac{v_{o1} - v_{o2}}{v_d} = -\frac{h_{fe} R_C}{h_{ie}} \quad (\text{differential-output}) \quad (2.52 (c))$$

In the above analysis, the source resistance R_s has not been taken into account.

Common-mode gain, A_{CM}

Now, consider the case when v_1 and v_2 both are increased by an incremental voltage v_c . The differential signal v_d now is zero and common-mode signal is v_c . Both the collector currents i_{C1} and i_{C2} will increase by an incremental current i_c . The current through R_E now increases by $2i_c$. The voltage, V_E at emitter node is now increased by $2i_c R_E$ and no longer constant. In order to draw the common mode half circuit, replace resistance R_E by $2R_E$ as shown in Fig. 2.14 (a). The common-mode gain, A_{CM} is calculated from the small-signal hybrid- π equivalent model shown in Fig. 2.14 (b). It can be seen,

$$A_{CM} = \frac{v_{o1}}{v_c} = \frac{v_{o2}}{v_c} = \frac{-\beta_0 R_C}{r_x + 2(1 + \beta_0)R_E} \quad (2.53 (a))$$

For $\beta_0 \gg 1$,

β_0 is the small signal CE current gain and is same as h_{fe} .

 


Fig. 2.14 (a) Common-mode half circuit (b) ac equivalent circuit using hybrid- π model

$$A_{CM} = \frac{-g_m R_C}{1 + 2g_m R_E} \approx -\frac{R_C}{2R_E} \quad (2.53 \text{ (b)})$$

It can be seen that, if the output is taken differentially, then the output voltage $v_{o1} - v_{o2}$ will be zero and the common-mode gain will be zero. In this analysis, we have assumed that the circuit is perfectly symmetrical. However, in practical circuits, it will not be so, and the differential output voltage will not be exactly zero. If the output is taken single ended, the common-mode gain will be finite and given by Eqs. (2.53 (a)) and (2.53 (b)).

The common mode gain, A_{CM} , using h -parameter model can be easily computed as

$$A_{CM} = \frac{v_{o1}}{v_c} = \frac{-h_{re} R_C}{h_{ie} + (1 + h_{ie}) 2R_E} \quad (2.54)$$

The common-mode rejection ratio (CMRR) is defined as

$$CMRR = \frac{|A_{DM}|}{|A_{CM}|}$$

For differential-input, differential-output, using Eqs. (2.50) and (2.53 b), we obtain

$$\begin{aligned} CMRR &\approx \frac{g_m R_C (1 + 2g_m R_E)}{g_m R_C} \\ &= 1 + 2g_m R_E \\ &\approx 2g_m R_E \end{aligned} \quad (2.55)$$

Output for Arbitrary Signals

In the previous analysis, we have assumed that either common mode signals (v_c) or a differential mode signals ($\frac{v_d}{2}$) are applied to the two input terminals. However, in a practical situation it will not be so. If, say, any arbitrary signals v_1 and v_2 are applied at the inputs of transistors Q_1 and Q_2 in Fig. 2.11(a), then we can represent these signals by the sum and difference of common mode component v_{CM} ($= v_c$) and differential mode component

$$v_{DM} \left(= \frac{v_d}{2} \right) \text{ as}$$

and such that,

$$v_1 = v_{CM} + v_{DM}$$

$$v_2 = v_{CM} - v_{DM}$$

$$v_{DM} = \frac{v_1 - v_2}{2} \quad (2.56(a))$$

$$v_{CM} = \frac{v_1 + v_2}{2} \quad (2.56(b))$$

The output voltage v_{o1} and v_{o2} at the output of transistor Q_1 and Q_2 in Fig. 2.11(a) are given by

$$v_{o1} = A_{DM} v_{DM} + A_{CM} v_{CM} \quad (2.57(a))$$

and
$$v_{o2} = -A_{DM} v_{DM} + A_{CM} v_{CM} \quad (2.57(b))$$

Example 2.6

Differential amplifier shown in Fig. 2.11 (a) uses a transistor with $\beta = 200$ and is biased at $I_{CQ} = 100 \mu A$. Determine the value of R_C and R_E if $|A_{DM}| = 500$ and $CMRR = 80 \text{ dB}$.

Solution

Given $I_{CQ} = 100 \mu A$

We know that $g_m = \frac{I_{CQ}}{V_T} = \frac{100 \times 10^{-6}}{25 \times 10^{-3}} = 4 \text{ mS}$ [for $V_T = 25 \text{ mV}$]

Using Eq. (2.50),

$$A_{DM} = -g_m R_C \quad [\text{For differential output}]$$

$$\therefore R_C = \frac{-A_{DM}}{g_m} = \frac{500}{4 \text{ mS}} = 125 \text{ k}\Omega \quad \text{Ans.}$$

As $CMRR = 80 \text{ dB}$,

$$\therefore CMRR = \log^{-1} \left(\frac{80}{20} \right) = 10^4$$

Using Eq. (2.55),

$$CMRR = 1 + 2g_m R_E = 1 + 2 \times 4 \times R_E$$

Solving for R_E , we get

$$R_E = 1.25 \text{ M}\Omega \quad \text{Ans.}$$

Example 2.7

In the basic differential amplifier of Fig. 2.11(a), Given: $R_C = 2 \text{ k}\Omega$; $R_E = 4.3 \text{ k}\Omega$, $V_{CC} = |V_{EE}| = 5 \text{ V}$; $\beta_0 = 200$, $V_{BE} = 0.7 \text{ V}$.

Determine:

- (i) For $V_1 = V_2 = 0$, that is for both the inputs grounded, the values of quiescent currents and voltages, I_{BQ} , I_{CQ} , V_{o1} , V_{o2} , V_{CEQ}
- (ii) A_{DM} , A_{CM} and $CMRR$.

Solution

(i) For $V_1 = V_2 = 0$, applying KVL for the base emitter loop, we may write,

$$V_{BE} + 2(1 + \beta_0)I_{BQ}R_E - V_{EE} = 0$$

$$\text{or } I_{BQ} = \frac{V_{EE} - V_{BE}}{2(1 + \beta_0)R_E} = \frac{5V - 0.7V}{2(1 + 200)4.3 \text{ k}\Omega}$$

$$= .0024 \text{ mA} = 2.4 \mu\text{A}$$

$$\therefore I_{CQ} = 200 \times I_{BQ} = 0.48 \text{ mA}$$

$$V_{o1} = V_{o2} = 5V - 2 \text{ k}\Omega \times 0.48 \text{ mA} \quad (\text{due to symmetry})$$

$$= 5V - .96V = 4.04V$$

$$V_{CEQ} = V_C - V_E$$

$$= V_{o1} - (-V_{BE}) = V_{o1} + V_{BE}$$

$$= 4.04V + 0.7V = 4.74V$$

$$(ii) \quad g_m = \frac{I_{CQ}}{V_T} = \frac{0.48 \text{ mA}}{25 \text{ mV}} = .0192 \text{ S} = 19.2 \text{ mS}$$

$$r_\pi = \frac{\beta_0}{g_m} = \frac{200}{19.2 \text{ mS}} = 10.4 \text{ k}\Omega$$

Using Eq. (2.50),

$$A_{DM} = -g_m R_C$$

$$= -19.2 \text{ mS} \times 2 \text{ k}\Omega = -38.4$$

From Eq. (2.53a)

$$A_{CM} = \frac{-\beta_0 R_C}{r_\pi + 2(1 + \beta_0)R_E}$$

$$= \frac{-200 \times 2 \text{ k}\Omega}{10.4 \text{ k}\Omega + 2(1 + 200)4.3 \text{ k}\Omega} = -0.23$$

$$\text{CMRR} = \frac{A_{DM}}{A_{CM}} = \frac{-38.4}{-0.23} = 166.9 = 44.4 \text{ dB}$$

Example 2.8

In the differential amplifier designed in Example 2.5, the following inputs are applied:

$$v_1 = 15 \sin 2\pi (60t) + 5 \sin 2\pi (1000t) \text{ mV}$$

$$v_2 = 15 \sin 2\pi (60t) - 5 \sin 2\pi (1000t) \text{ mV}$$

Here, the signal at 60 Hz is the interference signal and the signal to be processed is at 1 kHz. Determine the output voltages v_{o1} and v_{o2} .

Solution

We know from Example 2.6

$$g_m = 4 \text{ mS}; R_C = 125 \text{ k}\Omega, R_E = 1.25 \text{ k}\Omega$$

$$\text{and } r_\pi = \frac{\beta_0}{g_m} = \frac{200}{4 \text{ mS}} = 50 \text{ k}\Omega$$

Given, $A_{DM} = -500$,

We compute A_{CM} from Eq. (2.53(a))

$$A_{CM} = \frac{-\beta_0 R_C}{2(1 + \beta_0)R_E + r_\pi} = \frac{-200 \times 125 \text{ k}\Omega}{2(1 + 200)1250 \text{ k}\Omega + 50 \text{ k}\Omega} = -0.05$$

From Eqs. (2.56(a)) and (2.56(b))

$$v_{DM} = \frac{v_1 - v_2}{2} = 5 \sin 2\pi (1000t)$$

$$\text{and } v_{CM} = \frac{v_1 + v_2}{2} = 15 \sin 2\pi (60t)$$

From Eqs. (2.57a) and (2.57b), we get

$$v_{o1} = -500[5 \sin 2\pi (1000t)] - 0.05[15 \sin 2\pi (60t)]$$


$$= -2500 \sin 2\pi (1000t) - 0.75 \sin 2\pi (60t) \text{ mV}$$

$$\text{and } v_{o2} = -(-500)[5 \sin 2\pi (1000t)] - 0.05[15 \sin 2\pi (60t)]$$

$$= +2500 \sin 2\pi (1000t) - 0.75 \sin 2\pi (60t) \text{ mV}$$

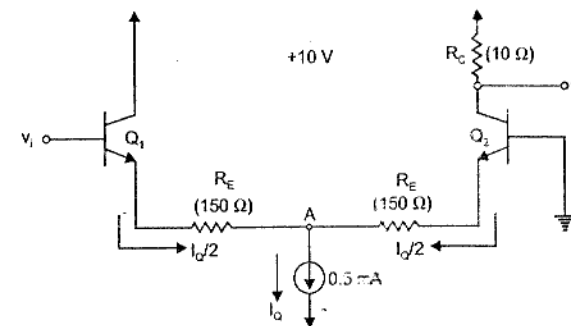Example 2.9

For the differential amplifier shown in Fig. (i) find the differential voltage gain. Given $\beta_0 = 100$



(i) Circuit for Example 2.9

Solution

Note that the circuit is a differential amplifier with single ended output taken at the collector of Q_2 . Also there is a 150Ω resistor between emitter and terminal A.

$$I_{CQ} = \frac{I_Q}{2} = \frac{0.5\text{mA}}{2} = 0.25\text{mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.25\text{mA}}{25\text{mV}} = \frac{1}{100}\text{S}$$

$$\text{and } r_\pi = \frac{\beta_0}{g_m} = \frac{100}{1/100} = 10\text{ k}\Omega$$

The differential mode gain for a single stage is found from the equivalent circuit shown in Fig. (ii) and can be written as

$$A_{DM} = \frac{1}{2} \left[\frac{\beta_0 R_C}{r_\pi + (1 + \beta_0) R_E} \right] \quad [\text{Eq. 2.51(b) modified on account of } R_E]$$

$$= \frac{1}{2} \left[\frac{100 \times 10\text{ k}\Omega}{10\text{ k}\Omega + 101 \times 150\Omega} \right] = 40\text{ V/V}$$

Note that the sign of A_{DM} is positive because the output is taken at the collector of Q_2 whereas input is applied at the base of Q_1 .

2.4.4 Circuits for Improving CMRR

For CMRR to be large, A_{CM} should be as small as possible. From Eq. (2.54), it can be seen that $A_{CM} \rightarrow 0$ as $R_E \rightarrow \infty$. There are, however, practical limitations on the magnitude of R_E because of the quiescent dc voltage across it. If R_E is made large, the emitter supply V_{EE} will also have to be increased in order to maintain the proper quiescent current. And if the operating currents of the transistors are allowed to decrease, then h_{fe} will decrease, thereby decreasing h_{fe} too. This too will decrease the common mode rejection ratio.

The use of a constant current bias in place of R_E is found to be a practical solution to the problem discussed above. In Fig. 2.15, R_E is replaced by a constant current transistor circuit in which R_1 , R_2 and R_3 can be adjusted to give the same quiescent conditions for the transistors Q_1 and Q_2 as in the original circuit of Fig. 2.11 (a). The modified circuit presents a very high effective emitter resistance R_E even for very small values of R_3 . Typically, R_E is hundreds of $\text{k}\Omega$ even if R_3 is as small as $1\text{ k}\Omega$.

Let us calculate the current I_Q and verify that the emitter circuit really behaves as a constant current source. Writing KVL for the base circuit of Q_3 , we get

$$V_{BE3} + I_3 R_3 = V_D + (V_{EE} - V_D) \frac{R_2}{R_1 + R_2} \quad (2.58)$$

Here V_D represents the drop across the diode D. If the base current is neglected, then

$$I_Q \approx I_3 = \frac{1}{R_3} \left(\frac{V_{EE} R_2}{R_1 + R_2} + \frac{V_D R_2}{R_1 + R_2} - V_{BE3} \right) \quad (2.59)$$

By proper choice of resistors R_1 and R_2 , it is possible to set,

$$\frac{V_D R_2}{R_1 + R_2} = V_{BE3} \quad (2.60)$$

$$\text{Then, } I_Q \approx \frac{1}{R_3} \left(\frac{V_{EE} R_2}{R_1 + R_2} \right) \quad (2.61)$$

So, it can be seen that the current I_Q will be essentially constant as it does not depend upon signal voltages v_1 and v_2 .


What is the use of the diode D in this circuit? The diode D makes I_Q independent of temperature. We know that V_{BE3} decreases approximately by $2.5\text{ mV}/^\circ\text{C}$ and the diode D also has the same temperature dependence. Hence, the two variations cancel each other and I_Q becomes independent of temperature. It is usually difficult to satisfy Eq. (2.60) with a single diode in the circuit of Fig. 2.15 as V_D and V_{BE3} have almost the same value. Hence two diodes are normally used for V_D .

With I_Q constant, it can be shown that the common-mode gain is zero, so that the circuit provides very high CMRR. Under quiescent conditions (no ac signal) the current I_Q gets divided equally in identical transistors Q_1 and Q_2 and $I_{C1} = I_{C2} = I_{Q2}$. Now if the same signal ($v_1 = v_2$) is applied to both the inputs, there will still be no change in the collector currents i_{C1} and i_{C2} as I_Q is constant. Thus the small signal current i_c flowing through the load resistor R_C is zero resulting in zero output voltage.

Thus we can state that a diff-amp, if supplied by a constant current bias gives very high CMRR. The constant current circuit of the type shown in Fig. 2.15 is used in Motorola MC1530 (Fig. 2.21). A more commonly used IC op-amp $\mu\text{A} 741$ uses a different type of constant current source which is very simple and uses less number of components. This circuit is called current mirror and offers extremely large resistance under a.c. conditions, thereby providing a high value of CMRR.

Constant Current Source (Current Mirror)

A constant current source makes use of the fact that for a transistor in the active mode of operation, the collector current is relatively independent of the collector voltage. In the basic circuit shown in Fig. 2.16 transistors Q_1 and Q_2 are matched as the circuit is fabricated using IC technology. It may be noted that bases and emitter of Q_1 and Q_2 are tied together and thus have the same V_{BE} . In addition, transistor Q_1 is connected as a diode by shorting its collector to base.

 

(ii) Equivalent circuit

 


Fig. 2.15 Differential amplifier using constant current bias

The input current I_{ref} flows through the diode-connected transistor Q_1 and thus establishes a voltage across Q_1 . This voltage in turn appears between the base and emitter of Q_2 . Since Q_2 is identical to Q_1 , the emitter current of Q_2 will be equal to emitter current of Q_1 which is approximately equal to I_{ref} . Thus, we can say that as long as Q_2 is maintained in the active region, its collector current $I_{C2} = I_o$ will be approximately equal to I_{ref} . Since the output current I_o is a reflection or mirror of the reference current I_{ref} , the circuit is often referred to as a current mirror.

This mirror effect is however, valid only for large values of β . To study the effect of β on the operation of the current mirror circuit, we analyze it further.

Analysis

The collector currents I_{C1} and I_{C2} for transistors Q_1 and Q_2 can be approximately expressed as

$$I_{C1} \cong \alpha_F I_{ES} e^{V_{BE1}/V_T} \quad (2.62)$$

$$I_{C2} \cong \alpha_F I_{ES} e^{V_{BE2}/V_T} \quad (2.63)$$

From Eqs. (2.62) and (2.63), we may write

$$\frac{I_{C2}}{I_{C1}} = e^{(V_{BE2} - V_{BE1})/V_T} \quad (2.64)$$

Since $V_{BE1} = V_{BE2}$, we obtain

$$I_{C2} = I_{C1} = I_C = I_o$$

Also since both the transistors are identical, $\beta_1 = \beta_2 = \beta$.

KCL at the collector of Q_1 gives

$$I_{ref} = I_{C1} + I_{B1} + I_{B2} \quad (2.65)$$

$$= I_{C1} + \frac{I_{C1}}{\beta_1} + \frac{I_{C2}}{\beta_2} = I_C \left(1 + \frac{2}{\beta} \right) \quad (2.66)$$

Solving Eq. (2.66), I_C may be expressed as

$$I_C = \frac{\beta}{\beta + 2} I_{ref} \quad (2.67)$$

where I_{ref} from Fig. 2.16 can be seen to be

$$I_{ref} = \frac{V_{CC} - V_{BE}}{R_1} \cong \frac{V_{CC}}{R_1} \quad (\text{as } V_{BE} = 0.7 \text{ V is small}) \quad (2.68)$$

From Eq. (2.67), for $\beta \gg 1$, $\beta/(\beta + 2)$ is almost unity and the output current I_o is equal to the reference current, I_{ref} which for a given R_1 is constant. Typically I_o varies by about 3% for $50 \leq \beta \leq 200$.

* $\beta = \beta_F$ and is the large signal CE current gain.

 


Fig. 2.16 The basic BJT current mirror

It is possible to obtain current transfer ratio other than unity simply by controlling the area of the emitter-base junction (EBJ) of the transistor Q_2 . For example, if the area of EBJ of Q_2 is 4 times that of Q_1 , then

$$I_o = 4 I_{ref}$$

The output resistance of the current source is the output resistance, r_o , of Q_2 ,

$$R_o = r_{o2} = \frac{V_A}{I_o} \cong \frac{V_A}{I_{ref}} \quad [V_A \text{ is the Early voltage}]$$

The circuit however operates as a constant current source as long as Q_2 remains in the active region. From the volt-ampere characteristics of Q_2 shown in Fig. 2.17, it can be seen that for $V_{CE2} < 0.3 \text{ V}$, Q_2 is saturated. For $V_{CE2} > 0.3 \text{ V}$, transistor operates in the active region and I_{C2} is essentially constant. The slight increase in I_{C2} is due to Early effect. The $1/\text{slope}$ of the curve in this region gives the output resistance r_o of the current source. For all practical purposes, early voltage may be assumed to be infinite, so that $r_o \rightarrow \infty$ and I_{C2} is constant.

 


Fig. 2.17 Volt-ampere characteristics for transistor Q_2

Example 2.10

The current mirror of Fig. 2.16 is to provide a 1.0 mA current with $V_{CC} = 10 \text{ V}$. Assume $\beta = 125$ and $V_{BE} = 0.7 \text{ V}$. Determine (a) the value of R_1 (b) value of R_1 for $I_C = 10 \mu\text{A}$.

Solution

(a) From Eq. (2.67), we have

$$1.0 \text{ mA} = \frac{125}{125 + 2} \times \frac{10 \text{ V} - 0.7 \text{ V}}{R_1}$$

$$R_1 = 9.15 \text{ k}\Omega$$

(b) Again using Eq. (2.67), the value of R_1 is found to be

$$R_1 = 915 \text{ k}\Omega$$

Widlar Current Source

The basic current mirror of Fig. 2.16 has a limitation. Whenever we need low value current source as in Example 2.6 part (b), the value of the resistance R_1 required is sufficiently high and can not be fabricated economically in IC circuits. In Fig. 2.18 is shown a Widlar current source which is particularly suitable for low value of currents. The circuit differs from the basic current mirror only in the resistance R_E that is included in the emitter lead of Q_2 . It can be seen that due to R_E , the base-emitter voltage V_{BE2} is less than V_{BE1} and consequently current I_0 is smaller than I_{C1} .

The ratio of collector currents I_{C1} and I_{C2} using Eqs. 2.62) and 2.63) is given by

$$\frac{I_{C1}}{I_{C2}} = e^{(V_{BE1} - V_{BE2})/V_T} \quad (2.69)$$

Taking natural logarithm of both sides, we get

$$V_{BE1} - V_{BE2} = V_T \ln \left(\frac{I_{C1}}{I_{C2}} \right) \quad (2.70)$$

Writing KVL for the emitter base loop

$$V_{BE1} = V_{BE2} + (I_{B2} + I_{C2})R_E \quad (2.71)$$

$$\text{or} \quad V_{BE1} - V_{BE2} = (1/\beta + 1)I_{C2}R_E \quad (2.72)$$

From Eqs. (2.70) and (2.72), we obtain

$$\left(\frac{1}{\beta} + 1 \right) I_{C2} R_E = V_T \ln \frac{I_{C1}}{I_{C2}} \quad (2.73)$$

$$\text{or} \quad R_E = \frac{V_T}{\left(1 - \frac{1}{\beta} \right) I_{C2}} \ln \frac{I_{C1}}{I_{C2}} \quad (2.74)$$

A relation between I_{C1} and the reference current I_{ref} is obtained by writing KCL at the collector point of Q_1 (node 'a')

$$I_{ref} = I_{C1} + I_{B1} + I_{B2} \quad (2.75)$$

$$= I_{C1} \left(1 + \frac{1}{\beta} \right) + \frac{I_{C2}}{\beta} \quad (2.76)$$

(Assuming $\beta_2 = \beta_1 = \beta$ for identical transistors)

 


Fig. 2.18 Widlar current source

In the Widlar current source $I_{C2} \ll I_{C1}$, therefore the term I_{C2}/β may be neglected in Eq. (2.76).

$$\text{Thus} \quad I_{ref} \cong I_{C1} \left(1 + \frac{1}{\beta} \right) \quad (2.77)$$

$$\text{or} \quad I_{C1} = \frac{\beta}{\beta + 1} I_{ref} \quad (2.78)$$

$$\text{where} \quad I_{ref} = \frac{V_{CC} - V_{BE}}{R_1} \quad (2.79)$$

$$\text{For } \beta \gg 1, \quad I_{C1} \cong I_{ref} \quad (2.80)$$

The design and advantages of Widlar current source are illustrated in the following example:

Example 2.11

Design a Widlar current source for generating a constant current $I_0 = 10 \mu\text{A}$. Assume $V_{CC} = 10 \text{V}$, $V_{BE} = 0.7 \text{V}$, $\beta = 125$. Use $V_T = 25 \text{mV}$.

Solution

For the Widlar current source of Fig. 2.18, we must first decide a suitable value for I_{ref} . If we choose $I_{ref} = 1 \text{mA}$, then, R_1 is given by

$$R_1 = \frac{10 \text{V} - 0.7 \text{V}}{1 \text{mA}} = 9.3 \text{k}\Omega$$

The value of R_E is determined from Eq. (2.74)

$$R_E = \frac{0.025}{\left(1 + \frac{1}{125} \right) 10 \times 10^{-6}} \ln \left(\frac{1 \text{mA}}{10 \mu\text{A}} \right) = 11.5 \text{k}\Omega$$

It is clearly seen that Widlar circuit allows the generation of small currents using relatively small resistors.

Sometimes, it is convenient to use emitter resistances in both the transistors Q_1 and Q_2 as shown in Fig. 2.19. If $R_1 = R_2$ the currents $I_{C1} = I_{C2}$. The same circuit can also be used to provide different currents in Q_1 and Q_2 , as we shall now see.

Analysis

Rewriting Eq. (2.64) as

$$V_{BE2} - V_{BE1} = V_T \ln \frac{I_{C2}}{I_{C1}} \quad (2.81)$$

Writing KVL in the base-emitter loop

$$V_{BE2} - V_{BE1} = I_{C1}R_1 - I_{C2}R_2 \quad (2.82)$$

(Neglecting base current)

$$\text{From Eqs. (2.81) and (2.82),} \quad I_{C1}R_1 - I_{C2}R_2 = V_T \ln \frac{I_{C2}}{I_{C1}} \quad (2.83)$$

 


Fig. 2.19 A current mirror with magnification ($I_{C2}/I_{C1} \cong R_1/R_2$)

$$\frac{I_{C2} R_2}{I_{C1} R_1} = 1 - \frac{V_T}{I_{C1} R_1} \ln \frac{I_{C2}}{I_{C1}} \quad (2.84)$$

$$\frac{I_{C2}}{I_{C1}} = \frac{R_1}{R_2} \left(1 - \frac{V_T}{I_{C1} R_1} \ln \frac{I_{C2}}{I_{C1}} \right) \quad (2.85)$$

For the range $0.1 < \frac{I_{C2}}{I_{C1}} < 10$, we can assume $\frac{I_{C2}}{I_{C1}} \approx \frac{R_1}{R_2}$. Thus even large ratios (say 10) is easily obtained by the modified circuit.

Current Repeaters

The basic current mirror of Fig. 2.16 can be used to source current to more than one load. Such a circuit is called current repeater and is shown in Fig. 2.20. If all the transistors are identical, then the current $I_C = I_{C1} = \dots = I_{CN} \equiv I_{ref}$.

 


Fig. 2.20 A current repeater to source current to N transistors Q_1, Q_2, \dots, Q_N

It can be seen from Fig. 2.20 at node 'a'

$$I_{ref} = I_C + I_B + NI_B \quad (\text{Assuming identical transistors}) \quad (2.86)$$

$$\begin{aligned} &= I_C + \frac{(1+N)}{\beta} I_C \\ &= I_C \left(1 + \frac{(1+N)}{\beta} \right) \end{aligned} \quad (2.87)$$

$$\text{Thus } I_C = I_{ref} \frac{\beta}{\beta + 1 + N} \quad (2.83)$$

It is possible to achieve different value of $I_{C1}, I_{C2}, \dots, I_{CN}$ by scaling the emitter area of transistors Q_1, Q_2, \dots, Q_N . The same can also be achieved by using emitter resistance as in the Widlar current source.

Example 2.12

For the circuit shown in Fig. 2.21 determine I_{C1}, I_{C2} , and I_{C3} . Assume $\beta = 125$

 


Fig. 2.21 Circuit for Example 2.12

Solution

$$I_{ref} = \frac{9V - 0.7V}{30 \text{ k}\Omega} = 0.277 \text{ mA}$$

Also at node 'a'

$$\begin{aligned} I_{ref} &= I_C + 3I_B \quad (\text{Assume } I_{B3} \text{ of Widlar source negligible}) \\ &= I_C \left(1 + \frac{3}{\beta} \right) \\ I_C &= I_{ref} \left(\frac{\beta}{3 + \beta} \right) \end{aligned}$$

Putting the values and solving, we get

$$I_{C1} = I_{C2} = 0.271 \text{ mA}$$

Calculate I_{C3} , using Eq. (2.74) gives

$$1.94 = \frac{0.025}{I_{C3} \left(1 + \frac{1}{125} \right)} \ln \frac{0.271}{I_{C3}}$$

Solving the transcendental equation by trial and error, we obtain

$$I_{C3} = 0.0287 \text{ mA}$$

Improved Current Source Circuits

A good current source must meet two requirements. The first is that the output current, I_o , should not be dependent upon β and secondly the output resistance of the current source should be very high. The need for high output resistance current source can be seen because the common-mode gain of the differential amplifier (used as basic building block in op-amps) can only be reduced by using high resistance current sources. Also, all differential amplifiers invariably use current source as a load. Thus to obtain high voltage gain a large output resistance load is required. Now, we discuss two circuits that exhibit reduced dependence on β or increased output resistance.

A Current Source with Gain

The circuit shown in Fig. 2.22 includes a transistor Q_3 whose emitter current supplies the base currents of Q_1 and Q_2 . The expression for the source current $I_o = I_{C2}$ can be derived by writing KCL at node 'a'

$$\begin{aligned} I_{\text{ref}} &= I_{C1} + I_{B3} \\ &= I_{C1} + \frac{I_{E3}}{1+\beta} \end{aligned} \quad (2.89)$$

Also
Thus,

$$I_{E3} = I_{B1} + I_{B2} = 2I_B \quad (\text{since } Q_1 \text{ and } Q_2 \text{ are identical})$$

$$I_{\text{ref}} = I_{C1} + \frac{2I_B}{1+\beta} \quad (2.90)$$

$$= I_C + \frac{2I_C}{\beta(1+\beta)} = I_C \left(1 + \frac{2}{\beta(1+\beta)} \right)$$

$$\text{or} \quad I_o = I_C = I_{\text{ref}} \frac{\beta(1+\beta)}{\beta^2 + \beta + 2} \quad [I_{C1} = I_{C2} = I_o] \quad (2.91)$$

where

$$I_{\text{ref}} = \frac{V_{CC} - 2V_{BE}}{R_1}$$

It is easily seen from Eq. (2.91) that the output current is essentially independent of β . The output resistance of the current source is only r_o . It can however be increased by using emitter resistances in Q_1 and Q_2 as is done in the modified Widlar source circuit in Fig. 2.19. The two emitter resistors can also be used to make I_o different from I_{ref} .

Wilson Current Source

The final current source shown in Fig. 2.23 provides an output current I_o , which is very nearly equal to I_{ref} and also exhibits a very high output resistance.

Analysis

Since

$$\begin{aligned} V_{BE1} &= V_{BE2} \\ I_{C1} &= I_{C2} \text{ and } I_{B1} = I_{B2} = I_B \end{aligned}$$

At node 'b'

$$I_{E3} = 2I_B + I_{C2} = \left(\frac{2}{\beta} + 1 \right) I_{C2} \quad (2.92)$$

 


Fig. 2.22 A current source with gain

 


Fig. 2.23 A Wilson current source

I_{E3} is also equal to

$$I_{E3} = I_{C3} + I_{B3} = I_{C3} \left(1 + \frac{1}{\beta} \right) \quad (2.93)$$

From Eqs. (2.92) and (2.93), we obtain

$$I_{C3} \left(1 + \frac{1}{\beta} \right) = I_{C2} \left(1 + \frac{2}{\beta} \right)$$

$$I_{C3} = I_o = \left(\frac{\beta+2}{\beta+1} \right) I_{C2} \quad (2.94)$$

Since

$$I_{C1} = I_{C2}$$

$$I_o = \left(\frac{\beta+2}{\beta+1} \right) I_{C1} \quad (2.95)$$

At node 'a'

$$I_{\text{ref}} = I_{C1} + I_{B3} = \frac{\beta+1}{\beta+2} I_o + \frac{I_o}{\beta} = \frac{\beta^2 + 2\beta + 2}{\beta^2 + 2\beta} I_o$$

or

$$I_o = \frac{\beta^2 + 2\beta}{\beta^2 + 2\beta + 2} I_{\text{ref}} \quad (2.96)$$

where

$$I_{\text{ref}} = \frac{V_{CC} - 2V_{BE}}{R_1} \quad (2.97)$$

$$\text{The difference} \quad I_o - I_{\text{ref}} = \frac{2}{\beta^2 + 2\beta + 2} I_{\text{ref}} \quad (2.98)$$

is extremely small error for modest values of β . The output resistance of a Wilson current mirror is substantially greater ($\cong \beta \frac{r_o}{2}$) than simple current mirror or Widlar current mirror.

More Solved Examples

Example 2.13

For the circuit shown in Fig. 2.24, determine the value of I_o for $\beta = 100$. Assume $V_{BE} = 0.7$ V

 


Fig. 2.24 Circuit for Example 2.13

Solution

Writing KVL for the indicated loop 1

$$5\text{ V} - V_{BE} - 10\text{ k}\Omega I_{\text{ref}} + 5\text{ V} = 0$$

$$I_{\text{ref}} = \frac{10\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega} = 0.93\text{ mA}$$

At emitter node 'E'

$$I_{\text{ref}} = 2I_E \quad (\text{Assuming identical transistors})$$

$$= 2(I_C + I_B) = 2I_C \left(1 + \frac{1}{\beta}\right)$$

$$\text{Then} \quad I_C = \frac{\beta}{2(1 + \beta)} I_{\text{ref}} = 0.46\text{ mA}$$

$$\text{Due to mirror effect} \quad I_o = I_{C1} = I_C = 0.46\text{ mA}$$

Example 2.14

For the circuit shown in Fig. 2.25.

- (a) Determine I_{C1} and I_{C2}
 (b) Find R_C so that $V_o = 6$ V. Assume $\beta = 200$.

Solution

$$(a) \quad I_{\text{ref}} = \frac{12\text{ V} - 0.7\text{ V}}{15\text{ k}\Omega} = 0.75\text{ mA}$$

and

$$I_1 = \frac{0.7\text{ V}}{2.8\text{ k}\Omega} = 0.25\text{ mA}$$

At node 'a'

$$\begin{aligned} I_{\text{ref}} &= I_{C1} + 2I_B + I_1 \\ &= I_{C1} \left(1 + \frac{2}{\beta}\right) + I_1 \end{aligned}$$

Solving for I_{C1} gives

$$I_{C1} = 0.495\text{ mA} \cong 0.5\text{ mA}$$

$$I_{C2} = I_{C1} \quad (\text{due to mirror effect})$$

(b) From the outer loop

$$12\text{ V} = I_{C2}R_C + V_o$$

$$R_C = \frac{12\text{ V} - 6\text{ V}}{0.5\text{ mA}} = 12\text{ k}\Omega$$

 


Fig. 2.25 Circuit for Example 2.14

Example 2.15

Figure 2.26 shows a modified current mirror circuit. Determine the emitter current in transistor Q_3 if $\beta = 100$ and $V_{BE} = 0.75$ V.

Solution

From Fig. 2.26 at node 'a'

$$I = I_{C1} + I_1 = I_{C1} + I_{B1} + I_1$$

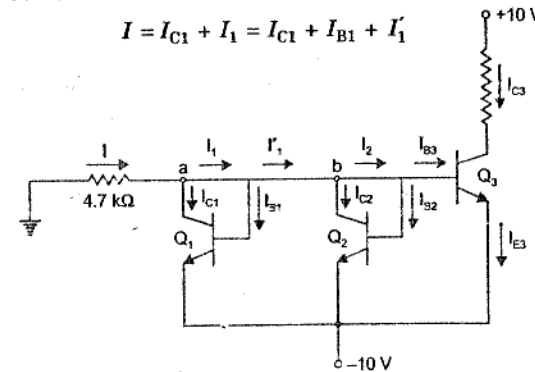


Fig. 2.26 Circuit of Example 2.15

or,

$$I = I_{C1} \left(1 + \frac{1}{\beta} \right) + I_1' \approx I_{C1} + I_1' \quad (\text{as } \beta \gg 1)$$

Also at node 'b'

$$I_1' = I_{C2} + I_2 = I_{C2} + I_{B2} + I_{B3} = I_{C2} \left(1 + \frac{1}{\beta} \right) + I_{B3} \approx I_{C2} + I_{B3}$$

Putting the value of I_1' , we get

$$I = I_{C1} + I_{C2} + I_{B3} = 2I_C + I_{B3} \quad [\text{as } I_{C1} = I_{C2} = I_C]$$

$$\approx I_C \left(2 + \frac{1}{\beta} \right) \approx 2I_C$$

The current I is given by,

$$I = \frac{10 - 0.75}{4.7 \text{ k}\Omega} = \frac{9.25}{4.7 \text{ k}\Omega} = 1.97 \text{ mA}$$

The collector current of Q_3 is equal to the collector current of Q_1 and Q_2 due to mirror action. Therefore, the emitter current

$$I_{E3} = I_{C3} = I_C = \frac{I}{2} = 0.98 \text{ mA}$$

2.4.5 Input Resistance

The resistance offered by the differential amplifier of Fig. 2.27 to the differential input signal ($v_1 - v_2$) is called differential input resistance R_{id} . The emitters of Q_1 and Q_2 are floating as R_E is replaced by a constant current source, therefore $R_{id} = h_{ie1} + h_{ie2} = 2 h_{ie}$. If input 2 is grounded, then input 1 is loaded by $2 h_{ie}$. The value of h_{ie} can be increased by reducing the biasing currents for Q_1 and Q_2 and input resistance of the order of 500 k Ω can be obtained.

Higher values of input resistance can be obtained by using a Darlington pair in place of transistor Q_1 and Q_2 of Fig. 2.27 as shown in Fig. 2.28. One drawback of the Darlington differential amplifier is the higher offset voltage V_{os} (due to cascaded stages) which is about 2 times larger than the ordinary two transistor differential amplifier.

The most important feature of the Darlington pair differential amplifier is its extraordinary large current gain. For the circuit shown in Fig. 2.28, the overall current gain is

$$\begin{aligned} \beta &= \frac{I_C}{I_{B1}} = \frac{I_{C1} + I_{C2}}{I_{B1}} \\ &= \frac{I_{C1}}{I_{B1}} + \frac{I_{C2}}{I_{B1}} \end{aligned}$$

 


Fig. 2.27 Differential amplifier

 


Fig. 2.28 Differential amplifier using Darlington pair

$$\begin{aligned} &= \frac{I_{C1}}{I_{B1}} + \frac{I_{C2}}{I_{B2}} \times \frac{I_{B2}}{I_{B1}} \\ &= \beta_1 + \beta_2 \cdot \beta_1 + 1 \quad \left[\begin{array}{l} I_{B2} = I_{E1} \\ = I_{C1} + I_{B1} \end{array} \right] \approx \beta_2 \beta_1 \end{aligned}$$

So, the overall current gain β of the Darlington circuit will be of the order of 10,000 if the current gain of the individual transistor is about 100. Another method to get higher input resistance is to fabricate a FET differential pair as the input stage with the rest of the stage made of BJTs. Input resistance of the order of $10^{12} \Omega$ is possible with such JFET inputs. A number of such op-amps are described in Sec. 2.6.

2.4.6 Active Load

The open circuit voltage gain of an op-amp should be as large as possible and this is achieved by cascading gain stages. However, this increases the phase shift too and amplifier becomes more susceptible to breaking out into oscillations. One can think of increasing gain by using large collector resistance values as gain is proportional to load resistor R_C . However, there are limitations to the maximum value of R_C to be used due to the following two reasons

- A large value of resistance requires a large chip area.
- For large R_C quiescent drop across it increases and hence a large power supply will be required to maintain a given quiescent collector current. These difficulties are circumvented by using a current source of the type shown in Fig. 2.16 as load in the place of R_C .

The current mirror discussed earlier has a dc resistance of the order of few kilohms, and the quiescent voltage across it is a fraction of the supply voltage and the current is in milliamperes. However, since it acts as a constant current source, its dynamic resistance (which is very high). Hence, a current mirror can also be used as an active load for an amplifier to obtain a very large voltage gain. Figure 2.29 (a) shows a diff-amp with an active load. The current mirror uses pnp transistors Q_3 and Q_4 . The constant current I_Q may also be obtained from a current mirror. The operation of the circuit in Fig. 2.29 (a) is as follows:

 


Fig. 2.29 (a) A differential amplifier with an active load Q_3 - Q_4

Under the quiescent conditions, $v_1 = v_2 = 0$. From symmetry of Q_1 and Q_2 , $I_1 = I_2 = I_Q/2$ where base currents are assumed to be neglected. Since Q_3 and Q_4 form a current mirror, $I = I_1 = I_2$. The load current I_L entering the next stage is

$$I_L = I - I_2 = 0 \quad (2.99)$$

However, when v_1 is increased over v_2 , I_1 increases whereas I_2 decreases, since $I_1 + I_2 = I_Q$ (constant). Also the current I always remains equal to I_1 due to the current mirror. The load current is given by

$$\begin{aligned} I_L &= I - I_2 = I_1 - I_2 \\ &= g_m v_1 - g_m v_2 = g_m (v_1 - v_2) \\ &= g_m v_d \end{aligned} \quad (2.100)$$

The circuit thus behaves as a transconductance amplifier.

A popular op-amp ($\mu A741$) by Fairchild uses an alternate active load as shown in Fig. 2.29 (b). The transistors Q_1 - Q_3 and Q_2 - Q_4 are in cascode configuration (CE-CB) with input signal as v_1 (v_2). The transistors Q_5 , Q_6 and Q_7 form the active load of the type shown in Fig. 2.22. The transistors Q_8 and Q_9 form the current mirror to provide the constant current I_Q required for high CMRR of the diff-amp. If base currents are neglected, then $I_Q \approx I_3$. The arrangement Q_{10} and Q_{11} is another current mirror where $I_3 \ll I_4$ due to $5 \text{ k}\Omega$ emitter resistor. Consequently $I_Q = I_3$ is small (of the order of μA) giving a very high input resistance.

Under the quiescent conditions, $I_1 = I_2 = I_Q/2$. Since I is always equal to I_1 , the load current $I_L = I_2 - I = I_2 - I_1 = 0$. Now if v_1 is increased and v_2 is decreased, I_1 rises and I_2 falls from the quiescent value of $I_Q/2$. With this excitation, $I_L = I_2 - I_1$ changes from zero to a negative value. Thus the circuit behaves as a transconductance amplifier because I_L is proportional to $v_1 - v_2$.

 


Fig. 2.29 (b) Active load (Q_5 - Q_6 - Q_7) of a low current differential amplifier $\mu A741$

2.4.7 Level Translator

There are two good reasons for using a level shifter in an IC op-amp. As we want an op-amp to operate down to dc, no coupling capacitor is used. Because of direct coupling, the dc level rises from stage to stage. The increase in dc level tends to shift the operating point of the next stage. This, in turn, limits the output voltage swing and may even distort the output signal. It, therefore, becomes essential that the quiescent voltage of one stage is shifted before it is applied to the next stage. Another requirement to be satisfied is that the output should have quiescent voltage level of 0 V for zero input signal.

The simplest type of a level shifter is shown in Fig. 2.30 (a). It may be noted that this is basically an emitter follower. Hence the level shifter also acts as a buffer to isolate the high gain stages from the output stage. The amount of shift obtained

$$V_o - V_i = -V_{BE} = -0.7 \text{ V} \quad (2.101)$$

If this shift is insufficient, the output can be taken at the junction of two resistors R_1 and R_2 , as shown in Fig. 2.30 (b). The voltage shift is now increased by the drop across R_1 . However, this arrangement has the disadvantage that signal voltage also gets attenuated by $R_2 / (R_1 + R_2)$. This can be easily circumvented if R_2 is replaced by a current mirror I as shown in Fig. 2.30 (c).

 


Fig. 2.30 (a)–(c) Level shifters using emitter follower buffer

The shift in level now is


$$V_o - V_i = -(V_{BE} + IR_1) \quad (2.102)$$

and there is no ac attenuation due to high resistance of the current source.

Another voltage source commonly used in $\mu A741$ op-amp is shown in Fig. 2.30 (d). It can be seen that if base current is negligible compared to the current in R_3 and R_4 , then the circuit behaves as a V_{BE} multiplier as,

$$V = \frac{V_{BE}}{R_4} (R_3 + R_4) = V_{BE} \left(1 + \frac{R_3}{R_4} \right) \quad (2.103)$$

This voltage source can also be used to replace R_1 in Fig. 2.30 (b).

 Fig. 2.30 (d) A voltage source V which is a multiple of V_{BE}

Example 2.16

Calculate $V_1 - V_2$ for the level shifter shown in Fig. 2.31. Assume identical silicon transistors with $V_{BE} = 0.7$ V and very large values of β .

Solution

Transistors Q_1 and Q_2 form a current mirror.

$$\text{So, } I_{C1} = I_{C2} = I$$

$$\text{and } I = \frac{15 - 0.7}{10 \text{ k}\Omega} = 1.43 \text{ mA}$$

 
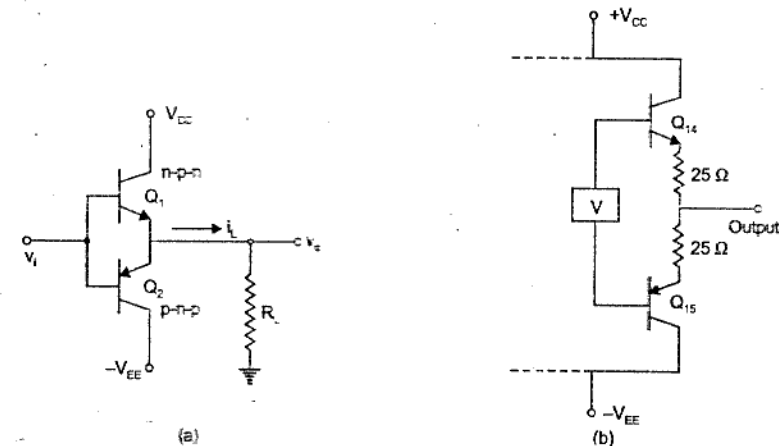


Fig. 2.31 Circuit of Example 2.16

$$V_1 - V_2 = V_{BE3} + I_{C2} \times 5 \text{ k}\Omega = 0.7 \text{ V} + 1.43 \times 5 \text{ k}\Omega = 7.85 \text{ V.}$$

2.4.8 Output Stage

The function of the last stage, that is, the output stage in an op-amp is to supply the load current and provide a low impedance output. It should also provide a large output voltage saving, ideally the total supply voltage i.e., $V_{CC} + V_{EE}$. A simple output stage consists of two complementary transistors Q_1 (*npn*) and Q_2 (*pnp*) connected as emitter followers as shown in Fig. 2.32 (a). It can be seen that for v_i positive, transistor Q_1 is *on* and supplies current to load R_L . And, if v_i is negative, Q_1 is cut off and Q_2 acts as a sink to remove current from the load R_L . There is, however, a limitation in this circuit. The output voltage v_o remain:

Fig. 2.32 (a) A complementary emitter follower output stage (b) Output stage of $\mu A741$

zero until the input v_i exceeds V_{BE} (cut in) = 0.5 V. This is called cross-over distortion. It can be eliminated by applying a bias voltage V slightly greater than $2V_{BE(\text{cut in})} = 1$ V between the two bases, so that a small current flows in the transistors even in the quiescent state. The output stage of $\mu\text{A}741$ op-amp is shown in Fig. 2.32 (b). The block marked V is the V_{BE} multiplier of the type shown in Fig. 2.30 (d). It is designed to supply a voltage of about 1 V between the bases of the complementary pair of transistors Q_{14} and Q_{15} . The small emitter resistors (25Ω) stabilize the quiescent base current.

2.5 EXAMPLES OF IC OP-AMPS

We are now in a position to analyse the complete circuit of commercially available op-amps. Two such IC op-amps discussed are Motorola MC 1530 and Fairchild $\mu\text{A}741$.

2.5.1 Motorola MC1530 Op-Amp

The circuit of MC 1530 is shown in Fig. 2.33. It is easily seen that the circuit consists of four stages. Transistors Q_2 and Q_3 form the first diff-amp stage driven by the constant current source Q_1 . The output of the first diff-amp drives the second diff-amp formed by Q_4 and Q_5 . The single ended output of the second diff-amp drives the level shifter Q_6 (emitter follower). Q_7 and diode D_3 forms another constant current source of the type shown in Fig. 2.15. The diode connected transistor Q_1 of Fig. 2.15 is shown by diode D_3 here. The output stage of MC1530 uses Q_8 , Q_9 and Q_{10} where Q_9 and Q_{10} are in totem-pole configuration.

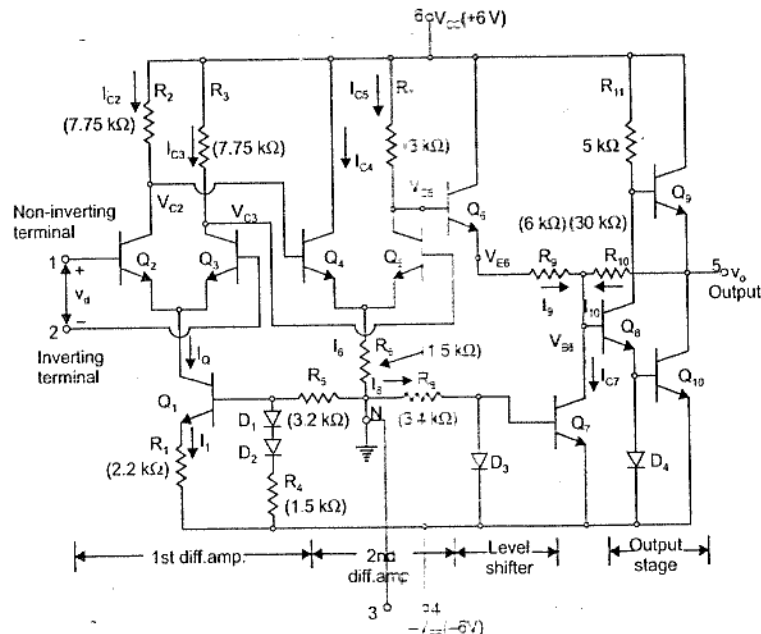


Fig. 2.33 Internal circuit of Motorola MC 1530

Example 2.17

From the circuit of Fig. 2.33 calculate,

- (1) The collector current in each transistor and the output voltage under quiescent conditions.
- (2) The open loop voltage gain.

Assume $h_{fe} = 100$ and $V_{BE} = V_D = 0.7$ V.

Solution

- (1) The d.c. analysis is performed by assuming that both the inverting and non-inverting terminals are at ground potential. To determine the collector current in Q_2 and Q_3 , first calculate the constant current I_Q . If the base current of Q_1 is neglected, then $I_Q = I_1$. The voltage V_{BN1} at the base of transistor Q_1 with respect to ground N is written using voltage divider rule as,

$$V_{BN1} = \frac{[-V_{EE} + V_D + V_D] R_5}{R_1 + R_5}$$

$$= \frac{(-6 \text{ V} + 1.4 \text{ V})(3.2 \text{ k}\Omega)}{1.5 \text{ k}\Omega + 3.2 \text{ k}\Omega} = -3.13 \text{ V}$$

$$I_1 = \frac{V_{EE} + V_{BN1} - V_{BE1}}{R_1} = \frac{6 \text{ V} - 3.13 \text{ V} - 0.7 \text{ V}}{2.2 \text{ k}\Omega} = 0.986 \text{ mA}$$

So $I_Q = 0.986 \text{ mA}$

Under dc conditions, half of the I_Q flows through each of transistors Q_2 and Q_3 . Therefore, $I_{C2} = I_{C3} = I_Q/2 = 0.493 \text{ mA}$. The voltage at the collector of Q_2 and Q_3 is,

$$V_{C2} = V_{C3} = V_{CC} - R_2 I_{C2} = 6 \text{ V} - (7.75 \text{ k}\Omega)(0.493 \text{ mA}) = 2.18 \text{ V}$$

So the voltage at the base of Q_4 and Q_5 is 2.18 V. The dc voltage at the emitter of Q_4 is,

$$V_{E4} = V_{C2} - V_{BE4} = 2.18 \text{ V} - 0.7 \text{ V} = 1.48 \text{ V}$$

So,

$$I_6 = \frac{V_{E4}}{R_6} = \frac{1.48 \text{ V}}{1.5 \text{ k}\Omega} = 0.987 \text{ mA}$$

This current divides equally in transistors Q_4 and Q_5 , so that

$$I_{C4} = I_{C5} = \frac{I_6}{2} = 0.494 \text{ mA}$$

$$V_{C5} = V_{CC} - I_{C5} R_7 = 6 \text{ V} - (0.494 \text{ mA})(3 \text{ k}\Omega) = 4.52 \text{ V}$$

$$V_{E6} = V_{C5} - V_{BE6} = 4.52 \text{ V} - 0.7 \text{ V} = 3.82 \text{ V}$$

Transistor Q_7 along with diode D_3 forms a current mirror of the type shown in Fig. 2.15. Hence,

$$I_{C7} = I_8 = \frac{V_{EE} - V_{D3}}{3.4} = 1.56 \text{ mA}$$

To calculate the current I_9 , first calculate the voltage at the base of Q_8 ,

$$V_{B8} = V_{BE8} + V_{D1} - V_{EE} = 0.7 \text{ V} + 0.7 \text{ V} - 6 \text{ V} = -4.60 \text{ V}$$

$$I_9 = \frac{V_{E8} - V_{E7}}{R_9} = \frac{3.82 \text{ V} - 4.6 \text{ V}}{6 \text{ k}\Omega} = 1.40 \text{ mA}$$

$$I_{10} = I_{C7} - I_9 = 1.56 \text{ mA} - 1.40 \text{ mA} = 0.16 \text{ mA}$$

The voltage V_i at the output terminal is,

$$V_o = I_{10} R_{10} + V_{E7} = (0.16 \text{ mA})(30 \text{ k}\Omega) - 4.60 \text{ V} = 0.20 \text{ V} \\ = 0 \text{ V (as expected)}$$

- (2) In order to calculate the overall voltage gain, we first calculate the voltage gain of the differential amplifier stages. For this we must know the ac emitter resistance h_{ie} of the transistor used.

$$h_{ie} = \frac{h_{ie} V_T}{|I_C|}$$

where V_T is the volt equivalent of temperature = 26 mV at room temperature.

$$\text{Since } I_{C2} = I_{C3} = I_{C4} = I_{C5} \approx 0.5 \text{ mA}$$

$$\text{So } h_{ie} = \frac{(100)(26 \text{ mV})}{0.5 \text{ mA}} = 5.2 \text{ k}\Omega$$

Since emitter of Q_4 - Q_5 is at ground potential under ac operation the input resistance h_{ie} of Q_4 and Q_5 is effectively in parallel to collector circuit load (R_2 and R_3) of first diff-amp. The effective load of Q_2 and Q_3 is

$$R_{L2} = R_{L3} = 7.75 \text{ k}\Omega \parallel 5.2 \text{ k}\Omega = 3.12 \text{ k}\Omega$$

The output of the first stage is double ended, its differential gain is given by Eq. (2.53)

$$\text{So, } A_{V1} = \frac{v_{C3} - v_{C2}}{v_i} = \frac{h_{ie} R_{L2}}{h_{ie}} = \frac{100 \times 3.12 \text{ k}\Omega}{5.2 \text{ k}\Omega} = 60$$

For the second stage, $h_{fe} = 100$, $h_{ie} = 5.2 \text{ k}\Omega$ and load $R_7 = 3 \text{ k}\Omega$ (neglecting loading on Q_5 of the emitter follower Q_7). The output of the second stage is single ended, so its differential gain is,

$$A_{V2} = \frac{v_{C5}}{v_{C3}} = -\frac{1}{2} \frac{h_{fe} R_7}{h_{ie}} = -\frac{100 \times 3 \text{ k}\Omega}{2 \times 5.2 \text{ k}\Omega} = -28.9$$

The third stage is the emitter follower, so, $A_{V3} = 1$

The last output stage uses voltage shunt feedback network R_9 - R_{10} ,

$$\text{so } A_{V4} = \frac{R_{10}}{R_9} = -\frac{30}{6} = -5$$

Hence the overall op-amp gain is,

$$A_V = (60)(-28.9)(-5) = 8670$$

2.5.2 741 Op-Amp

741 Op-amp has become an industry standard today. The pin configuration and the complete schematic circuit diagram for 741 op-amp is shown in Fig. 2.34 (a) and (b) respectively. Since this circuit is quite complex compared to MC1530, only the qualitative analysis is taken up.

In understanding an op-amp circuit as complex as this (24 transistors), first we identify the stages which provide signal gain. The input stage diff-amp consists of transistors Q_1 - Q_3 and Q_2 - Q_4 .

Transistors Q_{16} and Q_{17} provide the second stage voltage gain. Transistors Q_1 - Q_3 and Q_2 - Q_4 are in cascode (CE-CB) configuration. Two transistors in series (Q_1 feeds Q_3) provide high gain per stage needed to achieve the adequate open-loop gain in a two stage amplifier. The transistors Q_5 , Q_6 and Q_7 form the active load for Q_3 and Q_4 . Transistors Q_5 and Q_6 also function as a differential amplifier for the external offset nulling signal. The emitter current of transistors Q_5 and Q_6 can be controlled by varying a 10 k Ω potentiometer that is externally connected between offset null terminals as shown by dotted line in Fig. 2.34 (b). Bias currents for the input stage are provided by a complicated arrangement of current mirror pairs. Q_{12} generates a current in Q_{11} . This current is reflected over to Q_{10} (though reduced because of the emitter feedback due to R_4). This, in turn, generates a series current in Q_2 which is reflected across another mirror pair to Q_3 . The bias current of Q_3 and Q_4 is effectively driven by the mirror pair Q_{10} and Q_{11} . The output of the first diff-amp is taken at the junction of Q_4 and Q_6 (point X) which acts as a complementary symmetry amplifier. The output at this point is proportional to the differential input signal. The output is now amplified by the second stage consisting of transistor Q_{15} and Q_{17} in Darlington connection.

The output of common-collector-amplifier formed by Q_{16} and R_9 drives the CE-amplifier composed of Q_{17} , R_8 and a constant current load Q_{13} . The output of CE-amplifier is a bias source for transistors Q_{18} and Q_{19} . Transistors Q_{12} and Q_{13} form a current mirror and supply current to transistors Q_{17} , Q_{15} and Q_{15} . The network consisting of transistors Q_{15} , Q_{19} and R_{10} is a fixed voltage level shifter shifting the voltage output of Q_{17} by a fixed amount on its way to the output complementary stage formed by Q_{14} and Q_{20} . The level shifter network is designed to bias the output stage in the linear region. The transistors Q_{18} and Q_{19} also separate the bases of Q_{14} and Q_{20} by two diode drops and thus temperature compensate currents in Q_{14} and Q_{20} . Transistor Q_{22} performs two functions. It serves as a buffer between Q_{17} and Q_{20} and also provides a negative feedback to Q_{16} . The final output is taken at the junction of R_6 and R_7 . The output complementary pair operates so that depending upon the sign of the output, only one of the transistors Q_{14} or Q_{20} is conducting at any time. With no input signal, both devices are turned off, resulting in a low quiescent current drain in the output stage.

Transistors Q_{15} , Q_{21} and Q_{23} protect the circuit by limiting current to the output complementary stage. If the output (load) current exceeds the safe limit, the voltage drop across R_6 and R_7 increases. This turns on Q_{15} and Q_{21} which in turn makes Q_{22} on. This however shorts out, that is turns off the amplifier Q_{16} - Q_{17} . This reduces the emitter current in Q_{22} and in turn current in Q_{18} and Q_{19} . The reduction in the currents of Q_{15} and Q_{19} lowers the currents in Q_{14} and Q_{20} . The diode-connected transistor Q_{24} is a temperature

 


Fig. 2.34 (a) Pin configuration

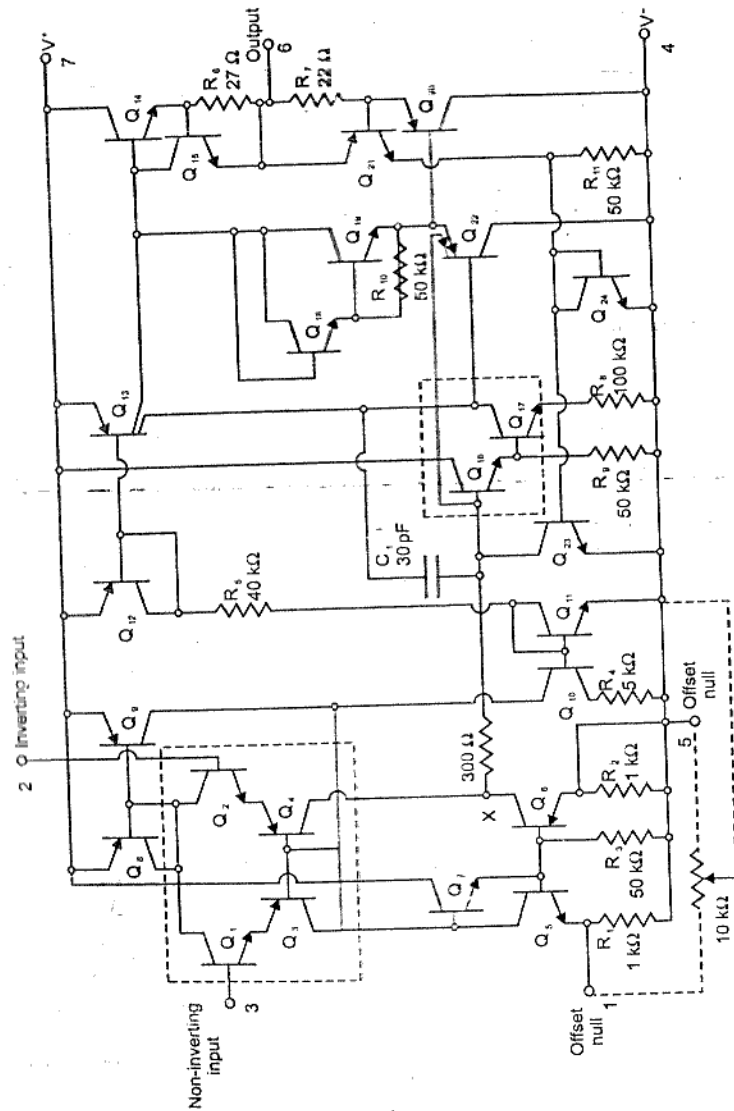


Fig. 2.34 (b) Schematic circuit diagram for 741 op-amp

compensating diode for transistor Q_{23} . Finally the internal 30-pF capacitor provides the high frequency roll-off to stabilize the circuit.

Example 2.18

For the op-amp circuit shown in Fig. 2.35, assume $h_{fe} = 100$, $V_{BE} = 0.7$ V.

- (i) Perform the dc analysis. Note that the transistor Q_7 has four times the areas of transistors Q_3 and Q_4 .
- (ii) Compute the overall voltage gain.

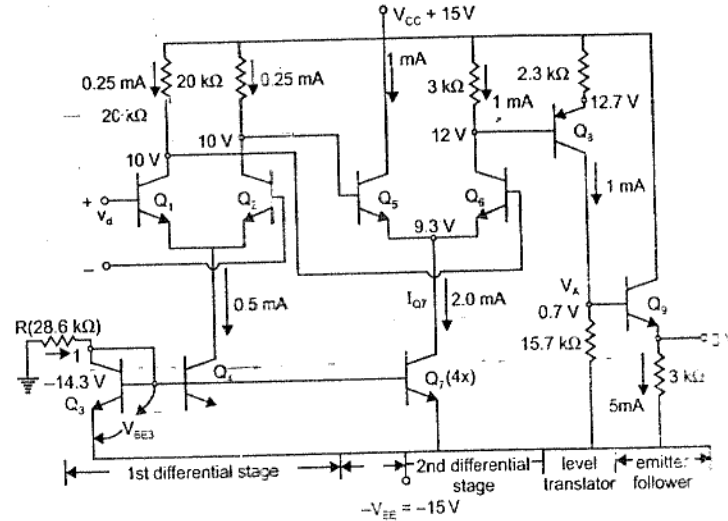


Fig. 2.35 Circuit for Example 2.18

Solution

It can be seen that the circuit has the following four stages:

- (i) Dual-input, differential-output
- (ii) Dual-input, single-ended output
- (iii) Level translator
- (iv) Emitter follower.

- (i) For dc analysis, assume that the input terminals are shorted to ground. The reference current I of the current mirror $Q_3 - Q_4$ is obtained as

$$I = \frac{V_{EE} - V_{BE3}}{R} = \frac{15V - 0.7V}{28.6 \text{ k}\Omega} = 0.5 \text{ mA}$$

Due to current mirror action,

$$I_{CQ4} = I = 0.5 \text{ mA}$$

and $I_{CQ1} = I_{CQ2} = I_{CQ4}/2 = 0.25 \text{ mA}$

Thus, each of Q_1 and Q_2 are biased at 0.25 mA. The collector voltages for Q_1 and Q_2 are

$$V_{CQ1} = V_{CQ2} = V_{CC} - I_{C2}R_{C1} = 15V - 0.25 \text{ mA} \times 20 \text{ k}\Omega = +10V$$

Now, proceeding to the next differential stage, voltage at the emitter of Q_5 and Q_6 will be
 $V_{EQ5} = V_{EQ6} = 16\text{ V} - 0.7\text{ V} = 9.3\text{ V}$

The differential pair Q_5 - Q_6 is biased by the current mirror transistor Q_7 . Since the area of Q_7 is 4 times that of Q_3 and Q_4 , the transistor Q_7 supplies a current $\frac{1}{4} \times 0.5 = 0.125\text{ mA}$.

Thus, collector currents of Q_5 and Q_6 are

$$I_{CQ5} = I_{CQ6} = \frac{I_{Q7}}{2} = 0.0625\text{ mA}$$

Hence, collector voltage of Q_6 is

$$V_{CQ6} = V_{CC} - I_{CQ6}R_{C6} = 15\text{ V} - 0.0625\text{ mA} \times 3\text{ k}\Omega = 14.81\text{ V}$$

This causes a voltage at the emitter of pnp transistor Q_8 at

$$V_{EQ8} = 12.7\text{ V}$$

The emitter current of Q_8 is

$$I_{EQ8} = \frac{15\text{ V} - 12.7\text{ V}}{2.3\text{ k}\Omega} = 0.99\text{ mA}$$

The voltage V_A at the collector of Q_8 or the base of Q_9 is

$$V_A = -15\text{ V} + 0.99\text{ mA} \times 15.7\text{ k}\Omega = -8.52\text{ V}$$

Since the emitter of Q_9 will be 0.7 V below the base terminal, the voltage at the output terminal 6 is 0 V as is expected. The emitter current of Q_9 is

$$I_{EQ9} = [0 - (-15\text{ V})] / 3\text{ k}\Omega = 5\text{ mA}$$

ii) **a.c. analysis.** The ac emitter resistance of the transistor Q_1 - Q_2 is

$$h_{ie} = \frac{h_{fe}V_T}{|I_C|} = \frac{100 \times 25\text{ mV}}{0.25\text{ mA}} = 10\text{ k}\Omega$$

The ac emitter resistance of transistor Q_5 - Q_6 is

$$h_{ie} = \frac{100 \times 25\text{ mV}}{1\text{ mA}} = 2.5\text{ k}\Omega$$

Since emitter of $(Q_5$ - $Q_6)$ is at ground potential under ac conditions, the effective load for Q_1 - Q_2 is

$$R_{L1} = R_{L2} = 20\text{ k}\Omega \parallel 2.5\text{ k}\Omega = 2.2\text{ k}\Omega$$

Voltage gain of the first differential stage is

$$A_{DM1} = \frac{h_{fe}R_{L1,2}}{h_{ie}} = \frac{100 \times 2.2\text{ k}\Omega}{10\text{ k}\Omega} = 22$$

Voltage gain of second stage which is differential input, single-ended is

$$A_{DM2} = -\frac{1}{2} \frac{h_{fe}R_{L5}}{h_{ie}}$$

Assuming no loading effect on this stage due to level translator stage,

$$A_{DM2} = -\frac{1}{2} \times \frac{100 \times 3\text{ k}\Omega}{2.5\text{ k}\Omega} = -60$$

The gain of the level translator stage is

$$A_3 = -\frac{R_L}{R_E} = -\frac{15.7\text{ k}\Omega}{2.3\text{ k}\Omega} = -6.82$$

The last stage is emitter follower, so its voltage gain $A_{V4} \approx 1$

So the overall voltage gain is

$$A_V = (22) \times (-60) \times (-6.82) \times 1 = 9002$$

2.6 FET OPERATIONAL AMPLIFIER

The op-amp circuits discussed so far are bipolar op-amps. Op-amps using field transistors (FETs) in the input stage offer some very significant advantages over bipolar op-amps, especially in areas as input impedance, input bias and offset currents and slewing rate as shown in Table 2.1.

Table 2.1

Parameter	BJT	JFET	MOSFET
Input resistance	k Ω	10^9 Ω (giga-ohms)	10^{12} Ω (tera-ohms)
Input gate current	μA	1 nA	1 pA
Input offset current	20 nA	2 pA	0.5 pA
Slewing rate	1 V/ μs	3 V/ μs	10 V/ μs

FET Differential Amplifier

The circuit of a basic source-coupled differential amplifier using MOSFET is shown in Fig. 2.36. The analysis for finding A_{DM} and A_{CM} is similar to what has been done for BJT differential amplifiers.

 


Fig. 2.36 A MOSFET differential amplifier

 


Fig. 2.37 a.c. equivalent circuit for (a) Differential-mode (b) Common-mode signals

The differential mode gain, A_{DM} , and common-mode gain, A_{CM} , can be obtained from the a.c. equivalent circuits shown in Fig. 2.37 (a) and (b) respectively as

$$A_{DM} = \frac{\mu R_D}{r_d + R_D} \quad (2.104)$$

$$A_{CM} = \frac{\mu R_D}{r_d + R_D + 2(1 + \mu)R_S} \quad (2.105)$$

$$CMRR = \frac{|A_{DM}|}{|A_{CM}|} = \frac{r_d + R_D + 2(1 + \mu)R_S}{r_d + R_D} = 1 + \frac{2(1 + \mu)R_S}{r_d + R_D} \quad (2.106)$$

For $r_d \gg R_D$ and $\mu \gg 1$, Equation reduces to

$$CMRR = 1 + 2 g_m R_S = 2 g_m R_S \quad (2.107)$$

It is now possible to fabricate JFET/MOSFET and BJTs on the same chip using ion implantation techniques. Op-amps which use FET input stages and BJT for the remaining stages are termed as BIFET/BLMOS. By the mid 1980s, BIMOS circuits were produced commercially. Some of the FET IC op-amps available are discussed here briefly.

JFET Op-amps

An example of a FET input hybrid op-amp is the LH0022/42/52 (National semiconductor) series. This op-amp uses a pair of JFET transistors only for the input-stage differential amplifier and the rest of the circuit uses bipolar transistors. A simplified diagram of this op-amp is shown in Fig. 2.38. The input-stage differential amplifier consists of Q_1 through Q_4 in which Q_1 and Q_2 are *n*-channel JFETs operating in a common-drain or source-follower configuration. These JFETs drive Q_3 and Q_4 which operate in the common-base configuration. Thus the differential amplifier uses a compound JFET/bipolar transistor configuration. This provides very high input resistance and very low input current characteristics of JFETs and high-voltage gain that is obtainable from bipolar transistors. This compound differential amplifier drives an active load consisting of Q_5 through Q_7 , operating as a current mirror. The rest of this op-amp is of conventional design as discussed for $\mu A741$. Here diodes D_1 and D_2 are used to provide a pre-bias across Q_{14} and Q_{20} to minimize cross-over distortion.

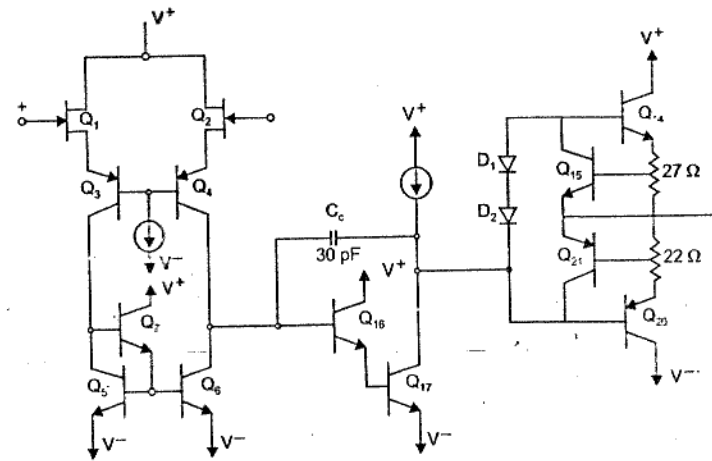


Fig. 2.38 Hybrid JFET-input op-amp LH00 22/42/52 series (National Semiconductor)

MOSFET Op-amps

An interesting example of a monolithic MOSFET op-amp is the CA3130 (RCA) which contains both MOSFETs and bipolar transistors on the same chip. A simplified schematic diagram of this device is shown in Fig. 2.39.

The input stage is a differential amplifier consisting of a pair of p-channel enhancement-mode MOSFETs Q_6 and Q_7 . This differential amplifier is biased by a $200 \mu A$ MOSFET current source, and it drives a current mirror active load using Q_9 and Q_{10} . Resistors R_5 and R_6 ($1 \text{ k}\Omega$) in the active load circuit are used together with an externally connected potentiometer (across pins 1 and 5) for offset voltage nulling. The quiescent voltage drop across these resistors in $100 \mu A \times 1 \text{ k}\Omega = 100 \text{ mV}$, so that a $\pm 100 \text{ mV}$ offset adjustment range is available. Diodes D_5 and D_8 are connected between the input terminal to protect the thin gate oxide of the input MOSFETs against excessive voltage spikes and static electricity discharge, which could cause breakdown of the oxide layer and result in irreversible damage to the transistors. The voltage gain of this first stage is only about 5, due to low transfer conductance of the MOSFETs.

The second stage consists of a bipolar transistor Q_{11} connected as a common-emitter amplifier, with a $200 \mu A$ MOSFET current source serving as the active load. As a result of the high dynamic impedance seen looking into the MOSFET output stage, the voltage gain of the second stage is very large (≈ 6000). The output stage is a complementary pair of MOSFETs (CMOS) with Q_8 being the PMOS and Q_{12} being the NMOS transistor. The use of CMOS pair in the output stage provides significantly low drainage of current from the power supply.

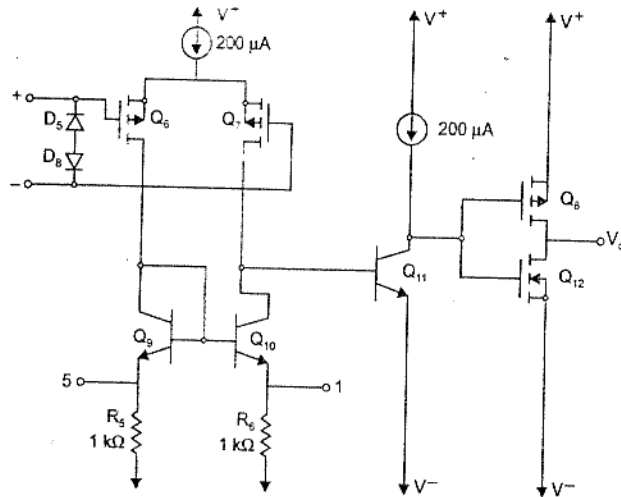


Fig. 2.39 MOSFET-input CMOS output op-amp: CH3130 (RCA Corporation)
a simplified schematic diagram

SUMMARY

1. An op-amp is available in three types of IC packages: metal can, dual-in-line and flat-pack.
2. There are five basic terminals: two input terminals, one output terminal and two supply terminals.
3. In open loop mode, the output of the op-amp is at positive or negative saturation level. It does not operate linearly in this mode.
4. Negative feedback stabilizes the gain. Two feedback connections used are: inverting amplifier and non-inverting amplifier.
5. A special case of non-inverting amplifier is the voltage follower.
6. A differential amplifier amplifies the difference between two input signals.
7. An operational amplifier is a direct coupled high gain amplifier consisting of one or more differential amplifiers, followed by a level translator and an output stage.
8. For proper operation of the differential amplifier, matched components must be used. The diff-amp can be biased by using emitter bias (a combination of R_E and V_{EE}), a constant current bias or a current mirror.
9. A current mirror can be used as an active load because it has high ac resistance.
10. MOSFET op-amps offer very high input resistance ($10^{12} \Omega$), low input current ($\sim 1 \text{ pA}$) and high slewing rate ($\sim 10 \text{ V}/\mu\text{s}$).

REVIEW QUESTIONS

- 2.1. What is an op-amp?
- 2.2. What are the different linear IC packages?
- 2.3. A 741 op-amp is available in a 14-pin dual-in-line package. What is the terminal number for (i) inverting input (ii) non-inverting input (iii) output?
- 2.4. Explain with figures how two supply voltages V^+ and V^- are obtained from a single supply.
- 2.5. List six characteristics of an ideal op-amp.
- 2.6. Explain the meaning of open loop and closed loop operation of an op-amp.
- 2.7. Name the type of the feedback used if an external component is connected between the output terminal and the inverting input.
- 2.8. What is the input impedance of a non-inverting op-amp amplifier?
- 2.9. If the open loop gain of an op-amp is very large, does the closed loop gain depend upon the external components or the op-amp?
- 2.10. What is a practical op-amp? Draw its equivalent circuit.
- 2.11. Define common mode rejection ratio.
- 2.12. Explain why $\text{CMRR} \rightarrow \infty$ for an emitter coupled differential amplifier when $R_E \rightarrow \infty$.
- 2.13. Why is R_E replaced by a constant current bias circuit in a diff-amp?
- 2.14. List and explain the function of all the basic building blocks of an op-amp.
- 2.15. Explain methods for increasing the input resistance of an op-amp.
- 2.16. Explain the difference between constant current bias and current mirror.
- 2.17. Explain why active load is used?
- 2.18. What is a V_{BE} multiplier?
- 2.19. What is cross-over distortion and how it is eliminated?
- 2.20. Why is cascode configuration used in an op-amp?
- 2.21. Why are FET op-amps better than BJT op-amps?
- 2.22. What is meant by a BIMOS or BIFET amplifier?

PROBLEMS

- 2.1. In an op-amp of Fig. 2.4 (a), $v_2 = 0$. What must be the voltage at v_1 to give an output of 5 V if $A_{OL} = 50000$?
- 2.2. Design an inverting amplifier with a gain of -5 and an input resistance of $10 \text{ k}\Omega$.
- 2.3. Design a non-inverting amplifier with a gain of 10.
- 2.4. For the circuit shown in Fig. P. 2.4, calculate the range of gain and input impedance.
- 2.5. Calculate the exact closed loop gain of the inverting amplifier of Fig. 2.5 (b) if $A_{OL} = 200,000$, $R_1 = 2 \text{ M}\Omega$ and $R_o = 75 \Omega$.

 


Fig. P. 2.4

2.6. For the circuit shown in Fig. P. 2.6, calculate the expression of v_o/v_i .

 


Fig. P. 2.6

2.7. In the circuit of Fig. P. 2.7 if $R_1 = \infty$ show that the output admittance Y_{of} is given by

$$Y_{of} = \frac{1}{R_0} \left(1 - A_{OL} \frac{R}{R+R'} \right) + \frac{1}{R+R'}$$

 


Fig. P. 2.7

2.8. Show that the input impedance for the non-inverting amplifier of Fig. P. 2.8 is

$$R_{if} = R_i \left(1 + \frac{Z_1}{Z_1 + Z_f} \cdot A_v \right)$$

where R_i the input resistance of op-amp is large and $R_o = 0$ and A_v is the gain without feedback.

 


Fig. P. 2.8

2.9. Refer to Fig. P. 2.9

 


Fig. P. 2.9

- Find v_o if CMRR = 100 dB at 1 kHz.
 - Find v_o resulting from 1% mismatches between the two R_1 resistors.
 - Find v_o resulting from 1% mismatch between two R_2 resistors.
- 2.10. Derive the expression for the output voltage v_o for the circuit shown in Fig. P. 2.10.

 


Fig. P. 2.10

- 2.11. Calculate the output voltage of the circuit in Fig. P. 2.11 if the input signal is a 5.5 mA current.

 


Fig. P. 2.11

- 2.12. What is the voltage at point A and B for the circuit shown in Fig. P. 2.12 if $v_1 = 5$ V and $v_2 = 5.1$ V?

 


Fig. P. 2.12

- 2.13. For op-amp, $CMRR = 10^5$ and differential gain $A_{DM} = 10^5$. Calculate the common mode gain A_{CM} of the op-amp.
- 2.14. The $CMRR$ of an op-amp is 10^4 . Two sets of signals are applied to it. First set is $V_1 = +20 \mu\text{V}$ and $V_2 = -20 \mu\text{V}$ and second set is $V_1 = 540 \mu\text{V}$ and $V_2 = 500 \mu\text{V}$. Calculate the per cent difference in output voltage for the two sets of signals.
- 2.15. For the current mirror shown in Fig. P. 2.15, determine R so that $I_o = 100 \mu\text{A}$.

 


Fig. P. 2.15

- 2.16. In the circuit of Fig. P. 2.16, $I_R = 50 \mu\text{A}$, what is the ratio R_1/R_2 needed for $I_o = 100 \mu\text{A}$?

 


Fig. P. 2.16

- 2.17. Design a current source for generating $I_o = 25 \mu\text{A}$. Assume: $V_{CC} = 15 \text{V}$, $\beta = 100$.
- 2.18. For a modified current mirror shown in Fig. P. 2.18, calculate (i) the current through the collector resistor R_C and (ii) the collector current in each transistor. Assume $V_{BE} = 0.7 \text{V}$ and $\beta = 100$.

 


Fig. P. 2.18

- 2.19. For the circuit of Fig. P. 2.19, show that $V_o = (V_Z + V_{BE})(1 + R_1/R_2)$.

 


Fig. P. 2.19

- 2.20. For the simple op-amp shown in Fig. P. 2.20, all *nnp* transistors have $\beta = 200$ and all *pnp* transistors have $\beta = 50$. Verify that $v_o = 0$ for $v_1 = v_2 = 0$. The current sources shown are realized by *pnp* current sources.
- 2.21. For the cascaded differential amplifier shown in Fig. P. 2.21 (i) perform the dc analysis and (ii) calculate the overall voltage gain. Assume $h_{fe} = 100$, $V_{BE} = V_D = 0.7 \text{V}$.

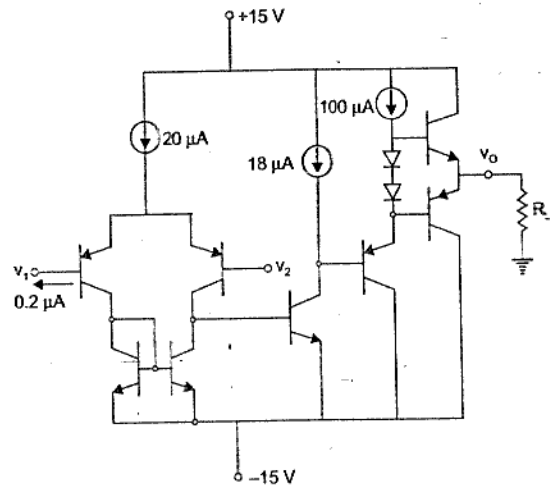


Fig. P. 2.20

 


Fig. P. 2.21

EXPERIMENT

To construct and verify experimentally the theoretical closed loop voltage gain using 741 op-amp for the following:

- (i) Inverting amplifier
- (ii) Non-inverting amplifier
- (iii) Voltage follower

PROCEDURE

- (1) Connect the op-amp as an inverting amplifier as shown in Fig. E. 2.1(a).

 


Fig. E. 2.1 (a) Inverting amplifier

- (2) Connect a dual channel scope to simultaneously view v_o and v_i . Adjust the signal generator to give 200 mV peak to peak sine wave at 100 Hz. Then measure and record the peak value of v_o for R_f 1 kΩ, 10 kΩ, 33 kΩ and 100 kΩ. Note the phase of v_o with respect to v_i .
- (3) Calculate the theoretical closed loop gain = R_f/R_i for each value of R_f and compare it with the experimental value of v_o/v_i .
- (4) Now connect the op-amp as a non-inverting amplifier as shown in Fig. E. 2.1 (b).
- (5) Repeat step 2.
- (6) Calculate the theoretical gain = $1 + R_f/R_1$ for each value of R_f and compare it with the experimental value of v_o/v_i .
- (7) Next make a voltage follower circuit as shown in Fig. E. 2.1. (c).

 


Fig. E. 2.1 (b) Non-inverting amplifier

 


Fig. E. 2.1 (c) Voltage follower

- (8) Measure and record the output voltage v_o for different input settings: 2 V peak at 100 Hz, 1 V peak at 500 Hz and 5 V peak at 1 kHz. Note the phase of v_o with respect to v_i in each case.
- (9) Verify that the voltage gain of the voltage follower is always equal to 1.

COMPUTER ANALYSIS

Program 2.1

Inverting Op-amp Amplifier

Figure C. 2.1 (a) shows an inverting op-amp amplifier with various terminals numbered for writing the PSPICE program. The PSPICE description is provided in program 2.1 listing. For circuit values of $R_1 = 1 \text{ k}\Omega$, $R_f = 10 \text{ k}\Omega$, the gain of the inverting amplifier is

$$A_V = -\frac{R_f}{R_1} = -10$$

 


Fig. C. 2.1 (a) Circuit for program 2.1

D.C. Analysis

For input $V_1 = 1 \text{ V}$, the output voltage V_o should be $V_o = -10 (1 \text{ V}) = -10 \text{ V}$. From the result file, it can be seen that the output V_o at node 5 is -9.998 V which gives an error of 0.02% only.

Transient Analysis

A sine wave signal of amplitude 0.1 V and frequency 1 kHz is applied at the input terminal. It can be seen from Fig. C. 2.1 (b) that the output is a sine wave of amplitude 1 V, 1 kHz. The output waveform is 180° out of the phase with the input waveform as expected.

Program 2.1: Listing

Inverting Amplifier: DC and Transient (Output Voltage vs Time) Analysis

```

* * * * * Circuit Description
* * * * *
R1 1 2 1K
RF 2 5 10K
* Op Amp Analysis
X1 0 2 3 4 5 uA 741
LIB EVAL LIB
* Power Supplies
VCC 3 0 DC 12V
VEE 0 4 DC 12V
    
```

```

* Input Signal Source
V1 1 0 DC 1V SIN(0 0.1V 1KHZ)
* Output
.DC V1 1 1 1
.TRAN 5us 5ms 0ms .01 ms
.PROBE
.PRINT DC V(5) V(1)
END
    
```

*** DC Transfer Curves Temperature = 27.00C DEG C

V1	V(5)	V(1)
1.000E+00	-9.998E+00	1.000E+00

 


Fig. C. 2.1 (b) Inverting amplifier: Transient analysis (output voltage vs time)

Program 2.2

Non-inverting Op-amp Amplifier

The circuit of a non-inverting op-amp amplifier for writing the PSPICE program is shown in Fig. C. 2.2 (a).

For the circuit values, $R_1 = 1 \text{ k}\Omega$ and $R_f = 9 \text{ k}\Omega$, the voltage gain is

$$A_V = 1 + \frac{R_f}{R_1} = 1 + \frac{9\text{k}\Omega}{1\text{k}\Omega} = +10 = 10$$

 


Fig. C. 2.2 (a) Circuit for program 2.2

D.C. Analysis

For input voltage $V_1 = 1\text{ V}$, the output voltage at node 5, $V(5) = 10\text{ V}$

Transient Analysis

For input voltage source of amplitude 0.1 V and frequency 1 kHz, the output voltage has an amplitude 1 V at 1 kHz as shown in Fig. C. 2.2 (b). It may be noted that there is no phase shift for a non-inverting amplifier.

 


Fig. C. 2.2 (b) Non-inverting amplifier: Transient analysis (Output voltage vs time)

Program 2.2 Listing

Non-inverting Amplifier: DC and Transient (Output Voltage vs Time) Analysis

```

**** Circuit Description
*****
***
R1 0 2 1K
RF 2 5 9K
* Op Amp Analysis
X1 1 2 3 4 5 uA741
. LIB EVAL.LIB
* Power Supplies
VCC 3 0 DC 12V
VEE 0 4 DC 12V
* Input Signal Source
V1 1 0 DC 1V SIN(0 0.1V 1KHZ)
* Output
.DC V1 1 1 1
.TRAN .5us 5ms 0ms 0.01 ms
.PRINT DC V(5) V(1)
.PROBE
**** DC Transfer Curves          Temperature = 27.000 DEG C
*****
***
V1          V(5)          V(1)
1.000E+00  1.000E+01  1.000E+00
    
```

Program 2.3 Voltage Follower

The circuit diagram of a voltage follower and its PSPICE description are shown in Fig. C. 2.3 (a) and program 2.3 listing respectively.

The voltage gain for both d.c. and a.c. input is found to be unity and without change in phase as expected. The transient analysis is shown in Fig. C. 2.3 (b). It may be noted that waveforms at node 1 and 5 overlap each other indistinguishably.

 


Fig. C. 2.3 (a) Circuit for program 2.3

 


Fig. C. 2.3 (b) Transient response of voltage follower

Program 2.3 Listing

```

* Voltage Follower
**** Circuit Description
*****
***
RF 2 5 1M
* Op Amp Analysis
X1 1 2 3 4 5 uA741
. LIB EVAL.LIB
* Power Supplies
VCC 3 0 DC 12V
VEE 0 4 DC 12V
* Input Signal Source
V1 1 0 DC 2V SIN(0 0.1V 1KHZ)
* Output
.DC V1 2 2 2
* TRAN 0.5us 5ms 0ms 0.01 ms
* PRINT DC V(5) V(1)
* PROBE
**** DC Transfer Curves          Temperature = 27.000 DEG C
*****
***
V1          V(5)          V(1)
2.000E+00  2.000E+01  2.000E+00
    
```

3 OPERATIONAL AMPLIFIER CHARACTERISTICS

3.1 INTRODUCTION

Earlier we have used an ideal op-amp, and assumed that the op-amp responds equally well to both ac and dc input voltages. However, a practical op-amp does not behave this way. A practical op-amp has some dc voltage at the output even with both the inputs grounded. The factors responsible for this and the suitable compensating techniques are discussed. Also, under ac conditions the characteristics of an op-amp are frequency dependent. The limitations of an op-amp under ac conditions and methods of compensation are discussed.

3.2 DC CHARACTERISTICS

An ideal op-amp draws no current from the source and its response is also independent of temperature. However, a real op-amp does not work this way. Current is taken from the source into the op-amp inputs. Also the two inputs respond differently to current and voltage due to mismatch in transistors. A real op-amp also shifts its operation with temperature. These non-ideal dc characteristics that add error components to the dc output voltage are:

- Input bias current
- Input offset current
- Input offset voltage
- Thermal drift.

3.2.1 Input Bias Current

The op-amp's input is a differential amplifier, which may be made of BJT or FET. In either case, the input transistors must be biased into their linear region by supplying currents into the bases by the external circuit. In an ideal op-amp, we assumed that no current is drawn from the input terminals. However, practical inputs do conduct a small value of dc current to bias the input transistors. The base currents entering into the inverting and non-inverting terminals are shown as I_B^- and I_B^+ respectively in Fig. 3.1 (a). Even though non-inverting terminals are identical, I_B^- and I_B^+ are not exactly equal due to internal imbalances between the two inputs. Manufacturers specify input bias current I_B as the average value of the base currents entering into the terminals of an op-amp.

 


Fig. 3.1 (a) Input bias currents (b) Inverting amplifier with bias currents

$$\text{So, } I_B = \frac{I_B^+ + I_B^-}{2} \quad (3.1)$$

For 741, a bipolar op-amp, the bias current is 500 nA or less. The FET input op-amp will have bias currents as low as 50 pA at room temperature.

Consider the basic inverting amplifier of Fig. 3.1 (b). If input voltage V_i is set to zero volt, the output voltage V_o should also be zero volt. Instead, we find that the output voltage is offset by,

$$V_o = (I_B^-) R_f \quad (3.2)$$

For a 741 op-amp, with a 1 M Ω feedback resistor.

$$V_o = 500 \text{ nA} \times 1 \text{ M}\Omega = 500 \text{ mV}$$

The output is driven to 500 mV with zero input because of the bias currents. In applications where signal levels are measured in millivolts, this is totally unacceptable. This effect can be compensated for as shown in Fig. 3.1 (c) where a compensation resistor R_{comp} has been added between the non-inverting input terminal and ground. Current I_B^+ flowing through the compensating resistor R_{comp} develops a voltage V_1 across it. Then, by KVL, we get,

$$-V_1 + 0 + V_2 - V_o = 0$$

or

$$V_o = V_2 - V_1 \quad (3.3)$$

 


Fig. 3.1 (c) Bias current compensation in an inverting amplifier

By selecting proper value of R_{comp} , V_2 can be cancelled with V_1 and the output V_o will be zero. The value of R_{comp} is derived as

$$V_1 = I_B^+ R_{\text{comp}}$$

$$I_B^- = \frac{V_1}{R_{\text{comp}}} \quad (3.4)$$

The node 'a' is at voltage $(-V_1)$, because the voltage at the non-inverting input terminal is $(-V_1)$. So, with $V_i = 0$, we get,

$$I_1 = \frac{V_1}{R_1} \quad (3.5)$$

Also,

$$I_2 = \frac{V_2}{R_f} \quad (3.6)$$

For compensation, V_o should be zero for $V_i = 0$, that is, from Eq. (3.3) $V_2 = V_1$

So that,

$$I_2 = \frac{V_1}{R_f} \quad (3.7)$$

KCL at node 'a' gives,

$$I_B^- = I_2 + I_1 = \frac{V_1}{R_f} + \frac{V_1}{R_1} = V_1 \frac{(R_1 + R_f)}{R_1 R_f} \quad (3.8)$$

Assuming $I_B^- = I_B^+$ and using Eqs. (3.4) and (3.8) we get,

$$V_1 \frac{(R_1 + R_f)}{R_1 R_f} = \frac{V_1}{R_{\text{comp}}}$$

$$R_{\text{comp}} = \frac{R_1 R_f}{R_1 + R_f} = R_1 \parallel R_f \quad (3.9)$$

that is, to compensate for bias currents, the compensating resistor R_{comp} should be equal to the parallel combination of resistors tied to the inverting input terminal.

The effect of input bias current in a non-inverting amplifier can also be compensated by placing a compensating resistor, R_{comp} in series with the input signal V_i as shown in Fig. 3.1 (d).

The value of R_{comp} is again equal to

$$R_{\text{comp}} = R_1 \parallel R_f$$

as the circuits for inverting amplifier and non-inverting amplifier shown in Figs. 3.1 (c) and (d) become same with input signal V_i made equal to zero.

 


Fig. 3.1 (d) Bias current compensation in a non-inverting amplifier

3.2.2 Input Offset Current

Bias current compensation will work if both bias currents I_B^+ and I_B^- are equal. Since the input transistors cannot be made identical, there will always be some small difference between I_B^+ and I_B^- . This difference is called the offset current I_{os} and can be written as

$$|I_{os}| = I_B^- - I_B^+ \quad (3.10)$$

The absolute value sign indicates that there is no way to predict which of the bias currents will be larger.

Offset current I_{os} for BJT op-amp is 200 nA and that for FET op-amp is 10 pA. Even with bias current compensation, offset current will produce an output voltage when the input voltage V_i is zero. Referring to Fig. 3.1 (c),

$$V_1 = I_B^+ R_{\text{comp}} \quad (3.11)$$

and

$$I_1 = \frac{V_1}{R_1} \quad (3.12)$$

KCL at node 'a' gives,

$$I_2 = (I_B^- - I_1) = I_B^- - \left(I_B^+ \frac{R_{\text{comp}}}{R_1} \right) \quad (3.13)$$

Again

$$V_o = I_2 R_f - V_1 = I_2 R_f - I_B^+ R_{\text{comp}}$$

$$= \left(I_B^- - I_B^+ \frac{R_{\text{comp}}}{R_1} \right) R_f - I_B^+ R_{\text{comp}} \quad (3.14)$$

Substituting Eq. (3.9) and after algebraic manipulation,

$$V_o = R_f (I_B^- - I_B^+) \quad (3.15)$$

So,

$$V_o = R_f I_{os} \quad (3.16)$$

So even with bias current compensation and with the feedback resistor of 1 M Ω , a 741 BJT op-amp has an output offset voltage

$$V_o = 1 \text{ M}\Omega \times 200 \text{ nA} = 200 \text{ mV}$$

with a zero input voltage. It can be seen from Eq. (3.16) that the effect of offset current can be minimized by keeping feedback resistance small. Unfortunately, to obtain high input impedance, R_1 must be kept large. With R_1 large, the feedback resistor R_f must also be high so as to obtain reasonable gain.

The T-feedback network in Fig. 3.1 (e) is a good solution. This will allow large feedback resistance, while keeping the resistance to ground (seen by the inverting input) low as shown in the dotted network. The T-network provides a feedback signal as if the network were a single feedback resistor. By T to π conversion.

 


Fig. 3.1 (e) Inverting amplifier with T-feedback network