

## UNIT-2

### TRANSMISSION LINE PARAMETERS

#### Transmission line:

It acts as a medium to transfer energy from one point to another.

A transmission line can be classified as

- (i) - open wire or parallel wire or balanced wire.
- (ii) Co-axial cable.

#### ① Open wire:

- It is the basic form of transmission line.
- It is employed where <sup>at least</sup> two connectors are used.
- They are twisted in pairs, coming together and they are covered by a protective lead or sheath.


#### ② Co-axial cable

##### Disadvantages:

- High requirement of telephone cost and towers are needed.
- It is high initial cost.
- Maintain is difficult
- Possibility of short circuiting.
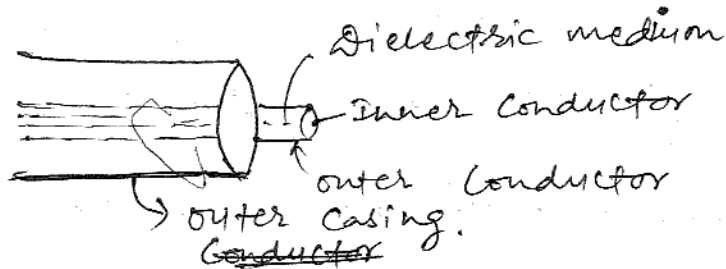
## ② Co-axial Cable

- It has got inner and outer conductors respectively.



- It is used for higher voltage level transmission
- It is used as ultra high frequency (UHF), microwave freq. (MHF).
- It is employed where one

### Wave guides

- It is employed where one conductor is used
- " " " at microwave frequencies - (high range of frequencies).

① ~~UHF~~ microwave freq.  $\rightarrow$  (  $10^8 \text{ Hz} - 10^{11} \text{ Hz}$   
 $10^9 \text{ Hz} - 10^{11} \text{ Hz}$  )


Eg. Rectangular wave guides

Circular " "

Parallel plates.

primary parameters of transmission line:

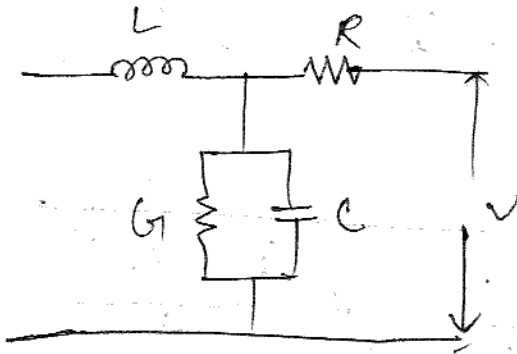- R → Resistance → loop resistance (ohm/km)
- L → Inductance → loop inductance per unit length (Henry/km)
- G → conductance → shunt conductance per unit length (mho/km)
- C → capacitance → shunt capacitance (Farad/km)




$Z \rightarrow$  series impedance  
 $Y \rightarrow$  shunt admittance

V. Imp.

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$

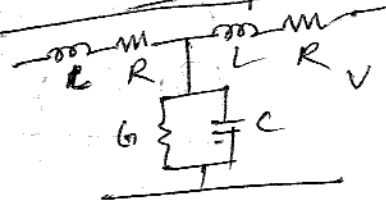

Secondary parameters

- \*  $Z_0 \rightarrow$  characteristic impedance
- \*  $\gamma$  or  $\Gamma$  (Gamma) → propagation constant.

$$Z_0 = \sqrt{Z/Y}$$

$$\gamma = \sqrt{ZY}$$

28/06/11

$$\gamma = \alpha + j\beta$$

- $\alpha \rightarrow$  Attenuation constant
- $\beta \rightarrow$  phase constant.

$$\gamma = \ln\left(\frac{Z_S}{Z_R}\right) \quad \text{or} \quad \ln\left(\frac{V_S}{V_R}\right)$$

$$Z_0 = \sqrt{Z/Y}$$



$$Z_{0T} = \sqrt{Z_1 Z_2 + \frac{Z_1^2}{4}} \quad \text{--- (1)}$$

T-Network

Total series imp  $\rightarrow Z_1 \rightarrow (R + j\omega L)$  length.

Total shunt impedance of T-N/W  $\rightarrow Z_2 \rightarrow \left( \frac{1}{G + j\omega C} \right)$  length. } (2)


from (1) & (2)

$$Z_{0T} = \sqrt{(R + j\omega L) \frac{1}{(G + j\omega C)} + \frac{(R + j\omega L)^2}{4}}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z_0 = \sqrt{Z/Y}$$

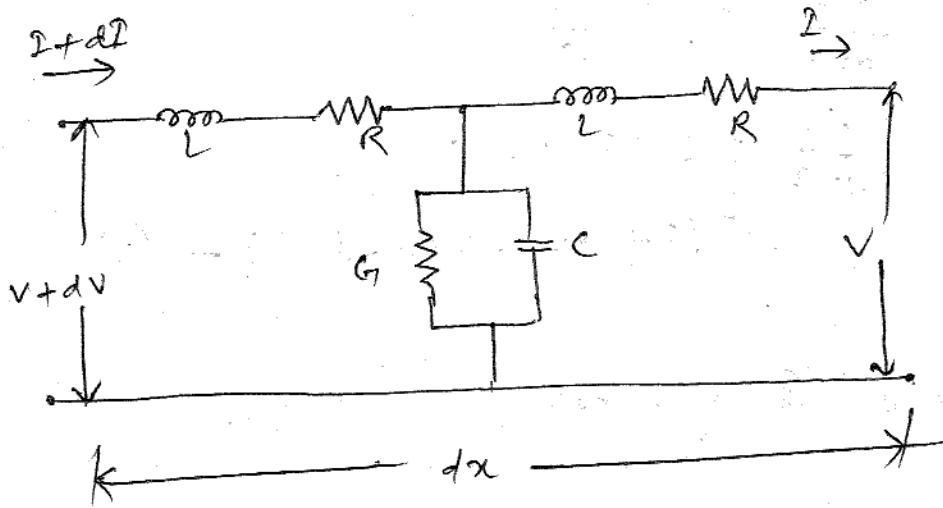V. Imp.  
General Solution of transmission



Series impedance  $(Z) = R + j\omega L$

admittance  $Y = G + j\omega C$

Series impedance of small section which can be expressed as  $\rightarrow (R + j\omega L) dx$

Shunt admittance of small section can be expressed as  $\rightarrow (G + j\omega C) dx$

The potential difference between two ends of the T-network is given by

$$(V + dV) - V = I (R + j\omega L) dx$$

$$\frac{dV}{dx} = I (R + j\omega L) = I Z \quad \text{--- (1)}$$

$$(I + dI) - I = V (G + j\omega C) dx$$

$$\frac{dI}{dx} = V (G + j\omega C) = V Y \quad \text{--- (2)}$$

diffn ① w.r. to  $x$

$$\frac{d^2 w}{dx^2} = 2 \frac{dI}{dx}$$

$$\frac{d^2 w}{dx^2} = 2 \cdot V(G + j\omega C)$$

$$= (R + j\omega L) \cdot V(G + j\omega C) \quad \text{--- (3)}$$

diffn ② w.r. to  $x$

$$\frac{d^2 y}{dx^2} = \frac{dV}{dx} \cdot Y$$

$$\frac{d^2 y}{dx^2} = I(R + j\omega L) (G + j\omega C) \quad \text{--- (4)}$$

But we know,

$$\gamma = \sqrt{ZY} = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

$$\frac{d^2 v}{dx^2} = \gamma^2 v \quad \text{--- (5)}$$

$$\frac{d^2 I}{dx^2} = \gamma^2 I \quad \text{--- (6)}$$

The soln of eqns ⑤ & ⑥ in terms of linear diffn. eqn.

$$V = A e^{\gamma x} + B e^{-\gamma x} \quad \text{--- (7)}$$

$$I = C e^{\gamma x} + D e^{-\gamma x} \quad \text{--- (8)}$$

26/06/2011

Given (9) write as

$$\frac{dv}{dx} = Ae^{\gamma x} \gamma - Be^{-\gamma x} \gamma \quad - (9)$$

$$\text{If, } \frac{dI}{dx} = A ce^{\gamma x} \gamma - De^{-\gamma x} \gamma \quad - (10)$$

we know,

$$\frac{dv}{dx} = IZ \quad - \text{[From (1)]}$$

Comparing (9) & (10)

$$IZ = Ae^{\gamma x} \gamma - B\gamma e^{-\gamma x}$$

$$I = \frac{Ae^{\sqrt{zy} x} \sqrt{zy} - Be^{-\sqrt{zy} x} \sqrt{zy}}{\sqrt{zy}} \quad [\because \gamma = \sqrt{zy}]$$

$$\therefore I = Ae^{\sqrt{zy} x} \frac{\sqrt{y}}{\sqrt{z}} - Be^{-\sqrt{zy} x} \frac{\sqrt{y}}{\sqrt{z}} \quad - (11)$$

again,

$$\frac{dI}{dx} = vY$$

$$Ce^{\gamma x} \cdot \gamma - De^{-\gamma x} \gamma = vY$$

$$Ce^{\sqrt{zy} x} \sqrt{zy} - De^{-\sqrt{zy} x} \sqrt{zy} = vY$$

$$Ce^{\sqrt{zy} x} \sqrt{z/y} - De^{-\sqrt{zy} x} \sqrt{z/y} = v$$

$$\therefore v = C\sqrt{z/y} e^{\sqrt{zy} x} - D\sqrt{z/y} e^{-\sqrt{zy} x} \quad - (12)$$

$$V = Ae \quad (\text{short ckt})$$

Being small transmission line,  $\alpha = 0$   
and voltage at receiving  $(V_R) = V$   
current " "  $(I_R) = I$

Sub. above values in (11) & (12),

Then,

$$V_R = A + B \rightarrow (13) \quad [\text{from eqn (9) \& (8)}]$$

$$I_R = C + D \rightarrow (14)$$

$\therefore V_R = A$  ~~from~~ again from (11) & (12)

$$I_R = A\sqrt{Y/Z} - B\sqrt{Y/Z} \quad (15)$$

$$V_R = C\sqrt{Z/Y} - D\sqrt{Z/Y} \quad (16)$$

$$\alpha = \sqrt{Z/Y}$$

$$1/\alpha = \sqrt{Y/Z}$$

$$I_R = \frac{A}{\alpha} - \frac{B}{\alpha} \quad (17) \quad (\text{from above})$$

$$V_R = C\alpha - D\alpha \quad (18)$$

we know

$$I_R = C + D \quad [\text{from (14)}]$$

By comparing,

$$C + D = \frac{1}{\alpha}(A - B)$$

$$C\alpha + D\alpha = A - B \quad (19)$$



$$V_R = Cx - Dx \quad (\text{From 18})$$

$$A+B = Cx - Dx \quad [\text{from (13) \& (18)}] \quad - (19) \quad (20)$$

Solving eqns (19) \& (20)

$$\cancel{A+B} + A+B$$

$$A+B + A+B = Cx - Dx + Cx + Dx$$

$$\boxed{A = Cx} \quad - (21)$$

Sub  $A = Cx$  in (20) then

$$Cx + B = Cx - Dx$$

$$\boxed{B = -Dx} \quad - (22)$$

$$\therefore \boxed{V_R = Cx - Dx} \quad - (23)$$

But  $I_R = C+D$ , multiply by  $x$  on both sides,

$$I_R x = Cx + Dx \quad - (24)$$

$$V_R = Cx - Dx$$

Adding (23) \& (24)

$$V_R + I_R x = Cx - Dx + Cx + Dx$$

$$V_R + I_R x = 2Cx$$

$$\therefore C = \frac{V_R}{2x} + \frac{I_R}{2} \quad - (25)$$

Sub: (24) from (23)

$$V_R - D_R x = Cx + Dn - Cx - Dn$$

$$\frac{V_R - D_R}{2a} = -D$$

$$D = \frac{D_R}{2} - \frac{V_R}{2a} \quad \text{--- (26)}$$

$$C = \frac{V_R}{2a} + \frac{D_R}{2} \quad \left[ \begin{array}{l} \text{from 25 \&} \\ x = \sqrt{2/4} \end{array} \right]$$
$$= \frac{D_R}{2} + \frac{V_R}{2\sqrt{2/4}}$$

$$C = \frac{D_R}{2} + \frac{V_R}{2} \sqrt{1/2} \quad \text{--- (27)}$$

$$D = \frac{D_R}{2} - \frac{V_R}{2a} \quad \left[ \begin{array}{l} \text{from 26 \& } x = \sqrt{2/4} \end{array} \right]$$

$$= \frac{D_R}{2} - \frac{V_R}{2} \sqrt{1/2} \quad \text{--- (28)}$$

we know,

$$A = Cx$$

$$\therefore \boxed{A = \frac{D_R}{2} x + \frac{V_R}{2}} \quad \text{--- (29)}$$

$$B = -Dn$$

$$\boxed{B = -\frac{D_R}{2} n + \frac{V_R}{2}} \quad \text{--- (30)}$$

3/06/11

$$A = Cx$$

$$B = \frac{V_R}{2} - \frac{I_R}{2} \sqrt{z/y} \quad [B = -Dx]$$

$$C = \frac{I_R}{2} + \frac{V_R}{2} \sqrt{y/z}$$

$$D = \frac{I_R}{2} - \frac{V_R}{2} \sqrt{y/z}$$

$$V_R = A \sqrt{z/y} e^{\sqrt{z/y} x} - B \sqrt{z/y} e^{-\sqrt{z/y} x}$$

$$I_R = C \sqrt{y/z} e^{\sqrt{z/y} x} - D \sqrt{y/z} e^{-\sqrt{z/y} x}$$

$$A = Cx$$

$$= \frac{I_R}{2} \sqrt{z/y} + \frac{V_R}{2}$$

$$[x = \sqrt{z/y}]$$

$$V = \frac{V_R}{2} \left[ 1 + \frac{z_0}{z_R} \right] e^{\sqrt{z/y} x} + \frac{V_R}{2} \left[ 1 - \frac{z_0}{z_R} \right] e^{-\sqrt{z/y} x}$$

$$A = \frac{V_R}{2} + \frac{I_R}{2} \sqrt{z/y}$$

$$\begin{aligned} \because V &= I_R z_R \\ V_R &= I_R z_R \\ V_R / z_R &= I_R \end{aligned}$$

$$A = \frac{V_R}{2} \left[ 1 + \frac{z_0}{z_R} \right]$$

$$- (31) \quad \left( z_0 = \sqrt{z/y} \right)$$

$$B = \frac{V_R}{2} \left[ 1 - \frac{z_0}{z_R} \right]$$

(32)

$$C = \frac{V_R}{2Z_R} - \frac{V_R}{2} \frac{1}{Z_0}$$

$$C = \frac{I_R}{2} \left[ 1 + \frac{Z_R}{Z_0} \right] \quad (33)$$

$$D = \frac{I_R}{2} \left[ 1 - \frac{Z_R}{Z_0} \right] \quad (34)$$

$$V = \frac{V_R}{2} \left( 1 + \frac{Z_0}{Z_R} \right) e^{\sqrt{2Y}x} + \frac{V_R}{2} \left( 1 - \frac{Z_0}{Z_R} \right) e^{-\sqrt{2Y}x} \quad (35)$$

$$I = \frac{I_R}{2} \left( 1 + \frac{Z_R}{Z_0} \right) e^{\sqrt{2Y}x} - \frac{I_R}{2} \left( 1 - \frac{Z_R}{Z_0} \right) e^{-\sqrt{2Y}x} \quad (36)$$

$$V = \frac{V_R}{2} \left[ \left( 1 + \frac{Z_0}{Z_R} \right) e^{\sqrt{2Y}x} + \left( 1 - \frac{Z_0}{Z_R} \right) e^{-\sqrt{2Y}x} \right] \quad (37)$$

$$I = \frac{I_R}{2} \left[ \left( 1 + \frac{Z_R}{Z_0} \right) e^{\sqrt{2Y}x} - \left( 1 - \frac{Z_R}{Z_0} \right) e^{-\sqrt{2Y}x} \right] \quad (38)$$

$$V = V_R \left[ \frac{e^{\sqrt{2Y}x} + e^{-\sqrt{2Y}x}}{2} \right] + I_R Z_0 \left[ \frac{e^{\sqrt{2Y}x} - e^{-\sqrt{2Y}x}}{2} \right]$$

$$V = V_R \cosh \sqrt{2Y}x + I_R Z_0 \sinh \sqrt{2Y}x \quad (39)$$

$$I = I_R \cosh \sqrt{2Y}x + \frac{V_R}{Z_0} \sinh \sqrt{2Y}x \quad (40)$$

## Physical significance of

physical significance of general solution ~~line~~ <sup>of</sup> transmission line.

From general solution,

$$\gamma = \sqrt{ZY}$$

$$x = l$$

$$V = V_S = V_R \cosh \gamma l + I_R Z_0 \sinh \gamma l \quad \text{--- (1)}$$

$$I = I_S = I_R \cosh \gamma l + \frac{V_R}{Z_0} \sinh \gamma l \quad \text{--- (2)}$$

$V_S \rightarrow$  sending voltage

$I_S \rightarrow$  " current.

v=32

we know that,  $V_R = I_R Z_R$  sub in (1) & (2)

$$V_S = I_R [Z_R \cosh \gamma l + Z_0 \sinh \gamma l] \quad \text{--- (3)}$$

$$I_S = I_R \left[ \cosh \gamma l + \frac{Z_R}{Z_0} \sinh \gamma l \right] \quad \text{--- (4)}$$

$$Z_S = \frac{V_S}{I_S} = \left[ \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{\cosh \gamma l + \frac{Z_R}{Z_0} \sinh \gamma l} \right]$$


$$Z_S = Z_0 \left[ \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \right] \quad \text{--- (5)}$$

When receiving end impedance is terminated by its characteristic impedance


$Z_0$  then the eqn (5) can be written as

$$i.e. Z_0 \leftrightarrow Z_R$$
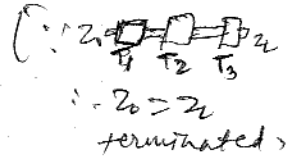
$$Z_s = Z_0 \left( \frac{Z_0 (\cosh \gamma l + \sinh \gamma l)}{Z_0 (\cosh \gamma l + \sinh \gamma l)} \right)$$


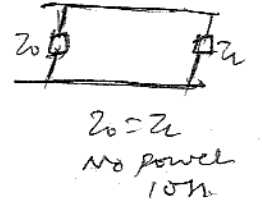
$$\therefore Z_s = Z_0 \left( \frac{\cosh \gamma l + \sinh \gamma l}{\cosh \gamma l + \sinh \gamma l} \right)$$



$$\therefore \boxed{Z_s = Z_0} \quad \text{--- (5)}$$

Now, consider an infinite length or infinite transmission line with length  $l \rightarrow \infty$ , so eqn (5)

$$Z_s = Z_0 \left( \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \right)$$

$$= Z_0 \frac{\cosh \gamma l}{\cosh \gamma l} \left( \frac{Z_R + Z_0 \tanh \gamma l}{Z_0 + Z_R \tanh \gamma l} \right)$$

$$= Z_0 \left( \frac{Z_R + Z_0 \tanh \gamma \infty}{Z_0 + Z_R \tanh \gamma \infty} \right)$$

$$\left( \begin{array}{l} l \rightarrow \infty \\ \tanh \gamma \infty = 1 \end{array} \right)$$

$$= Z_0 \left( \frac{Z_R + Z_0}{Z_0 + Z_R} \right)$$

$$= Z_0$$

$$\therefore \boxed{Z_s = Z_0} //$$

→ It is the ratio of reflected voltage at the load to the incident voltage at the load. It can be denoted as  $k'$ .

$$\text{i.e. } k = \frac{V_R}{V_S} \quad , \quad -k = \frac{I_R}{I_S}$$

Also,

$$k = \frac{Z_R - Z_0}{Z_R + Z_0}$$

$$V = \frac{V_R}{2} \left[ \frac{Z_R + Z_0}{Z_R} \cdot e^{\gamma x} + \frac{Z_R - Z_0}{Z_0} e^{-\gamma x} \right]$$

↗ incident voltage      ↖ reflected voltage

$$= \frac{V_R (Z_R + Z_0)}{2Z_R} e^{\gamma x} + \frac{V_R (Z_R - Z_0)}{2Z_0} e^{-\gamma x}$$