

→ It is the ratio of reflected voltage at the load to the incident voltage at the load.

It can be denoted as K' .

$$\text{i.e. } K = \frac{V_R}{V_S} \quad , \quad -K = \frac{I_R}{I_S}$$

Also,

$$K = \frac{Z_R - Z_0}{Z_R + Z_0}$$

$$V = \frac{V_R}{2} \left[\frac{Z_R + Z_0}{Z_R} e^{\gamma x} + \frac{Z_R - Z_0}{Z_0} e^{-\gamma x} \right]$$

↗ incident voltage
↖ reflected voltage

$$= \frac{V_R (Z_R + Z_0)}{2Z_R} e^{\gamma x} + \frac{V_R (Z_R - Z_0)}{2Z_0} e^{-\gamma x}$$

J.S
02107111

04/07/2011

By defn of K ,

$$\frac{V_R (Z_R - Z_0)}{2Z_R} = \frac{V_R (Z_R + Z_0)}{2Z_R}$$

$$\therefore K = \frac{Z_R - Z_0}{Z_R + Z_0} //$$

If transmission line is terminated by its characteristic eqn, then the value of K is,

$$K = 0 / Z_R + Z_0$$

$$\therefore K = 0 //$$

04/07/21/

Transmission line solution

$$\gamma = \alpha + j\beta$$

$$\gamma = \sqrt{ZY}$$

$$Y = G + j\omega C$$

$$Z = R + j\omega L$$

Distortionless line

$$\frac{R}{L} = \frac{G}{C}$$

$$RC = LG$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

$$\gamma^2 = RG + j\omega RC + j\omega LC - \omega^2 LC$$

$$\gamma^2 = RG - \omega^2 LC + j(\omega RC + \omega LC)$$

$$\gamma^2 = RG + 2j\omega \sqrt{RC LG} - \omega^2 LC$$

$$\gamma^2 = (\sqrt{RG} + j\omega\sqrt{LC})^2$$

$$(\alpha + j\beta)^2 = (\sqrt{RG} + j\omega\sqrt{LC})^2$$

$$\alpha + j\beta = \sqrt{RG} + j\omega\sqrt{LC}$$

Now by equating

$$\alpha = \sqrt{RG}$$

$$\beta = \omega\sqrt{LC}$$

$$\lambda = c/f$$

$$c \text{ or } v = \lambda f$$

$$= \lambda f \times \frac{2\pi}{2\pi}$$

$$= 2\pi f \cdot \lambda / 2\pi$$

Velocity
of
propagation

$$= \omega / \beta$$

$$= \frac{\omega}{\omega \sqrt{LC}}$$

$$(\because \beta = 2\pi/\lambda)$$

$$V = \frac{1}{\sqrt{LC}} = V_p$$

wavelength: distance travelled by electromagnetic wave along the transmission line with the phase change of 2π rad.

waveform distortion:

When the received signal is not the exact replica of transmitted signal, then we can say distortion occurs in a transmission line.

phase distortion: due to the variation of phase (β).

Frequency distortion: due to ~~with~~ variations of ~~α~~ attenuation (α).

$$\alpha = \sqrt{\frac{RG - \omega^2 LC + \sqrt{(RG - \omega^2 LC)^2 + \omega^2(LR + GC)^2}}{2}}$$

$$\beta = \sqrt{\frac{\omega^2 LC - RG + \sqrt{(RG - \omega^2 LC)^2 + \omega^2(LG + RC)^2}}{2}}$$

Distortionless line:

The line in which there is no phase or frequency distortion and also the line is ~~also~~ properly terminated. Then the line is said to be distortionless line.

then

$$\beta = \frac{(RG - \omega^2 LC)^2 + \omega^2(LG + RC)^2}{(RG + \omega^2 LC)^2}$$

For β to be a direct function of frequency,

०७१०७१११

$$(RG - \omega^2 LC)^2 + \omega^2(LG + RC)^2 = (RG + \omega^2 LC)^2$$

$$\Rightarrow R^2 G^2 - 2\omega^2 RGLC + \omega^4 L^2 C^2 + \omega^2 L^2 G^2 + 2\omega^2 LGR C + \omega^2 R^2 C^2 = R^2 G^2 + 2\omega^2 L^2 C RG + \omega^4 L^2 C^2$$

$$\Rightarrow \omega^2 L^2 G^2 + \omega^2 R^2 C^2 = 2\omega^2 L^2 C RG$$

$$\omega^2 (L^2 G^2 + R^2 C^2) = 2\omega^2 L^2 C RG$$

$$\Rightarrow L^2 \omega^2 + R^2 C^2 - 2 L G R C = 0$$

$$\Rightarrow (L G - R C)^2 = 0$$

$$L G = R C$$

$$\boxed{\frac{R}{L} = \frac{G}{C}}$$

TELEPHONE CABLE

They are twisted in pair combined together and covered by external loading. This construction results in negligible value of conductance (G) and Inductance.

$$Z = R + j \omega L$$

$$Y = G + j \omega C$$

$$L \omega \ll R$$

$$G \ll \omega C$$

$$\gamma = \sqrt{ZY} = \sqrt{j \omega R C} = \sqrt{\omega R C} \angle 90^\circ$$

$$= \sqrt{\omega R C} \angle 45^\circ$$

$$= \sqrt{\omega R C} (\cos 45^\circ + j \sin 45^\circ)$$

$$= \sqrt{\omega R C} \left[\frac{1}{\sqrt{2}} + j \frac{1}{\sqrt{2}} \right]$$

$$= \sqrt{\frac{\omega R C}{2}} + j \sqrt{\frac{\omega R C}{2}}$$

$$\gamma = \alpha + j \beta$$

$$\alpha = \sqrt{\frac{\omega R C}{2}} \quad \& \quad \beta = \sqrt{\frac{\omega R C}{2}}$$

$$v_p = \omega / \beta = \frac{\omega}{\sqrt{\frac{\omega RC}{2}}}$$

$$= \sqrt{\frac{2\omega}{\omega RC}}$$

$$v_p = \sqrt{\frac{2\omega}{RC}}$$

$$z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

↳ Negligible

$$z_0 = \sqrt{\frac{R}{j\omega C}}$$

$$z_0 = \sqrt{\frac{R}{\omega C}} \angle -45^\circ$$

LOADED LINES (To achieve distortionless line)

$$\uparrow \frac{1}{C}$$

- Lumped Loading
- patch
- Continuous loading

Input impedance of a transmission line!

$$Z = \frac{V}{I} = \frac{E}{H}$$

$$Z_s(\omega) Z_{in} = \frac{V_s}{I_s} =$$


$$\frac{V_s}{I_s} = \frac{V_R \left[\cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l \right]}{I_R \left[\cosh \gamma l + \frac{Z_R}{Z_0} \sinh \gamma l \right]}$$

$$\boxed{Z = l}$$

$$= \frac{I_R Z_R}{I_R} \left[\frac{Z_R \cosh \sqrt{ZY} l + Z_0 \sinh \sqrt{ZY} l}{Z_R} \right] \left[\frac{Z_0 \cosh \sqrt{ZY} l + Z_R \sinh \sqrt{ZY} l}{Z_0} \right]$$

$$\boxed{Z_s(\omega) Z_{in} = Z_0 \left[\frac{Z_R \cosh \sqrt{ZY} l + Z_0 \sinh \sqrt{ZY} l}{Z_0 \cosh \sqrt{ZY} l + Z_R \sinh \sqrt{ZY} l} \right]} \quad \text{--- (1)}$$

open and short ckted in tran line!

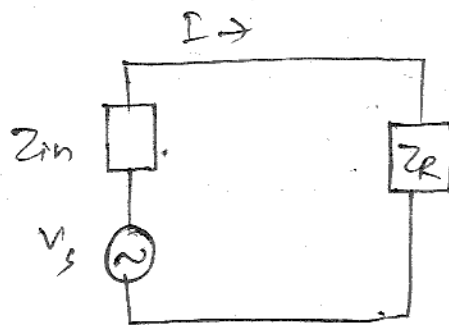

$$Z_{sc} \rightarrow Z_R = 0 \text{ in --- (1)}$$

$$Z_{sc} = Z_0 \tanh \sqrt{ZY} l$$

$$Z_{OC} \rightarrow Z_R = \infty$$

$$= Z_0 \frac{Z_R}{Z_R} \left[\frac{\cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l}{\sinh \gamma l + \frac{Z_0}{Z_R} \cosh \gamma l} \right]$$

$$= Z_0 [\coth \gamma l]$$

$$Z_{sc} \cdot Z_{oc} = Z_0^2$$

$$Z_0 = \sqrt{Z_{sc} Z_{oc}}$$

$$Z_T = \frac{V_S}{I_S} = \frac{I_{RZ_R}}{I_R} \left[\text{transfer impedance } (Z_T) \right]$$

$$V_S = \frac{Z_R}{2} \cdot \frac{Z_R + Z_0}{Z_R} \left[e^{\gamma l} + k e^{-\gamma l} \right]$$

↳ Reflection coefficient

$$k = \frac{Z_R - Z_0}{Z_R + Z_0}$$

$$= \frac{Z_R}{2Z_R} (Z_R + Z_0) \left[e^{\gamma l} + k e^{-\gamma l} \right]$$

$$= \left(\frac{Z_R + Z_0}{2} \right) e^{\gamma l} + \left(\frac{Z_R + Z_0}{2} \right) k e^{-\gamma l}$$


$$= \frac{Z_R + Z_0}{2} e^{\gamma l} + k \left(\frac{Z_R + Z_0}{2} \right) \frac{(Z_R - Z_0)}{Z_R + Z_0} e^{-\gamma l}$$

$$= Z_R \left[\frac{e^{\gamma l} + e^{-\gamma l}}{2} \right] + Z_0 \left[\frac{e^{\gamma l} - e^{-\gamma l}}{2} \right]$$

$$Z_T = Z_R \cosh \gamma l + Z_0 \sinh \gamma l$$

Insertion loss (I_L) : (loss of energy in tran. line)

$$I_L = 20 \log \frac{P_i}{P_o}$$

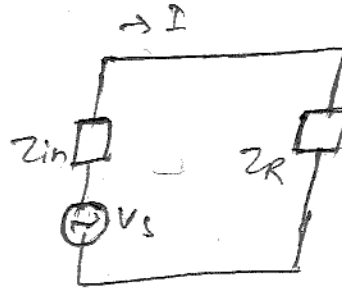

when Z_{in} & Z_R
are in same
phase.

