

eq (20) & (21) represents the general solution of Transmission line.

In another way of representing eq (20) as.

$$E = \frac{E_R}{2Z_R} \left[(Z_R + Z_0)e^{\sqrt{ZY}x} + (Z_R - Z_0)e^{-\sqrt{ZY}x} \right]$$

$$I = \frac{I_R}{2Z_0} \left[(Z_R + Z_0)e^{\sqrt{ZY}x} - (Z_R - Z_0)e^{-\sqrt{ZY}x} \right]$$

J.S.
01/07/11

$$E = \frac{E_R}{2Z_R} \left[Z_R e^{\sqrt{ZY}x} + Z_0 e^{\sqrt{ZY}x} + Z_R e^{-\sqrt{ZY}x} - Z_0 e^{-\sqrt{ZY}x} \right]$$

$$E = \frac{E_R}{\cancel{2Z_R}} \left[\frac{e^{\sqrt{ZY}x} + e^{-\sqrt{ZY}x}}{2} \right] + \frac{Z_0 E_R}{\cancel{2Z_R}} \left[\frac{e^{\sqrt{ZY}x} - e^{-\sqrt{ZY}x}}{2} \right]$$

Sub. $Z_R = \frac{E_R}{I_R} \Rightarrow \frac{E_R}{Z_R} = I_R$

$$E = E_R \left[\frac{e^{\sqrt{ZY}x} + e^{-\sqrt{ZY}x}}{2} \right] + I_R Z_0 \left[\frac{e^{\sqrt{ZY}x} - e^{-\sqrt{ZY}x}}{2} \right]$$

— (22)

Similarly,

$$I = I_R \left[\frac{e^{\sqrt{ZY}S} + e^{-\sqrt{ZY}S}}{2} \right] + \frac{E_R}{Z_0} \left[\frac{e^{\sqrt{ZY}S} - e^{-\sqrt{ZY}S}}{2} \right] \quad (23)$$

But $\frac{e^{\sqrt{ZY}S} + e^{-\sqrt{ZY}S}}{2} = \cosh \sqrt{ZY}S$ &

$$\frac{e^{\sqrt{ZY}S} - e^{-\sqrt{ZY}S}}{2} = \sinh \sqrt{ZY}S$$

sub in (22) & (23)

$$E = E_R \cosh \sqrt{ZY}S + I_R Z_0 \sinh \sqrt{ZY}S \quad (24)$$

$$I = I_R \cosh \sqrt{ZY}S + \frac{E_R}{Z_0} \sinh \sqrt{ZY}S \quad (25)$$

The eq. (24) & (25) gives the value of E & I at any pt along the length of the line.

' x ' distance of sending end (IX)

$$x = l - s$$

$s \rightarrow$ Receiving end distance.

eq. (24) & (25) get transferred in terms of E_s & I_s

$$E_R = E_s \quad \& \quad I_R = I_s \quad \& \quad s = x$$

$$E = E_s \cosh(\sqrt{ZY}x) + I_s Z_0 \sinh \sqrt{ZY}x \quad - (26)$$

$$I = I_s \cosh(\sqrt{ZY}x) + \frac{E_s}{Z_0} \sinh \sqrt{ZY}x \quad - (27)$$

Physical Significance of Transmission Line :-

Consider the general solution of transmission line in a receiving end is :-

$$E = E_R \cosh(\gamma s) + I_R Z_0 \sinh(\gamma s)$$

$$I = I_R \cosh(\gamma s) + \frac{E_R}{Z_0} \sinh(\gamma s)$$

sending end current can be obtained by substituting $s = l$

$$E = E_R \cosh(\gamma l) + I_R Z_0 \sinh(\gamma l) \quad - (1)$$

$$I = I_R \cosh(\gamma l) + \frac{E_R}{Z_0} \sinh(\gamma l) \quad - (2)$$

But,

$$Z_R = \frac{E_R}{I_R}$$

sub in (2) $Z_R = \frac{E_R}{I_R} \Rightarrow E_R = Z_R I_R$

$$I_S = I_R \cosh(\gamma l) + \frac{Z_R I_R \sinh(\gamma l)}{Z_0}$$

$$I_S = I_R \left[\cosh(\gamma l) + \frac{Z_R \sinh(\gamma l)}{Z_0} \right]$$

$$\frac{I_S}{I_R} = \cosh(\gamma l) + \frac{Z_R \sinh(\gamma l)}{Z_0} \quad (3)$$

$$\left[\because Z_R = Z_0 \right]$$

$$\frac{I_S}{I_R} = \cosh(\gamma l) + \sinh(\gamma l) = e^{\gamma l}$$

$$\frac{I_S}{I_R} = e^{\gamma l} \quad (4)$$

If the line is terminated in Z_0 & using $E_R = Z_R I_R$ in eq (1) we get

$$E_S = Z_R I_R \cosh(\gamma l) + I_R Z_0 \sinh(\gamma l)$$

$$E_S = I_R \left[Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l) \right] \quad (5)$$

Divide eq (5) by eq (3)

$$\frac{E_S}{I_S} = \frac{I_R \left[Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l) \right]}{I_R \left[\cosh(\gamma l) + \frac{Z_R \sinh(\gamma l)}{Z_0} \right]}$$

$$\frac{E_s}{I_s} = \frac{Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l)}{\cosh(\gamma l) + \frac{Z_R}{Z_0} \sinh(\gamma l)}$$

$$Z_s = Z_0 \left[\frac{Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l)}{\cosh(\gamma l) + \frac{Z_R}{Z_0} \sinh(\gamma l)} \right]$$

$$\left[\frac{Z_0 \cosh(\gamma l) + Z_R \sinh(\gamma l)}{\cosh(\gamma l) + \frac{Z_R}{Z_0} \sinh(\gamma l)} \right] \quad \text{--- (6)}$$

$$\left[Z_R = Z_0 \right]$$

$$\boxed{Z_s = Z_0}$$

When the line is terminated in Z_0 , $Z_R = Z_0$

This shows that line terminated in Z_0 , its i/p impedance is characteristic impedance

Consider an infinite line with $l \rightarrow \infty$ sub in eq (6)


Multiplying $\frac{1}{\cosh(\gamma l)}$ in num. & denom in eq (6)

$$Z_s = Z_0 \left[\frac{Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l)}{Z_0 + Z_R \tanh(\gamma l)} \right] \quad \left[\begin{array}{l} \tanh(\infty) \\ = 1 \end{array} \right]$$

$$Z_s = \frac{Z_0 [Z_A + Z_0]}{Z_A + Z_0}$$

$$Z_s = Z_0$$

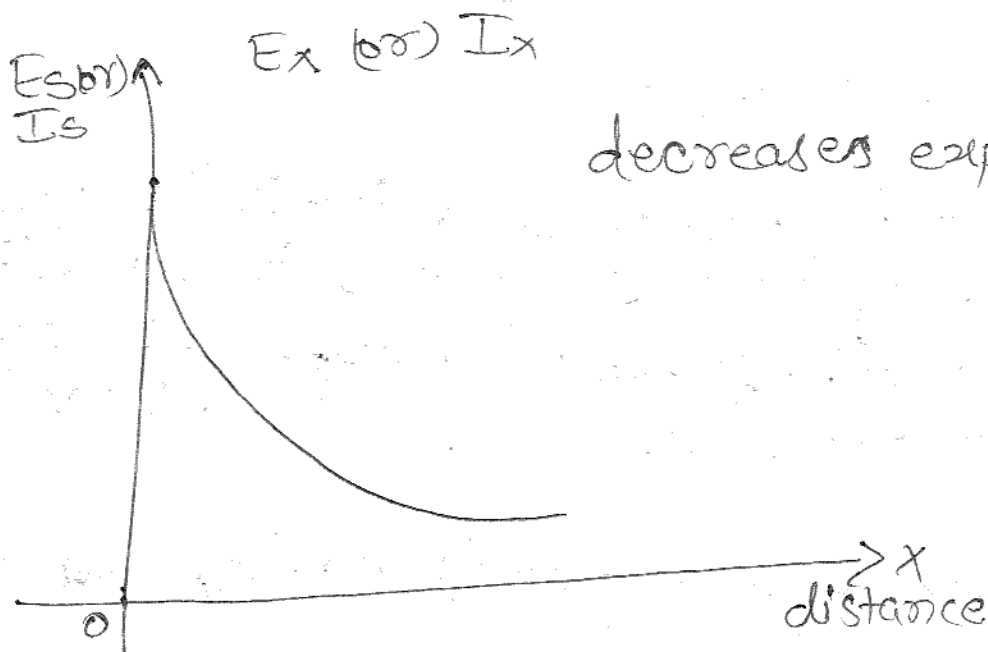This shows that finite line terminated in its characteristic impedance behaves like an infinite line




$$E_x = E_s e^{-\alpha x}$$

$$I_x = I_s e^{-\alpha x}$$

If the instruments are connected along the line, then the instruments will show the magnitude while the phase angle cannot be obtained.

$$\tan(\infty) = 1$$

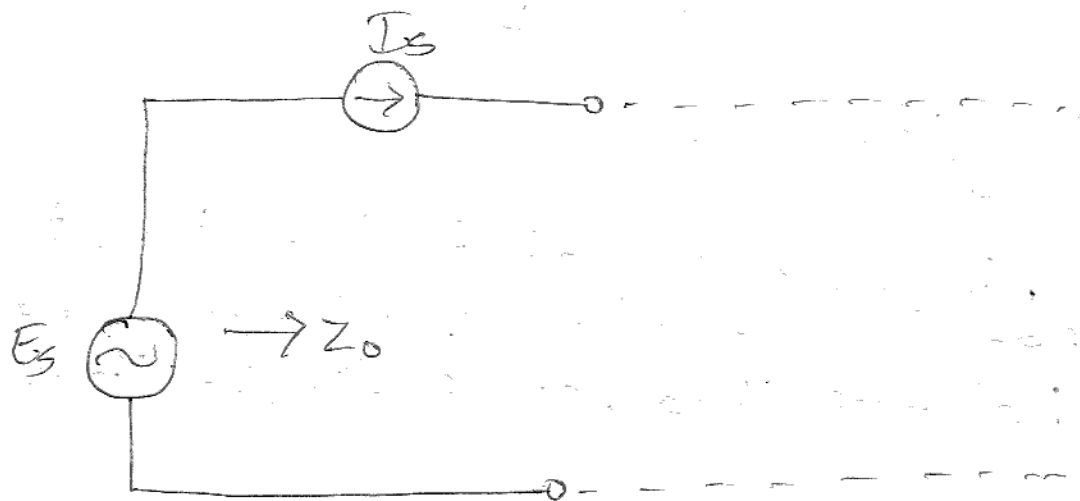Infinite line: - (only sender
not receiver)



$$Z_s = \frac{E_s}{I_s}$$

Input impedance of infinite line is Z_0 of transmission line and it is denoted by Z_0 . Therefore, Z_0 plays important role in Transmission line.

Z_0 is phasor quantity having magnitude $|Z_0|$ & angle is ϕ

Magnitude and angle of Z_0 is vary with freq.

Important Property of Infinite line

1. As the line as infinite length, no waves will reach the receiving end & hence there is no possibility of reflection at receiving end.

under
river)

Thus there cannot be any reflected waves & the complete power is observed by the transmission line.

2. As reflected waves are absent, Z_0 decides the flow of current when a vge is applied to the sending end. The current will not be affected by terminated impedance (Z_R) at receiving end. This condition is fulfilled by long line in practice.

line
and it
to plays
in line.

Distortion less line :-

magnitude

A line in which there is no phase or frequency distortion and also it is correctly terminated called as distortion less line.

vary

Consider $\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$

Squaring on both sides:-

finite
line

$$\gamma^2 = (R+j\omega L)(G+j\omega C)$$

with no

$$\gamma^2 = RG + Rj\omega C + Gj\omega L + j^2\omega^2 LC$$

giving
possibility

$$\gamma^2 = RG + Rj\omega C + Gj\omega L - \omega^2 LC$$

end.

$$\gamma^2 = (RG - \omega^2 LC) + j\omega(RC + GL) \quad \text{--- (1)}$$

For minimum attenuation one condition is there :-

$$L = \frac{CR}{G}$$

~~For minimum~~

$$LG = CR \text{ sub in (1)}$$

$$\gamma^2 = (RG - \omega^2 LC) + j\omega(RC + RC)$$

$$\gamma^2 = (RG - \omega^2 LC) + j2\omega RC$$

$$\text{But } RC = LG = \sqrt{RCLG}$$

$$\gamma^2 = (RG - \omega^2 LC) + j2\omega \sqrt{RCLG}$$

$$\gamma^2 = (\sqrt{RG} + j\omega\sqrt{LC})^2$$

$$\gamma = \sqrt{RG} + j\omega\sqrt{LC} \quad \text{--- (2)}$$

$$\text{But } \gamma = \alpha + j\beta$$

$$\alpha = \sqrt{RG} \quad \text{--- (3)}$$

$$\beta = \omega\sqrt{LC} \quad \text{--- (4)}$$

22) - (1) It can be seen from eq (3) that α does not vary with frequency which eliminates the ~~dist~~ freq. distortion.

$$v = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$v = \frac{1}{\sqrt{LC}}$$

Thus for condition $LG = RC$ the velocity becomes independent of frequency. This eliminates the phase distortion.

It is already proved that $RC = LG$, Z_0 become resistive and line can be correctly terminated to eliminate distortion due to Z_0 varying with frequency. Thus the overall distortion are eliminated.

$$\therefore \boxed{RC = LG} \Rightarrow \boxed{\frac{R}{G} = \frac{L}{C}}$$

Telephone Cable :-

(It is underground cable)

Since inductance & conductance is negligible it can be neglected and hence impedance & admittance of such a cable can be written by

$$Z = R$$

$$Y = j\omega C$$

$$\gamma = \sqrt{ZY} = \sqrt{j\omega RC}$$

Divide by 2 in num. & denom.

$$\gamma = \sqrt{\frac{j2\omega RC}{2}}$$

$$\sqrt{j} = \sqrt{1 \angle 90^\circ}$$

$$= 1 \angle 45^\circ$$

$$\sqrt{2j} = (1+j1)$$

$$\gamma = (1+j1) \sqrt{\frac{\omega RC}{2}}$$

$$\left\{ j = 1 \angle 90^\circ \right\}$$

$$\left\{ \sqrt{\angle 90^\circ} = \angle 90^\circ / 2 \right\}$$

$$\gamma = \sqrt{\frac{\omega RC}{2}} + j\sqrt{\frac{\omega RC}{2}} = \alpha + j\beta$$

$$\alpha = \sqrt{\frac{\omega RC}{2}}, \quad \beta = \sqrt{\frac{\omega RC}{2}}$$

$$v = \frac{\omega}{\beta} = \frac{\omega \sqrt{2}}{\sqrt{\omega RC}}$$


$$v = \sqrt{\frac{2\omega}{RC}}$$

Both α & v are the functions of frequency ω

Hence for high frequencies there is large attenuation & also velocity

Hence wave travels very fast than lower frequencies when freq. is high.

Wavelength and Velocity

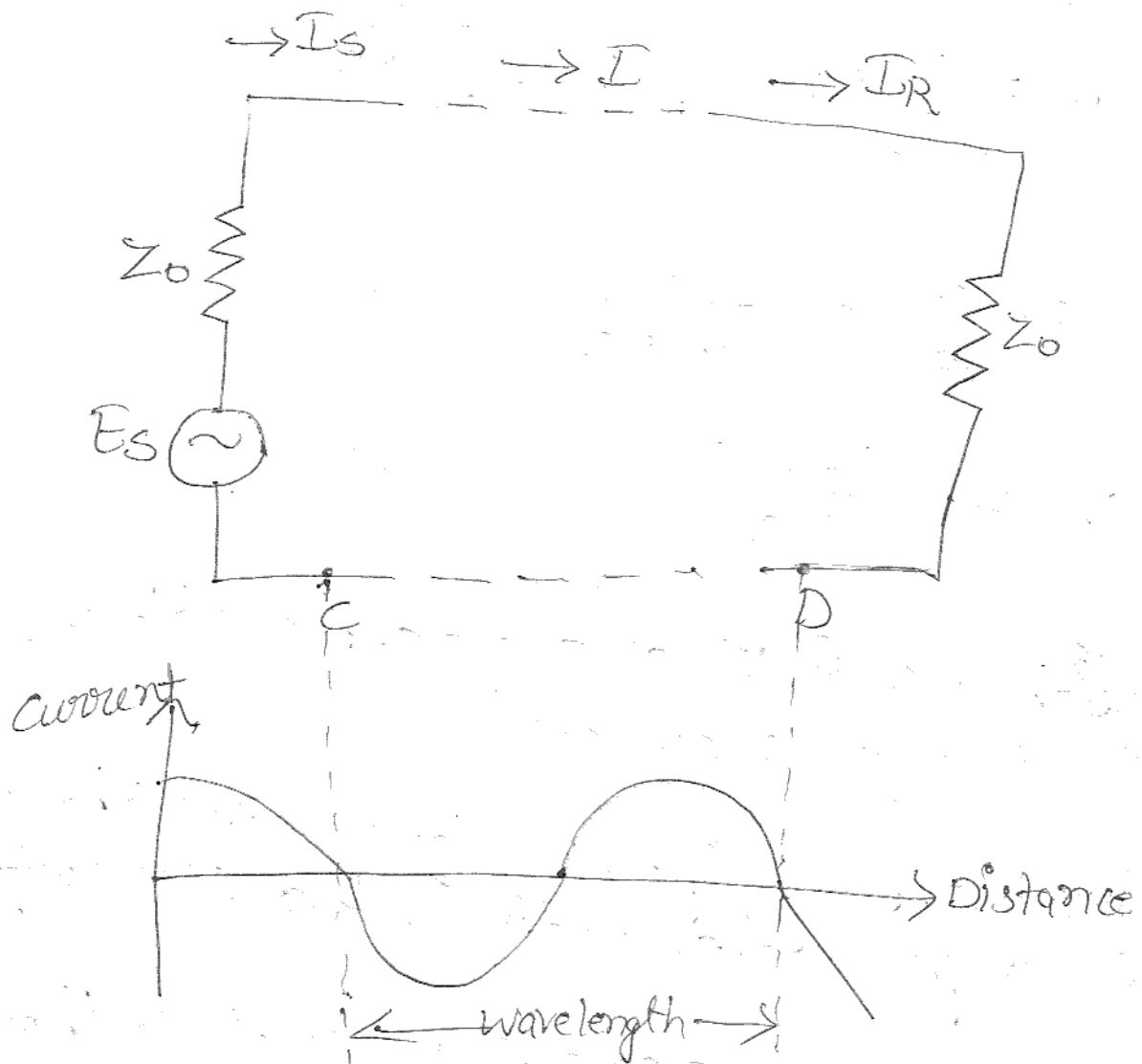

The distance b/w two points along the line at which current & vge differs in phase by 2π radian. it is called wavelength & denoted by λ .

$$\lambda = \frac{2\pi}{\beta}$$

Phase constant β : It is defined as radians per unit length of line.

If the frequency is f Hertz i.e. cycles/second. Then for one cycle the time required is called time period.

$$T = \frac{1}{f} \text{ sec/cycle.}$$

$$V = \frac{\text{distance travelled}}{\text{time taken}}$$

$$V = \frac{\lambda}{1/f}$$

$$\boxed{V = \lambda f}$$

$$V = \frac{\omega}{\beta} = \frac{2\pi f}{\beta}$$

Open and short Circuited lines

The expressions for vge and current at the sending end of a transmission line of length l are given by

$$E_s = E_R \cosh(\gamma l) + I_R Z_0 \sinh(\gamma l) \quad \text{--- (1)}$$

$$I_s = I_R \cosh(\gamma l) + \frac{E_R}{Z_0} \sinh(\gamma l) \quad \text{--- (2)}$$

$$V_s = V_R \cosh(\gamma l) + \frac{V_R Z_0}{Z_R} \sinh(\gamma l) \quad \left[\because Z_R = \frac{V_R}{I_R} \right]$$

$$V_s = V_R \left[\cosh(\gamma l) + \frac{Z_0}{Z_R} \sinh(\gamma l) \right] \quad \text{--- (3)}$$

$$I_s = I_R \left[\cosh(\gamma l) + \frac{Z_R}{Z_0} \sinh(\gamma l) \right] \quad \text{--- (4)}$$

The i/p impedence of a transmission line is given by

$$Z_0 = \frac{V_s}{I_s}$$

divide ~~(2)~~ (4) by (3)

$$Z_s = \frac{V_R \left[\cosh(\gamma l) + \frac{Z_0}{Z_R} \sinh(\gamma l) \right]}{I_R \left[\cosh(\gamma l) + \frac{Z_R}{Z_0} \sinh(\gamma l) \right]}$$

$$= \frac{V_R}{Z_R} \frac{\left[Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l) \right]}{\frac{I_R}{Z_0} \left[Z_0 \cosh(\gamma l) + Z_R \sinh(\gamma l) \right]}$$

$$Z_s = \frac{Z_0 V_R}{Z_R I_R} \frac{\left[Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l) \right]}{\left[Z_0 \cosh(\gamma l) + Z_R \sinh(\gamma l) \right]} \left[\frac{V_R}{I_R} = Z_R \right]$$

$$Z_s = Z_0 \frac{\left[Z_R \cosh(\gamma l) + Z_0 \sinh(\gamma l) \right]}{\left[Z_0 \cosh(\gamma l) + Z_R \sinh(\gamma l) \right]}$$

If short circuited, the receiving end impedance is zero.

i.e. $Z_R = 0$

$$Z_{sc} = Z_0 \left[\frac{Z_0 \sinh(\gamma l)}{Z_0 \cosh(\gamma l)} \right]$$

$$Z_{sc} = Z_0 \tanh(\gamma l)$$

If open circuited the receiving end impedance is infinite.

$$\text{i.e. } Z_R = \infty$$

$$Z_S = Z_0 \left[\frac{\cosh(\gamma l) + \frac{Z_0}{Z_R} \sinh(\gamma l)}{\frac{Z_0}{Z_R} \cosh(\gamma l) + \sinh(\gamma l)} \right]$$

$$Z_{oc} = Z_0 \left[\frac{\cosh(\gamma l)}{\sinh(\gamma l)} \right]$$

$$Z_{oc} = Z_0 \coth(\gamma l)$$

By multiplying open circuited impedance & short circuited impedance

$$\boxed{Z_{oc} Z_{sc} = Z_0^2}$$

The characteristic impedance is given by

$$Z_0 = \sqrt{Z_{oc} Z_{sc}}$$

receiving
finite.

By dividing short circuited impedance
and open circuited impedance is

$$\frac{Z_{sc}}{Z_{oc}} = \frac{Z_0 \tanh(\gamma l)}{Z_0 \coth(\gamma l)}$$

$$\frac{\tanh(\gamma l)}{\coth(\gamma l)}$$

$$\frac{Z_{sc}}{Z_{oc}} = \tanh^2(\gamma l)$$

$$\tanh(\gamma l) = \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$

$$\gamma l = \tanh^{-1} \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$

ted
ted

Reflection :-

When the load impedance is not
equal to the characteristic
impedance of transmission line,
reflection takes place.

ance is

The exp. for vge & current
on the transmission line are:-

$$V = \frac{V_R}{2} \left[\frac{Z_R + Z_0}{Z_R} e^{\sqrt{ZY}x} + \frac{Z_R - Z_0}{Z_R} e^{-\sqrt{ZY}x} \right]$$

[$\because s = \alpha$]

$$I = \frac{I_R}{2} \left[\frac{Z_R + Z_0}{Z_R} e^{\sqrt{ZY}x} - \frac{Z_R - Z_0}{Z_0} e^{-\sqrt{ZY}x} \right]$$

$$V = \frac{V_R}{2} \left[\frac{Z_R + Z_0}{Z_R} \right] \left[e^{\gamma x} + \frac{Z_R - Z_0}{Z_R + Z_0} e^{-\gamma x} \right]$$

[$\because \gamma = \sqrt{ZY}$]

$Z_R \neq Z_0$ (mismatched condition)

If the transmission line is not terminated with characteristic impedance, then the above exp exist & this condition is called mismatched condition.

It consists of two waves one is moving in the forward direction called incident wave & other one is moving in backward direction called reflected wave.