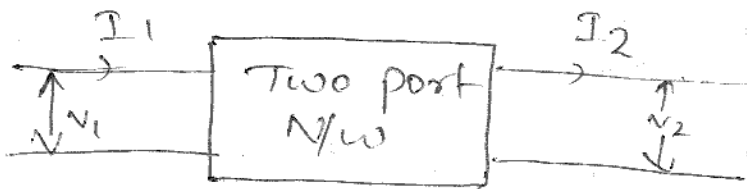


## UNIT - I

### Nepers and Decibels

Nepers :- It is defined as the natural logarithm of the ratio of i/p voltage or current to that of output voltage or current, provided the n/w is properly terminated with  $Z_0$ .




$$\therefore N = \log_e \left| \frac{V_1}{V_2} \right| = \log_e \left| \frac{I_1}{I_2} \right| \quad \text{--- (1)}$$

$$\Rightarrow e^N = \left| \frac{V_1}{V_2} \right| = \left| \frac{I_1}{I_2} \right|$$

Hence two voltage or currents differs by 1 nepers when one of them is  $e$  times as large as the other.

Nepers can be expressed in terms of i/p, o/p power as

$$N = \frac{1}{2} \log_e \left| \frac{P_1}{P_2} \right| \quad \text{--- (2)}$$

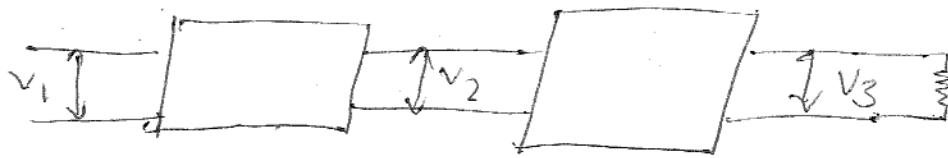

$$N_1 = \log_e \left| \frac{V_1}{V_2} \right|$$

$$N_2 = \log_e \left| \frac{V_2}{V_3} \right|$$

The total attenuation 'N' through the combination is obtained by adding the attenuation of separate  $N_1$  &  $N_2$ .

$$N = N_1 + N_2$$

$$= \log_e \left| \frac{V_1}{V_2} \right| + \log_e \left| \frac{V_2}{V_3} \right|$$

$$= \log_e \left| \frac{V_1 \times \cancel{V_2}}{\cancel{V_2} \times V_3} \right|$$

$$N = \log_e \left| \frac{V_1}{V_3} \right|$$

Thus the addition of logarithm is equivalent to multiplying the voltage ratio. Similarly the subtraction of the log is equivalent to dividing the voltage ratio.

Decibels :-

It is the 10 times common algorithm of the ratio of the input power to the O/P power.

$$\therefore D = 10 \log_{10} \frac{P_1}{P_2} \quad - (1)$$

If the powers  $P_1$  &  $P_2$  are associated with equal impedances, the power ratio can be expressed as the square of either the voltage or the current ratio under this condition eqn (1) can be written as

$$D = 20 \log_{10} \left| \frac{V_1}{V_2} \right| = 20 \log_{10} \left| \frac{I_1}{I_2} \right| \quad - (2)$$

Neither nepers nor decibel is an absolute unit each gives the ratio b/w i/p & o/p power.

WKT

$$\log_e x \approx \log_{10} x \times \log_e 10 \quad - (1)$$

Sub  $x = \frac{P_1}{P_2}$  &  $\log_e 10 = 2.3026$  in (1)

$$\log_e \frac{P_1}{P_2} = \log_{10} \frac{P_1}{P_2} \times \log_e 10 = 2.3026 \quad - (2)$$

Sub

$$N = \frac{1}{2} \log_e \frac{P_1}{P_2} \quad \&$$

$$D = 10 \log_{10} \frac{P_1}{P_2} \text{ in } (2)$$

$$2N = \frac{D}{10} \times 2.3026$$

$$1 \text{ nepers} = 8.686 \text{ dB}$$

$$1 \text{ dB} = 0.115 \text{ nepers}$$

## Networks

An electrical n/w is any inter-connection of electric elements or branches.

N/w elements are impedances and sources. Each branch may include R, L, C or other types of elements.

### Passive N/w

A n/w containing ext elements without energy sources.

### Active n/w

A n/w containing generator or energy sources as well as other elements.

## Nodes

A terminal of any branch of a n/w or the terminal common to n branches.

## Resonance :-

The property of cancellation of reactance when inductor & capacitor reactance are in series (or) cancellation of susceptance is when inductor & capacitor are in parallel.

## Filters :-

A n/w which freely passes desired band of freq while almost suppresses other band of frequencies called filters.

## Active filters :-

The filters which contain active element is called active filters such as transistor, op-amp.

The disadvantage is it req. additional Power Supply.

voltage, current, power gain is possible.

## Passive filters :-

The filter consists of passive element like R, L, C is called passive filters.

It does not req. additional power supply.

Now of gain is possible.

## Pass Band :

The range in which the attenuation is zero.

Stop Band :- (attenuation band)

The range of freq. over which the attenuation is infinite.

## Cutoff frequencies :-

The freq. which separates the pass band from the stop band is called cutoff freq ( $f_c$ ).

We know that

$$I = \frac{I_R (Z_R + Z_0)}{2Z_0} \left[ e^{\gamma s} - \frac{Z_R - Z_0}{Z_R + Z_0} e^{-\gamma s} \right]$$

Sub  $s = l$

$$I_s = \frac{I_R (Z_R + Z_0)}{2Z_0} \left[ e^{\gamma l} - \frac{Z_R - Z_0}{Z_R + Z_0} e^{-\gamma l} \right]$$

$$I_s = \frac{I_R (Z_R + Z_0)}{2Z_0} \left[ e^{\gamma l} - K e^{-\gamma l} \right]$$

$$\Rightarrow Z_s = \frac{E_s}{I_s} \quad \& \quad E_s = 1 \angle 0^\circ \text{ V}$$

$$I_s = \frac{E_s}{Z_s} = \frac{1 \angle 0^\circ}{124.733 \angle 1.7301^\circ}$$

$$I_s = 1.600 \times 10^{-3} \angle -1.7301^\circ$$

$$Z_R + Z_0 = 200 \angle 0^\circ + 696.204 \angle -10.825^\circ$$

$$= 893.23 \angle -8.414^\circ$$

$$K e^{-\gamma l} = (0.5608 \angle 173.289^\circ) (0.4676 \angle -208.38^\circ)$$

$$K e^{-\gamma l} = 0.2622 \angle -35.091^\circ$$

Q<sub>2</sub> →

$$1.600 \times 10^{-3} \angle -1.7301^\circ = \frac{I_R (893.23 \angle -8.414^\circ)}{2 \times 696.204 \angle -10.825^\circ}$$

$$\left[ 2.138 \angle 208.38^\circ - 0.2622 \angle -35.091^\circ \right]$$

$$1.600 \times 10^{-3} \angle -1.7301^\circ = \text{IR} \left[ \frac{893.23 \angle -8.414^\circ}{1392.408 \angle -10.825^\circ} \right] \times$$

$$1.600 \times 10^{-3} \angle -1.7301^\circ = \text{IR} \left[ \frac{0.6415 \angle 2.411^\circ}{2.138 \angle 208.38^\circ - 0.262 \angle -35.091^\circ} \right]$$

$$\text{IR} = \frac{1.600 \times 10^{-3} \angle -1.7301^\circ}{\left[ 0.6415 \angle 2.411^\circ \right] \left[ 2.138 \angle 208.38^\circ - 0.262 \angle -35.091^\circ \right]}$$

$$= \frac{1.600 \times 10^{-3} \angle -1.7301^\circ}{(0.6415 \angle 2.411^\circ) (1.876 \angle 173.289^\circ)}$$

$$= \frac{1.600 \times 10^{-3} \angle -1.7301^\circ}{1.2034 \angle 175.7^\circ}$$

$$\text{IR} = \frac{1.329 \times 10^{-3} \angle -177.429^\circ}{10^{-3}}$$

$$\text{IR} = 0.001329 \angle -177.429^\circ$$

$$\text{ER} = \text{IR ZR}$$

$$= 1.329 \times 10^{-3} \angle -177.429^\circ \times 200 \angle 0^\circ$$

$$= 265.8 \times 10^{-3} \angle -177.429^\circ$$

$$\boxed{\text{ER} = 265.8 \angle -177.42^\circ}$$



$$P_S = E_S I_S \cos(\theta_{E_S} \wedge \theta_{I_S})$$

$$= 1 \angle 0^\circ \times 1.599 \times 10^{-3} \angle -1.7301^\circ$$

$$\cos(1 \angle 0^\circ \wedge 1.599 \times 10^{-3} \angle -1.7301^\circ)$$

$$= 1.599 \angle -1.7301^\circ \cos(1 \angle 0^\circ \wedge$$

$$P_R = I_R^2 R$$

$$= 2.38$$

# ~~FILTER FUNDAMENTAL~~

## FILTERS FUNDAMENTALS

If  $\alpha = 0$ , or  $I_1 = I_2$  then there is no attenuation, only phase shift occurs.

1)  $\alpha = 0 \rightarrow [I_1 = I_2] \rightarrow \beta$  exist

These conditions occurs only in pass band

2)  $\alpha = +ve \rightarrow [I_1 < I_2]$ ,  $\alpha$  exist.

It occurs in stop Band.

3) The propagation constant  $\gamma$  for symmetrical T section is given by

$$\sinh \frac{\gamma}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\sinh \frac{\gamma}{2} = \sinh \left( \frac{\alpha}{2} + j \frac{\beta}{2} \right)$$

$$\sinh \frac{\gamma}{2} = \sinh \frac{\alpha}{2} \cdot \cos \frac{\beta}{2} + \cosh \frac{\alpha}{2} \cdot \sin \frac{\beta}{2}$$

— (1)

$$\sinh \frac{\alpha}{2} \cdot \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \cdot \sin \frac{\beta}{2} = \sqrt{\frac{Z_1}{4Z_2}} \quad \text{— (2)}$$

From the above two eqns  $\alpha$  &  $\beta$  depends on  $Z_1$  &  $Z_2$

Case 1: If  $Z_1$  and  $Z_2$  are the same type of reactance then  $\frac{Z_1}{4Z_2}$  should be greater than zero or the ratio is positive and real

$$Z_1 = Z_2, \quad \frac{Z_1}{4Z_2} > 0 \rightarrow \text{real}$$

$$\sin \beta/2 \cdot \cos \frac{h\alpha}{2} = 0 \rightarrow \textcircled{3} \quad \left. \begin{array}{l} \text{Imaginary} \\ \text{Part zero} \end{array} \right\}$$

$$\sin \frac{h\alpha}{2} \cdot \cos \frac{\beta}{2} = \sqrt{\frac{Z_1}{4Z_2}} \quad \textcircled{4}$$

from eqn  $\textcircled{3}$

$$\sin \frac{\beta}{2} = 0, \quad \beta = n\pi, \quad n = 0, 1, 2, \dots$$

from eqn  $\textcircled{4}$

$$\sin \frac{h\alpha}{2} = \sqrt{\frac{Z_1}{4Z_2}}, \quad [\because \cos 0 = 1]$$

$$\alpha = 2 \sinh^{-1} \sqrt{\frac{Z_1}{4Z_2}}$$

Thus the condition that  $\frac{Z_1}{4Z_2} > 0$  implies a stop band or attenuation band of frequencies.

Case 2: If  $z_1$  &  $z_2$  are opposite types of reactance than  $\frac{z_1}{4z_2} = -ve$   
 Real part becomes zero.

$$\cosh \frac{\alpha}{2} \cdot \sin \frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}} \quad \text{--- (6)}$$

$$\sinh \frac{\alpha}{2} \cdot \cos \frac{\beta}{2} = 0 \quad \text{--- (5)}$$

from eqn (5)

$$\sinh \frac{\alpha}{2} = 0$$

$$\boxed{\alpha = 0}, \quad \boxed{\beta \neq 0}$$

$$\sin \frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}} \quad \left\{ \cosh \frac{\alpha}{2} = 1 \right\}$$

from eqn (6)

$$\cos \frac{\beta}{2} = 0, \quad \sin \frac{\beta}{2} = \pm 1 \text{ \& } \alpha \neq 0$$

$$\cosh \frac{\alpha}{2} = \sqrt{\frac{z_1}{4z_2}}$$

$$\text{from } \sin \frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}}$$

$$B = 2 \sin^{-1} \left( \sqrt{\frac{z_1}{4z_2}} \right) \quad \text{--- (7)}$$

$$\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}} \quad \text{--- (6)}$$

Condition (1) gives a passband as infinity i.e. zero attenuation. Then the phase angle in the passband is given by

$$\beta = 2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}} \quad \text{--- (7)}$$

Condition (2) gives a stopband. Then the phase angle is  $\pi$  and attenuation is given by

$$\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}} \quad \text{--- (8)}$$

From eqns (7) & (8), we can easily calculate  $\alpha$  in the stop band in which  $\beta$  is  $\pi$  and the phase shift  $\beta$  in PB in which  $\alpha = 0$ .

The frequencies at which the network changes from a pass network to the stop network called cutoff frequency. These frequencies occur when

$$\frac{Z_1}{4Z_2} = 0 \quad (\text{or}) \quad Z_1 = 0 \rightarrow \text{(9)}$$

HW

$$\frac{Z_1}{4Z_2} = -1 \quad \text{or} \quad Z_1 = -4Z_2 \rightarrow \textcircled{10}$$

Where  $Z_1$  &  $Z_2$  are opposite type of reactance.

HW

Q. An open wire telephone line has  $R = 10 \Omega/\text{km}$ ,  $L = 0.004 \text{ H}/\text{km}$ ,  $C = 0.008 \times 10^{-6} \text{ F}/\text{km}$  and  $G = 0.4 \times 10^{-6} \text{ mho}/\text{km}$ . Find  $Z_0$ ,  $\alpha$ ,  $\beta$  at  $1 \text{ kHz}$

Sol<sup>n</sup>

$$Z = R + j\omega L$$

$$= 10 + j \times 2\pi \times 10^3 \times 0.004$$

$$= 10 + 25.132j$$

$$= 27.0484 \angle 68.30^\circ$$

$$Y = G + j\omega C$$

$$= 0.4 \times 10^{-6} + j \times 2\pi \times 10^3 \times 0.008 \times 10^{-6}$$

$$= 5.0267 \times 10^{-6} \angle 89.54^\circ$$

$$Z_0 = \sqrt{\frac{Z}{Y}}$$

$$Z = \sqrt{\frac{27.0484 \angle 68.36^\circ}{5.0267 \times 10^{-5} \angle 89.54^\circ}}$$

$$Z = \sqrt{5.3810 \times 10^5 \angle 21.24^\circ}$$

$$Z = 733.552 \angle -10.62^\circ$$

$$Z = \sqrt{24}$$

$$Z = \sqrt{5.0267 \times 10^{-5} \times 27.0484 \angle 157.84^\circ}$$

$$Z = \sqrt{135.967 \times 10^{-5} \angle 157.84^\circ}$$

$$Z = 36.8456 \times 10^{-3} \angle 78.92^\circ$$

$$Z = 7.0809 \times 10^{-3} + 0.0361 j \Omega$$

$$\alpha = 7.0809 \times 10^{-3}, \beta = 0.0361 \text{ s/m}$$

Q3. A telephone line has  $R = 20 \Omega$ ,  $L = 10 \text{ mH}$ ,  $C = 0.1 \mu\text{f}$  & insulation resistance of  $100 \text{ k}\Omega/\text{km}$ . Find the i/p impedance at angular frequency  $5000 \text{ rad/sec}$  if the line is very long.

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{20 + j \times 5000 \times 10^{-2} \times 10 \times 10^{-3}}{0.01 \times 10^{-6} + j \times 5000 \times 10^{-2} \times 0.1 \times 10^{-6}}}$$

$$Z = \sqrt{\frac{20 + j \times 5000 \times 10^{-4}}{0.01 + j \times 5000 \times \frac{0.1}{10} \times 10^{-8}}}$$

$$Z = \sqrt{\frac{20.0062 \angle 1.432}{0.0100 \angle 0.0286}}$$

$$Z = \sqrt{2000.62 \angle 1.4034}$$

$$Z = 44.72 \angle 0.701^\circ$$



## Behaviour of characteristic impedance

In the symmetrical T network, the charac. impedance is given by

$$Z_0 = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$

For pure reactances this expression for the characteristic impedance becomes

$$Z_0 = \sqrt{-X_1 X_2 \left(1 + \frac{X_1}{4X_2}\right)}$$

## Constant K Filters

1. A T or  $\pi$  section in which series & shunt impedances  $Z_1$  &  $Z_2$  satisfy the relationship

$$Z_1 Z_2 = R_0^2$$

where  $R_0$  is a real constant, it is denoted as  $K$  or  $R_K$ , where  $R_K$  is constant independent of frequency.

$$Z_1 Z_2 = K^2$$

or

$$Z_1 Z_2 = R_K^2$$

Networks are filter sections for which this relationship holds for constant  $K$  filters.

Constant K LPF

In low pass filters the series impedance

$$Z_1 = j\omega L \quad \& \quad Z_2 \text{ shunt impedance}$$

$$\text{is } Z_2 = -\frac{j}{\omega C}$$

Then


$$Z_1 Z_2 = -j\omega L \cdot \frac{j}{\omega C}$$

$$Z_1 Z_2 = \frac{L}{C} = R_k^2$$


The term  $R_k$  is used since  $k$  is real and constant if  $Z_1$  &  $Z_2$  are opposite type.

$$R_k^2 = \frac{L}{C} \quad \boxed{R_k = \sqrt{\frac{L}{C}}}$$

(a)

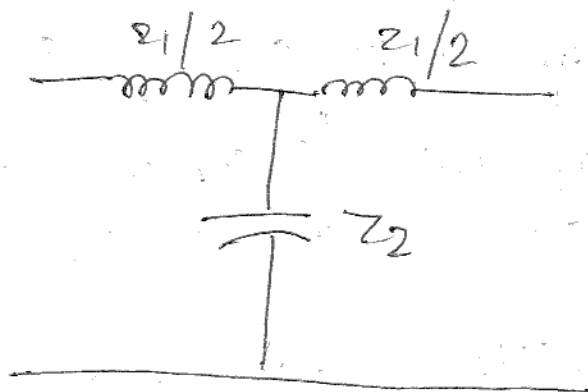

LPF section.

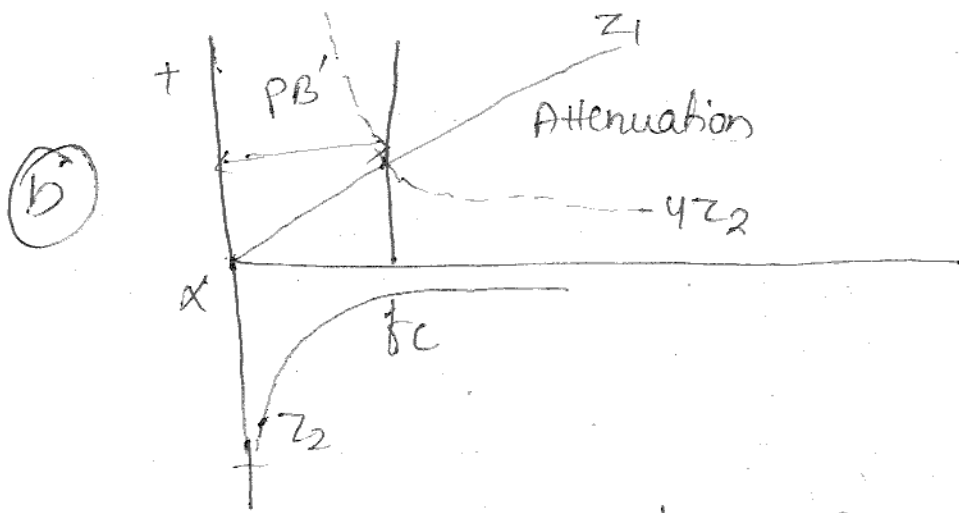

The reactances of  $Z_1$  &  $4Z_2$  will vary with frequency

WKT

$$Z_1 = -4Z_2$$

Since it is varying with freq.,  
Thus the reactance shows that the PB starts at  $f=0$  & continues to  $f_c$ .  
All frequencies above  $f_c$  lies in the Attenuation or stop band. Thus the network is called LPP.

The cutoff frequency  $f_c$  may be obtained by using  $Z_1 = -4Z_2$  - (1)

Sub  $Z_1 = j\omega L$  &  $Z_2 = -\frac{j}{\omega C}$  in equ (1)

$$j\omega L = +4 \frac{j}{\omega C}$$

$$\omega^2 = \frac{4}{LC}$$

$$(2\pi f_c)^2 = \frac{4}{LC}$$

$$4\pi^2 f_c^2 = \frac{4}{LC}$$

$$f_c^2 = \frac{4}{4\pi^2 LC}$$

$$f_c = \frac{1}{\pi\sqrt{LC}} \quad \text{--- (3)}$$

constant  $\beta$  with frequency

for passband  $\alpha$  is zero and  $\beta$  is  $\pi$  then

$$\sinh \frac{\alpha}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$$= \sqrt{\frac{j\omega L}{-4j \frac{1}{\omega C}}} = \sqrt{\frac{j\omega L \times \omega C}{-4j}}$$

$$\sinh \frac{\alpha}{2} = \sqrt{-\frac{\omega^2 LC}{4}}$$

$$\sinh \frac{\alpha}{2} = j \frac{\omega \sqrt{LC}}{2}$$

WKT

$$f_c \text{ is } \frac{1}{\pi\sqrt{LC}} \quad \Delta \omega = 2\pi f_c$$

$$\cancel{\sinh \frac{\alpha}{2}} = \frac{\cancel{j 2\pi f L}}{\cancel{\sqrt{LC}}}$$

$$\sinh \frac{\alpha}{2} = \frac{j 2\pi f L}{2} \cdot \frac{1}{\sqrt{LC}}$$

$$\sinh \frac{\alpha}{2} = \frac{j f}{f_c}$$

$$\left. \begin{array}{l} \therefore \text{For } \beta, \alpha = 0, \\ \sin \frac{\beta}{2} = \frac{f}{f_c} \end{array} \right\}$$

$$\beta = 2 \sin^{-1} \left( \frac{f}{f_c} \right)$$

The characteristic impedance of T section can be calculated by

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$= \sqrt{\frac{j^2 \omega^2 L^2}{4} + j \omega L \cdot \frac{-j}{\omega C}}$$

$$= \sqrt{-\frac{\omega^2 L^2}{4} + \frac{L}{C}}$$

$$= \sqrt{\frac{L^2}{C^2}} \cdot \sqrt{1 - \frac{\omega^2 LC}{4}}$$

WKT

$$R_0 = \sqrt{\frac{L}{C}}$$

$$\therefore Z_0 = R_0 \sqrt{1 - \frac{\omega^2 LC}{4}}$$

From the above expression it is clear that  $Z_0$  is Real if  $\frac{\omega^2 LC}{4}$  is lesser than 1 and imaginary if  $\frac{\omega^2 LC}{4} > 1$ . Hence condition  $\frac{\omega^2 LC}{4} - 1 = 0$

which gives

$$\frac{\omega^2 LC}{4} = 1$$

$$\omega^2 LC = 4$$

$$\omega = 2 \sqrt{\frac{1}{LC}}$$

$$\omega = \frac{2}{\sqrt{LC}}$$

Thus the above expression shows it passes all frequencies below  $\omega = \frac{2}{\sqrt{LC}}$  which attenuates all frequencies above  $\frac{2}{\sqrt{LC}}$ .

$\therefore$  The cutoff frequency of LPR is given by

$$\omega_c = \frac{2}{\sqrt{LC}}$$

$$2\pi f_c = \frac{2}{\sqrt{LC}}$$

$$f_c = \frac{1}{\pi\sqrt{LC}}$$

variation of  $Z_0$  with frequency

Consider  $Z_0 = R_0 \sqrt{1 - \frac{\omega^2 LC}{4}}$  — (1)

$$\omega_c = \frac{2}{\sqrt{LC}} \quad \text{or} \quad \omega_c^2 = \frac{4}{LC}$$

$$Z_0 = R_0 \sqrt{1 - \frac{4 \times LC \times \omega^2}{LC \times 4 \times \omega^2}}$$

$$Z_0 = R_0 \sqrt{1 - \left(\frac{\omega}{\omega_c}\right)^2}$$

$$Z_0 = R_0 \sqrt{1 - \left(\frac{2\pi f}{2\pi f_c}\right)^2}$$

$$Z_{0T} = R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}$$

M/W K/T

$$Z_{0T} = \frac{Z_1 Z_2}{Z_{0T}}$$

$$Z_{0T} = \frac{Z_1 Z_2}{R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$

WKT

$$z_1 z_2 = R_0^2$$

$$\therefore z_{0\pi} = \frac{R_0^2}{R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$

$$z_{0\pi} = \frac{R_0}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$

Variation of attenuation constant  $\alpha$  with frequency

$$\alpha \neq 0, \quad \beta = \pi$$

$$\sinh \frac{\alpha}{2} = \sqrt{\frac{z_1}{4z_2}}$$

$$= \sqrt{\frac{j\omega L \times \omega C}{4(-j)}}$$

(For LPP)

$$z_1 = j\omega L$$

$$z_2 = \frac{j}{\omega C}$$

$$\sinh \frac{\alpha}{2} = \sqrt{\frac{j f}{f_c}}$$

$$\frac{\sinh(\alpha + j\beta)}{2} = \frac{j f_0}{f_c}$$



$$\sinh \frac{\alpha}{2} \cdot \frac{\cos j\beta}{2} + \cosh \frac{\alpha}{2} \cdot \frac{\sin j\beta}{2} = \frac{j}{fc}$$

W.K.T

$$\sinh j\theta = j \sin \theta$$

$$\cosh j\theta = \cos \theta$$

$$\sinh \frac{\alpha}{2} \cdot \frac{\cos \beta}{2} + \cosh \frac{\alpha}{2} \cdot j \frac{\sin \beta}{2} = j \left( \frac{1}{fc} \right)$$

W.K.T

$$\alpha = 0 \quad \& \quad \beta = \pi$$

$$\sinh(0) = 0, \quad \cos \frac{\pi}{2} = 0; \quad \sin \frac{\beta}{2} = \sin \frac{\pi}{2} = 1$$

$$j \cosh \frac{\alpha}{2} = j \left( \frac{1}{fc} \right)$$

$$\alpha = 2 \cosh^{-1} \left( \frac{1}{fc} \right)$$

Finding Inductance & capacitance by using  $R_0$  and  $fc$

$$R_0 = \sqrt{\frac{L}{C}} \quad \text{--- (1)}$$

$$fc = \frac{1}{\pi \sqrt{LC}}$$

Divide (1) & (2)

$$\frac{R_0}{fc} = \sqrt{\frac{L}{C}} \times \pi \sqrt{LC} = \frac{L\pi\cancel{C}}{\cancel{C}}$$

$$\frac{R_0}{f_c} = \pi L$$

$$\therefore L = \frac{R_0}{\pi f_c}$$

Multiply (1) & (2)

$$R_0 f_c = \sqrt{\frac{L}{C}} \times \frac{1}{\pi \sqrt{LC}} = \frac{1}{\pi C}$$

$$C = \frac{1}{\pi R_0 f_c}$$

### CONSTANT K HIGH PASS FILTER

In high pass filter the series impedance

$Z_1 = -\frac{j}{\omega C}$  & shunt impedance is

$$Z_2 = j\omega L$$

$$Z_1 Z_2 = -\frac{j}{\omega C} \times j\omega L = \frac{L}{C}$$

$$\boxed{Z_1 Z_2 = \frac{L}{C}} \quad \text{--- (1)}$$

WKT


Constant K Section

$$Z_1 Z_2 = R_0^2$$


Sub in eqn (1)

$$R_0^2 = \frac{L}{C}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

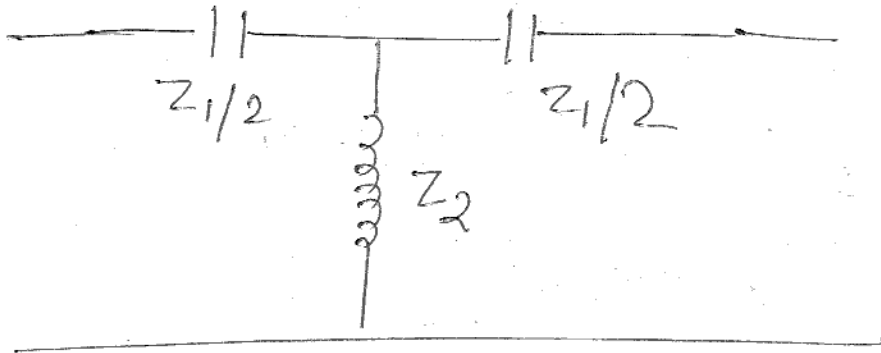

HPF section

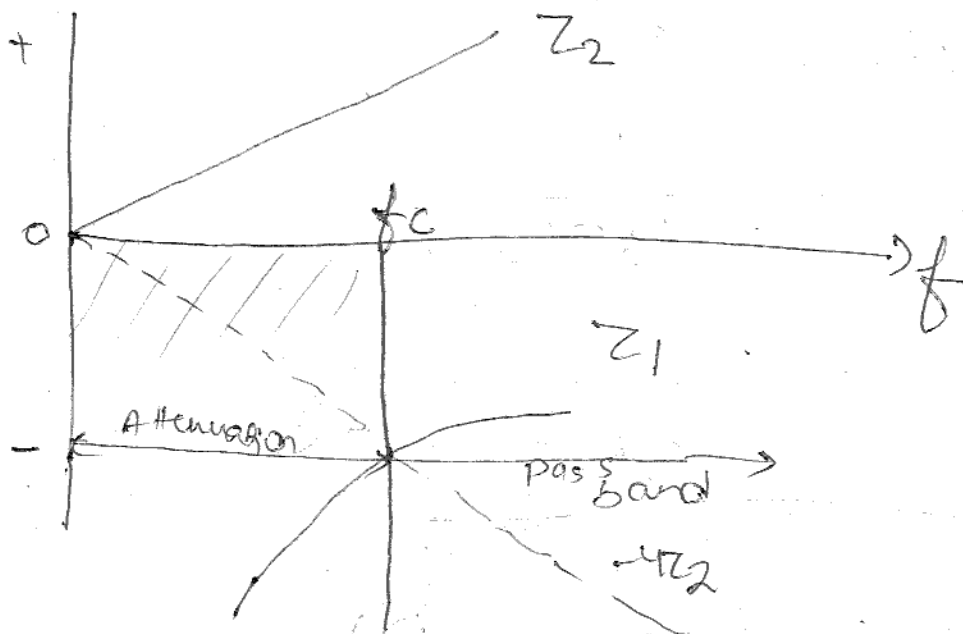

$Z_1$  is compared with  $-4Z_2$  showing a cutoff frequency at the point at which  $Z_1 = -4Z_2$ . This network

is high pass filter all frequencies below  $f_c$  lie in a attenuation or stopband.

The cutoff frequency is determined at the frequency at which  $Z_1 = -4Z_2$  - (2)

$$\text{Sub } Z_1 = \frac{-j}{\omega C} \quad \& \quad Z_2 = j\omega L$$

$$\frac{-j}{\omega C} = -4j\omega L \times 4$$

$$\frac{1}{2\pi f_c C} = 4 \times 2\pi f_c L$$

$$\frac{1}{8\pi L \cdot 2C} = f_c^2$$

$$f_c^2 = \frac{1}{16\pi^2 LC}$$

$$f_c = \frac{1}{4\sqrt{LC}} \quad \text{--- (4)}$$

$$\omega_c = \frac{1}{2\sqrt{LC}} \quad \text{--- (3)}$$

i) Variation of attenuation with frequency

The propagation constant

$$\sinh \frac{\gamma}{2} = \sqrt{\frac{Z_1}{4Z_2}} \quad \text{--- (5)}$$

$$\sinh \frac{\gamma}{2} = \sqrt{\frac{-j\omega C}{4 \times j\omega L}}$$

$$= \sqrt{\frac{-j}{4\omega C \cdot j\omega L}} = \sqrt{\frac{-1}{4\omega^2 LC}}$$

$$= \frac{j}{2\omega} \cdot \frac{1}{\sqrt{LC}} = \frac{j}{\omega} \cdot \frac{1}{\sqrt{LC}}$$

$$\sinh \frac{\gamma}{2} = \frac{j}{2\omega} \cdot \frac{1}{\sqrt{LC}} \quad \text{--- (6)}$$

sub  $\omega_c = \frac{1}{2\pi\sqrt{LC}}$

$$\sinh \frac{\gamma}{2} = j \left( \frac{\omega_c}{\omega} \right)$$

$$\sinh \frac{\gamma}{2} = j \left( \frac{2\pi f_c}{2\pi f} \right)$$

$$\sinh \frac{\gamma}{2} = j \left( \frac{f_c}{f} \right) \quad \text{--- (7)}$$

$$\text{Now } \gamma = \alpha + j\beta$$

$$\frac{\sinh(\alpha + j\beta)}{2} = j \left( \frac{fc}{f} \right)$$

$$\sinh \frac{\alpha}{2} \cdot \cos \frac{j\beta}{2} + \cosh \frac{\alpha}{2} \cdot \sin \frac{j\beta}{2} = j \left( \frac{fc}{f} \right)$$

w.k.f

$$\cosh j\theta = \cos \theta$$

$$\sinh j\theta = j \sin \theta$$

$$\sinh \frac{\alpha}{2} \cdot \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \cdot \sin \frac{\beta}{2} = j \left( \frac{fc}{f} \right) \quad \text{--- (8)}$$

$$\alpha = 0, \quad \beta = \pi$$

$$0 + j \cosh \frac{\alpha}{2} \cdot \sin \frac{\pi}{2} = j \frac{fc}{f}$$

$$\cancel{j} \cosh \frac{\alpha}{2} = \cancel{j} \frac{fc}{f}$$

$$\alpha = 2 \cosh^{-1} \left( \frac{fc}{f} \right)$$

ii) Variation of  $\beta$  with frequency  
from eqn (8)

$$\sinh \frac{h\alpha}{2} \cdot \cos \frac{\beta}{2} + j \cosh \frac{h\alpha}{2} \cdot \sin \frac{\beta}{2} = j \left( \frac{fc}{f} \right)$$

Put  $\alpha = 0$  in eqn (8)

$$\sinh(0) = 0, \cosh(0) = 1$$

$$j \sin \frac{\beta}{2} = j \frac{fc}{f}$$

$$\boxed{\beta = 2 \sin^{-1} \left( \frac{fc}{f} \right)}$$

(iii) Variation of  $Z_0$  with frequency.

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$Z_0 = \sqrt{\left( \frac{-j}{\omega c} \right)^2 + \frac{-j}{\omega c} \times j \omega L}$$

$$Z_0 = \sqrt{\frac{j^2}{4\omega^2 c^2} + \frac{L}{c}}$$

$$Z_0 = \sqrt{\frac{-1}{4\omega^2 c^2} + \frac{L}{c}}$$

$$Z_0 = \sqrt{\frac{L}{c}} \sqrt{1 - \frac{1}{4\omega^2 LC}}$$

$$Z_0 = R_0 \sqrt{1 - \frac{1}{4\omega^2 LC}} \quad \left[ \omega_c^2 = \frac{1}{4LC} \right]$$

$$Z_{0T} = R_0 \sqrt{1 - \frac{\omega_c^2}{\omega^2}}$$

$$Z_{0T} = R_0 \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$

iii) y

$$Z_{0\pi} = \frac{Z_1 Z_2}{Z_{0T}}$$

$$Z_{0\pi} = \frac{R_0^2}{R_0 \sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

$$Z_{0\pi} = \frac{R_0}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}$$

iv) Finding Inductance & Capacitance values by using  $R_0$  &  $f_c$

$$R_0 = \sqrt{\frac{L}{C}} \quad \text{--- (1)}$$

$$f_c = \frac{1}{4\pi\sqrt{LC}} \quad \text{--- (2)}$$

divide (1) & (2)



$$\frac{R_0}{f_c} = \frac{\sqrt{\frac{L}{C}}}{\frac{1}{4\pi\sqrt{LC}}}$$

$$= \sqrt{\frac{L}{C}} \times 4\pi\sqrt{LC}$$

$$\frac{R_0}{f_c} = 4\pi L$$

$$L = \frac{R_0}{4\pi f_c}$$

Multiply (1) & (2)

$$R_0 f_c = \sqrt{\frac{L}{C}} \cdot \frac{1}{4\pi\sqrt{LC}}$$

$$= \frac{1}{4\pi C}$$

$$C = \frac{1}{4\pi R_0 f_c}$$

Disadvantages of Constant K filter


i) Attenuation does not increase rapidly beyond cutoff frequencies.

ii) Characteristic impedances varies widely in the transmission or passband from the desired value.

8. Design m-derived LPF (T or  $\pi$ ) having design impedance

1)  $R_0 = 500 \Omega$ ,  $f_c = 1500 \text{ Hz}$  & infinite attenuation freq  $f_a = 2000 \text{ Hz}$

m-derived LPF T-section

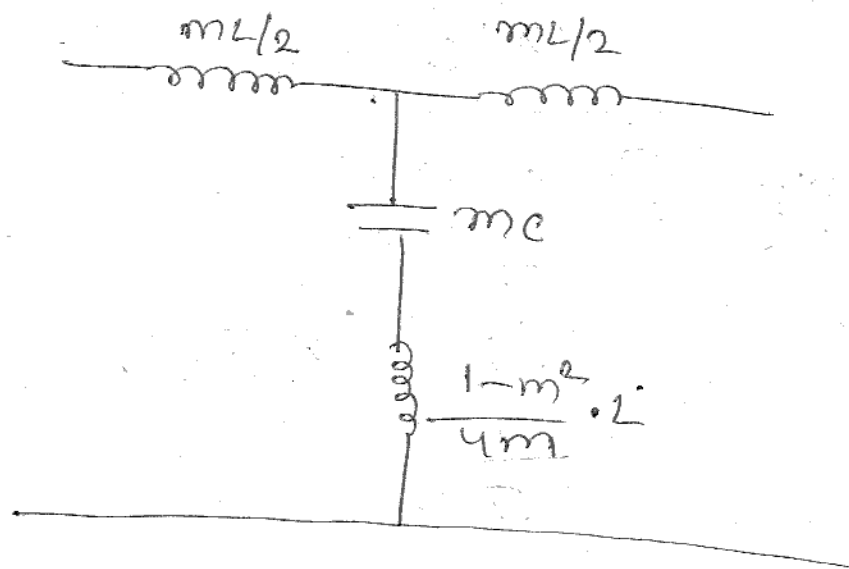

$$1) \quad L = \frac{R_0}{\pi f_c} = \frac{500}{\pi \cdot 1500} \approx 0.106 \text{ mH}$$

$$2) \quad C = \frac{1}{\pi R_0 f_c} = \frac{1}{\pi \cdot 500 \cdot 1500} = 4.24 \times 10^{-7} \text{ F} = 0.424 \text{ nF}$$

$$3) \quad m = \sqrt{1 - \left(\frac{f_c}{f_a}\right)^2} = \sqrt{1 - \left(\frac{1500}{2000}\right)^2} = \sqrt{1 - \frac{25}{16}}$$

$$= \sqrt{1 - \frac{9}{16}} = \sqrt{\frac{7}{16}}$$

$$\approx 0.661$$

$$\frac{mL}{2} = \frac{0.661 \times 0.106}{2} = 0.035$$

$$= 35.03 \text{ mH}$$

$$mC = 0.661 \times 0.424 \times 10^{-6} \text{ F}$$


$$= 0.28 \text{ } \mu\text{F}$$

$$\frac{1 - m^2 L}{4m} = \frac{1 - (0.661)^2}{4 \times 0.661} \times 0.106$$


$$= \frac{0.5638}{4 \times 0.661} \times 0.106$$

$$= 0.022$$

$$= 22.257 \text{ mH}$$

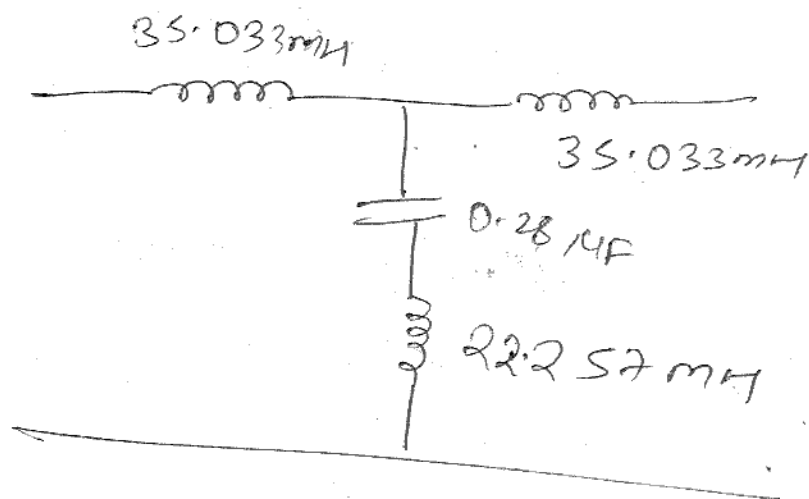

# $\pi$ Section

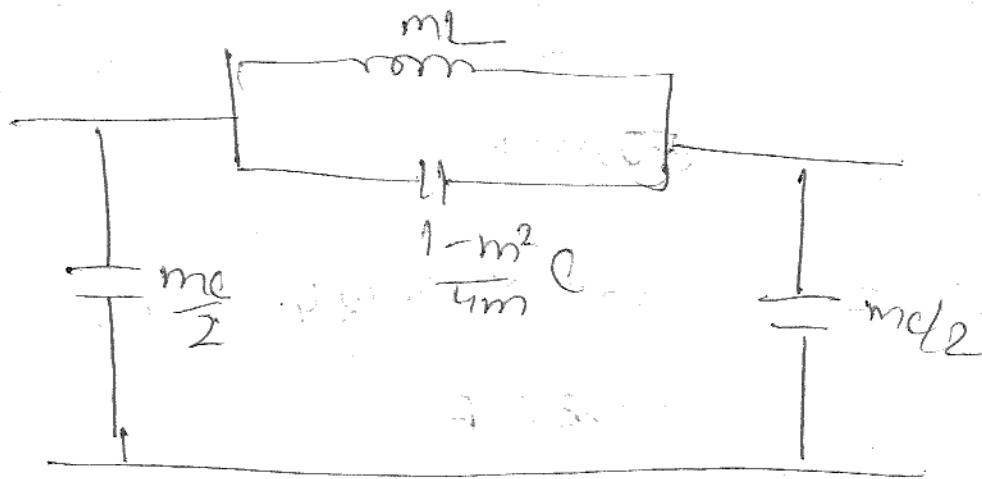

$$mL = 0.661 \times 0.106 = 0.070$$


$$= 70.066 \text{ mH}$$

$$\frac{mc}{2} = \frac{0.661 \times 0.424}{2} = 0.140 \text{ MF}$$

$$\frac{1-m^2}{4m} c = \frac{1 - (0.661)^2}{4 \times 0.661} \times 0.424$$

$$= \text{~~0.090 MF~~}$$

$$= 0.090 \text{ MF}$$

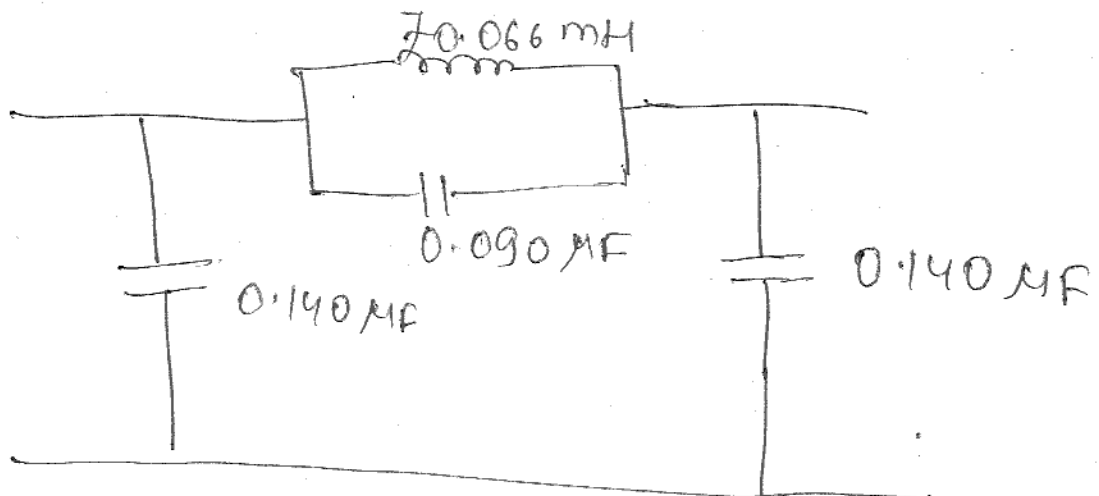

Q2. Design a prototype Band pass filter section having cutoff frequencies of 3000 Hz & 6000 Hz. And nominal characteristic impedance of 600  $\Omega$ . Also find the resonant frequency of shunt arm.

sol<sup>n</sup>. - Band pass  
 $R_0 = 600 \Omega$

Cutoff frequency  $f_1 = 3000 \text{ Hz} = 3 \text{ kHz}$   
 $f_2 = 6000 \text{ Hz} = 6 \text{ kHz}$

$$i) L_1 = \frac{R_0}{\pi(f_2 - f_1)} = \frac{600}{\pi \times \frac{3000}{10^3}} = 63.66 \text{ mH}$$

$$ii) C_1 = \frac{f_2 - f_1}{R_0 4\pi f_1 f_2} = \frac{3 \times 10^3}{600 \times 4 \times \pi \times 18 \times 10^6} = 0.22 \mu\text{F}$$

$$iii) L_2 = \frac{R_0 (f_2 - f_1)}{4\pi f_1 f_2} = \frac{600 \times 3 \times 10^3}{4\pi \times 18 \times 10^6} = 7.957 \text{ mH}$$

$$iv) C_2 = \frac{1}{\pi R_0 (f_2 - f_1)} = \frac{1}{\pi \times 600 \times 3 \times 10^3}$$


$$0.1768 \mu\text{F}$$

$$\text{Resonant frequency } (f_0) = \sqrt{f_1 \cdot f_2}$$


$$= \sqrt{18 \times 10^6}$$

$$= 4.24 \times 10^3$$
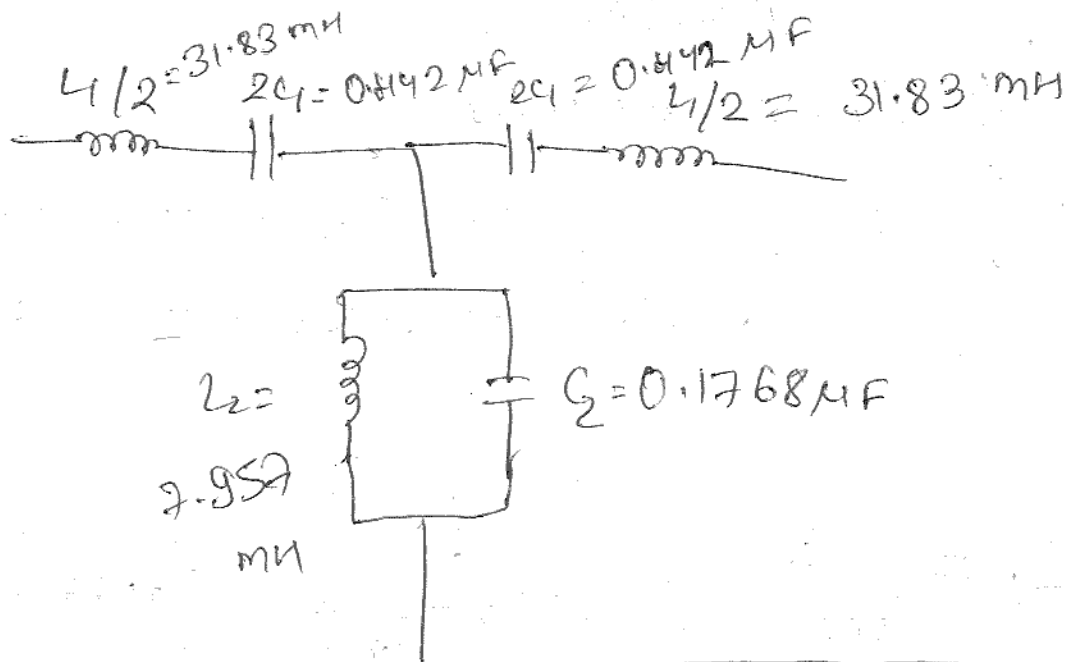
$$= 4.24 \text{ kHz} = 4242.64 \text{ Hz}$$




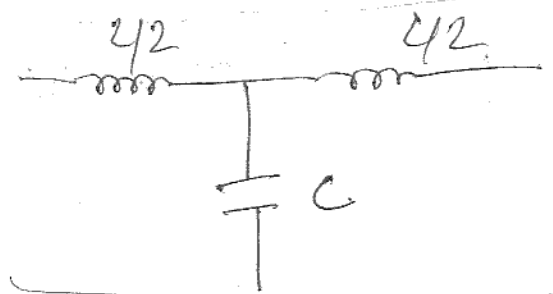(constant  $K$ )  
 Q. Design a prototype LPF (constant  $K$ )  
 section, if design impedance  
 $R_0 = 500 \Omega$  and cutoff frequency  
 $f_c = 2000 \text{ Hz}$



$$1) L = \frac{R_0}{\pi f c} = \frac{500}{\pi \times 2000} = 79.57 \text{ mH}$$
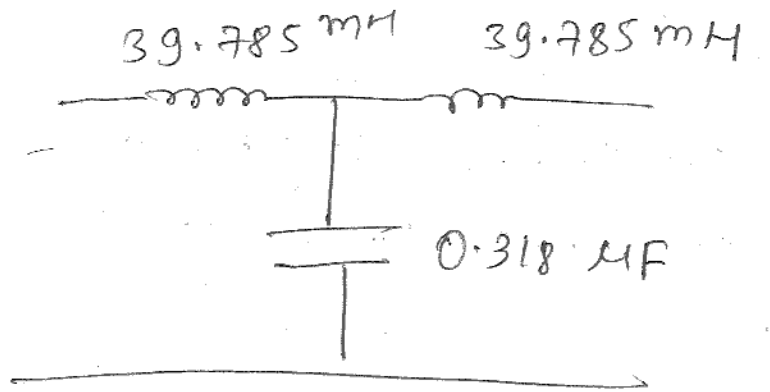
$$2) C = \frac{1}{\pi R_0 f c} = 0.318 \text{ } \mu\text{F}$$



LPF (Constant K)

Unit

Q. A transmission line of 2 miles long operates at 1 kHz & has parameters

$$R = 10.4 \text{ } \Omega/\text{mile}, \quad L = 0.00367 \text{ H/mile}$$

$$C = 0.00835 \text{ } \mu\text{F}/\text{mile}, \quad G = 0.8 \text{ } \mu\text{mho}/\text{mile}$$

Find the characteristics impedance  $Z_0$ ,  $\gamma$ ,  $\alpha$ ,  $\beta$ ,  $d$ ,  $V_p$  (Phase velocity).

$$\rightarrow \omega = 2\pi f$$

$$\rightarrow \text{Series impedance } (Z) = R + j\omega L$$

$$\rightarrow \text{Shunt admittance } (Y) = G + j\omega C$$

$$Z_0 = \sqrt{\frac{Z}{Y}} \text{ } \angle \text{ angle}, \quad \gamma = \sqrt{ZY} \text{ } \angle \text{ complex} \quad \alpha = \beta = \frac{2\pi}{\beta}$$

$$V_p = \frac{\omega}{\beta} \text{ } \angle \text{ (2 miles)}$$

Q2. The transmission line having resistance  
 $R = 6 \Omega$ ,  $L = 2.2 \text{ mH}$ ,  $C = 0.005 \mu\text{F}$ ,  
&  $G = 0.05 \mu\text{S}$

Calculate

At freq.  $1 \text{ kHz}$

(i) The terminating impedance for which no reflection will be set up in the line.

ii)  $\gamma$ ,  $v_p$ ,  $\alpha$ ,  $\beta$  &  $\lambda$

→ when

$$\rightarrow \omega = 2\pi f$$

$$\rightarrow Z = R + j\omega L$$

$$Y = G + j\omega C$$

$$Z_0 = \sqrt{\frac{Z}{Y}}$$

$$\gamma = \sqrt{ZY} = \alpha + j\beta$$

$$\rightarrow v_p = \frac{\omega}{\beta}, \quad \lambda = \frac{2\pi}{\beta}$$



Q1.  $R = 10.4 \Omega/\text{mile}$ ,  $L = 0.00367 \text{ H}/\text{mile}$   
 $C = 0.00835 \text{ MF}/\text{mile}$ ,  $G = 0.8 \mu\text{S}/\text{mile}$

$$Z = R + j\omega L$$

$$\omega = 2\pi f$$

$$\omega = 2\pi \times 10^3$$

$$Z = 10.4 + j(2\pi \times 10^3 \times 0.00367)$$

$$= 10.4 + j(23.059)$$

$$Z = 25.29 \angle 65.72^\circ$$

$$Y = G + j\omega C$$

$$= 0.8 \times 10^{-6} + j(2\pi \times 10^3 \times 0.00835 \times 10^{-6})$$

$$= 0.8 \times 10^{-6} + j(5.246 \times 10^{-5})$$

$$= 5.246 \times 10^{-5} \angle 89.126^\circ$$

$$Z_0 = \sqrt{\frac{Z}{Y}}$$

$$= \sqrt{\frac{25.29 \angle 65.72^\circ}{5.246 \times 10^{-5} \angle 89.126^\circ}}$$

$$= \sqrt{4.82 \times 10^5 \angle -23.406^\circ}$$

$$Z_0 = 692.53 \angle -11.703^\circ$$

$$\gamma = \sqrt{24}$$

$$= \sqrt{25.29 \angle 65.72^\circ \times 5.246 \times 10^{-5} \angle 89.126^\circ}$$

$$= \sqrt{0.00132 \angle 154.846^\circ}$$

$$= 0.0364 \angle 77.423^\circ$$

$$\gamma = 0.00792 + 0.03552j$$

$$\gamma = \alpha + j\beta$$

$$\alpha = 0.00792 \quad \beta = 0.03552$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2 \times 3.14}{0.03552}$$

$$\lambda = 176.88 \text{ km}$$

$$v_p = \frac{\omega}{\beta} = \frac{2\pi \times 1000}{0.03552}$$

$$= \frac{6283.185}{0.03552} \text{ cm/sec}$$

$$v_p = 1.76 \times 10^5 \text{ cm/sec}$$

$$Q2. R = 6 \Omega, L = 2.2 \text{ mH}, C = 0.005 \mu\text{F}$$

$$G = 0.05 \mu\text{S}$$

$$\omega = 2\pi \times 1000$$

$$Z = R + j\omega L$$

$$= 6 + j(2\pi \times 1000 \times 2.2 \times 10^{-3})$$

$$= 6 + j(13.823)$$

$$Z = 15.06 \angle 66.53^\circ$$

$$Y = G + j\omega C$$

$$= 0.05 \times 10^{-6} + j(2\pi \times 10^3 \times 0.005 \times 10^{-6})$$

$$= 0.05 \times 10^{-6} + j(3.142 \times 10^{-5})$$

$$= 3.141 \times 10^{-5} \angle 89.96^\circ$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{15.06 \angle 66.53^\circ}{3.141 \times 10^{-5} \angle 89.96^\circ}}$$

$$= \sqrt{4.79 \times 10^5 \angle -23.32^\circ}$$

$$Z_0 = 692.098 \angle -11.685^\circ$$

$$\gamma = 2 \sqrt{27}$$

$$= \sqrt{15.06 \angle 66.53^\circ \times 3141 \times 10^{-5} \angle 89.96^\circ}$$

$$= \sqrt{47.30 \times 10^{-5} \angle 156.43^\circ}$$

$$= 0.0217 \angle 78.215^\circ$$

$$\gamma = 0.0044 + 0.0212j$$

$$\alpha = 0.0044 \text{ nepers/km}$$

$$\beta = 0.0212 \text{ radians/km}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{0.0212} = 296.37 \text{ km}$$

$$\lambda = 296.37 \text{ km}$$


$$V_p = \frac{\omega}{\beta} = \frac{2\pi \times 1000}{0.0212}$$

$$V_p = 2.96 \times 10^5 \text{ km/sec miles}$$

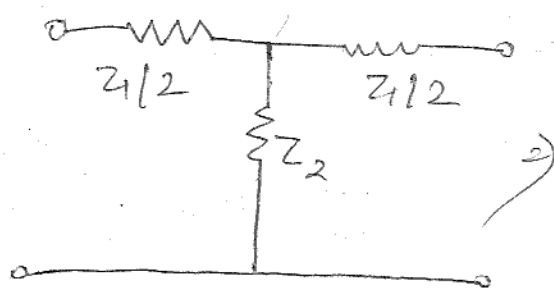
# M-derived T-Section

10/8/11

The attenuation characteristics of the filter and very high value of attenuation is achieved at a frequency near the cutoff frequency called frequency of infinite or high attenuation ( $f_{\infty}$ ) using m-derived filters.



Prototype

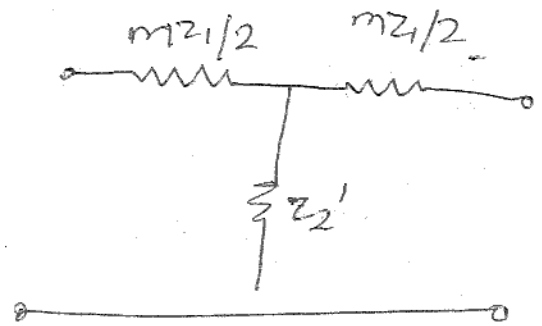

m-derived.

Consider T n/w as the series arm modified by some constant  $m$  and shunt impedance  $z_2$  modified by  $z_2'$

W.K.T

$$Z_{0T} = \sqrt{\frac{z_1^2}{4} + z_1 z_2} \quad \text{--- (1)}$$

For modified n/w.

$$z_1 = mz_1 \quad \text{and} \quad z_2 = z_2', \text{ sub in (1)}$$

$$Z_{0T} = \sqrt{\frac{m^2 z_1^2}{4} + mz_1 z_2'} \quad \text{--- (2)}$$

Sub in  $Z_{0T}$  and equate.

$$\sqrt{\frac{m^2 Z_1^2}{4} + m Z_1 Z_2'} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

Squaring both sides

$$\frac{m^2 Z_1^2}{4} + m Z_1 Z_2' = \frac{Z_1^2}{4} + Z_1 Z_2$$

$$\frac{Z_1^2}{4}(m^2 - 1) + m Z_1 Z_2' = Z_1 Z_2$$

$$m Z_1 Z_2' = \frac{4 Z_1 Z_2 (m^2 - 1)}{Z_1^2}$$

$$Z_2' = \frac{4 Z_2 (m^2 - 1)}{m Z_1}$$


$$Z_2' = \frac{4 Z_2 (m^2 - 1)}{m Z_1}$$

$$m Z_1 Z_2' = Z_1 Z_2 - \frac{Z_1^2}{4} (m^2 - 1)$$

$$Z_2' = \frac{Z_2}{m} + \frac{(1 - m^2) Z_1^2}{4m}$$

The above eqn gives that  $Z_2'$  must  
impedance  $\frac{Z_2}{m}$  in series with an  
impedance  $\frac{(1 - m^2) Z_1^2}{4m}$ .

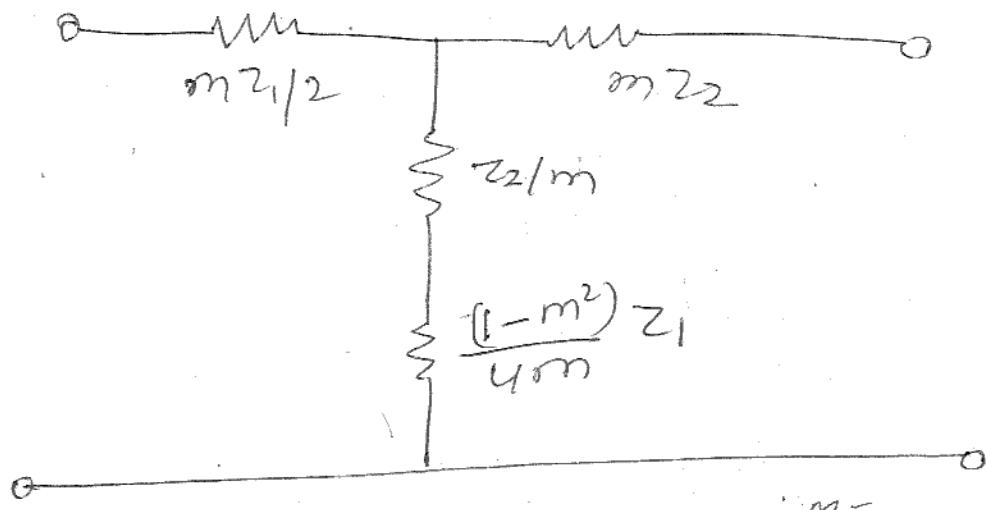and these can be physically realisable  
if  $0 < m < 1$




This is the complete <sup>m-</sup>derived ~~part~~ section.

### M-derived LPF

Consider the shunt arm of T-section  
Resonates at the frequency of infinite  
impedance i.e.  $f_0$  which is selected just  
above cutoff frequency  $f_c$ . Hence the  
frequency of resonance is given by

$$\left| \frac{Z_2}{m} \right| = \left| \frac{(1-m^2)Z_1}{4m} \right| \quad \text{--- (1)}$$

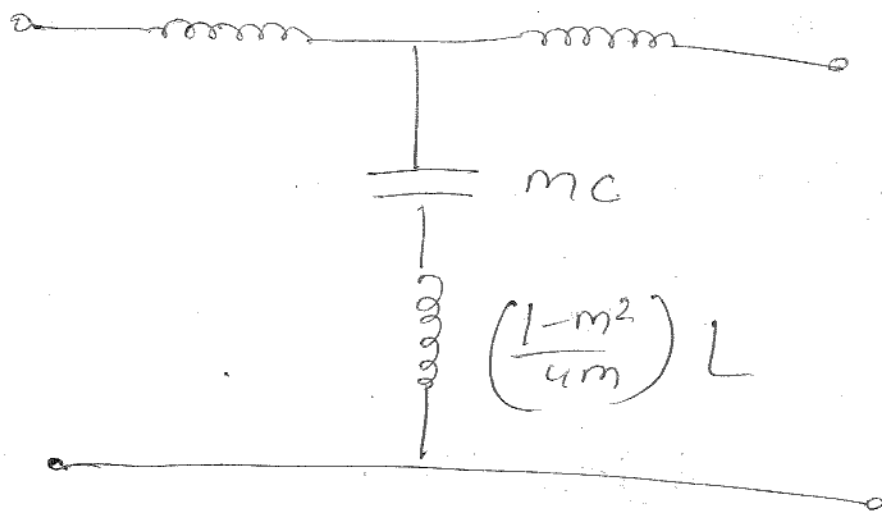for LPF,  $Z_1 = j\omega L$ ,  $Z_2 = -j\omega C$



Sub  $Z_1 = j 2\pi f_{\infty} L$ ,  $Z_2 = \frac{-j}{2\pi f_{\infty} C}$  in (1)

$$\left(\frac{Z_2}{m}\right) = \left(\frac{-j}{2\pi f_{\infty} C m}\right) = \left(\frac{(1-m^2) j 2\pi f_{\infty} L}{4m}\right)$$

$$m \frac{1}{2\pi f_{\infty} C} = \frac{(1-m^2)}{4m} \cdot 2\pi f_{\infty} L$$

$$f_{\infty}^2 = \frac{4m}{4\pi^2 m^2 (1-m^2) LC}$$

$$f_{\infty}^2 = \frac{1}{\pi^2 (1-m^2) LC}$$

$$f_{\infty} = \frac{1}{\pi \sqrt{(1-m^2) LC}} \quad \text{--- (2)}$$

$\therefore$  cutoff frequency of LCR is



$$f_c = \frac{1}{\pi \sqrt{LC}} \rightarrow (3)$$

$$f_{\infty} = \frac{f_c}{\sqrt{1-m^2}}$$

$$f_{\infty}^2 = \frac{f_c^2}{1-m^2}$$

$$1-m^2 = \frac{f_c^2}{f_{\infty}^2}$$

$$1 - \frac{f_c^2}{f_{\infty}^2} = m^2$$

$$m^2 = 1 - \left( \frac{f_c}{f_{\infty}} \right)^2$$

$$m = \sqrt{1 - \left( \frac{f_c}{f_{\infty}} \right)^2}$$

Variation of attenuation constant ( $\alpha$ ) and phase constant ( $\beta$ ) with frequency.

The variation of attenuation over the attenuation band for a LPF m-derived section in the stop band is dependent on the sign of the reactance.

$$\alpha = 2 \cosh^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|} \quad \text{for } f_c < f < f_{\infty}$$

$$\alpha = 2 \sin^{-1} \sqrt{\left| \frac{z_1}{4z_2} \right|} \quad \text{for } \text{fact}$$

For  $z_1 = j\omega L$  and  $z_2 = \frac{-j}{\omega C}$ , then

$$\left| \frac{z_1}{4z_2} \right| = \left| \frac{j\omega L \cdot \omega C}{-j4} \right|$$

$$= \frac{\omega^2 LC}{4}$$

In terms of  $m$  derived

$$\left| \frac{z_1}{4z_2} \right| = \frac{z_1 m}{4z_2}$$

$$\left| \frac{j\omega L \omega C}{4(-j)} \right| = \frac{m^2 \cancel{j\omega L}}{4 \left[ \frac{z_2}{m} + \frac{(1-m^2)z_1^2}{4m} \right]}$$

$$\frac{\omega^2 LC}{4} = \frac{m^2 z_1}{\frac{4z_2}{m} + \frac{(1-m^2)z_1^2}{m}}$$

$$\frac{\omega^2 LC}{4} = \frac{m^2 z_1 \cancel{z_2}}{4z_2 + (1-m^2)z_1^2}$$

$$\frac{\omega^2 LC}{4} = \frac{m^2 z_1}{4z_2 + (1-m^2)z_1^2} \quad \checkmark$$

$$\frac{\omega^2 LC}{4} = \frac{m^2 (j\omega L)}{-\frac{4j}{\omega C} + (1-m^2)j\omega L}$$

$$\frac{\omega^2 LC}{4} = \frac{j\omega L \cdot m^2 \omega C}{-4j + (1-m^2)j\omega^2 LC}$$

$$\frac{\omega^2 LC}{4} = \frac{m^2 j \cdot \omega^2 LC}{j(-4 + (1-m^2)\omega^2 LC)}$$

$$\frac{\omega^2 LC}{4} = \frac{m^2 \omega^2 LC}{(1-m^2)\omega^2 LC - 4}$$

$$\frac{1}{4} = \frac{m^2}{(1-m^2)\omega^2 LC - 4}$$

$$4m^2 = (1-m^2)\omega^2 LC - 4$$

$$4(m^2+1) = (1-m^2)\omega^2 LC$$


$$\omega^2 = \frac{4(m^2+1)}{(1-m^2)LC}$$

$$(2\pi f_{\infty})^2 = \frac{4(m^2+1)}{(1-m^2)LC}$$

$$4\pi^2 f_{\infty}^2 = \frac{4(m^2+1)}{(1-m^2)LC}$$


$$f_{\infty}^2 = \frac{1(m^2+1)}{\pi^2 (1-m^2)LC}$$
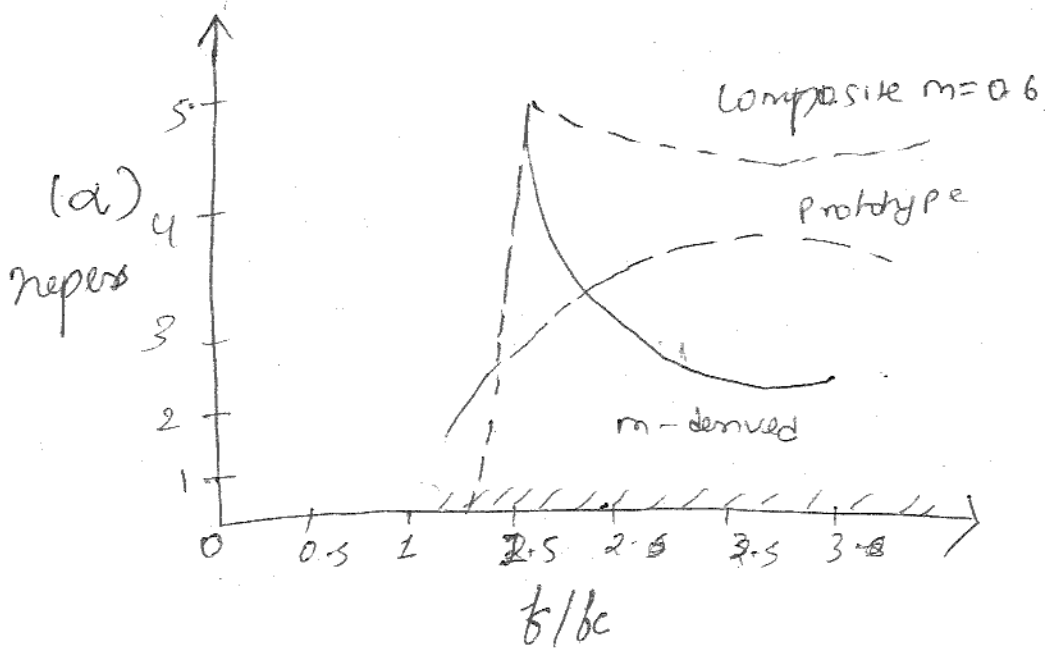
$$f_{\infty} = \frac{1}{\pi} \sqrt{\frac{m^2+1}{(1-m^2)LC}}$$




Similarly for phase constant - determine in passband given by  $\beta = 2 \sin^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|}$  and
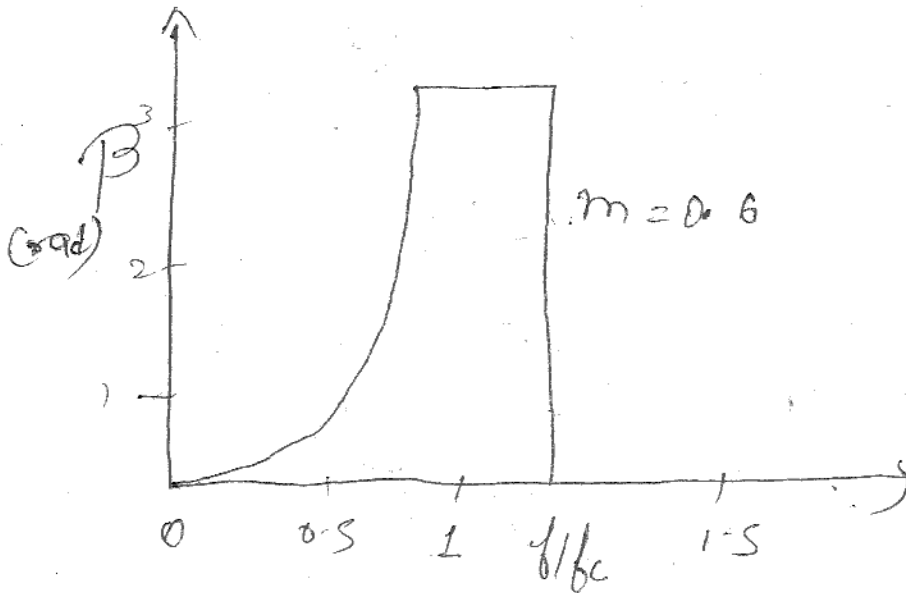
$$\beta = \frac{2 \sin^{-1} m f/f_c}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2 (1 - m^2)}}$$



# M-derived High pass filter

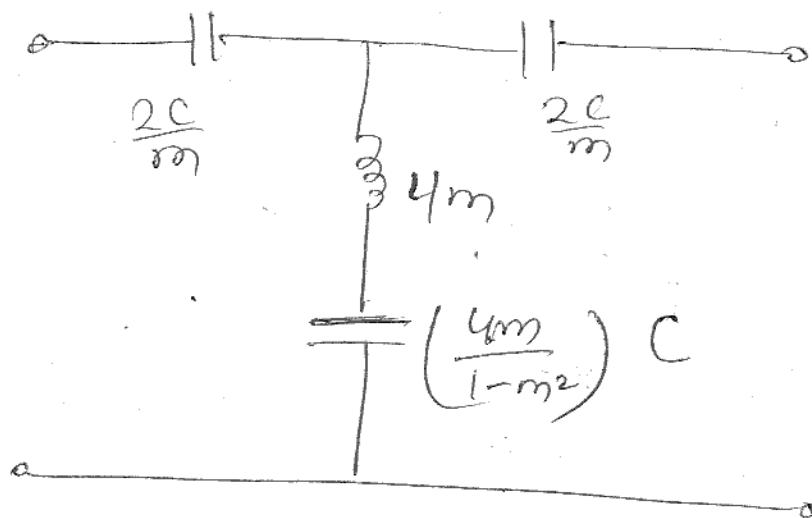

Consider the shunt arm of T-section resonates at frequency of infinite attenuation which is selected just below cutoff frequency. This frequency of resonance is given by

$$Z_1 = \frac{-j}{\omega C} \quad \text{and} \quad Z_2 = j\omega L$$

$$\left| \frac{Z_2}{m} \right| = \left| \frac{(1-m^2) Z_1}{4m} \right|$$

$$\left| \frac{j\omega L}{m} \right| = \left| \frac{(1-m^2)(-j)}{\omega C \cdot 4m} \right|$$

$$\frac{2\pi f_{\infty} L}{m} = \frac{(1-m^2)}{4m \cdot 2\pi f_{\infty} C}$$

$$f_{\infty}^2 = \frac{(1-m^2) \times m}{4m \cdot 2\pi C \times 2\pi L}$$

$$f_{\infty}^2 = \frac{(1-m^2)}{16\pi^2 LC}$$

$$f_{\infty} = \frac{1}{4\pi} \sqrt{\frac{1-m^2}{LC}}$$

$$f_c = \frac{1}{4\pi \sqrt{LC}}$$

$$\left| \frac{Z_2}{m} \right| = \sqrt{1-m^2}$$

$$f_{\infty} = f_c \sqrt{1-m^2}$$

Squaring both side

$$f_{\infty}^2 = f_c^2 (1-m^2)$$

$$f_{\infty}^2 = f_c^2 - m^2 f_c^2$$

$$m^2 f_c^2 = f_c^2 - f_{\infty}^2$$

$$m^2 = 1 - \left(\frac{f_{\infty}}{f_c}\right)^2$$

$$m = \sqrt{1 - \left(\frac{f_{\infty}}{f_c}\right)^2}$$

Variation of attenuation constant  $\alpha$  and phase constant  $\beta$  with frequency.

$$\alpha = 2 \cosh^{-1} \left[ \frac{m (fc/f)}{\sqrt{1 - (f/f_c)^2}} \right] \quad f < f_c$$


$$\alpha = 2 \sinh^{-1} \left[ \frac{m (fc/f)}{\sqrt{(f/f_c)^2 - 1}} \right] \quad f > f_c$$

For phase constant ' $\beta$ '


$$\beta = 2 \sin^{-1} \left[ \frac{m (fc/f)}{\sqrt{1 - (f/f_c)^2}} \right]$$

M derived  $\pi$  section

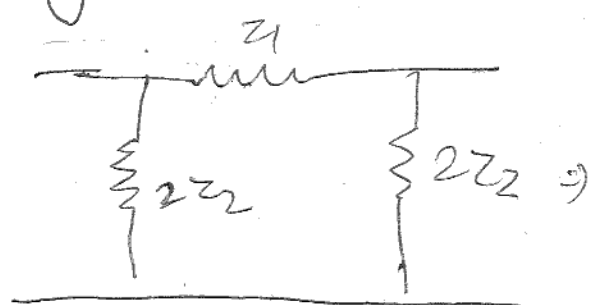Consider  $\pi$  network of  $m$ -derived section,  $Z_1'$  be series impedance &  $2Z_2'$  being the shunt impedance.



Prototype -  $\pi$  section

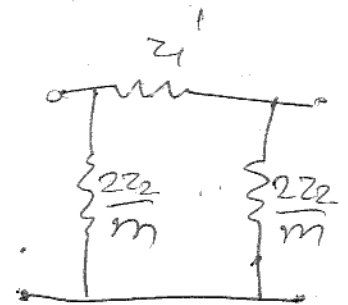

$m$ -derived.

$$Z_{0T} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}} \quad \text{--- (1)}$$

For modified n/w

$$Z_1 = Z_1', \quad Z_2 = \frac{Z_2}{m} \quad \text{--- m (1)}$$

$$Z_{0T} = \sqrt{\frac{Z_1' \cdot \frac{Z_2}{m}}{1 + \frac{Z_1' m}{4Z_2}}} \quad \text{--- (2)}$$

$$Z_{0T} = \sqrt{\frac{\frac{Z_1' Z_2}{m} \times 4Z_2}{4Z_2 + Z_1' m}}$$

$$Z_{0T} = \sqrt{\frac{4Z_1' Z_2^2}{4Z_2 m + Z_1'}} \quad \text{--- (3)}$$

Equate (1) & (2)

$$\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}} = \frac{4Z_1' Z_2^2}{4Z_2 m + Z_1'} \cdot \frac{\frac{Z_1' Z_2}{m}}{1 + \frac{Z_1' m}{4Z_2}}$$

$$\frac{Z_1}{1 + \frac{Z_1}{4Z_2}} = \frac{Z_1'}{m + \frac{Z_1'}{4Z_2}}$$

$$mZ_1 + \frac{Z_1' Z_1}{4Z_2} = Z_1' + \frac{Z_1' Z_1}{4Z_2}$$



$$z_1' = m z_1 + \frac{z_1' z_1}{4z_2} - \frac{z_1' z_1}{4z_2}$$

$$z_1' = m z_1 + \cancel{\frac{z_1' z_1}{4z_2}}$$

$$z_1' = m z_1$$

$$z_1 \frac{z_1'}{z_1} \left( 1 + \frac{m z_1'}{4z_2} \right) = \frac{z_1' z_1}{m} \left( 1 + \frac{z_1}{4z_2} \right)$$

$$z_1' = \frac{z_1 m \left( 1 + \frac{m z_1'}{4z_2} \right)}{\left( 1 + \frac{z_1}{4z_2} \right)}$$

$$z_1' = \frac{z_1 m (4z_2 + m z_1')}{(4z_2 + z_1)}$$

$$z_1' = \frac{4z_1 z_2 m + m^2 z_1' z_1}{4z_2 + z_1}$$

$$z_1' = \left[ z_1 m + \frac{z_1 z_1' m^2}{4z_2} \right] \left[ \frac{1}{1 + \frac{z_1}{4z_2}} \right]$$

$$z_1' - \frac{z_1 z_1' m^2}{4z_2} \cdot \frac{1}{1 + \frac{z_1}{4z_2}} = \frac{z_1 m}{1 + \frac{z_1}{4z_2}}$$

$$z_1' \left( 1 - \frac{z_1 m^2 \times 4z_2}{4z_2 \cdot 4z_2 + z_1} \right) = \frac{z_1 m}{1 + \frac{z_1}{4z_2}}$$

$$z_1' \left( 1 - \frac{z_1 m^2}{4z_2 + z_1} \right) = \frac{4z_2 z_2 m}{4z_2 + z_1}$$

$$z_1' \left[ \frac{4z_2 + z_1 - z_1 m^2}{4z_2 + z_1} \right] = \frac{4z_2 z_2 m}{4z_2 + z_1}$$

$$z_1' = \frac{4z_2 z_2 m}{4z_2 + z_1}$$

Divide by  $4m$ .

$$z_1' = \frac{z_1 z_2}{\frac{z_1 (1-m^2)}{4m} + \frac{4z_2}{4m}}$$


$$z_1' = \frac{z_1 z_2}{\frac{z_2}{m} + \frac{z_1 (1-m^2)}{4m}}$$

multiply num & deno by  $\frac{4m^2}{1-m^2}$

$$z_1' = \frac{z_1 z_2 \left( \frac{4m^2}{1-m^2} \right)}{\frac{z_2}{m} \times \frac{4m^2}{1-m^2} + \frac{z_1 (1-m^2)}{4m} \times \frac{4m^2}{1-m^2}}$$

$$z_1' = \frac{z_1 z_2 \left( \frac{4m^2}{1-m^2} \right)}{z_1 m + \frac{4z_2 m}{(1-m^2)}}$$

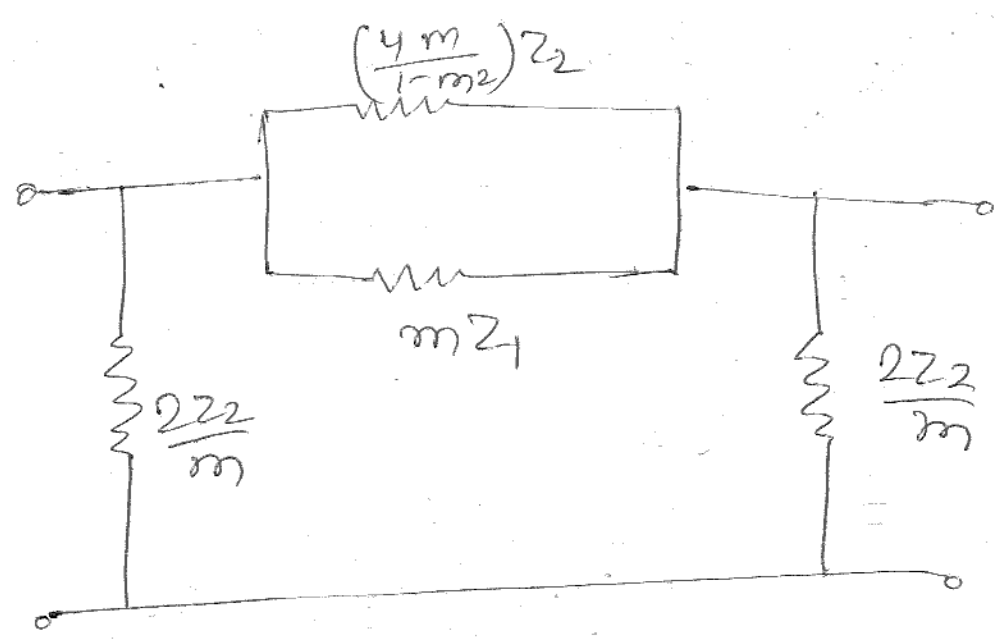
$$Z_1' = \frac{mZ_1 + \frac{4m}{1-m^2} Z_2}{2}$$



The above equation  $Z_1'$  it is a combination of two parallel impedances namely  $Z_1$  &  $\frac{4m}{1-m^2} Z_2$ .

11/8/11

## BPF

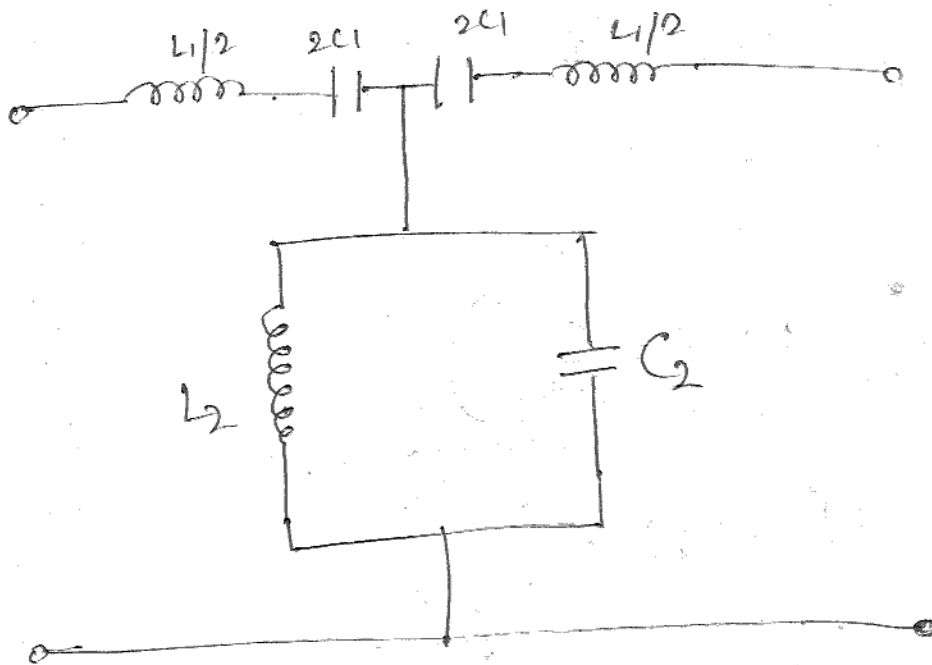

It consists of two parallel L & C connected.  
Hence at Resonance for each of the  
Series and shunt arm

$$\omega_0^2 L_1 C_1 = 1 \quad - \textcircled{1}$$

$$\omega_0^2 L_2 C_2 = 1 \quad - \textcircled{2}$$

Series impedance is  $Z_1$  & shunt impedance  
is  $Z_2$ .

Equate  $\textcircled{1}$  &  $\textcircled{2}$

$$\omega_0^2 L_1 C_1 = \omega_0^2 L_2 C_2 = 1$$

$$L_1 C_1 = L_2 C_2$$

$$\boxed{\frac{L_1}{C_2} = \frac{L_2}{C_1}}$$

The impedance of the arms are

$$Z_1 = j\omega L_1 + \frac{1}{j\omega C_1}$$

$$Z_1 = j\omega L_1 - \frac{j}{\omega C_1}$$

$$Z_1 = j \left( \frac{\omega^2 L_1^2 - 1}{\omega C_1} \right)$$

$$Z_2 = \frac{j\omega L_2 \left( \frac{-j}{\omega C_2} \right)}{j\omega L_2 - \frac{j}{\omega C_2}}$$

$$= \frac{\cancel{j} L_2}{C_2}$$

$$j \left( \frac{\omega^2 L_2 C_2 - 1}{\omega C_2} \right)$$

$$Z_2 = \frac{\frac{L_2}{C_2} \times \omega C_2}{j(\omega^2 L_2 C_2 - 1)} = \frac{\omega L_2}{j(\omega^2 L_2 C_2 - 1)}$$

$$Z_2 = \frac{+j\omega L_2}{1 - \omega^2 L_2 C_2}$$

w.k.t for constant K-filters

$$Z_1 Z_2 = R_0^2$$

$$Z_1 Z_2 = \left( j\omega L_1 + \frac{1}{j\omega C_1} \right) \left( \frac{j\omega L_2}{1 - \omega^2 L_2 C_2} \right)$$

$$= j \left( \frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right) \left( \frac{j\omega L_2}{1 - \omega^2 L_2 C_2} \right)$$

$$= \frac{(1 - \omega^2 L_1 C_1) \omega L_2}{\omega C_1 (1 - \omega^2 L_2 C_2)}$$

$$Z_1 Z_2 = \frac{L_2}{C_1} \cdot \frac{(1 - \omega^2 L_1 C_1)}{(1 - \omega^2 L_2 C_2)}$$

$$\therefore L_1 C_1 = L_2 C_2$$

$$Z_1 Z_2 = \frac{L_2}{C_1} \cdot \frac{(1 - \omega^2 L_2 C_2)}{(1 - \omega^2 L_2 C_2)}$$

$$Z_1 Z_2 = \frac{L_2}{C_1} = R_0^2 \quad \text{--- (3)}$$

(00)

$$\frac{L_1}{C_2} = R_0^2 \quad \text{--- (3a)}$$

$$R_0 = \sqrt{\frac{L_2}{C_1}} \quad \text{--- (3b)}$$

At the cutoff frequencies.

$$Z_1 = -4Z_2 \quad \text{--- (4)}$$

multiply  $Z_1$  in eqn (4)

$$Z_1^2 = -4Z_1Z_2$$

$$Z_1^2 = -4R_0^2$$

$$Z_1 = \pm 2jR_0 \rightarrow \text{(5)}$$

So that  $Z_1$  at lower cutoff frequency

$f_1 = -Z_1$  at upper cutoff frequency  
 $f_2$

$$j(\omega_1 L_1 + \frac{j}{\omega_1 C_1}) = -j(\omega_2 L_1 + \frac{-j}{\omega_2 C_1})$$

$$j(\omega_1 L_1 + \frac{1}{\omega_1 C_1}) = -j(\omega_2 L_1 + \frac{1}{\omega_2 C_1})$$

$$\frac{1 - \omega_1^2 L_1 C_1}{\omega_1 C_1} = \frac{\omega_2^2 C_1 L_1 - 1}{\omega_2 C_1}$$

$$(1 - \omega_1^2 L_1 C_1) = \frac{\omega_1}{\omega_2} (\omega_2^2 C_1 L_1 - 1) \quad \text{--- (6)}$$

from (1)

$$\omega_0^2 L_1 C_1 = 1$$

$$L_1 C_1 = \frac{1}{\omega_0^2} \quad - (7)$$

sub (7) in (6)

$$\left(1 - \frac{\omega_1^2 \cdot 1}{\omega_0^2}\right) = \frac{\omega_1}{\omega_2} \left(\frac{\omega_2^2}{\omega_0^2} - 1\right)$$

$$\left(1 - \frac{\omega_1^2}{(\omega_0)^2}\right) = \frac{\omega_1}{\omega_2} \left(\frac{\omega_2^2}{\omega_0^2} - 1\right)$$

$$\left[1 - \left(\frac{f_1}{f_0}\right)^2\right] = \frac{f_1}{f_2} \left[\left(\frac{f_2}{f_0}\right)^2 - 1\right]$$

$$\frac{f_0^2 - f_1^2}{f_0^2} = \frac{f_1}{f_2} \left(\frac{f_2^2 - f_0^2}{f_0^2}\right)$$

$$f_0^2 - f_1^2 = \frac{f_1}{f_2} (f_2^2 - f_0^2)$$

$$f_0^2 - f_1^2 = f_1$$

$$1 - \left(\frac{f_1}{f_0}\right)^2 = \frac{f_1 f_2}{f_0^2} - \frac{f_1}{f_2}$$

$$1 + \frac{f_1}{f_2} = \frac{f_1 f_2}{f_0^2} + \frac{f_1^2}{f_0^2}$$



$$1 + \frac{b_1}{f_2} = \frac{b_1 b_2 + b_1^2}{f_0^2}$$

$$f_0^2 = \frac{b_1 b_2 + b_1^2}{\cancel{f_0^2}}$$

$$f_0^2 = \frac{1 + \frac{b_1}{f_2}}{\left( \frac{b_1 b_2 + b_1^2}{f_2 + b_1} \right) f_2}$$

$$= \frac{f_1 (f_1 + f_2)}{(f_2 + f_1) f_2}$$

$$f_0^2 = b_1 f_2$$

$$\boxed{f_0 = \sqrt{b_1 \cdot b_2}} \quad (8)$$

## Design of BPF

At lower cutoff frequency

$$* Z_1 = -j2R$$

$$Z_1 = j\omega L - \frac{j}{\omega C_1} = -j2R$$

$$-j \left( -\omega L + \frac{1}{\omega C_1} \right) = -j2R$$

$$\frac{1 - \omega_1^2 L_1 C_1}{\omega_1 C_1} = 2R$$

from eqn (7)  
 $L_1 C_1 = \frac{1}{\omega_0^2}$

$$1 - \omega_1^2 L_1 C_1 = 2R \omega_1 C_1$$

$$1 - \frac{\omega_1^2}{\omega_0^2} = 2R \omega_1 C_1$$

$$\Rightarrow \frac{\omega_0^2 - \omega_1^2}{\omega_0^2} = 2R \times 2\pi f_1 C_1$$

$$\Rightarrow 1 - \frac{f_1^2}{f_0^2} = 4\pi R f_1 C_1$$

$$C_1 = \frac{f_0^2 - f_1^2}{(4\pi R f_1 f_0^2)}$$

$$C_1 = \frac{f_1 f_2 - f_1^2}{4\pi R f_1 \cdot f_1 f_2}$$

$$\sqrt{f_0^2} = \sqrt{f_1 f_2}$$

$$C_1 = \frac{f_1 (f_2 - f_1)}{4\pi R f_1^2 f_2}$$

$$C_1 = \frac{f_2 - f_1}{4\pi R f_1 f_2} \quad \text{--- (9)}$$

from eqn (7) & (8)

$$L_1 C_1 = \frac{1}{\omega_0^2}, \quad f_0 = \sqrt{f_1 f_2}$$

$$f_0^2 = f_1 f_2$$

$$L_1 = \frac{1}{\omega_0^2 C_1}$$

$$L_2 = \frac{1}{(2\pi f_0)^2 \left( \frac{f_2 - f_1}{4\pi R f_1 f_2} \right)}$$

$$= \frac{4\pi R f_1 f_2}{4\pi^2 f_0^2 (f_2 - f_1)}$$

$$= \frac{4\pi R f_1 f_2}{4\pi^2 f_1 f_2 (f_2 - f_1)}$$

$$L_2 = \frac{R}{\pi(f_2 - f_1)} \quad \text{--- (10)}$$

from eqn (3)

$$\frac{L_2}{C_1} = R^2 \quad \text{--- (11)}$$

sub  $C_1$  in (11)

$$\frac{L_2 4\pi R f_1 f_2}{(f_2 - f_1)} = R^2$$

$$\therefore L_2 = \frac{R(f_2 - f_1)}{4\pi f_1 f_2} \quad (12)$$

from (9)


$$\frac{L_1}{C_2} = R_o^2 \quad (13)$$

$$C_2 = \frac{L_1}{R_o^2}$$

$$C_2 = \frac{R}{\pi(f_2 - f_1) \cdot R_o^2}$$

$$C_2 = \frac{1}{\pi R (f_2 - f_1)} \quad (13)$$

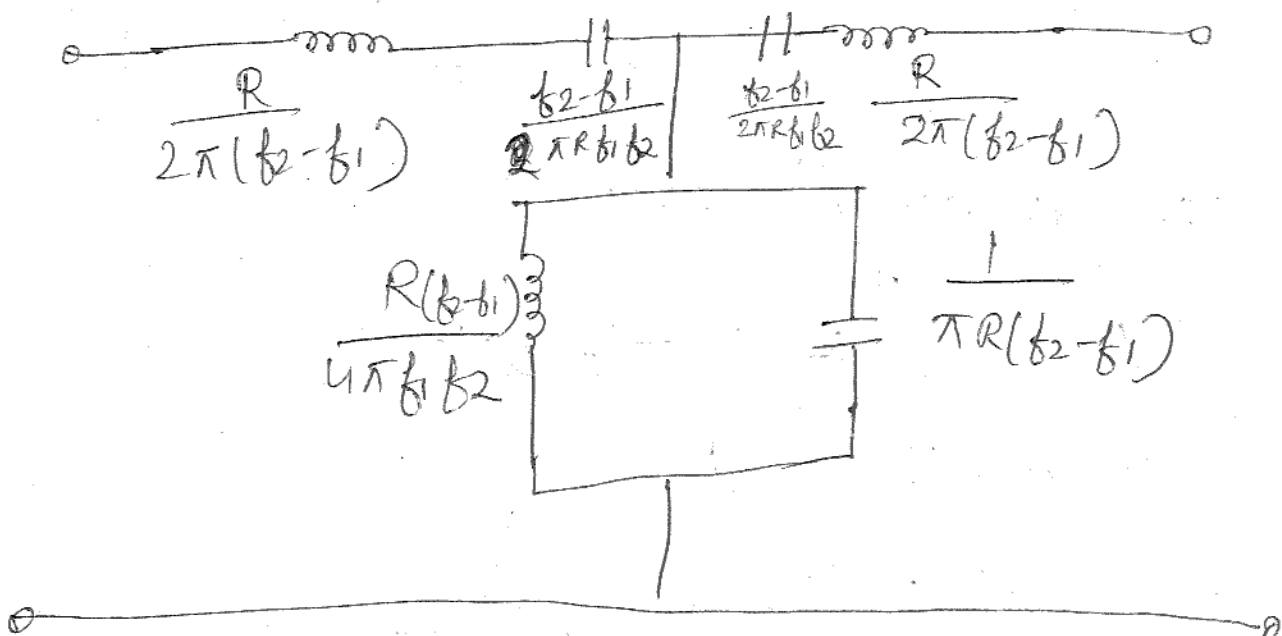
This completes the design of prototype BP filter.


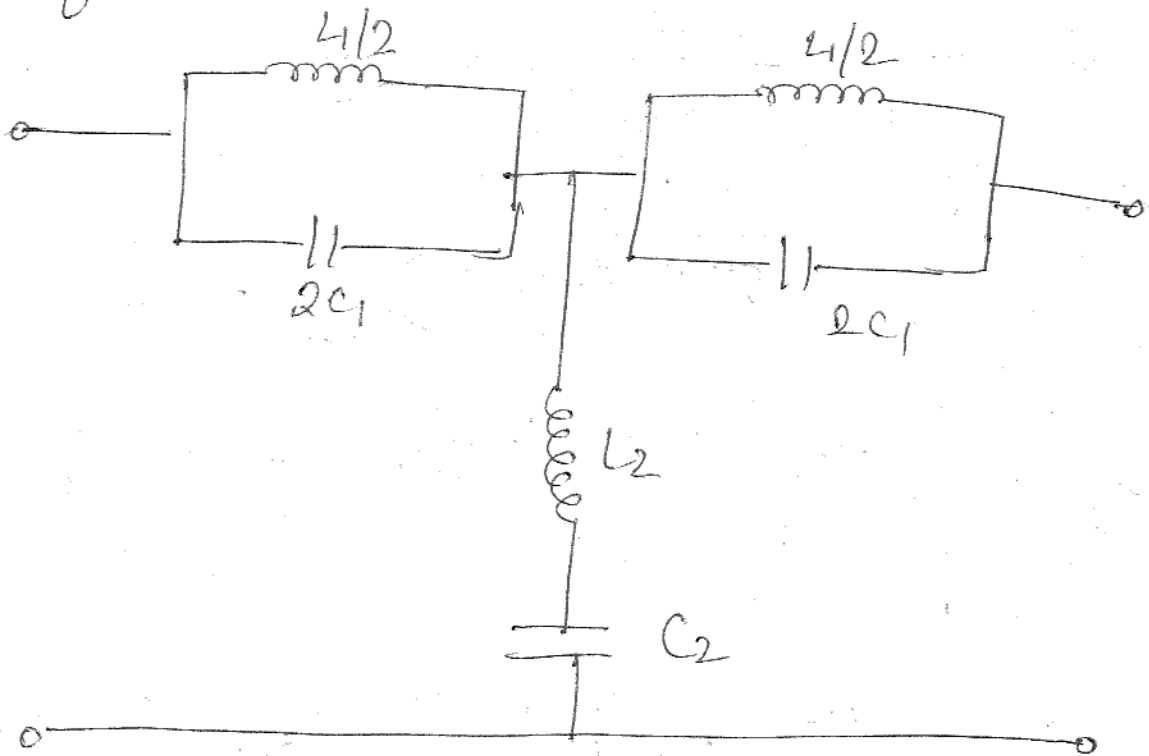
## Band Elimination Filters

If the series and parallel tuned circuits or parallel tuned arms of the Band Pass filter are interchanged, then the result is Band Elimination filter.

Here the cutoff frequency of HPF is higher than the cutoff frequency of LPF.



At frequency response

$$\omega_0^2 L_1 C_1 = \omega_0^2 L_2 C_2 = 1 \quad \text{--- (1)}$$

from eqn (1)

$$L_1 C_1 = L_2 C_2 = \frac{1}{\omega_0^2} \quad \text{--- (2)}$$

$$\frac{L_1}{C_2} = \frac{L_2}{C_1} = \frac{R_0^2}{\omega^2} \quad (3)$$

$$f_0 = \sqrt{f_1 f_2} \quad (4)$$

At  $f_c$

$$Z_1 = -4Z_2 \quad (5)$$

multiply  $Z_2$  in eqn (5)

$$Z_1 Z_2 = -4Z_2^2$$

$$\cancel{Z_1 Z_2} = \cancel{R_0^2} = -4Z_2^2$$

$$-\frac{R_0^2}{4} = Z_2^2$$

$$Z_2 = \pm j \frac{R_0}{2} \quad (6)$$

If the ~~low~~ filter is terminated in a load  $R = R_0$ , then lower cut-off frequency

$$Z_2 = j \left( \frac{1}{\omega C_2} - \omega L_2 \right) = j \frac{R_0}{2}$$
$$1 - \omega^2 L_2 C_2$$

$$1 - \frac{\omega_1^2}{\omega_0^2} = \frac{2\pi f_1 C_2 R}{2} \quad \left[ \because L_2 C_2 = \frac{1}{\omega_0^2} \right]$$

$$1 - \frac{b_1^2}{f_0^2} = \pi f_1 C_2 R$$

$$C_2 = \frac{f_1 f_2 - b_1^2}{f_1 f_2 \pi f_1 R} = \frac{f_1 (f_2 - b_1)}{f_1^2 f_2 \pi R}$$

$$C_2 = \frac{f_2 - b_1}{\pi f_1 f_2 R} \quad \text{--- (7)}$$

from eqn (2) & (4)

$$L_2 C_2 = \frac{1}{\omega_0^2} \quad \text{--- (8)} \quad f_0 = \sqrt{b_1 f_2}$$

$$\omega \cdot R \cdot T \quad \omega_0^2 = (2\pi f_0)^2$$

$$L_2 = \frac{1}{4\pi^2 f_0^2 C_2}$$

$$= \frac{1}{\pi^2 f_1 f_2 R}$$

$$4\pi^2 f_1 f_2 (f_2 - b_1)$$

$$L_2 = \frac{R}{4\pi (f_2 - b_1)} \quad \text{--- (9)}$$

11/10/14 The values for the series arm obtained as

$$\frac{L_1}{C_2} = R_0^2$$

$$L_1 = R^2$$

$$\frac{f_2 - f_1}{\pi f_1 f_2 R}$$

$$L_1 = R^2 \cdot \frac{f_2 - f_1}{\pi f_1 f_2 R}$$

$$L_1 = \frac{R (f_2 - f_1)}{\pi f_1 f_2} \quad \text{--- (10)}$$

$$\frac{L_2}{C_1} = R_0^2$$

$$C_1 = \frac{L_2}{R_0^2}$$

$$= \frac{R}{4\pi (f_2 - f_1) R^2}$$

$$C_1 = \frac{1}{4\pi R (f_2 - f_1)} \quad \text{--- (11)}$$

eqns (7), (9), (10), (11), computes the design the prototype Band Elimination filter.



The Resistance of a Copper coaxial line is given by  $R_{ac} = 4.16 \times 10^{-8} \sqrt{f} \left( \frac{1}{b} + \frac{1}{a} \right)$   $\Omega/m$ .

where  $a$  and  $b$  are outer radius of inner conductor and inner radius of outer conductor respectively.

The Shunt Susceptance and power factor are

$$Y = G + j\omega C$$

$$P.F = \frac{G}{\sqrt{G^2 + \omega^2 C^2}}$$

If  $G \ll \omega C$  then

$$P.F = \frac{G}{\omega C}$$

$$G = \omega C \times P.F$$

Dissipation factor, - The ratio of Energy dissipated and to the Energy stored in the Dielectric per cycle and it is proportional to the tangent of angle  $\phi$ .

If  $G \gg \omega C$ , the dissipation factor and power factor are equal in

magnitude.

## Constants for the line of zero-dissipation

For transmission of energy at high frequencies where the power efficiency is high, it is possible to assume negligible losses are zero.

The line parameters of the line of zero dissipation are

$$Z = j\omega L, \quad Y = j\omega C$$

Characteristic impedance  $Z_0 = \sqrt{\frac{Z}{Y}}$

$$Z_0 = \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}}$$

$$\boxed{Z_0 = \sqrt{\frac{L}{C}} \Omega}$$

Propagation constant,  $\gamma = \sqrt{ZY}$

$$\gamma = \sqrt{j\omega L \cdot j\omega C} = \sqrt{-\omega^2 LC}$$

$$\boxed{\gamma = j\omega \sqrt{LC}} \quad - (1)$$

W.K.T

$$\gamma = \alpha + j\beta \quad - (2)$$

$$\alpha = 0, \quad \beta = \omega\sqrt{LC}$$

Velocity of propagation  $v_p = \frac{\omega}{\beta}$

$$= \frac{\omega}{\omega\sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$v_p = \frac{1}{\sqrt{LC}} \text{ m/sec}$$

$$[\because v = 3 \times 10^8 \text{ m/s}]$$

wavelength  $\lambda = \frac{2\pi}{\beta}$

$$\lambda = \frac{2\pi}{\omega\sqrt{LC}}$$

$$= \frac{2\pi}{2\pi f\sqrt{LC}}$$

$$\lambda = \frac{1}{f\sqrt{LC}}$$

## Voltages and currents on the dissipation line

The voltage at any point distant  $s$  units from the receiving end of a transmission line is

$$E = \frac{ER(z_R + z_0)}{2z_R} (e^{\alpha s} + ke^{-\alpha s}) \quad \text{--- (1)}$$

For zero dissipation line,  $\alpha = 0$ ,  
and  $z_0 = R_0$

$$E = \frac{ER(z_R + z_0)}{2z_R} (e^{j\beta s} + ke^{-j\beta s}) \quad \text{--- (2)}$$

where  $e^{j\beta s}$  is nothing but incident wave moves from source to load.

$e^{-j\beta s}$  is reflected wave moves from load to source (L-S).

$$E = \frac{ER(z_R + z_0)}{2z_R} e^{j\beta s} + k \cdot \frac{ER(z_R + z_0)}{2z_R} e^{-j\beta s}$$

$$= \underbrace{\frac{ERz_R}{2z_R} (e^{j\beta s} + ke^{-j\beta s})}_{k=1} + \underbrace{\frac{ERz_0}{2z_R} (e^{j\beta s} + ke^{-j\beta s})}_{k=1}$$

$$= \frac{ERz_R}{z_R} \left( \frac{e^{j\beta s} + e^{-j\beta s}}{2} \right) + \frac{jERz_0}{z_R} \left( \frac{e^{j\beta s} - e^{-j\beta s}}{2j} \right)$$

$$= \frac{ERz_R}{z_R} (\cosh \beta s) + \frac{jERz_0}{z_R} \sinh \beta s$$

$$E = ER (\cos \beta s) + j I R Z_0 \sin \beta s \quad (3)$$

Similarly

$$I = I R \cos \beta s + j \frac{ER}{Z_0} \sin \beta s \quad (4)$$

W.K.T

$$\beta = \frac{2\pi}{\lambda} \quad \text{In eqn } (3) \& (4)$$

$$E = ER \left( \cos \frac{2\pi s}{\lambda} \right) + j I R Z_0 \sin \frac{2\pi s}{\lambda}$$

$$I = I R \left( \cos \frac{2\pi s}{\lambda} \right) + j \frac{ER}{Z_0} \sin \frac{2\pi s}{\lambda}$$

Therefore, the voltage and current distribution is the sum of cosine & sine distribution.

If the line is open circuited,  $I_R = 0$   
then

$$E_{oc} = ER \cos \frac{2\pi s}{\lambda}$$

$$I_{oc} = j \frac{ER}{Z_0} \sin \frac{2\pi s}{\lambda}$$

If the line is short-circuited  $ER = 0$ ,  
then

$$E_{sc} = j I R Z_0 \sin \frac{2\pi s}{\lambda}$$

$$I_{sc} = I R \left( \cos \frac{2\pi s}{\lambda} \right)$$


From eqn (2) the incident and Reflected voltage waves, if the line is terminated in  $Z_R = Z_0$ , the reflection coefficient & reflected waves becomes zero.

$$E = E_R \cdot e^{j\beta s}$$

$$I = I_R \cdot e^{j\beta s}$$

2 marks

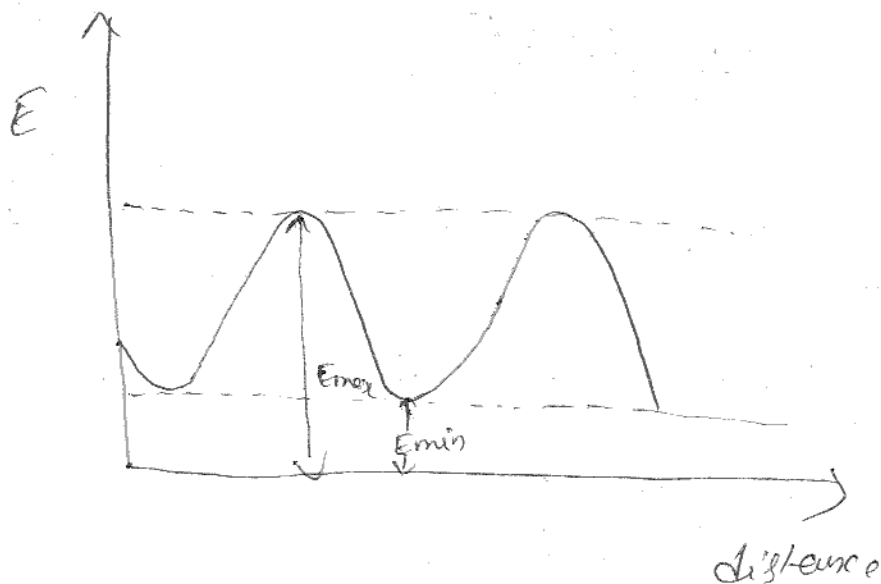
Standing waves :- The total voltage or current wave appears to stand on the line, oscillating in magnitude with time but having fixed position of maxima and minima, such a wave is known as standing waves.



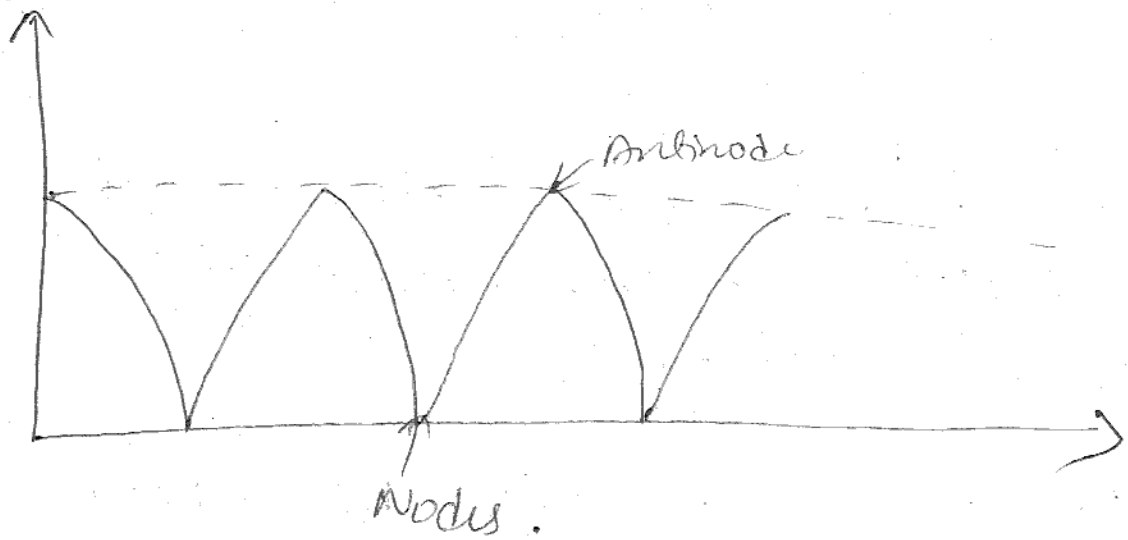
## Nodes and Antinodes; -

The point along the line where the magnitude of voltage or current is zero is called Nodes.

The point along the line where magnitude of voltage or current is maximum are called Antinodes.



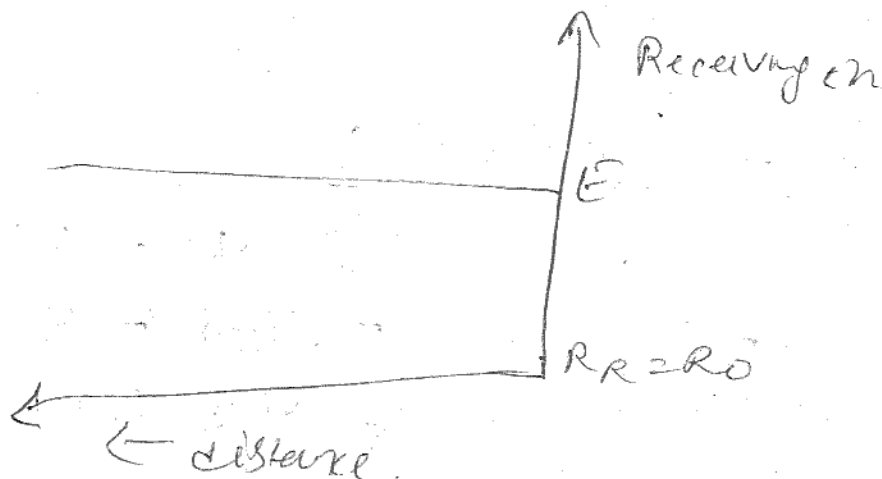Smooth line; - When a line is terminated in  $Z_0$ , the standing waves are absent. Such a line is smooth line.



Standing wave Ratio (SWR) :-

The ratio of the maximum to minimum magnitudes of current or voltage on a line having standing waves is called as Standing wave Ratio. It is denoted by  $S$ .

$$S = \frac{|E_{max}|}{|E_{min}|} \quad \text{or} \quad S = \frac{|I_{max}|}{|I_{min}|}$$

The standing wave Ratio  $S$  is measured by RF voltmeter across the line at a point.

The ratio of  $E_{max}$  to  $E_{min}$  is referred as VSWR.

Similarly the ratio of  $I_{max}$  to  $I_{min}$  is referred as ISWR.

24/8/11

One Eight wave line

For the transmission line the voltage and current at any point distant  $x$  from the receiving end of the transmission line is given by



$$V = \frac{V_R (Z_R + Z_0)}{2Z_R} \left( e^{\gamma x} + k e^{-\gamma x} \right)$$

$$I = \frac{I_R (Z_R + Z_0)}{2Z_0} \left( e^{\gamma x} - k e^{-\gamma x} \right)$$

The term with  $\gamma x$  is defined as the incident wave progressing forward from the source to the load whereas the term involving  $-\gamma x$  is the reflected wave ~~caused~~ travelling from the load back toward towards the source.

For the line of zero dissipation, the attenuation constant  $\alpha = 0$

$$\text{i.e. } \gamma = j\beta, \quad Z_0 = R_0 \text{ (zero dissipation line)}$$

$$V_0 = \frac{V_R (Z_R + R_0)}{2Z_R} \left( e^{j\beta x} + k e^{-j\beta x} \right)$$

Similarly

$$I_0 = \frac{I_R (Z_R + R_0)}{2R_0} \left( e^{j\beta x} - k e^{-j\beta x} \right)$$

and

$$\text{Here } k = \frac{Z_R - R_0}{Z_R + R_0}$$

$$V_o = \frac{V_R (Z_R + R_o)}{2Z_R} \left( e^{j\beta x} + \frac{Z_R R_o}{Z_R + R_o} e^{-j\beta x} \right)$$

$$= \frac{V_R (Z_R + R_o)}{2Z_R} e^{j\beta x} + \frac{V_R (Z_R + R_o)}{2Z_R} \left( \frac{Z_R - R_o}{Z_R + R_o} \right) e^{-j\beta x}$$

$$V_o = \frac{V_R (Z_R + R_o)}{2Z_R} e^{j\beta x} + \frac{V_R (Z_R - R_o)}{2Z_R} e^{-j\beta x}$$

$$= \frac{V_R}{2Z_R} \left[ (Z_R + R_o) e^{j\beta x} + (Z_R - R_o) e^{-j\beta x} \right]$$

$$= \frac{V_R}{2Z_R} \left[ Z_R (e^{j\beta x} + e^{-j\beta x}) + R_o (e^{j\beta x} - e^{-j\beta x}) \right]$$

$$= \frac{V_R}{2Z_R} \left[ Z_R \left( \frac{e^{j\beta x} + e^{-j\beta x}}{2} \right) + R_o j \left( \frac{e^{j\beta x} - e^{-j\beta x}}{2j} \right) \right]$$

$$= \frac{V_R}{Z_R} \left[ Z_R \cos \beta x + j R_o \sin \beta x \right]$$

$$V_o = V_R \cos \beta x + j R_o Z_R \sin \beta x$$

using

$$I_o = I_R \cos \beta x + j \frac{R_o V_R}{R_o} \sin \beta x$$

The i/p impedance of a dissipation line is

$$Z_S = \frac{V}{I}$$

$$Z_S = \frac{V_R \cos \beta x + j R_0 I_R \sin \beta x}{I_R \cos \beta x + j \frac{V_R}{R_0} \sin \beta x}$$

$$Z_S =$$

$$V_R = I_R Z_R$$

$$Z_S = \frac{I_R Z_R \cos \beta x + j R_0 I_R \sin \beta x}{I_R \cos \beta x + j \frac{I_R Z_R}{R_0} \sin \beta x}$$

$$Z_S = \frac{Z_R \cos \beta x + j R_0 \sin \beta x}{\cos \beta x + j \frac{Z_R}{R_0} \sin \beta x}$$

$$= R_0 \left[ \frac{Z_R \cos \beta x + j R_0 \sin \beta x}{R_0 \cos \beta x + j Z_R \sin \beta x} \right]$$

Divide  $\cos \beta x$  in num & deno

$$Z_S = R_0 \left[ \frac{Z_R + j R_0 \tan \beta x}{R_0 + j Z_R \tan \beta x} \right] \quad \text{--- (1)}$$

For an eight wavelength waveguide,  
 $\alpha = \frac{\pi}{8}$ ,  $\beta\alpha = \frac{2\pi}{\lambda} \times \frac{\lambda}{8} = \frac{\pi}{4}$

Put  $\beta\alpha = \frac{\pi}{4}$  in eqn<sup>n</sup> (1)

$$Z_s = R_0 \left[ \frac{Z_R + j R_0 \tan \frac{\pi}{4}}{R_0 + j Z_R \tan \frac{\pi}{4}} \right]$$

$$Z_s = R_0 \left[ \frac{Z_R + j R_0 \cdot 1}{R_0 + j Z_R} \right]$$

If such a line is terminated with  
Pure resistance i.e.  $Z_R = R_R$ .

$$Z_s = R_0 \left[ \frac{R_R + j R_0}{R_0 + j R_R} \right]$$

Thus the magnitude of input impedance

$$|Z_{in}| = R_0 \left[ \frac{\sqrt{R_R^2 + R_0^2}}{\sqrt{R_0^2 + R_R^2}} \right]$$

$$|Z_{in}| = |Z_s| = R_0$$

## Quarter wave line and impedance matching

The i/p impedance of a dissipation transmission line is.

$$Z_S = R_0 \left[ \frac{Z_R + j R_0 \tan \beta x}{R_0 + j Z_R \tan \beta x} \right]$$

divide  $\tan \beta x$  in num & deno

$$Z_S = R_0 \left[ \frac{\frac{Z_R}{\tan \beta x} + j R_0}{\frac{R_0}{\tan \beta x} + j Z_R} \right]$$

$$x = \frac{d}{4}, \quad \beta x = \frac{2\pi}{\lambda} \times \frac{d}{4} = \frac{\pi}{2}$$

Put  $\beta x = \frac{\pi}{2}$  in above eqn

$$Z_S = R_0 \left[ \frac{\frac{Z_R}{\tan \frac{\pi}{2}} + j R_0}{\frac{R_0}{\tan \frac{\pi}{2}} + j Z_R} \right]$$

$$Z_S = R_0 \left[ \frac{j R_0}{j Z_R} \right]$$

$$Z_S = \frac{R_0^2}{Z_R}$$

A quarter wave section of a line may be considered as transformer to match a load of  $Z_R$  to a source i.e.  $Z_S$ . Such a match can be obtained if the characteristic impedance  $R_0'$  of the matching quarter wave section of the line is properly chosen.

$$R_0' = \sqrt{Z_S \cdot Z_R}$$

The  $R_0'$  of the matching section should be equal to geometric mean of source & load impedance.

A quarter wave transformer may also be used, if the load is not a pure resistance. It should then be connected b/w points corresponding to  $I_{max}$  or  $V_{min}$ , at which places the transformation line as resistive impedance given by  $\frac{R_0}{S}$  or  $R_0 \cdot S$ .

→ Thus for step up down in impedance from value of  $R_0$ , the characteristic impedance of the matching section  $R_0'$  can be given by

$$R_0' = \sqrt{R_0 \left( \frac{R_0}{S} \right)}$$

$$R_0' = \frac{R_0}{\sqrt{S}}$$

The step up in impedance from value of  $R_0$  the characteristic impedance of material

$$R_0' = \sqrt{R_0 (R_0 S)}$$

$$R_0' = R_0 \sqrt{S}$$

Half wave line

one i/p impedance of dissipation less wire is given by

$$Z_S = R_0 \left[ \frac{Z_R + j R_0 \tan \beta x}{R_0 + j Z_R \tan \beta x} \right]$$

$$x = \frac{l}{2}, \quad \beta x = \frac{2\pi}{\lambda} \times \frac{l}{2} = \pi$$

$$Z_S = R_0 \left[ \frac{Z_R \mp j R_0 \tan \pi}{R_0} \right] \quad \tan \pi = 0$$

$$Z_S = Z_R$$