

$$Z_{sc} \times Z_{oc} = \frac{14 \Omega}{Z_1 + Y Z_2}$$

~~28/6/11~~

28/6/11

8 Calculate characteristic impedance & propagation constant, if each series impedance is 50Ω ($\frac{Z_1}{2}$) & shunt impedance is 500Ω .

82 Design symmetric T-section, to have $Z_0 = 600 \Omega$ & $Y = 0 + j\frac{\pi}{4}$.

solⁿ

$$Z_2 = \frac{Z_0}{\sinh \beta V} = \frac{600}{\sinh \left(j\frac{\pi}{4} \right)}$$


$\frac{2\pi^2}{4}$

Ideal filter

0 attenuatⁿ in P.B.


∞ " in S.B.

L.P.F

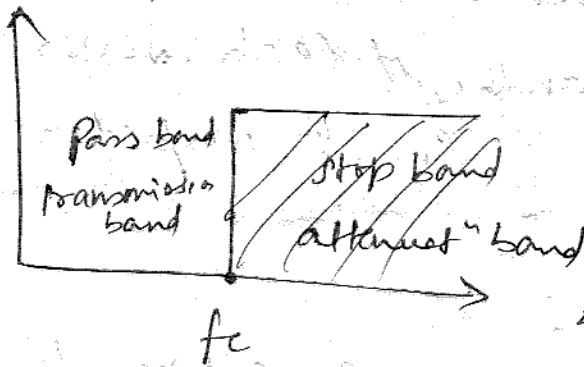


f_c = cutoff freq
 L.P.F passes all freq. greater than cutoff freq.


H.P.F

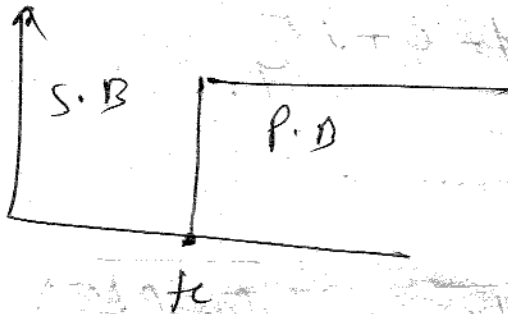

B.P.F

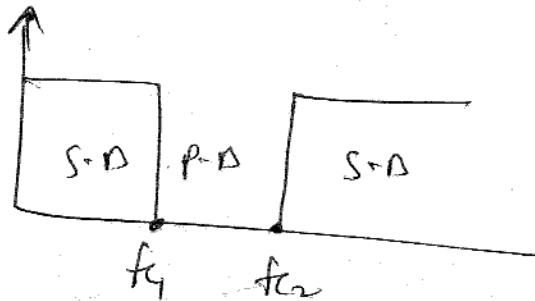

B.S.F

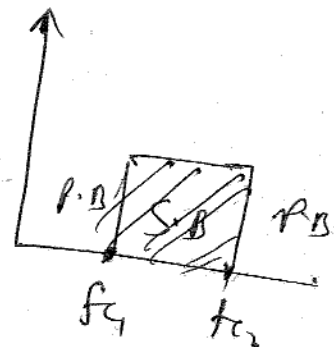

Ideal filter :- An ideal filter ~~to~~ could have zero attenuation in Pass Band & infinite attenuation in stop Band. But practically, in the stop Band attenuation gradually changes.

It cannot change either from zero to infinite ~~and~~ or infinite to zero.

Filter fundamentals - The complete study

of behaviour of any filter section needs the calculation of $Z_0, \gamma, \alpha, \beta$.

→ An important consideration of all filter is that they are constructed from purely reactive element ^(Z_1, Z_2); otherwise the attenuation could never become zero.

→ From the expression of characteristics of T & π net, the Z_0 depends on the reactance i.e. on Z_1 & Z_2 offered by purely reactive elements.

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$


Hence the characteristic impedance Z_0

varies with frequency, as like Z_1 & Z_2 .

Both varies with frequency.

\Rightarrow The theorem connects α & d ,
under the assumptions :- that filter
 is currently terminated in its characteristic
 impedance. The theorem states that
 "over the range of frequency ^{for} which
 the characteristic impedance _{of} filter
 is purely resistive (real). The attenuation
 d is zero.

~~\Rightarrow OV~~

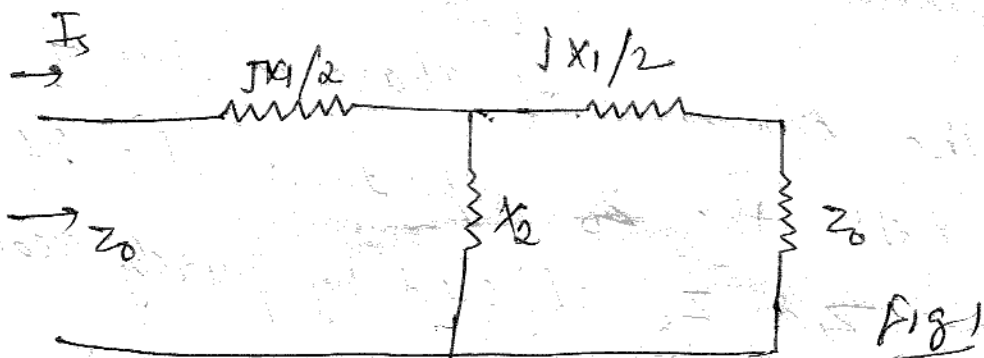

\Rightarrow over the range of frequencies for
 which Z_0 is purely reactive, than the
 attenuation is greater than zero.

\Rightarrow All the elements in the T-section are
 reactive hence all are represented
 in the form of JX , here X is
 a real, but it may be +ve
 or -ve

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$e^{\gamma} = \frac{I_S}{I_R} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2}$$

$$\alpha = 20 \log_{10} \left| \frac{I_S}{I_R} \right| \text{ in dB.}$$

from fig 1

$$Z_1 = jX_1 \quad \& \quad Z_2 = jX_2$$

$$Z_0 = \sqrt{\frac{j^2 X_1^2}{4} + j^2 X_1 X_2}$$

$$= \sqrt{-\frac{X_1^2}{4} - X_1 X_2} = \sqrt{-\left(\frac{X_1^2}{4} + X_1 X_2\right)}$$

$$= \sqrt{\left(\frac{X_1^2}{4} + X_1 X_2\right) j^2}$$

$$Z_0 = j \sqrt{\frac{X_1^2}{4} + X_1 X_2}$$

① Eq:

$$e^{\gamma} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{Z_2}$$

$$= 1 + \frac{jX_1}{2jX_2} + \frac{Z_0}{jX_2}$$

$$= 1 + \frac{x_1}{2x_2} - j \frac{z_0}{x_2}$$

$$e^r = \left[1 + \frac{x_1}{2x_2} \right] - j \left[\frac{z_0}{x_2} \right]$$

⇒ Depending on the sign of x_1 & x_2
we get two cases ..

Case i) when $\frac{x_1^2}{4} + x_1 x_2$ is negative,
then it is '-A'

Case ii) when $\frac{x_1^2}{4} + x_1 x_2$ is +ve, then
it is '+B'.

where A and real and constant values

then for case (i),

$$z_0 = j \sqrt{-A}$$

$$= j \sqrt{A (j^2)}$$

$$= j^2 \sqrt{A}$$

$$\boxed{z_0 = -\sqrt{A}}$$

$$z_0 = \sqrt{\sqrt{-A}}$$

$$= \sqrt{J^2(-A)}$$

$$\frac{x_1^2}{4} + x_1 x_2 = -A$$

$$\boxed{z_0 = \sqrt{A}}$$

$\Rightarrow z_0$ is +ve, it is purely resistive.

9/6/14

then

$$e^r = \frac{I_s}{I_r}$$

$$e^r = \left[1 + \frac{x_1}{2x_2} \right] - J \left[\frac{z_0}{x_2} \right]$$

$$= \left[1 + \frac{x_1}{2x_2} \right] - J \left[\frac{\sqrt{A}}{x_2} \right]$$

$$\text{Attenuation in dB} = 20 \log_{10} \left| \frac{I_s}{I_r} \right|$$

$$d = 20 \log_{10} \left| \left[1 + \frac{x_1}{2x_2} \right] - J \left[\frac{\sqrt{A}}{x_2} \right] \right|$$

$$= 20 \log_{10} \sqrt{\left(1 + \frac{x_1}{2x_2} \right)^2 + \left(\frac{\sqrt{A}}{x_2} \right)^2}$$

$$= 20 \log_{10} \sqrt{\left(1 + \frac{x_1}{2x_2} \right)^2 + \frac{A}{x_2^2}}$$

$$= 20 \log_{10} \sqrt{\left(1 + \frac{x_1}{2x_2} \right)^2 + \frac{1}{x_2^2} \left(-\frac{x_1^2}{4} - x_1 x_2 \right)}$$

$$\underline{\underline{20 \log_{10} \left| \right.}}$$

$$= 2 \log_{10} \sqrt{1 + \frac{x_1}{2x_2} + \frac{x_1}{x_2} - \frac{x_1}{2x_2} - \frac{x_1}{x_2}}$$

$$= 2 \log_{10} \sqrt{1}$$

$$\alpha = 2 \log_{10} \sqrt{1}$$

$$\alpha = 2 \log_{10} 1$$

$$\boxed{\alpha = 0}$$

for case ii)

$$z_0 = j\sqrt{B}$$

$$e^{\gamma} = \left[1 + \frac{x_1}{2x_2} \right] - j \left[\frac{j\sqrt{B}}{x_2} \right]$$

$$e^{\gamma} = 1 + \frac{x_1}{2x_2} + \frac{\sqrt{B}}{x_2}$$

$$\alpha = 2 \log_{10} \left| \frac{I_s}{I_r} \right|$$

$$= 2 \log_{10} \left| 1 + \frac{x_1}{2x_2} + \frac{\sqrt{B}}{x_2} \right| \Rightarrow \alpha > 1$$

\Rightarrow The ratio is real and greater

than 1. Thus α is not zero.

If z_0 is not real, i.e. it is imaginary

$$\alpha = 20 \log_{10} \left| 1 + \frac{X_1}{2X_2} + \frac{\sqrt{\frac{X_1^2}{4} + X_1 X_2}}{X_2} \right|$$

Cutoff frequency :- The frequency ^{at} which separates the pass band and stop band.
 or,
 the frequency at which Z_0 changes from real to imaginary.

The cutoff freq' at which Z_0 changes from being real to being imaginary.

For T-section

$$Z_0 = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

for purely ~~real~~ imaginary.

$$Z_1 = jX_1$$

$$Z_2 = jX_2$$

$$Z_0 = \sqrt{-\frac{X_1^2}{4} - X_1 X_2}$$

$$Z_0 = \sqrt{-X_1 \left[\frac{X_1}{4} + X_2 \right]}$$

The Z_0 is purely imaginary, if

X_1 & $\frac{X_1}{4} + X_2$ have the same sign, this gives the stop band

When Z_0 is purely real

If X_1 & $\left(\frac{X_1 + X_2}{4}\right)$ has opposite sign, and it gives ~~stop~~ ^{pass} band.

Case iii) when $X_1 \left(\frac{X_1 + X_2}{4}\right) = 0$, we get Cut off frequency.

$$\boxed{X_1 = -4X_2} \leftarrow \text{Cond}^n \text{ of Cut off frequency}$$

Pass Band & stop Band

for P.B

$$\boxed{\gamma = \alpha + j\beta}$$

$\gamma =$ propagation constant
 $\alpha =$ attenuation

The ability of a TL to work as filter is decided by propagation constant γ .

When $\alpha = 0$, the O/P current = I/P current
 $E = E_0$

indicating no attenuation in the o/p but only the phase shift in o/p.

$$\therefore \alpha = 0$$

$$\boxed{\gamma = j\beta}$$

The magnitude of o/p current becomes very less than the i/p current indicating the attenuation in the o/p current.

we know that:-

$$\sin \frac{hV}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\sin h \left(\frac{\alpha + j\beta}{2} \right) = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\sinh \left[\frac{\alpha}{2} + j \frac{\beta}{2} \right] = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\sin h \frac{\alpha}{2} \cos h \left(\frac{j\beta}{2} \right) + \cos h \frac{\alpha}{2} \sin h \left(\frac{j\beta}{2} \right) = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\sinh \frac{\alpha}{2} \cos \frac{\beta}{2} + \cos h \frac{\alpha}{2} j \sin \frac{\beta}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

Condition

If Z_1 and Z_2 are reactances of opposite

then

$$\sinh \left(\frac{\alpha}{2} \right) \cos \frac{\beta}{2} = 0 \quad \text{--- (1) eq.}$$

$$\cosh \left(\frac{\alpha}{2} \right) \sin \frac{\beta}{2} = \sqrt{\frac{Z_1}{4Z_2}} \quad \text{--- (2) eq.}$$

form ①

$$\sinh\left(\frac{\alpha}{2}\right) = 0$$

$$\Rightarrow \boxed{\alpha = 0}$$

form eqn ②

$$\cosh\left(\frac{\alpha}{2}\right) \sin\frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}} \quad \text{--- ①}$$

$$\Rightarrow \sin\frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}}$$

$$\Rightarrow \boxed{\beta \neq 0} \quad \text{i.e. } \beta = (2n-1)\pi$$

~~$\cosh\frac{\alpha}{2}$~~

$$\cosh\frac{\alpha}{2} = \sqrt{\frac{z_1}{4z_2}} \quad \text{--- ②'}$$

$$\boxed{\beta = 2 \sin^{-1} \sqrt{\frac{z_1}{4z_2}}} \quad \text{form ①'}$$

form ②'

$$\boxed{\alpha = 2 \cosh^{-1} \sqrt{\frac{z_1}{4z_2}}} \quad \text{--- ②'}$$

Constant K Section Filter :-

A - T or π -Section in which series & shunt amp impedance Z_1 & Z_2 satisfy the relationship $Z_1 \cdot Z_2 = R_o^2$, then it is a constant K section.

Where,

$R_o \rightarrow$ Real Constant, also called as design impedance.

$$Z_{o\pi} = \frac{Z_1 Z_2}{Z_{oT}} \quad \leftarrow \text{Characteristic impedance for } \pi \text{ sect}^n$$

for Constant T-section


$$Z_{oT} = \frac{R_o^2}{Z_{o\pi}}$$

Constant T or π sectⁿ filter is also called as prototype section filters.

The Constant
PROTOTYPE FILTERS


LOW PASS FILTER :-

LOW PASS FILTER

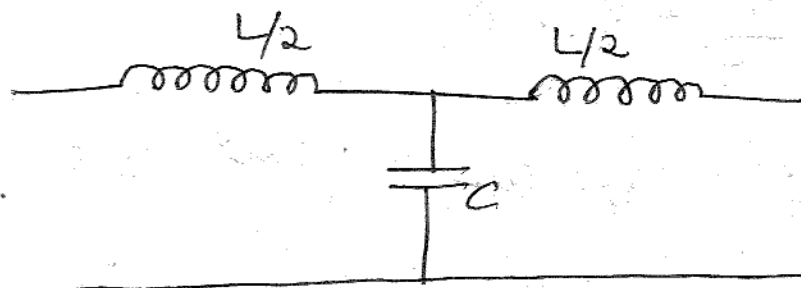

↑ Constant k section

Constant k-section

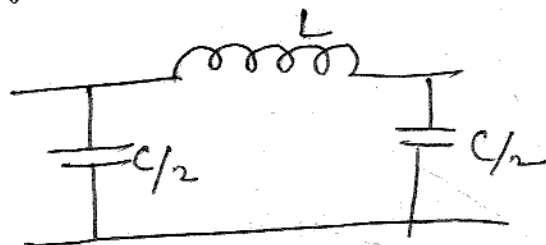

Design section :-

$$Z_1 = j\omega L$$

$$Z_2 = \frac{-j}{\omega C}$$

$$R_0^2 = Z_1 Z_2$$

$$R_0^2 = \frac{\omega L}{\omega C}$$

$$\Rightarrow R_0 = \sqrt{\frac{\omega L}{\omega C}} = \sqrt{\frac{L}{C}}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

Z_1 = Total series amp resistance

Z_2 = Total shunt amp res.


Reactance Curves & Cut off frequency Expr

$$\therefore \frac{X_1}{4} + X_2 = 0$$

for also $X_1 = \omega L$ and $X_2 = -\frac{1}{\omega C}$

C $\Rightarrow \frac{X_1}{4} + X_2 = \frac{\omega L}{4} - \frac{1}{\omega C} = 0$ $\text{---} \textcircled{D}$

For LPF, reactance curve is given by

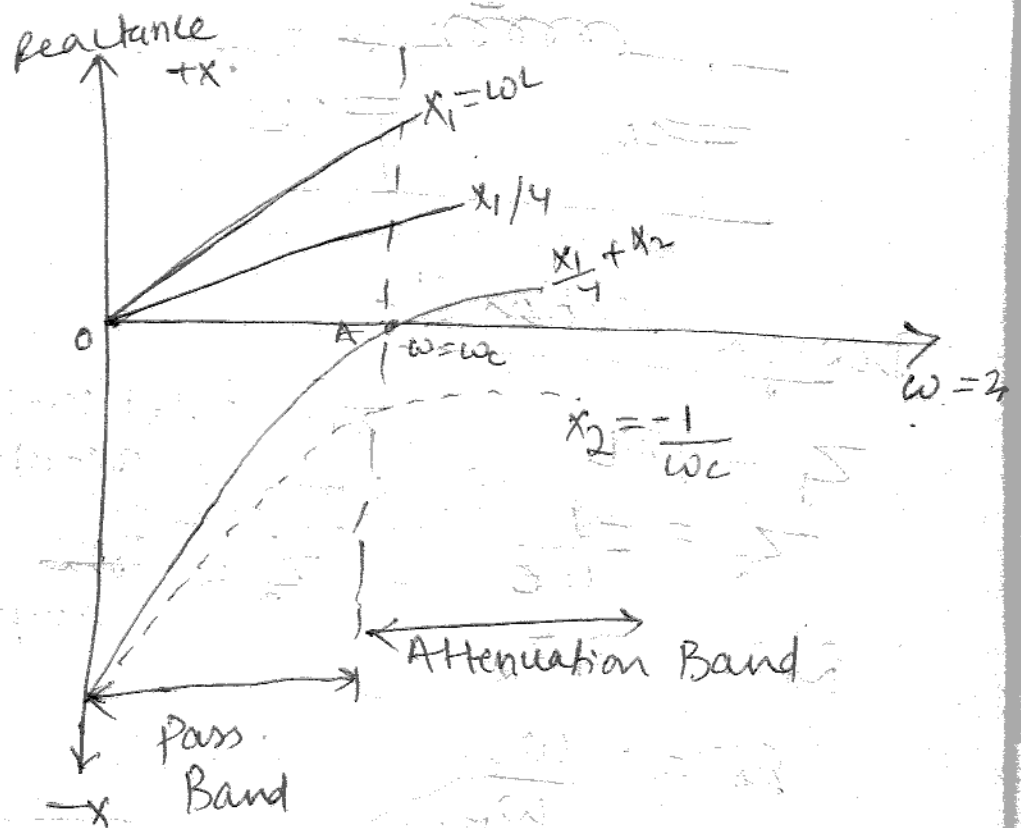

Hence all the frequencies upto point A gives Pass Band, above point A gives stop band. Thus the point A is the cut off frequency given by $\omega = \omega_c$.

frequency Exp

from (b),
at point, $\omega = \omega_c$

Eqⁿ (b) becomes,

$$\frac{\omega_c L}{4} - \frac{1}{\omega_c C} = 0$$

$$\Rightarrow \frac{\omega_c L}{4} = \frac{1}{\omega_c C}$$

$$\Rightarrow \omega_c^2 LC = 4$$

$$\Rightarrow \omega_c^2 = \frac{4}{LC}$$

$$\Rightarrow \omega_c = \frac{2}{\sqrt{LC}}$$

$$\Rightarrow 2\pi f_c = \frac{2}{\sqrt{LC}}$$

$$\Rightarrow f_c = \frac{1}{\pi \sqrt{LC}}$$

By Algebraically -

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$= \sqrt{\frac{-\omega^2 L^2}{4} + \frac{L}{C}}$$

$$= \sqrt{\frac{L}{C}} \cdot \sqrt{1 - \frac{\omega^2 LC}{4}}$$

$$Z_{OT} = R_0 \sqrt{1 - \frac{\omega^2 LC}{4}}$$

A gives
stop band

frequency

From the above expression Z_{OT} is real

When $\frac{\omega^2 L_c}{4} < 1$ and Z_{OT} is Imj when

$$\frac{\omega^2 L_c}{4} > 1.$$

So at cut off frequency,

$$\frac{\omega^2 L_c}{4} - 1 = 0$$

$$\Rightarrow \frac{\omega^2 L_c}{4} = 1$$

$$\Rightarrow \omega^2 = \frac{4}{L_c}$$

$$\omega = \sqrt{\frac{4}{L_c}} = \frac{2}{\sqrt{L_c}}$$

$$\boxed{\omega_c = \frac{2}{\sqrt{L_c}}}$$

Thus above prototype section passes all frequencies of $\frac{2}{\sqrt{L_c}}$, while attenuates all frequency above cut off frequency.

Variation of Z_{OT} and Z_{OX} with

frequency :-

$$Z_{OT} = R_0 \sqrt{1 - \frac{\omega^2}{\omega_c^2}}$$

is real
img when

$$Z_{OT} = R_0 \sqrt{1 - \frac{f^2}{f_c^2}}$$

$$Z_{OK} = \frac{Z_1 Z_2}{Z_{OT}}$$

$$Z_{OK} = \frac{R_0^2}{R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$


passes all
attenuate
frequency

th

the frequency increases from zero to f_c .
It decreases R_o to zero in pass band.

~ Passband as frequency \uparrow from zero to f_c ,
 $Z_{oK} \uparrow$ from R_1 to ∞ .

Characteristic Curve :-

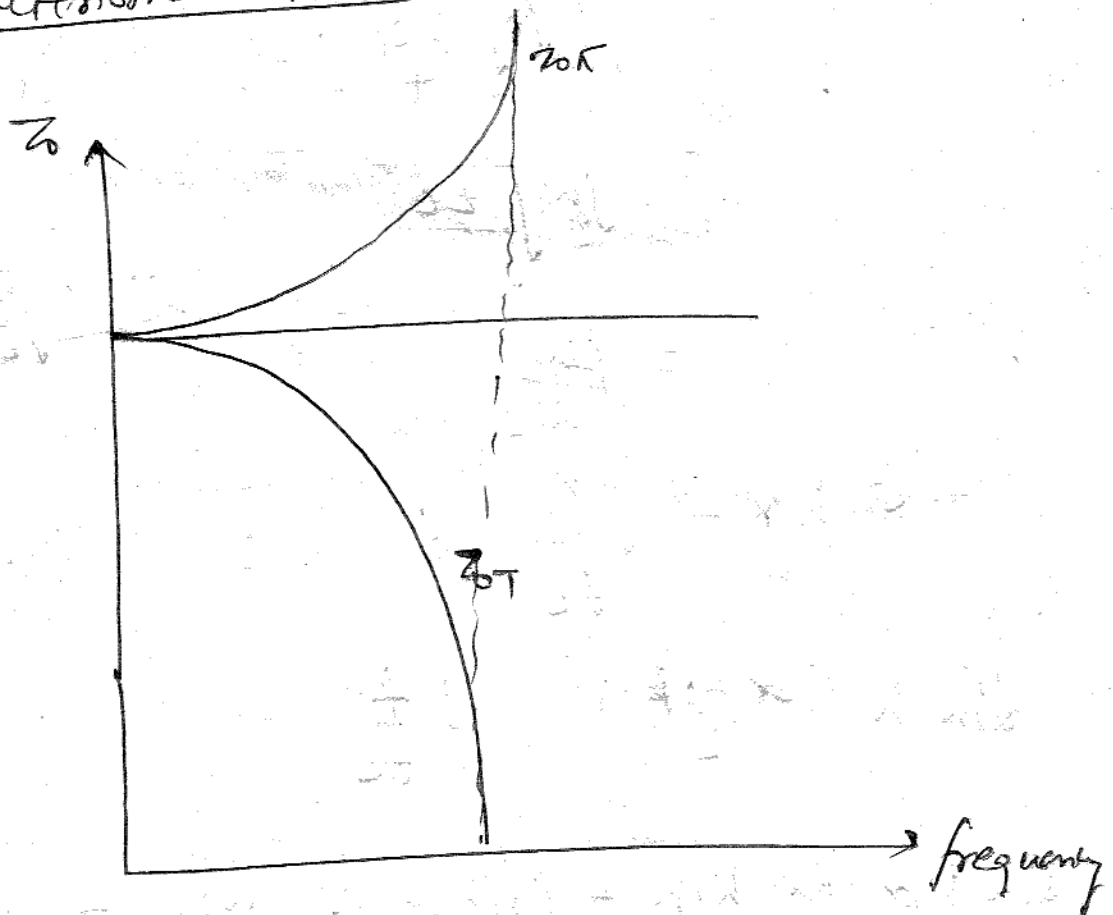

Variation of attenuation Constant α with frequency :-

$$\text{we have } \sinh \frac{\alpha}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$$Z_1 = j\omega L, \quad Z_2 = \frac{-j}{\omega C}$$

$$\sinh \frac{\gamma}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$$= \sqrt{\frac{j\omega L}{4\left(\frac{-j}{\omega C}\right)}}$$

$$= \sqrt{j\omega L \times \frac{\omega C}{-4j}}$$

$$= j\omega \sqrt{\frac{LC}{4}}$$

$$= j\omega \sqrt{\frac{LC}{4}}$$

$$= \frac{j\omega}{\omega C}$$

$$\because \omega C = \frac{2}{\sqrt{LC}}$$

$$\sinh \frac{\gamma}{2} = \frac{j f}{f_c}$$

$$\sinh \left(\frac{\alpha + j\beta}{2} \right) = \frac{j f}{f_c}$$

$$\sinh \frac{\alpha}{2} \cosh \frac{j\beta}{2} + \cosh \frac{\alpha}{2} \sinh \frac{j\beta}{2} = j \left(\frac{f}{f_c} \right)$$

$$\Rightarrow \sinh \frac{\alpha}{2} \cosh \frac{j\beta}{2} + j \cosh \frac{\alpha}{2} \sinh \frac{\beta}{2} = j \left(\frac{f}{f_c} \right)$$

①

For Ideal filter $\alpha = 0$, $\beta = \pi$

$$\cosh \frac{\alpha}{2} = 0, \quad \sinh \frac{\alpha}{2} = 1.$$

So eqⁿ becomes,


~~$$\cosh \frac{\alpha}{2} = 1 - j \left(\frac{f}{f_c} \right)$$~~

$$j \cosh \frac{\alpha}{2} = j \left(\frac{f}{f_c} \right)$$

$$\Rightarrow \boxed{\alpha = 2 \cosh^{-1} \left(\frac{f}{f_c} \right)}$$

In stop band, as the frequency increases above f_c , the attenuation α also \uparrow .

Plot betⁿ attenuation α & frequency f ,

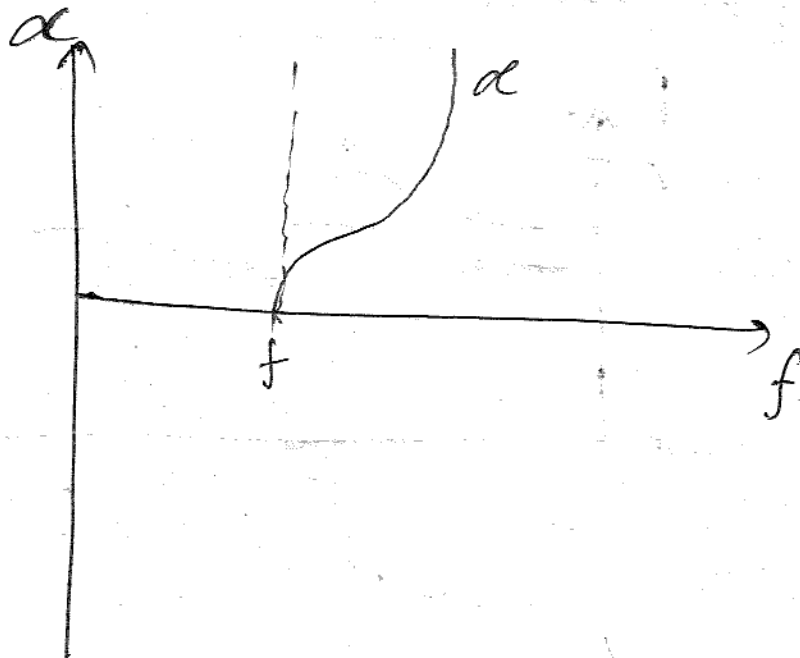

Variation of Phase Constant β with frequency :-

$$\text{Put } \alpha = 0, \beta = \pi \text{ in (1)}$$

$$\text{we get } \boxed{j \sinh \frac{\alpha}{2} = j \frac{f}{f_c}}$$


Now, in stop band, phase constant $\beta = \pi$

and $\alpha =$

$$\text{we get } j \sinh \frac{\beta}{2} = j \frac{f}{f_c}$$

$$\Rightarrow \boxed{\beta = 2 \sinh^{-1} \frac{f}{f_c}}$$

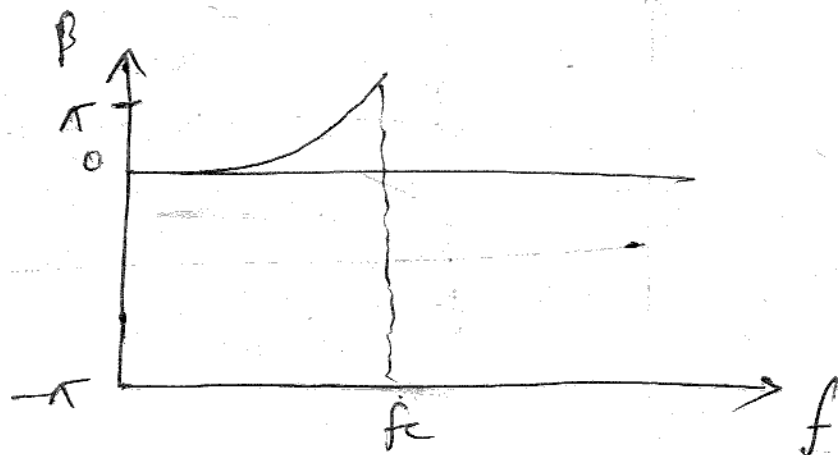As frequency increases from zero to f_c , β also \uparrow from 0 to π values.



Design Eq for Prototype low pass filter :-

$$R_0 = \sqrt{\frac{L}{C}}$$

$$f_c = \frac{1}{\pi \sqrt{LC}}$$

$$\frac{R_0}{f_c} = \sqrt{\frac{L}{C}} \div \frac{1}{\pi \sqrt{LC}}$$

$$= \sqrt{\frac{L}{C}} \times \pi \sqrt{LC}$$

$$= \frac{\sqrt{L} \times \pi \sqrt{L} \sqrt{C}}{\sqrt{C}}$$

$$\frac{R_0}{f_c} \times \pi = L \pi$$

$$L = \frac{R_0}{\pi f_c}$$

Design a prototype LFF if design
imp $R_0 = 500 \Omega$, & $f_c = 2000 \text{ Hz}$.

$$L = 79.57$$

$$L = \frac{R_0}{\pi f_c} = \frac{500 \Omega}{3.14 \times 2000} = 79.57$$

$$f_c = \frac{1}{\pi \sqrt{LC}}$$

$$\Rightarrow 2000 = \frac{1}{\pi \sqrt{79.57 C}}$$

$$\Rightarrow (2000)^2 = \frac{1}{\pi^2 (79.57 C)}$$

$$\Rightarrow C = \frac{1}{\pi^2 (79.57) \times (20000)^2}$$

$$R_{ofc} = \sqrt{\frac{L}{C}} = \frac{1}{\pi \sqrt{LC}}$$

$$= \frac{1}{\pi C}$$

\Rightarrow

$$C = \frac{1}{\pi R_{ofc}}$$


$$= \frac{1}{3.14 \times 500 \times 2000}$$

$$= 0.3184 \times 10^{-6}$$


$$= 3.1 \mu\text{f}$$

$$= 0.31 \mu\text{f}$$


Final $C = 0.31 \mu\text{f}$

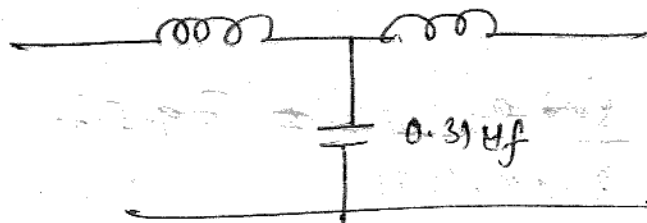

Prototype π -secⁿ

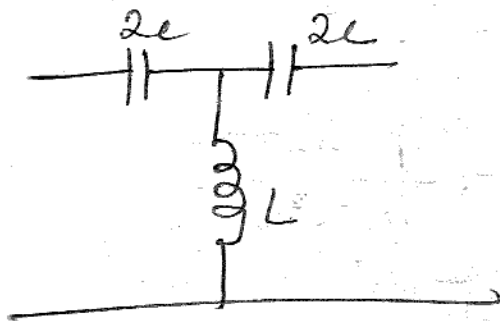

T-sectionⁿ

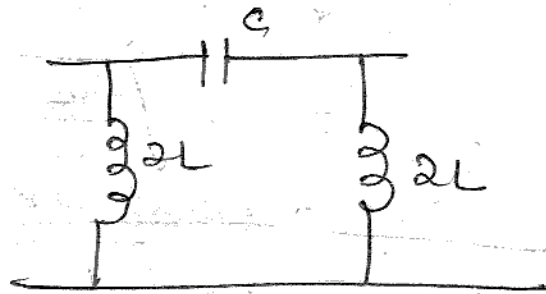

find R_0

$\therefore Z_1 = \frac{1}{\omega c}$ $Z_2 = j\omega L$

$Z_1 Z_2 = R_0^2$

$\Rightarrow \frac{L}{C} = R_0^2$

$\Rightarrow R_0 = \sqrt{\frac{L}{C}}$

Total series amp resistance
Total shunt amp resistance

for cut off freq :

$X_1 = \frac{1}{\omega c}$
 $X_2 = \omega L$

$\frac{X_1}{4} + X_2 = 0$

$\Rightarrow \frac{-1}{\omega c} + \omega L = 0$

$\Rightarrow \omega L = \frac{1}{\omega c}$

$\omega^2 = \frac{1}{LC}$

$\omega = \frac{1}{\sqrt{LC}}$

$X_1 + 4X_2 = 0$

$\Rightarrow \frac{-1}{\omega c} + 4\omega L = 0$

$4\omega L = \frac{1}{\omega c}$

$\Rightarrow \omega^2 = \frac{1}{4LC}$

$\Rightarrow \omega = \frac{1}{2\sqrt{LC}}$

$\Rightarrow \omega c L - \frac{1}{4\omega c} = 0$

$\Rightarrow \omega c L = \frac{1}{4\omega c}$

$\Rightarrow \omega^2 = \frac{1}{4LC}$

$\Rightarrow \omega_c = \frac{1}{2\sqrt{LC}}$

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}, \quad R_0 = \sqrt{\frac{L}{C}}$$

$$= \sqrt{\frac{-1}{4\omega^2 LC} + \frac{L}{C}}$$

$$= \sqrt{\frac{L}{C}} \sqrt{1 - \frac{1}{4\omega^2 LC}}$$

$$\boxed{Z_{OT} = R_0 \sqrt{1 - \frac{1}{4\omega^2 LC}}}$$

$\Rightarrow Z_{OT}$ is real $\frac{1}{4\omega^2 LC} < 1$

$\Rightarrow Z_{OT}$ is imag when $\frac{1}{4\omega^2 LC} > 1$.

at cutoff frequ

$$1 - \frac{1}{4\omega^2 LC} = 0$$

$$\Rightarrow 1 = \frac{1}{4\omega^2 LC}$$

$$\Rightarrow \omega^2 = \frac{1}{4LC}$$

$$\Rightarrow \boxed{\omega = \frac{1}{2\sqrt{LC}}}$$

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

2/7/11

(Major drawbacks) :-

Disadvantage of Prototype Section :-

(1) The attenuation should ideally, attenuate sharply in the attenuation band, but in all the prototype filter section changes gradually. ~~in the~~ in the attenuation band.

Hence the frequency near cut off frequency are passed through the filter.

(2) Ideally in the pass band, the o/p of filter ^{should remain,} is constant. i.e Z_0 is constant.

This indicates that the characteristic impedance should remain constant. but it is observed that characteristic impedances varies with the frequency. from value R_0 , through the passband.

~~M-ARRAY~~


M-Derived filter section :-

If two sections ^{of} same type are cascaded the attenuation in the attenuation band gets double and giving much sharper cut-off characteristics.


Derivation of M-derived section :-

It is necessary to design a new section filter having same cut off frequency, but different attenuation characteristic. So both the section (Constant & M-derived) must have same characteristic impedance.

General T-section

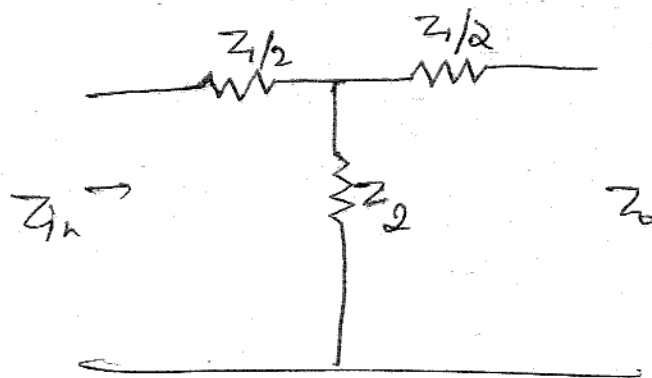

For M-derived section:-

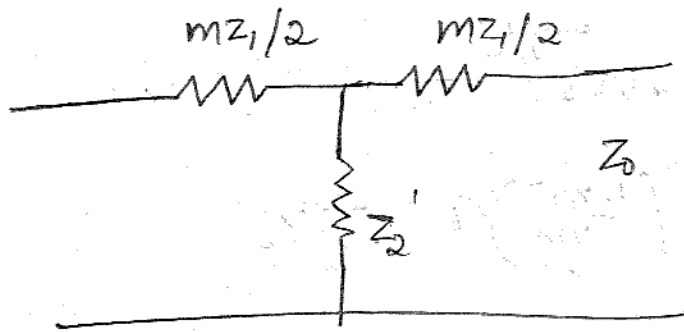

$$\frac{Z_1}{2} = \frac{mZ_1}{2} \quad \& \quad \frac{Z_1}{2} = mZ_2 \quad Z_2 = Z_2'$$

For prototype sectⁿ

$$Z_{0T} = \sqrt{\frac{Z_1^2 + 4Z_1Z_2}{4}} \quad \text{--- (1)}$$

$$Z_{0T} = \sqrt{\frac{mZ_1^2 + \frac{mZ_1Z_2'}{2}}{4}} \quad \text{--- (2)}$$

$$\text{(1) = (2)}$$

$$\Rightarrow \sqrt{\frac{Z_1^2 + 4Z_1Z_2}{4}} = \sqrt{\frac{mZ_1^2 + mZ_1Z_2'}{4}}$$


$$\Rightarrow \frac{Z_1^2 + 4Z_1Z_2}{4} = \frac{mZ_1^2 + mZ_1Z_2'}{4}$$

$$\Rightarrow \frac{Z_1^2}{4} - \frac{mZ_1^2}{4} = mZ_1Z_2' - 4Z_1Z_2$$



$$\Rightarrow \frac{Z_1^2}{4} (1-m) = mZ_1Z_2'$$

$$\Rightarrow \frac{Z_1^2}{4} + 4Z_1Z_2 - \frac{mZ_1^2}{4} = mZ_1Z_2'$$
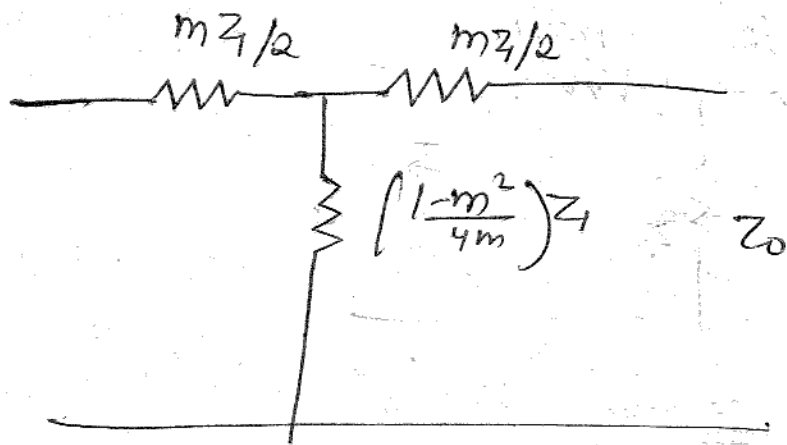
$$\Rightarrow Z_2' = \frac{Z_1}{4m} + \frac{Z_2}{m} - \frac{Z_1}{4} = \left(\frac{1-m}{4m}\right)Z_1 + \frac{Z_2}{m}$$



For Constant k-section :-

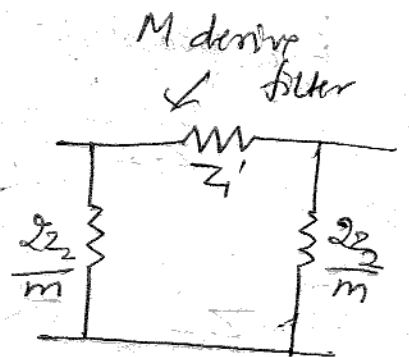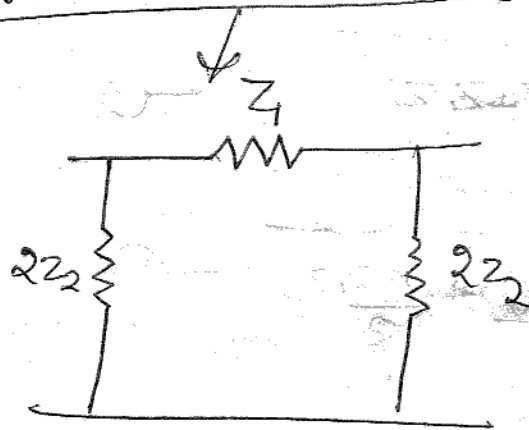

$$Z_{OT} = \frac{Z_1 Z_2}{\sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}} \quad \text{--- (1)}$$

$$Z_{OT} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}}$$

$$= \sqrt{\frac{Z_1' \left(\frac{Z_2}{m}\right)}{1 + \frac{Z_1}{4 \left(\frac{Z_2}{m}\right)}}} = \sqrt{\frac{\frac{Z_1' Z_2}{m}}{1 + \frac{m Z_1}{4 Z_2}}}$$

--- (2)

$$\textcircled{1} = \textcircled{2}$$

$$\frac{Z_1 Z_2}{\sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}} = \sqrt{\frac{\frac{Z_1' Z_2}{m}}{1 + \frac{m Z_1'}{4 Z_2}}}$$

$$\Rightarrow \frac{(Z_1 Z_2)^2}{\frac{Z_1^2}{4} + Z_1 Z_2} = \frac{\frac{Z_1' Z_2}{m}}{1 + \frac{m Z_1'}{4 Z_2}}$$

$$\Rightarrow \frac{(Z_1 Z_2)^2}{\frac{Z_1^2}{4} + Z_1 Z_2}$$


$$\Rightarrow \frac{Z_1 Z_2}{\frac{Z_1^2}{4} + Z_1 Z_2} = \frac{\frac{Z_1' Z_2}{m}}{1 + \frac{m Z_1'}{4 Z_2}}$$

$$\Rightarrow Z_1 Z_2 \left(1 + \frac{m Z_1'}{4 Z_2}\right) = \frac{Z_1' Z_2}{m}$$

$$Z_1' \left[\frac{Z_2}{m} + \frac{Z_1 (1-m^2)}{4m} \right] = Z_1 Z_2$$

$$Z_1' = \frac{Z_1 Z_2}{\frac{Z_2}{m} + \left(\frac{1-m^2}{4m}\right) Z_1}$$
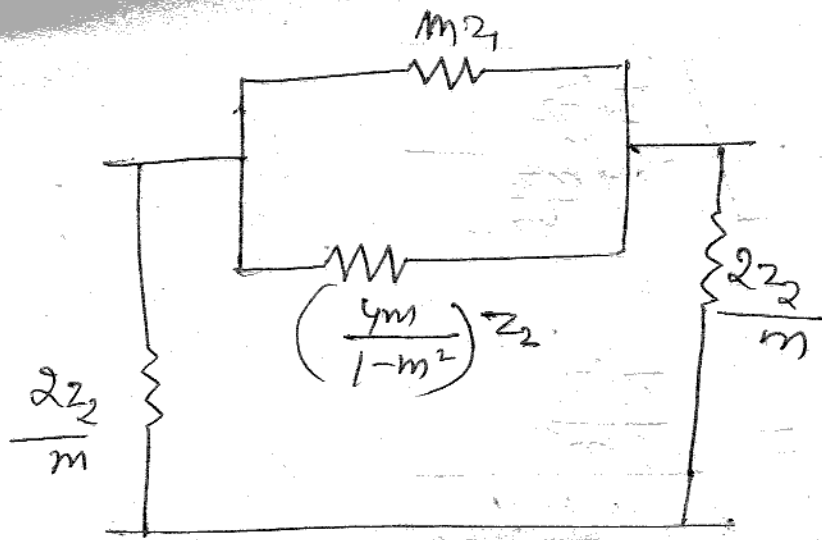
$$Z_1' = \frac{(m Z_1) \left(\frac{4m}{1-m^2}\right) Z_2}{\left(\frac{4m}{1-m^2}\right) Z_2 + m Z_1}$$



13/7/14:-

M-Derived Low Pass Filter Section

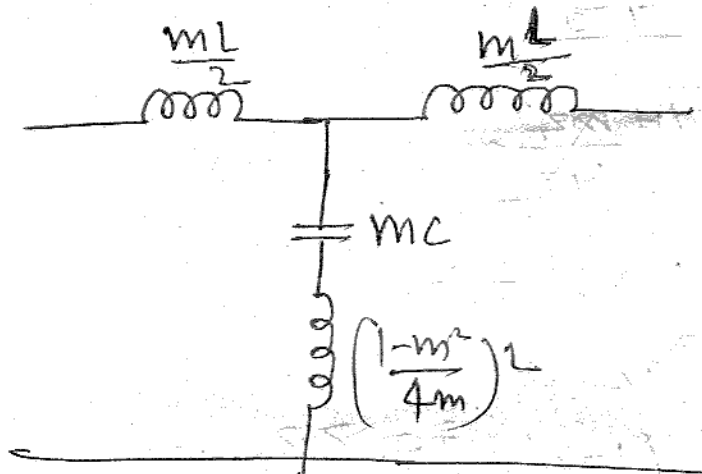


Fig (a)

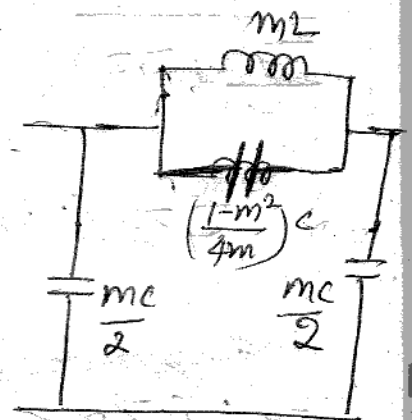


Fig (b)

$$f_{\infty} = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{\left(\frac{1-m^2}{4m}\right)L mc}}$$

$$= \frac{1}{2\pi\sqrt{\frac{(L-m^2L)c}{4}}}$$

$$= \frac{1}{2\pi \sqrt{\frac{LC - m^2 LC}{4}}}$$

$$= \frac{1}{2\pi \sqrt{\frac{LC(1-m^2)}{4}}}$$

$$= \frac{1}{\pi \sqrt{LC(1-m^2)}}$$

$$f_c = \frac{1}{\pi \sqrt{LC}}$$


$$f_\infty = \frac{f_c}{\sqrt{1-m^2}}$$

$$f_\infty = \frac{f_c}{\sqrt{1-m^2}} = \frac{1}{\pi \sqrt{LC}} \Rightarrow = \frac{1}{\pi \sqrt{LC}} \frac{\sqrt{1-m^2}}{f_c} = \frac{f_c}{\sqrt{1-m^2}}$$

$$\Rightarrow 1-m^2 = \left(\frac{f_c}{f_\infty}\right)^2$$

$$m = \sqrt{1 - \left(\frac{f_c}{f_\infty}\right)^2}$$

TS ON

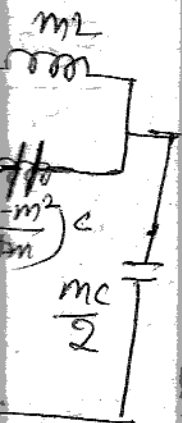

Design m -derived T-type LPF to work into the load of $500\ \Omega$, & cut off frequency of 4000 kHz & peak attenuation is 4.5 dB .

$$L = \frac{R_0}{\pi f_c} \text{ for posttype}$$

solⁿ 1. $f_c = 4000\text{ kHz}$

$$R_0 = 500\ \Omega$$

$$f_\infty = 4.5$$

$$C = \frac{1}{\pi f_c R_0}$$

$$L = \frac{500}{3.14 \times 4 \times 10^3} = \frac{5}{12.56 \times 10^3} = 0.039 = 39.8\ \text{mH}$$

$$C_c = \frac{1}{\pi f_c R_o} = \frac{1}{2\pi \times 4 \times 10^3 \times 500}$$


$$= 0.159 \mu\text{F}$$

$$M = \sqrt{1 - \left(\frac{f_c}{f_o}\right)^2}$$


$$= \sqrt{1 - (4 \times 10^3)^2}$$

$$= \sqrt{1 - \left(\frac{4}{4.5}\right)^2}$$
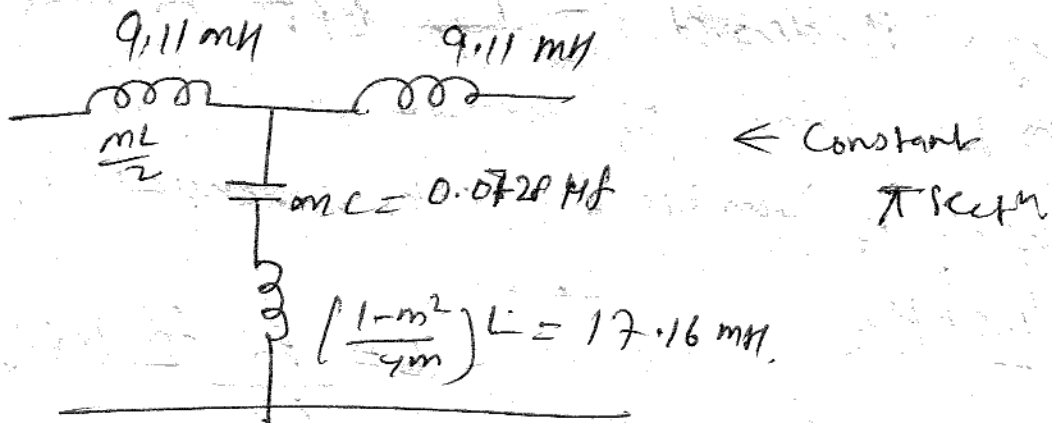
$$= \sqrt{1 - \frac{16}{(4.5)^2}} = 0.458$$



Constant T-section

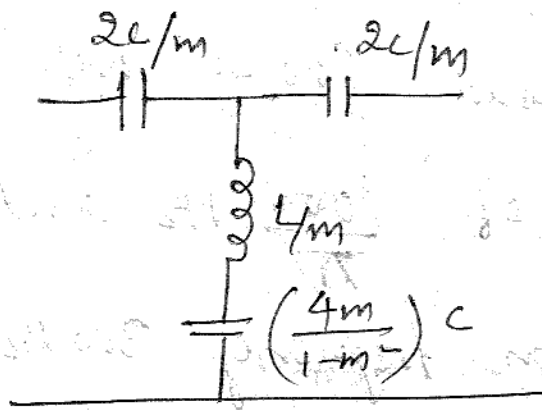

$$f_c = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{\frac{L}{m} \times \frac{4mC}{1-m^2}}}$$

$$= \frac{1}{2\pi\sqrt{\frac{4LC}{1-m^2}}}$$

$$= \frac{1}{4\pi\sqrt{\frac{LC}{1-m^2}}}$$

$$f_{\infty} = \frac{\sqrt{1-m^2}}{4\pi\sqrt{LC}}$$

$$f_{\infty} = f_c \sqrt{1-m^2} \Rightarrow \frac{f_{\infty}}{f_c} = \sqrt{1-m^2}$$

$$\Rightarrow \left(\frac{f_{\infty}}{f_c}\right)^2 = 1-m^2$$

$$m = \sqrt{1 - \left(\frac{f_{\infty}}{f_c}\right)^2}$$



Q2 Design M-derived HPF π section to
 work into the load 600Ω , with
 Cut off frequency of $\frac{1000}{\pi}$ Hz and
 Peak attenuation frequency 300 Hz.

Solⁿ

$$R_0 = 600 \Omega,$$

$$f_c = \frac{1000}{\pi}$$

$$f_\infty = 300 \text{ kHz}$$

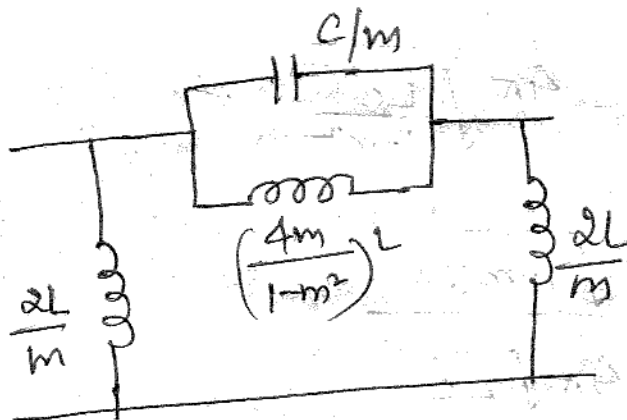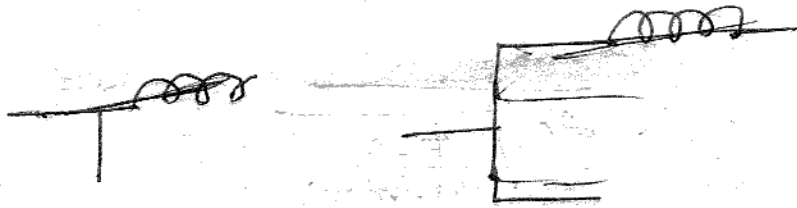

Constant π section

$$L = \frac{R_0}{4\pi f_c} = \frac{600}{4\pi \times 1000}$$

$$= \frac{600}{4000} = \frac{6}{40} = \frac{3}{20} = 0.15$$

$$C = \frac{1}{\pi f_c R_0}$$

$$= \frac{1}{4 \times 10^6 \times \frac{1000}{\pi} \times 600} = \frac{1 \times 10^{-5}}{4 \times 6} = 4.16 \times 10^{-7}$$

$$m = \sqrt{1 - \left(\frac{f_{\omega}}{f_c}\right)^2}$$

$$= \sqrt{1 - \left(\frac{300}{\frac{1000}{\pi}}\right)^2} = 0.335$$

$$m = 0.335$$

$$\frac{C}{m} = \frac{4.16 \times 10^{-7}}{0.335} = 1.24$$

$$\frac{2L}{m} = \frac{2 \times 0.15}{0.335} = \frac{0.30}{0.335} = \frac{2 \times 0.15}{0.335} = 0.8939 = 893.9 \text{ mH}$$
$$= \frac{2 \times 150}{0.335} =$$

$$\left(\frac{4m}{1-m^2}\right) L = \frac{4 \times 0.335 \times 150}{1 - (0.335)^2} = 225.6 \text{ mH}$$

3
20
0.15

19/7/11

UNIT 2

Relationship between Primary & Secondary

Constants:

Primary Constant	Unit
R - Resistance	(Ω)
G - Conductance	(mho) or σ
L - Inductance	(Henry)
C - Capacitance	(Farad)

\Rightarrow Primary Constants are independent of frequency.


secondary
Constant

Z_0	- o/p impedance
γ	-
α	- attenuation constant
β	-

\Rightarrow Secondary constants are dependent on frequency.


Consider a short length of line l (mbs),
this section will have resistance R ,
conductance G , inductance L , & capacitance

C

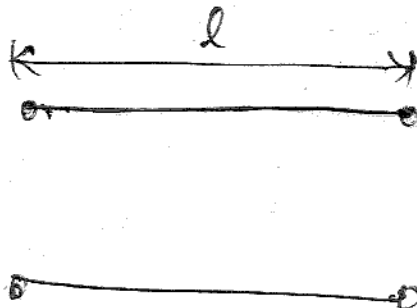

Symmetric
T-NWT.

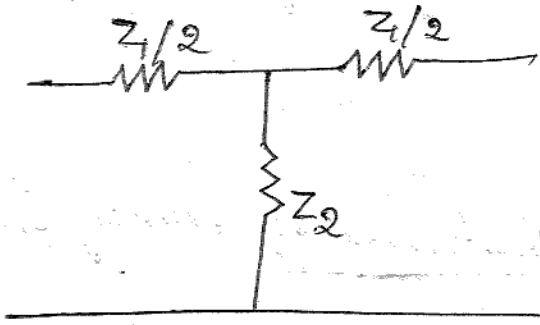Also it has Characteristic Impedance Z_0 .




T-Node'

If the length of the line is very small, than series amp resistance is represented as

$$Z_1 = (R_1 + j\omega L) l$$

$$Z_2 = \frac{1}{(G_1 + j\omega C) l}$$

T-section can be represented as:-

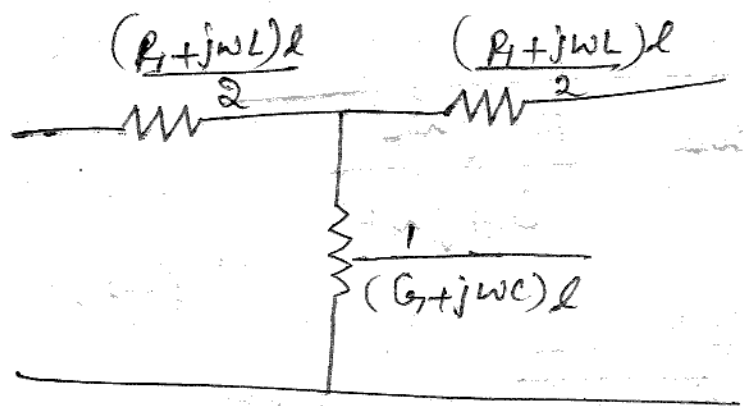

Determine The total series amp impedance per unit length is denoted as $Z_0 'Z'$

$$Z = R + j\omega L$$

||y The total parallel impedance per unit length is denoted as

$$Y = Z_{shunt} = \frac{1}{Z_0} = G + j\omega C$$

This assumption is valid only when the length of line is very very small.

$$\text{i.e. } l \rightarrow 0$$

Determination of Z_0 in terms of Primary Constants

$$Z_{0T} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

$$= \sqrt{\frac{[(R+j\omega L)l]^2}{4} + \frac{[(R+j\omega L)l] \{ (G+j\omega C)l \}}{(G+j\omega C)l}}$$

$$= \sqrt{\frac{(R+j\omega L)^2 l^2}{4} + \frac{R+j\omega L}{G+j\omega C}}$$

$$= \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

$$\therefore l \rightarrow 0$$

$$Z_0 = \sqrt{\frac{Z}{Y}}$$

where
 $Z = R+j\omega L$

$$Y = \frac{1}{G+j\omega C}$$

Determination of γ in terms of Primary

Constant :-

$$e^{\gamma l} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{2Z_2}$$

$$= 1 + \frac{(R + j\omega L)l}{(G + j\omega C)l} + \frac{Z_0}{(G + j\omega C)l}$$

$$= 1 + \frac{(R + j\omega L)l \times (G + j\omega C)l}{2} + \frac{Z_0(G + j\omega C)l}{2}$$

$$= \frac{1 + (R + j\omega L)(G + j\omega C)l^2 + Z_0(G + j\omega C)l}{2}$$