
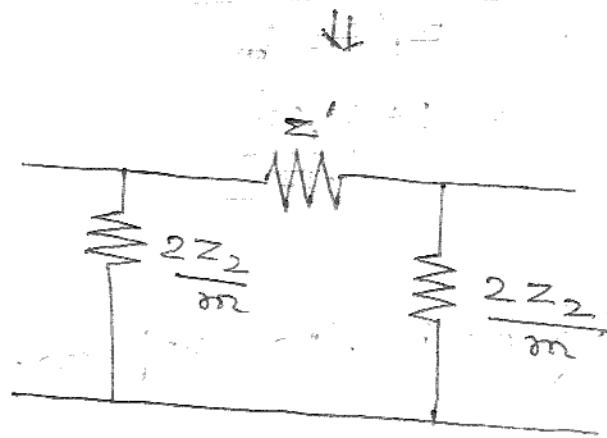


13.7.11

M derived π -section

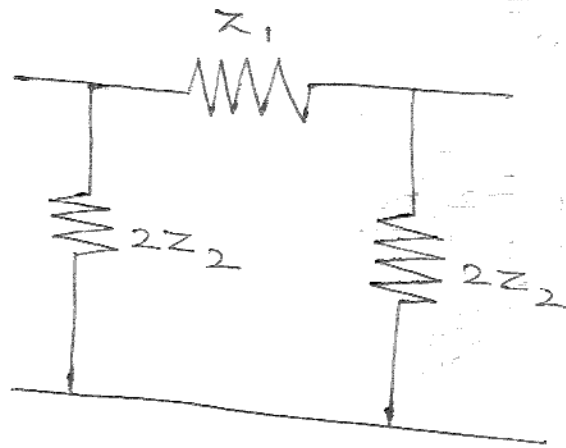

The characteristic impedance of constant K π -section

$$Z_{0\pi} = \frac{Z_1 Z_2}{Z_{0T}} = \frac{Z_1 Z_2}{\sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}}$$

$$= \frac{\sqrt{Z_1 Z_2} Z_1 / Z_2}{\sqrt{\frac{Z_1}{Z_2} \left(1 + \frac{Z_1}{4Z_2}\right)}} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}}$$

$$Z_1 = Z_1'$$

$$Z_2 = \frac{Z_2}{m}$$

$$Z_{oK} = \sqrt{\frac{Z_1' Z_2/m}{1 + \frac{Z_1'}{4Z_2}}}$$

$$= \sqrt{\frac{Z_1' Z_2/m}{1 + \frac{Z_1' m}{4Z_2}}}$$

equating both the impedance

$$\sqrt{\frac{Z_1 Z_2}{1 + Z_1/4}} = \sqrt{\frac{Z_1' Z_2/m}{1 + \frac{Z_1' m}{4Z_2}}}$$

Squaring on both side we get

$$\frac{Z_1 Z_2}{1 + Z_1/4Z_2} = \frac{Z_1' Z_2/m}{1 + \frac{Z_1' m}{4Z_2}}$$

$$\left(\cancel{Z_1 Z_2}\right) \left(\frac{4Z_2 + Z_1 m}{4\cancel{Z_2}}\right) = \left(\frac{Z_1' \cancel{Z_2}}{m}\right) \left(\frac{4\cancel{Z_2}^2 + Z_1}{4\cancel{Z_2}}\right)$$

$$\frac{4z_1 z_2 + z_1' z_1 m}{\cancel{4}} = \frac{4z_2 z_1' + z_1' z_2}{\cancel{4} m}$$

$$4z_1 z_2 m + z_1' z_1 m^2 = 4z_2 z_1' + z_1' z_1$$

$$z_1' z_1 m^2 - z_1' z_1 = 4z_2 z_1' - 4z_1 z_2 m$$

$$z_1' z_1 (m^2 - 1) = 4z_2 (z_1' - z_1 m)$$

$$z_1' z_1 (m^2 - 1) - 4z_2 z_1' = -4z_1 z_2 m$$

$$z_1' [z_1 (m^2 - 1) - 4z_2] = -4z_1 z_2 m$$

$$z_1' = \frac{-4z_1 z_2 m}{z_1 (m^2 - 1) - 4z_2}$$

$$= \frac{-\cancel{4} z_1 z_2 m}{\cancel{4} [z_1 (m^2 - 1) - \frac{z_2}{4}]}$$


$$= \frac{z_1 z_2 m}{\frac{z_2}{4} - z_1 (m^2 - 1)}$$

$$z_1' = \frac{z_1 z_2}{\frac{z_2}{m} + \left(\frac{1 - m^2}{4m}\right) z_1}$$

mult. num and deno by $\frac{4m^2}{1-m^2}$

$$Z_1' = \frac{Z_1 Z_2 \left(\frac{4m^2}{1-m^2} \right)}{Z_2 \left(\frac{4m}{1-m^2} \right) + \left(\frac{1-m^2}{4m} \right) \times \frac{4m^2}{1-m^2} Z_1}$$
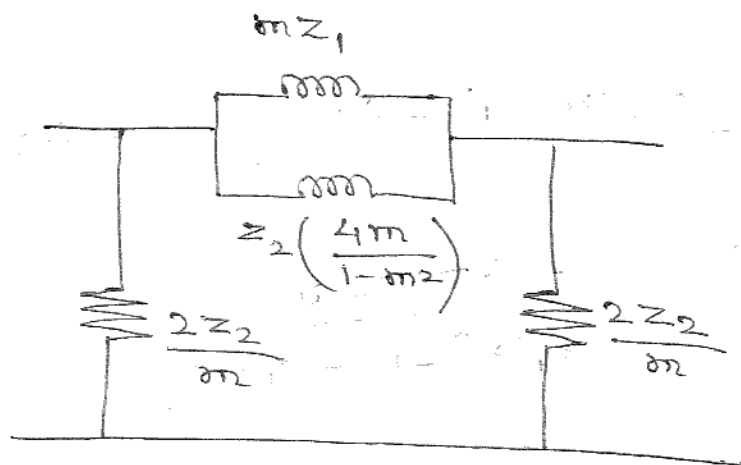
$$= \frac{Z_1 Z_2 \left(\frac{4m^2}{1-m^2} \right)}{Z_2 \left(\frac{4m}{1-m^2} \right) + m Z_1}$$



- M derived low pass filter

The constant K low pass filter the series impedance

$$Z_1 = j\omega L$$

Shunt impedance $Z_2 = \frac{1}{j\omega C}$

For m-derived low pass filter T-section

the series impedance of m -derived T section is

$$\frac{mZ_1}{2} = \frac{m j \omega L}{2} = j \omega \left(\frac{mL}{2} \right)$$

$$\frac{mL}{2} = L'$$

$$\therefore \frac{mZ_1}{2} = j \omega L'$$

Shunt impedance

$$Z_2' = \frac{Z_2}{m} + \left(\frac{1-m^2}{4m} \right) Z_1$$

$$Z_2' = \frac{1}{j \omega C m} + \left(\frac{1-m^2}{4m} \right) j \omega L$$

$$\frac{1}{j \omega C m} = C'' \quad C m = C''$$

$$Z_2' = \frac{1}{j \omega C''} + \left(\frac{1-m^2}{4m} \right) j \omega L$$


$$Z_2' = \frac{1}{j \omega C''} + j \omega L''$$

Here,

$$\left(\frac{1-m^2}{4m} \right) L = L''$$

filter is

ter T-se

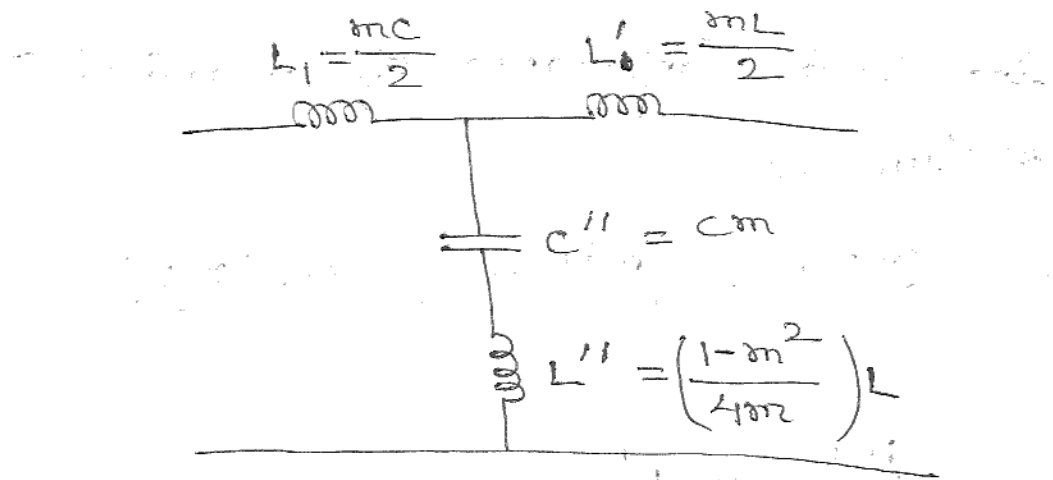

• m derived LPF in π section

Series Shunt imp $\frac{2Z_2}{m} = \frac{1}{j\omega \frac{mC}{2}}$

$\frac{2Z_2}{m} = \frac{1}{j\omega C''}$

Here,

$\frac{mC}{2} = C''$

Series imp $Z'_1 = mZ_1, \frac{4m}{1-m^2} Z_2$

$Z'_1 = j\omega(mL) = j\omega L'$

Here,


$mL = L'$

$Z'_1 = \frac{4m}{1-m^2} Z_2 = \frac{1}{j\omega C \left(\frac{1-m^2}{4m} \right)}$

$$Z_1' = \frac{1}{j\omega C'}$$

Here,

$$\frac{1-m^2}{4m} = C'$$

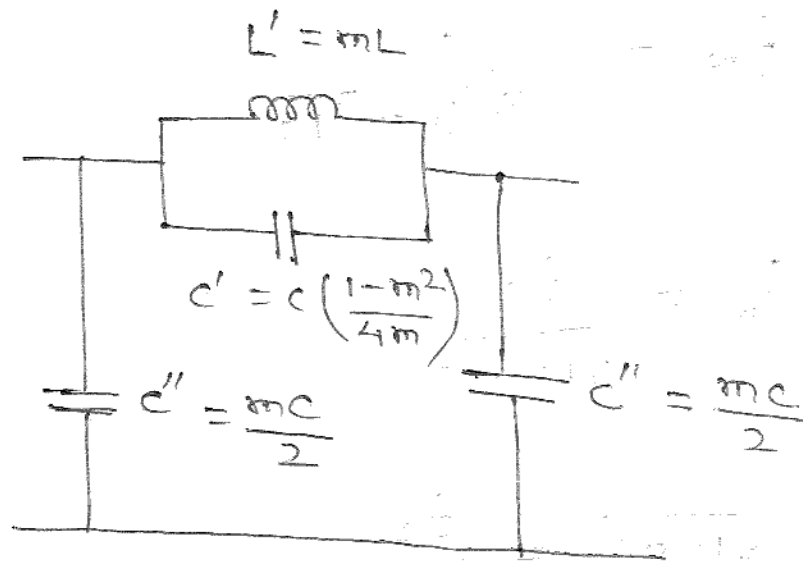

In m -derived T-section filter it has finite impedance. If the condition is

$$X_L = X_C$$

$$\omega L'' = \frac{1}{\omega C''}$$

$$\omega^2 = \frac{1}{L'' C''} = \frac{1}{(mC) \left(\frac{1-m^2}{4m} \right) L}$$

$$\omega^2 = \frac{4}{(1-m^2)LC}$$

$$4\pi^2 f_{\infty}^2 = \frac{4}{(1-m^2)LC}$$

$$f_{\infty}^2 = \frac{1}{\pi^2 (1-m^2)LC}$$

$$f_{\infty} = \frac{1}{\pi \sqrt{(1-m^2)LC}}$$

$$f_{\infty} = \frac{f_c}{\sqrt{1-m^2}}$$

$$\sqrt{1-m^2} = \frac{f_c}{f_{\infty}}$$

$$m^2 = 1 - \left(\frac{f_c}{f_{\infty}}\right)^2$$

$$m = \sqrt{1 - \left(\frac{f_c}{f_{\infty}}\right)^2}$$

M-derived high pass filter

The series impedance of constant K-filter

$$Z_1 = \frac{1}{j\omega C}$$

The shunt impedance of constant K-filter

$$Z_2 = j\omega L$$

The series impedance of m-derived T-section

$$\frac{MZ_1}{2} = \frac{M}{2j\omega C} = \frac{1}{j\omega \left(\frac{2C}{m}\right)}$$

Assume

$$\frac{2C}{m} = C'$$

$$\therefore \frac{1}{j\omega C'} = \frac{Z_1 M}{2}$$

Shunt impedance of m-derived T-section

$$Z_2' = \frac{Z_2}{m} + \left(\frac{1-m^2}{4m}\right) Z_1$$

$$Z_2' = \frac{j\omega L}{m} + \left(\frac{1-m^2}{4m}\right) \frac{1}{j\omega C}$$


$$Z_2' = j\omega \left(\frac{L}{m} \right) + \frac{1}{j\omega \left(\frac{4m}{1-m^2} \right)}$$

Let

$$\frac{L}{m} = L''$$

$$\frac{4mC}{1-m^2} = C''$$
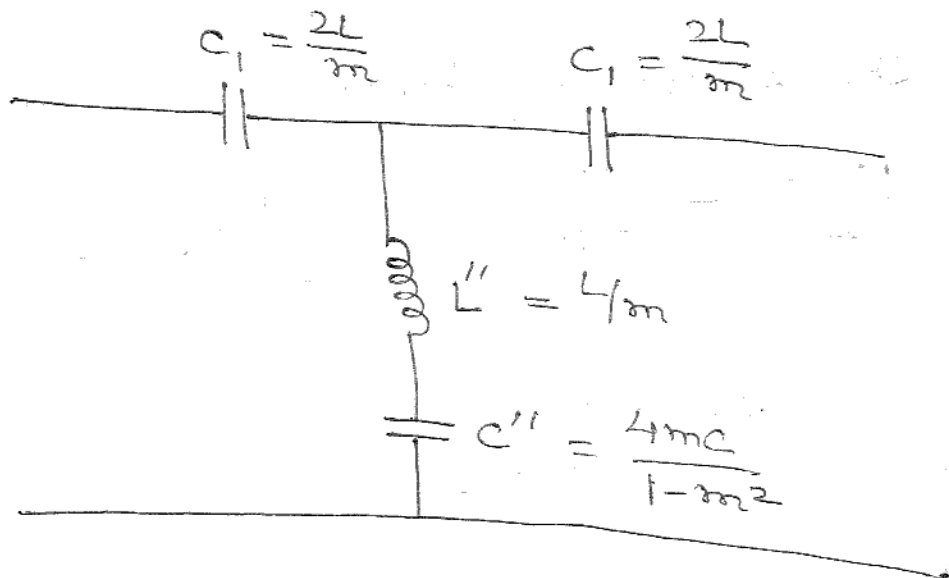
$$Z_2' = j\omega L'' + \frac{1}{j\omega C''}$$



For π section

Shunt impedance $\frac{2Z_2}{m} = \frac{2j\omega L}{m}$

$$\frac{2Z_2}{m} = j\omega \left(\frac{2L}{m} \right) \quad \text{Here, } \frac{2L}{m} = L''$$

$$\frac{2Z_2}{m} = j\omega L''$$


Series impedance

$$Z' = mZ_1 = \frac{m}{j\omega C} = \frac{1}{j\omega\left(\frac{C}{m}\right)} = \frac{1}{j\omega C'}$$

Here, $\frac{C}{m} = C'$

$$Z_2\left(\frac{4m}{1-m^2}\right) = j\omega L\left(\frac{4mL}{1-m^2}\right) = \frac{j\omega(L \cdot 4m)}{(1-m^2)}$$

$$Z_1' = j\omega L_1'$$

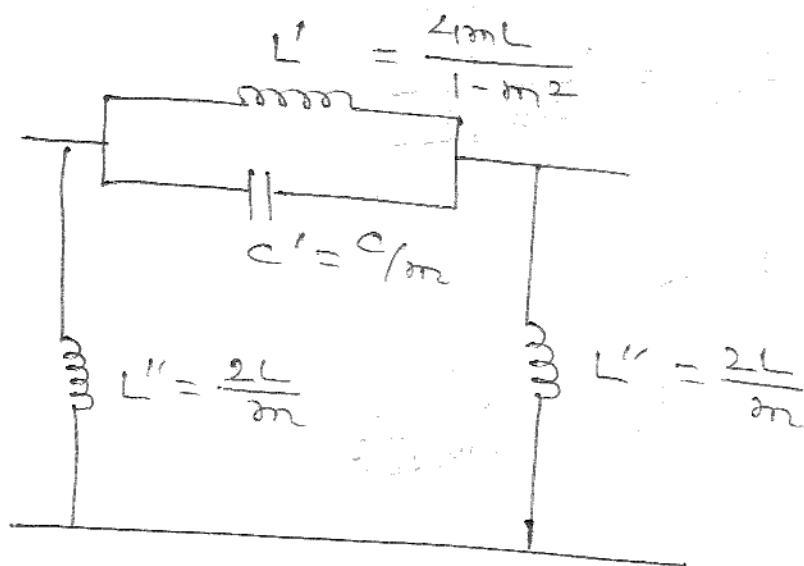

In m-derived T-section filter it has finite impedance.

$$X_L = X_C$$

$$\omega L'' = \frac{1}{\omega C''}$$

$$\omega^2 = \frac{1}{L'' C''}$$

$$\omega^2 = \frac{1}{\left(\frac{L}{m}\right) \left(\frac{4mC}{1-m^2}\right)}$$

$$\omega^2 = \frac{1-m^2}{4LC}$$

$$(2\pi f_a)^2 = \frac{1-m^2}{4LC}$$

$$f_a^2 = \frac{1-m^2}{16\pi^2 LC}$$

$$f_a = \frac{\sqrt{1-m^2}}{4\pi\sqrt{LC}}$$

Here,

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

$$f_a = \frac{\sqrt{1-m^2}}{1} \cdot f_c$$

$$\sqrt{1-m^2} = \frac{f_a}{f_c}$$

Squaring both side


$$(1-m^2) = \left(\frac{f_x}{f_c}\right)^2$$

$$-m^2 = \left(\frac{f_x}{f_c}\right)^2 - 1$$

$$m^2 = 1 - \left(\frac{f_x}{f_c}\right)^2$$

$$m = \sqrt{1 - \left(\frac{f_x}{f_c}\right)^2}$$

- m-derived band pass filter

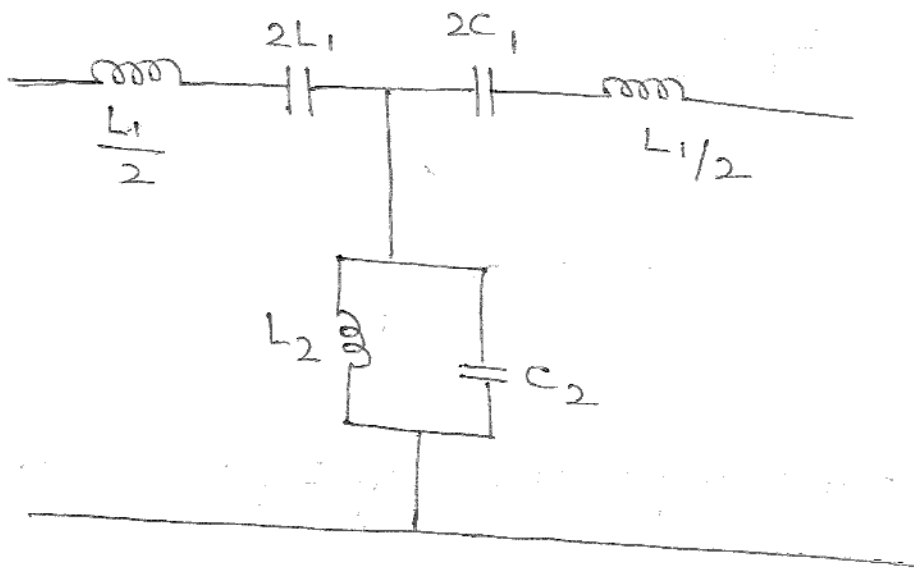

The resonance of each series and shunt

$$\omega_0^2 L_1 C_1 = 1 \quad \text{--- (1)}$$

$$\omega_0^2 L_2 C_2 = 1 \quad \text{--- (2)}$$

equating both eq

$$L_1 C_1 = L_2 C_2$$

~~$$\frac{L_1}{C_2} = \frac{L_2}{C_1}$$~~

$$\frac{L_1}{C_2} = \frac{L_2}{C_1}$$

Consider the series impedance

~~$$Z_1 = jX_L + jX_C$$~~
$$Z_1 = Z_1' + Z_1''$$

~~$$Z_1 = j$$~~
$$Z_1 = j\omega L + \frac{1}{j\omega C}$$

$$Z_1 = j\omega L - \frac{j}{\omega C}$$

$$= j \left(\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right)$$

Shunt impedance of $Z_2 = X_{L_2} \parallel X_{C_2}$

$$Z_2 = \frac{X_{L_2} X_{C_2}}{X_{L_2} + X_{C_2}} = \frac{j\omega L_2 \cdot 1/j\omega C_2}{j\omega L_2 + 1/j\omega C_2}$$

$$Z_2 = \frac{L_2/C_2}{j(\omega^2 L_2 C_2 - 1)}$$

$$Z_2 = \frac{\omega L_2}{j(\omega^2 L_2 C_2 - 1)}$$

$$Z_2 = \frac{j\omega L_2}{1 - \omega^2 L_2 C_2}$$

we know that

$$Z_1 Z_2 = R_0^2$$

$$Z_1 Z_2 = \frac{j(\omega^2 L_1 C_1 - 1)}{\cancel{j\omega C_1}} \times \frac{j\cancel{\omega} L_2}{(1 - \omega^2 L_2 C_2)}$$

$$Z_1 Z_2 = \frac{(1 - \omega^2 L_1 C_1) L_2}{(1 - \omega^2 L_2 C_2) C_1}$$

~~$$L_1 = L_2 \text{ and } L_2 = C_2$$~~

$$L_1 C_1 = L_2 C_2$$

$$Z_1 Z_2 = \frac{L_2}{C_1}$$

$$\therefore R_0^2 = \frac{L_2}{C_1}$$

$$R_0 = \sqrt{\frac{L_2}{C_1}}$$

$$z_1 + 4z_2 = 0$$

$$z_1 = -4z_2$$

multiply both side by z_1

$$z_1^2 = -4z_1z_2$$

$$z_1^2 = -4R_0^2$$

$$z_1 = \pm j2R_0$$

$$z_1 = \pm 2jR_0$$

To find lower cut off frequency the impedance

$-z_1$ value is a lower cut off freq.

$-z_1(f_1) = +ve z_1$ of upper cut off frequency f_2 .

$$z_1 = -z_1$$

$$\cancel{j\omega_1 L_1} \cdot \cancel{j\omega}$$

$$j\omega_1 L_1 + \frac{1}{j\omega_1 C_1} = - \left(j\omega_2 L_1 + \frac{1}{j\omega_2 C_1} \right)$$

$$j\omega_1 L_1 - \frac{j}{\omega_1 C_1} = - \left(j\omega_2 L_1 - \frac{j}{\omega_2 C_1} \right)$$

$$\cancel{j} \left(\frac{1}{\omega_1 C_1} - \omega_1 L_1 \right) = -\cancel{j} \left(\omega_2 L_1 + \frac{1}{\omega_2 C_1} \right)$$

$$\frac{1 - \omega_1^2 L_1 C_1}{\omega_1 \cancel{j}} = \frac{\omega_2 L_1 C_1 - 1}{\omega_2 \cancel{j}}$$

$$\frac{1 - \omega_1^2 L_1 C_1}{\omega_1} = \frac{\omega_2 L_1 C_1 - 1}{\omega_2}$$

$$1 - \omega_1^2 L_1 C_1 = \frac{\omega_1}{\omega_2} (\omega_2 L_1 C_1 - 1)$$

$$\omega_0^2 L_1 C_1 = 1$$

$$L_1 C_1 = \frac{1}{\omega_0^2}$$

$$1 - \frac{\omega_1^2}{\omega_0^2} = \frac{\omega_1}{\omega_2} \left(\frac{\omega_2^2}{\omega_0^2} - 1 \right)$$

$$\omega_1 = 2\pi f_1$$

$$\omega_0 = 2\pi f_0$$

$$\omega_2 = 2\pi f_2$$

$$1 - \left(\frac{f_1}{f_0} \right)^2 = \frac{f_1}{f_2} \left[\left(\frac{f_2}{f_0} \right)^2 - 1 \right]$$

$$1 - \left(\frac{f_1}{f_0}\right)^2 = \frac{f_1 f_2}{f_0^2} - \frac{f_1}{f_2}$$

$$1 + \frac{f_1}{f_2} = \frac{f_1 f_2}{f_0^2} + \frac{f_1^2}{f_0^2}$$

$$\frac{f_1 + f_2}{f_2} = \frac{1}{f_0^2} (f_1 f_2 + f_1^2)$$

$$f_0^2 = \frac{(f_1 f_2 + f_1^2) f_2}{f_1 + f_2}$$

$$f_0^2 = \frac{f_1 f_2 \cancel{(f_1 + f_2)}}{\cancel{f_1 + f_2}}$$

$$f_0^2 = f_1 f_2$$

$$f_0 = \sqrt{f_1 f_2}$$

20.11.11

At lower cut off freq

$$Z_1 = -2jR$$

$$j\omega L_1 + \frac{1}{j\omega C_1} = -2jR$$

$$\Rightarrow j\omega_1 L_1 - \frac{j}{\omega_1 C_1} = -j2R$$

$$\cancel{j} \left(\frac{1}{\omega_1 C_1} - \omega_1 L_1 \right) = \cancel{j} 2R$$

$$\frac{1}{\omega_1 C_1} - \omega_1 L_1 = 2R$$

$$\frac{1 - \omega_1^2 L_1 C_1}{\omega_1 C_1} = 2R$$

$$\frac{1 - \omega_1^2}{\omega_0^2} = 2R \omega_1 C_1$$

Here,

$$L_1 C_1 = \frac{1}{\omega_0^2}$$

$$\frac{1 - f_1^2}{f_0^2} = 2R \cdot 4\pi R f_1 C_1$$

$$\frac{f_0^2 - f_1^2}{f_0^2} = 4\pi R f_1 C_1$$

$$C_1 = \frac{f_0 - f_2^2}{f_0^2 4\pi R f_1}$$

$$1 - \frac{f_2^2}{f_0^2} = 4\pi R f_1 C_1$$

$$\frac{f_2 - f_1}{f_2} = 4\pi R f_1 C_1$$

$$C_1 = \frac{f_2 - f_1}{f_1 4\pi R f_2}$$

$$C_1 = \frac{f_2 - f_1}{4\pi R f_1 f_2}$$

we know that,

$$L_1 C_1 = \frac{1}{\omega_0^2}$$

$$L_1 = \frac{1}{\omega_0^2 C_1} = \frac{1}{\omega_0^2 \left(\frac{f_2 - f_1}{4\pi R f_1 f_2} \right)}$$

$$L_1 = \frac{1}{4\pi^2 f_0^2 \frac{(f_2 - f_1)}{4\pi R f_1 f_2}}$$

$$L_1 = \frac{R f_1 f_2}{\pi f_0^2 (f_2 - f_1)}$$

$$L_1 = \frac{R}{\pi (f_2 - f_1)}$$

We know that

$$\frac{L_2}{C_1} = R^2$$

$$L_2 = R^2 C_1$$


$$L_2 = \frac{R^2 (f_2 - f_1)}{4\pi R f_1 f_2}$$

$$L_2 = \frac{R(f_2 - f_1)}{4\pi f_1 f_2}$$


Also,

$$\frac{L_1}{C_2} = R^2$$
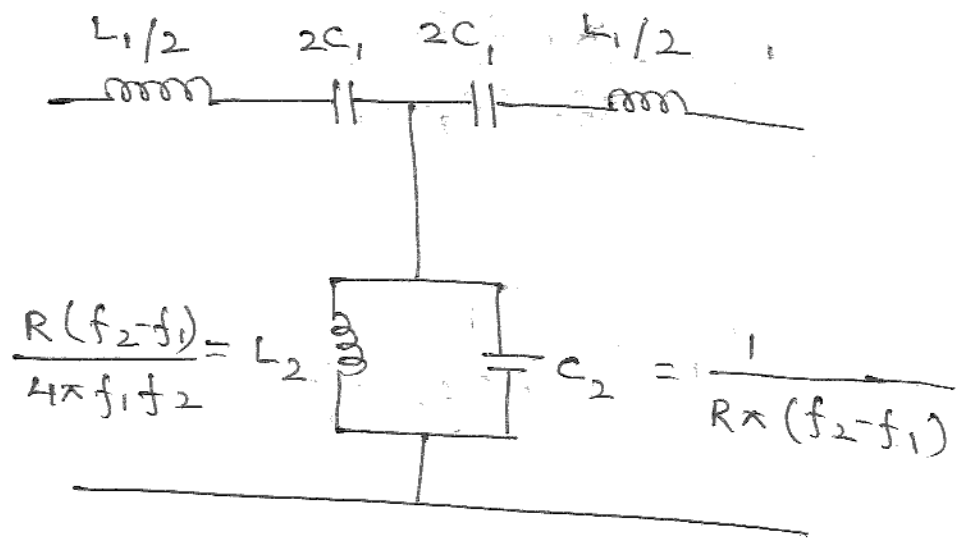
$$\Rightarrow C_2 = \frac{R^2}{L_1} = \frac{1}{R\pi(f_2 - f_1)}$$



* Band elimination filter

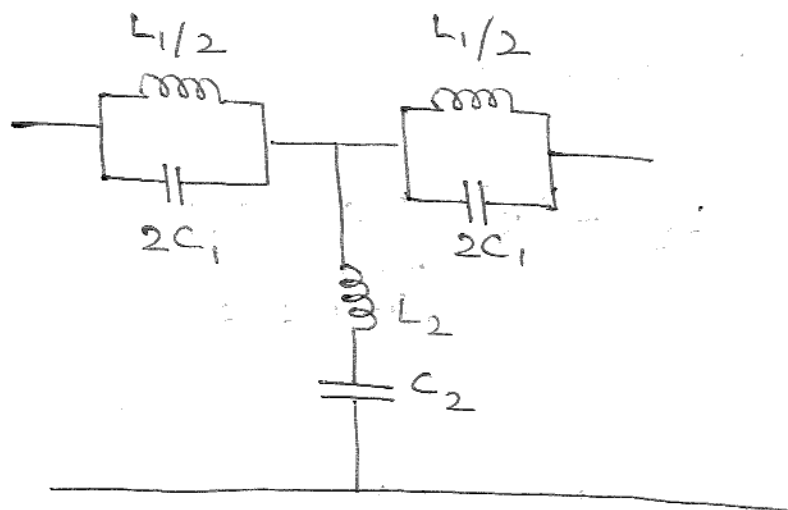

The resonance freq of

$$\omega_0^2 L_1 C_1 = \omega_0^2 L_2 C_2 = 1$$

$$L_1 C_1 = L_2 C_2 = \frac{1}{\omega_0^2}$$

$$L_1 / C_2 = \frac{L_2}{C_1} = R_0^2$$

$$f_0^2 = f_1 f_2$$

$$f_0 = \sqrt{f_1 f_2}$$

For cut off freq

$$z_1 + 4z_2 = 0$$

$$z_1 = -4z_2$$

multi by z_2 on both side

$$z_2 z_1 = -4 z_2^2$$

$$R_0^2 = -z_2^2 4$$

$$z_2 = \frac{jR_0}{2}$$

$$z_2 = -\frac{jR_0}{2}$$

$$j\omega_1 L_2 + \frac{1}{j\omega_1 C_2} = \frac{-jR_0}{2}$$

$$j\left(\omega_1 L_2 - \frac{1}{\omega_1 C_2}\right) = \frac{-jR_0}{2}$$

$$1 - \omega_1^2 L_2 C_2 = \frac{R_0}{2} \omega_1 C_2$$

$$1 - \frac{\omega_1^2}{\omega_0^2} = R \pi f_1 C_2$$

$$1 - \frac{f_1^2}{f_0^2} = R \pi f_1 C_2$$

$$1 - \frac{f_1}{f_2} = R \pi f_1 C_2$$

$$\frac{f_2 - f_1}{f_2} = R \pi f_1 C_2$$

$$C_2 = \frac{f_2 - f_1}{R \pi f_1 f_2}$$

$$L_2 C_2 = \frac{1}{\omega_0^2}$$

$$L_2 = \frac{1}{C_2 \omega_0^2}$$

$$= \frac{1}{\left(\frac{f_2 - f_1}{R \pi f_1 f_2}\right) (2\pi f_0)^2}$$

$$L_2 = \frac{R}{4\pi(f_2 - f_1)}$$

$$\frac{L_2}{C_1} = \frac{L_1}{C_2} = R$$

Using series circuit A transformer is referred to

primary side $\frac{L_2}{C_1} = R$ referred

$$C_1 = L_2 / R^2$$

$$C_1 = \frac{R}{4\pi R^2 (f_2 - f_1)}$$

$$C_1 = \frac{1}{4\pi R (f_2 - f_1)}$$

$$\frac{L_1}{C_2} = R^2$$

$$L_1 = R^2 C_2$$

$$= \frac{R^2 (f_2 - f_1)}{R\pi f_1 f_2}$$

$$L_1 = \frac{R(f_2 - f_1)}{\pi f_1 f_2}$$

22.7.11

Q- Design a constant k bandpass filter terminate $R_0 = 600 \Omega$ the cut off freq is 5KHz. Find L_1, L_2 and C_1 and C_2 .

$$f_1 = 2 \text{ KHz}$$

Sol-
$$L_1 = \frac{R_0}{\pi(f_2 - f_1)}$$

$$= \frac{600}{\pi(5-2)} = \frac{600}{\pi(5-2)}$$

$$L_1 = 63.66 \text{ mH}$$

$$L_2 = \frac{R_0(f_2 - f_1)}{4\pi f_1 f_2} = \frac{600(5-2)}{4\pi \cdot 10}$$

$$= \frac{60 \times 3}{4\pi} = 14.32 \text{ mH}$$

$$C_1 = \frac{f_2 - f_1}{R_0 4\pi f_1 f_2} = \frac{5-2}{600 \times 4 \times \pi \times 10}$$

$$C_1 = 3.97 \times 10^{-5}$$

$$= 0.0397 \mu\text{f}$$

$$C_2 = \frac{1}{R_0 \pi (f_2 - f_1)} = \frac{1}{600 \pi \times 3}$$

$$= 1.76 \times 10^{-4}$$


$$= 0.177 \mu\text{f}$$

$$L_1 C_1 = L_2 C_2 = R^2$$

$$L_1/2 = 31.83$$

$$2C_1 = 0.078$$

$$L_1/2 = 31.83$$

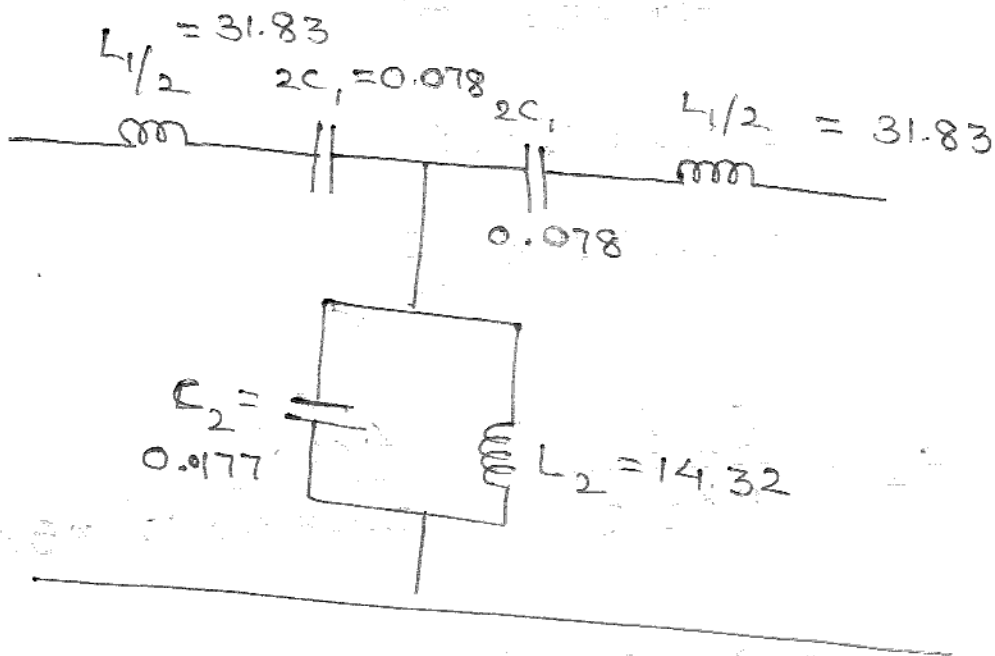

Q. Design a band elimination filter having a design impedance 500Ω and cut off freq $f_1 = 1 \text{ KHz}$ and $f_2 = 5 \text{ KHz}$.

$$\text{Sol. } L_1 = \frac{R(f_2 - f_1)}{\pi f_1 f_2} = \frac{500(5 \times 10^3 - 1 \times 10^3)}{\pi \times 5 \times 10^3 \times 1 \times 10^3}$$

$$= 127.3 \text{ H}$$

$$L_2 = \frac{R}{4\pi(f_2 - f_1)} = \frac{500}{4\pi(4 \times 10^3)}$$

$$L_2 = 9.95 \text{ mH}$$

$$C_1 = \frac{1}{4\pi R(f_2 - f_1)}$$

$$= \frac{1}{4\pi \times 500(4)}$$

$$= 3.978 \times 10^{-5}$$

$$= 0.03978 \text{ } \mu\text{f}$$

$$C_2 = \frac{f_2 - f_1}{R\pi f_1 f_2} = \frac{4 \times 10^3}{500 \times \pi \times 10^3 \times 5 \times 10^3}$$

$$= 0.509 \text{ } \mu\text{f}$$

