

Constant :-

$$e^{xL} = 1 + \gamma L + \frac{\gamma^2 L^2}{2!} + \frac{\gamma^3 L^3}{3!} + \dots$$

$$\therefore e^{xL} = 1 + \frac{Z_1}{2Z_2} + \frac{Z_0}{2Z_2}$$

$$= 1 + \frac{(R + j\omega L)L}{2} + \frac{Z_0}{2}$$
$$\frac{(R + j\omega L)L}{(G + j\omega C)L} \quad \frac{Z_0}{(G + j\omega C)L}$$

$$= 1 + \frac{(R + j\omega L)L \times (G + j\omega C)L}{2} + \frac{Z_0(G + j\omega C)L}{2}$$

$$= 1 + \frac{(R + j\omega L)(G + j\omega C)L^2}{2} + Z_0(G + j\omega C)L$$

J.S.
19107111

20/7/14

$$= 1 + \frac{(R + j\omega L)(G + j\omega C)L^2}{2} + \sqrt{\frac{R + j\omega L}{G + j\omega C}} (G + j\omega C)L$$

$$= 1 + \frac{(R + j\omega L)(G + j\omega C)L^2}{2} + (R + j\omega L)^{1/2} (G + j\omega C)^{1/2} L$$

$$e^{xL} = 1 + \frac{(R + j\omega L)(G + j\omega C)L^2}{2} + \sqrt{(R + j\omega L)(G + j\omega C)} L$$

(1)

$$e^{rd} = 1 + rd + \frac{r^2 d^2}{2!} + \frac{r^3 d^3}{3!} + \dots$$

when $d \rightarrow 0$.

$$e^{rd} = 1 + rd + \frac{r^2 d^2}{2!} \quad \text{--- (2)}$$

Comparing (1) & (2),

$$Y^2 = (R + j\omega L)(G + j\omega C)$$

$$Y = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\boxed{Y = \sqrt{ZY}}$$

Determination of α & β in terms of

Primary Constant :-

$$Y = \alpha + j\beta$$

$$\equiv \sqrt{\alpha^2 + \beta^2} \angle \tan^{-1} \frac{\beta}{\alpha}$$

$$\therefore Y = \sqrt{ZY}$$

$$= \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{RG + jR\omega C + Gj\omega L + j^2\omega^2 LC}$$

$$= \sqrt{\sqrt{R^2 + \omega^2 L^2} \tan^{-1} \frac{\omega L}{R} \cdot \sqrt{G^2 + \omega^2 C^2} \tan^{-1} \frac{\omega C}{G}}$$

$$= \sqrt[4]{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} \angle \frac{1}{2} \left[\tan^{-1} \frac{\omega L}{R} + \tan^{-1} \frac{\omega C}{G} \right]$$

\therefore If $\sqrt{\alpha^2 + \beta^2}$

$$\Rightarrow \sqrt{\alpha^2 + \beta^2} = \sqrt[4]{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}$$

& taking squaring on both sides,

$$\alpha^2 + \beta^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}$$

$$\Rightarrow (\alpha^2 + \beta^2)^2 = R$$

$$(\alpha + j\beta)^2 = (R + j\omega L)(G + j\omega C)$$

$$\alpha^2 - \beta^2 + 2j\alpha\beta = (R + j\omega L)(G + j\omega C)$$

$$= RG + Rj\omega C + Gj\omega L$$

$$- \omega^2 LC$$

$$\boxed{\alpha^2 - \beta^2 = RG - \omega^2 LC}$$

$$\& \boxed{2j\alpha\beta = Rj\omega C + Gj\omega L}$$

$$\boxed{\alpha^2 + \beta^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}}$$

$$2\alpha^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} + R G - \omega^2 L C$$

$$\Rightarrow \alpha = \sqrt{\frac{1}{2} \left\{ \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} + R G - \omega^2 L C \right\}}$$

$$2\beta^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} - R G + \omega^2 L C$$

$$\Rightarrow \beta = \sqrt{\frac{1}{2} \left\{ \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)} - R G + \omega^2 L C \right\}}$$

General Solution of Transmission line

OR, Determinⁿ of voltage & current in Transmission line

The general solⁿ of transmission line includes the expression for current & voltage at any point along the line of any length having uniformly distributed constants.

The various notation used in the derivation are:-

$R =$ Series resistance (Ω).

$L =$ Series Inductance (Henry, H) / length.

$C =$ Series Capacitance betⁿ two
Conductors. (farad per unit length).

$G =$ Shunt leakage conductance (mho).

ωL
 ~~ωL~~ = Angular frequency
series reactance per unit length.

ωC
 ~~ωC~~ = Shunt Susceptance per unit length.

$Y =$ ^{shunt} Admittance (mho)


$Z =$ ^{series} Impedance in Ω / length (Ω).

$$\boxed{Z = R + j\omega L}$$

$$\boxed{Y = \frac{1}{Z}}$$

$$\boxed{Y = G + j\omega C}$$

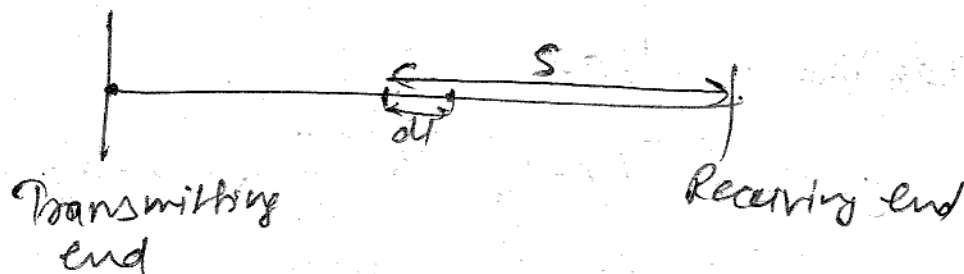$S =$ Distance upto point of Consideration
measured from receiving




$I =$ Current in a line at any point

$V =$ voltage between conductors,

at any point.

$l =$ length of transmission line.

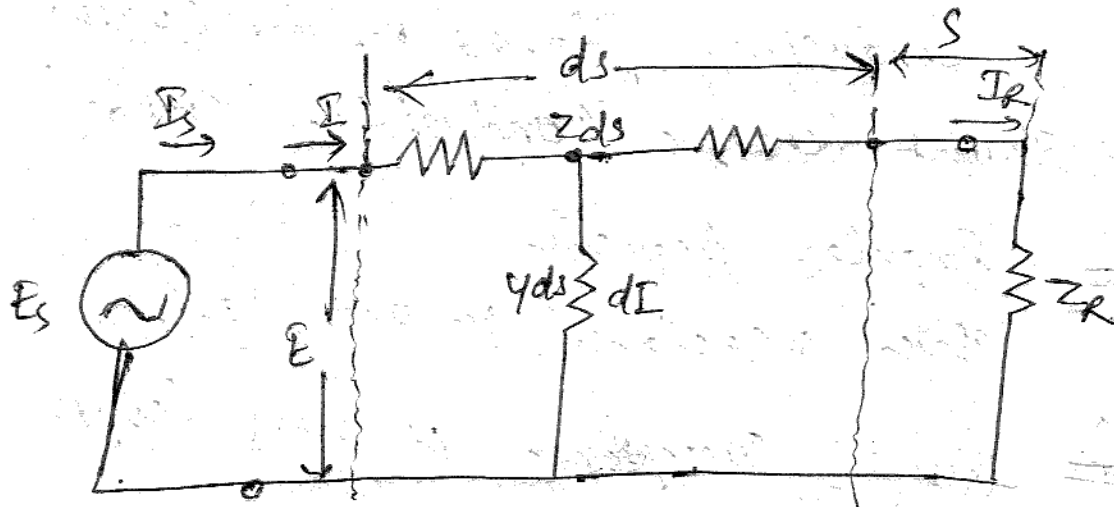

Transmission line of length l can be considered to be made up of infinitely small π -sections.

At the point of consideration the length of the section is ds . Hence, its series impedance is Z_{ds} , and shunt admittance Y_{ds} .

Current passing is I & voltage is V .

$dE =$ Elemental Voltage drop. $= IZ ds$

$$dI = E Y ds$$

↑
leakage current flowing through shunt amp
resistance

$$\frac{dE}{ds} = IZ \quad \text{--- (1)}$$

$$\frac{dI}{ds} = EY \quad \text{--- (2)}$$

Diff (1) & (2) w.r.to s ,

$$\frac{d^2E}{ds^2} = Z \frac{dI}{ds} \quad \text{--- (2)} = ZEY \quad \text{--- (3)}$$

$$\frac{d^2I}{ds^2} = Y \frac{dE}{ds} \quad \text{--- (1)} = YIZ \quad \text{--- (4)}$$

Taking LCM as Z_R and taking $\frac{Z_R + Z_0}{Z_R}$

out from eqⁿ (18),

$$E = \frac{E_R}{2} \left(\frac{Z_R + Z_0}{Z_R} \right) \left[e^{\sqrt{Z_0 Y} s} + \left(\frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\sqrt{Z_0 Y} s} \right] \quad (20)$$

Taking LCM as $\frac{Z_R + Z_0}{Z_R}$ out from eqⁿ (19)

$$I = \frac{I_R}{2} \left(\frac{Z_R + Z_0}{Z_R} \right) \left[e^{\sqrt{Z_0 Y} s} - \left(\frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-\sqrt{Z_0 Y} s} \right] \quad (21)$$

Eqⁿ (20) & (21) is the general solⁿ for the transmission line.

26/7/11

Physical Significance of general solⁿ of Transmission line :-

Take the Expression E , as :-

$$E = \frac{E_R}{2Z_R} \left[(Z_R + Z_0) e^{\sqrt{Z_0 Y} s} + (Z_R - Z_0) e^{-\sqrt{Z_0 Y} s} \right]$$

$$E = \frac{E_R}{2Z_R} \left[Z_R e^{\sqrt{Z_0 Z_R} s} + Z_0 e^{\sqrt{Z_0 Z_R} s} + Z_R e^{-\sqrt{Z_0 Z_R} s} - Z_0 e^{-\sqrt{Z_0 Z_R} s} \right]$$

$$= \frac{E_R}{2Z_R} \left[Z_R (e^{\sqrt{Z_0 Z_R} s} + e^{-\sqrt{Z_0 Z_R} s}) + Z_0 (e^{\sqrt{Z_0 Z_R} s} - e^{-\sqrt{Z_0 Z_R} s}) \right]$$

$$= \frac{E_R}{2Z_R} \left[Z_R \left(\frac{e^{\sqrt{Z_0 Z_R} s} + e^{-\sqrt{Z_0 Z_R} s}}{2} \right) + Z_0 \left(\frac{e^{\sqrt{Z_0 Z_R} s} - e^{-\sqrt{Z_0 Z_R} s}}{2} \right) \right]$$

$$= \frac{E_R}{2Z_R} \left[\dots \right]$$

$$= \frac{E_R}{2Z_R} \left[\dots \right]$$

$$\left[\because \frac{E_R}{Z_R} = I_R \right]$$

$$E = E_R \cosh \sqrt{Z_0 Z_R} s + I_R Z_0 \sinh \sqrt{Z_0 Z_R} s$$

Similarly,

$$I = I_R \cosh \sqrt{Z_0 Z_R} s + \frac{E_R}{Z_0} \sinh \sqrt{Z_0 Z_R} s$$

-(25) eq.

(24) & (25)
 form that eqⁿ sending n current is
 obtained by $S=l$, i.e. measured from
 receiving end.

$$E_s = E_R \cosh(\gamma l) + I_R Z_0 \sinh(\gamma l) \quad \text{--- (1)}$$

$$\therefore \sqrt{ZY} = \gamma$$

$$S=l$$

$$I_s = I_R \cosh(\gamma l) + \frac{E_R}{Z_0} \sinh(\gamma l) \quad \text{--- (2) eqⁿ}$$

$$\therefore Z_R = \frac{E_R}{I_R}$$

$$I_s = I_R \cosh(\gamma l) + \frac{Z_R I_R}{Z_0} \sinh(\gamma l)$$

$$I_s = I_R \left[\cosh(\gamma l) + \frac{Z_R}{Z_0} \sinh(\gamma l) \right]$$

If the line is terminated to characteristic
 impedance,

$$I_s = I_R \left[\cosh(\gamma l) + \sinh(\gamma l) \right] \quad \text{--- (3)}$$

$$\frac{I_s}{I_R} = \cosh(\gamma l) + \sinh(\gamma l)$$

$$\text{But } \frac{I_S}{I_R} = e^{rL}$$

$$\Rightarrow \boxed{e^{rL} = \cosh(rL) + \sinh(rL)}$$

I_S = Sending Current

— (4) eqⁿ

I_R = Receiving Current

~~Now taking E:~~

$$E_S = E_R \cosh h$$

$$E_S = E_R \cosh(rL) + I_R Z_0 \sinh(rL) = \dots$$

$$E_S = I_R [Z_R \cosh(rL) + Z_0 \sinh(rL)]$$

— (5) eqⁿ

divide eqⁿ (5) by (4),

$$\frac{E_S}{I_R} = \frac{I_R [Z_R \cosh(rL) + Z_0 \sinh(rL)]}{I_R [\cosh(rL) + \frac{Z_R}{Z_0} \sinh(rL)]}$$

$$= \frac{Z_0 Z_R \cosh(rL) + Z_0^2 \sinh(rL)}{Z_0 \cosh(rL) + Z_R \sinh(rL)}$$

$Z_0 = Z_R$ (consider for symmetrical n/wire)

\Rightarrow

$$\frac{E_s}{I_R} = \frac{Z_0 [\cosh(\gamma l) + \cancel{\sin h(\gamma l)}]}{Z_0 [\cosh(\gamma l) + \cancel{\sin h(\gamma l)}]}$$

$= Z_0$

$$\frac{E_s}{I_R} = Z_0$$

This shows that a line terminated its characteristic impedance. Its i/p impedance (Z_s) = o/p impedance Z_R .

WAVELENGTH AND VELOCITY OF PROPAGATION CONSTANT

\rightarrow

$$\gamma = \alpha + j\beta$$

$$\gamma = \sqrt{ZY}$$

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\Rightarrow (\alpha + j\beta)^2 = (R + j\omega L)(G + j\omega C)$$

$$= RG + Rj\omega C + Gj\omega L - \omega^2 LC$$

\Rightarrow ~~$\alpha + j\beta$~~

$$\alpha^2 - \beta^2 + 2j\alpha\beta = RG - \omega^2 LC + j\omega(RC + GL)$$

So, eqⁿ real & imag parts,

$$\alpha^2 - \beta^2 = RG - \omega^2 LC$$

$$\alpha^2 = \beta^2 + RG - \omega^2 LC \quad \text{--- (1)}$$

imag parts

$$2j\alpha\beta = \omega(RC + GL)$$

$$\Rightarrow 4\alpha^2\beta^2 = \omega^2(LG + RC)^2$$

$$\Rightarrow \alpha^2\beta^2 = \frac{\omega^2(LG + RC)^2}{4} \quad \text{--- (2)}$$

Sub (1) in (2).

$$\Rightarrow (\beta^2 + RG - \omega^2 LC)\beta^2 = \frac{\omega^2(LG + RC)^2}{4}$$

$$\Rightarrow (\beta^4 + \beta^2 R_G - \beta^2 \omega^2 LC) - \frac{\omega^2}{4} (L_G + R_C)^2 = 0$$

$$\Rightarrow \beta^4 + \beta^2 (R_G - \omega^2 LC) - \frac{\omega^2}{4} (L_G + R_C)^2 = 0$$

or

$$\beta^2 = \frac{-(R_G - \omega^2 LC) \pm \sqrt{(R_G - \omega^2 LC)^2 + \omega^2 (L_G + R_C)^2}}{2}$$

42)

$$\beta = \frac{-(R_G - \omega^2 LC) + \sqrt{\omega^2 LC - R_G + \sqrt{(R_G - \omega^2 LC)^2 + \omega^2 (L_G + R_C)^2}}}{2}$$

$$\beta = \frac{\omega^2 LC - R_G + \sqrt{(R_G - \omega^2 LC)^2 + \omega^2 (L_G + R_C)^2}}{2}$$

Substitute the value of β in eq 2

$$\therefore d^2 \beta^2 = \frac{\omega^2 (L_G + R_C)^2}{4}$$

$$\Rightarrow \frac{d^2}{L} = \frac{\omega^2 (L_G + R_C)^2}{4}$$

for Perfect transmission, $R=0$, $G=0$, M

$$\beta^2 = \frac{-(-\omega^2 LC) \pm \sqrt{(-\omega^2 LC)^2 + \omega^2}}{2}$$

$$= \frac{\omega^2 LC + \omega^2 LC}{2}$$

$$\Rightarrow \frac{2\omega^2 LC}{2} = \omega^2 LC$$

$$\beta^2 = \omega^2 LC$$

$$\Rightarrow \boxed{\beta = \omega \sqrt{LC}}$$

Velocity, $v = \lambda f$

$$= \frac{2\pi \lambda f}{2\pi}$$

$$= 2\pi f \cdot \frac{\lambda}{2\pi}$$

$\therefore \beta = \frac{2\pi}{\lambda}$, $f = \frac{\omega}{2\pi}$ in terms of freq.

$$\boxed{v = \frac{\omega}{\beta}}$$

$$V = \frac{\omega}{\omega \sqrt{LC}}$$

$$V = \frac{1}{\sqrt{LC}}$$

velocity of transmission line.

$$\lambda = \frac{2\pi}{\beta} \Rightarrow \frac{2\pi}{\beta}$$

TELEPHONE CABLES :-

In telephone cables the wires are insulated with paper twisted in pairs, this construction results in negligible values of inductance and conductance. for perfect transmission, $R=0$ & $G=0$.

Conditions :- ~~$L\omega \ll R$~~ , $L\omega \ll R$
and $G \ll C\omega$.

Impedance, $Z = R + j\omega L = R$ ^{for transmission line} \approx _{for telephone lines.}

Admittance, $Y = G + j\omega C = j\omega C$

$$Y = \sqrt{ZY} = \sqrt{j\omega RC} \quad \frac{\sqrt{ZY}}{Y}$$

$$= \sqrt{\frac{2j\omega RC}{2}}$$

$$\alpha + j\beta = \sqrt{\frac{j2\omega RC}{2}} \quad \because j = 1 + j^2$$

$$= (1 + j) \sqrt{\frac{\omega RC}{2}}$$

$$= \sqrt{\frac{\omega RC}{2}} + j \sqrt{\frac{\omega RC}{2}}$$

$$\alpha = \sqrt{\frac{\omega RC}{2}}$$

$$\beta = \sqrt{\frac{\omega RC}{2}}$$

$$V = \frac{\omega}{\beta} = \frac{\omega}{\sqrt{\frac{\omega RC}{2}}} = \sqrt{\frac{2\omega}{RC}}$$

$$V = \sqrt{\frac{2\omega}{RC}}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R}{j\omega C}}$$

Line Distortion :-

Signal transmitted over a transmission line is a complex and consist of many frequency component.

Such ~~as~~ voice signal voltage, will not have equal attenuation and equal time delay. The received signal will not be identical with i/p signal. These variation is known as distortion.

Types :- (i) frequency Distortion
ii) Time ^{Delay} Distortion

~~The~~ Condition ^{6 marks} for distortion less line :-

If a line is to have neither frequency nor delay distortion, then attenuation factor and velocity of propagation ' v ' cannot be function of frequency.

$V = \frac{C_0}{\beta}$, and β must be
the direct function
of frequency.

$$\beta = \sqrt{\frac{\omega^2 LC - R_0 + \sqrt{(R_0 - \omega^2 LC)^2 + \omega^2 (L_0 + CR_0)^2}}{2}}$$

$$(R_0 - \omega^2 LC)^2 + \omega^2 (L_0 + CR_0)^2 = (R_0 + \omega^2 LC)^2$$

$$\Rightarrow \cancel{R_0^2} + \omega^2 \cancel{L_0^2} - \cancel{2R_0\omega^2 LC} + \omega^2 L_0^2 + \omega^2 C^2 R_0^2 + 2\omega^2 L_0 CR_0 = \cancel{R_0^2} + \omega^4 \cancel{L_0^2} + 2R_0\omega^2 LC$$

$$\Rightarrow \omega^2 L_0^2 + \omega^2 C^2 R_0^2 = 2R_0\omega^2 LC$$

$$\Rightarrow \omega^2 L_0^2 + \omega^2 C^2 R_0^2 - 2R_0\omega^2 LC = 0$$

$$\Rightarrow \omega^2 (L_0^2 + C^2 R_0^2 - 2R_0 LC) = 0$$

$$\Rightarrow \omega^2 (L_0 - RC)^2 = 0$$

$$\Rightarrow \text{Either } \boxed{\omega = 0},$$

& ~~$L_0 = RC$~~

$$\boxed{L_0 = RC}$$

$$\Rightarrow \boxed{\frac{R}{L} = \frac{1}{C}}$$

Line at Radio-frequency

1st Assumption

For a radio frequency line of either open wire type or coaxial line type, the standard assumptions made for the analysis of the performance of the line.

Assumptions :-

- (1) At very high frequency the skin effect is affectable.

~~Skin effect :- Current flows over the cond~~

It is assumed that the current may flow ~~over~~ surface of conductor, then ~~the~~ internal conductance becomes zero.

- (2) Due to skin effect, the resistance R increases with frequency. $\Rightarrow \omega L \gg R$

Hence ωL (reactance) also increased with frequency.

- (3) The line at radio frequency is constructed such that the leakage ~~conductor~~ conductance $G \rightarrow$ zero.

Consideration: - (i)

(1) R is slightly small with respect to ωL .

(ii) R is completely negligible, when $\omega L \gg R$.

Case 2 If R is ^{completely} negligible, then such a line is

called as zero dissipation line.

Case 1 If R is small then such a line is called small dissipation line.

PARAMETERS OF LINE AT HIGH FREQUENCY

Basic parameter, R, L, C, G .

For open wire line:

$$L = 10^{-7} \left(\frac{\mu}{\mu_0} + 4 \ln \frac{d}{a} \right) \text{ H/m}$$

for closed wire:

$$L = 10^{-7} \left[2 \ln \frac{b}{a} + 2 C' \ln \frac{C}{a} - \frac{C^2}{(C^2 - b^2)^2} \frac{C^2}{C^2 - b^2} \right]$$

where,

H/m.

$$C = \frac{\pi \Sigma}{\ln \frac{d}{a}} \text{ f/m} \leftarrow \text{for open line,}$$

$$\text{for closed line, } C = \frac{2\pi \Sigma}{\ln \frac{d}{a}}$$

Line Constant for zero dissipation line

$$\text{for general, } Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

But for high frequency,

$$j\omega L \gg R, \quad \& \quad j\omega C \gg G$$

$$Z_0 \approx \sqrt{\frac{j\omega L}{j\omega C}} \Rightarrow \boxed{Z_0 = \sqrt{\frac{L}{C}}}$$

Propagation Constant $\gamma = \sqrt{ZY}$

$$= \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{j^2 \omega^2 LC}$$

$$\boxed{\gamma = j\omega \sqrt{LC}}$$

$$\therefore \gamma = \alpha + j\beta$$

$$= 0 + j\omega \sqrt{LC}$$

$$\Rightarrow \boxed{\begin{matrix} \alpha = 0 \\ \beta = \omega \sqrt{LC} \end{matrix}}$$

$j \leftarrow$ for high freq.

11/11/21

Velocity of wave propagation

$$V_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow \boxed{V_p = \frac{1}{\sqrt{LC}}}$$

Voltage & Current on dissipation less line
(Zero dissipation line) :-

$$E = E_R \cosh \gamma(l-x) + I_R Z_0 \sinh \gamma(l-x)$$

$$\text{Put } l-x = S$$

$$\Rightarrow E = E_R \cosh \gamma S + I_R Z_0 \sinh \gamma S$$

$$\text{at high freq, } Z_0 = R_0, \gamma = j\beta$$

$$E = E_R \cosh j\beta S + I_R R_0 \sinh j\beta S$$

$$\boxed{E = E_R \cos \beta S + I_R j \sin \beta S \cdot R_0}$$

$$\text{By, } \boxed{I = I_R \cos(\beta S) + j \frac{E_R}{R_0} \sin(\beta S) \cdot R_0}$$

$$\therefore \beta = \frac{2\pi}{\lambda}$$

$$\therefore E = E_R \cos\left(\frac{2\pi S}{\lambda}\right) + I_R j \sin\left(\frac{2\pi S}{\lambda}\right) R_0$$

$$\bar{I} = I_R \cos\left(\frac{2\pi t}{\lambda}\right) + j \frac{E_R}{R_0} \sin\left(\frac{2\pi t}{\lambda}\right) R_0$$

Assumptions :-

(i) open loop ckt. $\Rightarrow I_R = 0$.

$$E_{oc} = E_R \cos\left(\frac{2\pi t}{\lambda}\right)$$

(ii) line is short circuit, $\Rightarrow E_R = 0$

$$\Rightarrow E_{sc} = j I_R R_0 \sin\left(\frac{2\pi t}{\lambda}\right)$$