

Behaviour of The characteristic Impedance.

For Symmetric T network, the characteristic impedance is

$$Z_{0T} = \sqrt{z_1 z_2 \left(1 + \frac{z_1}{4z_2}\right)}$$

If the impedance z_1 and z_2 are purely reactive

$$z_1 = jx_1 \text{ and } z_2 = jx_2$$

$$\therefore Z_{0T} = \sqrt{-x_1 x_2 \left(1 + \frac{x_1}{4x_2}\right)}$$

If x_1 and x_2 are the same type of reactance, a stop band exists. The ratio $\frac{x_1}{4x_2}$ will be real and positive and the characteristic impedance will be pure reactance in attenuation region.

If x_1 and x_2 are the opposite type of reactance and $-1 < \frac{x_1}{4x_2} < 0$, a pass band exists. The characteristic impedance will be real and positive in pass band region.

If x_1 and x_2 are the opposite type of reactance and $\frac{x_1}{4x_2} < -1$, a stop band exists.

The characteristic impedance will be pure reactance in stop region.

CONSTANT K-FILTER:

If Z_1 is series impedance and Z_2 is the shunt impedance of T or π network, then

$$Z_1 Z_2 = K^2$$

where, K is a constant independent of frequency

This network is called as constant K-filter


If $Z_1 = j\omega L$ and $Z_2 = -j/\omega C$ then

$$Z_1 Z_2 = (j\omega L) \left(\frac{-1}{\omega C} \right) = \frac{L}{C}$$


$$= \frac{L}{C} = \underline{R^2 K} = K$$

Constant K low pass filter:

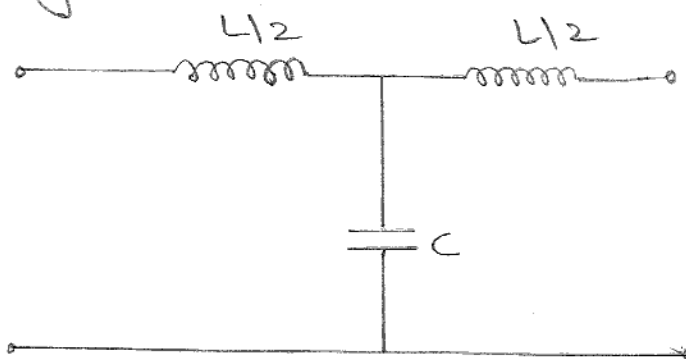The constant K low pass filter in T and π type is shown.



(a) T-network

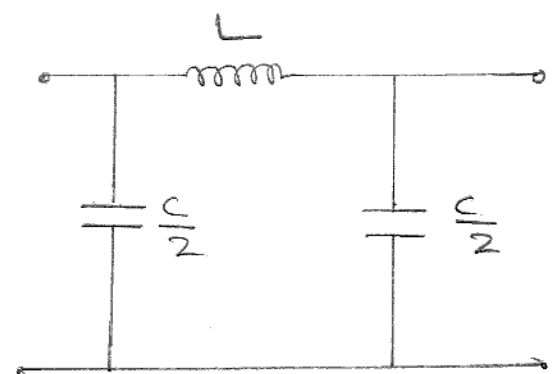

(b) π -network

Constant K low pass filter.

Pass band starts at the frequency at which $Z_1 = 0$ and continues to the frequency (f_c) at which $Z_1 = -4Z_2$. This frequency f_c is called cut-off

frequency.

At cut-off frequency

$$Z_1 = -4Z_2$$

$$j\omega_c L = \frac{4j}{\omega_c C}$$

$$\omega_c^2 = \frac{4}{LC}$$

$$\omega_c = \frac{2}{\sqrt{LC}}$$

$$f_c = \frac{1}{\pi\sqrt{LC}}$$

All frequency above cut-off frequencies lie in a stop band. This network is known as low pass filter

The characteristic impedance of T-network.

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$

$$Z_1 = j\omega L \text{ and } Z_2 = \frac{-j}{\omega C}$$

$$Z_{OT} = \sqrt{j\omega L \left(\frac{-j}{\omega C}\right) \left(1 + \frac{j\omega L}{4\left(\frac{-j}{\omega C}\right)}\right)}$$

$$= \sqrt{\frac{L}{C} \left(1 - \frac{\omega^2 LC}{4}\right)}$$

$$= \sqrt{\frac{L}{C} \left(1 - \frac{\omega^2}{\omega_c^2}\right)}$$

$$\left\{ \because \omega_c^2 = \frac{LC}{4} \right\}$$

$$\sqrt{\frac{L}{C} \left[1 - \left(\frac{f}{f_c} \right)^2 \right]}$$

$$= \sqrt{\frac{L}{C}} \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$

$$= R_k \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$

$$\left\{ \because R_k = \sqrt{\frac{L}{C}} \right\}$$

If $f < f_c$, Z_{OT} becomes real indicating the pass band. If $f > f_c$, Z_{OT} becomes imaginary indicating the stop band

At $f = f_c$, $Z_{OT} = R_k$

Design: At cut-off

$$Z_1 = -4Z_2$$

$$L\omega_c = \frac{4}{C\omega_c}$$

$$\omega_c^2 = \frac{4}{LC}$$

$$f_c^2 = \frac{1}{\pi^2 LC}$$

$$\text{But } Z_1 Z_2 = R_k^2$$

$$L\omega \left(\frac{1}{C\omega} \right) = R_k^2$$

$$\frac{L}{C} = R_k^2$$

$$L = R_k^2 C$$

Substituting the value of L in f_c^2 equation

$$f_c^2 = \frac{1}{\pi^2 R_k^2 C^2}$$

$$C^2 = \frac{1}{\pi^2 f_c^2 R_k^2}$$


$$\therefore C = \frac{1}{\pi f_c R_k}$$

$$\therefore L = \frac{R_k}{\pi f_c}$$


$$\left\{ \because L = R_k^2 C \right\}$$

Constant K - High Pass filter

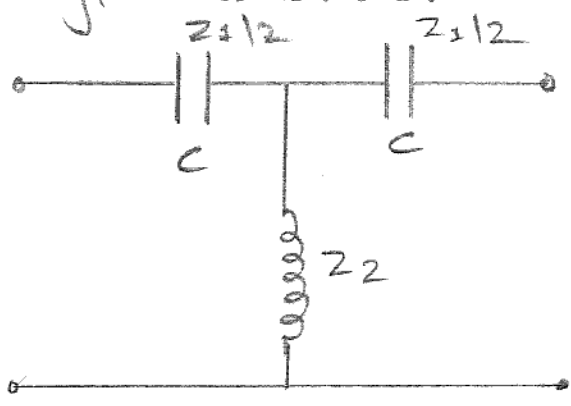The constant K high pass filter in T and π type is shown



T-filter

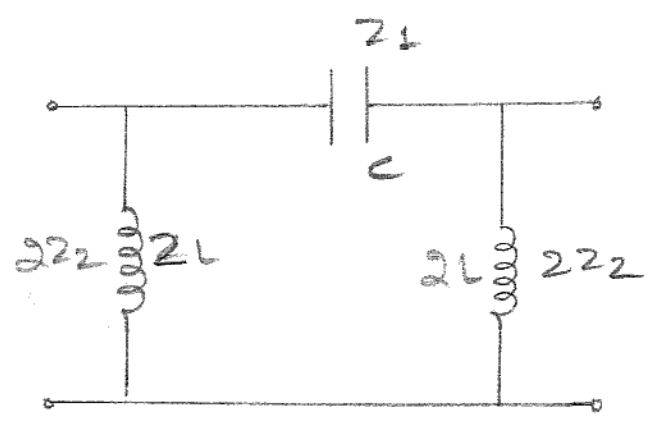

π -filter

Constant K high pass filter.

If $Z_1 = \frac{-j}{\omega_c C}$ and $Z_2 = j\omega_c L$; then

$$Z_1 Z_2 = \left(\frac{-j}{\omega_c C} \right) (j\omega_c L) = \frac{L}{C} = K = R_k^2$$

Pass band starts at cut-off frequency (f_c) at which $Z_1 = -4Z_2$ to infinity at which $Z_1 = 0$

$$Z_1 = -4Z_2$$

$$\frac{-j}{\omega_c C} = -j4L\omega_c$$

$$4LC\omega_c^2 = 1$$


$$\omega_c^2 = \frac{1}{4LC}$$

$$\omega_c = \frac{1}{2\sqrt{LC}}$$


$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

All the frequency below cut-off frequency (f_c) lie in stop band. This network is said to be high pass filter.

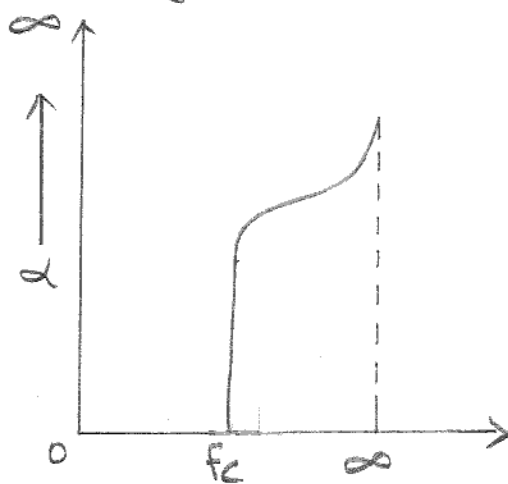The frequency response of constant K low pass and high pass filter are shown in fig.



Low pass filter

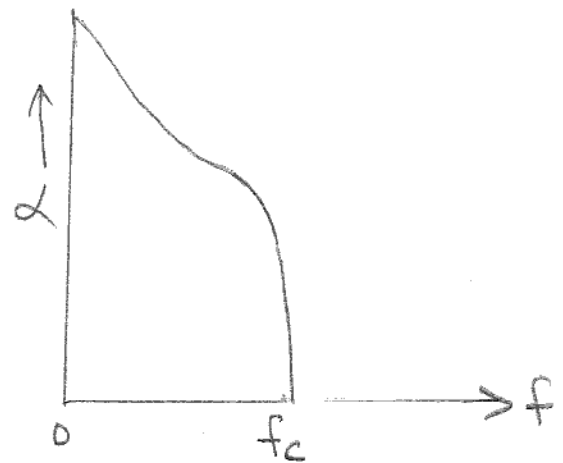

High pass filter.

4
Frequency response of constant K low pass and high pass filter.

The characteristic impedance of T network

$$Z_{OT} = \sqrt{z_1 z_2 \left(1 + \frac{z_1}{z_2}\right)}$$

$$= \sqrt{\left(\frac{-j}{c\omega}\right)(jL\omega) \left(1 + \frac{-j/c\omega}{4jL\omega}\right)}$$

$$= \sqrt{\frac{L}{c} \left(1 - \frac{1}{4Lc\omega}\right)}$$

$$= \sqrt{\frac{L}{c} \left(1 - \frac{\omega c^2}{\omega^2}\right)}$$

$$= \sqrt{\frac{L}{c} \left(1 - \frac{f_c^2}{f^2}\right)}$$

$$\left\{ \because \omega^2 = \frac{1}{4Lc} \right.$$

$$= \sqrt{\frac{L}{c}} \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$

$$= R_K \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$

If $f < f_c$, Z_{OT} becomes imaginary stop band
If $f > f_c$, Z_{OT} become real indicating pass band
At $f = f_c$, $Z_{OT} = R_K$

Design: At cut-off

$$z_1 = -4z_2$$

$$\frac{-j}{\omega c} = -j4L\omega c$$

$$\omega c^2 = \frac{1}{4LC}$$

$$f_c^2 = \frac{1}{16\pi^2 LC}$$

But $z_1 z_2 = Rk^2$

$$\left(\frac{-j}{\omega c}\right)(j\omega L) = Rk^2$$

$$\frac{L}{c} = Rk^2$$

$$L = Rk^2 c$$

Substituting the value of L in f_c^2 equation

$$f_c^2 = \frac{1}{16\pi^2 Rk^2 c^2}$$

$$f_c = \frac{1}{4\pi Rk c}$$

$$\therefore c = \frac{1}{4\pi f_c Rk}$$

$$\therefore L = \frac{Rk}{4\pi f_c}$$

$$\left\{ \because L = Rk^2 c \right\}$$