

Transmission Line And Wave Guides

27)

Unit 1. Filters

PART-A

Q1. Neper :- It is defined as

$$N \text{ nepers} = \ln \left(\frac{V_1}{V_2} \right) = \ln \left(\frac{I_1}{I_2} \right)$$

Also,

It is defined as the natural logarithm of input voltage or current to the output voltage or current.

Bel :- The bel is defined as the logarithm of a power ratio,

$$\text{no. of bels} = \log \frac{P_1}{P_2}$$

Q2. Decibel :- It is the 10 times of common logarithm of ratio of input power to output power.

i.e.

$$D = 10 \log \left(\frac{P_1}{P_2} \right)$$

where,

P_1 = i/p power

$$D = 8.686 N$$

Q3. Filter :- It is the electronics device which is designed to separate and pass or suppress a group of signal through a mixer of signals. And it also passes freely a desired band of frequency. While almost suppressed other band of frequency.

Q11.

Q4. Types of filters :-

Q12.

a) Active Filters - They contain transistor, inductors and op-amp.

b) Passive Filters - They contain resistor, capacitor.

Q5. When $Z_1 = Z_2$ or the two series arms of a T network are equal, or $Z_a = Z_b$ and the shunt arms of a π network are equal the network works are said to be symmetrical.

Q6. 1 Neper = 8.686 db.
or,

Q13.

$$N = 0.115 \text{ dB}$$

which
and pass
ugh a
res
. While
frequency.

Q11. The characteristic impedance of symmetrical network is the impedance measured at the input terminal of the 1st channel in the chain of infinite network in cascade and it is represented by Z_0 .

Q12. Propagation constant is defined as the natural logarithm of the ratio of sending end current or voltage to receiving end current or voltage.

$$\gamma = \ln \frac{I_s}{I_R} \quad \text{or} \quad \gamma = \ln \frac{V_s}{V_R}$$

$$\text{or, } \gamma = \alpha + j\beta$$

It is also known as

$$\gamma = \sqrt{ZY}$$

$$= \sqrt{(R + j\omega L)(G + j\omega C)}$$

Q13. If Z_1 and Z_2 of a reactance n/w are unlike reactance arms, then

$$Z_1 Z_2 = k^2$$

where k is a constant independent of frequency. N/w or filter sections for which this relation hold are called constant- k filters.



Q14. Types of constant K filter

Q18.

- The const K low pass filter
 - The const K high pass filter
- } T, π

Q15. The low pass filter passes all frequencies upto the cut off frequency. Also attenuates all frequencies above the cut off frequency.

Q19.

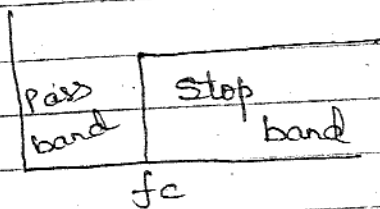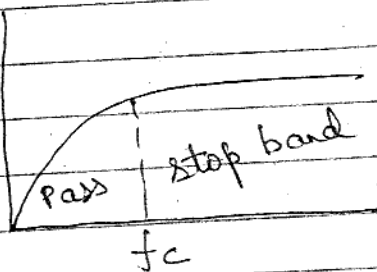

Q21.

Q17. Disadvantage of const K filters -

- The attenuation does not rise very rapidly at cutoff, so that frequencies just outside the pass band are not appreciably attenuated with respect to frequencies just inside the pass band.
- The characteristic impedance varies widely over the pass band, so that a satisfactory impedance match is not possible.

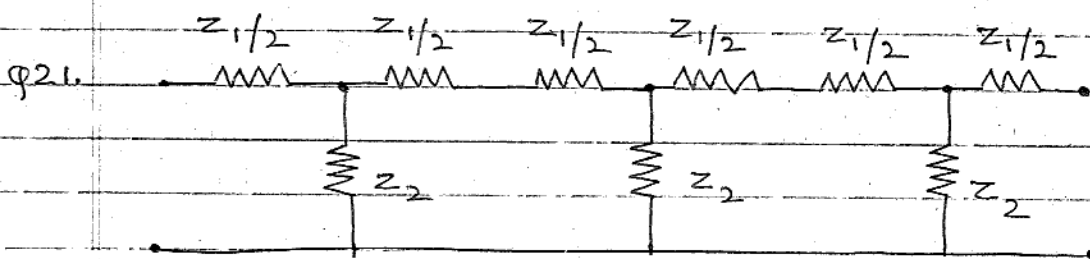
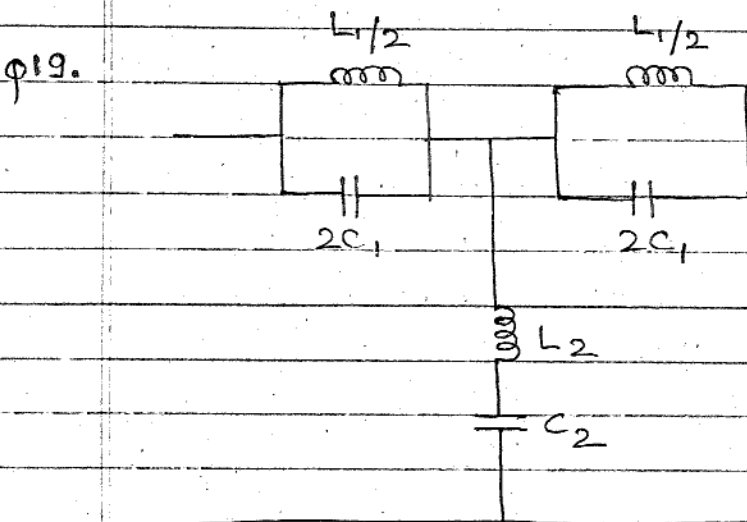
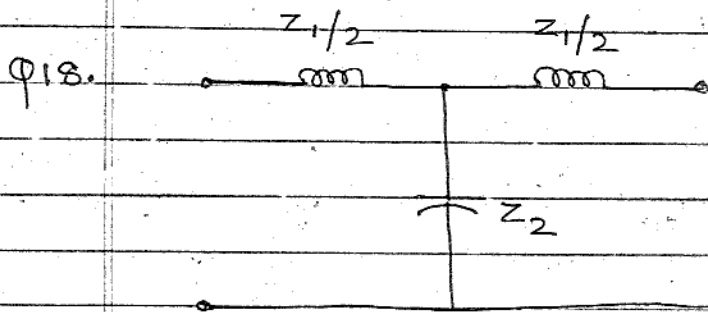


Fig - Ladder n/w formed by symmetrical T-n/w

pidly
outside

s just

widly
factory

q23. It is a combination of constant k filters, m derived filters and m derived half sections.

q25.


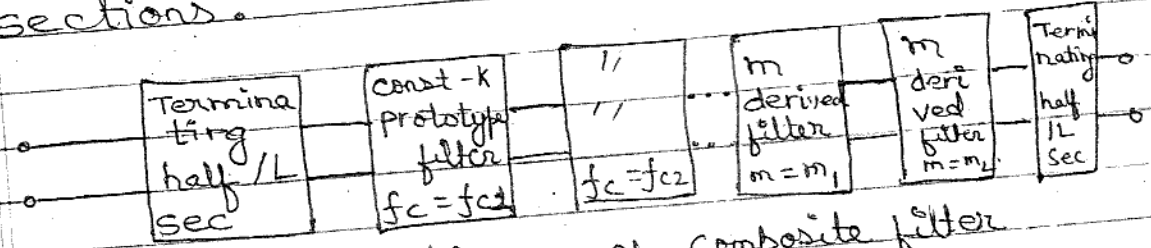
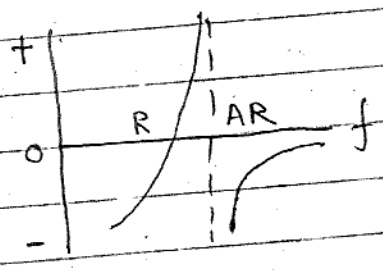


Fig - Block diagram of composite filter

In this, const k filters provides high attenuation away from cut-off freq, in stop band, m derived filters provides high attenuation close to f_0 and m derived half sections with $m=0.6$ provide uniform characteristic impedance in pass band.

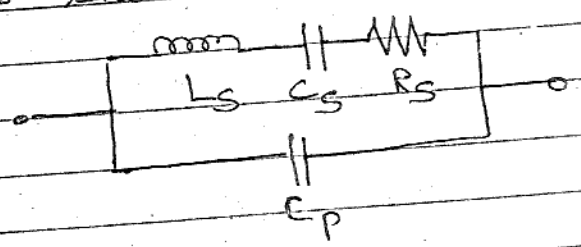q20. Crystal filter is made up of piezo electric crystal with very high Q . It acts as a very narrow band filter. The equivalent ckt and reactance curve of crystal filter is shown below -



a) Equi ckt



b) Reactance curve

q10. When pass band starts at freq at which $Z_1 = 0$ and continues to freq (f_c) at which $Z_1 = 4Z_2$. This freq is called cut-off freq.


$$f_c = \frac{1}{\pi \sqrt{LC}}$$

filters,

Q25.

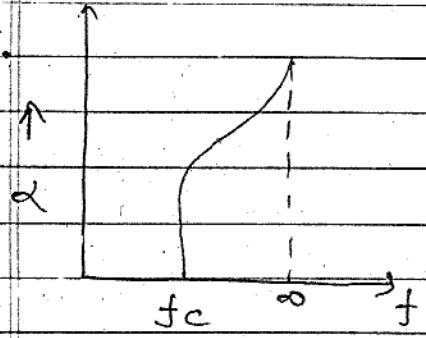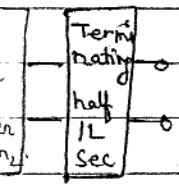

Low pass filter

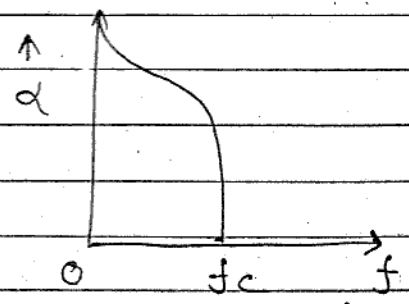

High pass filter

Equation

close
with m =
dance

tric
a
t
filter

= f

wave

h z = 0
= 4z.

Unit-2

Part-A

Q1. The transfer of energy from one point to another through either transmission line or wave guide.

The electrical lines which transmit the electrical wave one place to another.

Q2. Types of Transmission line -

- Open wire line
- Cables
- Co-axial cable
- Wave guides.

Q3. Parameter of transmission line -

- Resistance (R)
- Inductance (L)
- Capacitance (C)
- Conductance (G) = $1/R$

Q4. Written in 1st unit.

Q9. The line in which there is no phase and frequency distortion is called distortion-less line.

It is also represented by β .

$$\beta = \frac{(W^2 LC - RG) + \sqrt{(RG - W^2 LC)^2 + W^2(LG + RC)^2}}{2} \quad \text{Q11.}$$

Condition for distortionless line is

$$LG = RC$$

$$\text{i.e. } \boxed{\frac{G}{C} = \frac{R}{L}}$$

Q12.

Q10. In using ordinary telephone cable the wires are insulated with paper and twisted in pairs. This construction results in negligible values of inductance and conductance so that reasonable assumptions in the audio range of frequencies are that

$$Z = R$$

$$Y = j\omega C$$

Q7.

velocity of propagation

$$v = \frac{W}{\beta} = \sqrt{\frac{2W}{CR}}$$

It should be observed that both α and the velocity are functions of freq., such that higher frequencies are attenuated more and travel faster than lower frequencies.

Q18.

$G+RC)^2$

Q11. It is necessary to increase L/C ratio to achieve distortionless condition in a transmission line. This can be done by increasing the inductance of transmission line. Increasing inductance by inserting inductances in series with line is termed as loading and such lines are loaded lines.

Q12. It is defined as the ratio of reflected voltage to the incident voltage at the receiving end. Denoted by K .

wires
in pairs.

$$K = \frac{\text{Reflected voltage}}{\text{Incident voltage}} = \frac{V_R}{V_0}$$

values

reason-

of

$$K = \frac{Z_R - Z_0}{Z_R + Z_0}$$

Q17. Line distortion types

- Frequency distortion
- Delay distortion

and
such
dimore
ries.

Q18. Wave length :- The distance the wave travels along the line while the phase angle is changing through 2π radians is called wave length.

$$\lambda = \frac{2\pi}{\beta}$$

Q 19. Velocity of propagation is defined as

$$V = \frac{\omega}{\beta}$$

Q 8. Frequency distortion is reduced by the use of equalisers.

Q 20. If the received waveform on a transmission line is not identical with the ip waveform at sending end is called waveform distortion, this occurs in transmission line due to the fact that all frequencies applied on the transmission line are not equally attenuated and are not delayed equally.

Unit-3
PART-A

Q1. → At very high frequencies the skin effect is considerable. Hence it is assumed that the current may flow at the surface of the conductor when the internal inductance becomes zero.

→ Due to the skin the resistance R increases with the frequency. Hence $\omega L \gg R$.

Q2. Nodes - The points along the line where magnitude of voltage and current is zero is known as nodes.

Antinodes - The point where the magnitude of voltage and current is maximum is known as antinodes.

Q3. When the transmission line is not terminated by Z_0 i.e. the load impedance is not equal to characteristic impedance
 $Z_0 \neq Z_R$

The combination of incident and reflected waves give rise to the standing wave.

Q5. It is the ratio of maximum to mini the mag. of voltage or current.

Q9. 11

$$SWR = \frac{V_{max}}{V_{min}} \quad \text{or} \quad \frac{I_{max}}{I_{min}}$$

$$Q6. \quad Z_S = R_0 \left[\frac{1 + |K| \angle \phi - \beta s}{1 + |K| \angle \phi - \beta s} \right]$$

$$Z_{S(max)} = R_0 \left[\frac{1 + |K|}{1 - |K|} \right] = S R_0$$

Q10. →

$$Z_{S(min)} = R_0 \left(\frac{1 - |K|}{1 + |K|} \right) = \frac{R_0}{S}$$

→

Q11.

Q7. Application of quarter-wave matching section is to couple a transmission line to a resistive load such as an antenna.

- It is also used if the load is not pure resistance.
- It is used as an insulator to support an open-wire line or the center conductor of co-axial line.

→

Q9. The stub length L' will be

$$L' = \frac{\lambda}{2} - L$$

or,

$$L = \frac{\lambda}{2\pi} \tan^{-1} \frac{\sqrt{S}}{S-1} \quad \checkmark$$

Q10. → Determination of SWR, sending end imp and load impedance.


→ The solution of stub matching problem may be easily carried out using Smith chart.

Q11. It is a polar chart. It is used to determine SWR and sending end imp and load admittance. It is also used to measure impedance and admittance.

It contains

two circles

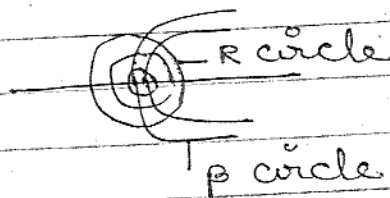→ Const R circle and → Const X circle or
β circle



Q14.) Double stub matching does not require that the stub should be placed at definite point on the line like single stub matching.

Q17.

ii) Double stub matching requires only the length of stub being changed while the position of the stub over the transmission line can be arbitrary.

Q24.) It is used as one to one transformer.

- In connecting a load to a source in cases when the load and source cannot be made adjacent.

Q15. Given, $Z_0 = 50 \Omega$
 $Z_R = 90 + j60$

Reflection coeff, $K = \frac{Z_R - Z_0}{Z_R + Z_0}$

Q21.

$$K = \frac{90 + j60 - 50}{90 + j60 + 50} = \frac{40 + j60}{140 + j60}$$

$$K = \frac{72.11 / 56.30}{152.31 / 23.19} = 0.473 / 33.11$$

$$K = 0.473 \angle 33.11$$

$$\therefore \text{VSWR} = \frac{1 + |K|}{1 - |K|} = \frac{1 + 0.473}{1 - 0.473} = \frac{1.473}{0.527}$$

$$\therefore \text{VSWR} = 2.795$$

quired
at
angle

Q17. Given,

$$Z_0 = 200 \Omega$$

$$Z_R = 692 \angle -12^\circ$$

the
the
transmission

$$\text{or, } Z_R = 676.87 - j143.87$$

$$\therefore K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{676.87 - j143.87 - 200}{676.87 - j143.87 + 200}$$

or.

$$K = \frac{476.87 - j143.87}{876.87 - j143.87}$$

cases
made

$$K = \frac{498.09 \angle -16.78}{888.59 \angle -9.32}$$

$$K = 0.5605 \angle -7.46 \quad \langle \text{Ans} \rangle$$

Q21. Given, $Z_0 = 300 \Omega$
 $Z_R = 300 + j400$

$$\text{Ref coeff } K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{300 + j400 - 300}{300 + j400 + 300}$$

$$K = \frac{j400}{600 + j400} = \frac{400 \angle 90}{721.1 \angle 33.69}$$

$$K = 0.5547 \angle 56.31$$

$$\text{SWR} = \frac{1 + |K|}{1 - |K|} = \frac{1 + 0.55}{1 - 0.55} = \frac{1.55}{0.45}$$

$$= \frac{1.473}{0.527}$$

$$\text{SWR} = 3.4$$

Q19. Given,

$$L = 9 \mu\text{H/m}$$

$$C = 16 \text{ pf/m}$$

$$Z_0 = 1000 \Omega = R$$

$$\text{So, } Z = R + j\omega L = 1000 + j$$

Q25. The dissipation line for which attenuation constant is zero i.e. $\alpha = 0$ is called the zero dissipation line.

$$\text{if } \gamma = \alpha + j\beta$$

$$\alpha = 0$$

$$\text{i.e. } \gamma = j\beta$$

Q23. i) In Smith chart the impedance is represented in circular line.

ii) Smith chart is based on two sets of orthogonal circles.

iii) It is the modified form of circle diagram for dissipationless transmission line.

iv) Its radius is unity.

v) The transformation utilized for formulating it is called bilinear transformation.

Q13. i) Because it radiates more power as compared to short ckted stub.

ii) its effective length cannot be varied.

~~Q.1~~


~~Part - A~~

Linear Integrated Circuit

Unit - 2

Part - B

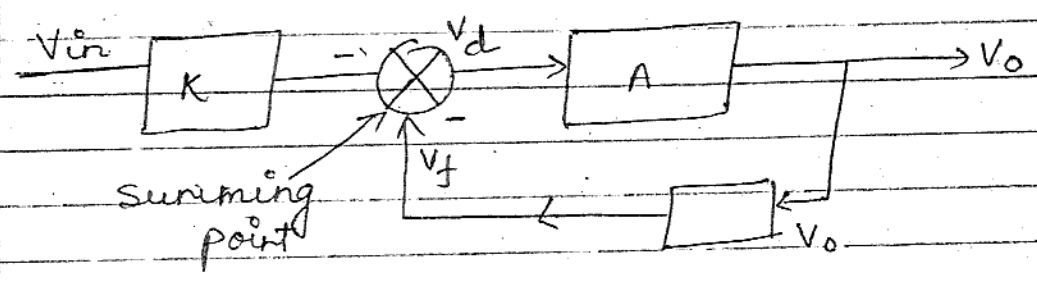Q3. Closed loop block diagram of inverting amplifier



Let us obtain the closed loop transfer function V_o/V_{in} of the block diagram.

At the summing pt, we can write

$$-V_{in} K - V_f = V_d \quad \text{--- (1)}$$

$$V_d A = V_o \quad \text{--- (2)}$$

$$V_o \beta = V_f \quad \text{--- (3)}$$

where, $A =$ open loop gain
 $\beta =$ fb ckt gain
 $K =$ fb c attenuation factor

sub ① and ③ in ②

$$(-V_{in} K - V_f) A = V_o$$

i.e. $-V_{in} K A - V_o \beta A = V_o$

$$\therefore -V_{in} K A = V_o (1 + \beta A)$$

amplifier

$$\frac{V_o}{V_{in}} = -\frac{AK}{1 + \beta A} \quad \text{--- (4)}$$

$\rightarrow V_o$

Now let us consider the expression of obtained earlier and rearranging it similar to eq ④

$$A_{CL} = \frac{-A_{OL} R_f}{R_i + R_f + R_i A_{OL}} \quad \text{--- (5)}$$

function

divide numerator and denominator by $(R_i + R_f)$

$$A_{CL} = \frac{-\frac{A_{OL} R_f}{R_i + R_f}}{1 + \frac{R_i A_{OL}}{R_i + R_f}}$$

comparing eq ④ and ⑤ we can write

$A = A_{OL} =$ forward path gain

$$\beta = \frac{R_i}{R_i + R_f} = \text{f/b path gain}$$

tor

$$K = \frac{R_f}{R_i + R_f} = \text{voltage attenuation factor.}$$

$$A_{CL} = - \frac{A_{OL} K}{1 + A_{OL} \beta}$$


Ideally $A_{OL} \beta \gg 1$ hence $1 + A_{OL} \beta \approx A_{OL} \beta$

hence we get

$$A_{CL} = \frac{-K}{\beta}$$

$$= \frac{-R_f (R_1 + R_f)}{R_1 + R_f R_f} = - \frac{R_f}{R_1}$$

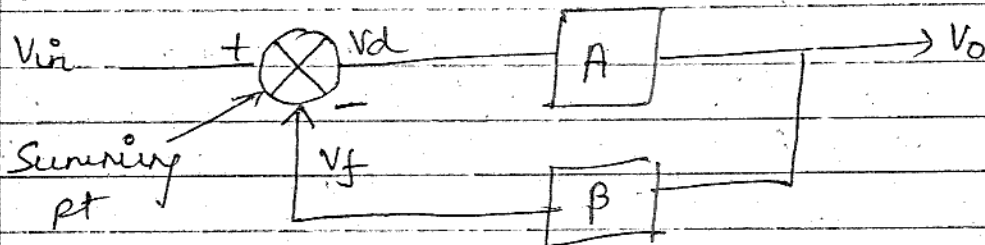Closed loop block diagram of non-inverting amplifier -



Let us obtain the ratio V_o/V_{in} in terms of forward path gain A and flb path gain β .

At the summing pt we can write

$$V_{in} - V_f = V_d \quad \text{--- (1)}$$

$$V_d A = V_o \quad \text{--- (2)}$$

$$V_o \beta = V_f \quad \text{--- (3)}$$

where

$A = \text{open loop gain}$
 $\beta = \text{fb path gain}$

$$\beta \approx A_{OL}\beta$$

subtracting ① and ③ in ② we get
substituting

$$(V_{in} - V_f) A = V_o$$

$$\therefore (V_{in} - V_o \beta) A = V_o$$

$$\frac{R_f}{R_i} V_{in} A - V_o A \beta = V_o$$

$$V_o (1 + A\beta) = A V_{in}$$

Inverting

$$\therefore \frac{V_o}{V_{in}} = \frac{A}{1 + A\beta} \quad \text{--- (4)}$$

V_o
Now consider the expression of A_{CL} obtained and rearranging it similar to eq (4)

$$A_{CL} = \frac{A_{OL} (R_i + R_f)}{R_i + R_f + R_i A_{OL}}$$

terms of
gain β .

dividing numerator and denominator by
($R_i + R_f$)

$$\therefore A_{CL} = \frac{A_{OL} (R_i + R_f)}{R_i + R_f} \cdot \frac{1}{1 + \frac{A_{OL} R_i}{R_i + R_f}}$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL} \left(\frac{R_1}{R_1 + R_f} \right)} \quad \text{--- (5)}$$

Comparing the eq (4) and (5) we get,

$A = A_{OL}$ = forward path gain

$\beta = \frac{R_1}{R_1 + R_f}$ = f/b path gain

$$\therefore A_{CL} = \frac{A_{OL}}{1 + A_{OL} \beta}$$

Ideally $A_{OL} \beta \gg 1$ hence $1 + A_{OL} \beta \approx A_{OL} \beta$

$$A_{CL} = \frac{1}{\beta} = \frac{R_1 + R_f}{R_1} = 1 + \frac{R_f}{R_1}$$

$$A_{CL} = \frac{1}{\beta} \quad (\text{ideal})$$

CONTROL SYSTEM

Unit - 2

LONG

Q2. The input is unit impulse
i.e. $\delta(t) = \delta(t)$

$$\therefore R(s) = L[\delta(t)] = 1$$

Given,

$$G(s) = \frac{C(s)}{R(s)} = \frac{9}{s^2 + 4s + 9}$$

As $R(s) = 1$

$$\therefore C(s) = R(s) \cdot \frac{9}{s^2 + 4s + 9}$$

$$= \frac{9}{s^2 + 4s + 9}$$

$$C(s) = \frac{9}{s^2 + 4s + 4 + 9 - 4}$$

$$= \frac{9}{(s+2)^2 + (\sqrt{5})^2}$$

$$C(s) = \frac{9}{\sqrt{5}} \left[\frac{\sqrt{5}}{(s+2)^2 + (\sqrt{5})^2} \right]$$

Taking inverse Laplace transform function

$$c(t) = \frac{9}{\sqrt{5}} e^{-2t} \sin \sqrt{5} t$$

$$\left\{ \because L^{-1} \left[\frac{\omega}{(s+a)^2 + \omega^2} \right] = e^{-at} \sin \omega t \right\}$$

Unit-05
 ~~~~~

Q1. Freq. response of lag compensator -

Consider the general form of lag compensator,

$$G_c(s) = \frac{(s + 1/T)}{(s + 1/\beta T)} = \frac{(sT + 1)/T}{(s\beta T + 1)/\beta T} = \beta \frac{(1 + sT)}{(1 + s\beta T)}$$

sinusoidal transfer function of lag compensator is obtained by letting  $s = j\omega$  in the above equation

$$\therefore G_c(j\omega) = \frac{\beta (1 + j\omega T)}{(1 + j\omega \beta T)} \quad \text{--- (1)}$$

$$\text{When } \omega = 0, G_c(j\omega) = \beta \quad \text{--- (2)}$$

From eq (2) we can say that the lag compensator provides a dc gain of  $\beta$  (here  $\beta > 1$ ). If the dc gain of the



compensator is not desirable then it can be eliminated by a suitable attenuation.

Let us assume that the gain  $\beta$  is eliminated by a suitable attenuation  $n/\omega$ . Now,  $G_c(j\omega)$  is given by

$$G_c(j\omega) = \frac{1+j\omega T}{1+j\omega \beta T} = \frac{\sqrt{1+(\omega T)^2} \angle \tan^{-1} \omega T}{\sqrt{1+(\omega \beta T)^2} \angle \tan^{-1} \omega \beta T} \quad \text{--- (3)}$$

The sinusoidal transfer function shown in eq (3) has two corner frequencies and they are denoted as  $\omega_{c1}$  and  $\omega_{c2}$ .

$$\text{Here, } \omega_{c1} = \frac{1}{\beta T} \text{ and } \omega_{c2} = \frac{1}{T}$$

since,  $\beta T > T$ ,  $\omega_{c1} < \omega_{c2}$

$$\text{Let, } A = |G_c(j\omega)| \text{ in db} = 20 \log \frac{\sqrt{1+(\omega T)^2}}{\sqrt{1+(\omega \beta T)^2}} \quad \text{--- (4)}$$

At very low frequencies i.e. upto  $\omega_{c1}$ ,  $\omega T \ll 1$  and  $\omega \beta T \ll 1$ .

$$\therefore A \approx 20 \log 1 = 0$$

In the freq range from  $\omega_{c1}$  to  $\omega_{c2}$ ,  $\omega T \ll 1$  and  $\omega \beta T \gg 1$

$$\therefore A \approx 20 \log \frac{1}{\sqrt{(\omega \beta T)^2}} = 20 \log \frac{1}{\omega \beta T}$$

At very high frequencies i.e. after  $\omega_{c2}$ ,  $\omega T \gg 1$   
and  $\omega \beta T \gg 1$ .

$$\therefore A \approx 20 \log \frac{\sqrt{(\omega T)^2}}{\sqrt{(\omega \beta T)^2}} = 20 \log \frac{1}{\beta}$$

The approx. magnitude plot of lag compensator is in fig below. The mag plot of Bode plot of  $G_c(j\omega)$  is a straight line through 0 dB to  $\omega_{c1}$ , then it has a slope of -20 dB/dec upto  $\omega_{c2}$  and after  $\omega_{c2}$  it is a straight line with a const gain of  $20 \log \left(\frac{1}{\beta}\right)$ .

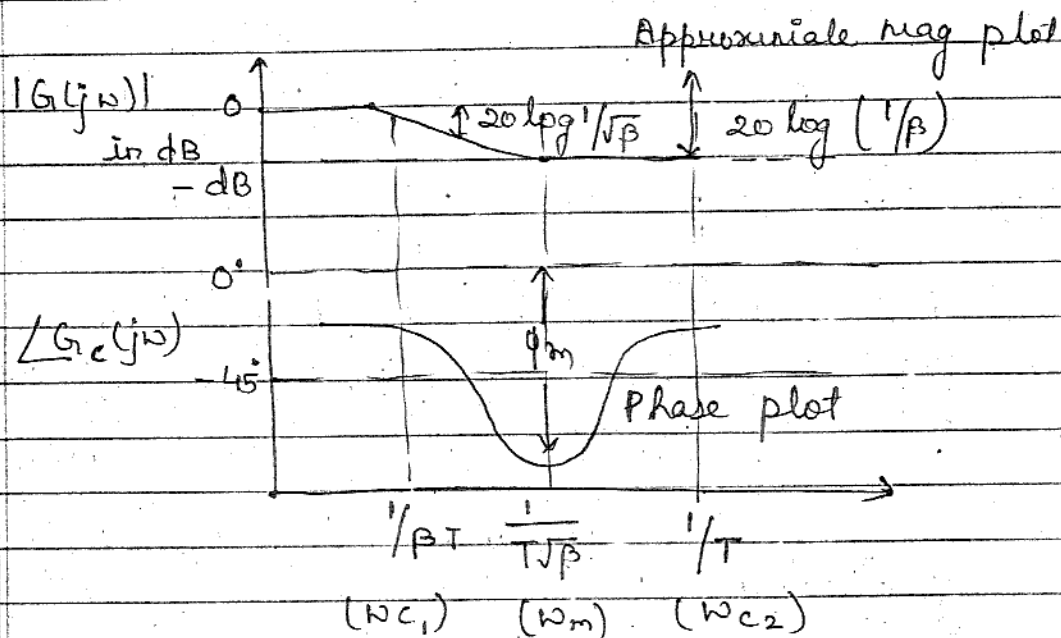


Fig- Bode plot of lag compensator

Let  $\phi = \angle G_c(j\omega)$

$$\therefore \phi = \tan^{-1} \omega T - \tan^{-1} \omega \beta T$$

$\omega T \gg 1$

As  $\omega \rightarrow 0$ ,  $\phi \rightarrow 0$   
As  $\omega \rightarrow \infty$ ,  $\phi \rightarrow 0$

$\frac{1}{\beta}$

As  $\omega$  is varied from 0 to  $\infty$ , the phase angle decreases from 0 to a -ve max value of  $\phi_m$  at  $\omega = \omega_m$ , then increases from this max to 0. The phase plot of lag compensator is shown above. It can be shown that that freq at which max phase lag occurs is the geometric mean of two corner freq.

compensator of bode through of  $\omega_c$  it gain

Freq of max phase lag,  $\omega_m = \sqrt{\omega_{c1} \omega_{c2}}$

mag plot

$$= \sqrt{\frac{1}{\beta T} \cdot \frac{1}{T}} = \frac{1}{T\sqrt{\beta}}$$

( $\beta$ )

From the bode plot of lag compensator, we observe that lag compensator has a dc gain of unity while it offers a high freq gain of  $(\frac{1}{\beta})$ . It means that the high freq noise is  $\beta$  attenuated in passing through the n/w and so the signal to noise ratio is improved. A typical choice of  $\beta = 10$ .

tor

### Q2. Freq Response of lead compensator -

Consider the general form of lead compensator

$$G_c(s) = \frac{s + 1/T}{s + 1/2T} = \frac{(1 + sT)/T}{(1 + s(2T))/2T} = \alpha \frac{(1 + sT)}{(1 + 2sT)}$$

— (1)

The sinusoidal transfer function of lead compensator is obtained by letting  $S = j\omega$  in eq (1).

$$\therefore G_c(j\omega) = \alpha \frac{(1 + j\omega T)}{(1 + j\omega \alpha T)} \quad \text{--- (2)}$$

$$\text{When } \omega = 0, \quad G_c(j\omega) = \alpha \quad \text{--- (3)}$$

From eq (3) we can say that the lead compensator provides an attenuation of  $\alpha$  (Here  $\alpha < 1$ ). If the attenuation of the compensator is not desirable then it can be eliminated by suitable amplifier.

Let us assume that the attenuation  $\alpha$  is eliminated by a suitable amplifier network. Now,  $G_c(j\omega)$  is given by,

$$G_c(j\omega) = \frac{1 + j\omega T}{1 + j\omega \alpha T} = \frac{\sqrt{1 + (\omega T)^2} / \tan^{-1} \omega T}{\sqrt{1 + (\omega \alpha T)^2} / \tan^{-1} \omega \alpha T} \quad \text{--- (4)}$$

sinusoidal transfer function shown in (4) has two corner freq  $\omega_{c1}$  and  $\omega_{c2}$ .

$$\text{Here, } \omega_{c1} = \frac{1}{T} \quad \text{and} \quad \omega_{c2} = \frac{1}{\alpha T}$$

$$\therefore T > \alpha T, \quad \omega_{c1} < \omega_{c2}$$

$$\text{Let } A = |G_c(j\omega)| \text{ in db} = 20 \log \frac{\sqrt{1 + (\omega T)^2}}{\sqrt{1 + (\omega \alpha T)^2}} \quad \text{--- (5)}$$

lead  
 $S = j\omega$  in

At very low frequencies i.e. upto  $\omega_{c1}$ ,  $\omega T \ll 1$   
 and  $\omega \times T \ll 1$ .

∴  $A = 20 \log 1 = 0$


In the frequency range from  $\omega_{c1}$  to  $\omega_{c2}$ ,  
 $\omega T \gg 1$  and  $\omega \times T \ll 1$ .

∴  $A \approx 20 \log \sqrt{(\omega T)^2} = 20 \log (\omega T)$

At very high frequencies i.e. after  $\omega_{c2}$ ,  $\omega T \gg 1$   
 and  $\omega \times T \gg 1$ .

∴  $A = 20 \log \frac{\sqrt{(\omega T)^2}}{\sqrt{(\omega \times T)^2}} = 20 \log \frac{1}{\alpha}$

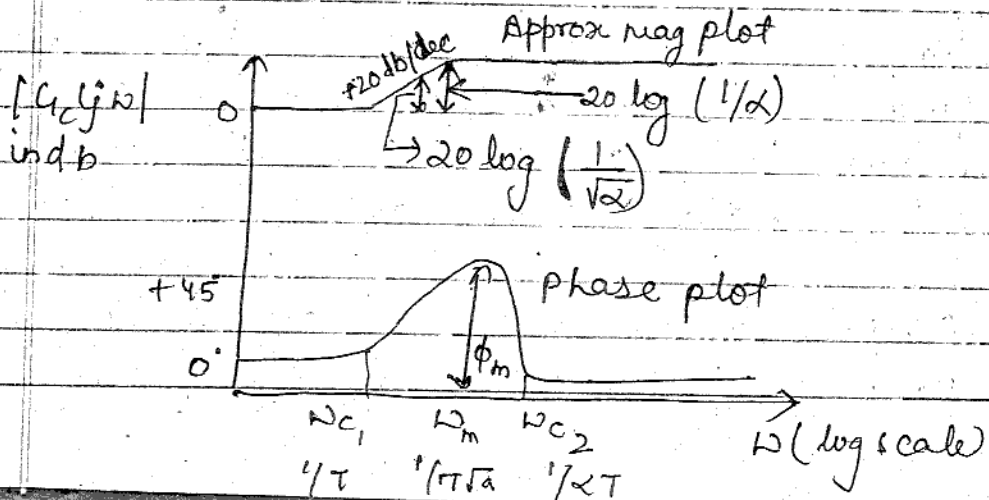The approx. magnitude plot of lead compensator is shown in fig. The magnitude plot of Bode plot of  $G_c(j\omega)$  is a straight line through 0 db upto  $\omega_{c1}$ , then it has a slope of +20 db/decade upto  $\omega_{c2}$  and after  $\omega_{c2}$ , it is a straight line with constant gain of  $20 \log \left(\frac{1}{\alpha}\right)$ .



$$\text{Let } \phi = \angle G_c(j\omega)$$

$$\therefore \phi = \tan^{-1} \omega T - \tan^{-1} \omega \alpha T$$

$$\text{As } \omega \rightarrow 0, \quad \phi \rightarrow 0$$

$$\text{As } \omega \rightarrow \infty, \quad \phi \rightarrow 0$$

As  $\omega$  is varied from 0 to  $\infty$ , the phase angle increases from 0 to a max. value of  $\phi_m$  at  $\omega = \omega_m$ , then decreases from this max value to 0.

It can be shown that the freq. at which max phase lead occurs is the geometric mean of the two corner frequencies

$$\text{Freq. of max phase lead, } \omega_m = \sqrt{\omega_{c1} \cdot \omega_{c2}}$$

$$\omega_m = \sqrt{\frac{1}{T} \cdot \frac{1}{\alpha T}} = \frac{1}{T\sqrt{\alpha}}$$

The choice of  $\alpha$  is governed by the inherent noise in control system. From the Bode plot of the lead  $\alpha$ , we observe that the high freq. noise  $\Delta f$  are amplified by a factor  $\frac{1}{\alpha}$ , while the low freq. control signal  $\Delta$  undergoes unit amplification. Thus the  $\frac{S}{N}$  ratio at the opp. of the lead

compensator is poorer than its i/f. To prevent  $\frac{S}{N}$  ratio at the opp. from

deteriorating excessively, it is recommended that the value of  $\alpha$  should not be less than 0.07. A typical choice of  $\alpha = 0.6$ .

angle  
of  $\phi_m$   
max

freq  
the  
resonances

$\omega_c$

erent  
plot  
the  
y a  
trial  
thus

to

# Electronics Circuits - II

## Unit - 1

### Part - A

Q1. -ve f/b - When part of o/p sig and i/p signal are in out of phase the f/b is called -ve f/b.

+ve f/b - When i/p sig and part of o/p sig are in phase, the f/b is called positive f/b.

Q2. The feedback o/w provides reduced portion of the output as f/b s/p to the i/p mixer o/w. It is given as

$$V_f = \beta V_o$$

In this  $\beta$  is a feedback factor or f/b ratio. It is used in f/b ckt represents f/b factor which always lies b/w 0 and 1.

Q3. The reciprocal of the sensitivity is called desensitivity. Denoted by  $D$ .

It is given as

$$D = 1 + \beta A$$



Sensitivity is given as  $\frac{1}{1 + \beta A}$ .



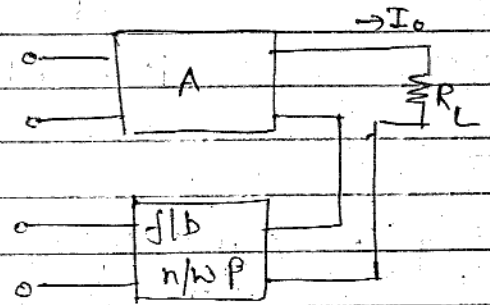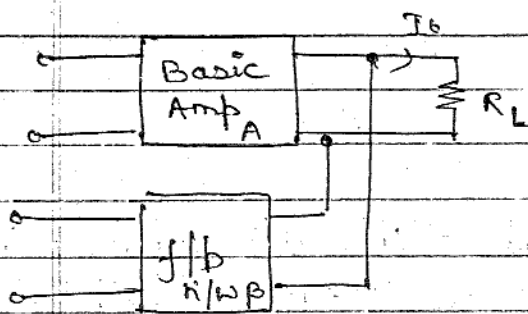Q4. There are two ways to sample the o/p, a/c to the sampling parameter, either voltage or current.

The o/p voltage is sampled by connecting f/b n/w in shunt across the o/p. This type of connection is referred to as voltage, or node sampling.

The o/p current is sampled by connecting the f/b n/w in series with the o/p. This type of connection is referred to as current, or loop, sampling.



a) Voltage or node sampling

b) Current or loop sampling


Q5. Normally high i/p resistance of a voltage amplifier can be made higher but in +ve f/b it doesn't happen.

→ In case of -ve f/b low output resistance of a voltage amplifier can be lowered.

→ The proper use of -ve f/b improves freq response of amplifier.

→ There is a significant improvement in the linearity of operation of ffb amplifier compare with that of the amp without ffb.

φ8.

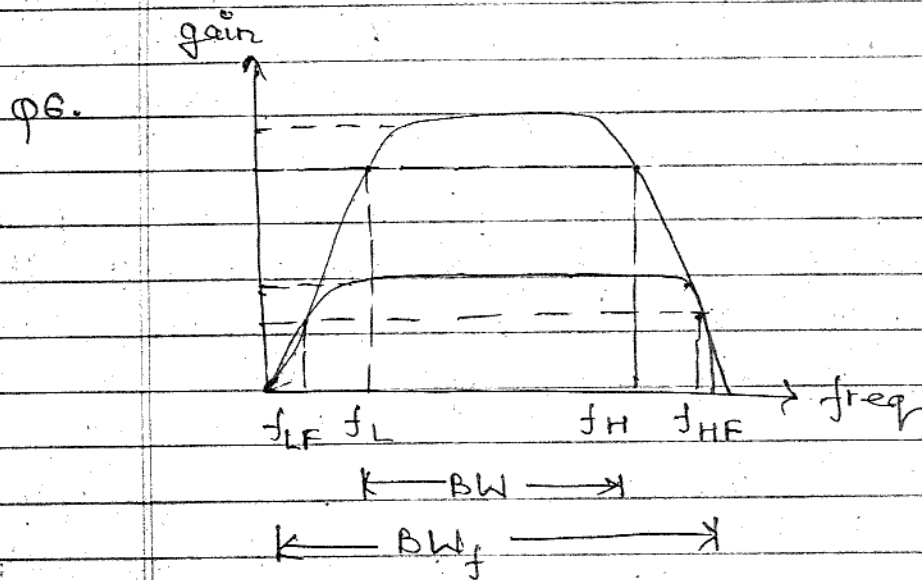

φ11.

φ12.

φ7. Effect of -ve ffb on gain - In this case gain decreases by the factor  $(1 + A\beta)$  by which the band width increases. The gain - BW product of an amplifier does not altered.

Effect on distortion - The frequency distortion reduces and noise distortion also reduces in the amplifier due to the -ve ffb.


φ13.

in the  
compare

Q8. The fractional change in amplification with f/b divided by the fractional change without f/b is called sensitivity of the transfer gain.


$$\text{Sensitivity} = \frac{1}{(1+A\beta)}$$

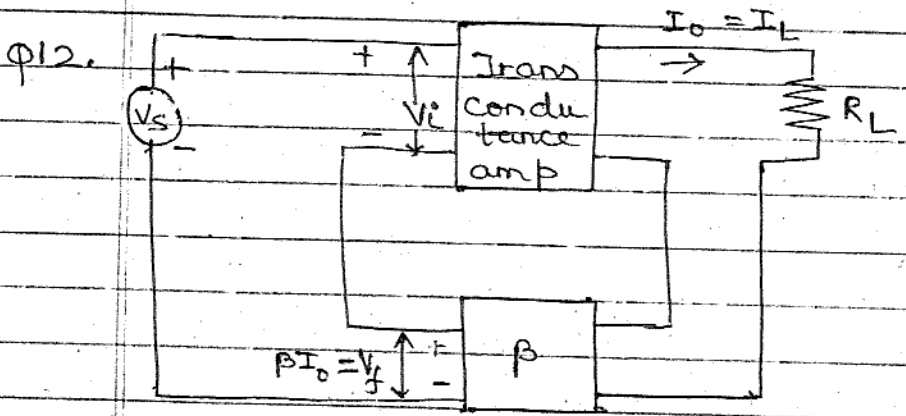- Q11. Voltage amplifier with voltage series f/b
- Transconductance amplifier with current series f/b
  - Current amplifier with current shunt f/b.
  - Transresistance amp with voltage shunt f/b



gain  
which the  
effect of

distortion  
causes in

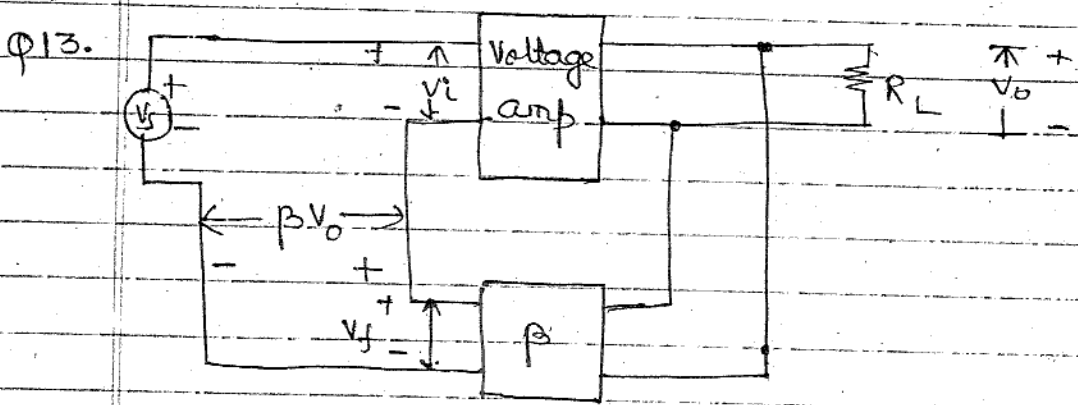

$$Q14 \quad A_{vf} = \frac{A_v}{1 + A_v \beta} = \frac{600}{1 + 600 \times 0.01} = 85.71$$

Q23.

Q15 → In case of voltage series and current series the input impedance increases and output impedances decrease in voltage series and increase in current series.

→ In case of current shunt and voltage shunt the input impedance decreases and output impedance increases in current shunt and decreases in voltage shunt.

Q18 There are three types of feedback connection

- i) Sampling output
- ii) Feedback output
- iii) Mixer output

Q24.

Q17.

Q20. The open loop gain can be defined as the gain without feedback.

$$Q25 \quad A_{vf} = \frac{A_v}{1 + A_v \beta} = \frac{200}{1 + 2 \times 0.05}$$

$$= \frac{200}{1.1} = 181.81$$

Q21

85.71

Q23. Positive f/b amp      Negative f/b amp

- Input signal and part of the output which is fed back to the input are in phase, the f/b is called +ve f/b.
- An oscillator works on this principle.
- When the input signal and part of the output which is fed back to input are not in phase i.e. out of phase, the f/b is called -ve f/b.
- Amplifiers work on this principle.

Q24. In emitter follower circuit the voltage series feedback has been used.

Q17. Gain of closed loop i.e. gain with feedback is given by

$$A_v = \frac{A_v}{1 + A_v \beta}$$

where,

$A_v$  = open loop gain i.e. gain without feedback

$\beta$  = f/b factor

Q21. -ve f/b is employed in high gain amplifier because

- It improves frequency response of amplifier
- Normally high input resistance of a voltage amp can be made higher.

- Normally low  $o/p$  resistance of a voltage amplifier can be lowered.

Q1.  $\phi$   
20  
a

Q2. C  
→ F  
→ F  
→ F  
→ F

Q3.  
and 1)  
Q5.

11)

Q6.

## Unit - 2

### Part - A

Q1.  $Q$  factor of the crystal is very high, typically 20,000. Value of  $Q$  upto  $10^6$  also can be achieved.

Q2. Classification of oscillators - 2-8

→ Based on the output waveform

→ Based on the circuit components

→ Based on the range of operating frequencies

→ Based on whether fb is used or not.

Q3. The Barkhausen Criterion states that :-


and 1) The total phase shift around a loop, as

Q5. the signal proceeds from ip through ampli, fb r/n back to ip again, completing a loop, is precisely  $0^\circ$  or  $360^\circ$ , or of course an integral multiple of  $2\pi$  radians.

ii) The mag. of the product of the open loop gain of the amp ( $A$ ) and the fb factor  $\beta$  is unity i.e.  $|A\beta| = 1$ .

Q6. The piezoelectric effect means under the influence of the mechanical pressure, the voltage gets generated across the opposite faces of the crystal. If the mechanical force is applied in such a way to force the crystal to vibrate, the a.c. voltage gets generated across it. Conversely, if the crystal is subjected to a.c. voltage, it vibrates causing mechanical distortion in the crystal shape.

Q7.

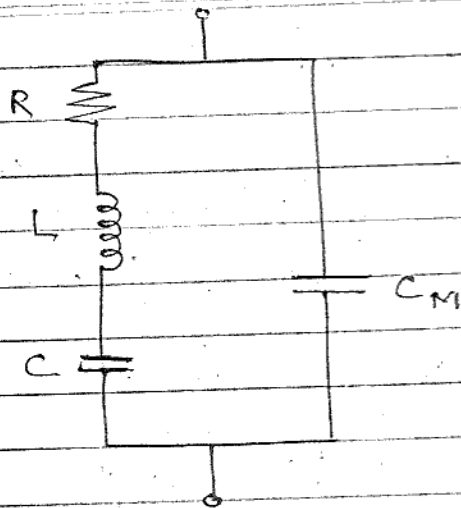

Q10.

Fig. Equivalent ckt of a crystal

Q11.

Q8. It is similar to <sup>the</sup> modification in colpitts oscillator, the Hartley oscillator ckt can be modified to get Miller crystal oscillator. In Hartley osc. ckt, two  $\mu$ res inductors and one capacitor is required in the tank ckt. One inductor ~~in it~~ is replaced by the crystal which acts as an inductor for the frequencies slightly greater than the series resonant frequency.

Q13.

Q9. The freq for RC phase shift oscillator is

$$f = \frac{1}{2\pi RC\sqrt{4K+6}}$$

This is the freq at which  $\angle A\beta = 0^\circ$ .  
At the same freq  $|A\beta| = 1$ .



Q10. An oscillator is a ckt which basically act as a generator, generating the o/p signal which oscillates with constant amplitude and constant desired frequency. It works on the principle of +ve f/b.


Q11. Amplifier

- It is a device which is used to amplify the signal to desired level.
- It works on the principle of -ve f/b.

Oscillator

- It is a device which acts as a generator, generating o/p sfl which oscillates with const amp and desired freq.
- It works on the principle of +ve f/b.

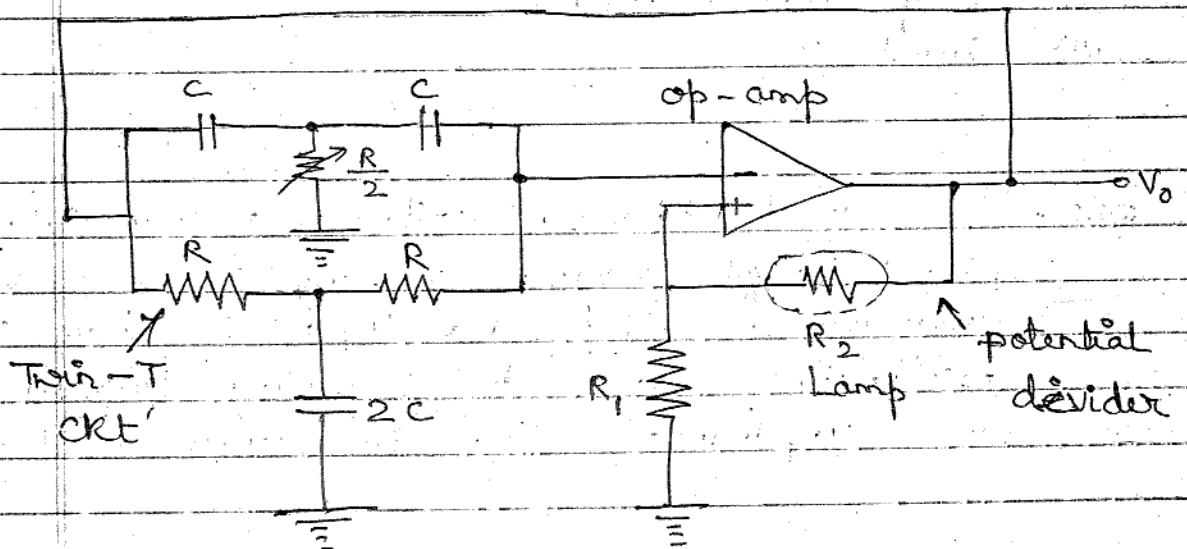Q13. Ckt diagram of Twin-T RC oscillator -



Q14. i) The freq is stable and accurate but in case of colpitt osc. the freq is not stable.

- ii) It is the good frequency stability.
- iii) The stray or capacitances have no effect on  $C_3$  which decides the freq.
- iv) Keeping  $C_3$  variable, freq can be varied in desired range.

Q15. The positive feedback is used in oscillator because whenever the part of the o/p that is fed back to the amplifier as its input, is in phase with the original i/p signal applied to the amplifier.

Q16. The crystal oscillator has a <sup>2-64</sup> higher degree of frequency stability because of

- i) the temp stability
- ii) long term stability
- iii) short " "

Q22. A/c to Barkhausen criterion, when total phase shift around a loop is  $0^\circ$  or  $360^\circ$  ensuring +ve f/b and  $|A\beta| = 1$  then the oscillations are with constant frequency and amplitude called sustained oscillations.

but is  
not

Q19. i) RC oscillators [ Wien Bridge Oscillators ]

ii) Twin-T oscillator

They are LF oscillators

effect

Q20. i) LC oscillators

ii)

They are HF oscillators

ried in

part of the  
amplifier  
the  
the

Q21. When total phase shift around a loop is  $0^\circ$   
or  $360^\circ$  but  $|A\beta| < 1$ . Then the oscillations  
are called damped oscillation i.e. such  
oscillation amplitude decreases exponentially  
and the oscillations finally cease.

or degree

Q24. Freq. of oscillation for Hartley

$$f = \frac{1}{2\pi \sqrt{C L_{eq}}}$$

where,  $L_{eq} = L_1 + L_2$

total

or  $360^\circ$

on the

frequency

oscillations.

Freq. of oscillation for Colpitt

$$f = \frac{1}{2\pi \sqrt{L C_{eq}}}$$

where,

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Q18. RC oscillator

- The oscillators using components resistor and capacitor are called RC oscillator.
- They are used at low freq range of 20 Hz to 100-200 kHz.

LC oscillator

Q23

- The oscillators using the component inductor and capacitor are called LC oscillator.
- They are used at high freq range, more than 200-300 kHz upto GHz.

Q25. Given,

$$L_1 = 0.2 \text{ mH}$$

$$L_2 = 0.3 \text{ mH}$$

$$C = 0.003 \mu\text{F}$$

$$L_{eq} = L_1 + L_2 = 0.2 + 0.3 = 0.6 \text{ mH}$$

$$C = 0.003 \mu\text{f} = 0.003 \times 10^{-10} \text{ F}$$

$$\therefore f = \frac{1}{2\pi \sqrt{L_{eq} C}}$$

$$f = \frac{1}{2\pi \sqrt{0.6 \times 10^{-3} \times 0.003 \times 10^{-10}}}$$

$$= \frac{1}{2\pi \sqrt{0.0006 \times 10^{-13}}}$$

Q23. It is difficult to have a variable frequency operation in an RC phase shift oscillator because if R and C will be changed then the values of R and C of all three sections must be changed simultaneously to satisfy the oscillating conditions. But it is not possible so, the phase shift oscillator is considered as a fixed freq oscillator.

6 mH

Unit - 3

Part - A

Q5.

→

Q1. To amplify the selective range of frequencies, the resistive load,  $R_c$  is replaced by a tuned circuit.

→

The tuned ckt is capable of amplifying a signal over a narrow band of frequencies centered at  $f_0$ . The amplifiers with such a tuned ckt as a load are known as tuned amplifier.

→

Q2. In order to obtain a high overall gain, several identical stages of tuned amplifiers can be used in cascade. The overall gain is the product of the voltage gains of the individual stages. All amplifier stages are assumed to be identical and to be tuned to the same freq.  $\omega_0$ . This is called synchronous tuning and amplifier is called synchronously tuned amplifier.

Q6.

Q7.

i)

ii)

iii)

Q4. Unloaded  $Q$  is the ratio of stored energy to dissipated energy in a reactor or RLC resonator.

The loaded  $Q$ , or  $Q_L$ , of a resonator is determined by how tightly the resonator is coupled to its terminations.

i)

ii)

Q5. There are three types of coil losses

→ Copper loss - total loss of coil is called copper loss.  $\propto \frac{1}{f}$ .

→ Hysteresis loss - It is independent of freq. It is proportional to area enclosed by the hysteresis loop.

→ Eddy current - It is due to the current flowing within the copper or core caused by inductor. It heats the copper or core  $\propto f$ .

Q6. The  $Q$  is the ratio of reactance to resistance. The  $Q$  factor also can be defined as the measure of efficiency with which inductor can store the energy.

Q7. Ad -

- i) They amplify defined frequencies.
- ii) Signal to noise ratio at o/p is good.
- iii) They are well suited for radio transmitters and receivers.

Disad -

- i) If the band of freq. is increased, design becomes complex.
- ii) They are not suitable to amplify audio frequencies.

- Q9. → Single tuned  
 → Double tuned  
 → Stagger tuned  
 → Synchronously tuned


Q11

Q12

Q10. \* The effect of cascading single tuned amplifiers on bandwidth is that it reduces the B.W.

Q11.

Q20.

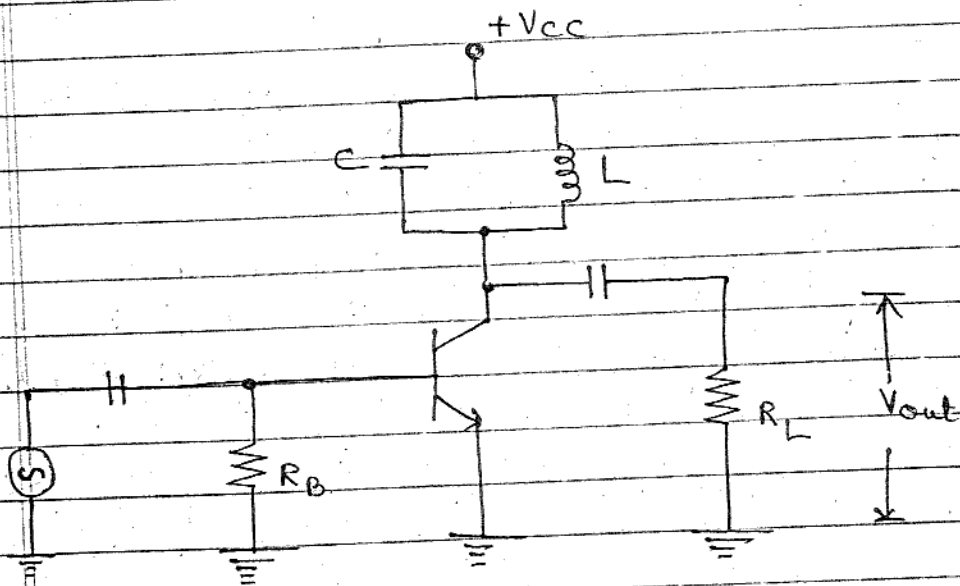


Tuned class-C amp

- Q13. Types of neutralization  
 → Hazeltine neutralization  
 → Neutrodyne "  
 → Neutralization using coil  
 → Rice neutralization



Q14.

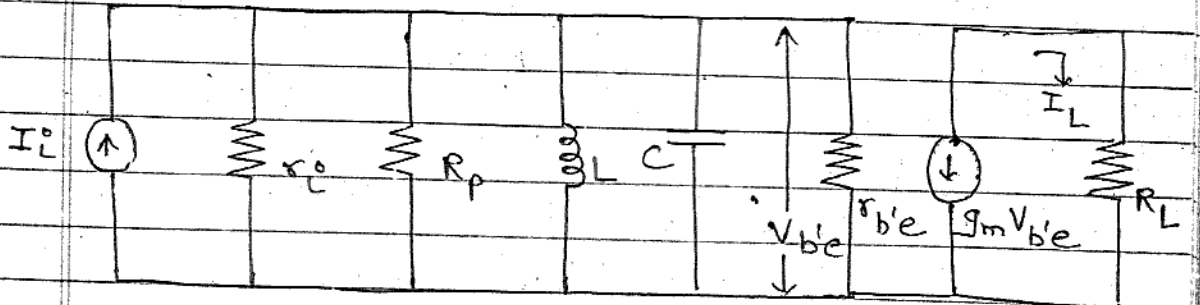

tuned  
reduces

Fig - Equi.ckt of single tuned amp

Q20.

# Transmission Line And Wave guides

## Unit - 02

### Part - B

Q2. Given,

$$R = 10 \Omega / \text{km}$$

$$L = 3.8 \text{ mH} / \text{km}$$

$$G = 1 \times 10^{-6} \text{ S} / \text{km}$$

$$C = 0.0085 \text{ } \mu\text{F} / \text{km}$$

$$f = 1 \text{ KHz}$$

$$\omega = 2\pi f$$

∴ impedance

$$Z = R + j\omega L$$

$$= 10 + j \times 2 \times \pi \times 1000 \times 3.8 \times 10^{-3}$$

$$Z = 10 + j23.86$$

$$Z = 25.87 \angle 67.26^\circ \Omega$$

$$l = 100 \text{ km}$$

$$Z_i = 200 \Omega$$

$$Y = G + j\omega C$$

$$= 10^{-6} + j \times 2 \times \pi \times 1000 \times 0.0085 \times 10^{-6}$$

$$= 10^{-6} + j53.38 \times 10^{-6}$$

$$= 53.38 \times 10^{-6} \angle 88.92^\circ$$

$$\therefore Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{25.87 \angle 67.26^\circ}{53.38 \times 10^{-6} \angle 88.92^\circ}}$$

$$= \sqrt{\frac{25.87}{53.38 \times 10^{-6}} \angle \frac{67.26 - 88.92}{2}}$$

$$Z_0 = 0.696 \times 10^3 \angle -11.33$$

$$= 696.15 \angle -11.33$$

$$Z_S = Z_0 = 682.5 - j137 \Omega$$

$$\gamma = \sqrt{ZY}$$

$$= \sqrt{25.87 \angle 67.26 \times 53.38 \times 10^{-6} \angle 88.92}$$

$$= 0.037 \angle 78.09$$

$$\times 10^{-3} \quad \gamma = 0.0076 + j0.0362 \text{ per km}$$

By formula,

Sending end current

$$I_S = \frac{V_i}{Z_i + Z_S}$$

$$\times 10^{-6} \quad I_S = \frac{1}{200 + 682.5 - j137}$$

$$= \frac{1}{\sqrt{882.5 + (137)^2}} \quad = \frac{1}{\sqrt{\phantom{882.5 + (137)^2}}}$$

$$8.92 \quad = \frac{1}{\sqrt{797575.25}} \quad = \frac{1}{893.07}$$

$$I_S = 1.12 \times 10^{-3} = 1.12 \text{ mA}$$

$$\text{Reflection co-efficient} = \frac{V_R}{V_S}$$

$$V_S = |I_S Z_S|$$

$$= 1.12 \times 10^{-3} \times \sqrt{(682.5)^2 + (137)^2}$$

$$= 1.12 \times 10^{-3} \times 696.1$$

$$= 0.779 \text{ V}$$

$$V_R = V_S e^{-\gamma l} \quad (\because \gamma = \alpha + j\beta)$$

$$= V_S e^{-(\alpha + j\beta)l}$$

$$= V_S e^{-\alpha l} \cdot e^{-j\beta l}$$

$$= 0.779 \times e^{-0.0076 \times 100} \cdot e^{-j0.0362 \times 100}$$

$$= 0.364 e^{-j3.62}$$

$$= 0.364 \angle -3.62 \text{ radian}$$

$$\text{magnitude of } V_R = 0.364 \text{ V}$$

$$\text{and } \beta = -3.62$$

$$\text{co-efficient} = \frac{V_R}{V_S} = \frac{0.364}{0.779}$$

$$= 0.467$$

Ans

Q1.

and

Q2.1.

Q2

and

Q11

Q5

Q

## Unit - 04

### Part - A

Q1. The symmetrical triggering uses only one and trigger up to the up of any one  
Q2.1. transistor.

Q2 In bistable mv, trigger is required to and change the state. The time required to change the state is called transition time. The speed-up capacitors are used to reduce the transition time without affecting the stable states. These capacitor allows fast rise and fall times and avoids the distortion in o/p.

Q5 The bistable mv has two stable states. The mv can exist indefinitely in either of the two stable states. It requires an external trigger pulse to change from one stable state to another. The ckt remains in one stable state unless an external trigger pulse is applied.

Q4. App of Schmitt trigger

- i) Squaring ckt
- ii) Amplitude Comparator
- iii) Reference level detector
- iv) As a flip-flop in digital cks

Q9. The basic difference is that in practical ckt, single supply voltage  $V_{cc}$  is used, instead of three supply voltages.

Q3.1)

I set

$A_{MKR}$